
Lecture 27 1 136/ 1.2/13 EXAMPLE -EE5210 ASSUME IMPEDANCE = X 12. IN ZERO SEQUENCE NETWORK = 3X 1 : ALL ZERO SEQUENCE CURRENTS ARE IN PHASE) Iao = Ibo - Ico PU. CURRENT . 300 x 1000A V3 #13.8 = 4183.7A

 $10 A = \frac{10}{4183.7 A} = 0.0024 pm$ 

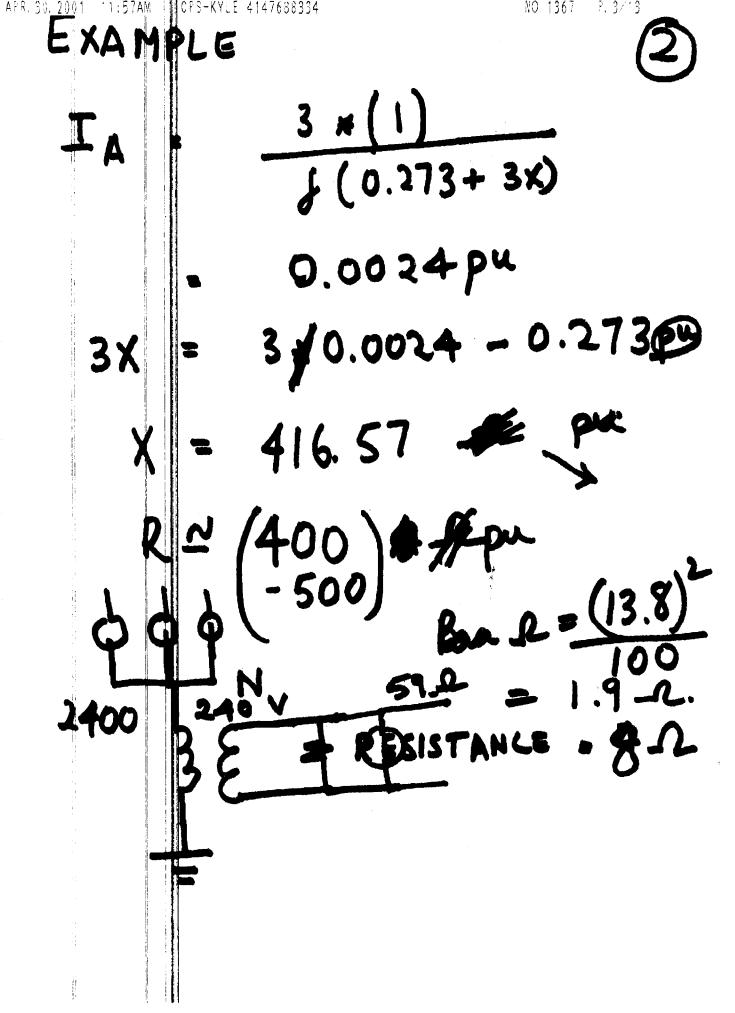

6

n technical requirements for these intersign, construction, and operation of the stomers, general public), and protection ctices, operating procedures, and design ese sources and their interconnections to igh quality of service and of safety for cooperation is very important between

usidered are as follows:

phase or ground faults in the stator and

: rotor and loss of field excitation r hertz protection (24) operational hazards r; generator motoring (32) tion: nonsynchronized connection (67) breaker pole flashover (61)

tion for large steam turbines nd overvoltage (59) : out of step llations


### ONS AND

grounded, or are delta-connected. They ower system or to the power system (eral) each through a circuit breaker to ors are as follows: 8.2: Usually they are wye-grounded

separate transfer trip channel from the IPF generators under- and overvoltage to restore service. This is important ed to assure that the IPP unit is not Hty, industrial, or IPP generators is are mandatory toward disconnecting

**Generator Protection** 


235

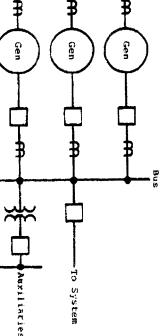


system bus. FIGURE 8.2 Direct-connected generator units (one or more) to a common

the utility loads in the island. where the IPP and industrial generation may be islanded and able to supply

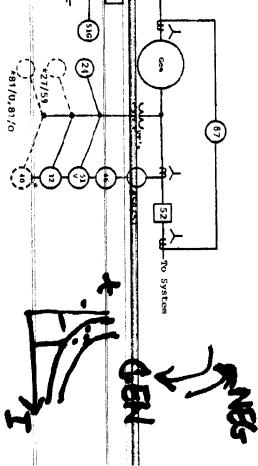in Fig. 8.4. This is the common connection for the large generators in util associated power transformer without a circuit breaker between, as shown 2. Unit connected, in which the generator is connected directly to an



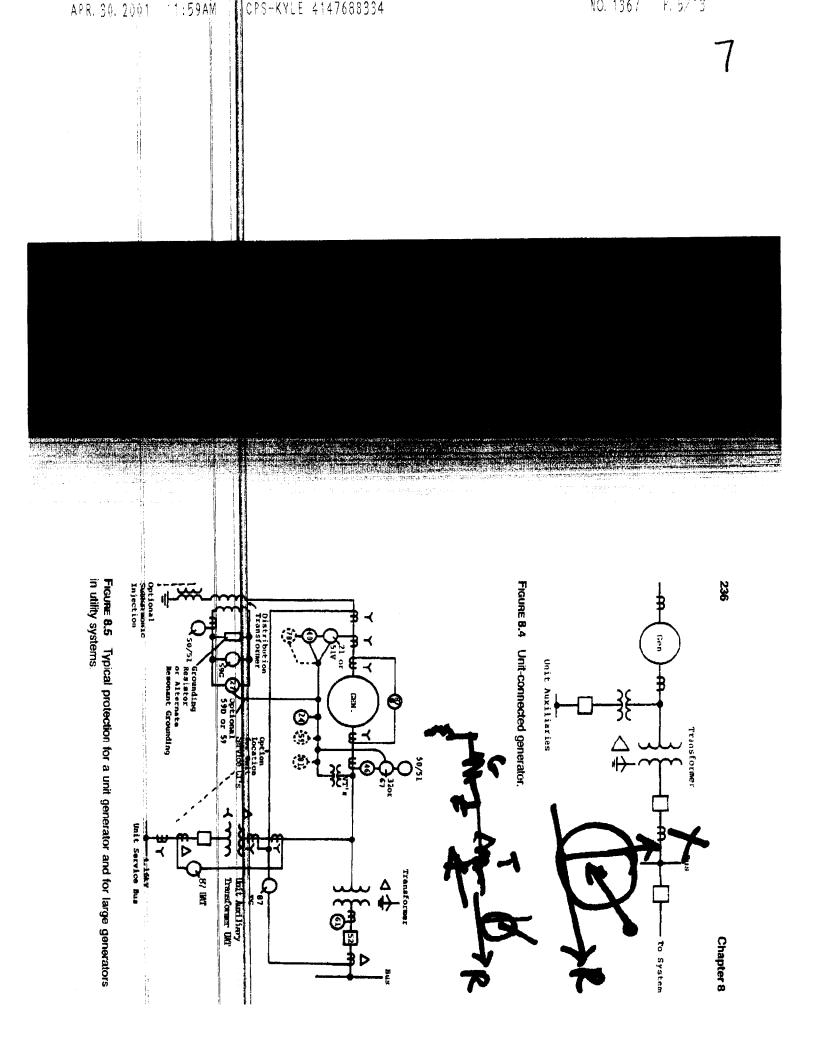always applicable voltage mandatory for nonutility generators connected to a utility; (#50) not lays are optional except 29/57 under- or overvoltage and 81 under- or over-FIGURE 8.3 Typical protection for a direct-connected generator. (\*) Dotted re



Generator

Generator

Grounded as Desired

FIGURE 8.6 Differential protection for small generator units with flux summation current transformers and an instantaneous overcurrent (50) relay.

\*50 For the 876 Function

side of the breaker and the generator neutral side leads are carried to that point. This is seldom practical, so other protection must be provided for this area between the flux summation (T and the breaker. In general, this scheme (see Fig. 8.6) is more sensitive as long as the generator CT ratio is greater than 150:5 to 200:5. If the flux summation CT is not applicable and differential protection is desired, the scheme of Fig. 8.7 can be used.

## 8.3.2 Multi-CT Differential Protection (87) for All Size Generators

The basic principles of this protection were covered in Section 6.2. It is widely used to provide fast and very sensitive protection for the generator and associated circuits. The 87 relays are consected to two sets in content.—transformers, one set in the neutral leads, the other in the line side. For

transformers; one set in the neutral leads, the other in the line side. For generators with associated breakers, the line-side CTs are usually associated with the breaker, as shown in Figs. 8.2 and 8.3.

For unit generators the line-side CTs are usually quite close to the generator, basically at the generator terminals. Typical connections for the three-phase units are shown in Fig. 8.7 for both wye- and delta-connected generators.

If current transformers are available at each end of the windings for the delta-connected generators of Fig. 8.7b, differential relays can be applied

the delta-connected generators of Fig. 8.7b, differential relays can be applied for winding protection. The connections would be similar to those shown in Fig. 8.7a. However, this would not provide protection for the junction points or the phase circuits that are within the protective zone (see Fig. 8.7b).

238

Ŋ

)



Chapter 8

**Generator Protection** 

rounded s Desired

for the 87G Function

eous overcurrent (50) relay. generator units with flux sum-

g. 8.7 can be used. T is not applicable and differe generator CT ratio is greater breaker. In general, this scheme ction must be provided for this I side leads are carried to that

## in (87) for All

ve protection for the generator covered in Section 6.2. It is mageted to two sets of current

are usually quite close to the side CD are usually associated he other in the line side. For

noth wye- and delta-connected ls. Typical connections for the


otection for the junction points ld be similar to those shown in ective zone (see Fig. 8.7h) ifferential relays can be applied each end of the windings for

# TURN-TO-TURN FAULT

239

000

**(B)** 

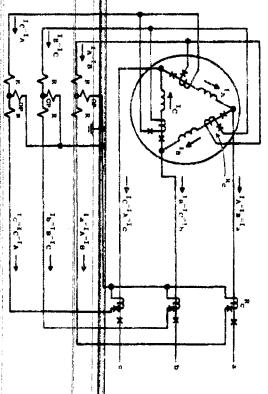

connected generator. and delta-connected generators: (a) wye-connected generator; (b) delta-FIGURE 8.7 Typical differential (87) connections for the protection of wye

CT RATIOS/MISOPERATIONS

દ

IEEE GUIDE FOR

#### CONTINUOUS UNBALANCE CURRENT CAPABILITY

A generator shall be capable of withstanding, without injury, the effects of a continuous current unbalance corresponding to a negative-phase-sequence current I of the following values, providing the rated kVA is not exceeded and the maximum current does not exceed 105 percent of rated current in any phase. (Negative-phase-sequence current is expressed as a percentage of rated stator current).

Type of Generator	Permissible I, (percent)
Salient Pole	
With connected anortisseur windings	10
With non-connected amortisseur windings	5
Cylindrical Rotor	
Indirectly cooled to 960 MVA	10
961 to 1200 MVA 201 to 1500 MVA	8 6 5
	•

These values also express the negative-phase-sequence current capability at reduced generator kVA capabilities.

#### UNBALANCED FAULT CAPABILITY

Negative sequence current is expressed in per unit of rated current and time is in

Type of Generator	Permissible I <sub>2</sub> <sup>2</sup> t
Salient pole generator  Synchronous condenser  Cylindrical rotor generators	40 30
Indirectly cooled Directly cooled (0-800 MVA) Directly cooled (001-1600 MVA)	20 10 see curve below

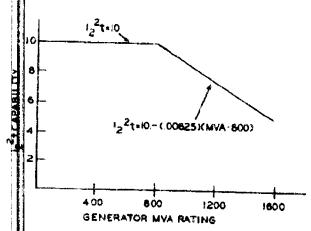


Fig 4.5.2-1 Continuous and Short-Time Unbalanced Current Capability of Generators (from ANSI C50.13-1977 [1])

current may be above relay pickup and the magnitudes of the harmonics may not be sufficient to provide adequate testraint.

Three approaches have been used to prevent such operations. One approach uses a volts/Hz relay to block tripping of or to desensitize the transformer differential relay when the volts/Hz exceeds a specified level.

The second approach uses a modified differential scheme which extracts and utilizes a third harmonic exciting current from the transformer delta winding to restrain the relay from operating during an overexcitation condition. It should be recognized that the first two approaches somewhat degrade the differential protection.

The third approach utilizes a differential relay


The third approach utilizes a differential relay that restrains on the fifth harmonic as well as the second harmonic. The fifth is the lowest harmonic flowing from the celta windings under balanced conditions.


4.5.4.4 Tripping. This protection is generally connected to trip the main generator breaker(s) and the field breaker(s) and transfer auxiliaries if necessary. Again, this permits fast resynchronization of the generator if the overexcitation condition can be remiddled quickly. When a unit is off-line, alarm and inhibit circuits may be required to prevent an operator from exceeding safe levels of excitation when preparing a unit for synchronizing. See the caution in 4.5.1.4.


4.5.5 Anti-Motoring. Motoring of a generator occurs when for some reason the energy supply to the prime mover is cut off while the generator is still on line. When this occurs, the generator will act as a synchronous motor and drive the prime mover. While this condition is defined as generator motoring, the primary concern is the protection of the prime mover which can be damaged during a motoring condition.

4.5.5.1 General Considerations. Motoring causes many undesirable conditions. For example, in a steam turbine, the rotation of the turbine rotor and blades in a steam environment causes idling or windage losses. Since windage loss is a function of the diameter of rotor disc and blade length, this loss will usually be greatest in the exhaust end of the turbine. Windage loss is also directly proportional to the density of enclosing steam. Thus, any situation in which the steam density is high will cause dangerous windage losses. For example, if vacuum is lost on the unit, the density of the exhaust steam will increase and cause the windage losses to be many times greater than normal. Also, when high density steam is entrapped between the throttle valve and the interceptor valve in reheat units, the windage losses in the high pressure turbine are very high.

Windage loss energy is dissipated as heat. The steam flow through a turbine has a two-fold purpose—to give up energy to cause rotation of

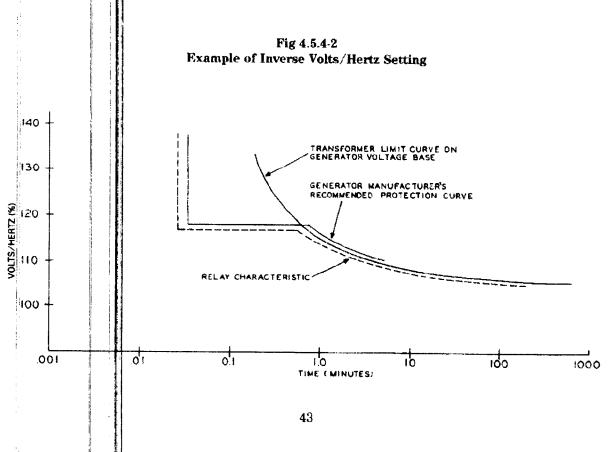

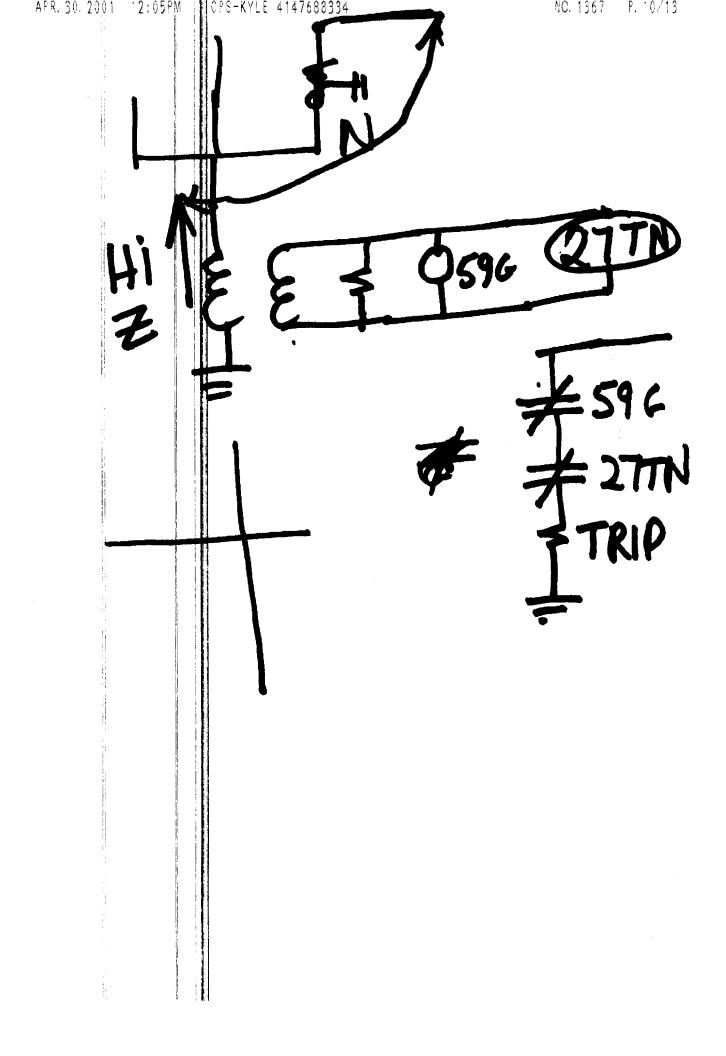

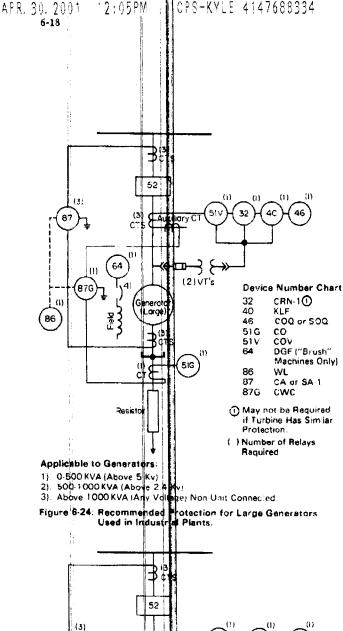

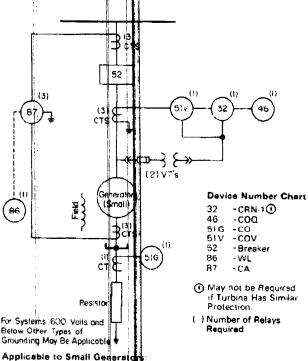


Figure 6-25: Recommended Potection for Small Generators as Used in Industrial Plants.

1) 0-500 KVA (Below 5 kv) 2) 500-1000 KVA (Below 2

#### XVI. BUS TRANSFER SYSTEMS FOR STATION AUXILIARIES

Automatic transfer of highly essential station auxiliary loads such as boiler feed pumps and induced draft fans is common practice. Paralleling the normal and emergency sources is not generally recommended, however, because the higher breaker interrupting duties involved can cause problems, as can circulating currents between systems. The transfer scheme requires interlocks to prevent paralleling of the supply sources. Transfers should not be made if voltage in the alternate supply is not satisfactory or the load circuits are faulted. Also, supply breaker tripping should be delayed long enough to permit fault sectionalizing in the load circuits. An example of a transfer scheme using type CP polyphase voltage relays is shown in Figure 6-26.

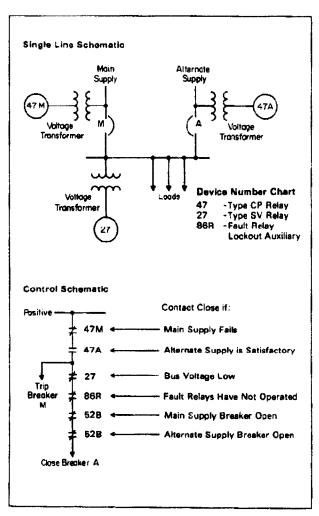


Figure 6-26: Bus Transfer Schame Utilizing Polyphase Voltage Relays.

The SC relay (of SV for the CV-8) recommended as supplementary protection in several areas indicated by an asterisk in Table 6-III. Use of this relay is optional in the A and B classifications and will depend on the need for additional sensitivity. The SC current relay has a flat characteristic, and increases slightly in sensitivity as the operating frequency drops. When an SC relay is operated on dc, it picks up at approximately 15 percent below its normal 60-Hz pickup. The pickup of the St voltage relay is almost directly proportional to frequency; its sensitivity at 15 Hz is thus 4 times the sensitivity 60 Hz. For this reason, the SV relay provides excellent backup protection for 60-Hz voltage relays that lose their sensitivity at low frequencies.


With one exception, the relays listed in Table 6-III will neither overheat nor operate incorrectly if left in the circuits when the generator is operated it reduced frequencies. The KLF and KLF-1 relays, when use in a cross-compound configuration, must have their trip in apacitated during start-up.

#### XIV. RECOMMENDED PROTECTION

Figures 6-22 and 6-23 show the recommended protection for large tandem-compound and cross-compound, unitconnected turbine generators. Figures 6-24 and 6-25 show the recommended protection for machines that are not unit connected. Generally, such generators are used in industrial applications.
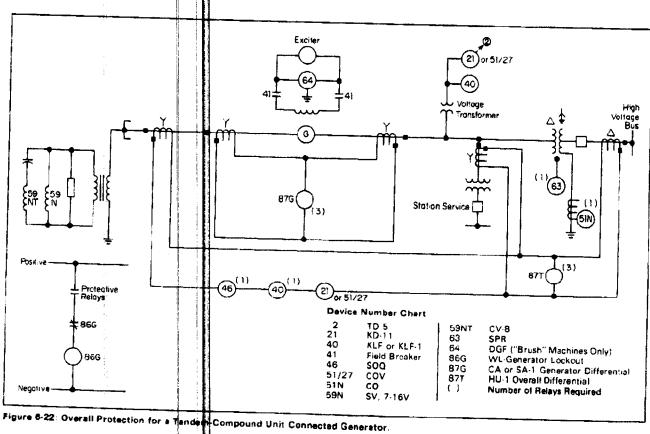
#### XV. OUT-OF-STEP PROTECTION

As generator impedances become larger in proportion to the system, the electrical center will be closer to the generator. This condition intensifies the need for out-of-step detection as part of the generator relaying complement. Such relaying schemes are described in Chapter 19, System Stability and Out-of-Step Relaying.



%.30.2001 12:0/PM 1||CFS-KYLE 4147688334 NO.1367 P. 13/13

