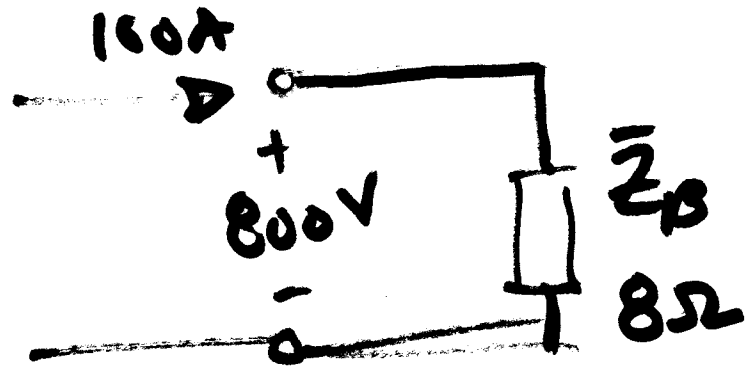



Ongoing List of Topics:


- URL: <http://www.ece.mtu.edu/faculty/bamork/EE5223/index.htm>
- Labs - EE5224 no labs during WC week.
- Term Project - guidance after WC break.
- Software - Aspen V15.6. remote.mtu.edu : confirm operation.
- **Team pre-req homework 3B - due Feb 21st. Short circuit calcs!**
- CT ratios, MR (multi-ratio) CTs - look at IEEE stds.
 - X/R ratio, dc offset, decay of dc offset
- Calculation of measurement error for given ratio & burden.
- Print out MOCT & CCVT handout from web page
- MOCTs - Magneto-Optic Current Transformers
 - Faraday effect, "faraday rotators," Verdet constant
 - shift of polarization angle due to strength of H-field
 - Design kept to low near-linear range
- Linear Couplers, Rogowski Coils
- CCVTs
- Voltage & Current relationships during faults, §3.5-3.10
 - relative angles and magnitudes of all Vs & Is during fault




$|\bar{Z}_B| < 8\Omega \Rightarrow \text{Error} < 10\%$
 $|\bar{Z}_B| > 8\Omega \Rightarrow \text{Error} > 10\%$
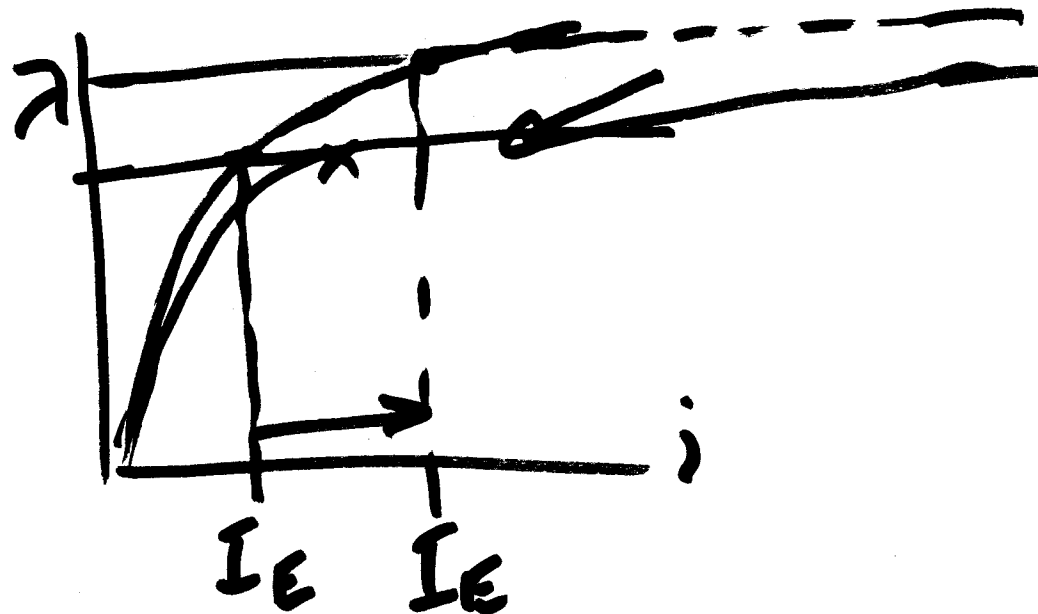
$$e = \frac{d\lambda}{dt} = N \frac{d\phi}{dt}$$




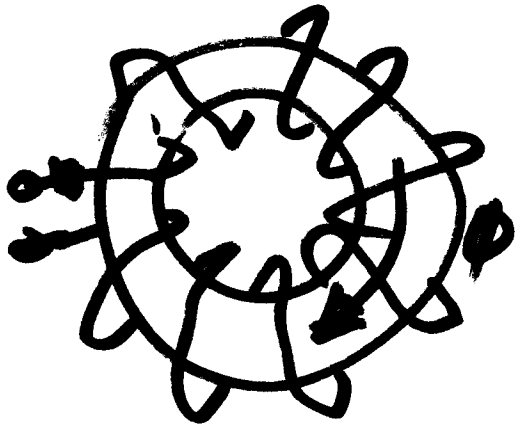

\bar{E}_{SE}

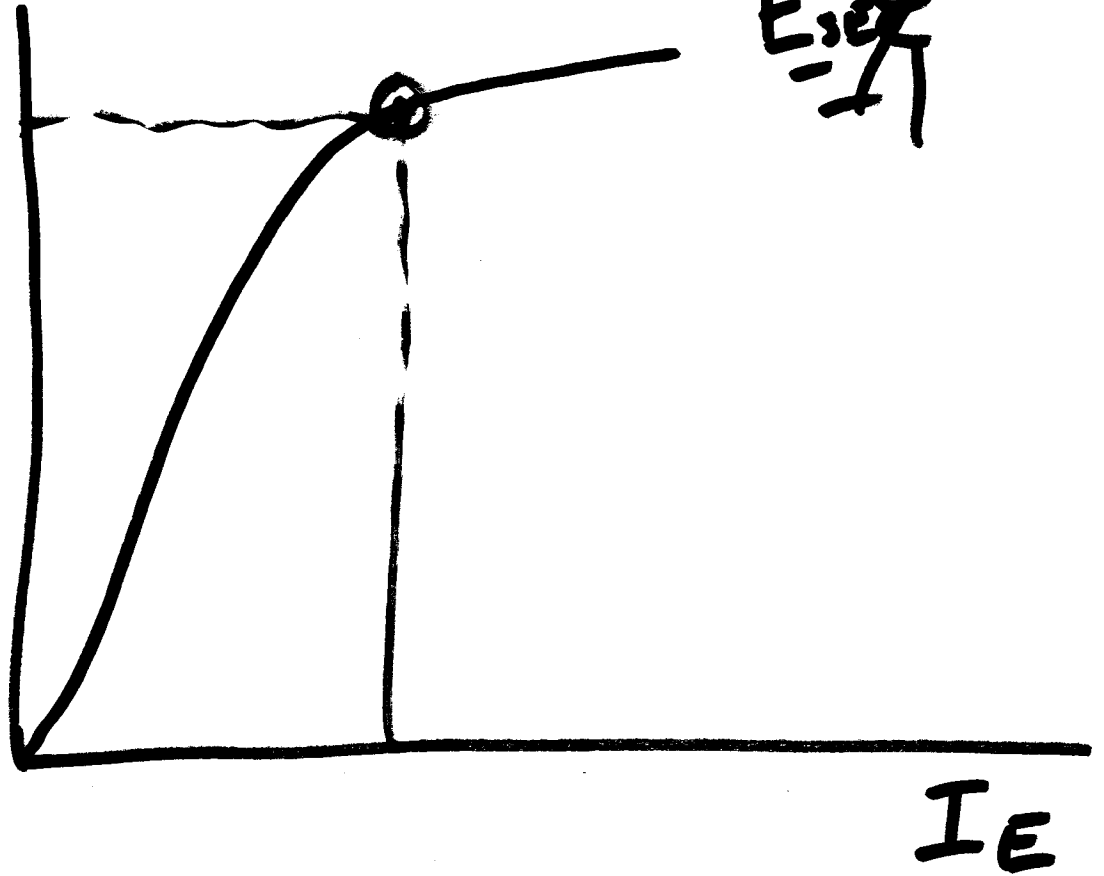


E_{SE}

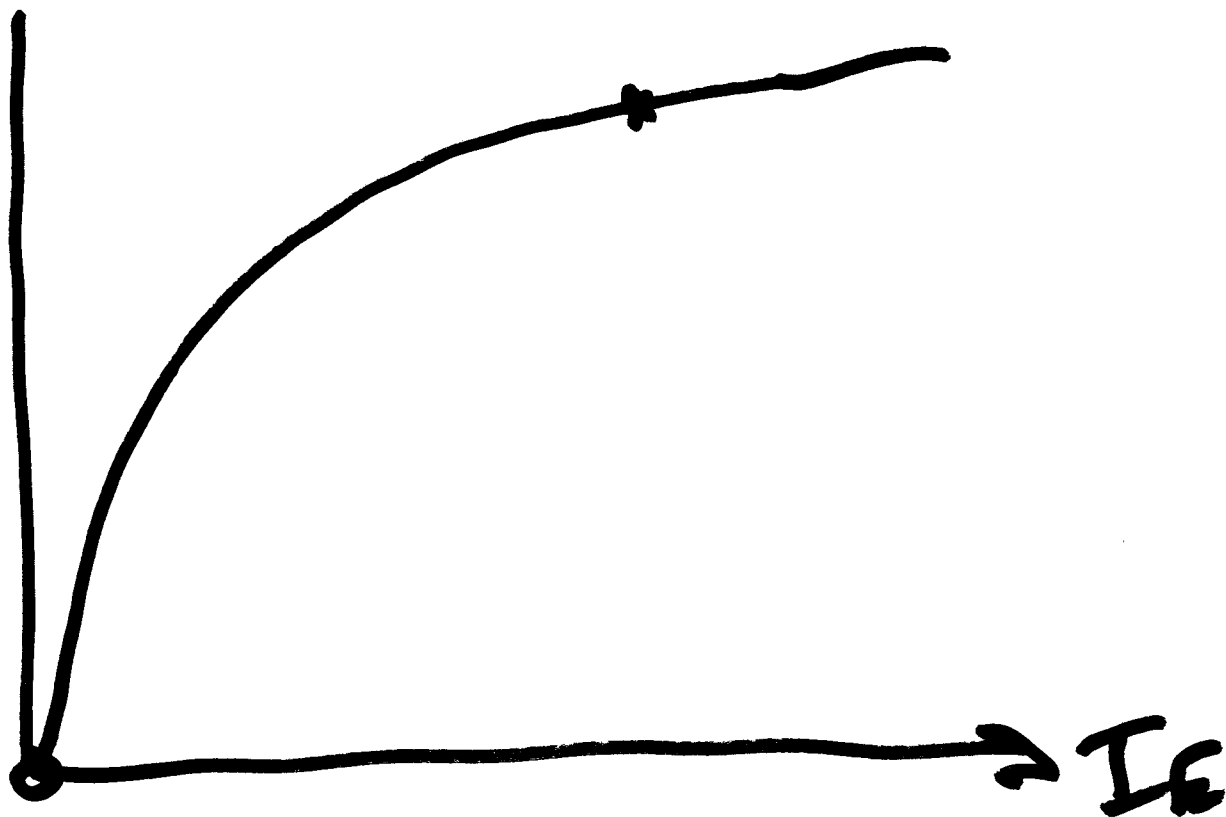

G1 Burden

$Z_B \Rightarrow$

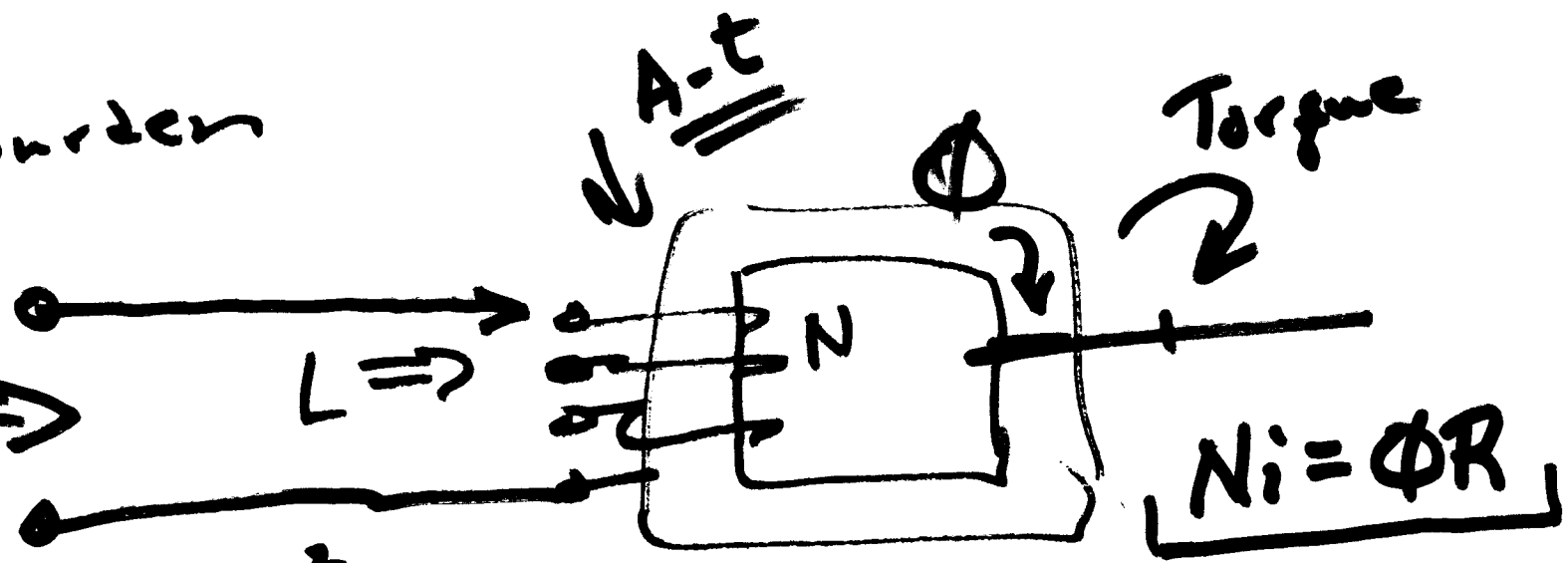

$$L = \frac{N^2}{R}$$

\Rightarrow Low top settings have highest Z_{Burden} !

51

Taps: 4 - 12 A


Z_B is max


Z_B is min

G2 & G3 relays:
much smaller Z_B
But: look at I.L.!


$$\left(\frac{1200}{5}\right) \times \underset{\substack{\uparrow \\ 1.004}}{\text{RCF}} =$$

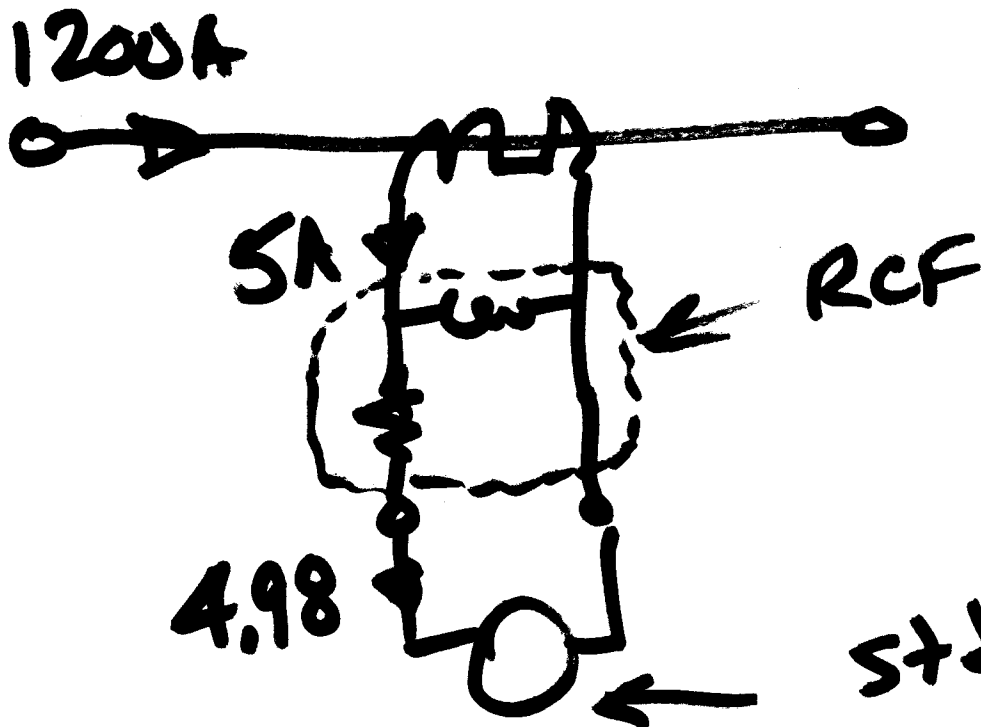
$$240 \times 1.004 = \underline{\underline{240.96}}$$




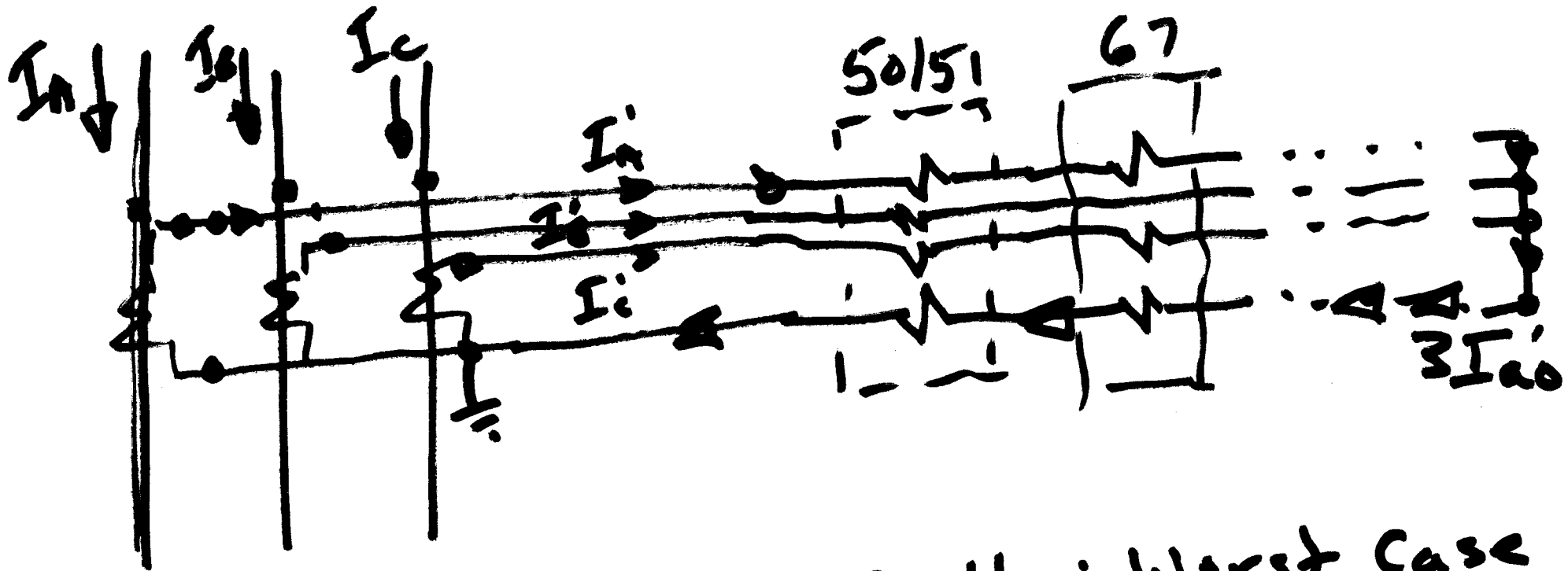


$\Phi A-G$ Fault : Worst Case Burden.

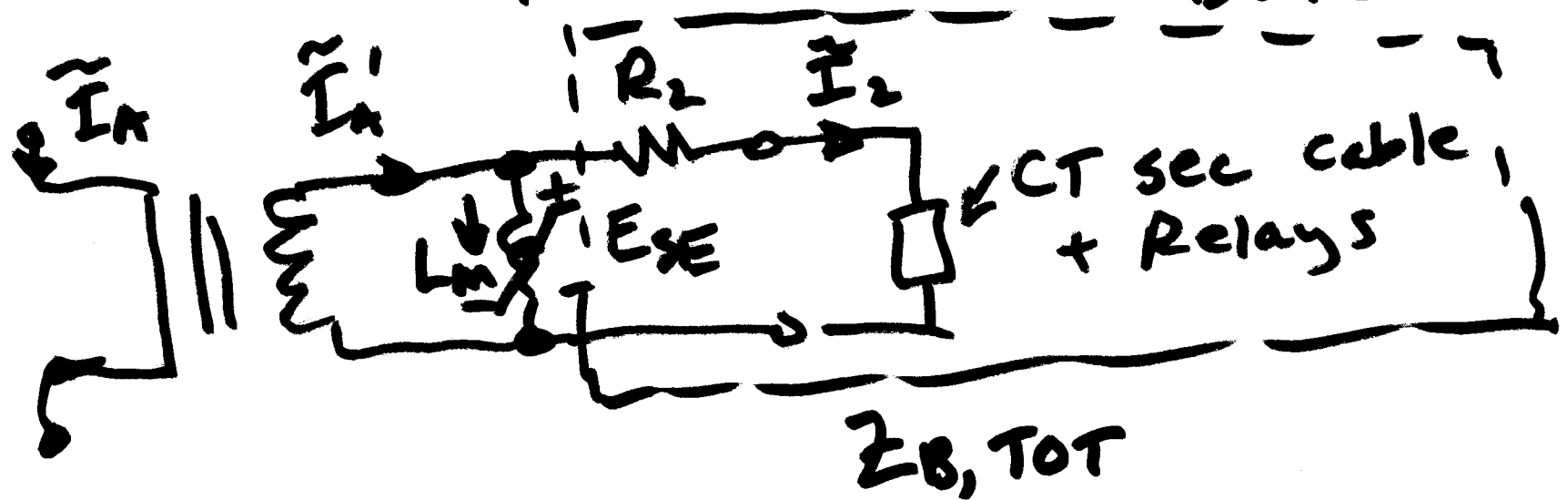

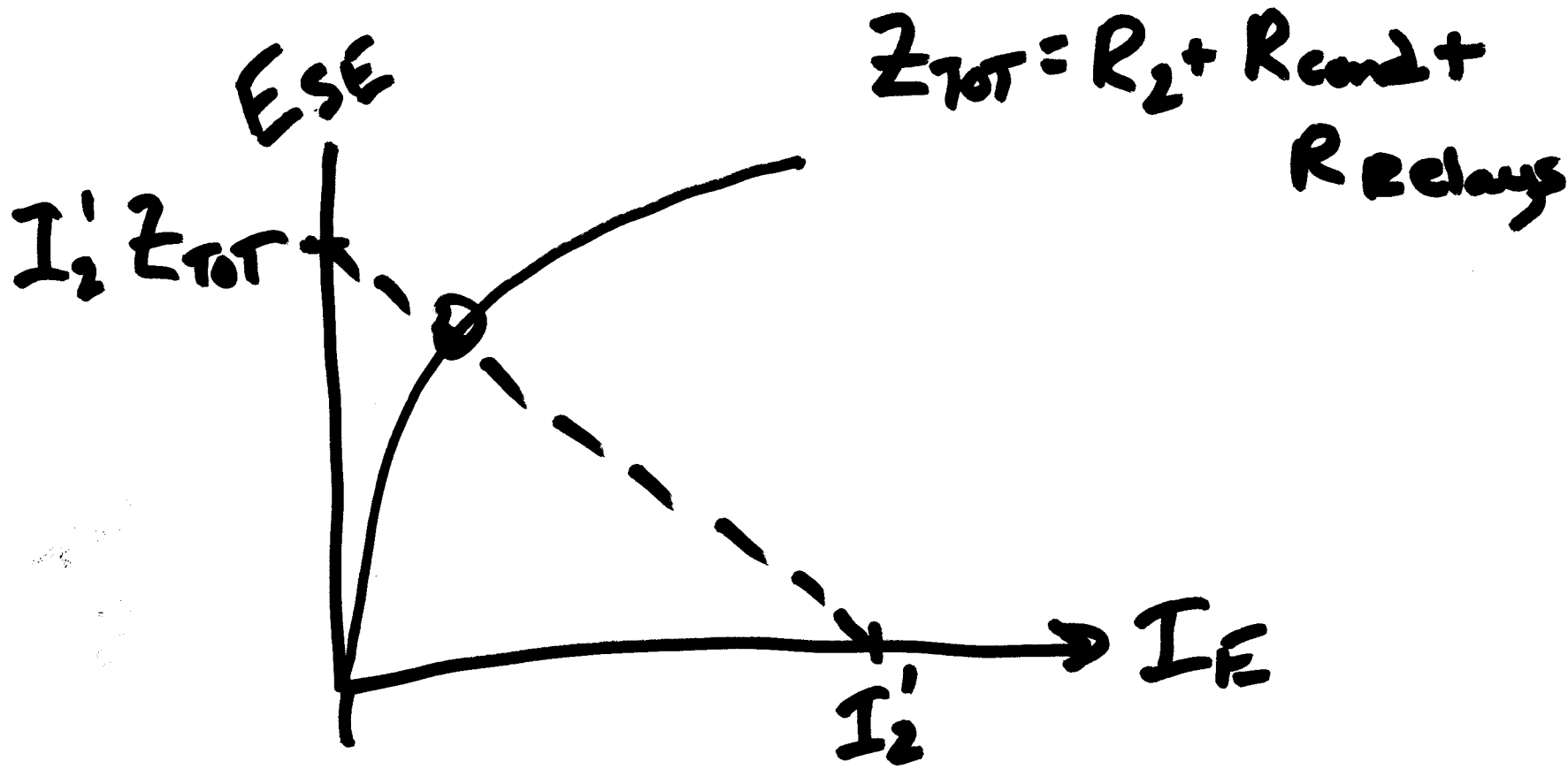

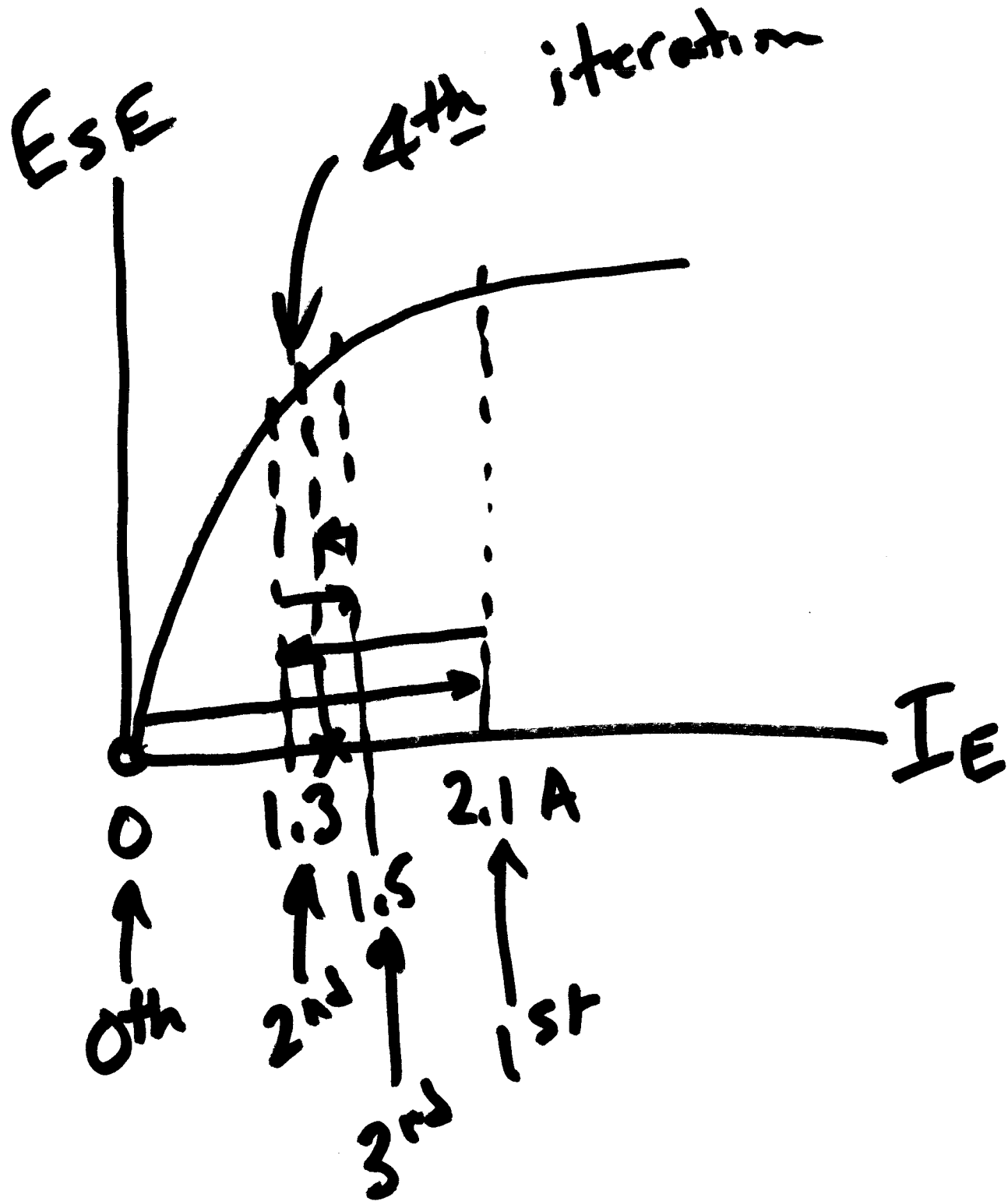


E_{SE}

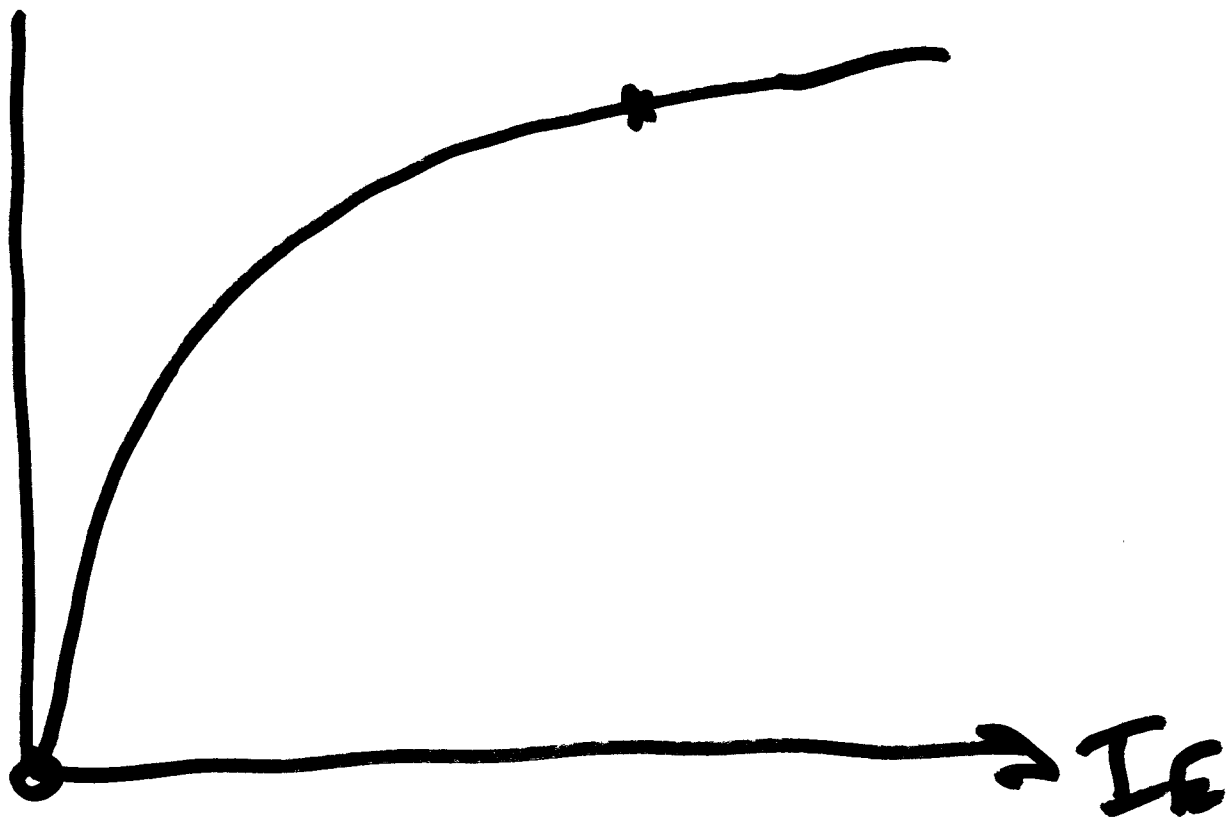

G1 Burden

$Z_B \Rightarrow$

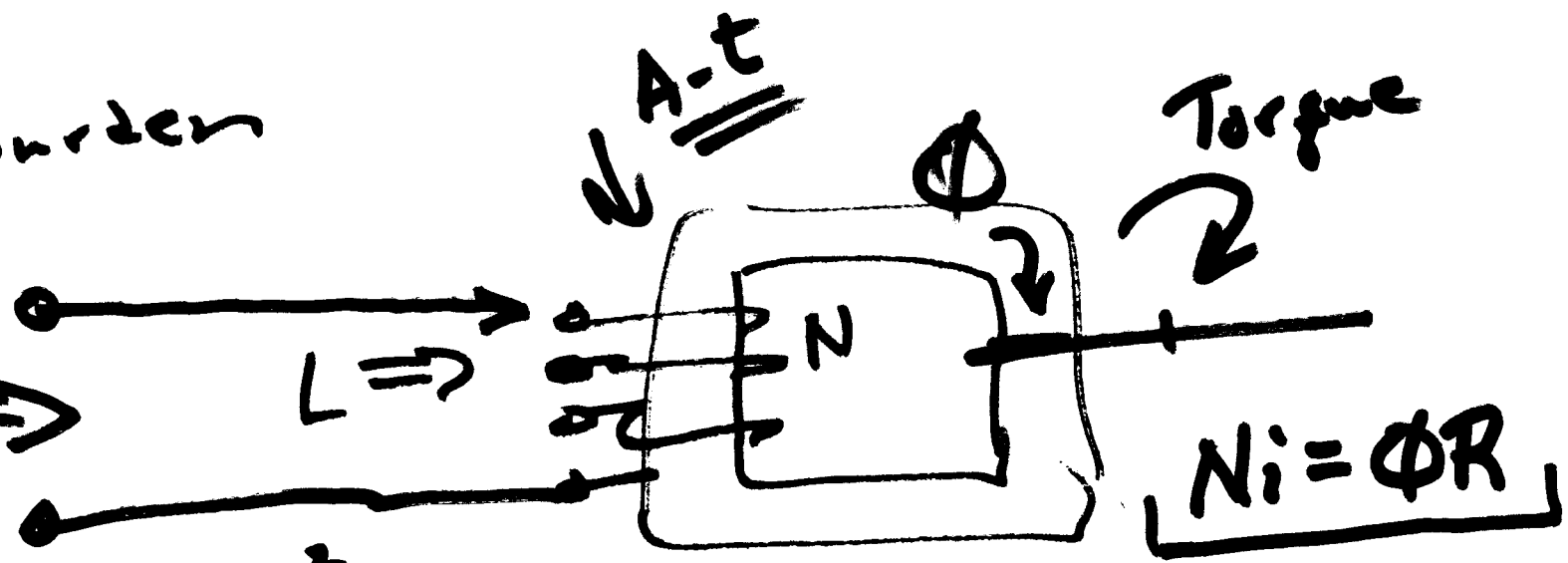

$$L = \frac{N^2}{R}$$

\Rightarrow Low top settings have highest Z_{Burden} !

51

Taps: 4 - 12 A

Z_B is max

Z_B is min

G2 & G3 relays:
much smaller Z_B
But: look at I.L.!


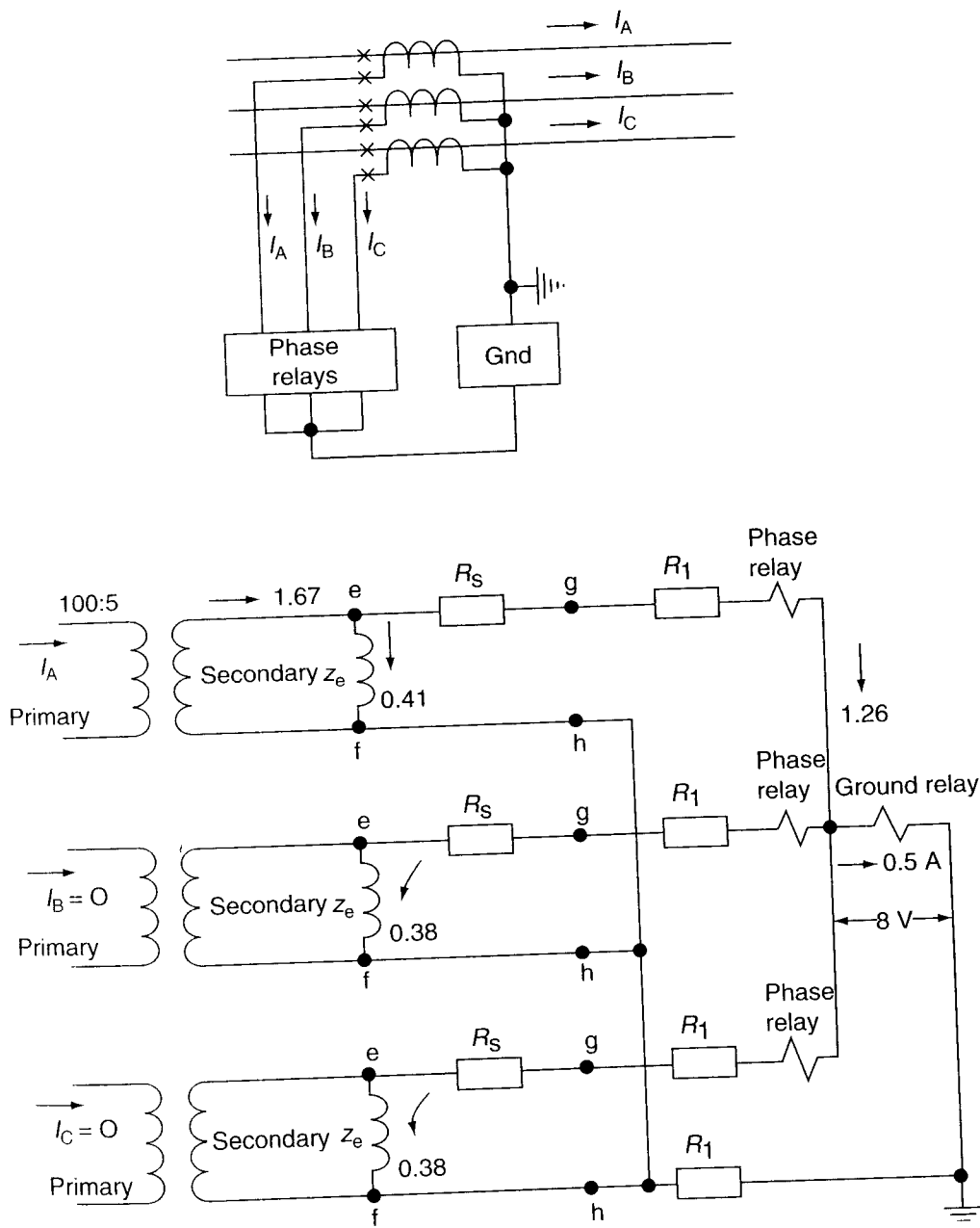


FIGURE 5.12 Phase-and-ground relays for the protection of a circuit and the current distribution for a phase-and-ground fault.


16 Ω on its 0.5 A tap 68° lag. To pass pickup current through the ground relay, $0.5 \times 16 = 8$ V is required. This voltage, less the small drop through the phase relay circuit, will appear across the phase B and C current transformer secondaries to excite them. The voltage V_{ef} depends on the current that, in turn, depends on the voltage, so the exact determination is a "cut-and-try" process. At the first try, assume that $V_{ef} = 8$ V. From the CT characteristic

L-G fault
on Phase A.

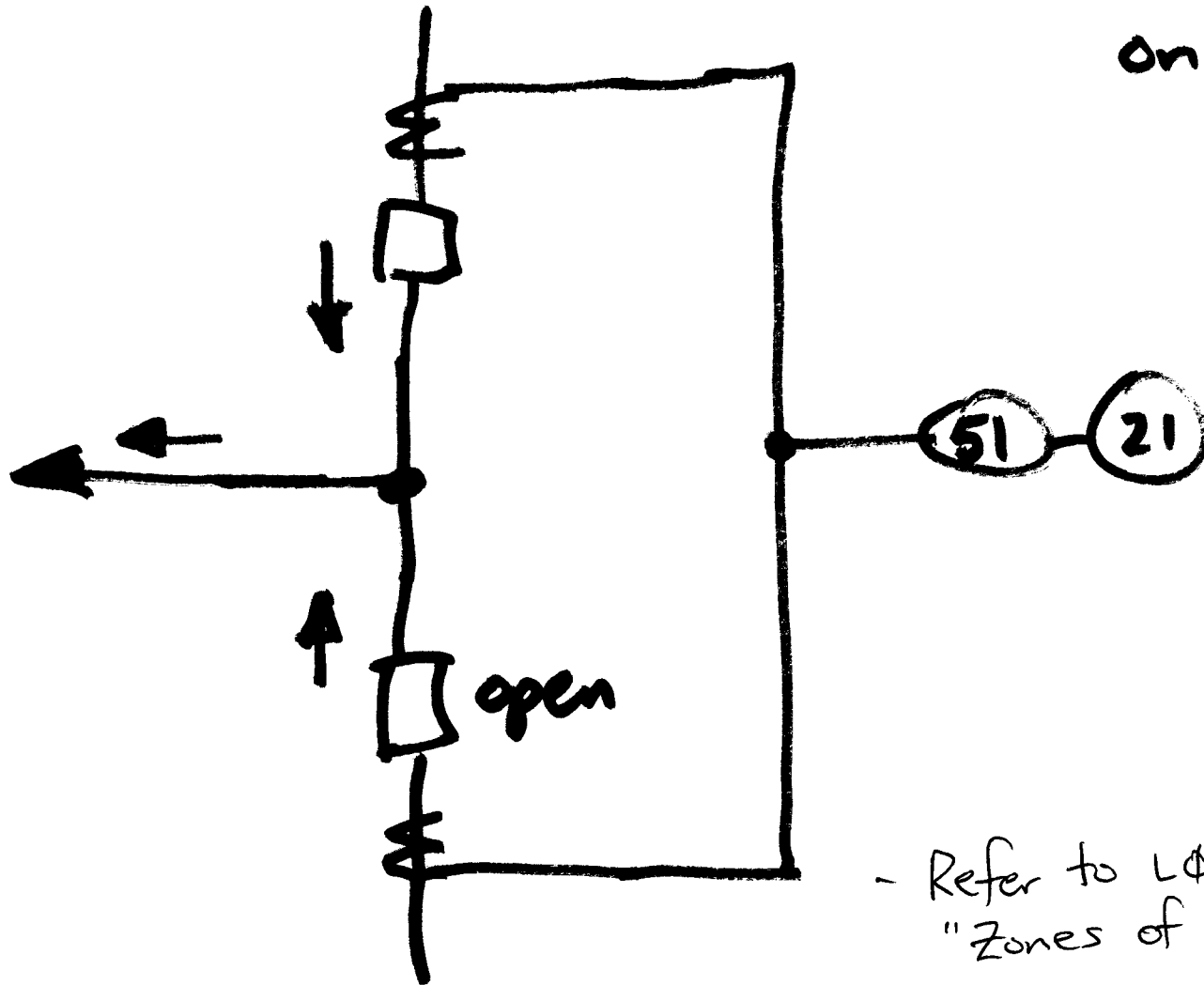

- Refer to LØ3 notes on "Zones of Protection"
- Refer to CT notes posted on Week 1 (web page).

DA-G Fault

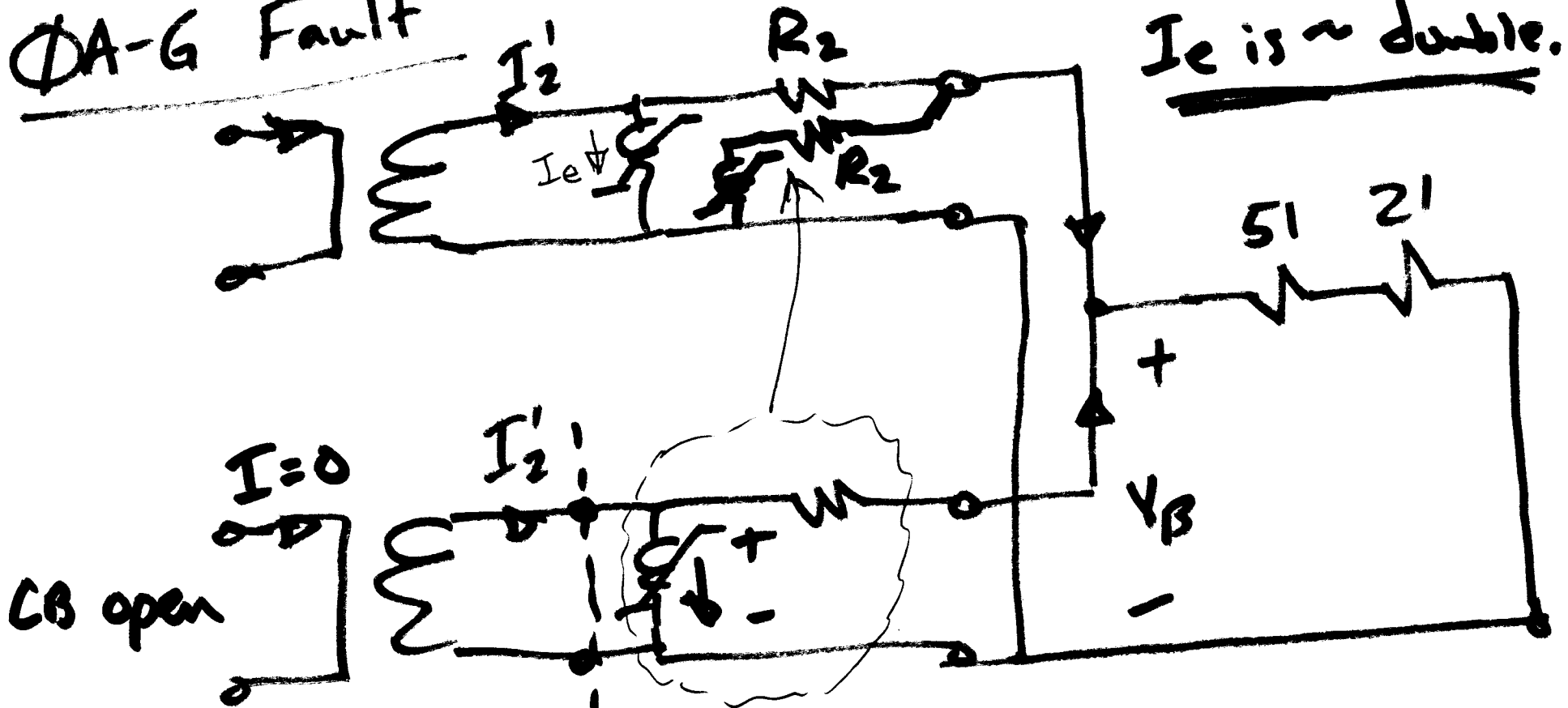

Ie is ~ double.

CB open
I=0

open ckt.


Ie flows in CT even though its Pri: current is zero!

RCF:

$$\text{Ratio}_{\text{ACTUAL}} = (\text{Ideal Ratio}) \times \text{RCF}$$

From previous example:
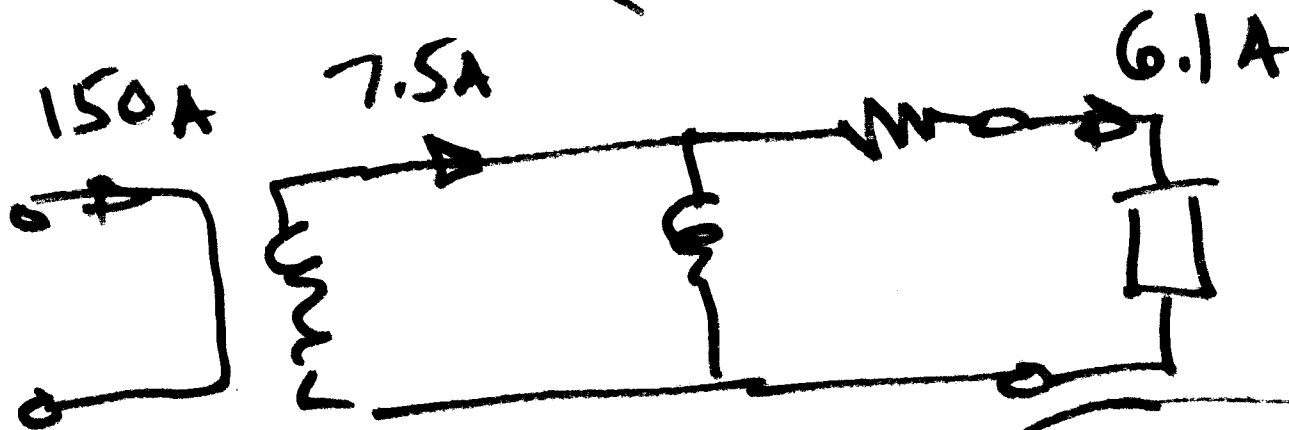
$$\frac{150}{6.1} = \left(\frac{100}{5}\right) \times \text{RCF} \Rightarrow \underline{\underline{\text{RCF} = 1.23}}$$



Typically,
 $\text{RCF} > 1$

$\text{RCF: Keep} \leq 1.1$
(10C800)

$$\left(\frac{1200}{5}\right) \times \underset{\substack{\uparrow \\ 1.004}}{\text{RCF}} =$$

$$240 \times 1.004 = \underline{\underline{240.96}}$$

