
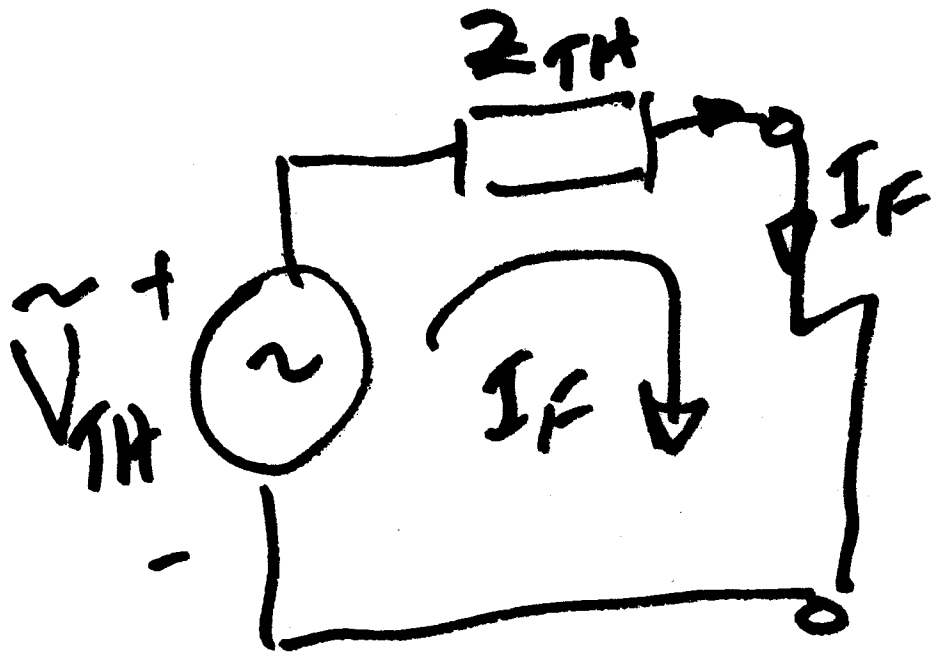

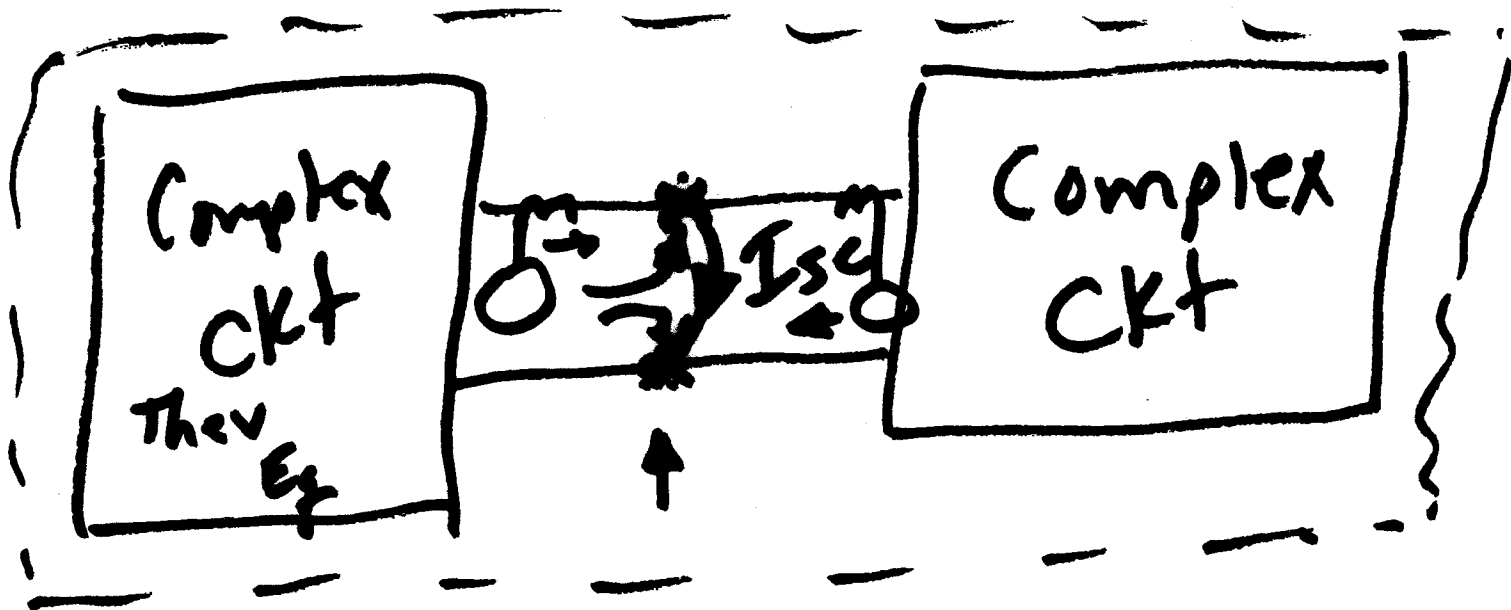
## Ongoing List of Topics:

- URL: <https://pages.mtu.edu/~bamork/EE5223/index.htm>
- Term Project - last few proj/teams being firmed up and getting moving.
  - Follow timeline, see posting on web page
  - Weeks 6 thru 9 - develop formal outline w/complete reference list
- Protection fundamentals (cont'd):
  - Again — overview of bus diff, xfmr diff, synch check, capacitor banks, generators, motors, etc. (take a quick run through Ch.6, also Glover & Sarma, Ch.10).
  - Sequence networks, fault calcs
    - Transformers: Y- $\Delta$ ,  $\Delta$ -Y, Auto- $\Delta$
    - Overall network calculations


- Protection fundamentals in preparation for next EE5224 relaying lab:
  - Gen diff 87G - quite simple, connect CTs so current flows in “do-nothing” loop through Restraint elements (resulting in near-zero current through Operate element). Use equal (preferably full) ratio with all CTs. Differential slope of trip characteristic is rather flat compared to 87T below. Example shown of how not to connect CT secondaries.
  - Xfmr diff 87T - a) must connect CT secondaries to provide proper phase shift so that restraint currents flowing through restraint elements are in phase; b) relay settings are used to compensate for pri voltage ratio and CT ratios. CT accuracy problems can be a big concern due to having to use less than full CT ratio, and having Pri and Sec CTs with different accuracy levels. Differential slope of trip characteristic can be 10%, 15%, 25% to allow for mismatch (measurement error) due to CT accuracy problems.




$$\tilde{V}_{TH} = \tilde{V}_{oc}$$

$$\tilde{Z}_{TH} = \tilde{V}_{oc} / \tilde{I}_{sc}$$


$$\tilde{I}_{sc} = \tilde{I}_N$$

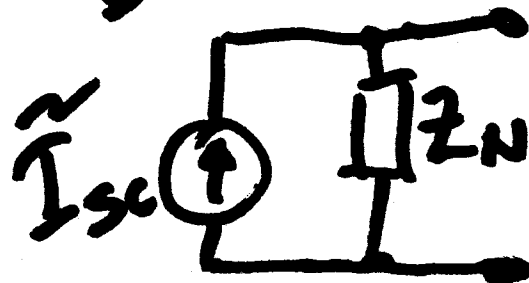

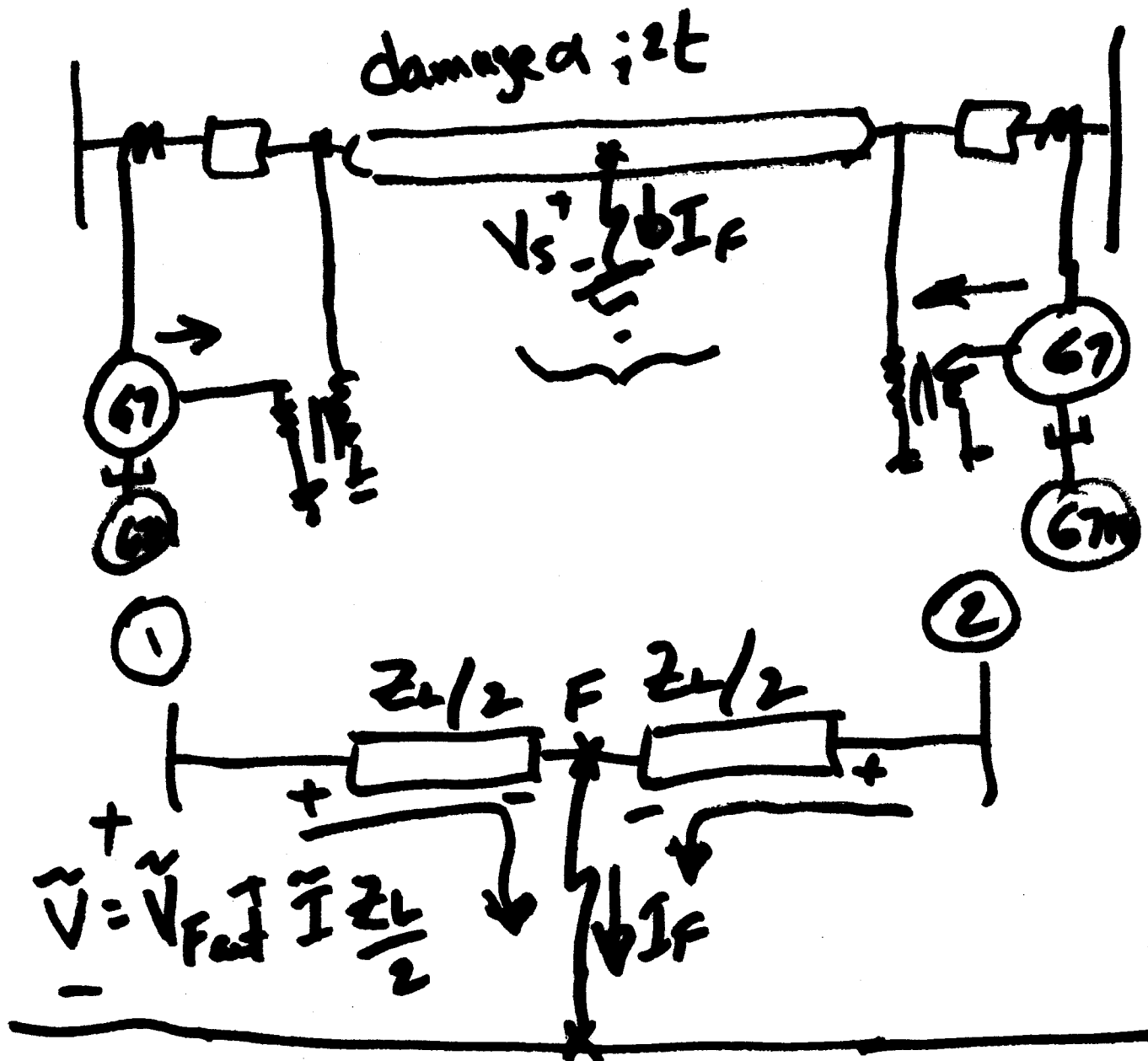

i.e. 
$$\begin{bmatrix} \tilde{V}_{a0} \\ \tilde{V}_{a1} \\ \tilde{V}_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} \tilde{V}_a \\ \tilde{V}_b \\ \tilde{V}_c \end{bmatrix}$$


Sequence Networks  
Per Phase, 4AN, P.U.

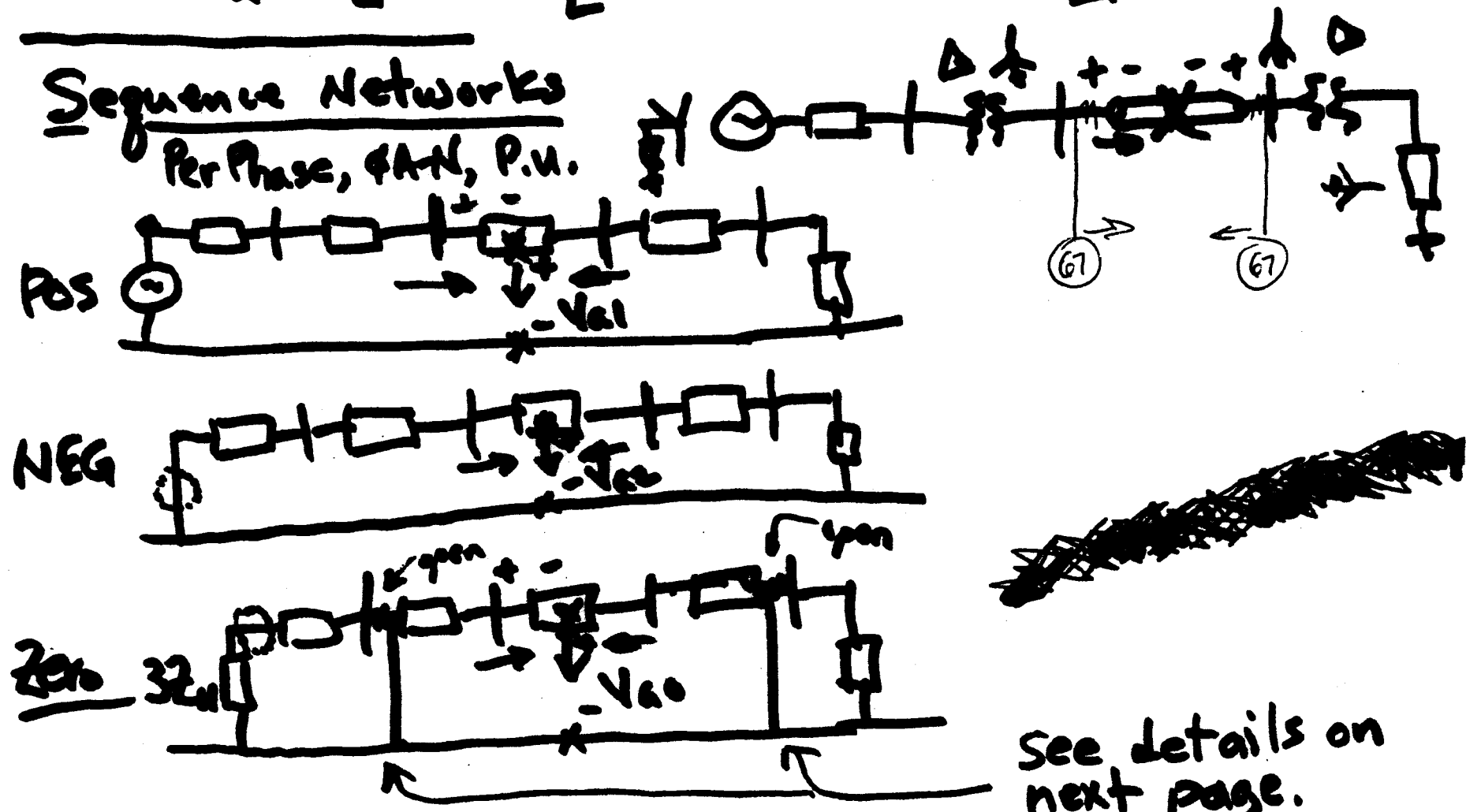

See details on next page.




L23


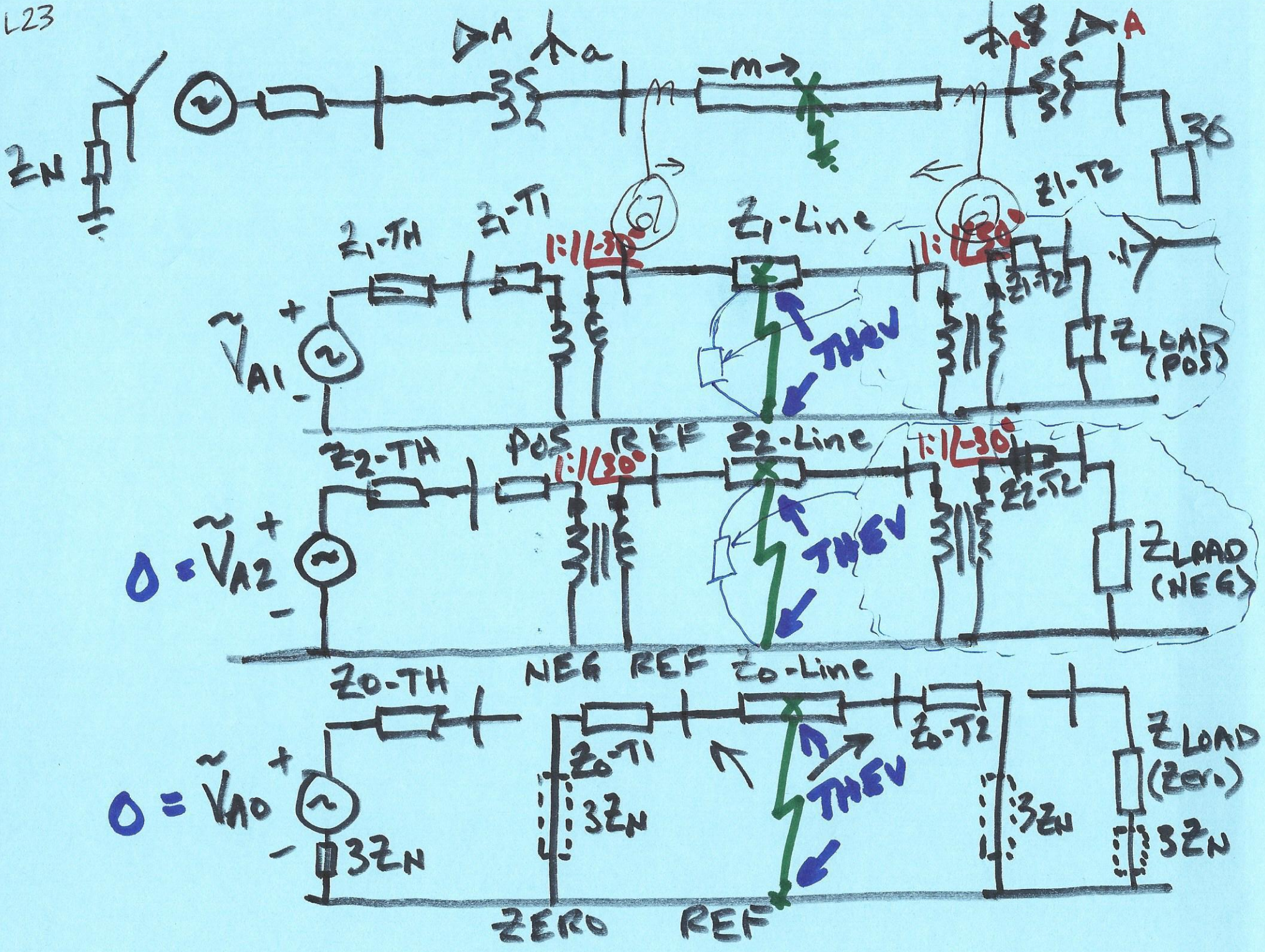







L23

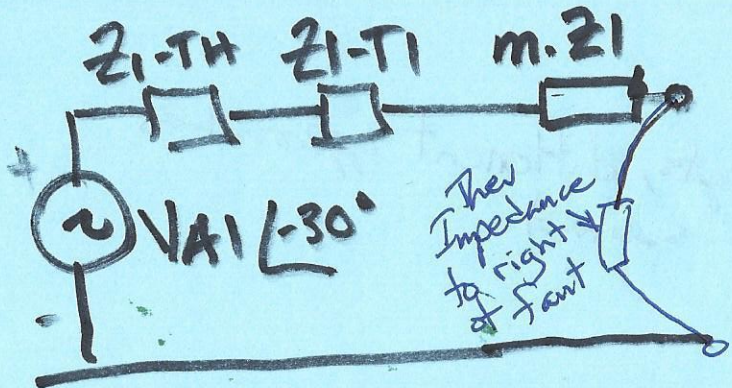

$\Rightarrow$

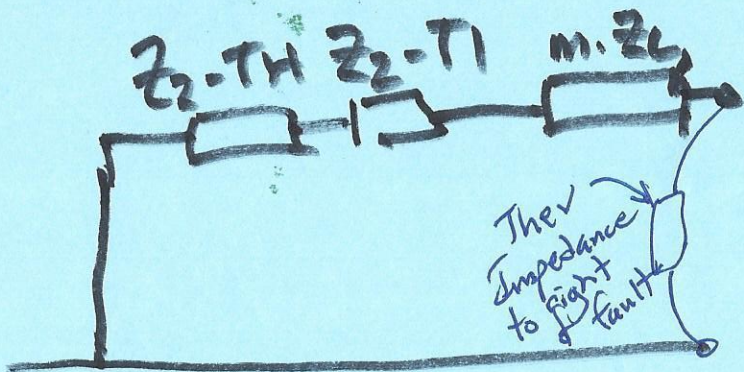
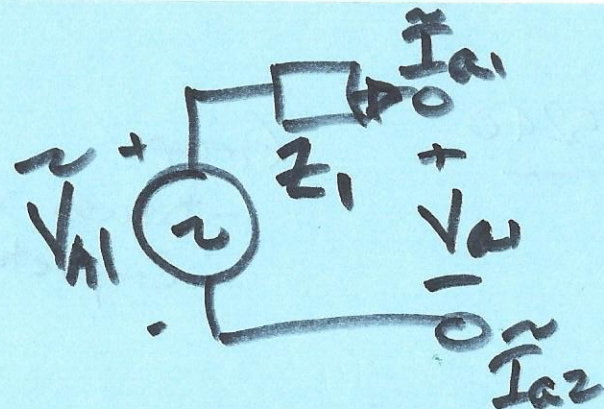


$\Rightarrow$

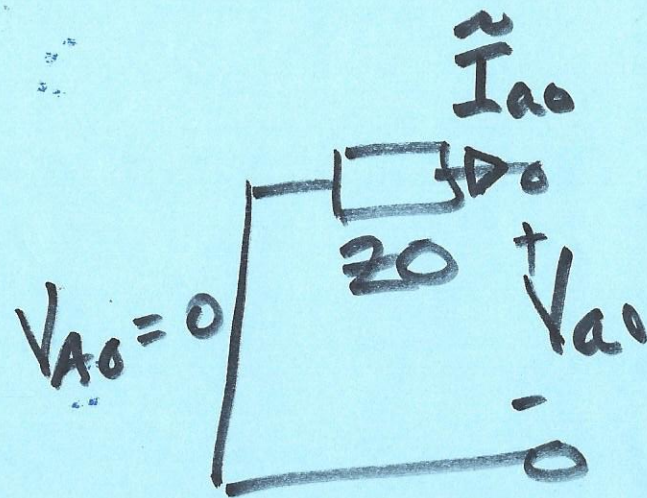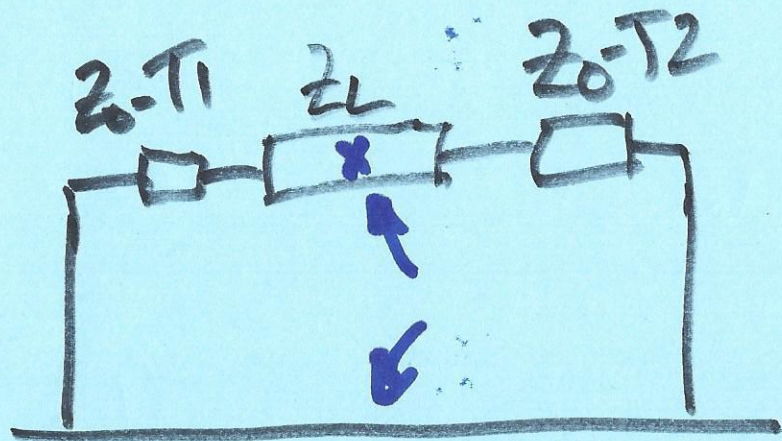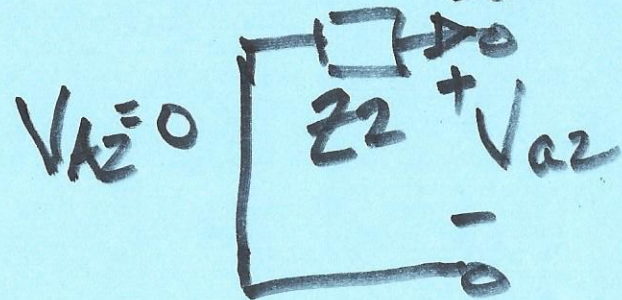




L23

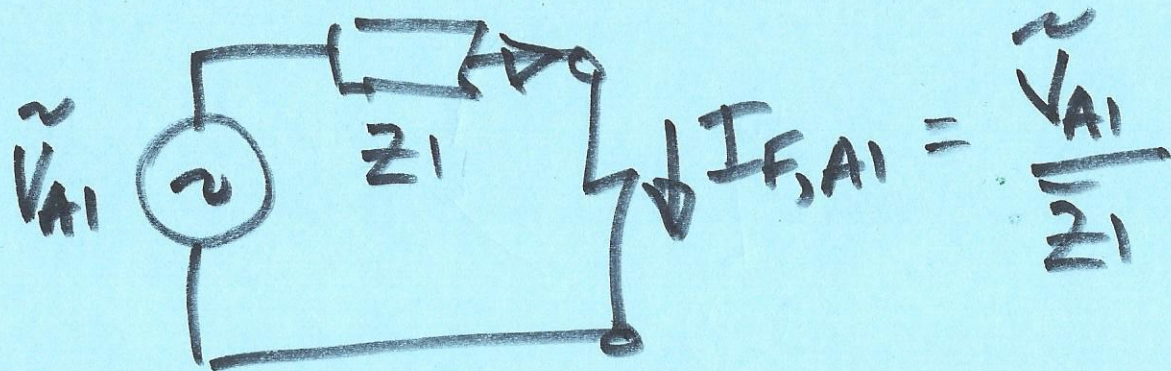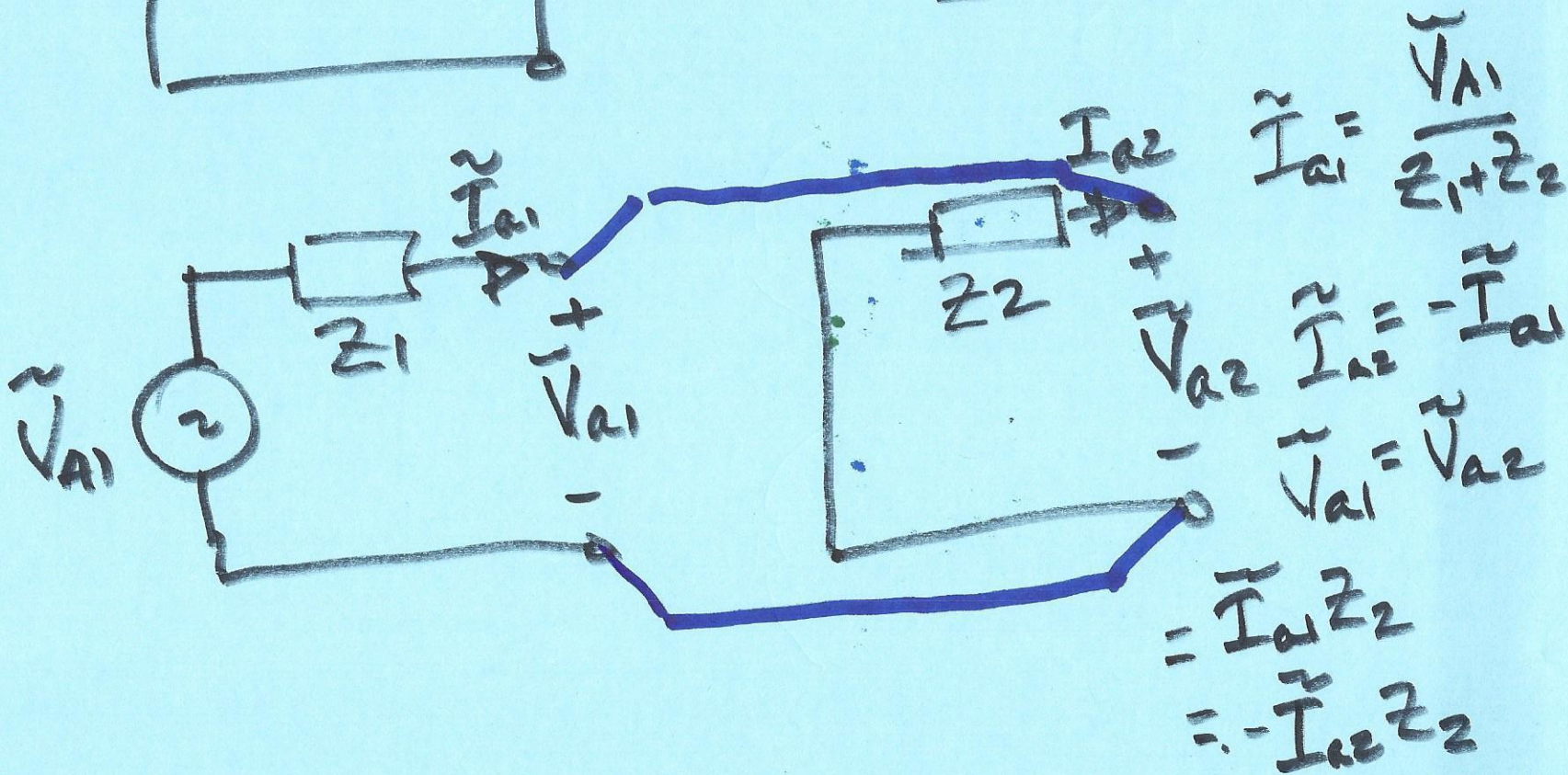3 $\phi$ L-L



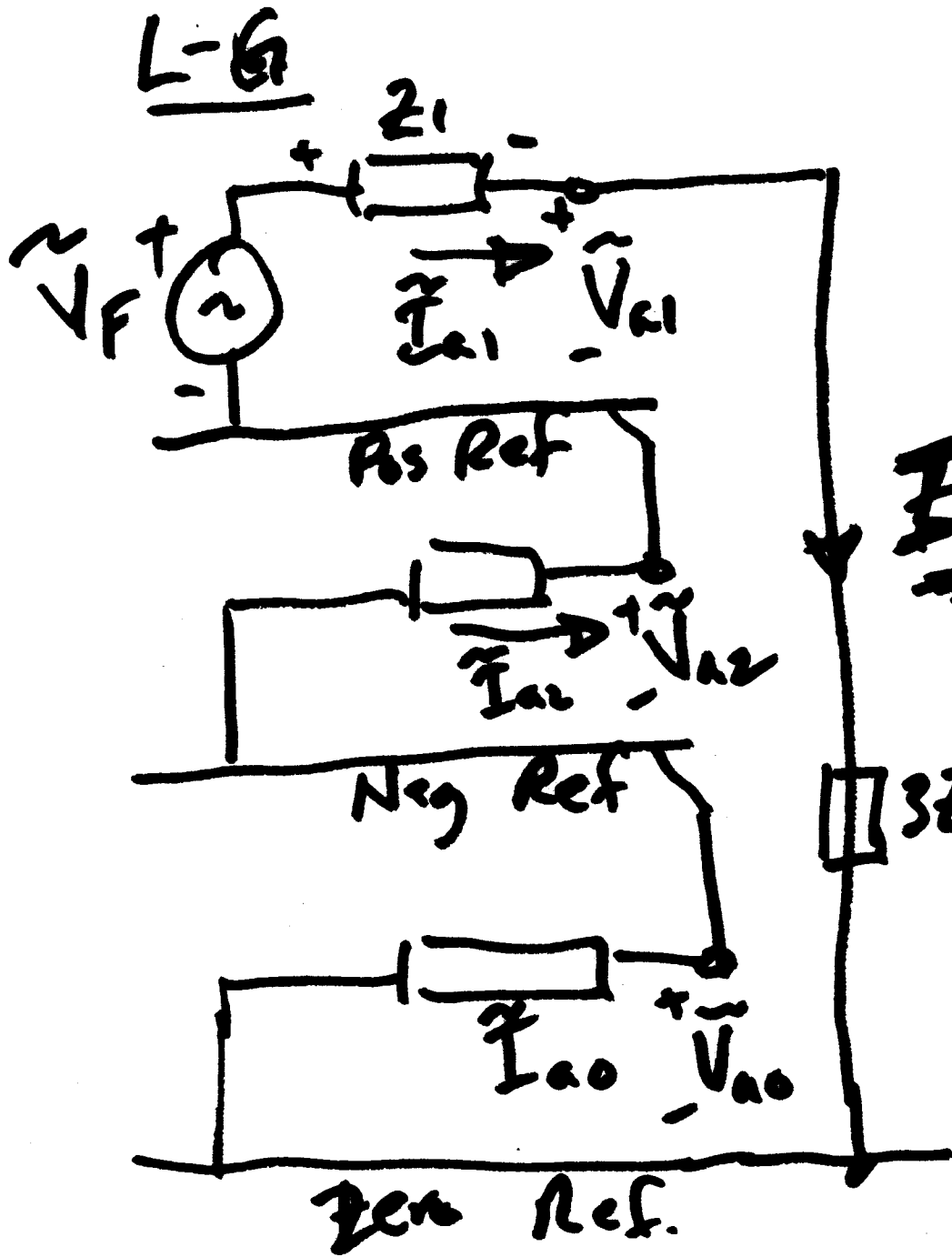


$$\tilde{I}_{a1} = \tilde{I}_{a2} = \tilde{I}_{a0}$$


$$\frac{\tilde{I}_F}{3} = \tilde{I}_{a1} = \tilde{I}_{a2} = \tilde{I}_{a0}$$

$$[3Z_f] [V_p] = [A] [V_s]$$

L-L-G

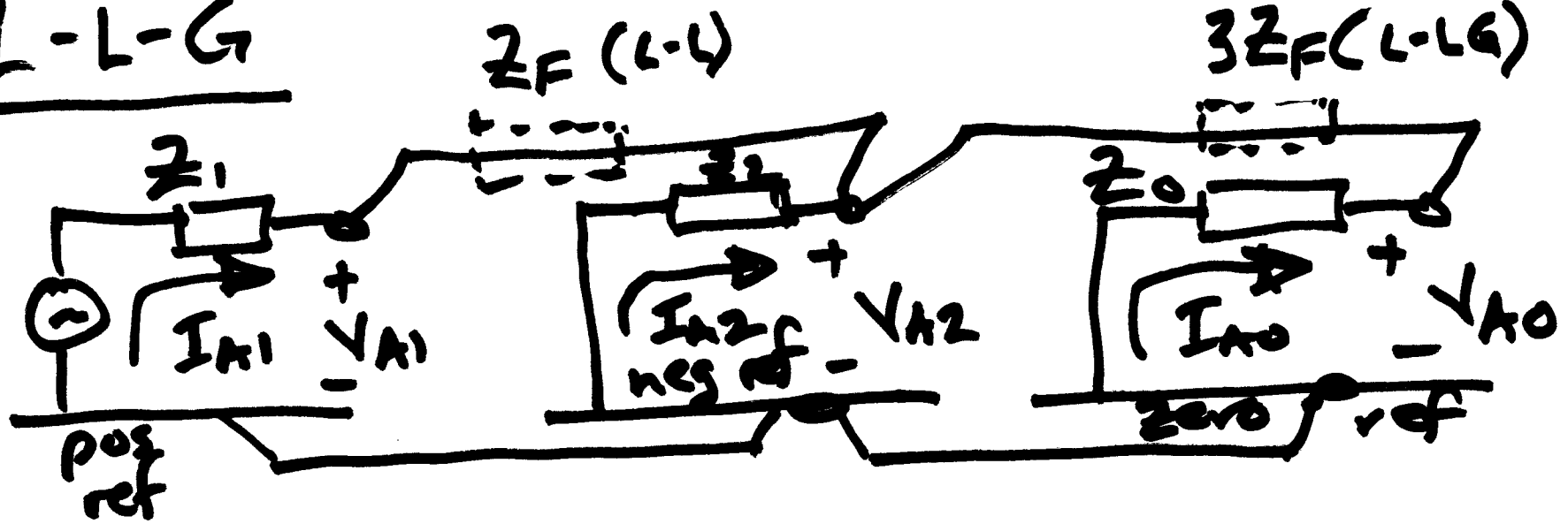

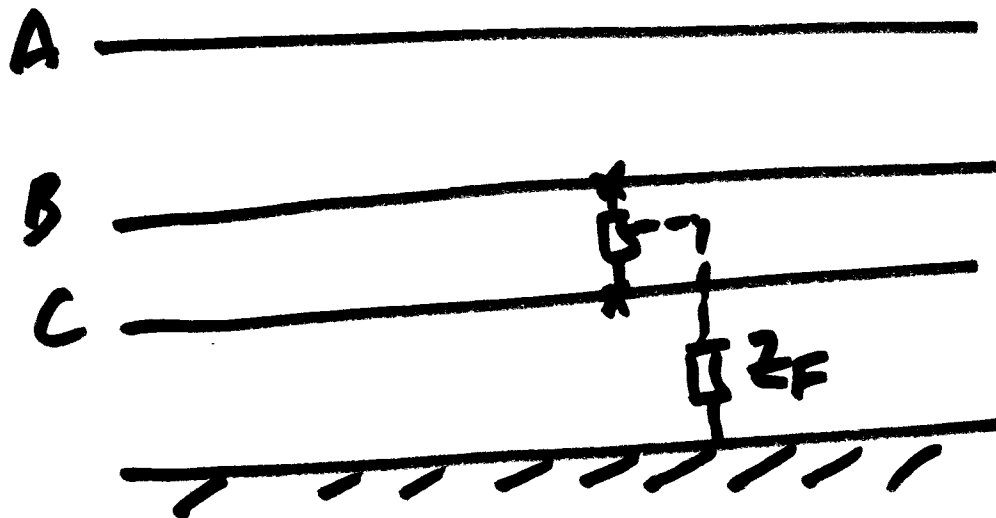L-L : Reduced case,  $Z_0 \approx \infty$





# Fault Impedance

$Z_F$ :

- LG

- LL

- LLG

- 3 $\phi$

Pos: Bus 1:  $V_{a1,1} = V_{a1,\text{fault}} + \tilde{I}_{1F}^{a1} \bar{Z}'_{L,1F}$

Bus 2:  $V_{a1,2} = V_{a1,\text{fault}} + \tilde{I}_{2F}^{a1} \bar{Z}'_{L,2F}$

---

NEG:

Bus 1  $\tilde{V}_{a2,1} = \tilde{V}_{a2,\text{fault}} + \tilde{I}_{a2,2F} \bar{Z}^2_{L,1F}$

Bus 2  $\tilde{V}_{a2,2} = \tilde{V}_{a2,\text{fault}} + \tilde{I}_{a2,2F} \bar{Z}^2_{L,2F}$

---

zero:

$\tilde{V}_{a0,1} = \tilde{V}_{a0,\text{fault}} + \tilde{I}_{a0,1F} \bar{Z}^0_{L,1F}$

$\tilde{V}_{a0,2} = \tilde{V}_{a0,\text{fault}} + \tilde{I}_{a0,2F} \bar{Z}^0_{L,2F}$



Then you'll have  $[I_s]$  &  $[V_s]$   
at each bus.

Then can "apply" relay.  
i.e. do settings.

Phase Qlys: 
$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = [A] \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix}$$

67 relays: Phase Qlys (i.e. A, B, C)

21 relays: Seq Qlys (i.e. pos, neg, zero)

$$\bar{Z}(\omega) = \frac{V(\omega)}{\tilde{I}(\omega)}$$

For Releys:

$$\bar{Z}_0 = \frac{\tilde{V}_{a0}}{\tilde{I}_{a0}}$$

$$\bar{Z}_1 = \frac{\tilde{V}_{a1}}{\tilde{I}_{a1}}$$

$$\bar{Z}_A = \frac{\tilde{V}_{AN}}{\tilde{I}_A}$$

Simplest case




If you use  $V_{LL}$

$$\bar{Z}_{AB} = \frac{\tilde{V}_{AB}}{\tilde{I}_{AB}} = \frac{\tilde{V}_A - \tilde{V}_B}{\tilde{I}_A - \tilde{I}_B}$$


"delta currents"



# 3-Winding XFMR

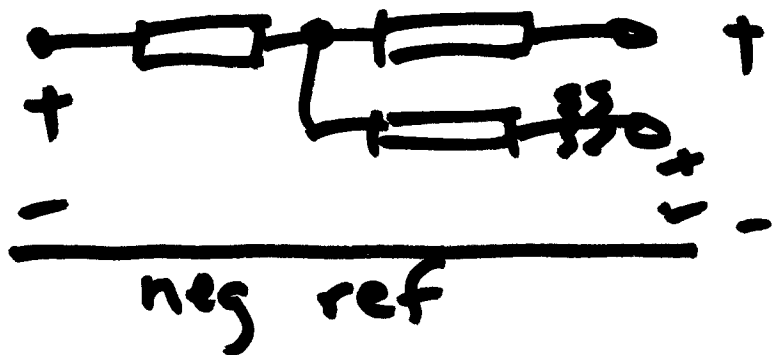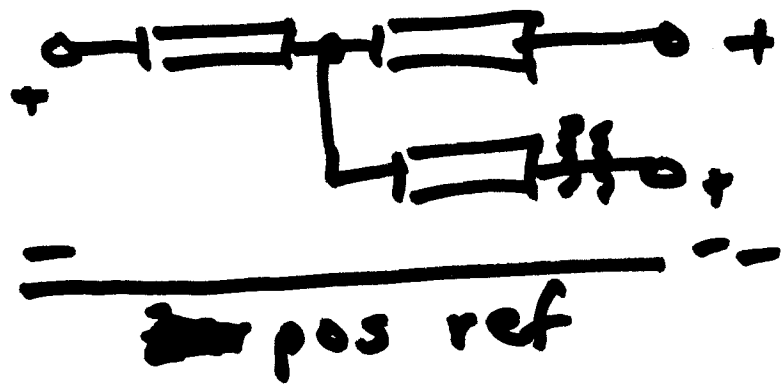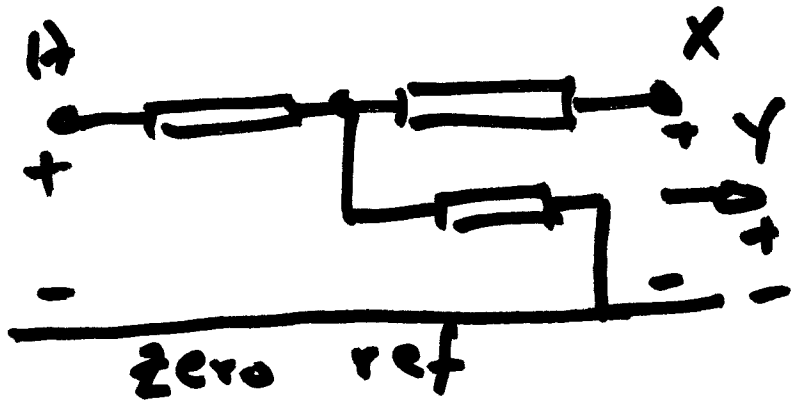

- Auto w/ $\Delta$  tert.

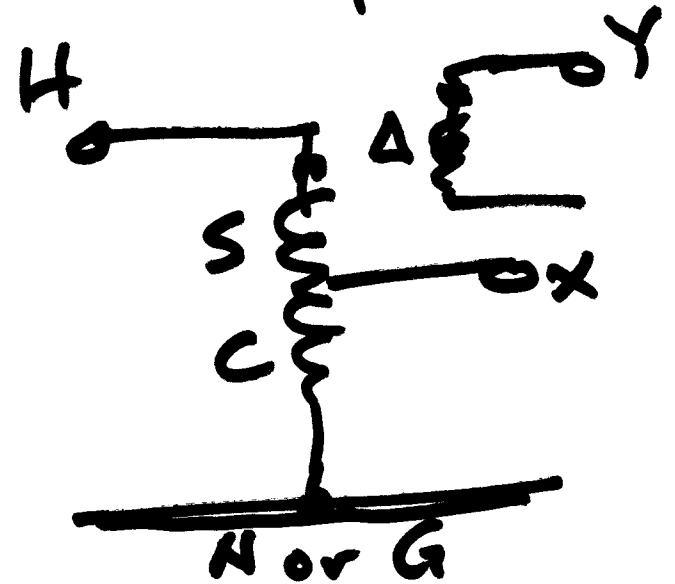

Key: External fault:  
It's enough to  
know line currents  
and voltages  
at the bushings.  
What about internal  
fault?

Also: How can we calculate  $I_{A0}$  in  
new or inside  $\Delta$  for ground  
polarization?

Thus: need to reconcile line  
currents into xfmr, with  
internal currents thru coils.

See last page of L21!


Objective: obtain CT currents  
of neutral and  $\Delta$  for  
ground polarization.



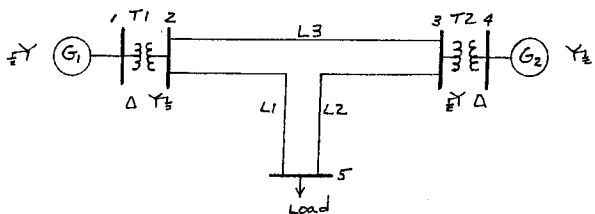1. In the 3-phase system below, the elements have the following values:

- G1: 250 MVA, 15.0 kV,  $X_0 = .05, X_1 = .25, X_2 = .20$
- G2: 500 MVA, 15.0 kV,  $X_0 = .05, X_1 = .25, X_2 = .20$
- T1: three single-phase units, high voltage side connected wye, low voltage side connected delta, Each unit is 15 kV:200 kV, 300 MVA, with a reactance of .10
- T2: A three-phase transformer, 345 kV wye:15 kV delta, 500 MVA, with a reactance of .10.
- L1:  $Z_0 = j40$  ohms/phase,  $Z_1 = Z_2 = j20$  ohms/phase
- L2:  $Z_0 = j20$  ohms/phase,  $Z_1 = Z_2 = j10$  ohms/phase
- L3:  $Z_0 = j30$  ohms/phase,  $Z_1 = Z_2 = j15$  ohms/phase

Choose a base of 345 kV, 1,000 MVA at the load and draw the per unit zero, positive, and negative impedance diagrams. Show all the impedance values on the diagrams. Assume all pre-fault bus voltages are 1.0 per unit. Neglect the load.




2. Construct the Thevenin equivalent zero, positive, and negative sequence networks for the system of problem 1 looking into the network at bus 3.
3. For a L-G fault with an impedance of  $j.1$  per unit on bus 3 in the problem above, find the a-b-c line currents flowing toward the fault:
  - A. Coming from line L2
  - B. Coming from generator G1
4. Repeat problem 3 for a solid L-L fault on bus 3
5. Repeat problem 3 for a solid 2L-G fault on bus 3

6. The 5-bus system shown below has the bus impedance matrices:

$$Z_0 = j \begin{bmatrix} 1.2847 & .02431 & .06597 & .10278 & .00000 \\ .02431 & .04514 & .03681 & .01944 & .00000 \\ .06597 & .03681 & .22847 & .05278 & .00000 \\ .10278 & .01944 & .05278 & .12222 & .00000 \\ .00000 & .00000 & .00000 & .00000 & .20000 \end{bmatrix}$$

$$Z_1 = j \begin{bmatrix} 1.3014 & .09589 & .10959 & .10411 & .07192 \\ .09589 & .12329 & .11233 & .07671 & .09247 \\ .10959 & .11233 & .17123 & .08767 & .08425 \\ .10411 & .07671 & .08767 & .12329 & .05753 \\ .07192 & .09247 & .08425 & .05753 & .10685 \end{bmatrix}$$
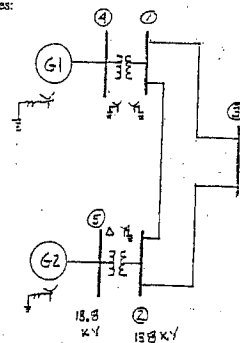
$$Z_2 = j \begin{bmatrix} 1.15517 & .12069 & .13448 & .12931 & .09655 \\ .12069 & .14943 & .13793 & .10057 & .11954 \\ .13448 & .13793 & .19655 & .11207 & .11034 \\ .12931 & .10057 & .11207 & .14943 & .08046 \\ .09655 & .11954 & .11034 & .08046 & .13563 \end{bmatrix}$$



Ignore pre-fault currents and assume a pre-fault voltage of 1.0. For a line-to-ground fault with an impedance of  $j.06792$  on bus 3, find the a-b-c per unit line currents:

- A. In the fault itself
  - B. From generator 2, which has:  $X_0 = .05, X_1 = .15, X_2 = .20, X_n = .05$
  - C. In line 1-3, which has:  $X_1 = X_2 = .15, X_0 = .45$
7. Repeat problem 6 for a line-to-line fault on bus 3 with an impedance of  $j.13222$
  8. Find the a-b-c fault current for a solid two-line-to-ground fault at bus 3 of the system of problem 6.

4) FINDING New Base Voltages:

$$V_{Base @ 2, 3, 5} = 345 \text{ kV}; \quad V_{Base @ 4} = \frac{15}{345} \cdot 1345 = 15 \text{ kV};$$

$$V_{Base @ 1} = \frac{15}{200\sqrt{3}} \cdot (345) = \left(\frac{15}{346.41}\right) \cdot (345) = 14.93894 \text{ kV}$$

FINDING Per Unit Values on new 1,000 MVA base.

$$G1: X_0 = .05 \left(\frac{15}{14.93894}\right)^2 \left(\frac{1000}{250}\right) = .20164; \quad X_1 = .25 \left(\frac{15}{14.93894}\right)^2 \left(\frac{1000}{250}\right) = 1.00819; \quad X_2 = .20 \left(\frac{15}{14.93894}\right)^2 \left(\frac{1000}{250}\right) = .80655$$





$$T1: X = .10 \left(\frac{15}{14.93894}\right)^2 \left(\frac{1000}{900}\right) = .11202; \quad L1: X_0 = \frac{40}{1000 \cdot 10^6} = .04; \quad X_1 = X_2 = \frac{20}{1000 \cdot 10^6} = .02$$

$$L1: X_1 = X_2 = \frac{1}{2} X_0 = .16803; \quad L2: X_0 = X_1 = X_2 = .16803; \quad X_1 = X_2 = \frac{1}{2} X_0 = .08402$$

$$L3: X_0 = \frac{30}{(345 \times 10^3)^2} = .25205; \quad X_1 = X_2 = \frac{15}{(345)^2} = .12602$$

$$T2: X = .10 \left(\frac{1000}{500}\right) = .20$$
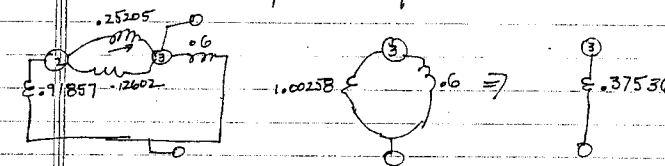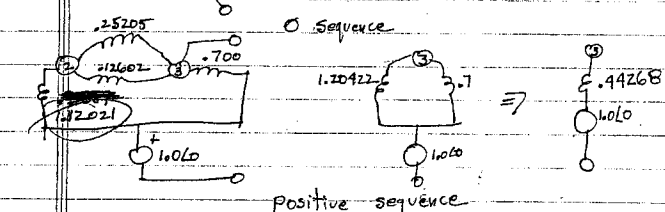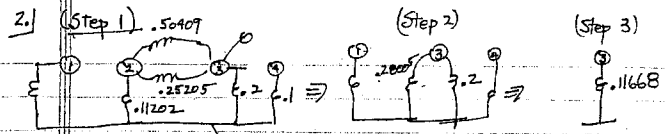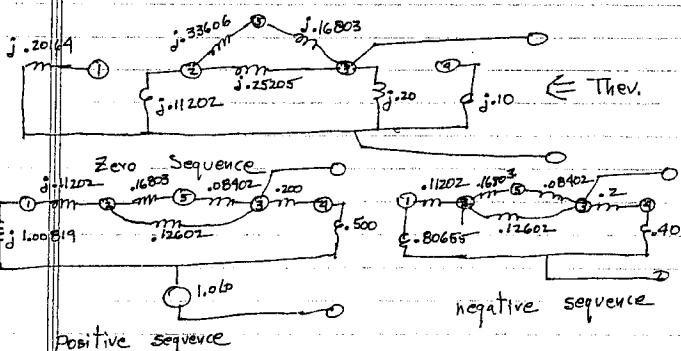
$$G2: X_0 = .05 \left(\frac{15}{15}\right)^2 \left(\frac{1000}{500}\right) = .10; \quad X_1 = 5 X_0 = .50; \quad X_2 = 4 X_0 = .40$$



$$I_0 = I_1 = I_2$$

$$E_{j=0} = j.11668 V_0$$

$$E_{j=1} = j.44268 V_1$$

$$E_{j=2} = j.37536 V_2$$

$$I_1 = \frac{1.06}{j(1.11668 + .44268 + .37536 + j.3)} = .80990 \angle -90$$

From bus 2 (Gen 1 pos & neg)

$$I_0 = \left(\frac{-2}{.28008 + j.2}\right) \cdot (.80990 \angle -90) = .33778 \angle -90$$

$$I_1 = \left(\frac{-7}{-.7 + j1.20422}\right) \cdot (.80990 \angle -90) = .29778 \angle -90$$

$$I_2 = \left(\frac{-6}{.6 + j1.00258}\right) \cdot (.80990 \angle -90) = .30328 \angle -90$$

From Line 2:

(3)


$$I_0 = \left( \frac{0.25205}{0.25205 + 0.50409} \right) \cdot 3374 \angle -90 = 1124 \angle -90$$

$$I_1 = \left( \frac{0.12602}{0.12602 + 0.25205} \right) \cdot 2977 \angle -90 = 0992 \angle -90$$

$$I_2 = \left( \frac{0.12602}{0.12602 + 0.25205} \right) \cdot (3032 \angle -90) = 1010 \angle -90$$

$$I_{a,b,c} = [A] \begin{bmatrix} 1124 \angle -90 \\ 0992 \angle -90 \\ 1010 \angle -90 \end{bmatrix} = \begin{bmatrix} 312 \angle -90 \\ 01242 \angle -82.667 \\ 01242 \angle -97.333 \end{bmatrix}$$
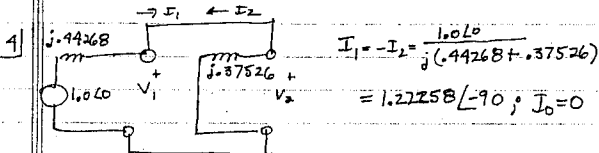
$$I_{a,b,c} = [A] \begin{bmatrix} 0 \\ 2977 \angle -120 \\ 3032 \angle -60 \end{bmatrix} = \begin{bmatrix} 52044 \angle -89.697 \\ 52044 \angle 86.697 \\ 00550 \angle 180.00 \end{bmatrix}$$



$$I_1 = -I_2 = \frac{1.0 \angle 0}{j(0.44268 + 0.37526)} = 1.22258 \angle -90; I_0 = 0$$

$$\text{From 8 vs 2: } I_1 = \left( \frac{0.7}{0.7 + 1.70422} \right) (1.22258 \angle -90) = 0.44943 \angle -90$$

$$I_2 = \left( \frac{0.6}{0.6 + 1.00258} \right) (1.22258 \angle -90) = 0.45773 \angle -90$$


$$\text{From Line 2: } I_1 = \left( \frac{0.12602}{0.12602 + 0.25205} \right) \cdot 44943 \angle -90 = 14981 \angle -90$$

$$I_2 = \left( \frac{0.12602}{0.12602 + 0.25205} \right) \cdot (45773 \angle -90) = 15257 \angle -90$$

$$I_{a,b,c} = [A] \begin{bmatrix} 0 \\ 14981 \angle -90 \\ 15257 \angle -90 \end{bmatrix} = \begin{bmatrix} 00274 \angle 90 \\ 26187 \angle 179.70 \\ 26187 \angle -30 \end{bmatrix}$$

$$I_{a,b,c} = [A] \begin{bmatrix} 0 \\ 44943 \angle -120 \\ 45773 \angle 120 \end{bmatrix} = \begin{bmatrix} 45364 \angle 179.09 \\ 45364 \angle -179.09 \\ 90716 \angle 0 \end{bmatrix}$$

5)

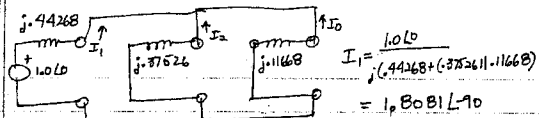

$$I_1 = \frac{1.0 \angle 0}{j(0.44268 + 0.37526 + 0.11668)} = 1.8081 \angle -90$$

$$I_{a,b,c} = [A] \begin{bmatrix} 1.43471 \angle 90 \\ 1.808081 \angle 90 \\ 0.44610 \angle 90 \end{bmatrix} = \begin{bmatrix} 0 \\ 2.94826 \angle 133.118 \\ -2.94826 \angle 46.882 \end{bmatrix}$$

6)

$$I_{F(0)} = I_{F(1)} = I_{F(2)} = \frac{1.0 \angle 0}{j(0.22847 + 0.17123 + 0.19655 + 3(0.06792))} = 1.25 \angle -90$$

$$I_{A,B,C} = [A] \begin{bmatrix} 1.25 \angle -90 \\ 1.25 \angle -90 \\ 1.25 \angle -90 \end{bmatrix} = \begin{bmatrix} 3.75 \angle -90 \\ 0 \\ 0 \end{bmatrix}$$

$$B) V_5(0) = 0; V_5(1) = 1.0 - (1.25 \angle -90)(0.8425 \angle 90) = 0.8469; V_5(2) = (1.25 \angle -90)(1.1084 \angle 90) = -0.13795$$

$$I_{g(0)} = 0; I_{g(1)} = \frac{1 - 0.8469}{0.15 \angle 90} = 7.0208 \angle -90; I_{g(2)} = \frac{0 - (-0.13795)}{0.15 \angle 90} = 0.68763 \angle -90$$

$$I_{a,b,c} g_a = [A] \begin{bmatrix} 0 \\ 7.0208 \angle -120 \\ 0.68763 \angle -60 \end{bmatrix} = \begin{bmatrix} 1.2053 \angle -90.296 \\ 1.2053 \angle 90.296 \\ 0.1245 \angle 0 \end{bmatrix}$$


$$C) I_{A(0)} = \frac{V_{1(0)} - V_5(0)}{Z_{line(0)}} = \frac{1.25 \angle -90(0.22847 \angle 90 - 0.68763 \angle 90)}{0.45 \angle 90} = 0.45139 \angle -90$$

$$I_{A(1)} = \frac{V_{1(1)} - V_5(1)}{Z_{line(1)}} = \frac{(1.7123 \angle 90 - 1.0959 \angle 90)(1.25 \angle -90)}{0.15 \angle 90} = 5.1367 \angle -90$$

$$I_{A(2)} = \frac{V_{1(2)} - V_5(2)}{Z_{line(2)}} = \frac{(1.9655 \angle 90 - 1.3448 \angle 90)(1.25 \angle -90)}{0.15 \angle 90} = 5.1725 \angle -90$$

$$I_{a,b,c} = [A] \begin{bmatrix} 0.45139 \angle -90 \\ 5.1367 \angle -90 \\ 5.1725 \angle -90 \end{bmatrix} = \begin{bmatrix} 1.48231 \angle -90 \\ 0.6919 \angle 87.2296 \\ 0.6919 \angle 72.7704 \end{bmatrix}$$

7)

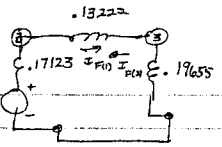

$$I_{F(0)} = -I_{F(2)} = \frac{1.0}{j(0.17123 + 0.13222 + 0.19655)} = 2 \angle -90$$

$$I_{a,b,c} \text{ fault} = [A] \begin{bmatrix} 0 \\ 2 \angle -90 \\ 2 \angle 90 \end{bmatrix} = \begin{bmatrix} 3.4641 \angle 180 \\ 3.4641 \angle 0 \end{bmatrix}$$

$$I_{g_2(0)} = \frac{+0.08425 \angle 90(2 \angle -90)}{0.15 \angle 90} = 1.12333 \angle -90$$


$$I_{g_2(2)} = \frac{(+0.11034 \angle 90)(2 \angle 90)}{0.20 \angle 90} = 1.10340 \angle 90$$

$$I_{1-3(0)} = \frac{2 \angle -90(0.17123 \angle 90 - 0.10959 \angle 90)}{0.15 \angle 90} = 0.82187 \angle -90$$

$$I_{1-3(2)} = \frac{2 \angle 90(0.19655 \angle 90 - 0.13448 \angle 90)}{0.15 \angle 90} = 0.82760 \angle 90$$

$$I_{A,B,C} = [A] \begin{bmatrix} 0 \\ 0.82187 \angle -90 \\ 0.82760 \angle 90 \end{bmatrix} = \begin{bmatrix} 0.00573 \angle 90 \\ 1.42849 \angle -179.815 \\ 1.42849 \angle -115 \end{bmatrix}$$

8)

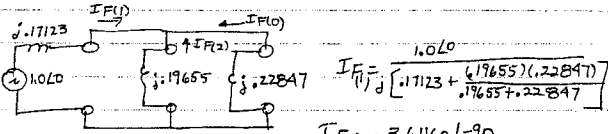

$$I_{F(1)} = \frac{1.0 \angle 0}{j[0.17123 + 0.19655 + 0.22847]} = 3.61160 \angle -90$$

$$I_{F(2)} = -I_{F(1)} \left( \frac{0.22847}{0.22847 + 0.19655} \right) = 1.94142 \angle 90$$

$$I_{F(0)} = -(I_{F(1)} + I_{F(2)}) = 1.67018 \angle 90$$

$$I_{a,b,c} \text{ fault} = [A] \begin{bmatrix} 1.67018 \angle 90 \\ 3.61160 \angle -90 \\ 1.94142 \angle 90 \end{bmatrix} = \begin{bmatrix} 0 \\ 5.42249 \angle 152.48 \\ 5.42249 \angle 27.52 \end{bmatrix}$$