

EE 5223 - Lecture 29


Ongoing List of Topics:


- URL: https://pages.mtu.edu/~bamork/EE5223/index.htm
- Term Project Detailed outlines submitted, can resubmit after feedback.
 - Follow timeline, see posting on web page (posted in Week 5)
 - Formal outline w/complete references complete, get/keep cranking...
- Homework set 10 can be divided into two parts/efforts
 - Handout problem, Probs 4.2, 4.3 (a,b,c) Complete by Tues 9am
 - Problem 4.4 complete by Wed 9am (if help is needed).
- Protection fundamentals for 87T, ongoing
- Transformer protection/maintenance issues
 - Load Tap Changer Voltage Reg
 - "Doble Test," Dissolved Gas in Oil
 - a) correct connection of CT secondaries to relays (Lectures 28,29)
 - b) relay settings, to compensate for pri voltage ratio and CT ratios.
 - c) Mismatch problems due to being forced to use less than full CT ratio, having Pri and Sec CTs with different accuracy levels, LTC. Differential slope of trip characteristic can be 10%, 15%, 25%, etc, to allow for mismatch. Refer to XFMR.pdf!

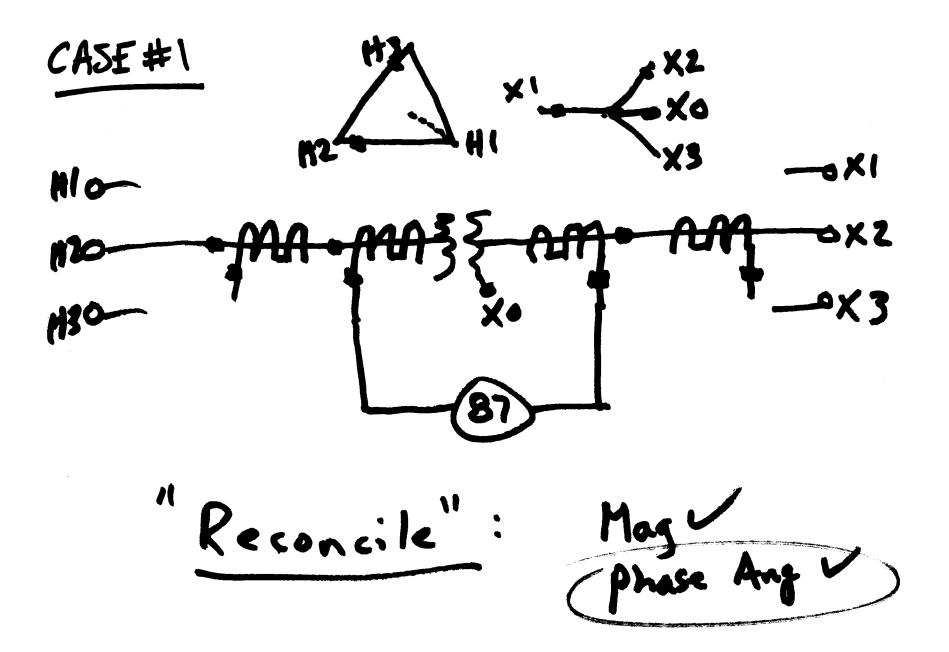

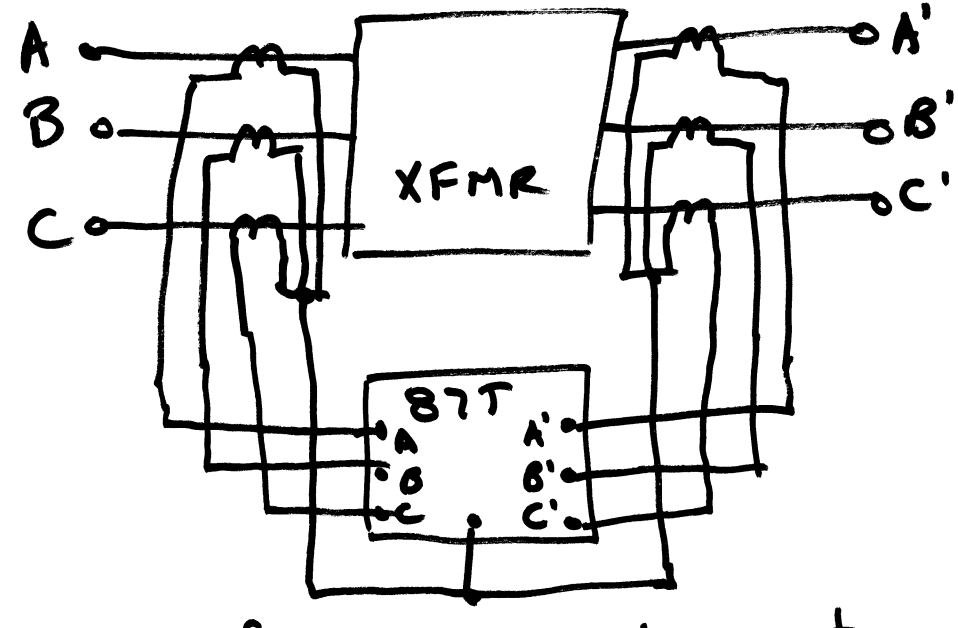


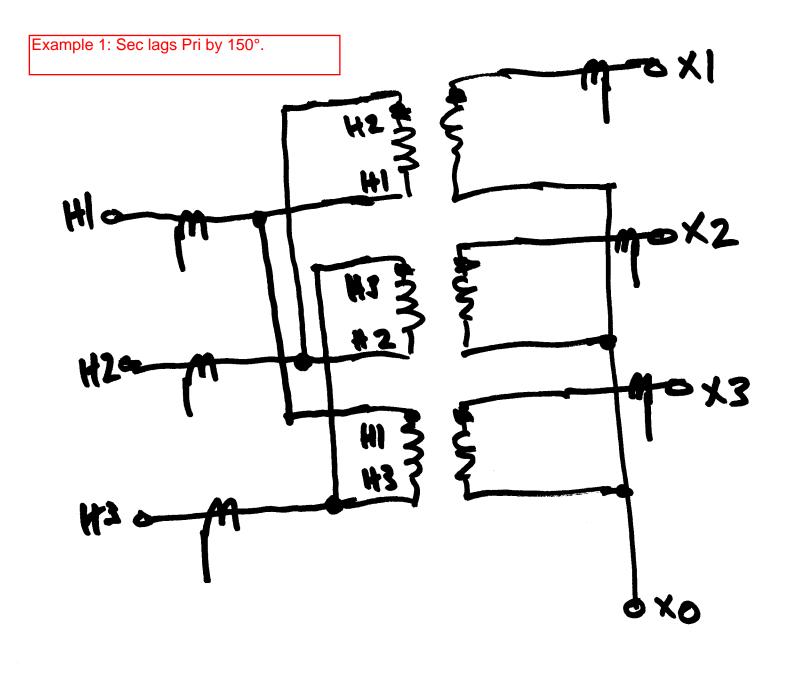Ideally: for 63 reby, just connect line currents & provide settings




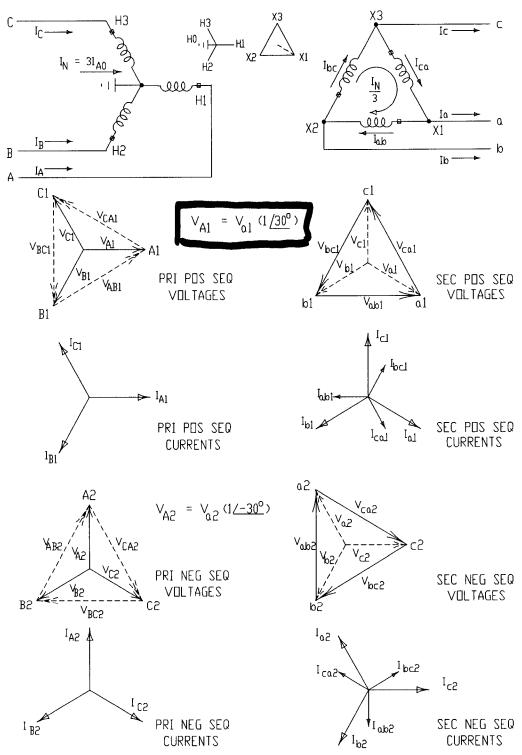


ANSI STANDARD 30-DEGREE SHIFT WYE-DELTA

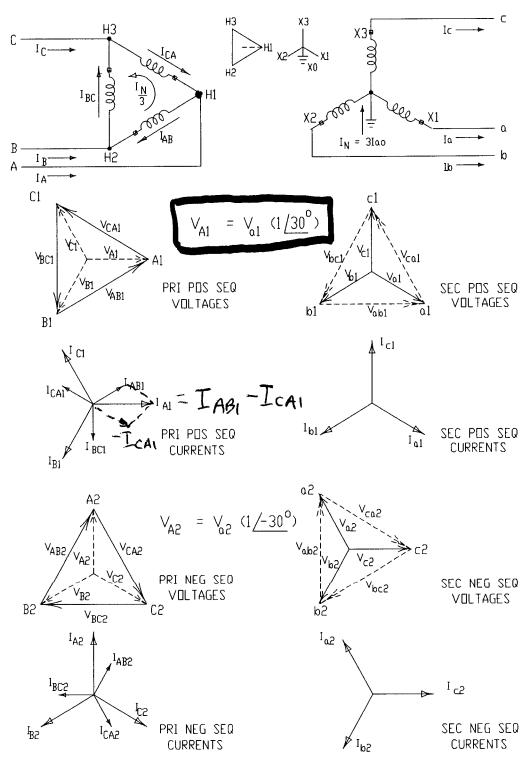



ANSI STANDARD 30-DEGREE SHIFT DELTA-WYE

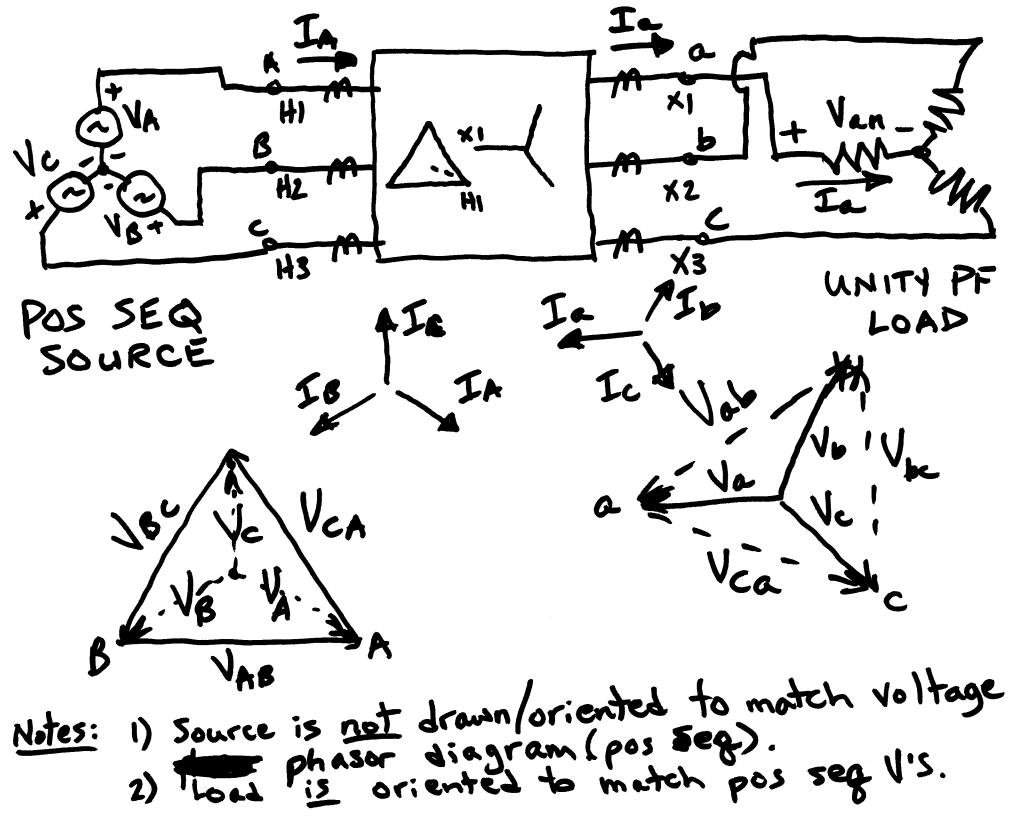


POWER CONN (LINE CHERENTS)

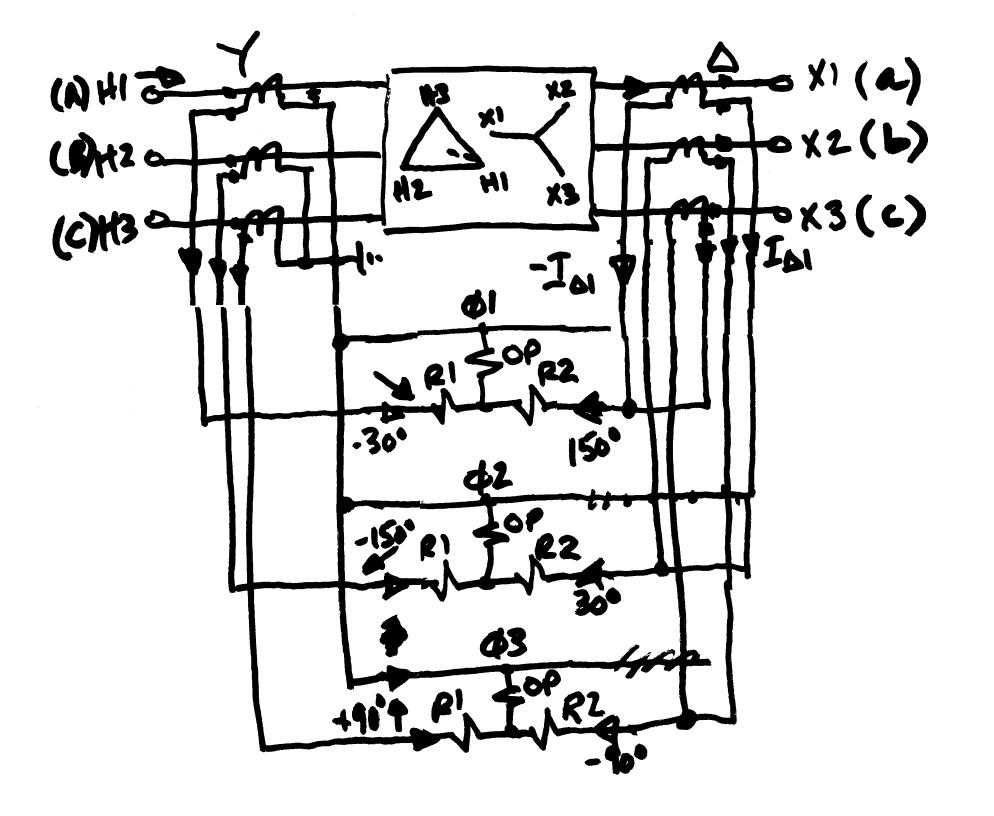


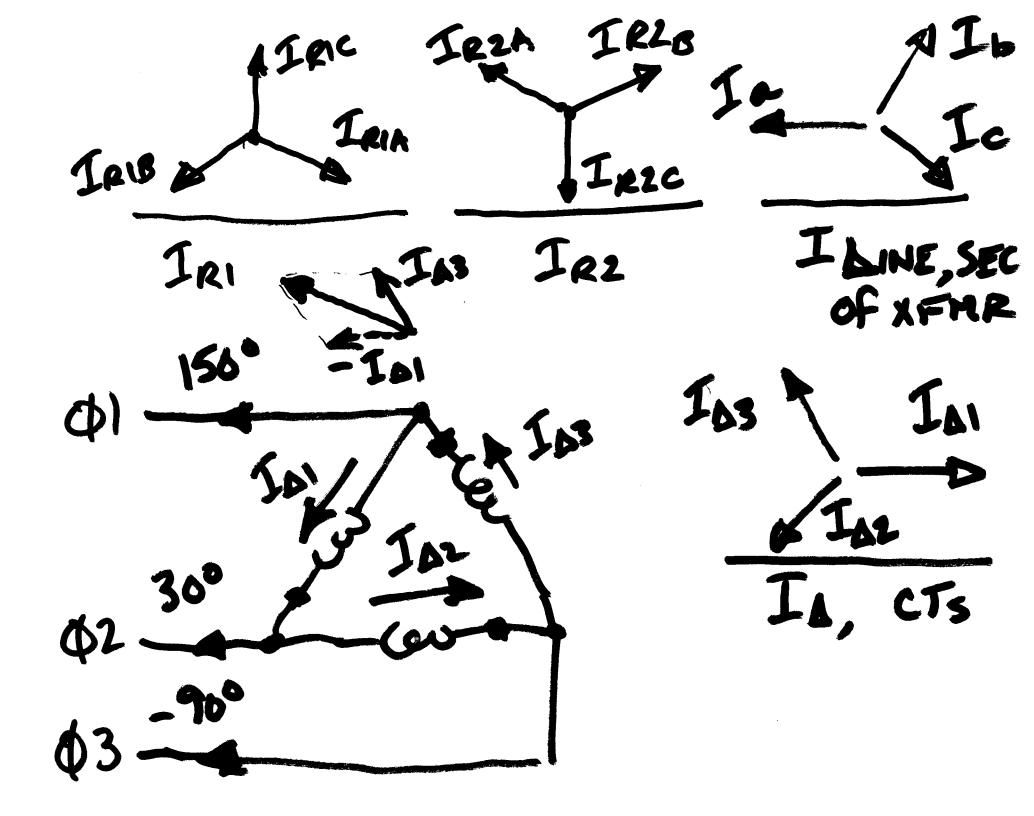


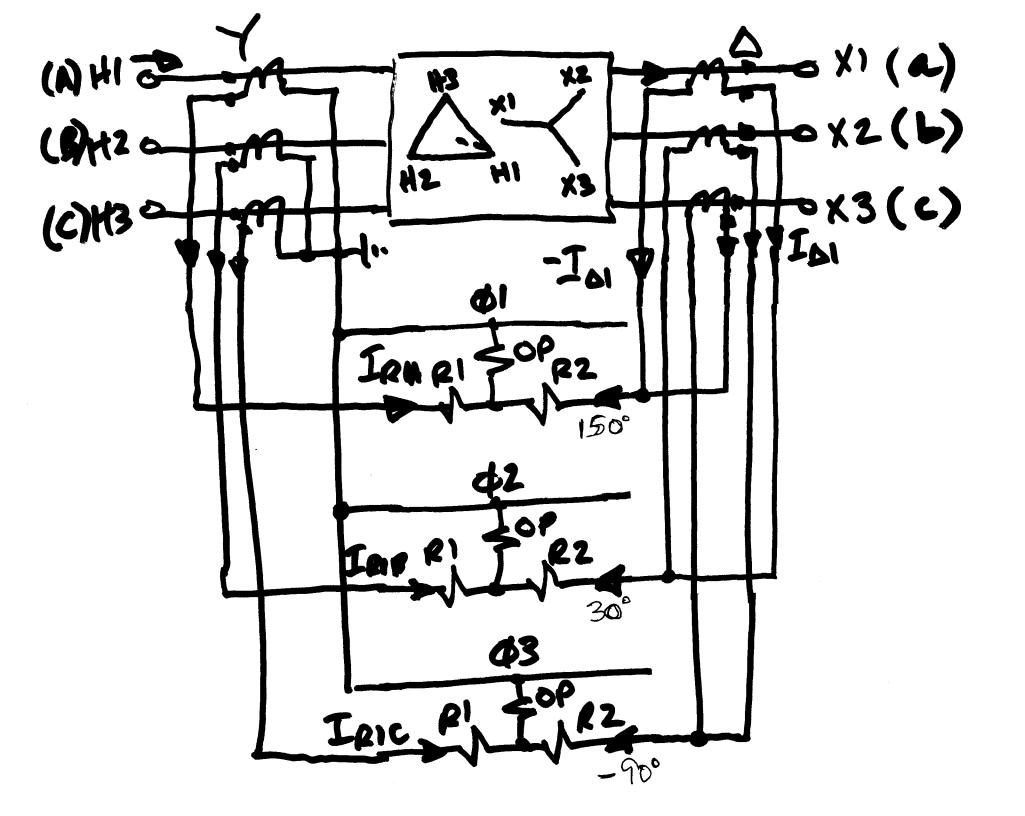


H3(c) H1(h) H2(B) X2(b) X3(c) X(a) X1(a)

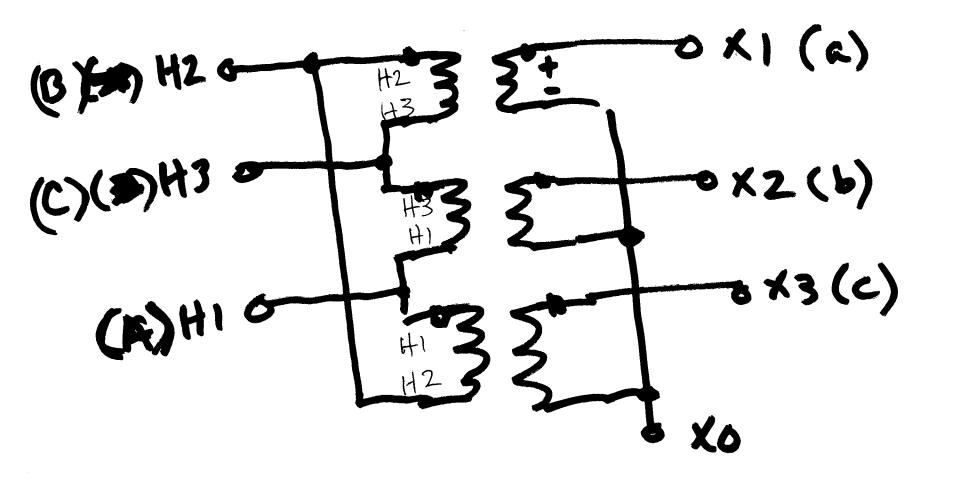


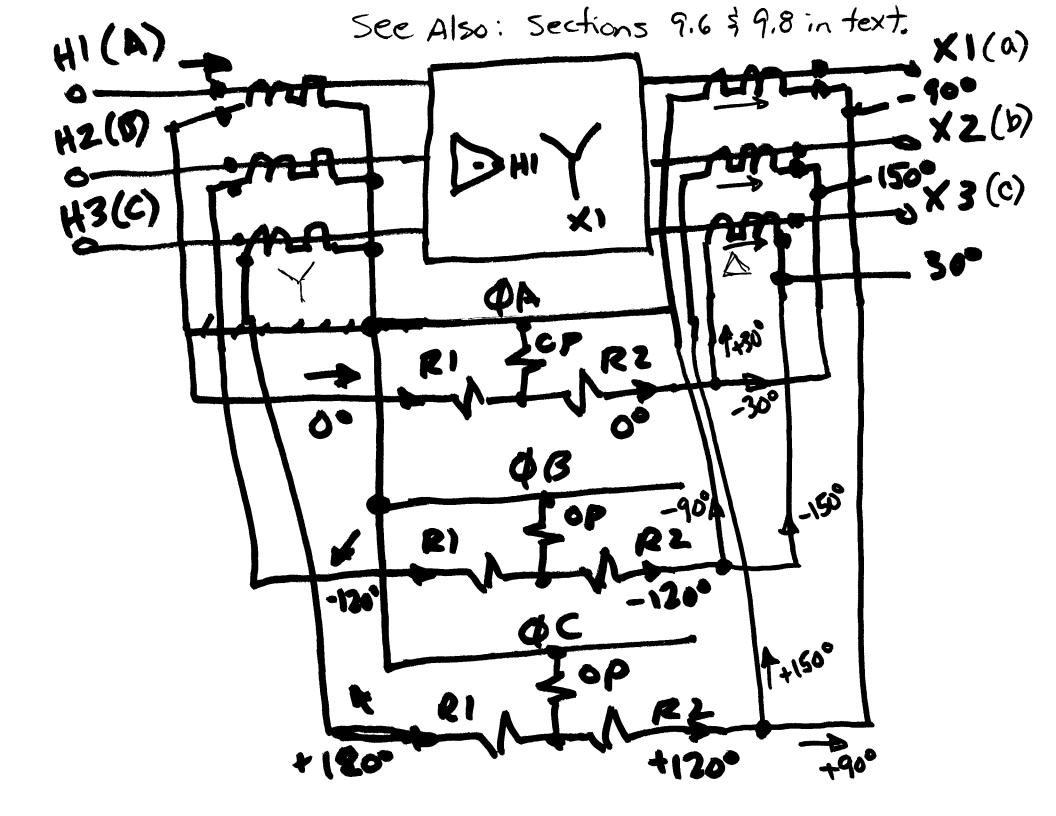

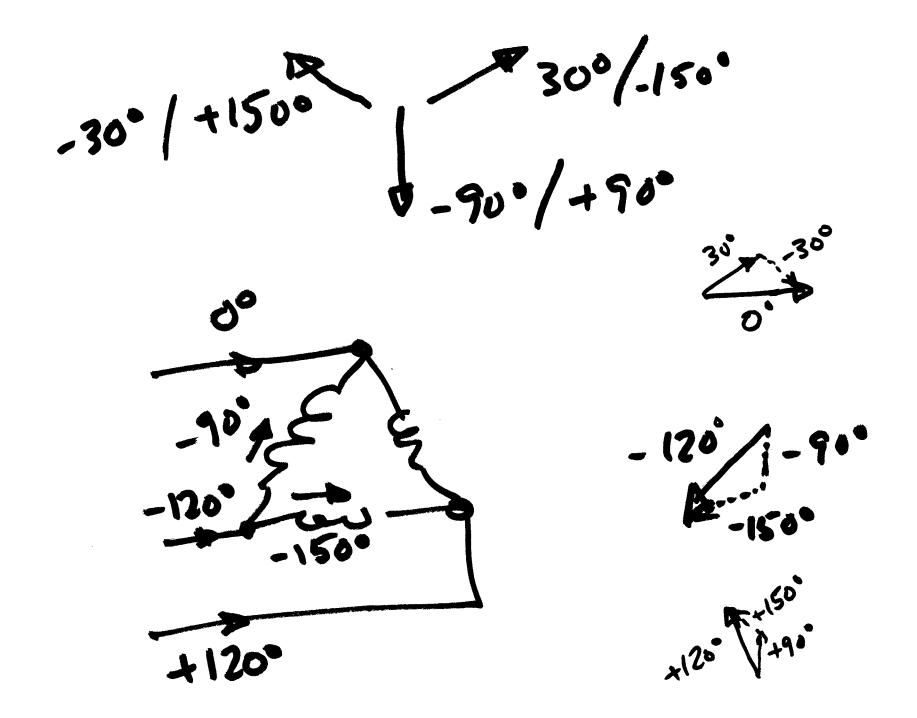

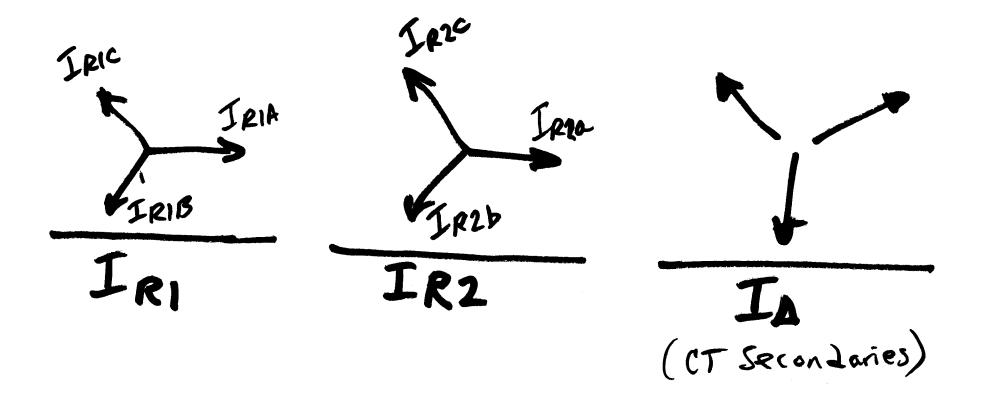

Another way to do "book keeping"

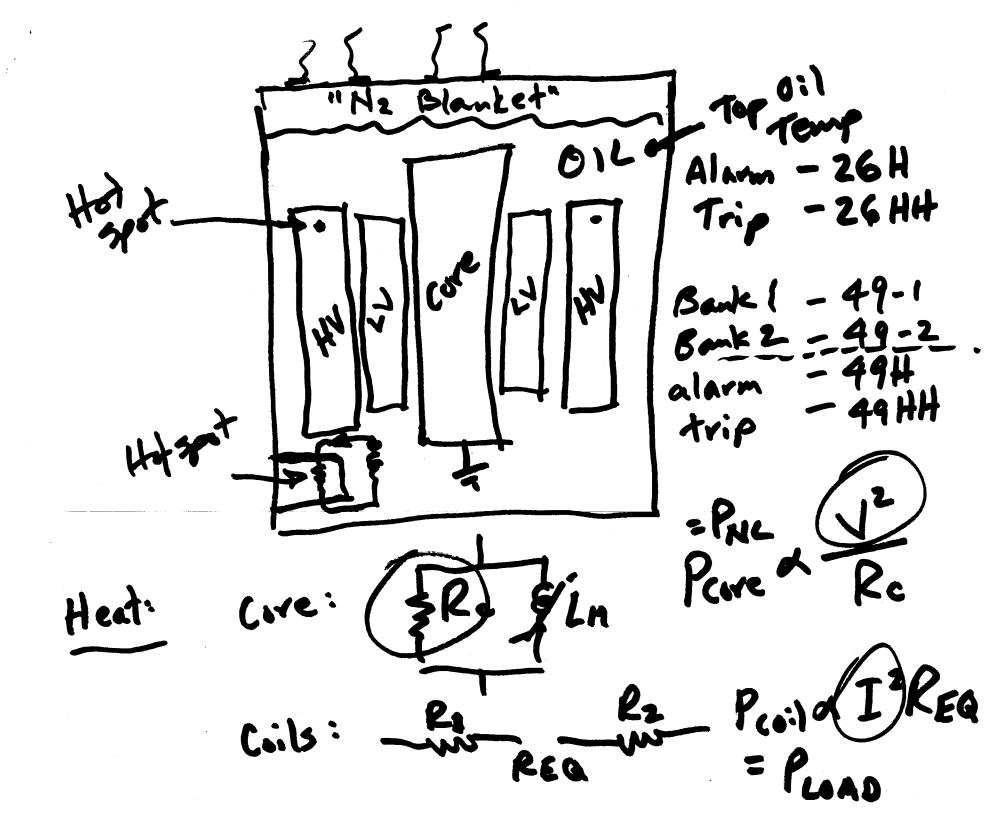

Phi 3/1 1/2 R2

.....