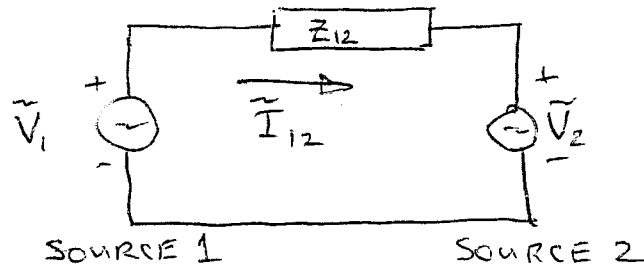


EE 5223 - Homework #3A - Due latest Tues Feb 7, 2023, 9am

(Form team of 3, a least one BSEE and one MSEE student per team!)

H1.1) For the following circuit, $v_1(t) = 120 \cos(\omega t + 0^\circ)$, $v_2(t) = 120 \sin(\omega t + 60^\circ)$ and $Z_{12} = 0.5 + j0.5\Omega$.

- Convert $v_1(t)$ and $v_2(t)$ to their phasor equivalents \tilde{V}_1 and \tilde{V}_2 . According to the "sign convention" used to label the current and sources, classify the two sources as "active" or "passive."
- Calculate \tilde{I}_{12} .
- Calculate the complex power \mathbf{S} consumed by source 2.
- Calculate the complex power \mathbf{S} produced by source 1.
- In terms of generator or load, what are sources 1 & 2? Was the correct guess made in labeling current direction?
- What is the power factor of source 2?





- H1.2) A 3-phase 480-Volt circuit has a positive-sequence Y-connected source and supplies a delta-connected load. The impedance of the lines between the source and load is negligible. The angle of V_{AB} is 0° and the phase impedance of the load is $20 - j8$ Ohms.
- Draw the circuit. Label the value of the phase voltages at the source. Label nodes A, B, and C.
Label the line currents I_A , I_B , and I_C . Label the L-L voltages at the load: V_{AB} , V_{BC} , and V_{CA} .
Label the phase currents at the load: I_{AB} , I_{BC} , and I_{CA} .
 - Determine the phasor values of the L-L voltages at the load. Draw the closed voltage phasor diagram for the system, showing all L-L and L-N voltages.
 - Determine the phasor value of the line currents.
 - Determine the phasor value of the phase currents in the source and the load.
 - Calculate the complex power S that is consumed by the load and draw the power triangle.
 - What is the power factor of the load?

H1.3) A 3-phase 480-Volt circuit has a positive-sequence Y-connected source and supplies a delta-connected load. The impedance of the lines between the source and load is $1/85^\circ$ Ohms. The angle of V_{AB} is 0° and the phase impedance of the load is $30/40^\circ$ Ohms.

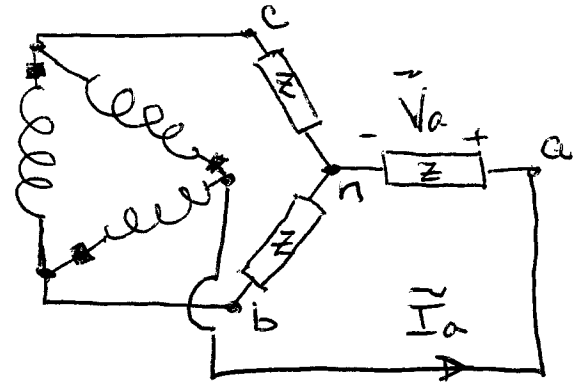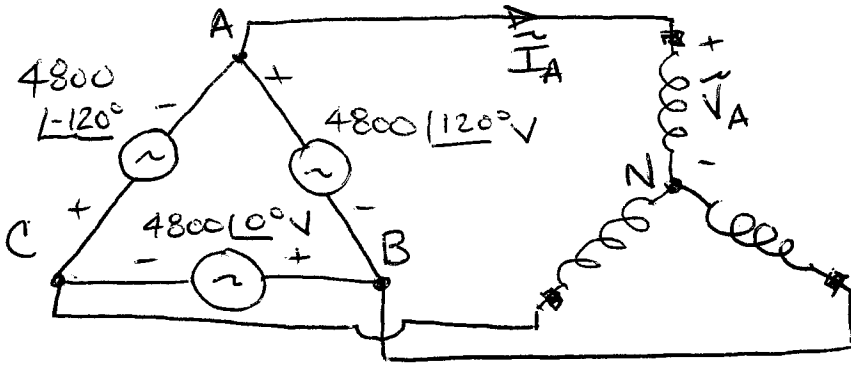- a) Draw the circuit. Label the value of the phase voltages at the source. Label nodes A, B, and C at source and A', B', and C' at load.
Label the line currents I_A , I_B , and I_C . Label L-L voltages at the load: V'_{AB} , V'_{BC} , and V'_{CA} .
Label the phase currents at the load: I_{AB} , I_{BC} , and I_{CA} .
- b) Convert the load to an equivalent Y-connected impedance and combine with the line impedances.
- c) Determine the phasor values of the L-L voltages at the source. Draw the closed voltage phasor diagram for the system, showing all L-L and L-N voltages.
- d) Using an A-N per phase equivalent, determine the phasor values of the line currents.
- e) Determine the L-N and L-L voltages at the terminals of the delta load.
- f) Determine the phasor value of the phase currents in the source and the load.
- g) Calculate the complex power S that is consumed by the load and draw the power triangle.
- h) What is the power factor of the load?

H1.4

A balanced 3 ϕ Δ -connected 4800V source supplies a balanced 208V Y-connected load through a Y- Δ transformer. $Z = 4 - j2\Omega$ in each phase of the load.



a) Determine the following voltage and current magnitudes:

$$V_{LL,PRI} = \underline{\hspace{2cm}} \quad V_{LN,PRI} = \underline{\hspace{2cm}} \quad V_{LL,SEC} = \underline{\hspace{2cm}} \quad V_{LN,SEC} = \underline{\hspace{2cm}}$$

$$I_{PH,SRC} = \underline{\hspace{2cm}} \quad I_{PH,PRI} = \underline{\hspace{2cm}} \quad I_{PH,SEC} = \underline{\hspace{2cm}} \quad I_{PH,LOAD} = \underline{\hspace{2cm}}$$


b) Draw closed phasor diagrams of the primary and secondary voltages, orienting all phasors to the nearest 30° angle. Label all phasors (i.e. V_A , V_{AB} , V_a , V_{bc} , etc.)

PRIMARY VOLTAGES

SECONDARY VOLTAGES

c) Find the phasor values of the following: V_a , I_a , V_A , and I_A .

H1.5

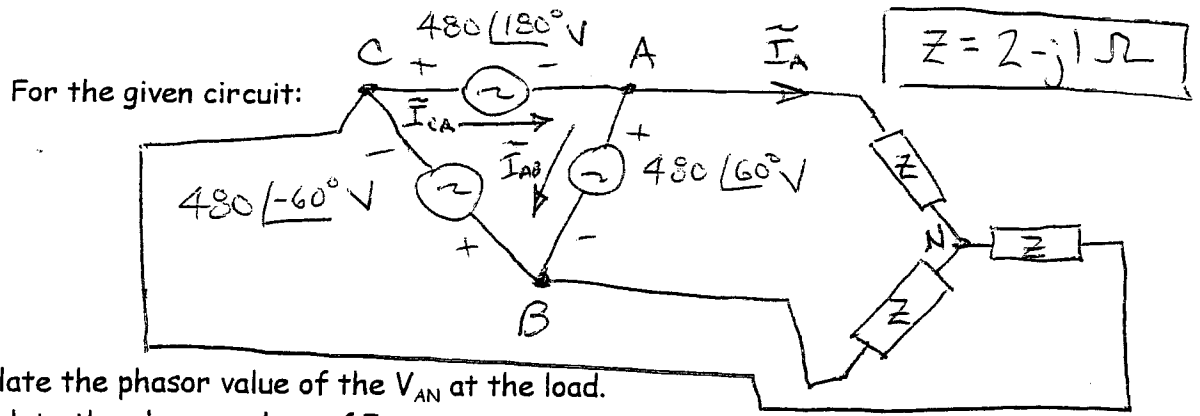

- Calculate the phasor value of the V_{AN} at the load.
- Calculate the phasor values of I_A .
- Calculate the phasor values of I_{AB} and I_{CA} .

H2.1) A single-phase autotransformer has an input voltage of 1380 Volts and supplies a 277-Volt 15-kW load of PF = 0.8 lag. Assuming that the voltage at the load has a reference angle of zero degrees,

- a) Draw the complete circuit, including source, transformer, and load. Label all voltages and currents. Show polarity markings on the transformer windings.
- b) Determine the phasor value of the current flowing into the load.
- c) Determine the phasor value of the currents in the 2 windings of the autotransformer, and specify the required voltage and current ratings for each of the windings.
- d) What is that phase angle of the source voltage?
- e) Calculate the volt-amp advantage of this particular transformer.
- f) Explain what the volt-amp advantage is, by contrasting the performance and cost of this autotransformer with an equivalent 2-winding transformer.