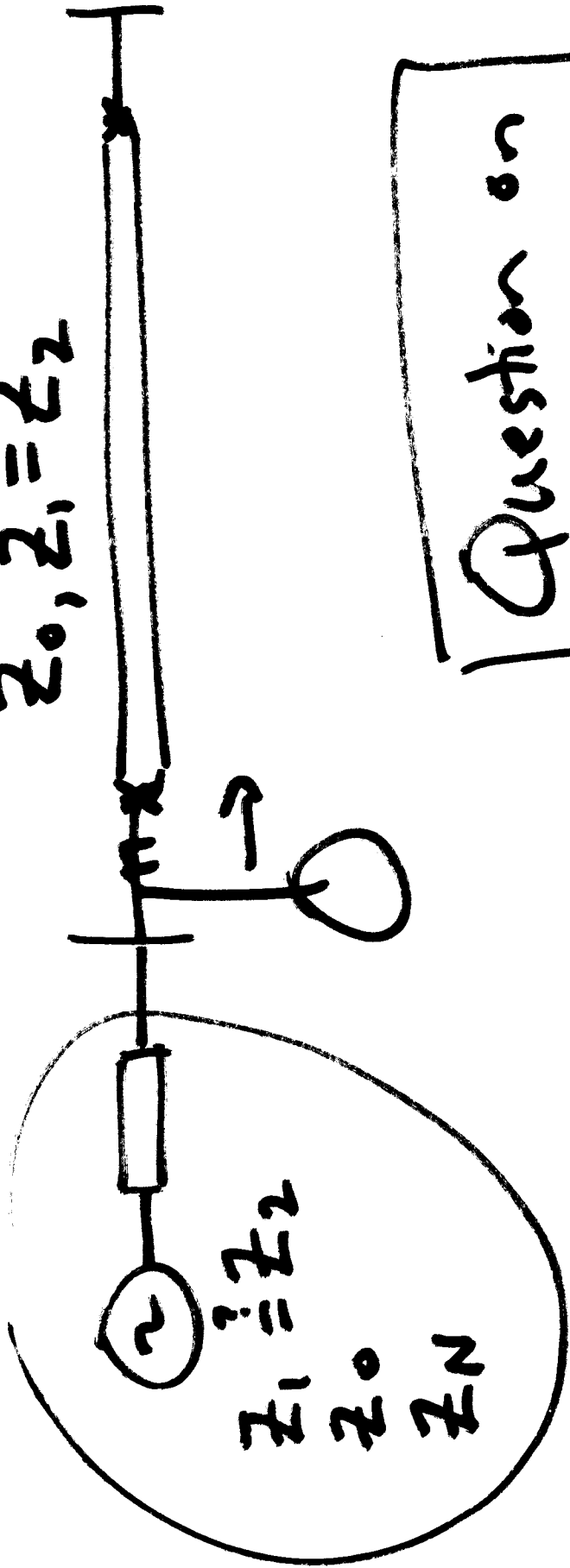


EE4223/5223

OFFICE HR 25 FEB '09

$Z_0, Z_1 = Z_2$



Question on
HWK 8



Symmetrical Components

9

- Deal w/ unbalanced 3 ϕ situations.

- Real-world situation: 'unbalanced

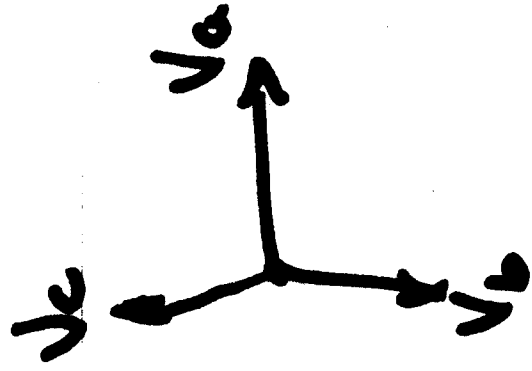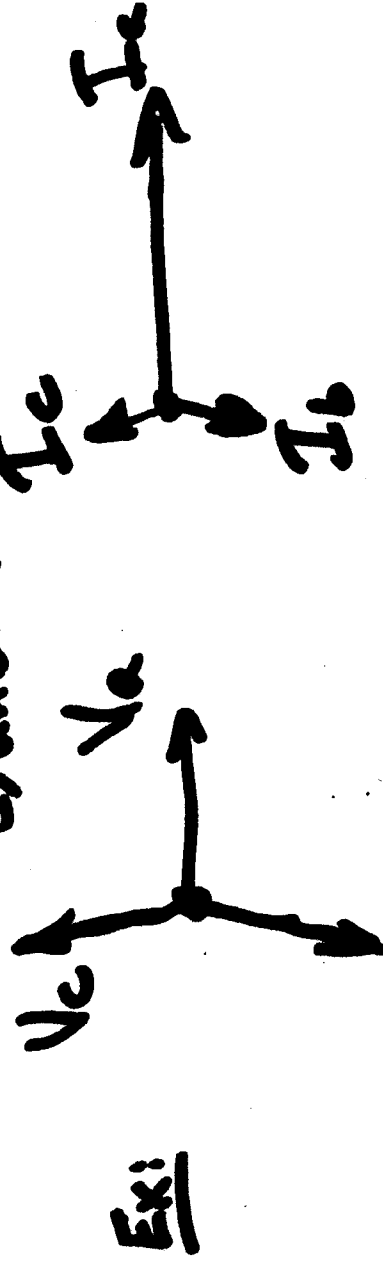load currents flowing thru system, also unbalanced faults: L-G, L-L, L-L-G



Zero

"a-b-c" "neg"
"a-b-c" "a-c-b"

Per Phase Analysis is typical - no need to track ϕ_b & ϕ_c if ϕ_a is known and each "group" (i.e. pos, neg, zero) is symmetric/balanced.

Convenience to define "a":

$$\bar{a} = 1 \angle 120^\circ$$

$$a = 1 \angle 120^\circ$$

$$a^2 = 1 \angle -120^\circ$$

$$\bar{V}_{b1} = \bar{V}_{a1} a^2 \quad \bar{V}_{b2} = \bar{V}_{a2} a$$

$$\bar{V}_{c1} = \bar{V}_{a1} a \quad \bar{V}_{c2} = \bar{V}_{a2} a^2$$

$$\begin{bmatrix} \bar{V}_a \\ \bar{V}_b \\ \bar{V}_c \end{bmatrix} = \begin{bmatrix} \bar{V}_{a0} + \bar{V}_{a1} + \bar{V}_{a2} \\ \bar{V}_{b0} + \bar{V}_{b1} + \bar{V}_{b2} \\ \bar{V}_{c0} + \bar{V}_{c1} + \bar{V}_{c2} \end{bmatrix} = \begin{bmatrix} \bar{V}_{a0} + \bar{V}_{a1} + \bar{V}_{a2} \\ \bar{V}_{a0} + a^2 \bar{V}_{a1} + a \bar{V}_{a2} \\ \bar{V}_{a0} + a \bar{V}_{a1} + a^2 \bar{V}_{a2} \end{bmatrix}$$

Note: $V_{a0} = V_{b0} = V_{c0}$

$$\begin{bmatrix} V_{c1} \\ V_{c2} \\ V_{c3} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} V_{a1} \\ V_{a2} \\ V_{a3} \end{bmatrix} = [A] \begin{bmatrix} V_{a1} \\ V_{a2} \\ V_{a3} \end{bmatrix} \quad ||$$

$$\begin{bmatrix} V_p \\ I_p \end{bmatrix} = [A] \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$



$$[A]^{-1} [V_p] = [A]^{-1} [A] [V_s]$$

$$[V_s] = [A]^{-1} [V_p]$$

Z_p = "phase impedances"

Z_s = "seq impedances"

§ 8.2
GFS

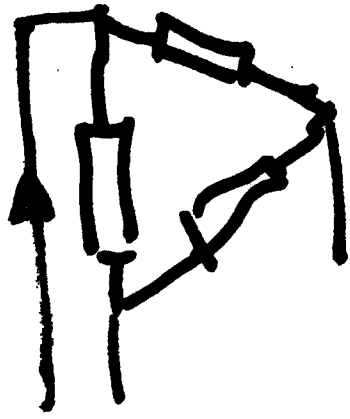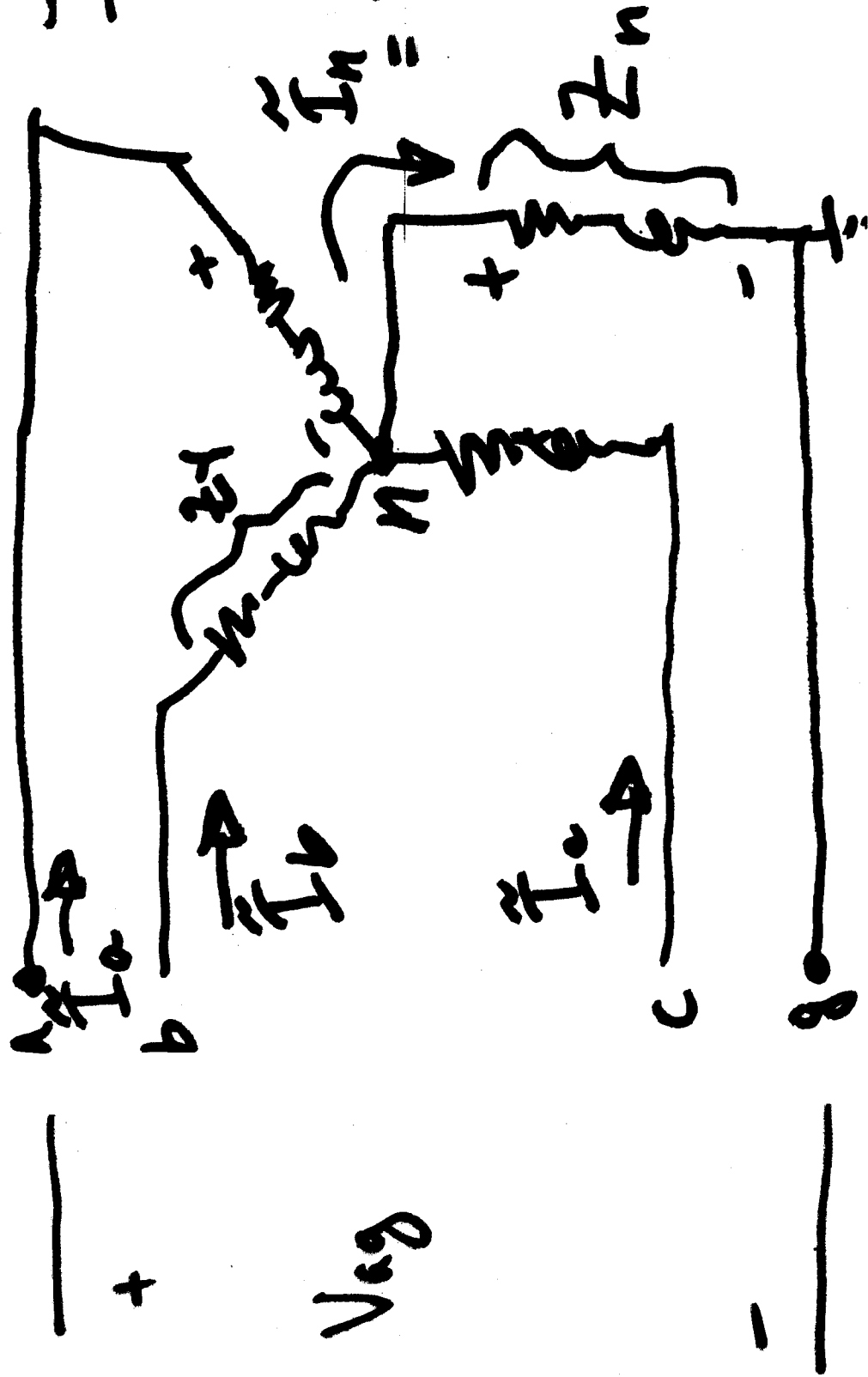

$$\vec{V}_{ag} = Z_Y I_a + Z_n I_n$$

$$= Z_Y I_a + Z_n (I_a + I_b + I_c)$$

$$= (Z_Y + Z_n) I_a + Z_n I_b + Z_n I_c$$

$$\vec{V}_{bg} = Z_n I_a + (Z_Y + Z_n) I_b + Z_n I_c$$

$$\vec{V}_{cg} = Z_n I_a + Z_n I_b + (Z_n + Z_Y) I_c$$

$$\begin{bmatrix} V_{ag} \\ V_{bg} \\ V_{cg} \end{bmatrix} = \begin{bmatrix} (Z_Y + Z_n) & Z_n & Z_n \\ Z_n & (Z_Y + Z_n) & Z_n \\ Z_n & Z_n & (Z_Y + Z_n) \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} Z_{aa} & Z_{ab} & Z_{ac} \\ Z_{ba} & Z_{bb} & Z_{bc} \\ Z_{ca} & Z_{cb} & Z_{cc} \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

$$[V_p] = [Z_p][I_p]$$

$$[V_p][Z] = [V_s]$$

$$Z_s = A^{-1} Z_p A$$

$$= \begin{bmatrix} z_{10} & z_{11} & z_{12} \\ z_{20} & z_{21} & z_{22} \end{bmatrix}$$

$$\begin{bmatrix} v_{s0} \\ v_{s1} \\ v_{s2} \end{bmatrix} = V_s = Z_s I_s$$





$$Z_p = A Z_s A^{-1}$$

$$\begin{bmatrix} z_{10} & 0 & 0 \\ 0 & z_{11} & 0 \\ 0 & 0 & z_{22} \end{bmatrix}$$

decoupled

$$i.e. \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

Sequence Networks
Per Phase, 440V, P.V.

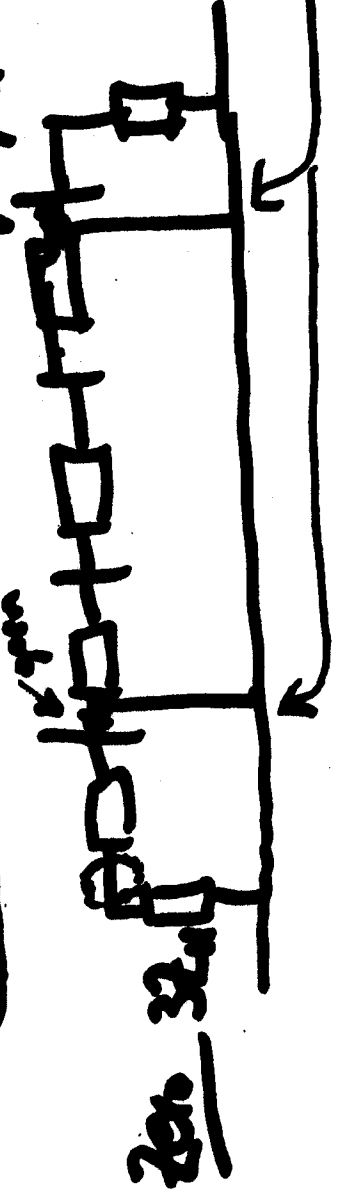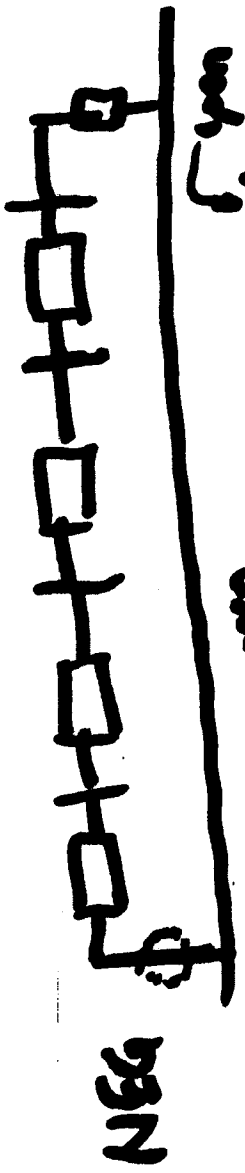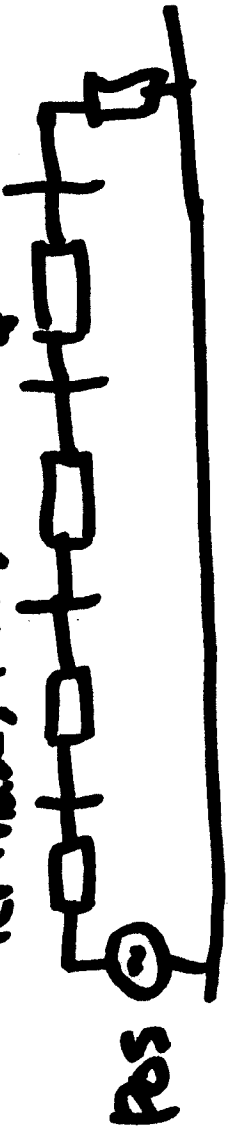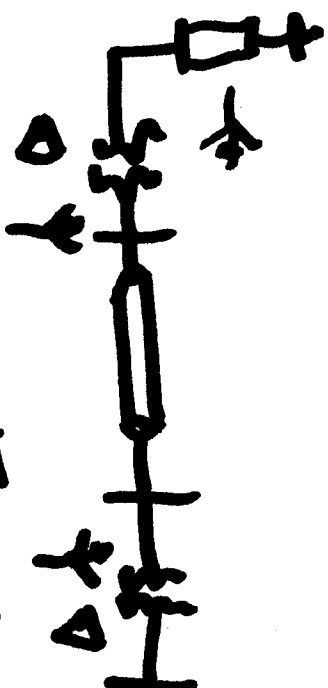

See details on next page.

For our simple GY load, see p.1 of these notes,



$$Z_s = A' Z_p A \Rightarrow$$

$$Z_s = \begin{bmatrix} Z_1 + 3Z_N & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_1 \end{bmatrix}$$


$$Z_1 = Z_{11}$$



$$Z_1 = Z_{22}$$

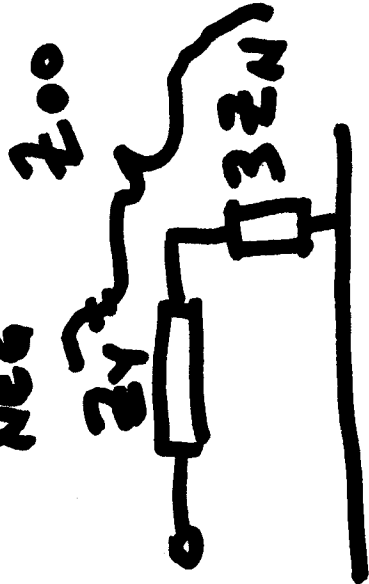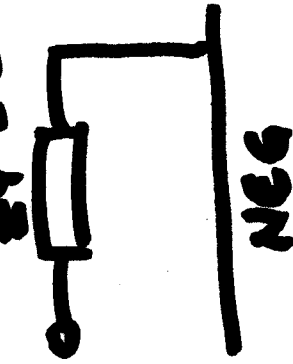



\therefore Can work with this either in Phase gty's or in sequence gty's

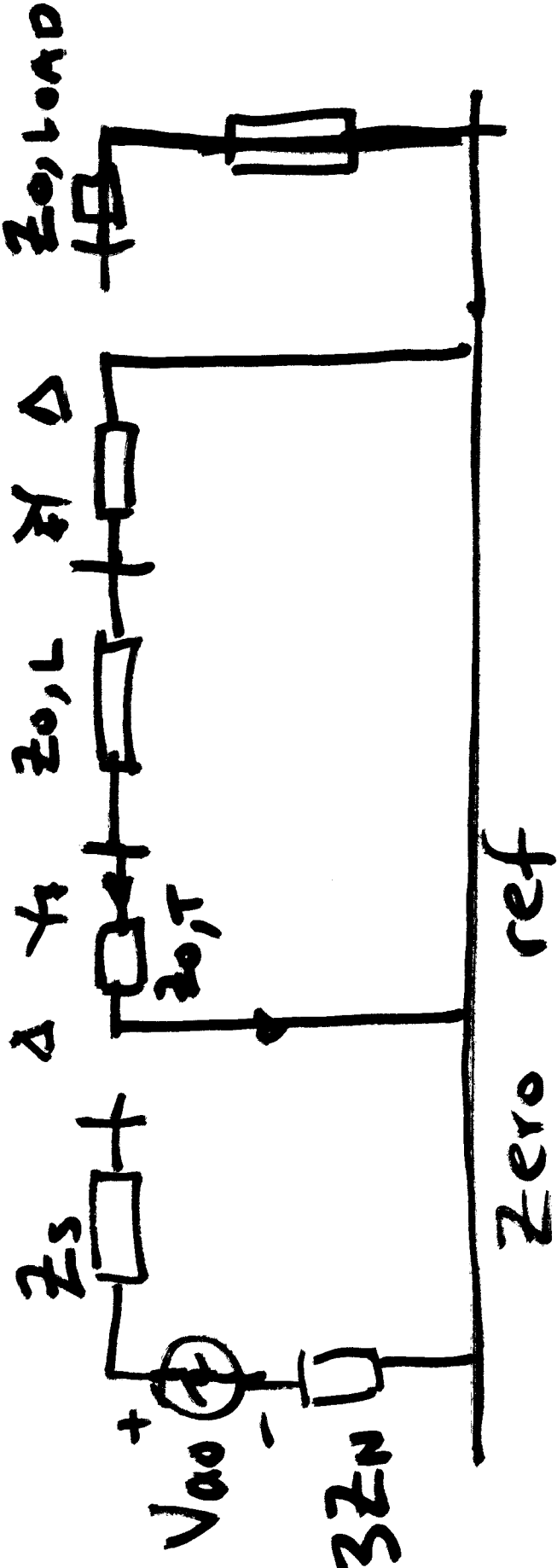


Ch. 6 - Overview "relay fundamentals"

§ 6.5.6, 6.5.7 - 3-4 pages - R-X

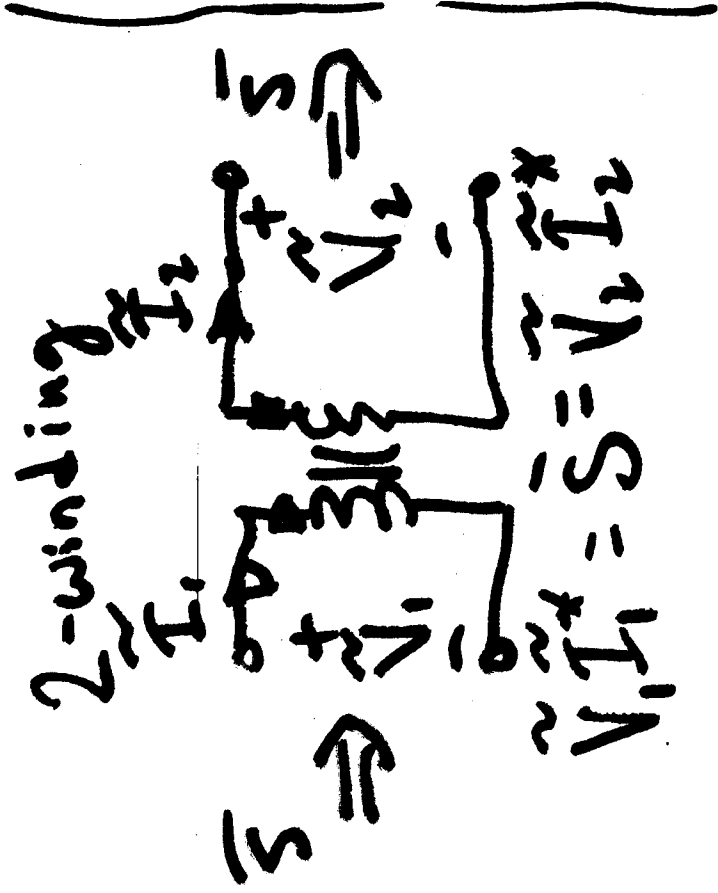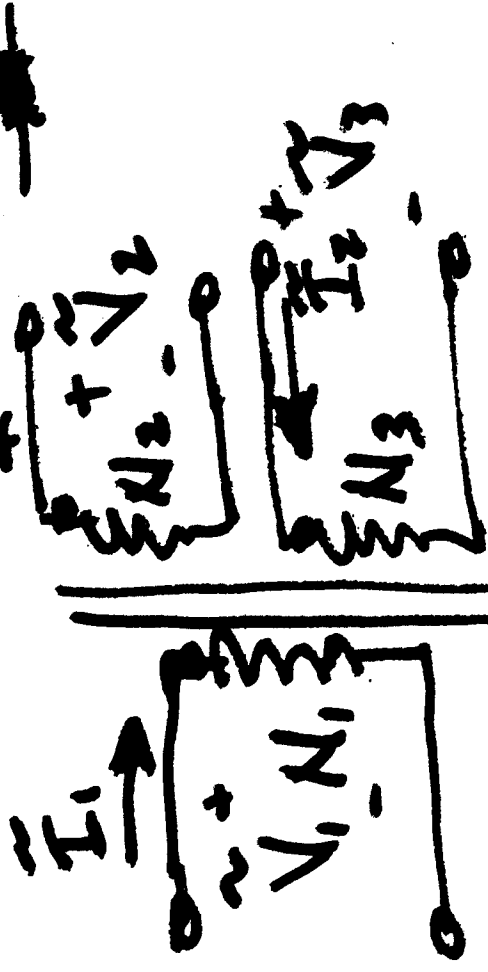3-Winding Xfms (ref. Hand 4.4)
(Ex. § 4.12)





$$\sum \vec{S}_M = 0 = \vec{V}_1 \vec{I}_1^* + \vec{V}_2 \vec{I}_2^* + \vec{V}_3 \vec{I}_3^*$$

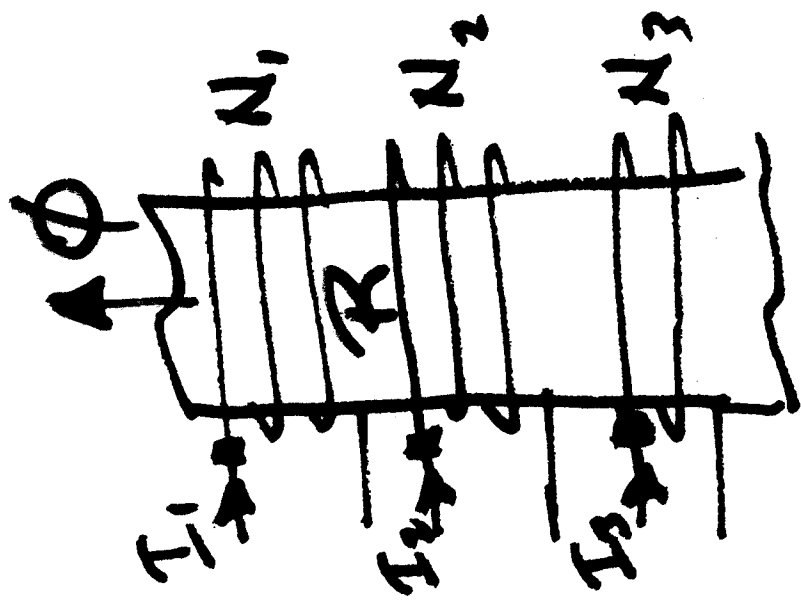

Prob 4.4


$$\begin{aligned}
 \sum MMFs &= 0 \\
 &= \underline{I_1 N_1 + I_2 N_2 + I_3 N_3} \\
 &= I_1 N_1 + I_2 N_2 + I_3 N_3
 \end{aligned}$$

MURK

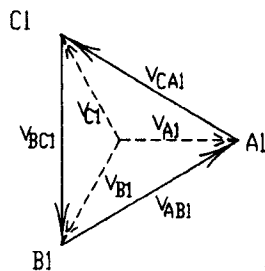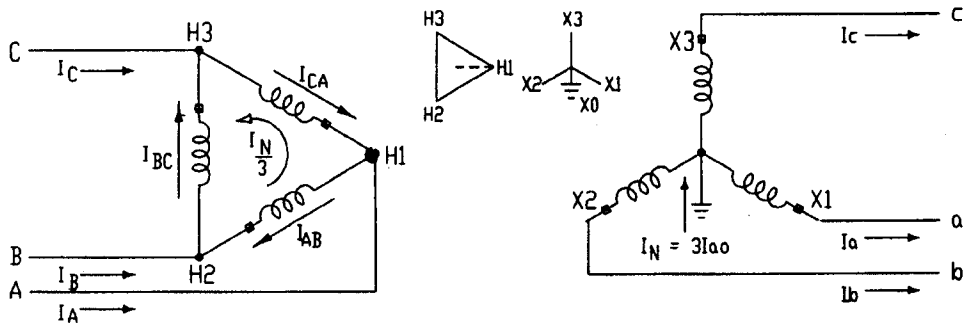


$$V_{A1} = V_{a1} (1/\sqrt{3} \angle 30^\circ)$$


PRI POS SEQ VOLTAGES

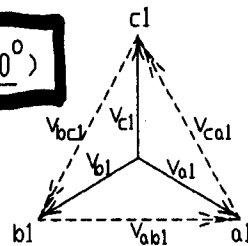


SEC POS SEQ VOLTAGES

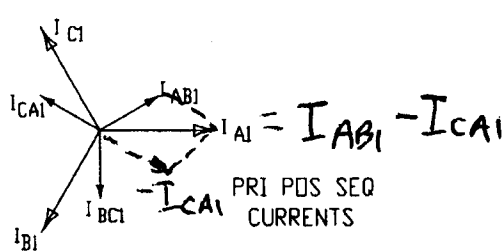

PRI POS SEQ CURRENTS

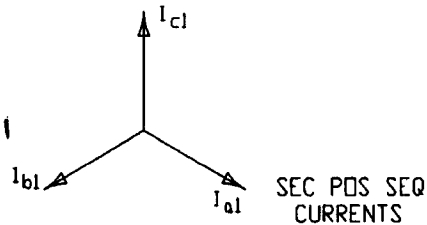


SEC POS SEQ CURRENTS

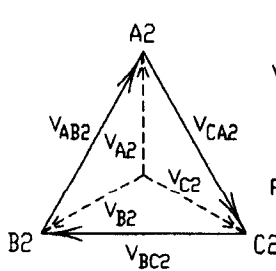


$$V_{A2} = V_{a2} (1/\sqrt{3} \angle -30^\circ)$$


PRI NEG SEQ VOLTAGES

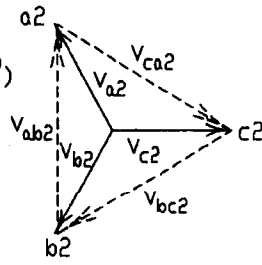

SEC NEG SEQ VOLTAGES

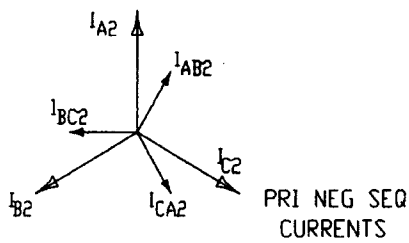



PRI NEG SEQ CURRENTS

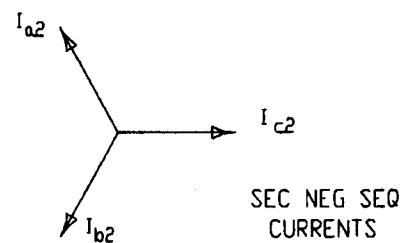

SEC NEG SEQ CURRENTS


ANSI STANDARD 30-DEGREE SHIFT DELTA-WYE

MORK

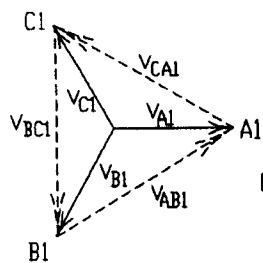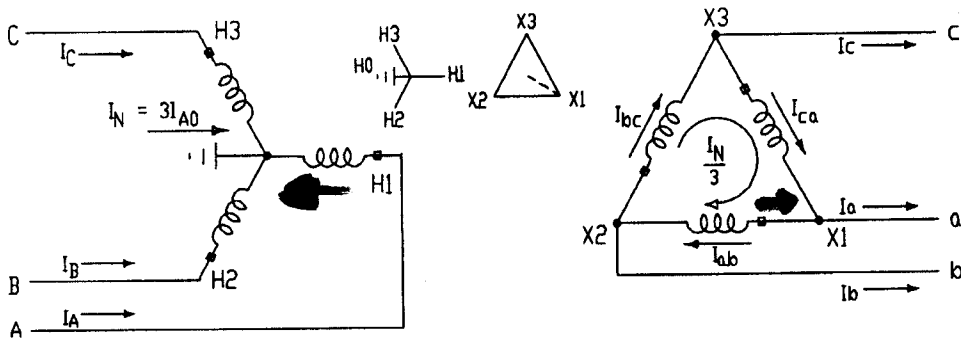


$$V_{A1} = V_{a1} (\angle 30^\circ)$$


PRI POS SEQ VOLTAGES

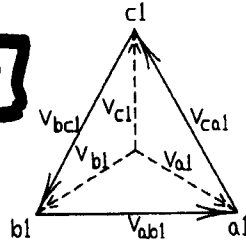


SEC POS SEQ VOLTAGES

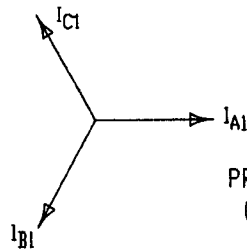

PRI POS SEQ CURRENTS

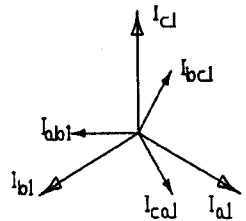


SEC POS SEQ CURRENTS

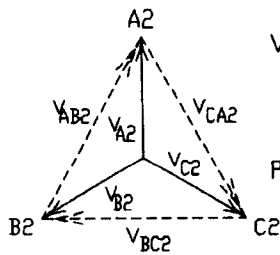


$$V_{A2} = V_{a2} (\angle -30^\circ)$$


PRI NEG SEQ VOLTAGES

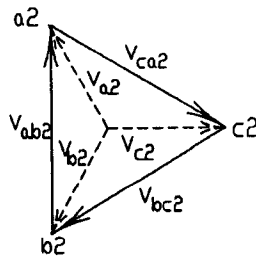

SEC NEG SEQ VOLTAGES

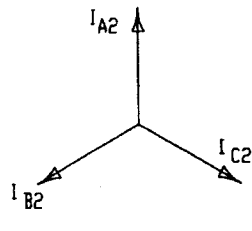

PRI NEG SEQ CURRENTS

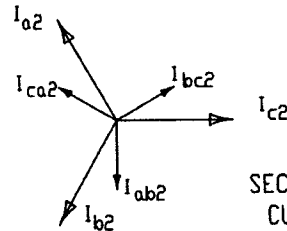

SEC NEG SEQ CURRENTS

ANSI STANDARD 30-DEGREE SHIFT WYE-DELTA