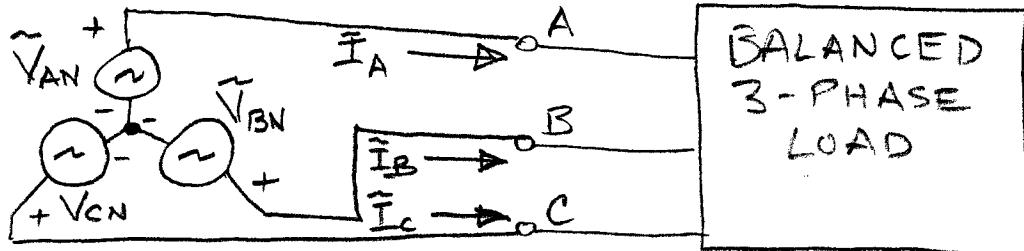



In each of the following cases, a balanced positive-sequence 3-phase source supplies a balanced 3-phase load. For all phasor calculations, assume that  $V_{AN}$  is the "reference." (The angle of  $V_{AN}$  is  $0^\circ$ )



For each case, first draw the power triangle for the load, labeling P, Q, S, and θ.

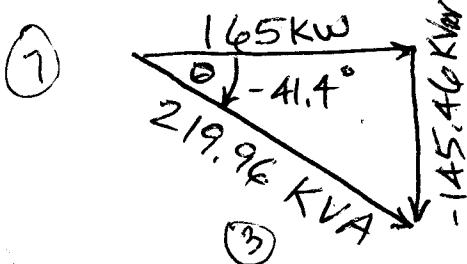a)  $V_{LL} = 34.5 \text{ kV RMS}$ . The load consumes 165 kW at a PF of 0.75 LEAD.

Calculate the phasor values of  $I_A$  and  $I_B$  flowing into the load.



(2)


$$I_A = \frac{165,000}{\sqrt{3} \times 34,500 \times \text{PF}} = 3.68 \text{ A}$$

(3)


$$\bar{I}_A = 3.68 (+41.4^\circ) \text{ A}$$

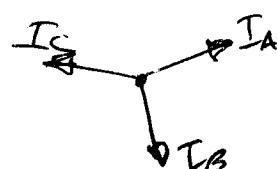(4)

$$\bar{I}_B = 3.68 (-78.6^\circ) \text{ A}$$



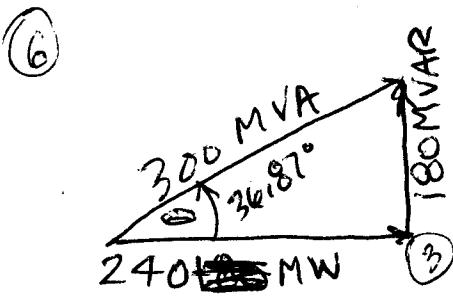b)  $V_{LL} = 69 \text{ kV RMS}$ . The load consumes 300 MVA at a PF of 0.8 LAG. Calculate the phasor value of  $I_A$  flowing into the load.




(6)

$$I_A = \frac{300 \times 10^6}{\sqrt{3} \times 69 \times 10^3} = 2,510 \text{ A}$$

(7)

$$\bar{I}_A = 2510 (-36.87^\circ) \text{ A}$$

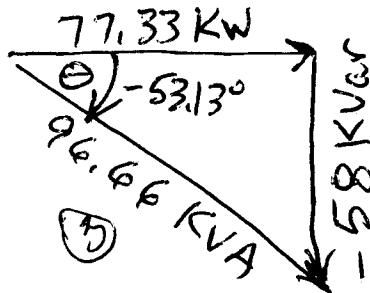c)  $V_{LL} = 480 \text{ V RMS}$ . The load generates 58 kVAR. The PF is known to be 0.6, but it was not noted whether it is LEAD or LAG. Calculate the phasor value of  $I_A$  flowing into the load. Is the PF LEAD or LAG? Explain.




(9)

(10)

$$\bar{I}_A = \frac{58,000}{\sqrt{3} \times 480 \times \sin \theta} (-\Theta)$$


$$\bar{I}_A = 87.2 (+53.13^\circ)$$

(11)  $\Rightarrow$  Leading PF

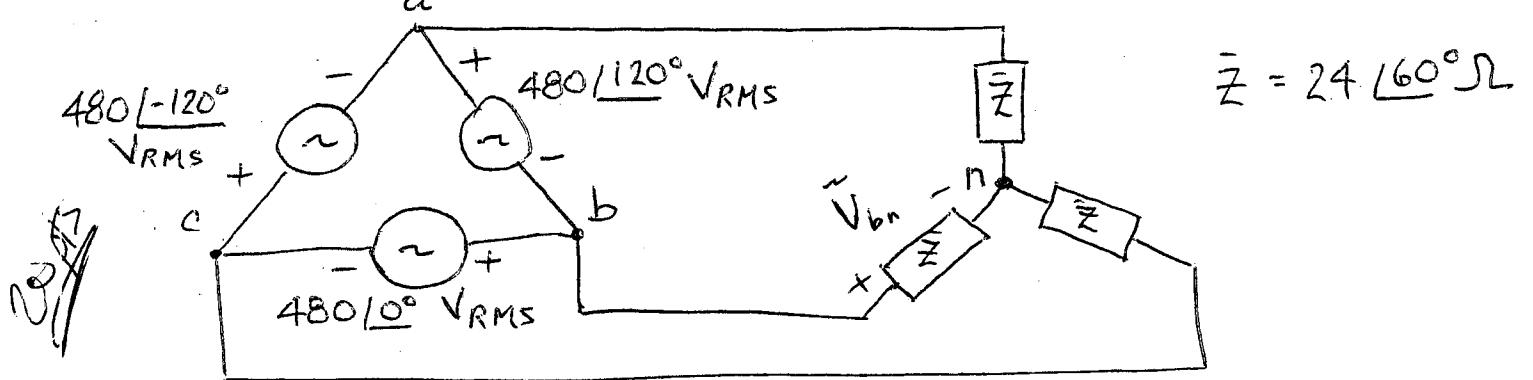

- a) Draw a phasor diagram showing the relationship between the L-L voltages of the source and the effective L-N voltages.

④

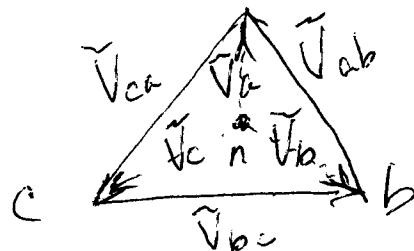

- b) Label  $\tilde{V}_{bn}$  at the load. What is its phasor value? What is the current  $\tilde{I}_{bn}$ ?

⑤

From a)  $\tilde{V}_{bn} = \underline{\underline{277}} \angle -30^\circ \text{ V}$

$$\tilde{I}_{bn} = \frac{\tilde{V}_{bn}}{\underline{\underline{Z}}} = \frac{\underline{\underline{277}} \angle -30^\circ}{24 \angle 60^\circ} = \underline{\underline{11.54}} \angle -90^\circ \text{ A}$$

- c) Is the voltage source positive sequence or negative? Explain or show why.

Positive Sequence

⑥

a-b-c for  
ccw rotation.



- d) What is the RMS magnitude of:

- The phase current of the load.  $\rightarrow \cancel{11.54} \quad 11.54$
- the line current.  $\rightarrow \cancel{11.54} \quad 11.54$
- the phase current of the source.  $\rightarrow \cancel{11.54} = \cancel{6.67}$

⑦