

$\vec{Z} = 18 \angle 30^\circ \Omega$




$V_\phi = 120 \text{ V}$
 $= V_{LN}$
 $V_\phi \angle \theta$
 \vec{I}_C

$\vec{I}_A = \frac{V_{AN}}{\vec{Z}}$


$= 10 \angle -30^\circ \text{ A}$

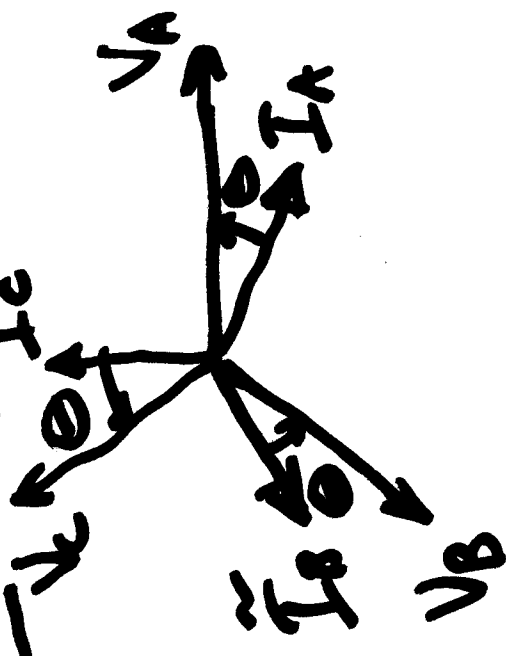$S_{3\phi} = \vec{V}_A \vec{I}_A^* \times 3$



$$\tilde{Z}_A = 36 \angle 30^\circ$$

$$\tilde{Z}_A = 3 \angle 4$$

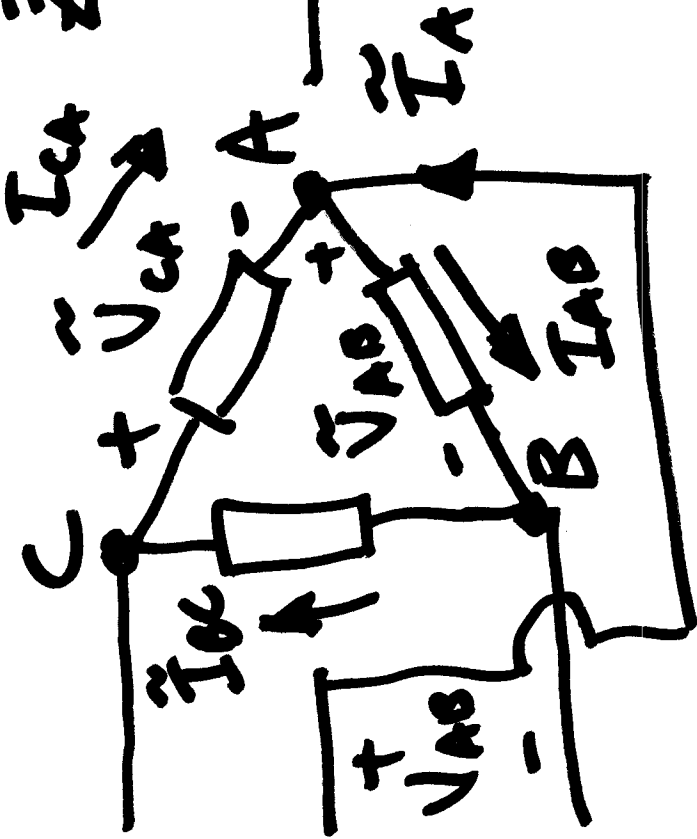

KCL @
node A

$$V_\phi = V_{LL}$$

$$\tilde{I}_{AB} = \frac{\tilde{V}_{AB}}{\tilde{Z}_A} = \frac{208 \angle 30^\circ}{36 \angle 30^\circ}$$

$$\tilde{I}_{CA} = \frac{\tilde{V}_{CA}}{\tilde{Z}_A} = \frac{208 \angle 150^\circ}{36 \angle 30^\circ}$$

$$\tilde{I}_A = \tilde{I}_{AB} - \tilde{I}_{CA}$$


$$= 5.778 \angle 0^\circ$$


$$- 5.778 \angle 120^\circ$$

$$= 10 \angle -30^\circ \text{ A}$$

$$V_{CA} = V_C - V_A$$



$$\vec{V}_{AB} = \vec{V}_A - \vec{V}_B$$

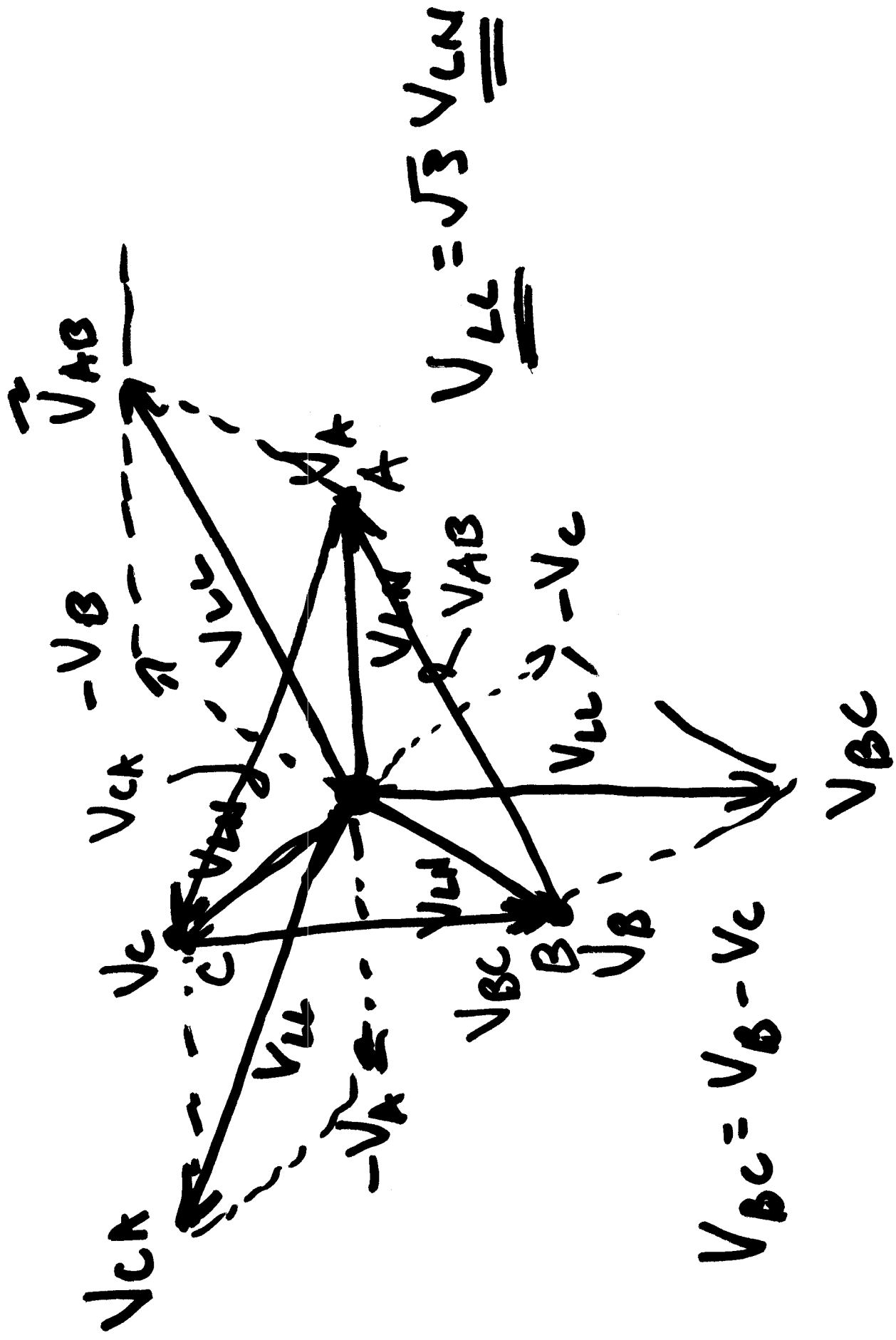


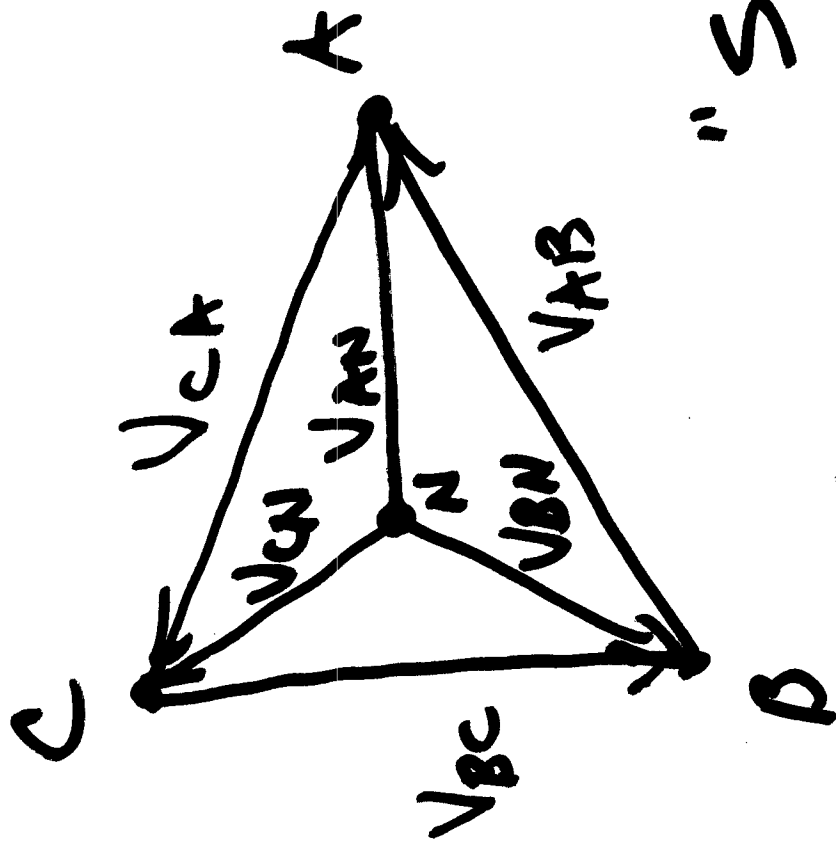



"Source
Conversion"



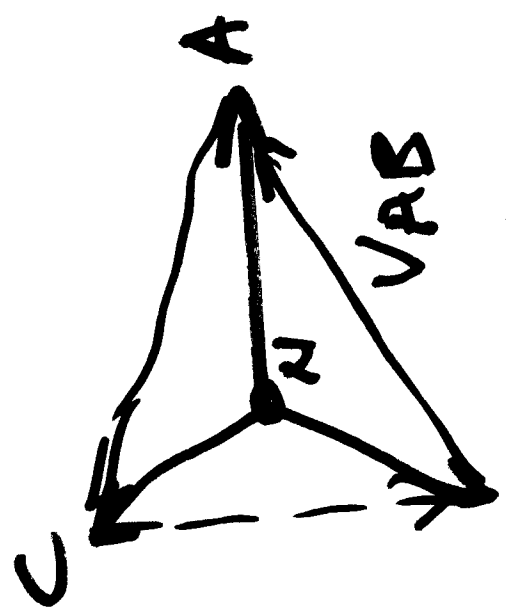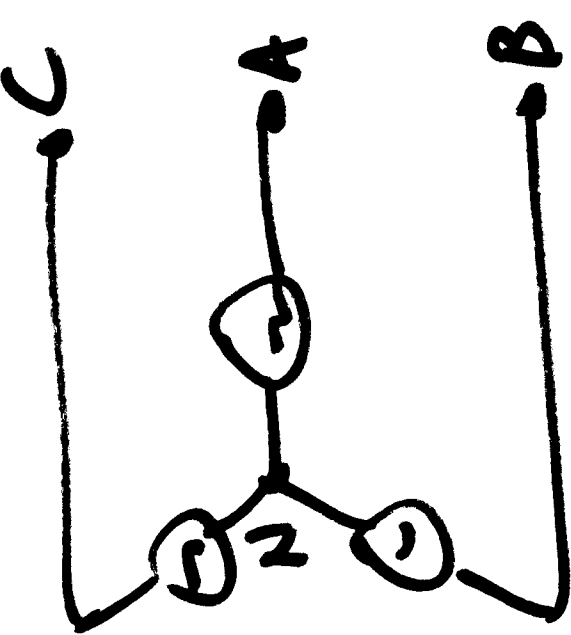

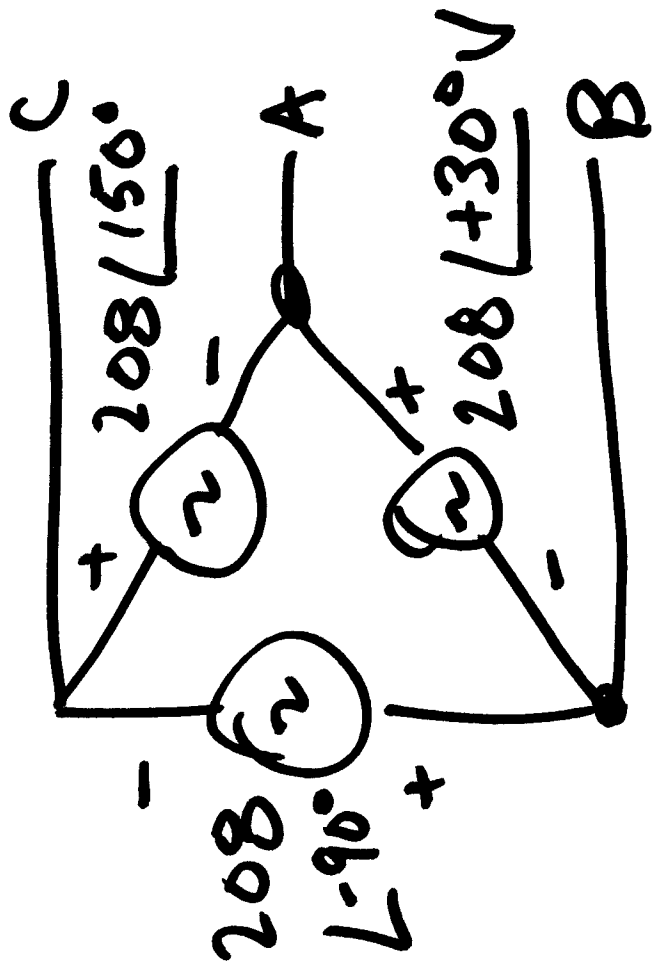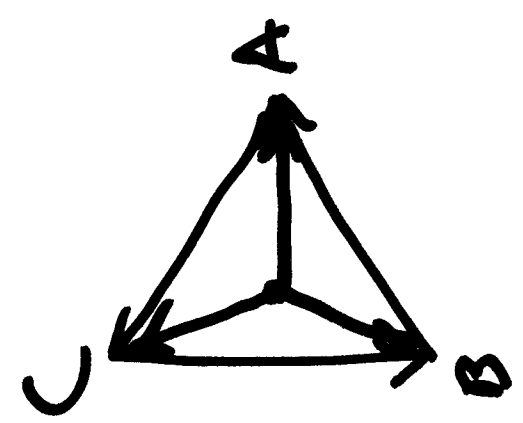$V_{LL} = \sqrt{3}(120)$
 $V_{LL} = \sqrt{3}(120)$
 $V_{LL} = 208V$



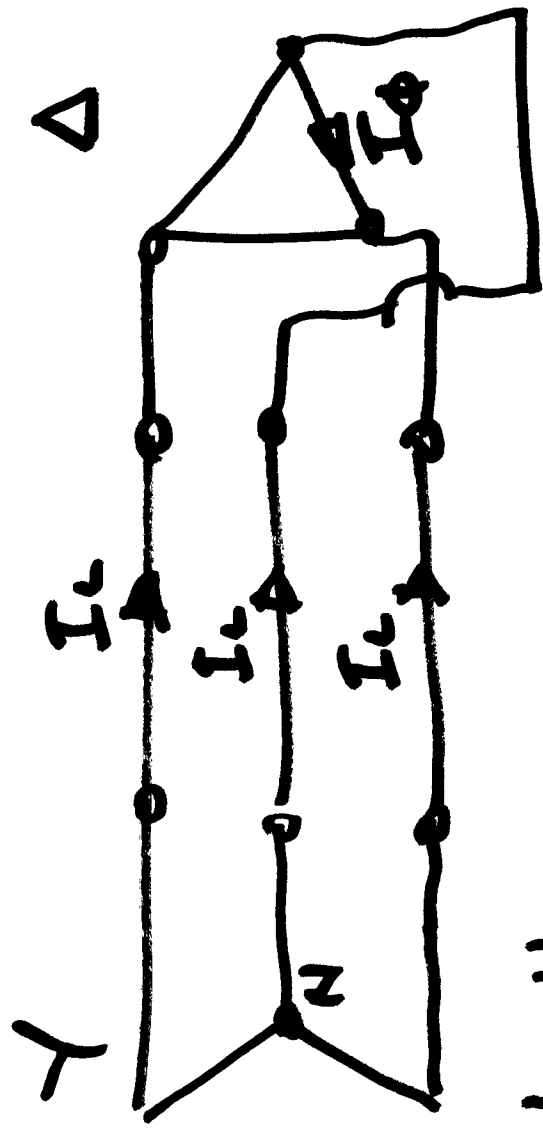

$$V_{\phi} = V_{LN}$$

$$I_{\phi} = I_L$$

$$V_{\phi} = V_{LL}$$

$$I_{\Delta} = I_{\phi} = I_L / \sqrt{3}$$

Be specific!

V_{LN}


V_{LL}

I_L

I_{Δ}


Phase gty's depend on whether

Y or Δ!

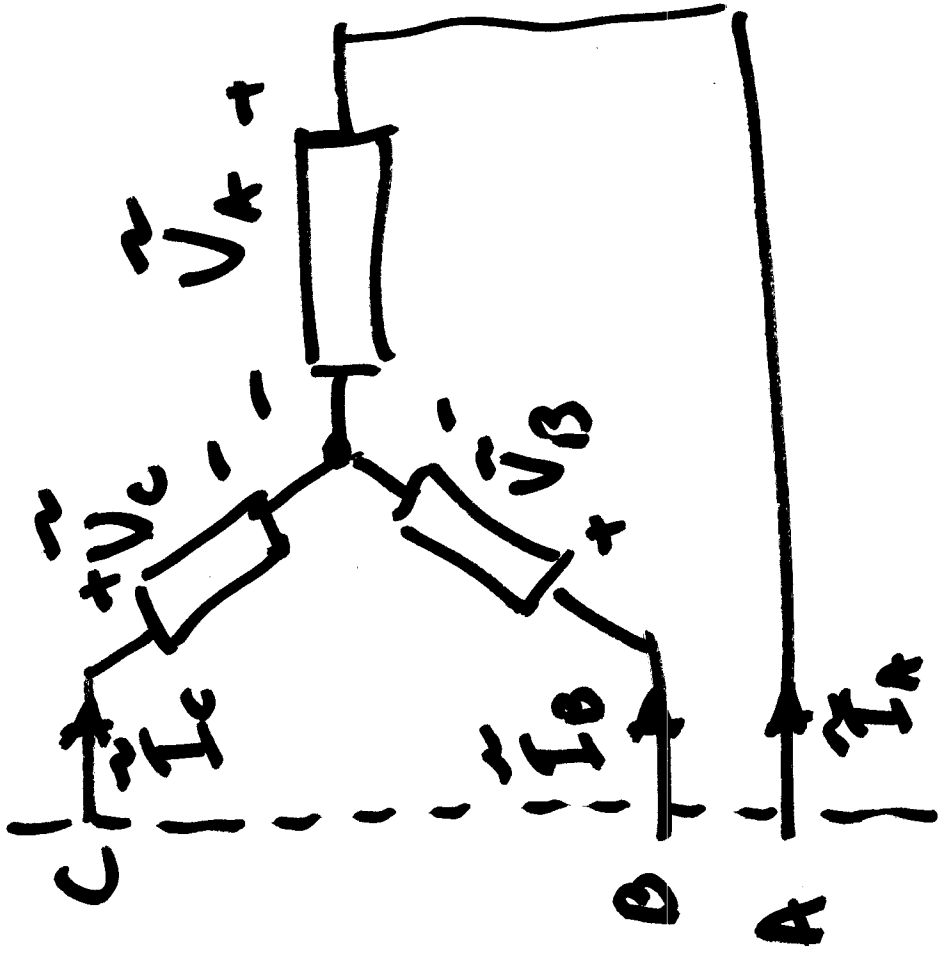

$$\begin{aligned}
 \bar{S}_{3\phi} &= \bar{V}_A \bar{I}_A^* + \bar{V}_B \bar{I}_B^* + \bar{V}_C \bar{I}_C^* \\
 &= 3 \bar{V}_A \bar{I}_A^* \\
 &= [V_A I_A \cos\theta + j V_A I_A \sin\theta] 3 \\
 &\quad P \quad + \quad j Q
 \end{aligned}$$
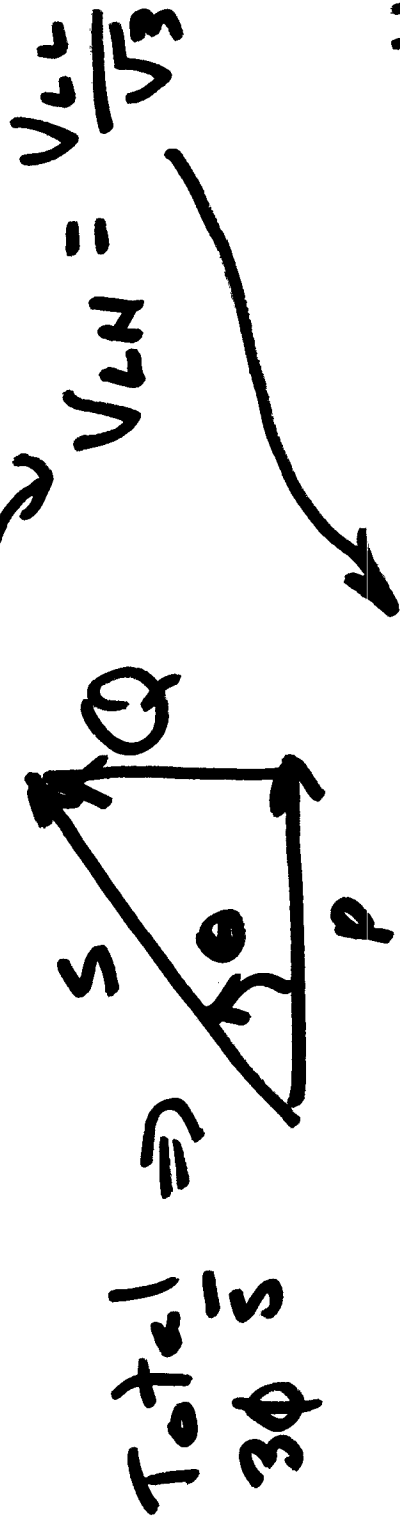
$$= 3 \left[\underbrace{V_{LN} I_L \cos \theta + j V_{LN} I_L \sin \theta} \right]$$




$$= \sqrt{3} \left[V_{LL} I_L \cos \theta + j V_{LL} I_L \sin \theta \right]$$

$$P_{3\phi} = \sqrt{3} V_{LL} I_L \cos \theta$$

$$Q_{3\phi} = \sqrt{3} V_{LL} I_L \sin \theta$$

$$S_{3\phi} = \sqrt{3} V_{LL} I_L$$

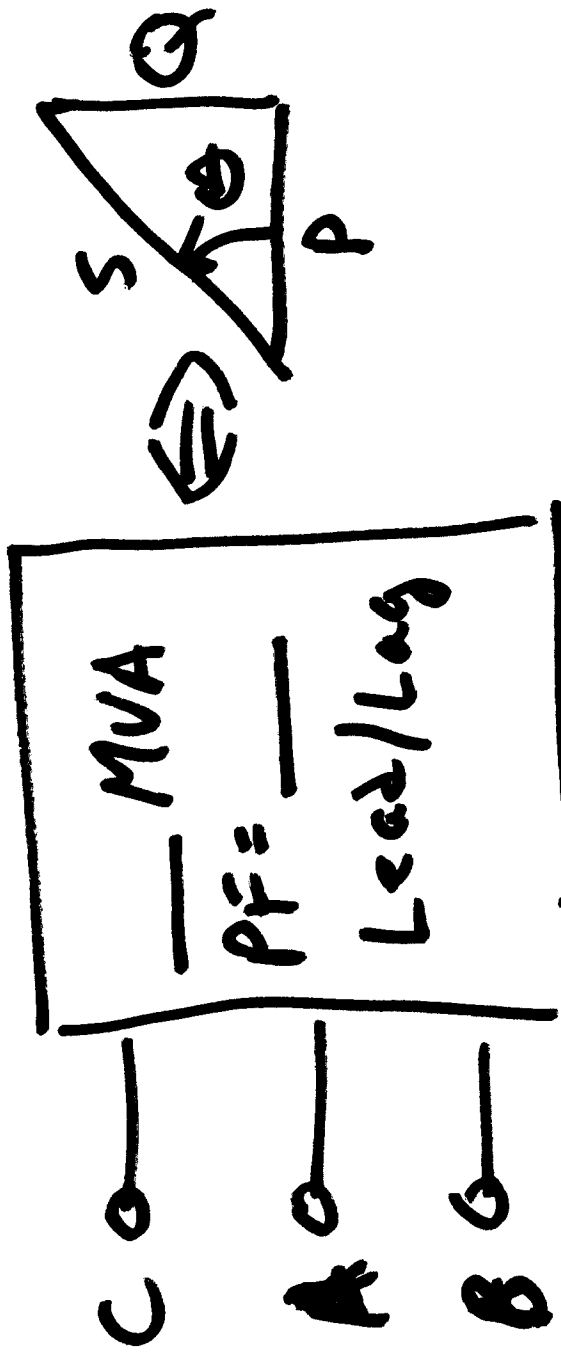

~~A/B/C~~
 →

BLACK BOX
 LOAD

Not shown for balanced 3ph Load...
 - Double subscripts
 - ϕ gty's