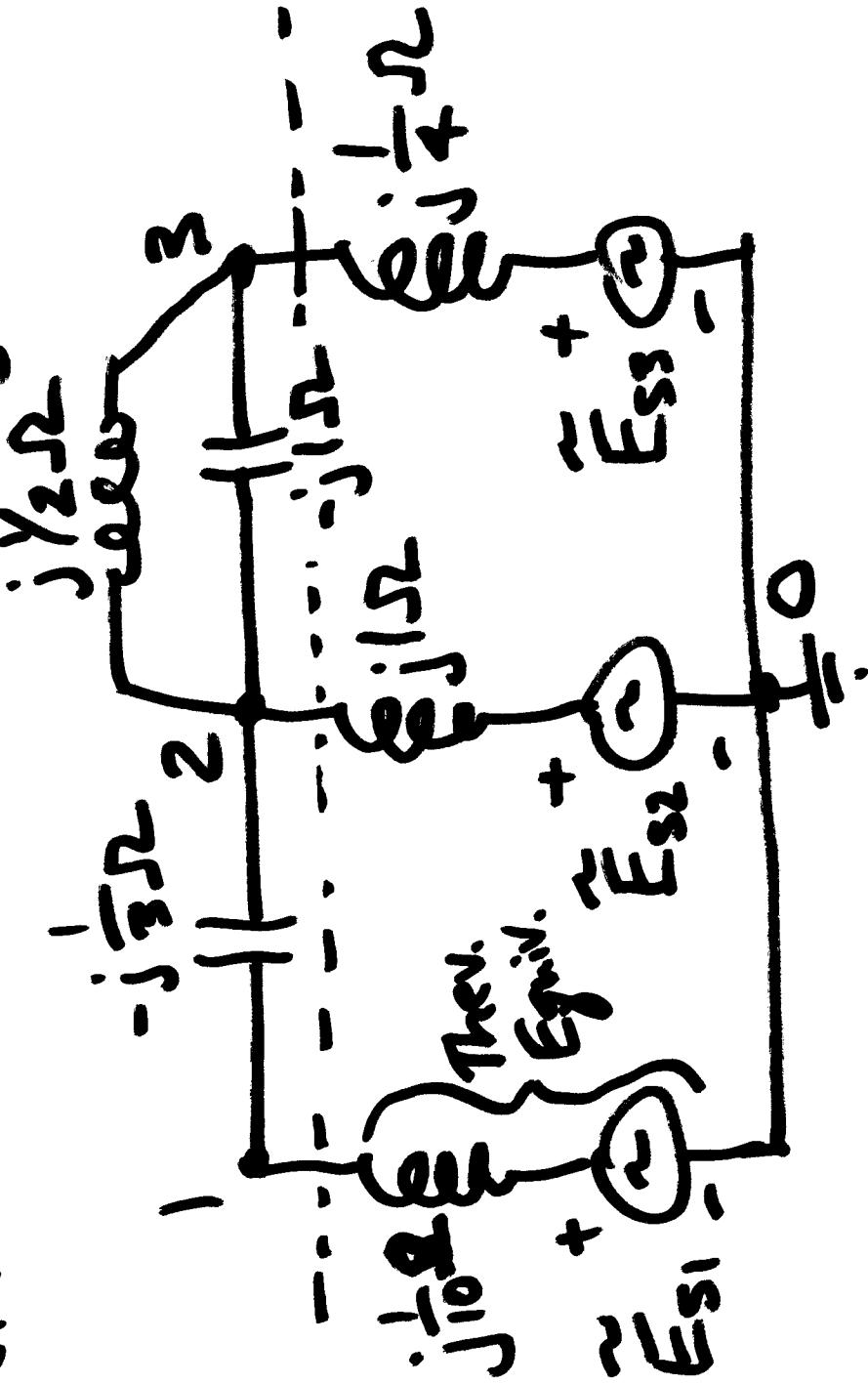


Topics for Today:

- Announcements
 - Text books should be in today, check w/book store.
 - Room B45 is open from 9am onward.
 - Office hrs: 1:30-2:30pm, Mon, Wed, Fri
 - Office: EERC 623. Phone: 906.487.2857
 - Ch.1 Solutions posted on web page. Finish by Sept. 5th.
 - Set of pre-req / review exercises given out this week.
- Continuing with Chapter 1 / Review:
 - Three-phase analysis, use of phasor diagrams
 - Per-phase (L-N phase-A) equivalent.
 - Per Unit system
 - Symmetrical Components
 - Sequence networks
- Next: Chapter 2 - Transformers and circuits w/transformers

Quick Review: Nodal Analysis


2



1) Convert Sources to Norton Equiv.

- 2) Convert all 2's into Y's
- 3) Construct $\{Y\}$ by inspection
- 4) Solve $\{Y\}_{\{V\}_{\text{node}}}$ = $\{I_{\text{inj}}\}$

3

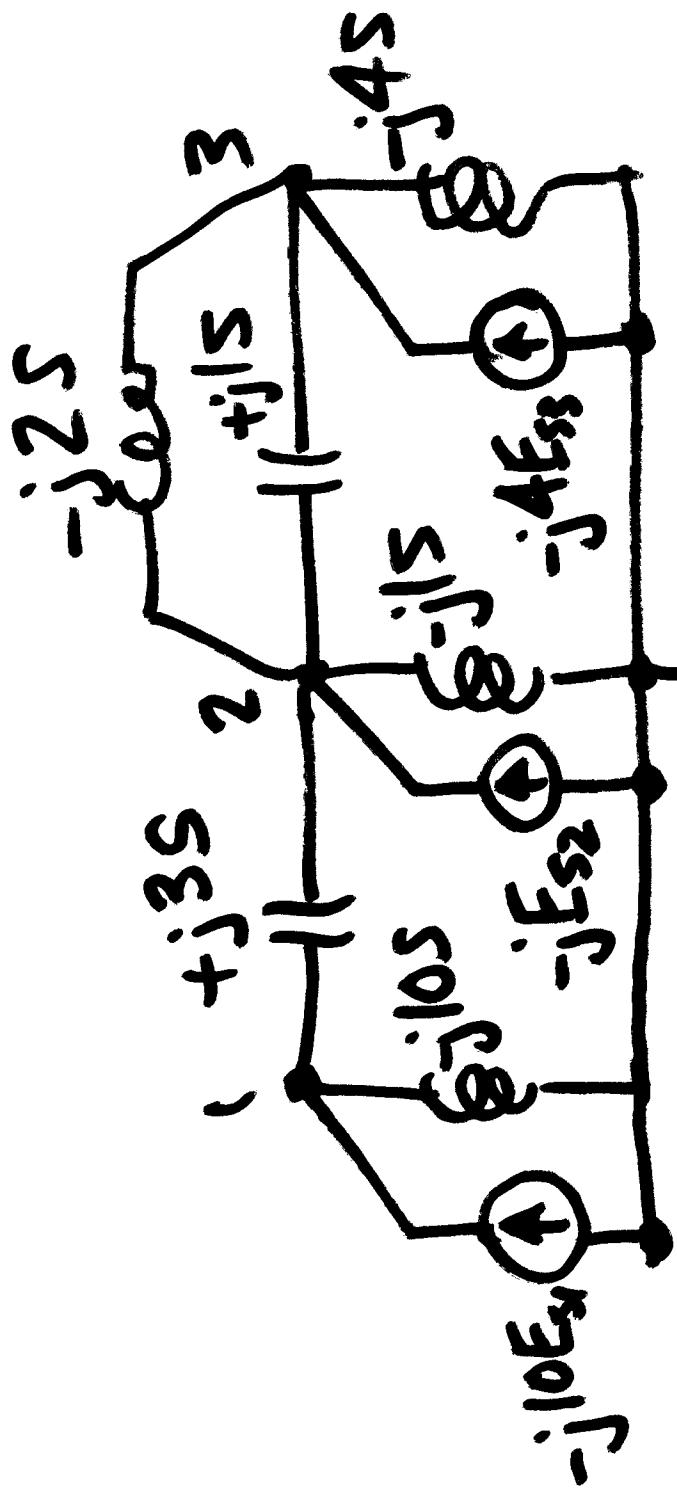

$$\begin{bmatrix} \mathbf{T}_{inj} \end{bmatrix} = \begin{bmatrix} T_{11} \\ -j10E_{s1} \\ -jE_{s2} \\ -j4E_{s3} \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{Y} \end{bmatrix} = \begin{bmatrix} Y_{node} \\ Y_1 \\ Y_2 \\ Y_3 \end{bmatrix}$$

$$\begin{bmatrix} j & -7 & -3 & 0 & -1 & -5 \end{bmatrix}$$

Ex: 1.2

3d ckt


4

- 3d Source, balanced $a-b-c$

$$- Y\text{-conn lead } Z_L = 10 \text{ } \Omega \text{ } (20^\circ \text{ } \Omega)$$

$$- V_{ab} = 173.2 \text{ } \text{V}_\text{rms} \quad V_{an} = \frac{100 \text{ } \text{V}_\text{rms}}{10 \text{ } \Omega}$$
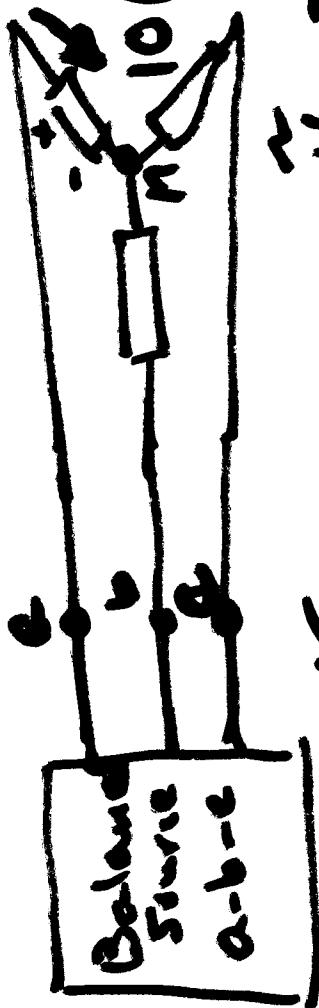
$$\tilde{V}_{an} = \frac{100}{10 \text{ } \Omega} = 10 \text{ } \text{V}_\text{rms}$$



$$\tilde{V}_{an} = 100 \text{ } (-30^\circ) \text{ } \text{V}_\text{rms}$$


$$V_{bn} = 100 \text{ } (-150^\circ) \text{ } \text{V}$$


$$V_{cn} = 100 \text{ } (+90^\circ) \text{ } \text{V}$$

$$\tilde{V}_{ab} = 173.2 \text{ } \text{V}_\text{rms}$$

$$V_{bc} = 173.2 \text{ } (-120^\circ) \text{ } \text{V}$$
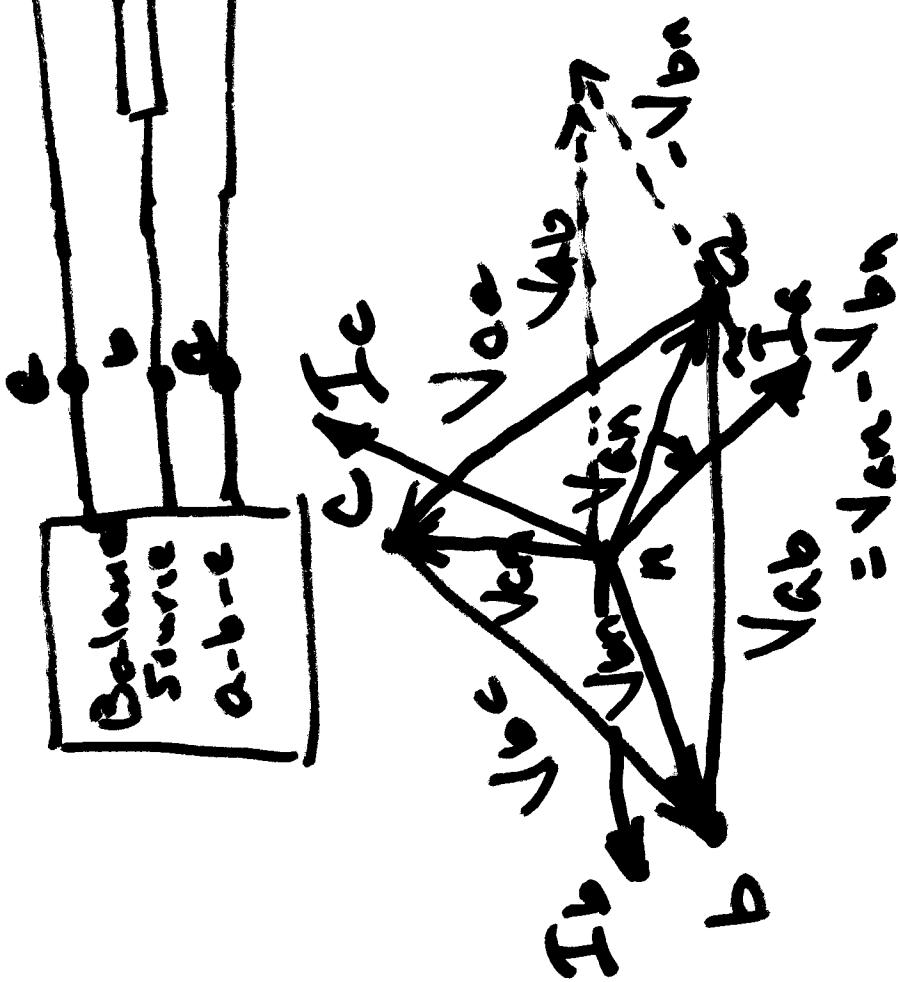
$$\tilde{V}_{ca} = 173.2 \text{ } (+120^\circ) \text{ } \text{V}$$



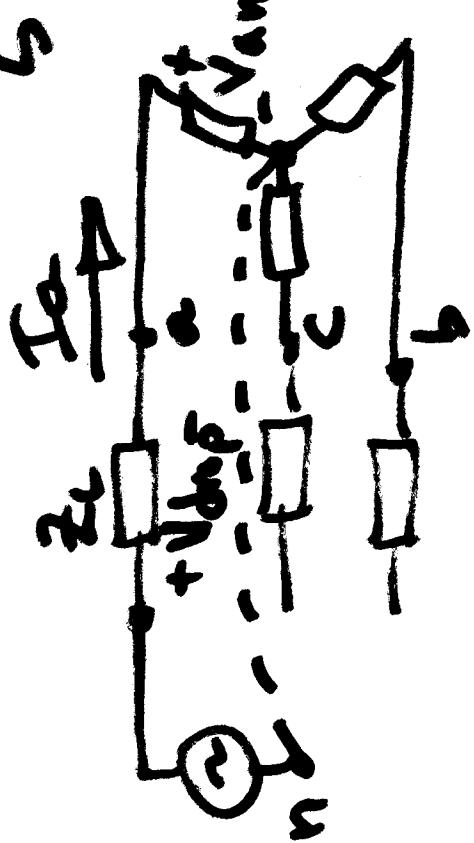

$$Z_{\Delta} = \frac{\text{sum of pairwise products of } Z_Y}{\text{the opposite } Z_Y}$$

Similar statements apply to the admittance transformations.

Example 1.3. The terminal voltage of a Y-connected load consisting of three equal impedances of $20\angle 30^\circ \Omega$ is 4.4 kV line to line. The impedance of each of the three lines connecting the load to a bus at a substation is $Z_L = 1.4\angle 75^\circ \Omega$. Find the line-to-line voltage at the substation bus.

Solution. The magnitude of the voltage to neutral at the load is $4400/\sqrt{3} = 2540$ V. If V_{an} , the voltage across the load, is chosen as reference,

$$V_{an} = 2540\angle 0^\circ \text{ V} \quad \text{and} \quad I_{an} = \frac{2540\angle 0^\circ}{20\angle 30^\circ} = 127.0\angle -30^\circ \text{ A}$$

The line-to-neutral voltage at the substation is

$$\begin{aligned} V_{an} + I_{an}Z_L &= 2540\angle 0^\circ + 127\angle -30^\circ \times 1.4\angle 75^\circ \\ &= 2540\angle 0^\circ + 177.8\angle 45^\circ \\ &= 2666 + j125.7 \quad 2670\angle 2.70^\circ \text{ V} \end{aligned}$$

and the magnitude of the voltage at the substation bus is

$$\sqrt{3} \times 2.67 = 4.62 \text{ kV}$$

Figure 1.22 shows the per-phase equivalent circuit and quantities involved.

$$\begin{aligned} \tilde{I}_{\Delta} &= \frac{\tilde{V}_{an}}{2L} = \frac{2540\angle 0^\circ \text{ V}}{20\angle 30^\circ \Omega} \\ &= 127\angle -30^\circ \text{ A} \\ \tilde{V}_{drop} &= \tilde{I}_{\Delta}(1.4\angle 75^\circ \Omega) \\ &\approx 177.8\angle 45^\circ \text{ V} \end{aligned}$$


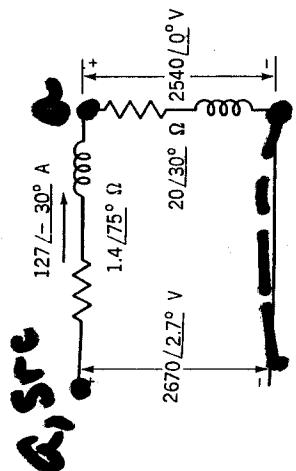
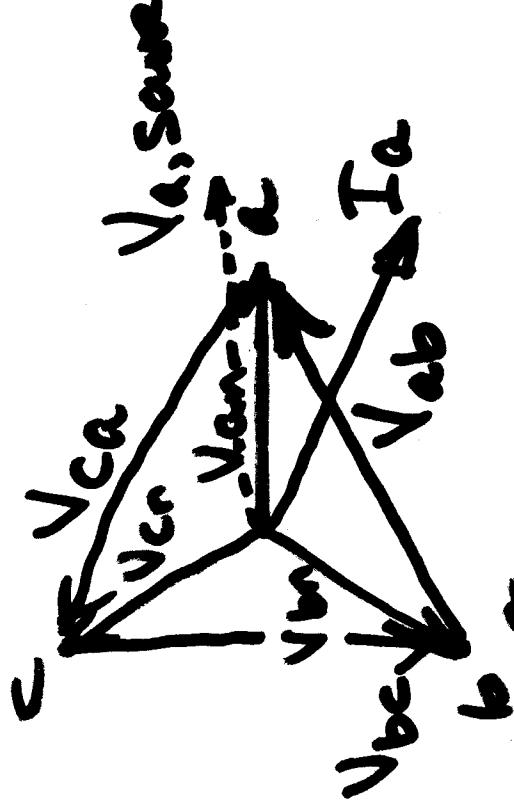


FIGURE 1.22
Per-phase equivalent circuit for Example 1.3.

Only need for
unbalanced
Y's or Δ 's.

For balanced Δ

$$Z_\Delta = 3Z_Y$$

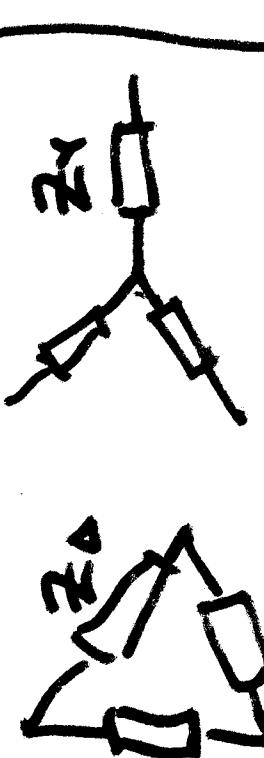

$$\begin{aligned} S_\Delta &= P_\Delta + Q_\Delta \\ P_\Delta &= R_\Delta \\ Q_\Delta &= \frac{V_{AC}^2}{R_\Delta} = \frac{V_{AC}^2}{R_Y} \end{aligned}$$

$$P_\Delta = \frac{V_{AC}^2}{3R_Y} = \frac{V_{AC}^2}{R_Y} = P_Y$$

TABLE 1.2
 Y_Δ and ΔY transformations[†]

$\Delta \rightarrow Y$		$Y \rightarrow \Delta$
$Z_A = \frac{Z_{AB}Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}}$		$Z_{AB} = \frac{Z_AZ_B + Z_BZ_C + Z_CZ_A}{Z_C}$
$Z_B = \frac{Z_{BC}Z_{AB}}{Z_{AB} + Z_{BC} + Z_{CA}}$		$Z_{BC} = \frac{Z_AZ_B + Z_BZ_C + Z_CZ_A}{Z_A}$
$Z_C = \frac{Z_{CA}Z_{BC}}{Z_{AB} + Z_{BC} + Z_{CA}}$		$Z_{CA} = \frac{Z_AZ_B + Z_BZ_C + Z_CZ_A}{Z_B}$
$\Delta \rightarrow Y$		$Y \rightarrow \Delta$
$Y_A = \frac{Y_{AB}Y_{CA} + Y_{BC}Y_{AB} + Y_{CA}Y_{BC}}{Y_{BC}}$		$Y_{AB} = \frac{Y_A Y_B}{Y_A + Y_B + Y_C}$
$Y_B = \frac{Y_{AB}Y_{CA} + Y_{BC}Y_{AB} + Y_{CA}Y_{BC}}{Y_{CA}}$		$Y_{BC} = \frac{Y_B Y_C}{Y_A + Y_B + Y_C}$
$Y_C = \frac{Y_{AB}Y_{CA} + Y_{BC}Y_{AB} + Y_{CA}Y_{BC}}{Y_{AB}}$		$Y_{CA} = \frac{Y_C Y_A}{Y_A + Y_B + Y_C}$


[†] Admittances and impedances with the same subscripts are reciprocals of one another.

Z_Y in terms of the delta impedances Z_Δ 's is

$$Z_Y = \frac{\text{product of adjacent } Z_\Delta\text{'s}}{\text{sum of } Z_\Delta\text{'s}}$$

So, when all the impedances in the Δ are equal (that is, balanced Z_Δ 's), the impedance Z_Y of each phase of the equivalent Y is one-third the impedance of each phase of the Δ which it replaces. Likewise, in transforming from Z 's to

Per Unit Quantities

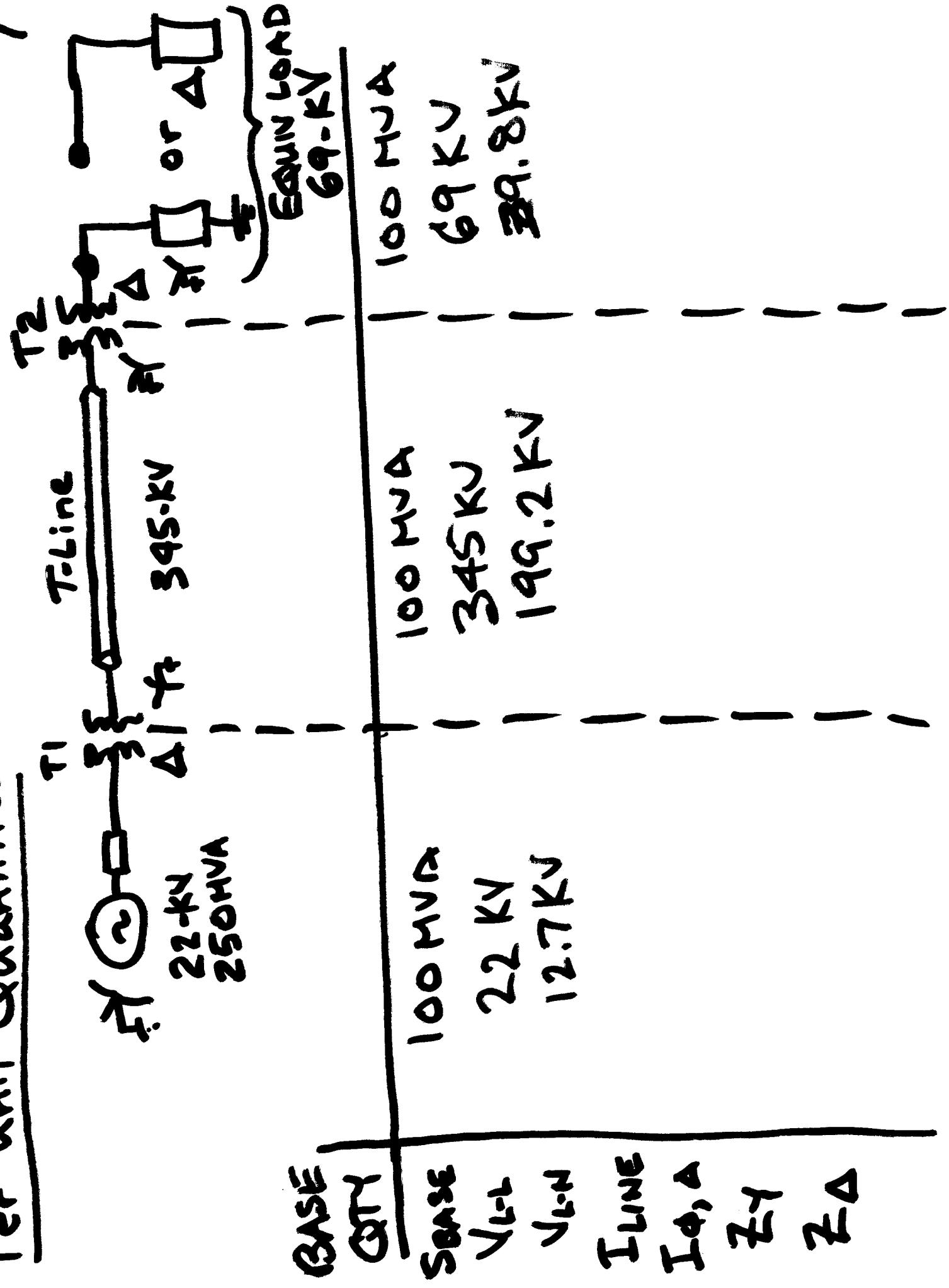

8

S_{BASE} : Assumed/defined, typ: ICOMIA

V_{Lc} : Rated V_L of system zone

$$V_{LN} = V_{Lc} / \sqrt{3}$$
$$\text{Time : } \frac{\text{Sbase}/3}{VA} \frac{V}{\sqrt{3}}$$

Continue from here on Thursday.