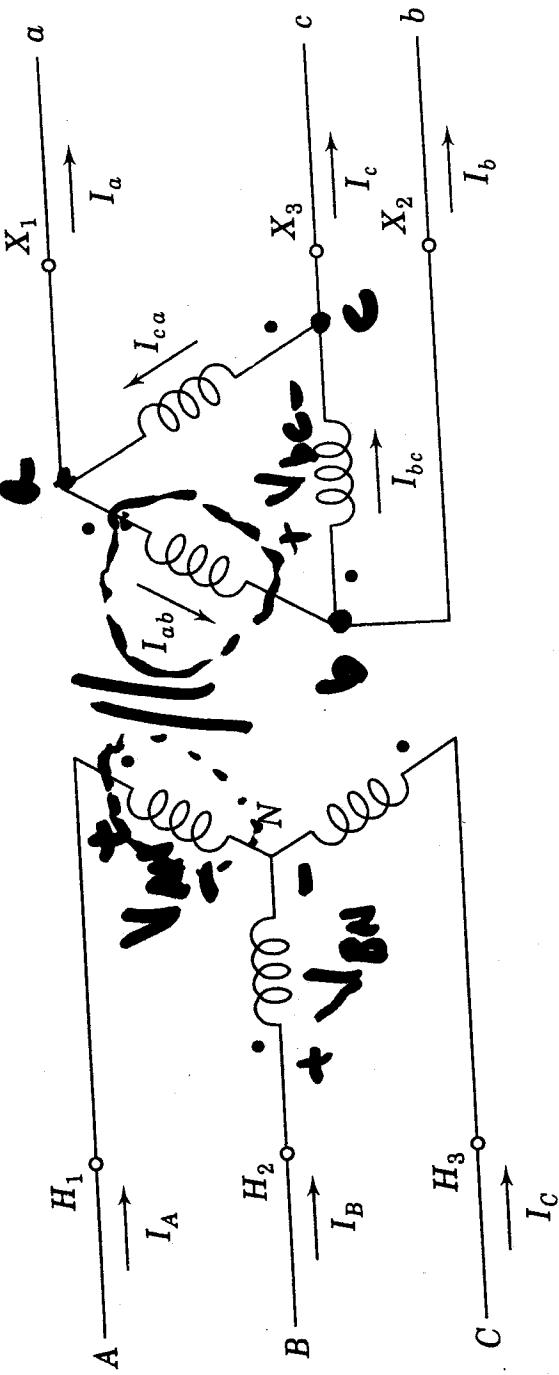


Topics for Today:

- Announcements
 - Software: Matlab? Will begin using as early as next week. —
 - Office hrs: 1:30-2:30pm, Mon, Wed, Fri
 - Office: EERC 623. Phone: 906.487.2857
- Exercises posted on web page, check e-mail for details. —
- Collected problems, solutions posted after collecting. —
- Recommended problems from Ch.2, solutions posted —
- Chapter 2 - Transformers and circuits w/transformers
 - 3-phase transformer banks and phase shifts (ANSI/IEEE vs. IEC)
 - Standard 30° shift transformers, non-standard connections
 - Pos/neg sequence phase shifts
 - Autotransformers —
 - Load Tap Changing (LTC) transformers
 - Phase shifting transformers
 - Paralleling transformers with a) unlike impedances; b) unlike tap positions
 - Three-winding transformers

2.6 THREE-PHASE TRANSFORMERS: PHASE SHIFT AND EQUIVALENT CIRCUITS 65





by the per-unit
is not important
with the
transformer impedances,
the resistance is

$220 \text{ Y}/22\Delta \text{ kV}$. The
-voltage side of the
, this value may be
per-unit reactance of
nsformer in a system
) MVA, 230 kV.


(a) Wiring diagram

Note: Phasor diagrams in text do not follow
common practice.

3

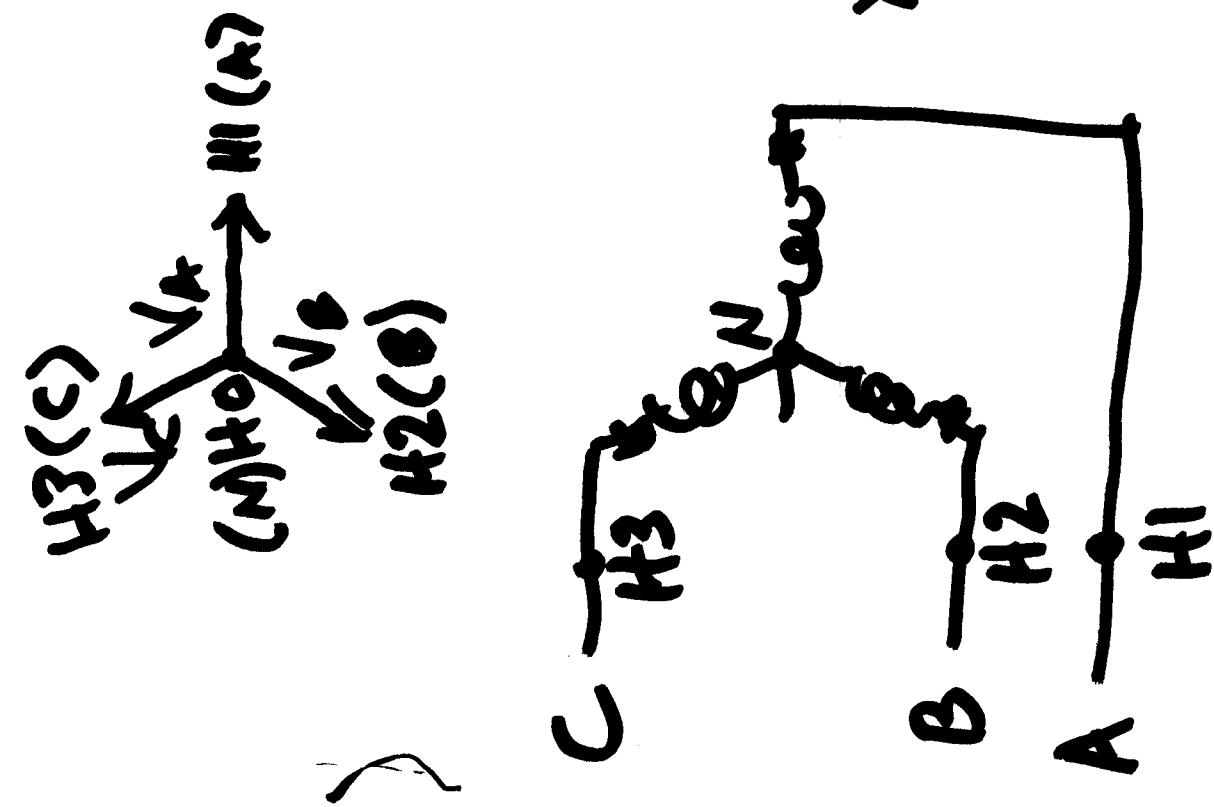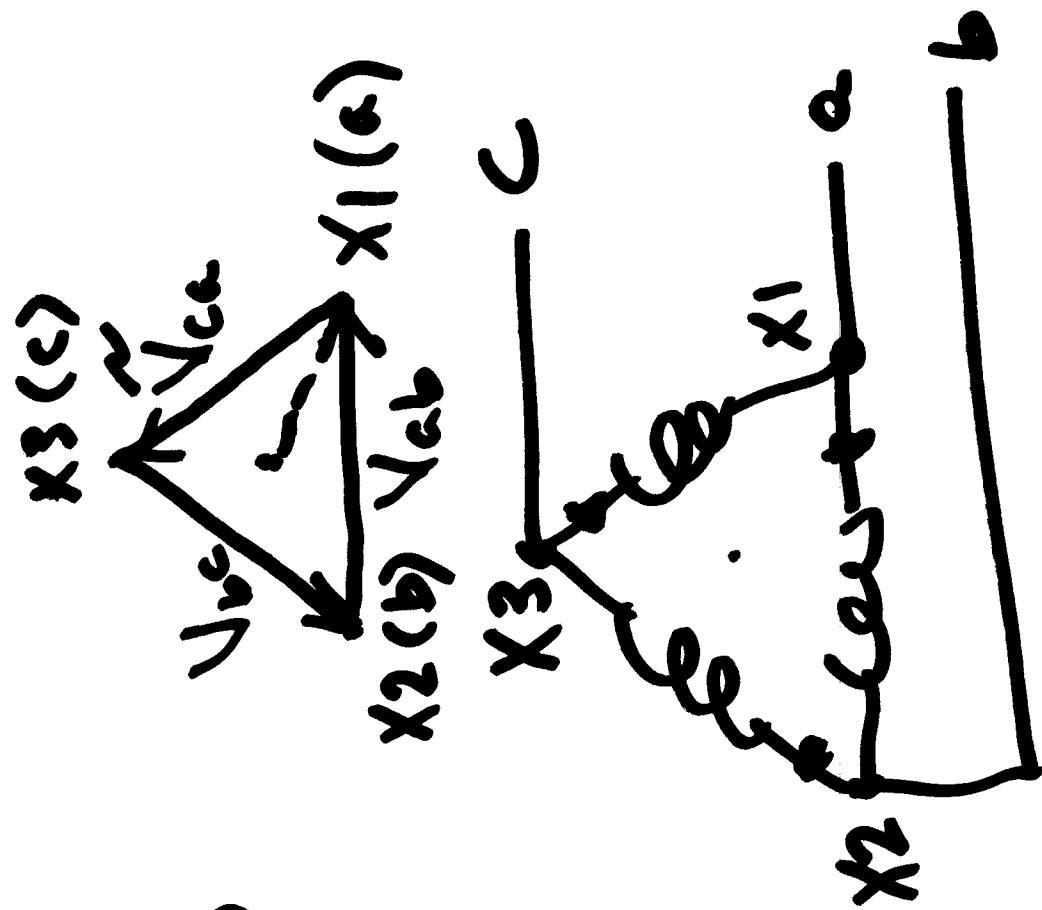


Possible Connections for (Phase-Shifts)

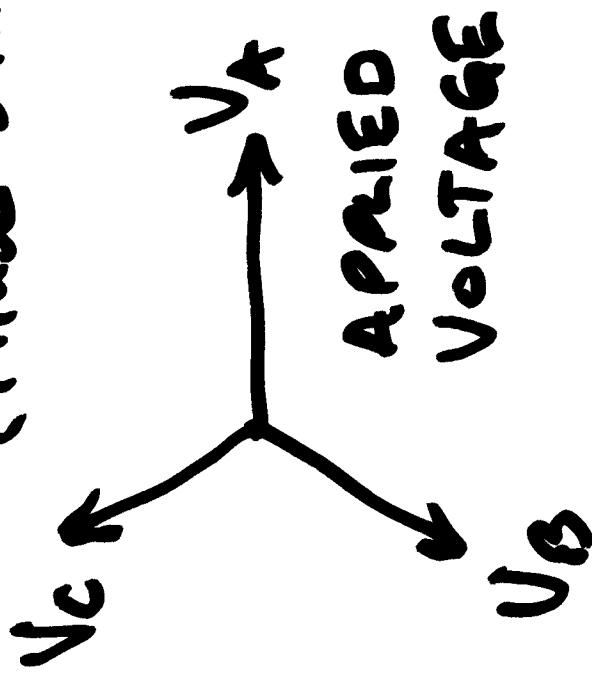

$\Delta\text{-}Y$ or $Y\Delta \times FDHRS?$

4

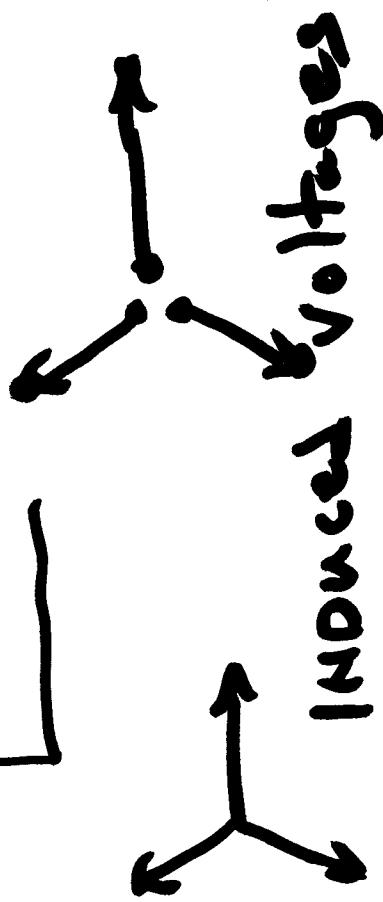
$\pm 30^\circ$
 $\pm 90^\circ$
 $\pm 150^\circ$



Note: Textbook "cookbook" gens are set up to assume 30° phase shift.






But - many transformers are non-std.
phase shift required by the grid tie requirements.
∴ learn to use phase shifts!
diagrams + figure out correct phase shifts!

MORK

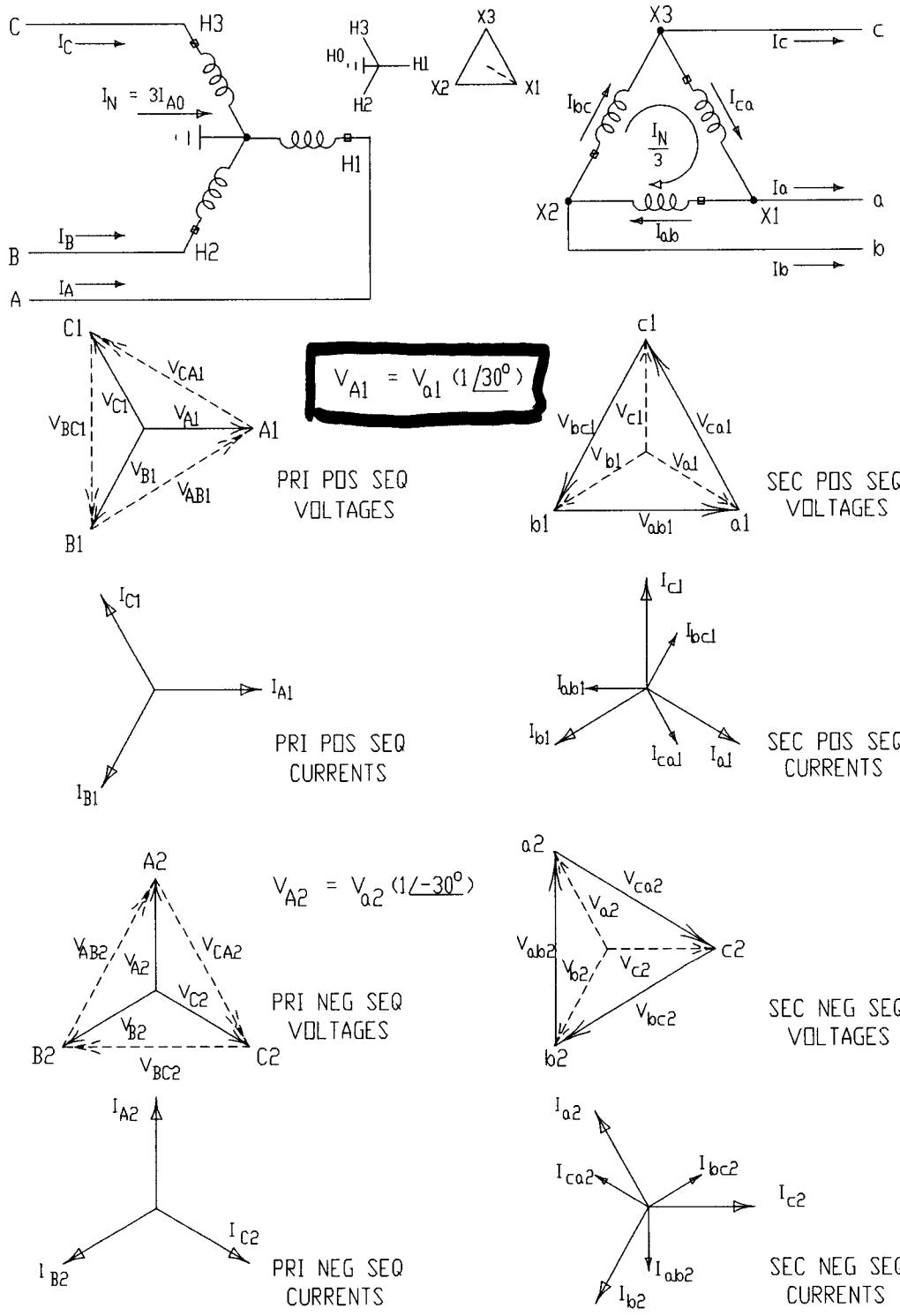

ANSI STANDARD 30-DEGREE SHIFT WYE-DELTA

MCRK

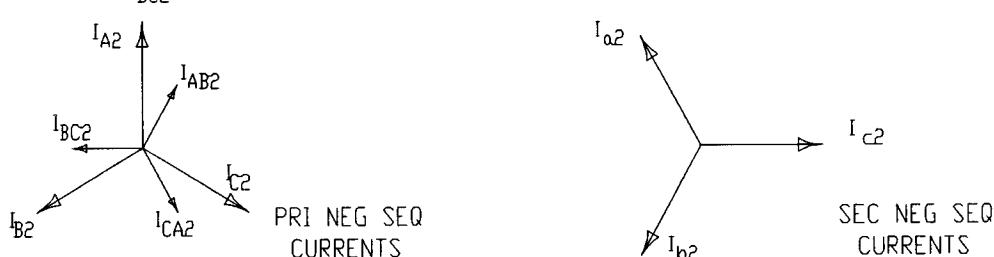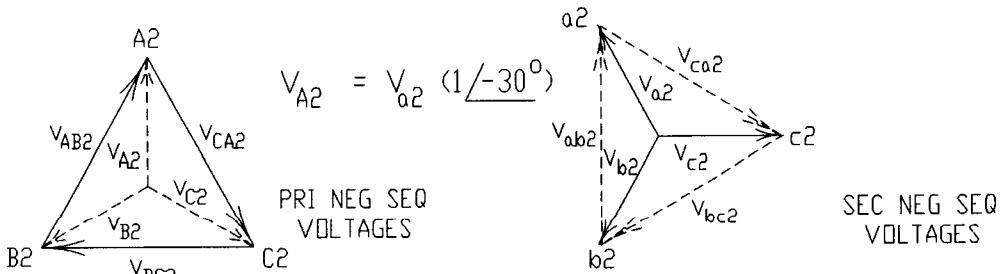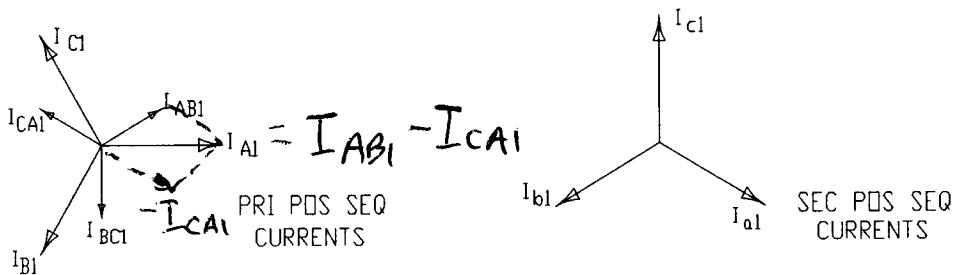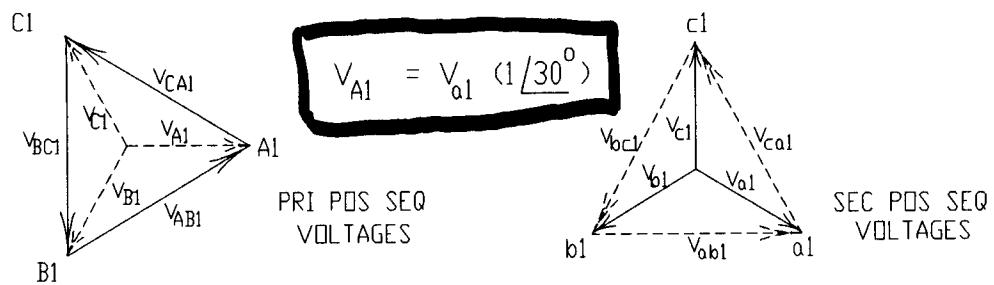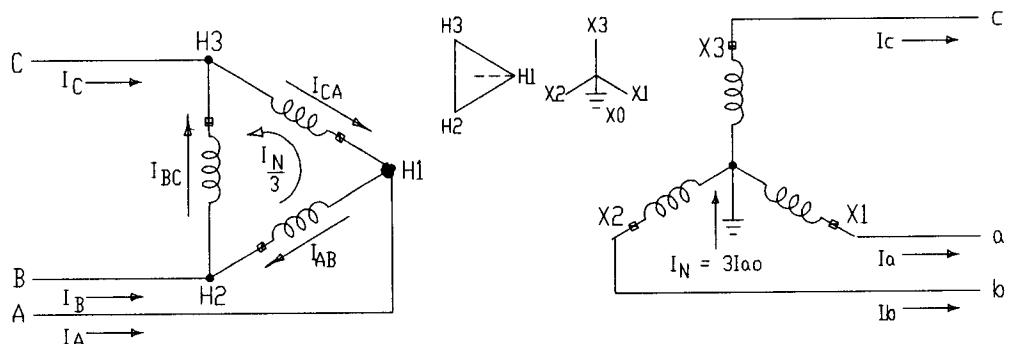

ANSI STANDARD 30-DEGREE SHIFT DELTA-WYE

5

$$\tilde{V}_P \tilde{I}_P^* = \tilde{V}_S \tilde{I}_S^*$$



AUTO-TRANSFORMERS

$$\begin{aligned}
 \tilde{V}_P \tilde{I}_P^* &= \tilde{V}_S \tilde{I}_S^* \\
 \tilde{V}_{\text{pri}} \tilde{I}_{\text{pri}}^* &= \tilde{V}_{\text{sec}} \tilde{I}_{\text{sec}}^* \\
 \tilde{V}_{\text{sec}} &= \tilde{I}_S + \tilde{I}_{\text{com}} \\
 \tilde{V}_{\text{sec}} &= \tilde{I}_{\text{sec}} + \tilde{V}_{\text{load}}
 \end{aligned}$$




Primary voltage \tilde{V}_{pri} and secondary voltage \tilde{V}_{sec} .

6

- Auto: transform more VA for same coil ratings (i.e. cheaper than 2-winding)
- 2-winding provides isolation between pri-sec.


- Auto doesn't.

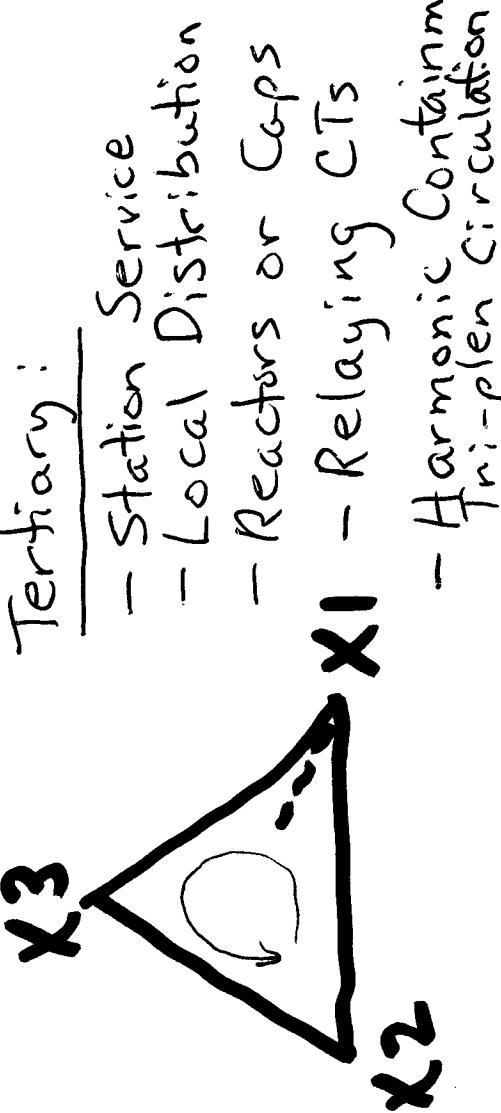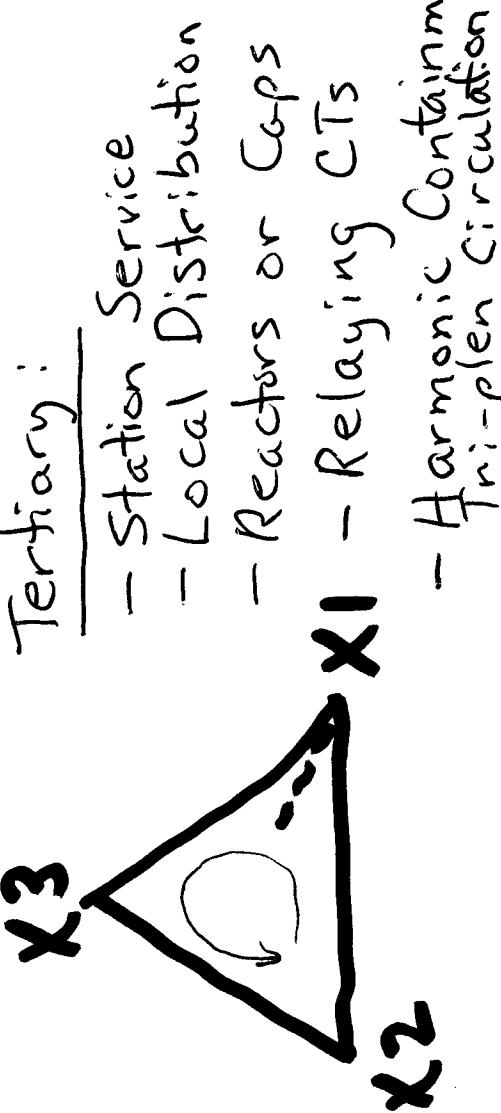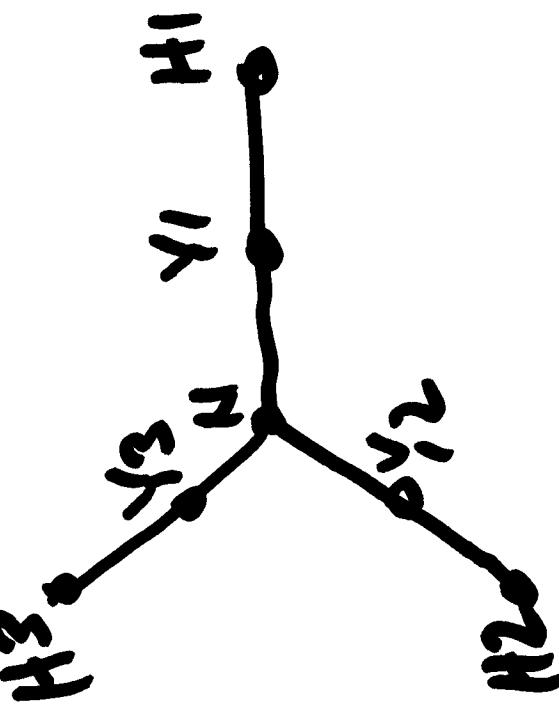- Auto transformer: no phase shift for 3-ph applications.



7

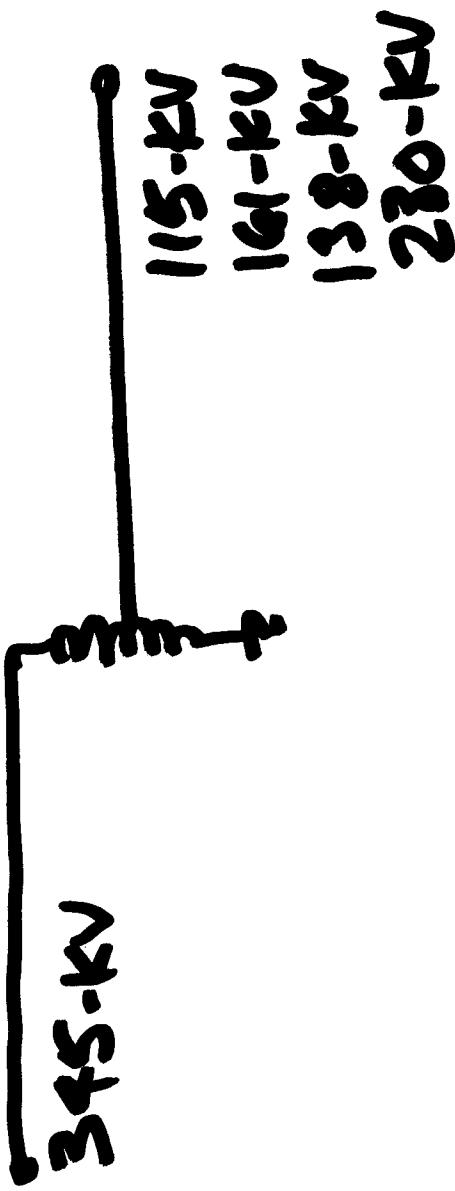
- Autotransformers usually limited to $\leq 3:1$ voltage ratio.
(Leakage impedance)



"VOLT-AMP ADVANTAGE"

$$\text{Ratio of } \frac{\text{VA}_{\text{Auto}}}{\text{VA}_{\text{2-winding}}} = \text{VA Advantage}$$

8

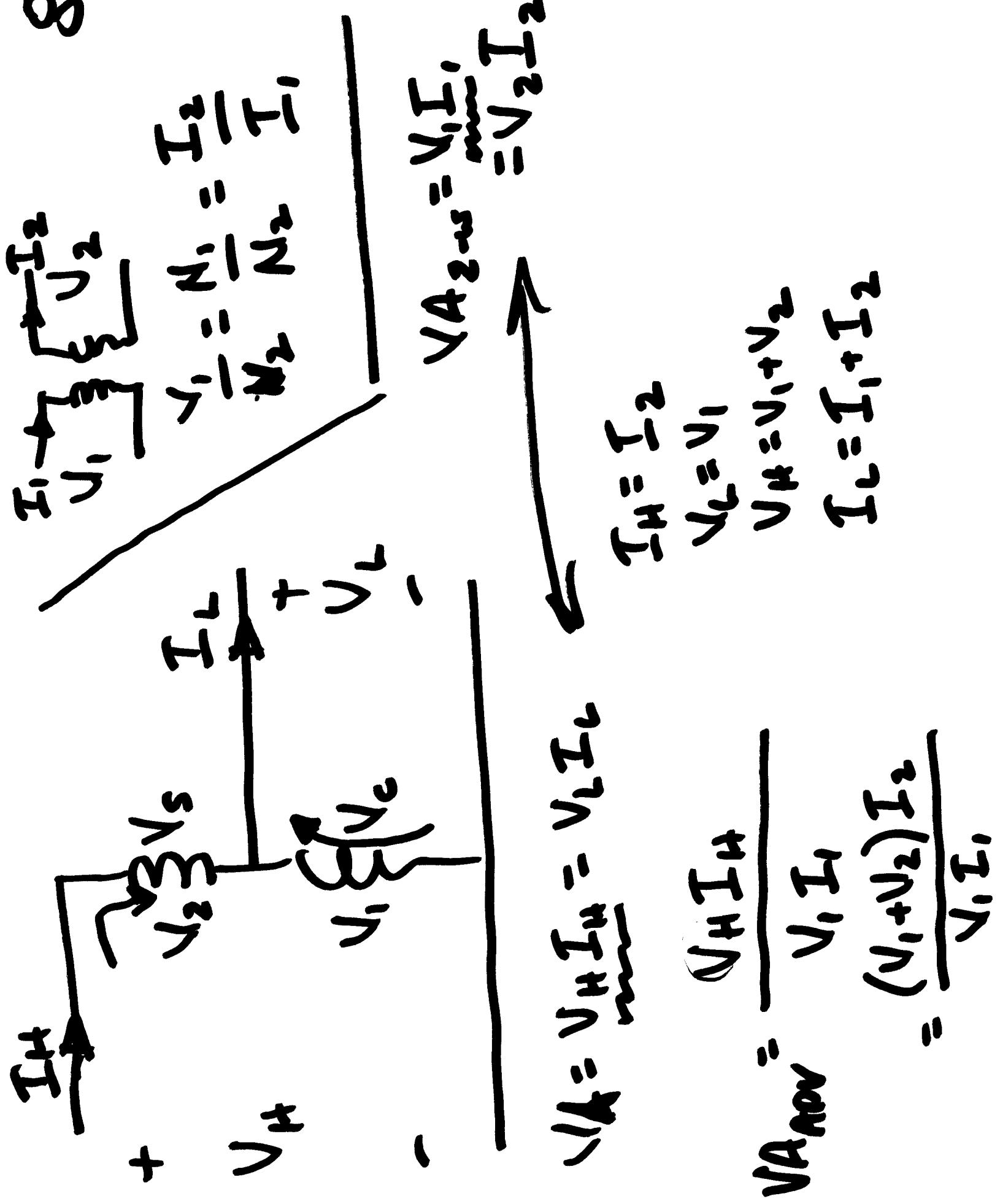


9

$$\frac{(V_1 + V_2)}{V_2} = \frac{\frac{V_1}{A_1} + \frac{V_2}{A_2}}{V_2}$$

VOLT-AMP>
ADVANTAGE

TAP-CHANGERS (LTC)

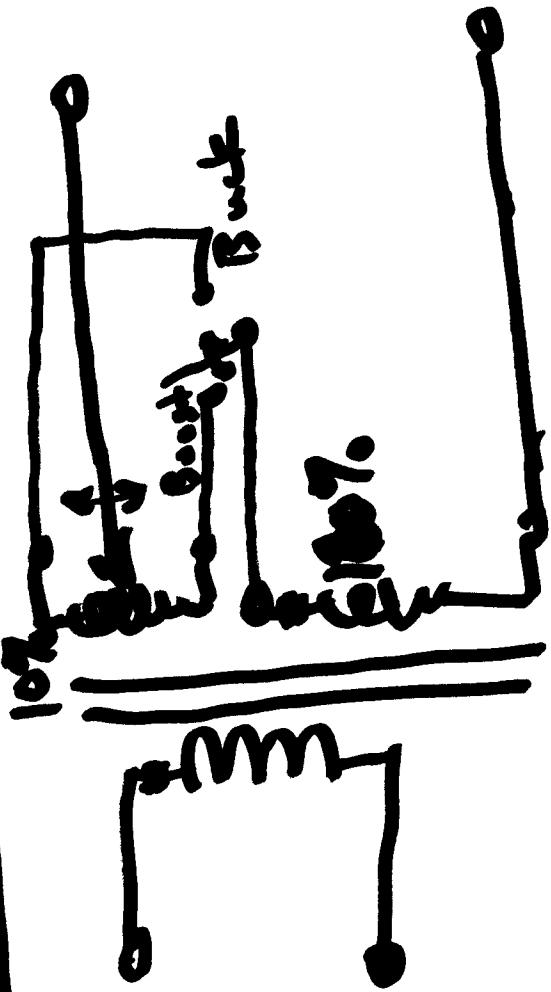

→ "Posistor" or "burst"
Nominal voltage
by 10% .



Thus: $V_{\text{nominal}} \pm 10\%$
16 tap positions
33 total positions
 $5/8\%$ each step.

APPENDIX

A

From
EE 5200 text

TABLE A.1
Typical range of transformer reactances†

Power transformers 25,000 kVA and larger

| Nominal system voltage, kV | Forced-air-cooled, % | Forced-oil-cooled, % |
|----------------------------|----------------------|----------------------|
| 34.5 | 5-8 | 9-14 |
| 69 | 6-10 | 10-16 |
| 115 | 6-11 | 10-20 |
| 138 | 6-13 | 10-22 |
| 161 | 6-14 | 11-25 |
| 230 | 7-16 | 12-27 |
| 345 | 8-17 | 13-28 |
| 500 | 10-20 | 16-34 |
| 700 | 11-21 | 19-35 |

† Percent on rated kilovoltampere base. Typical transformers are now designed for the minimum reactance value shown. Distribution transformers have considerably lower reactance. Resistances of transformers are usually lower than 1%.