

Topics for Today:


- Startup
 - Web page: <https://pages.mtu.edu/~bamork/ee5220/>
 - Book, references, syllabus, more are on web page.
 - Software - Matlab. ATP/EMTP [License - www.emtp.org]
 - **ATP tutorials posted on course web page. DO THEM!**
 - Circuit analysis tutorials posted, “Pre-Req Material”
 - EE5220-L@mtu.edu (participation = min half letter grade)
- HW#3 probs 3.2, 3.3, 3.4, 3.6, 3.12 due Tues Jan 30th.
- ATP Simulation pointers
- Cap Bank Switching (continued)
 - First (single) bank energization
 - Back-to-back switching
 - Outrush
 - TRV
 - Voltage Magnification

ATP Pointers

Your simulation circuit from *.acp file and PlotXY plot of *.pl4 file can be easily pasted into a .doc file for homework or writing a report.

Circuit diagram:

- Select/drag window around circuit diagram
- File > Save metafile (.wmf format)
- Insert graphics/file into your .docx file.

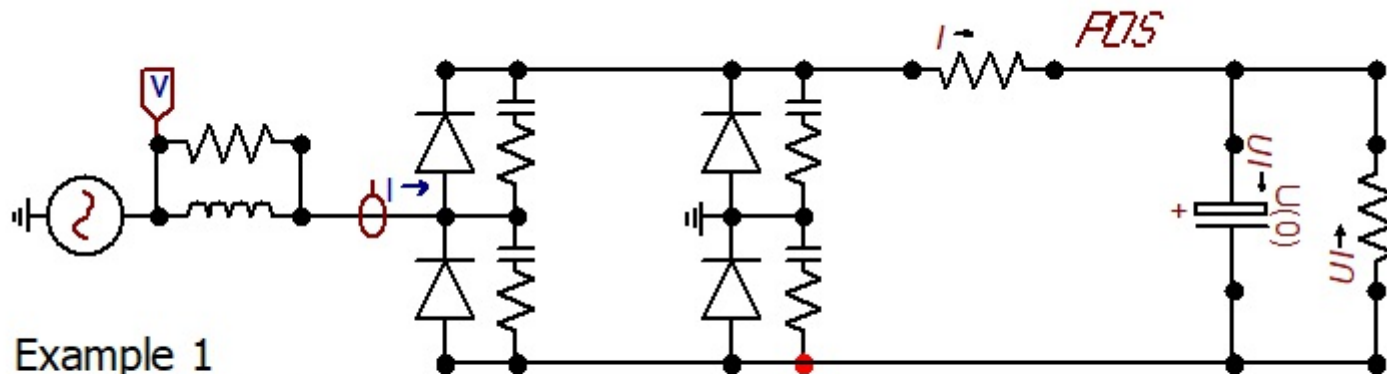


Example 1
Your first circuit
Rectifier bridge


What is the difference between vector graphics (.wmf) and raster/dot (.bmp)?

Plot file from PlotXY:

Copy plot into clipboard (lower right corner of Plot Window).

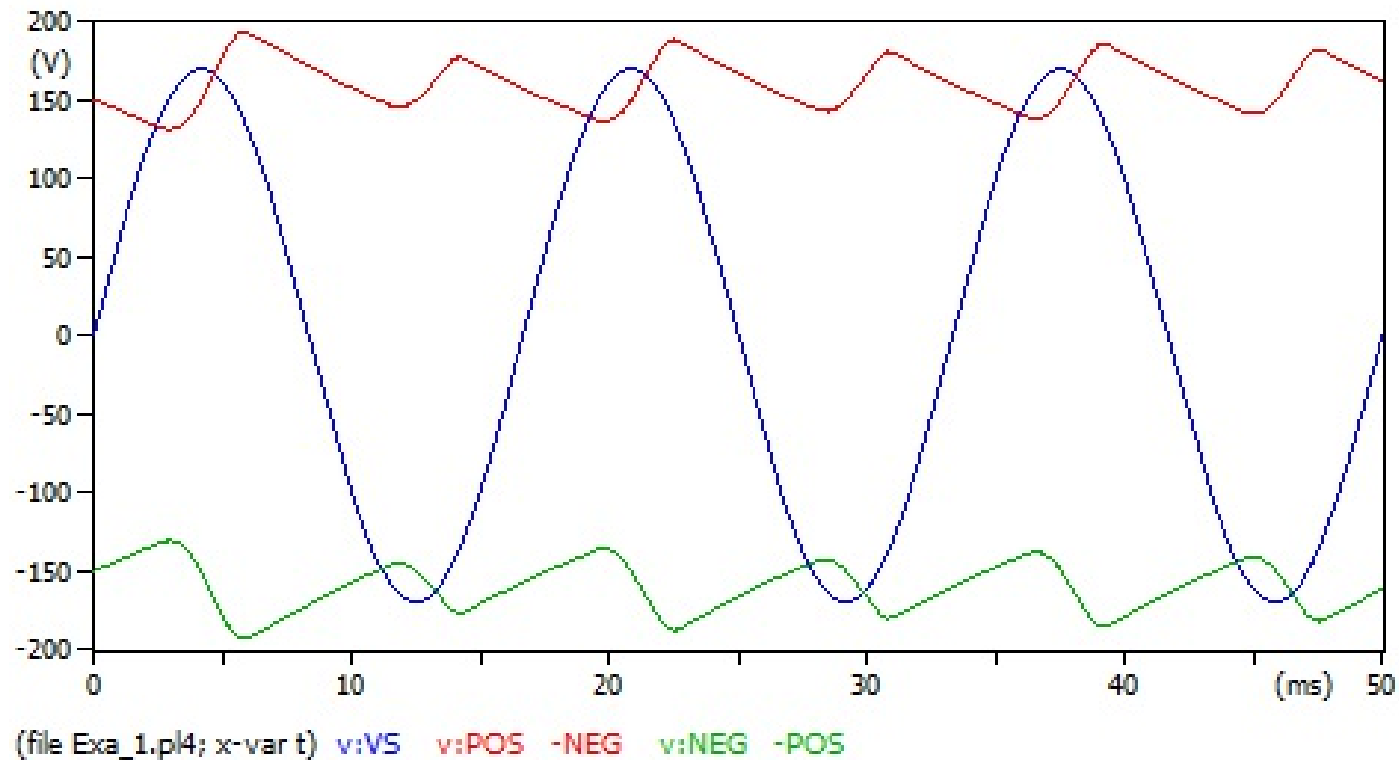Paste into your .docx file. This will be a bit-map file, low resolution. Can also save as *.svg (Scalable Vector Graphics, similar to metafile *.wmf) or *.png (raster/dot/pixel graphics).



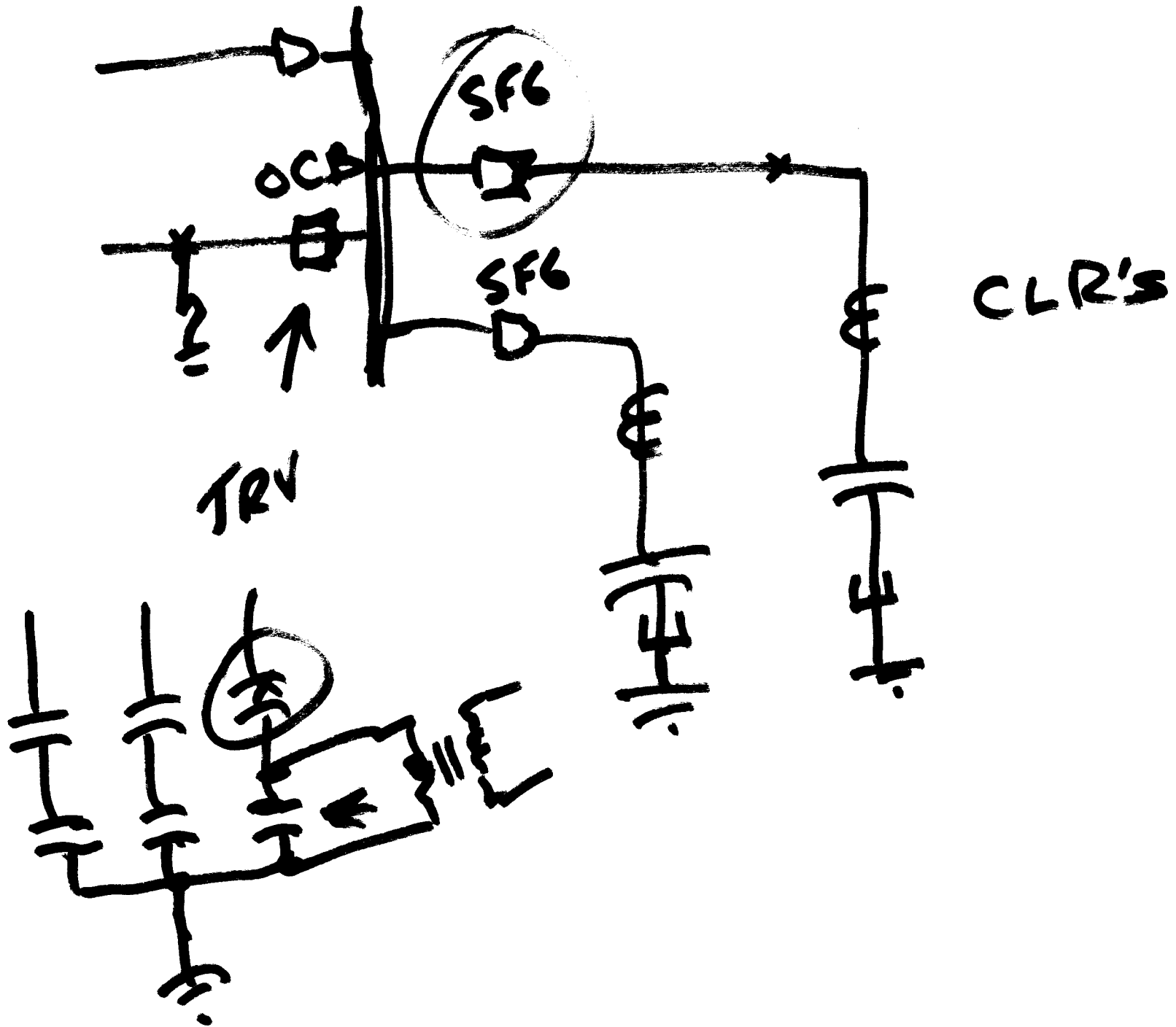


Shunt Cap Banks

- Voltage Support
- Var
- Power Flow



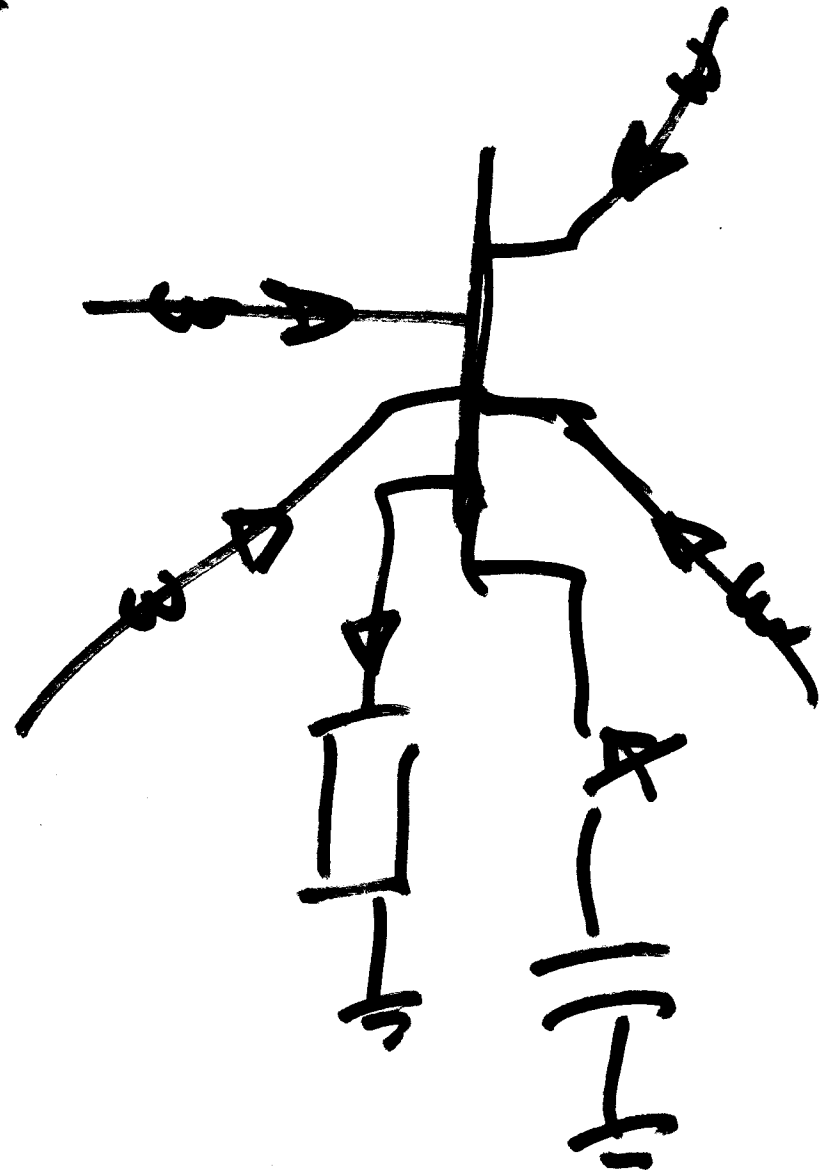
$$P_M = \frac{V_1 V_2}{X} \quad \uparrow \underline{\underline{21\%}}$$




Short Circuit Calcs / Sims

$$\bar{Z}_{33} = Z_{TH}$$

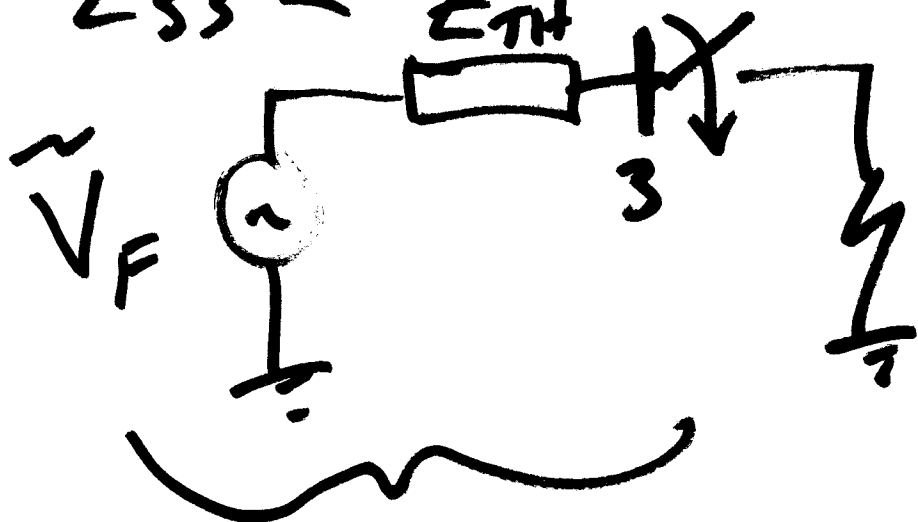


Thev Equiv

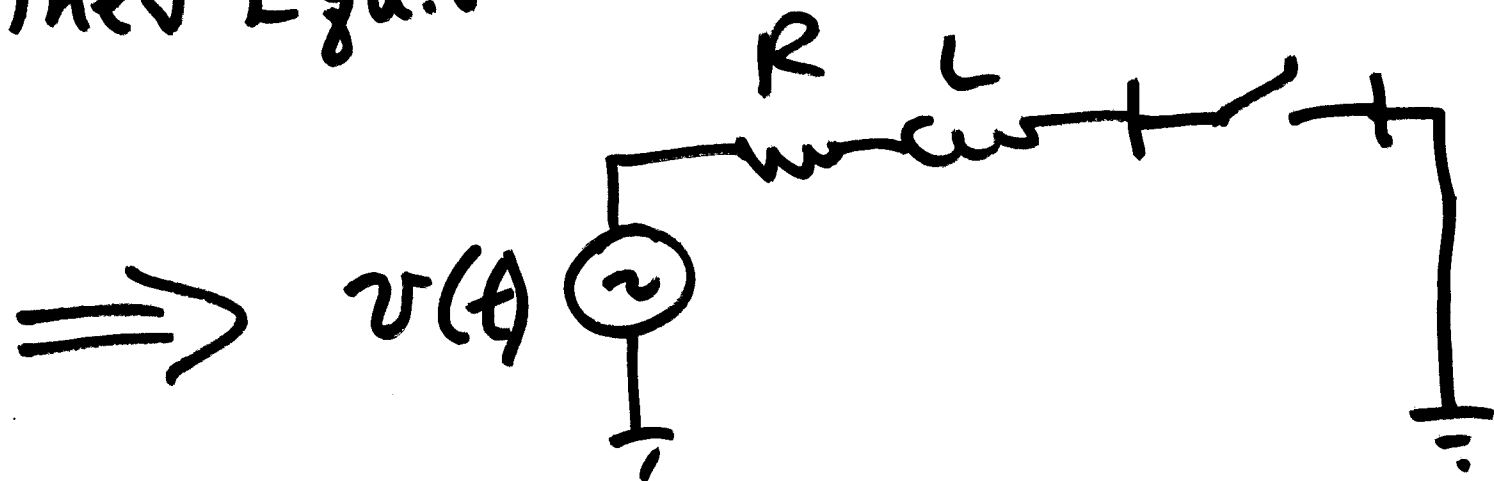



$$v(t) = V_p \cos(\omega t + \phi)$$



Euler's Identity

CCW rotation

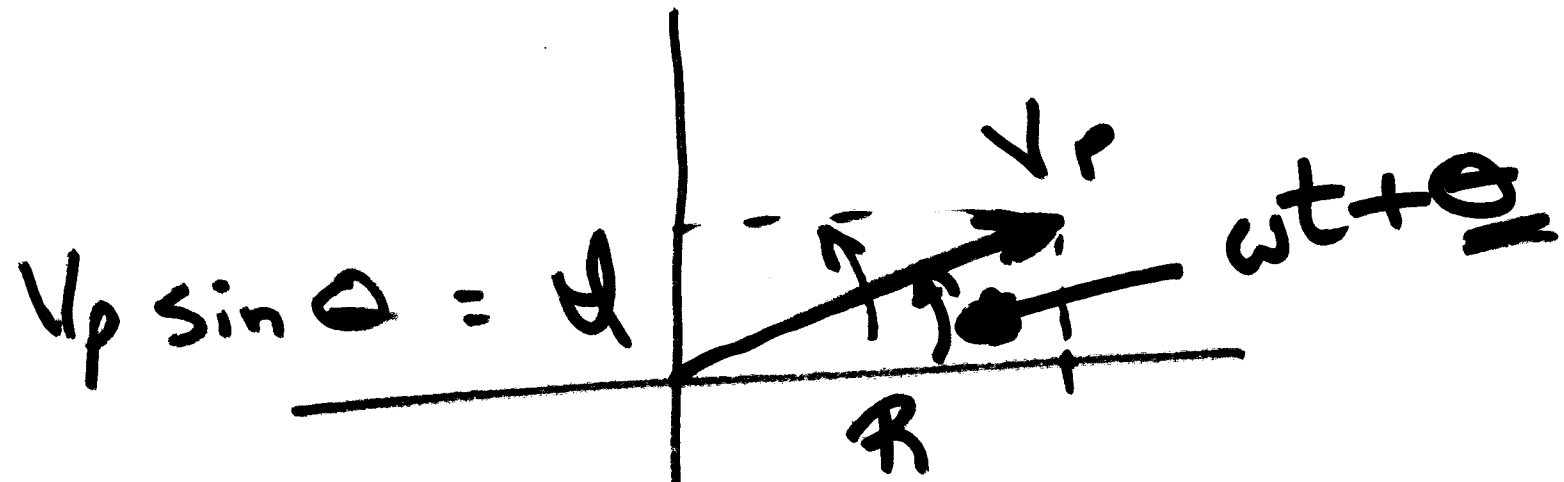


$$R = V_p \cos \theta$$

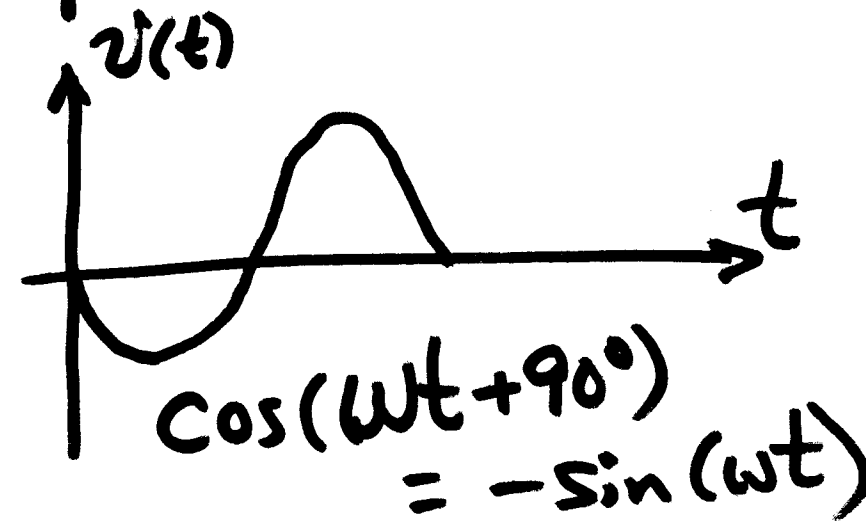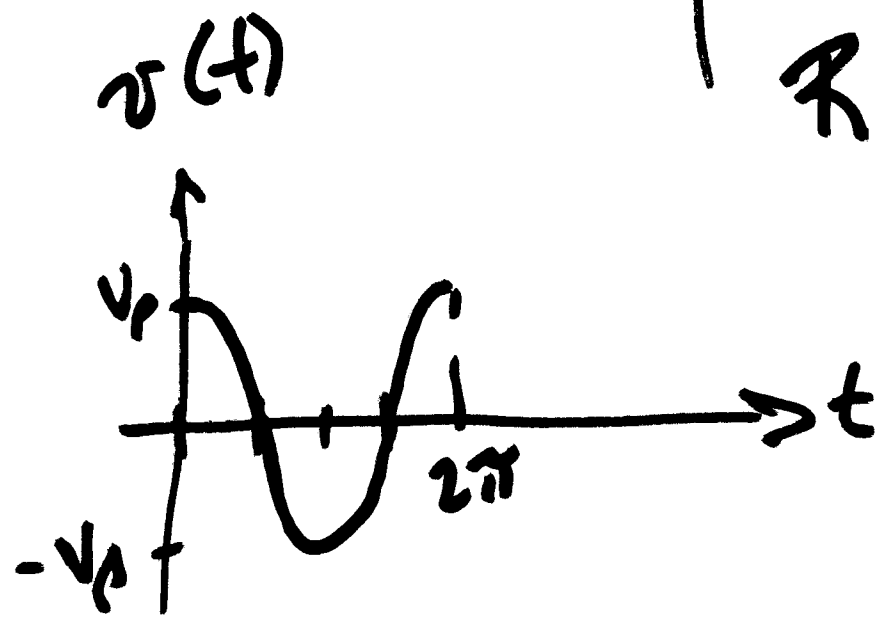


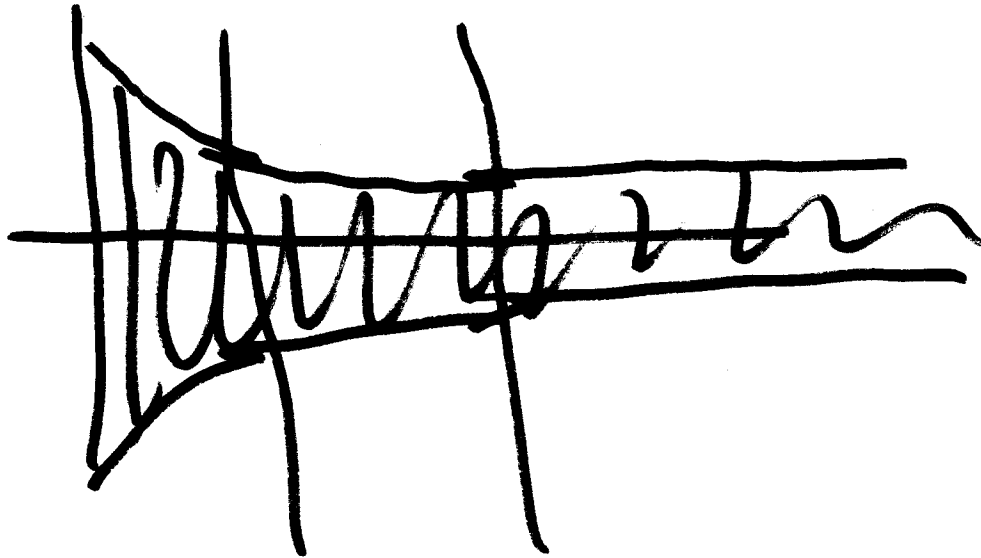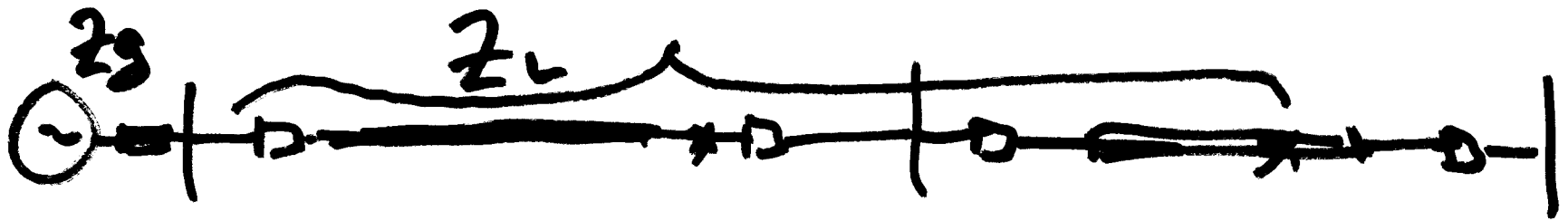


$$Z_g \approx Z_L$$

$$Z_L \gg Z_g$$


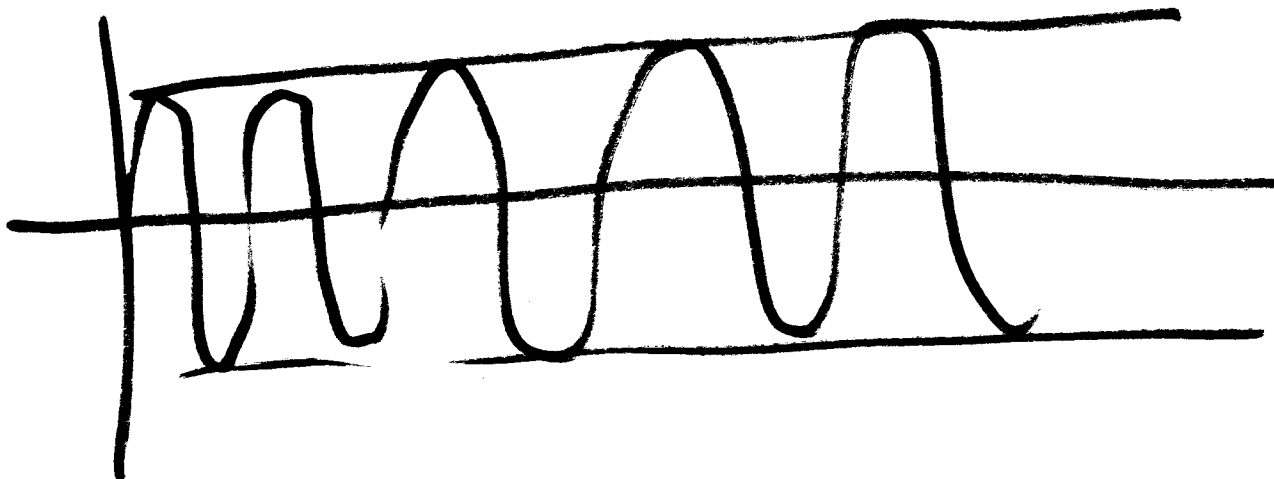


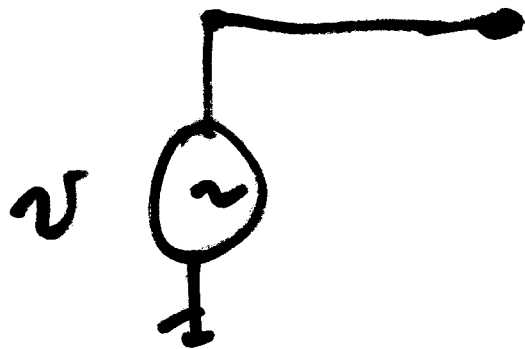


$T_{start} = 0.0$

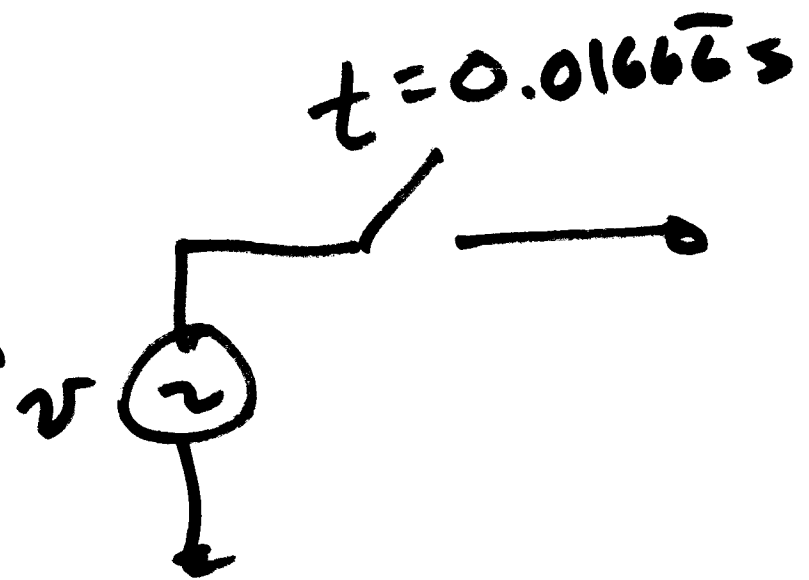

$T_{start} = -1.0$

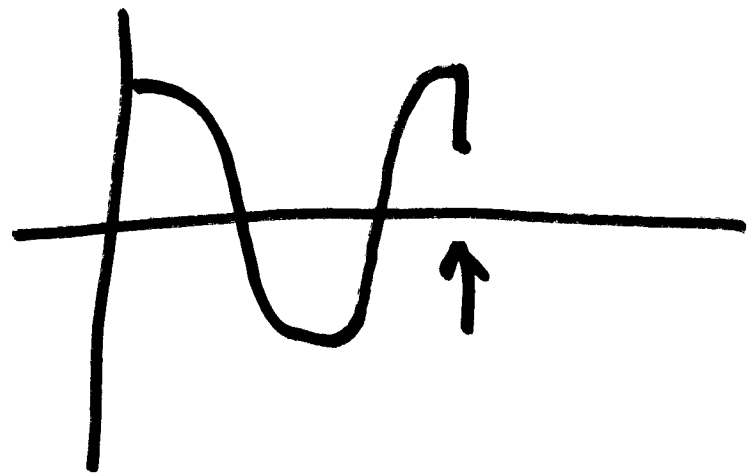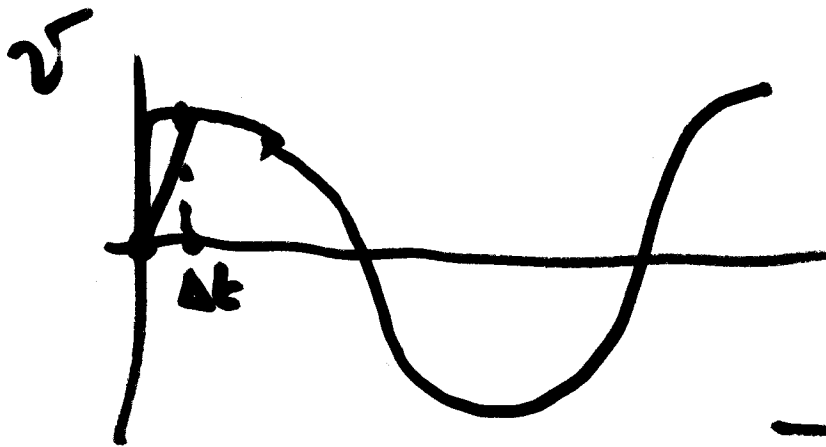


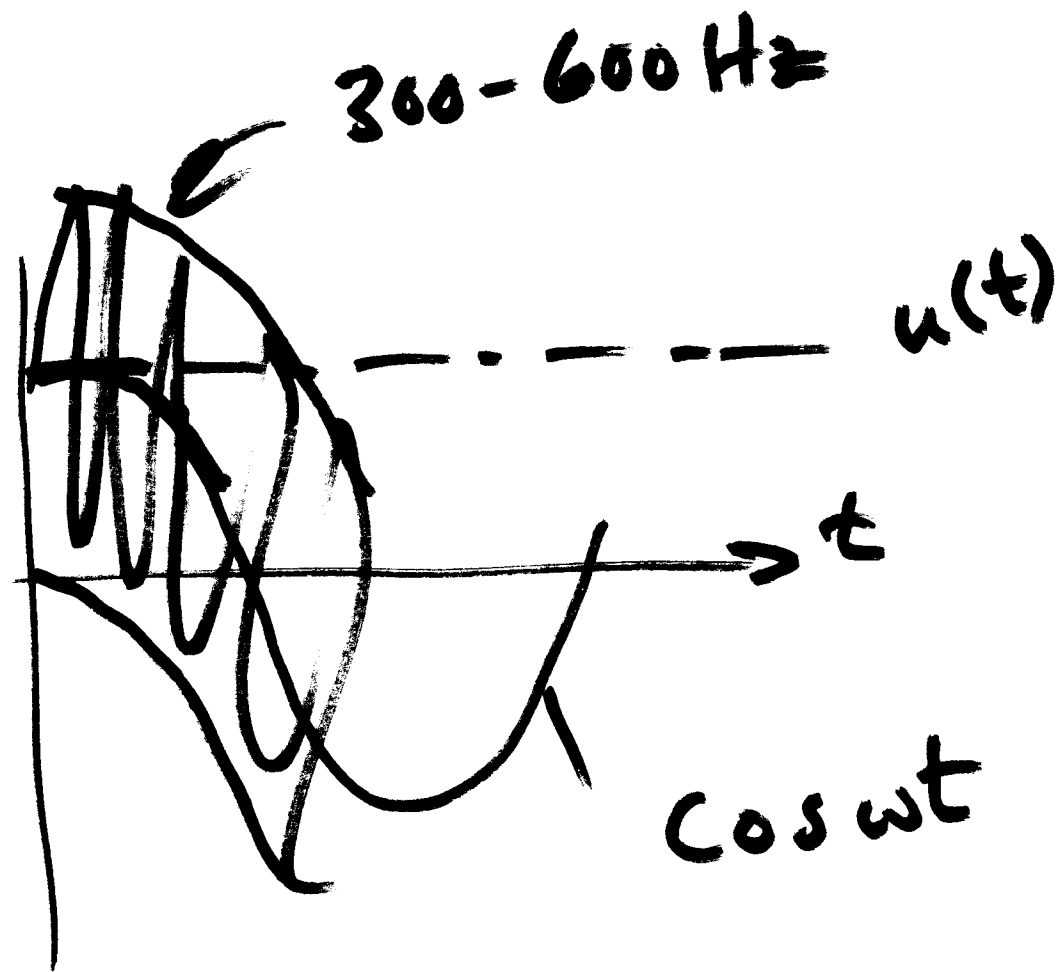

Forced RLC Responses


1

ERLC

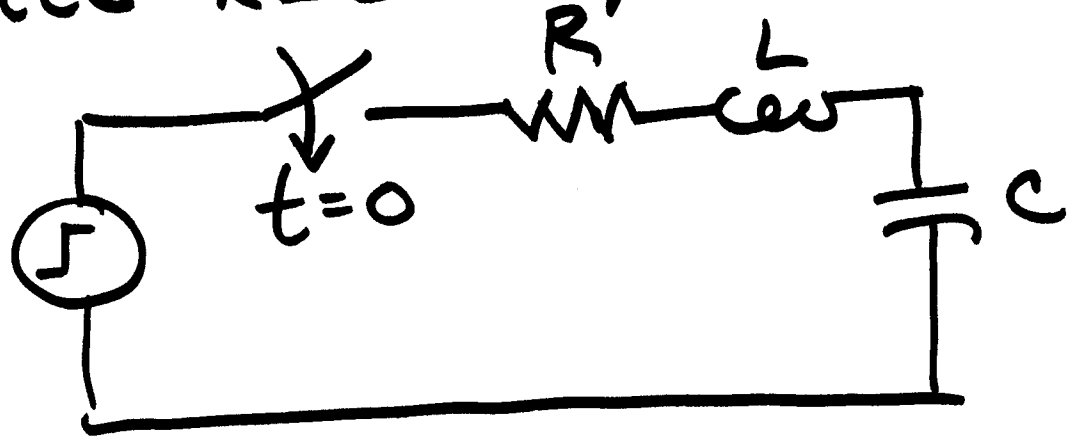

Note: Very similar to

SF-RLC.adp

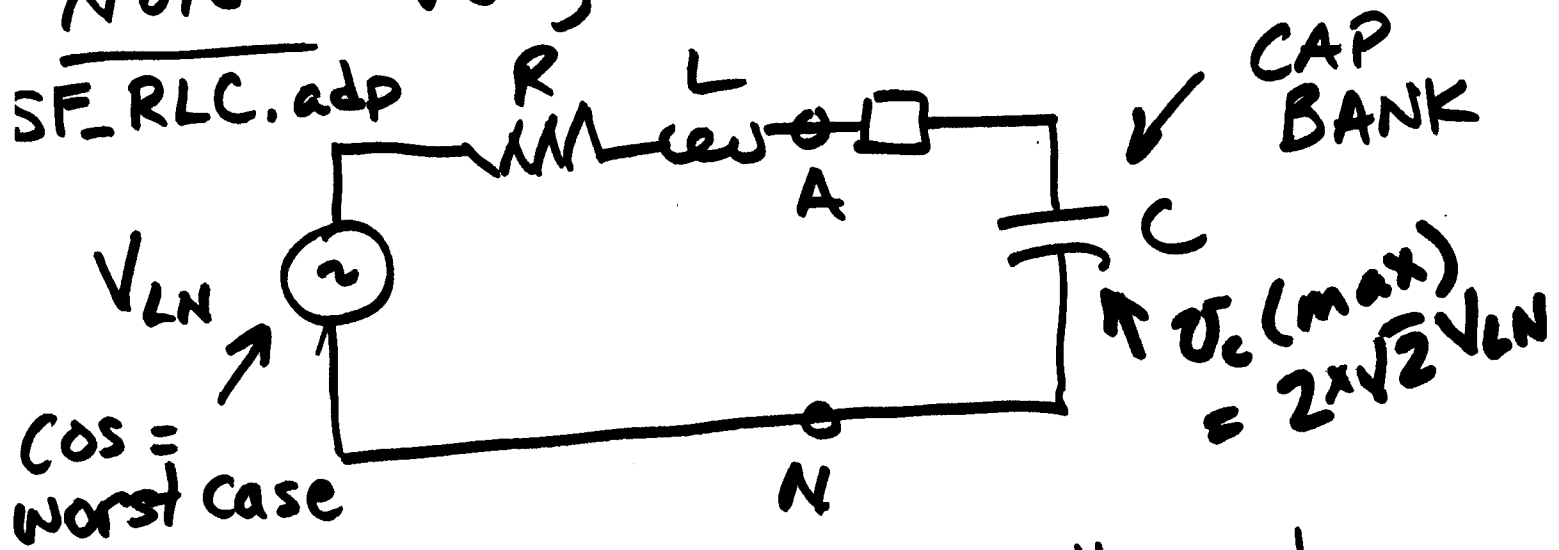



since L is very small and C is sizeable

Then $\omega_0 \gg 377$

Then we can assume that

$i_p \cos 377t$ \Leftrightarrow V_p

PARALLEL RLC - SERIES RLC ²

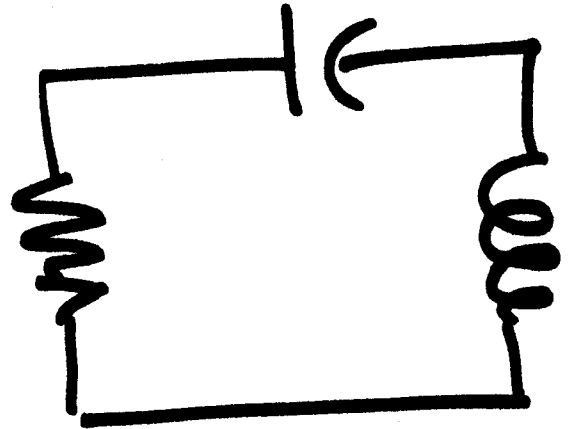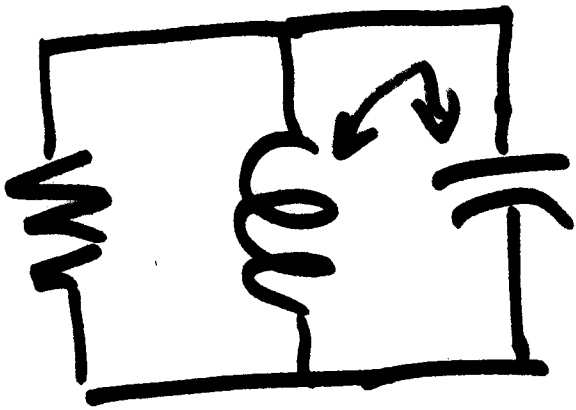

Resonant freq:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Exponential Damping Coefficient
(or Neper freq)

$$\alpha = \frac{1}{2RC}$$

$$\alpha = \frac{R}{2L}$$

Damped or "Natural" Resonant freq

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Damping:


3

Critical Damping: $\alpha = \omega_0$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 0$$

Overdamped:

$$\alpha > \omega_0$$

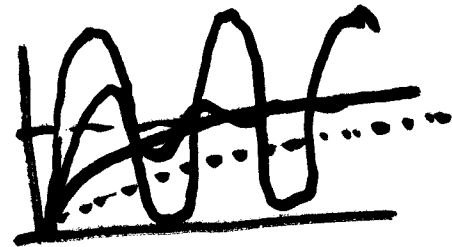

Underdamped:


$$\omega_0 > \alpha$$

Undamped: $\alpha = 0$


$$\omega_d = \omega_0$$

Look at series RLC


SER. RLC. adp

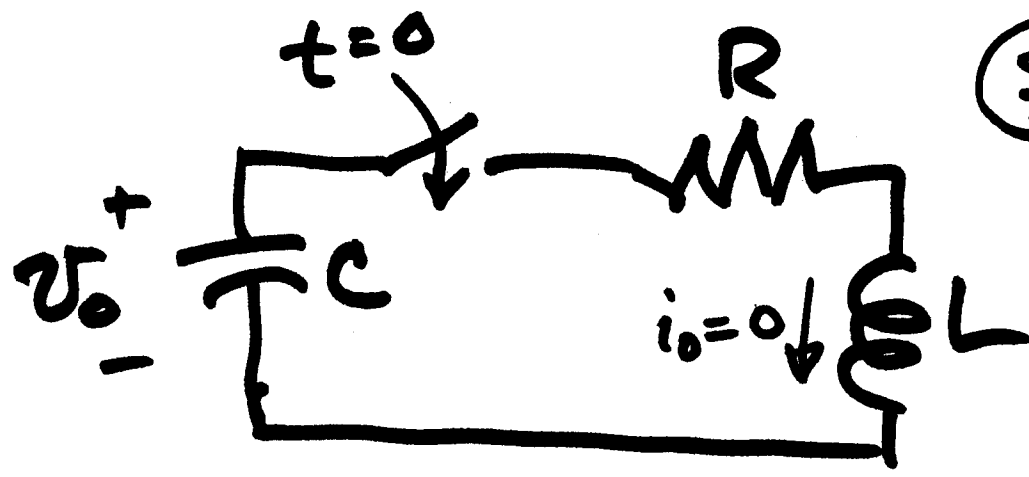

UNDAMPED $R = 0$

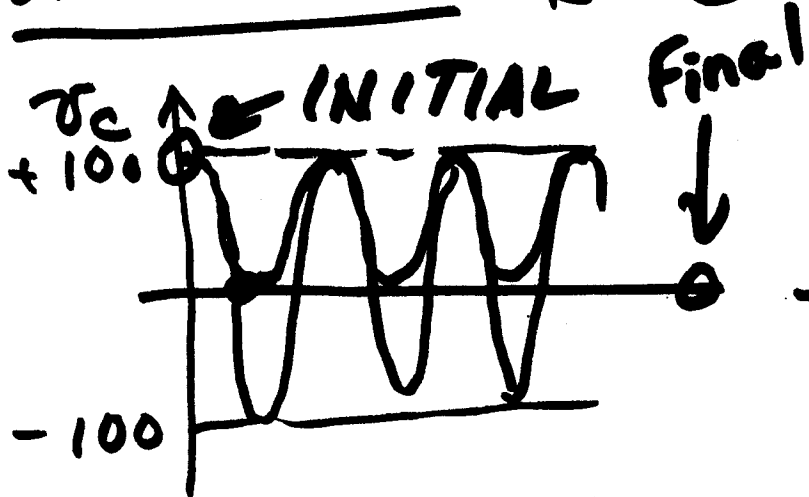

UNDAMPED

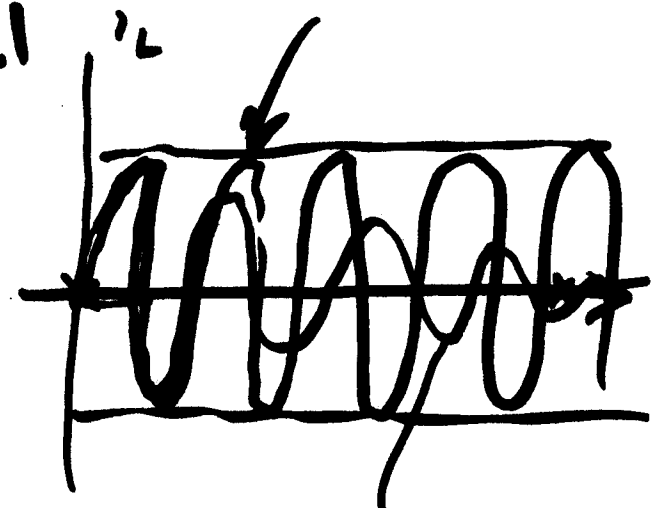

DAMPED

Ex: $L = 10 \text{ mH}$
 $C = 1 \mu\text{F}$
 $R \approx 0$

② $\omega_0 = 10,000 \text{ s}^{-1}$
 $f = \approx 1591 \text{ Hz}$
 $T = 0.63 \text{ ms}$
 $\Delta t \approx 20 \mu\text{s}$
 $T_{\text{END}} =$

① $Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{.01}{10^{-6}}} = 100 \Omega$

$I_p = \frac{\Delta V}{Z_0}$

Read Ch. 4 - § 4.3 - Damping⁵

Make transition from

$$\alpha, \omega_0, \omega_d$$

to $\boxed{s = \sigma + j\omega}$

~~int~~ in terms of Z_0, R, λ, τ

More on simulation:

Critically damped:

$$\alpha = \omega_0 = \frac{R}{2L}$$

Check: decrease R


$$\alpha = 10,000 = \frac{R}{(2)(.01)}$$

$$\Rightarrow \underline{R = 200 \Omega}$$


$$R = 190 \Omega \Rightarrow \alpha = \frac{R}{2L}$$
$$= \frac{190}{(2)(.01)}$$
$$= 9500$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$
$$= \sqrt{10,000^2 - 9500^2} = 3122 \text{ s}^{-1}$$
$$= 497 \text{ Hz}$$
$$T = 2 \text{ ms}$$

$R = 10,000 \rightarrow$ overdamped

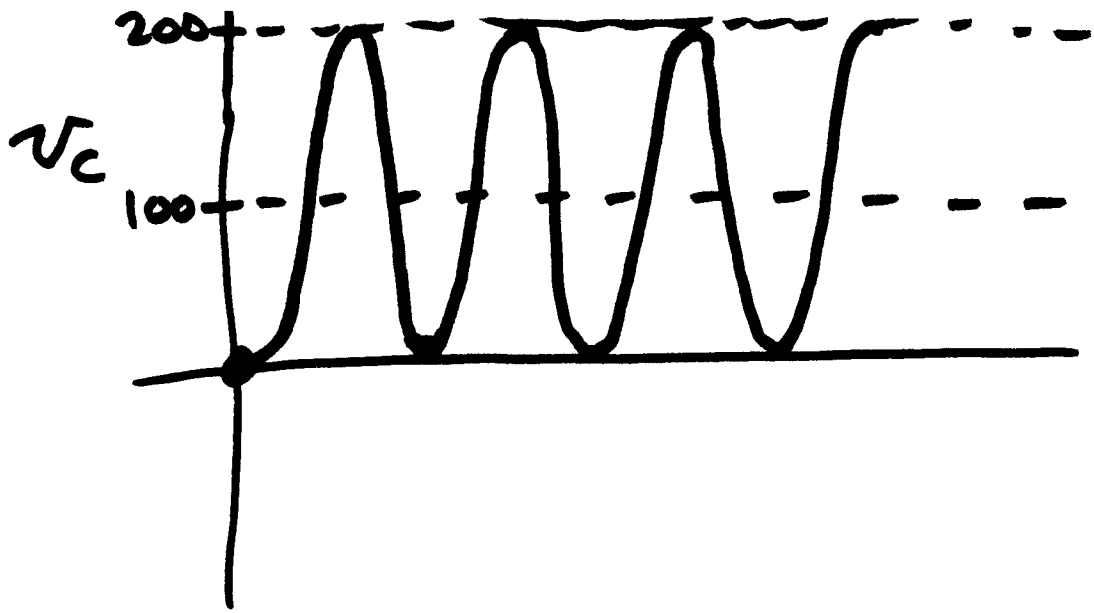

8

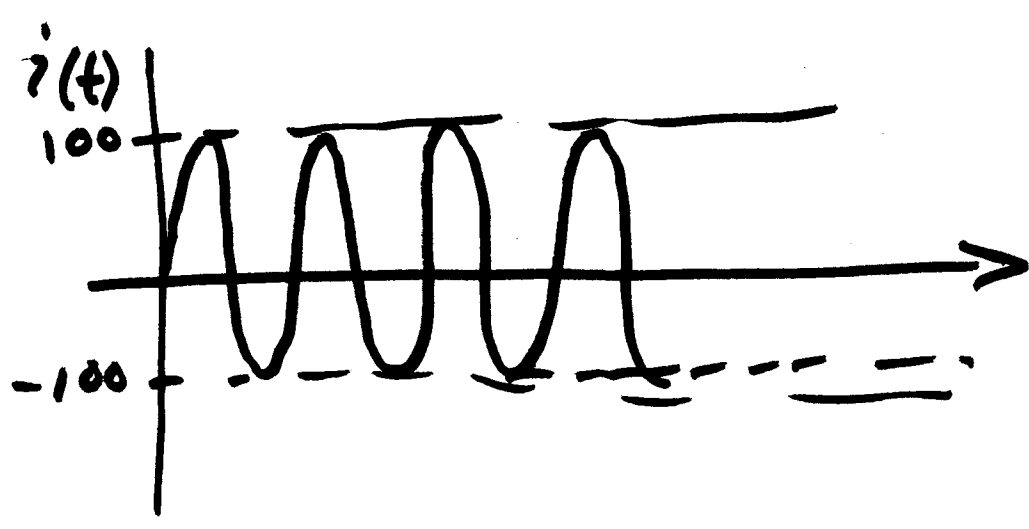

If $\frac{X}{R}$ ratio is 10, then


$$R = \frac{X}{10} = \frac{377L}{10} = \underline{\underline{0.377\Omega}}$$

CAP BANK SWITCHING

2

- 1 - Energization Inrush - Bus OV
- 2 - Back-to-Back Energization
- 3 - Outrush ← $\xrightarrow{\text{HF I}}$ thru CBS.
- 4 - Voltage Magnification
- 5 - TRV - Transient Recovery Voltage

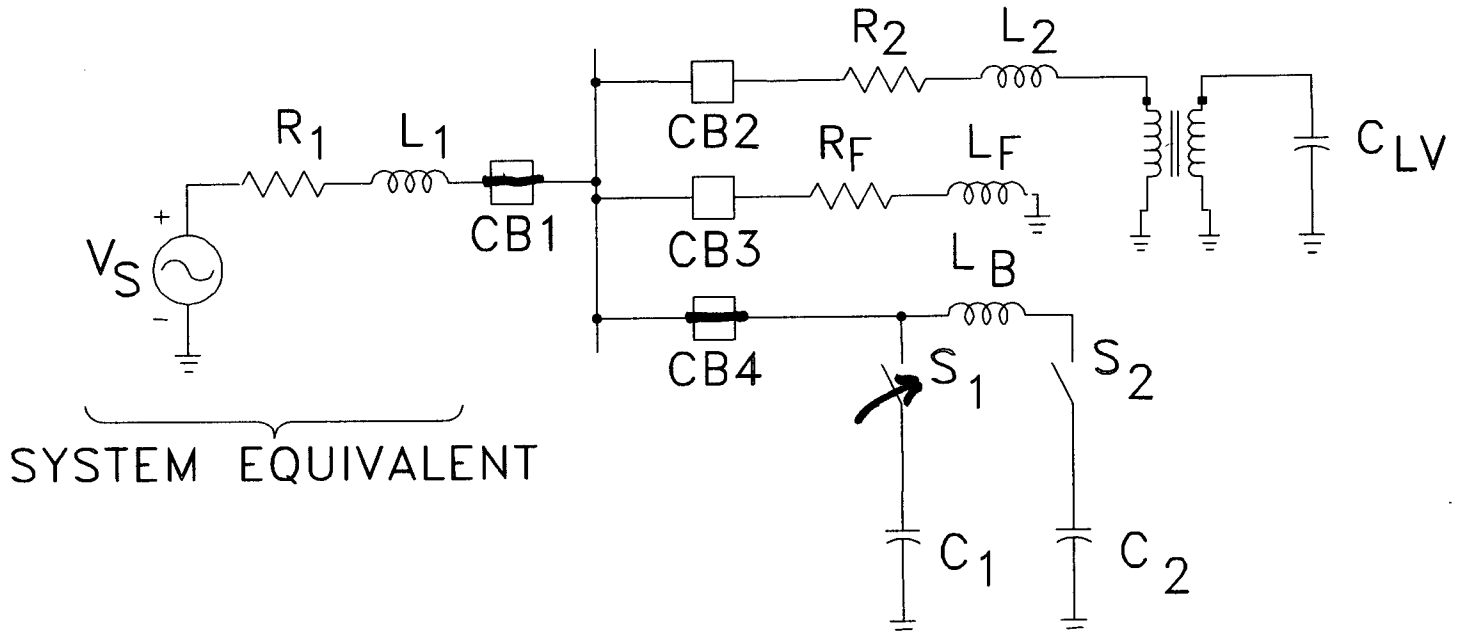Sample 34.5-kV system, developed from Fig. 3.4 in Greenwood.



$R_1 = 0.5 \text{ Ohms}$

$L_1 = 3 \text{ mH}$

$R_2 = 0.001 \text{ Ohms}$

$L_2 = 12 \text{ mH}$

$C_1 = 40.1 \mu\text{F}$ (18 MVAR)

$C_2 = 22.3 \mu\text{F}$ (10 MVAR)

$C_{LV} = 601 \mu\text{F}$

Dist. Transformer: 4:1 ratio

$L_B = 19 \mu\text{H}$

$C_{BUSH} = 300 \text{ pF}$ (see p.437)


①

Inrush - CB1 - Closed
 CB4 - Closed
 SW1 - Closing

Typical: $0.2 - 0.4 \mu\text{H}/\text{ft}$


Tube Bus


Strain Bus

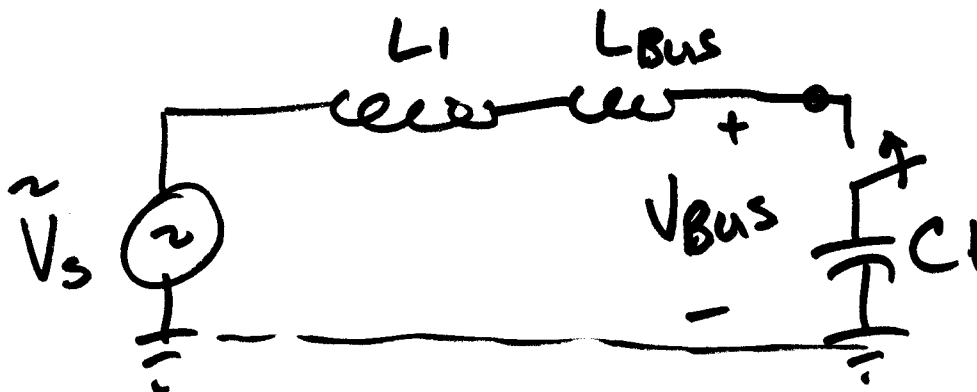

@ $t = 0^+$
 $V_{Bus} \downarrow 0\text{V}$

VOLT MAG

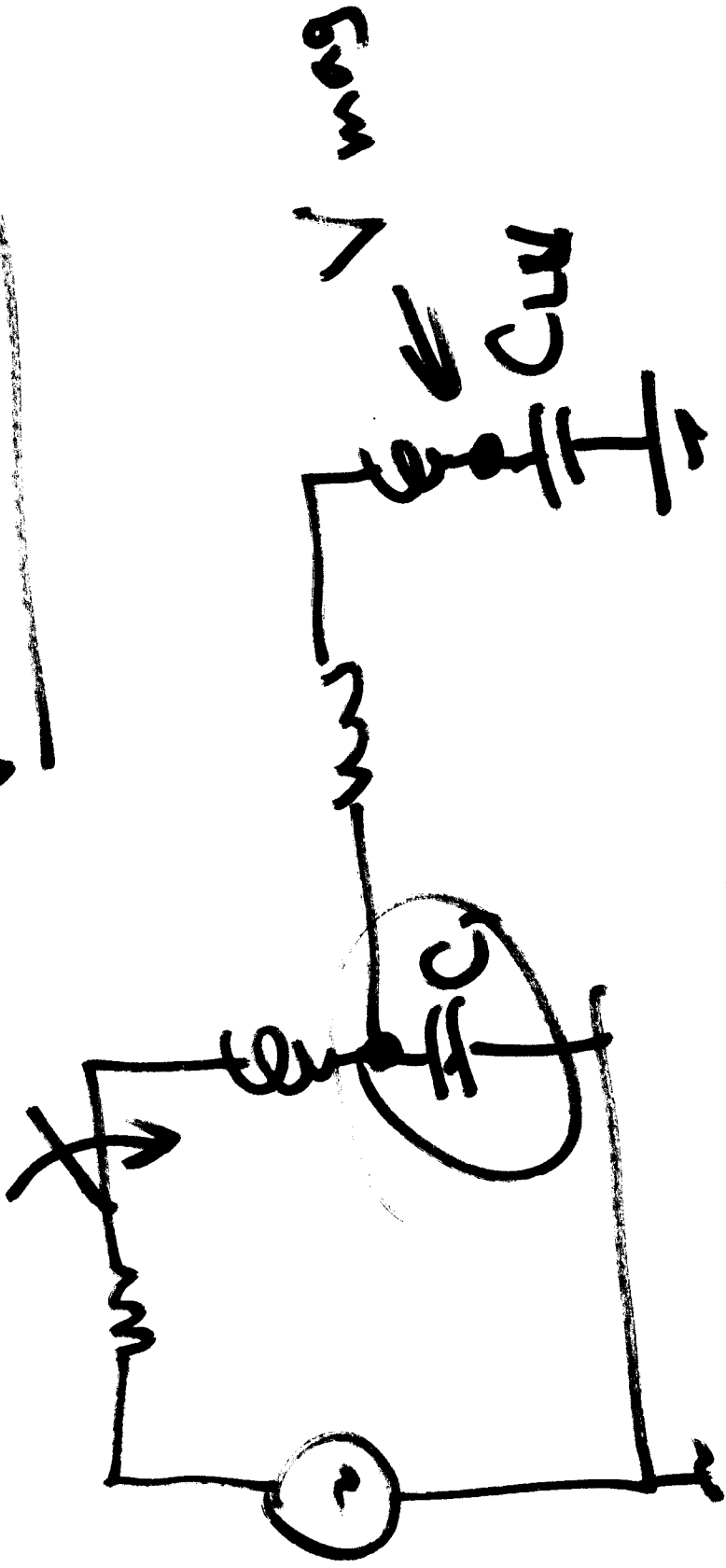

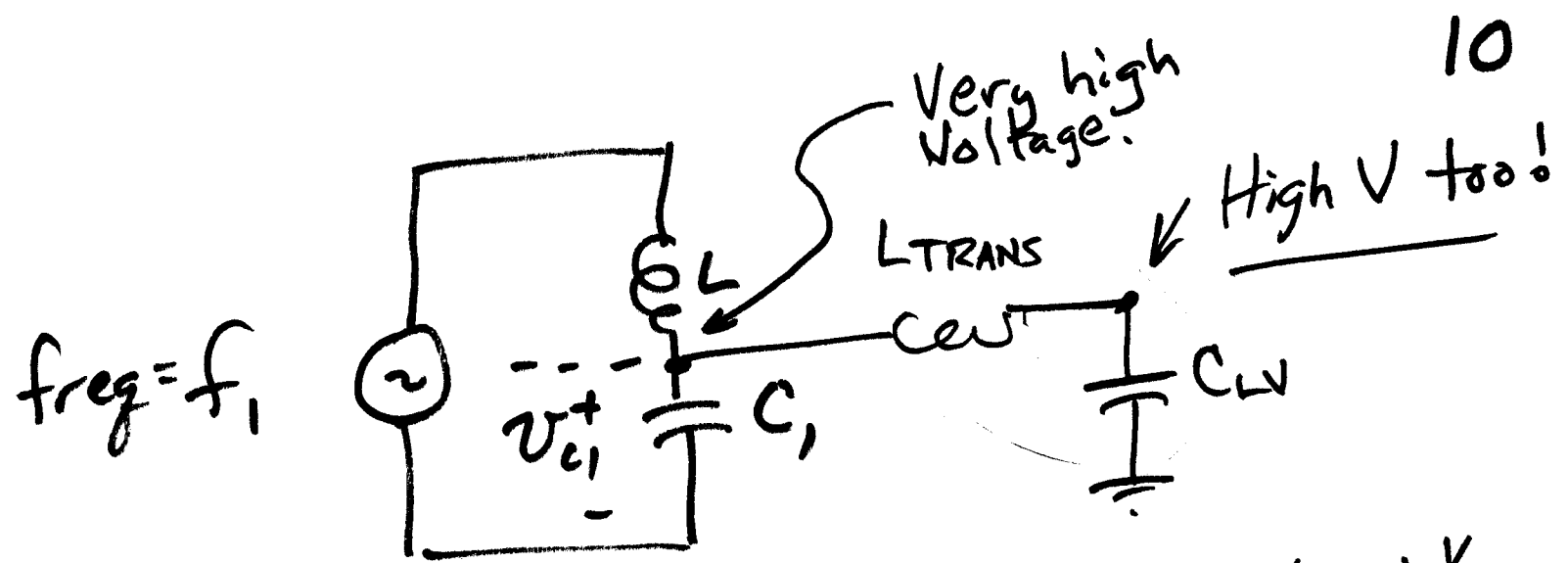

Series resonance: $Z_{TOT} = jX_L - jX_C$

$$X_L = X_C = 0$$

$$I \rightarrow \infty$$

$$V_L \rightarrow \infty$$

$$V_C \rightarrow \infty$$

$$2\pi f_1 L = \frac{1}{2\pi f_1 C_1}$$

Per Unit voltage at C_{2V} is higher than at C_1 , thus the name "voltage magnification."