

EE 5220 - Lecture 8+9 (over 2 days)


Wednesday Jan 26, 2022
Friday Jan 28, 2022

Topics for Today:

- Startup
- Web page: <https://pages.mtu.edu/~bamork/ee5220/>
- Book, references, syllabus, more are on web page.
- Software - Matlab. ATP/EMTP [License - www.emtp.org]
ATP tutorials posted on our course web page
- EE5220-L@mtu.edu (participation = half letter grade, 5%)

- Next week focus: Get up to speed with ATP!
- HW#4 updated/posted soon. Partnered. Due Tues Feb 15th.
- ATP Simulation pointers
- Cap Bank Switching (continued)
 - Back-to-back switching
 - Outrush
 - TRV
 - Voltage Magnification
- Discussion - how to carry out HW#4

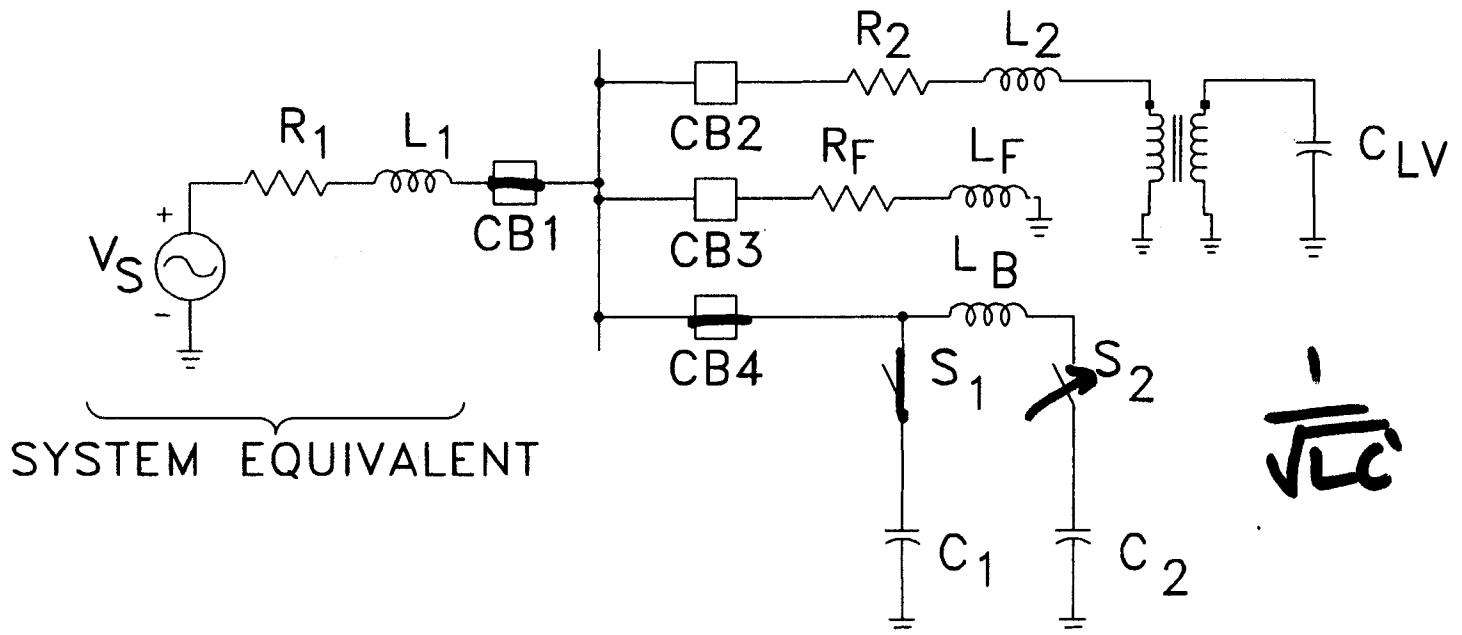
Sample 34.5-kV system, developed from Fig. 3.4 in Greenwood.



- $R_1 = 0.5 \text{ Ohms}$ $L_1 = 3 \text{ mH}$ $R_2 = 0.001 \text{ Ohms}$ $L_2 = 12 \text{ mH}$
- $C_1 = 40.1 \mu\text{F} (18 \text{ MVAR})$ $C_2 = 22.3 \mu\text{F} (10 \text{ MVAR})$ $C_{LV} = 601 \mu\text{F}$
- Dist. Transformer: 4:1 ratio $L_B = 19 \mu\text{H}$ $C_{BUSH} = 300 \text{ pF} (\text{see p.437})$

Back-to-Back

Operative Circuit:

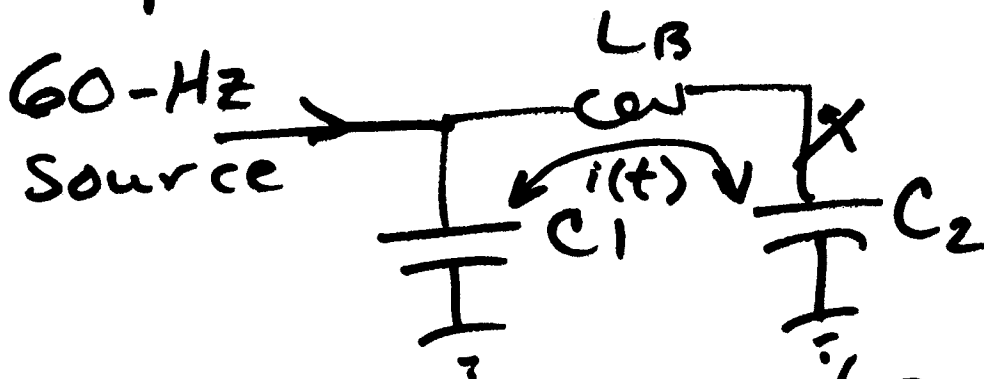


$$\omega_0 = \frac{1}{\sqrt{L_B \cdot \frac{C_1 C_2}{C_1 + C_2}}}$$

$$Z_0 = \sqrt{\frac{L_B}{\frac{C_1 C_2}{C_1 + C_2}}}$$

(Typ f_0 : 3-15 KHz)

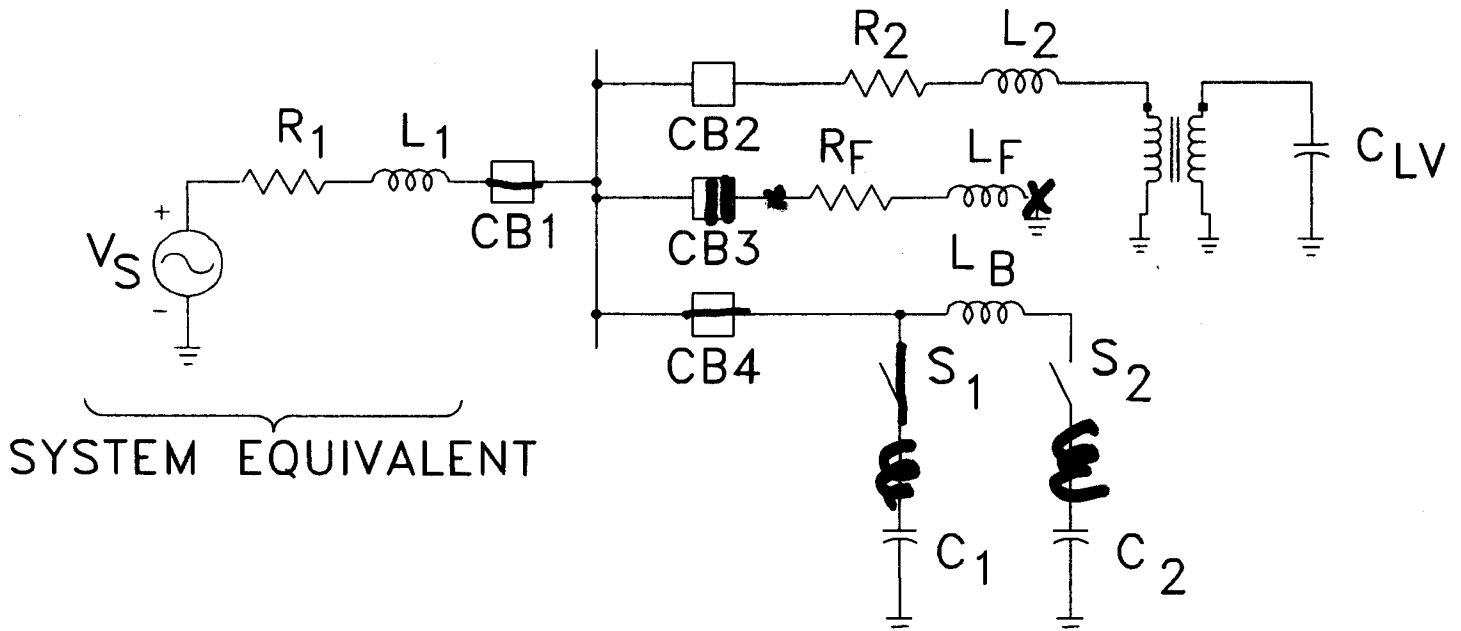Sample 34.5-kV system, developed from Fig. 3.4 in Greenwood.



$R_1 = 0.5 \text{ Ohms}$

$L_1 = 3 \text{ mH}$

$R_2 = 0.001 \text{ Ohms}$

$L_2 = 12 \text{ mH}$

$C_1 = 40.1 \mu\text{F} (18 \text{ MVAR})$

$C_2 = 22.3 \mu\text{F} (10 \text{ MVAR})$

$C_{LV} = 601 \mu\text{F}$

Dist. Transformer: 4:1 ratio


$L_B = 19 \mu\text{H}$

$C_{BUSH} = 300 \text{ pF} \text{ (see p.437)}$

Outrush - Cap banks discharge into nearby fault.
 (Close CB3) CBs may not handle it.

Ratings of CBs: $I_p \times t_0$

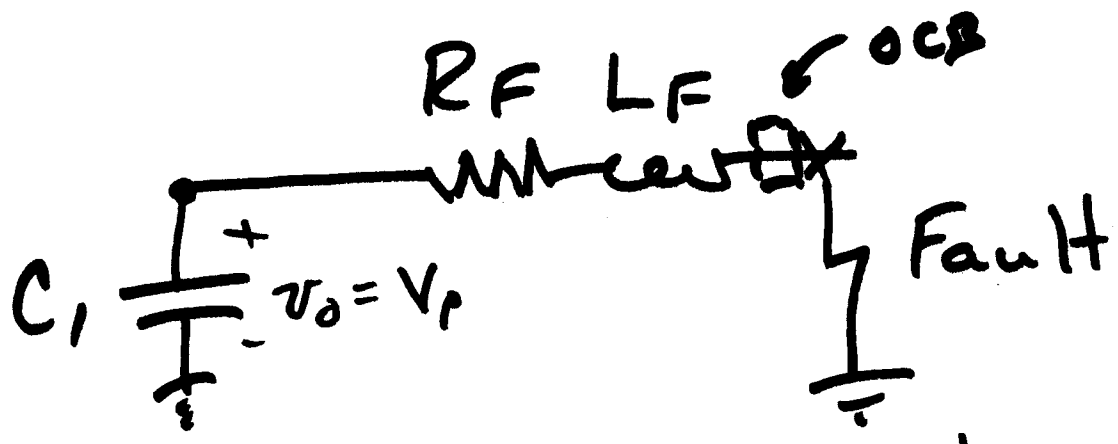- i) General Purpose
 $I_p \times t_0 \leq 2 \times 10^7$
- ii) Definite Purpose:
See IEEE Stds!




$$\omega_0 = \frac{1}{\sqrt{C_1 L_F}} \quad \text{or} \quad \frac{1}{\sqrt{(C_1 + C_2) L_F}}$$

$$Z_0 = \sqrt{\frac{L_F}{C_1}} \quad \text{(one Bank)} \quad \text{or} \quad \sqrt{\frac{L_F}{C_1 + C_2}} \quad \text{(Both Banks)}$$

$$I_p = \frac{V(0)}{Z_0}$$


$I_p \times t_0 = ?$

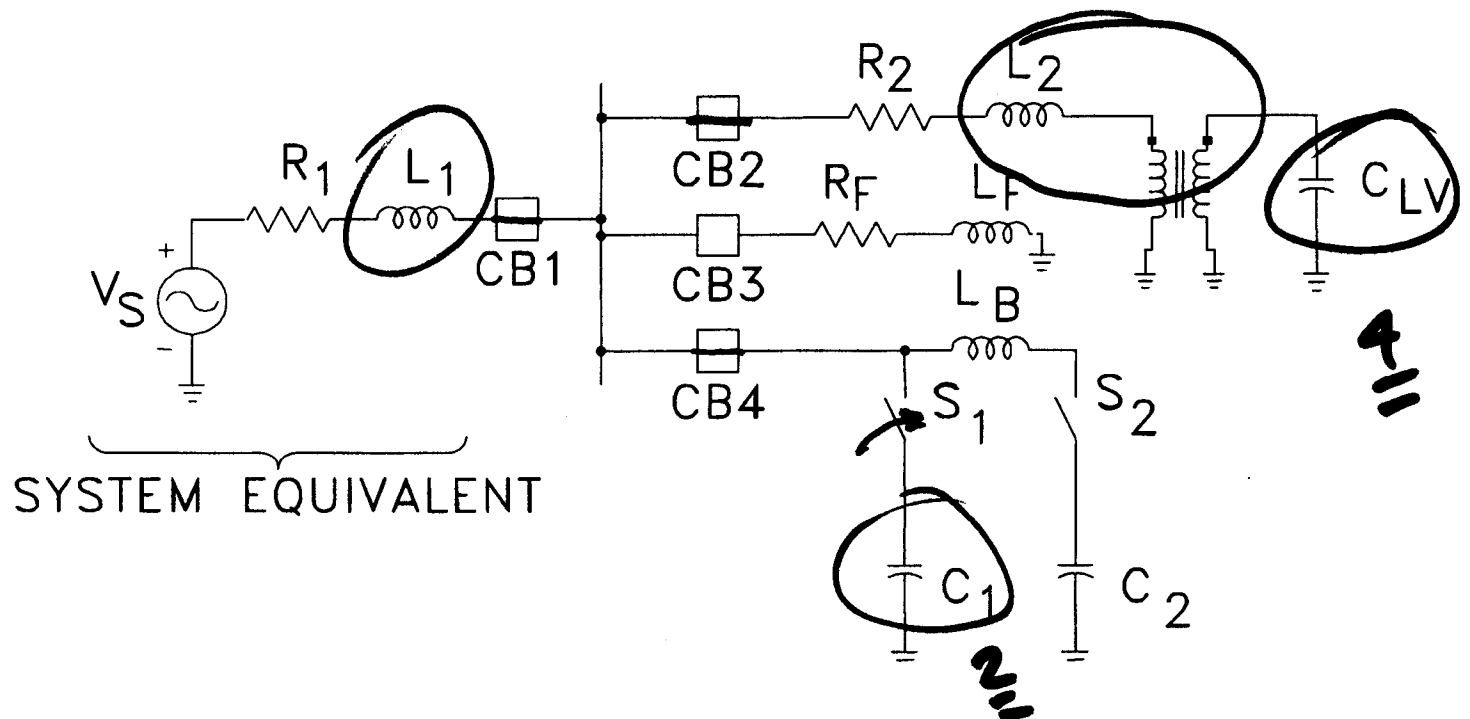Sample 34.5-kV system, developed from Fig. 3.4 in Greenwood.




- $R_1 = 0.5 \text{ Ohms}$ $L_1 = 3 \text{ mH}$ $R_2 = 0.001 \text{ Ohms}$ $L_2 = 12 \text{ mH}$
- $C_1 = 40.1 \mu\text{F} (18 \text{ MVAR})$ $C_2 = 22.3 \mu\text{F} (10 \text{ MVAR})$ $C_{LV} = 601 \mu\text{F}$
- Dist. Transformer: 4:1 ratio $L_B = 19 \mu\text{H}$ $C_{BUSH} = 300 \text{ pF} (\text{see p.437})$

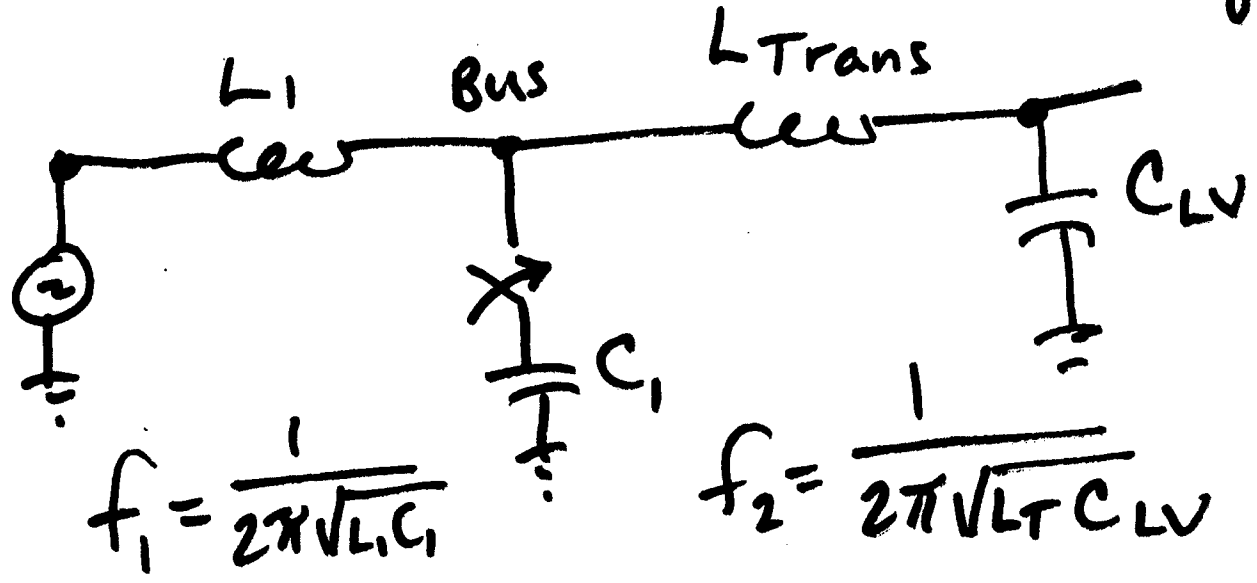5) Voltage Magnification - Usually Low Freq



$$f_1 = \frac{1}{2\pi\sqrt{L_1 C_1}}$$
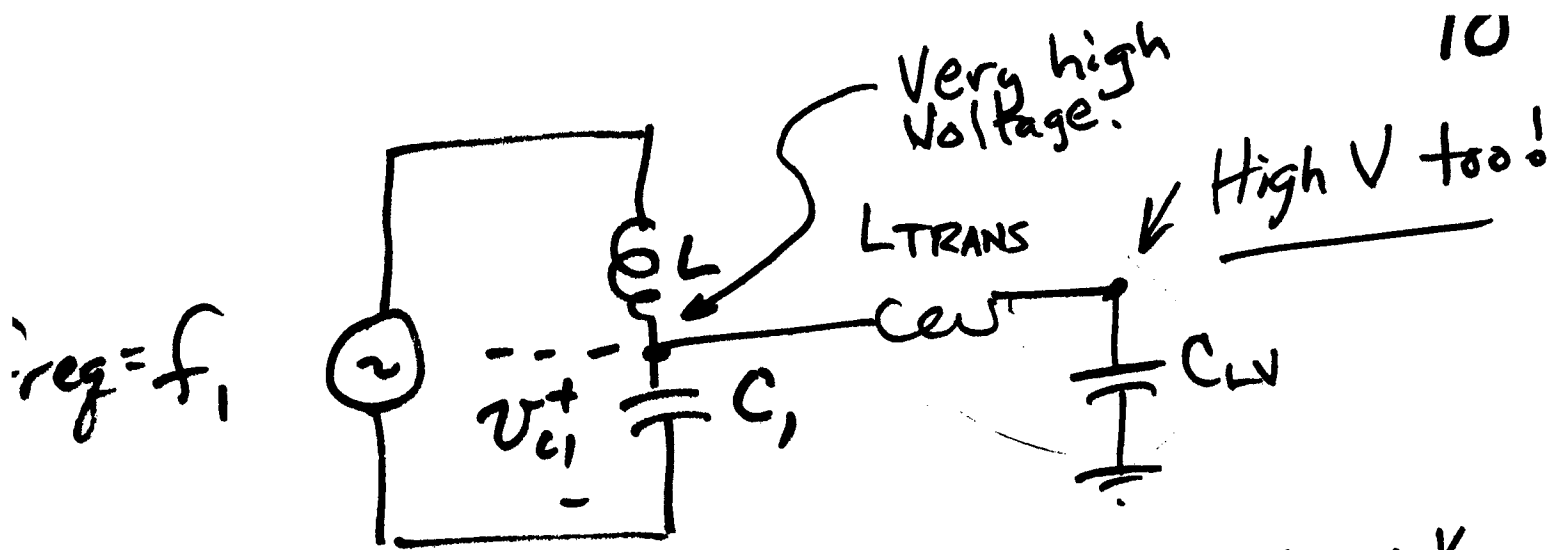
$$f_2 = \frac{1}{2\pi\sqrt{L_T C_{LV}}}$$



Series resonance: $Z_{TOT} = jX_L - jX_C$

$$X_L = X_C$$

$$2\pi f_1 L = \frac{1}{2\pi f_1 C_1}$$

$$= 0$$

$$I \rightarrow \infty$$

$$V_L \rightarrow \infty$$


$$V_C \rightarrow \infty$$

Per Unit voltage at C_{2V} is higher than at C_1 , thus the name "voltage magnification."

TRV-

Sample 34.5-kV system, developed from Fig. 3.4 in Greenwood.

Table 13.4

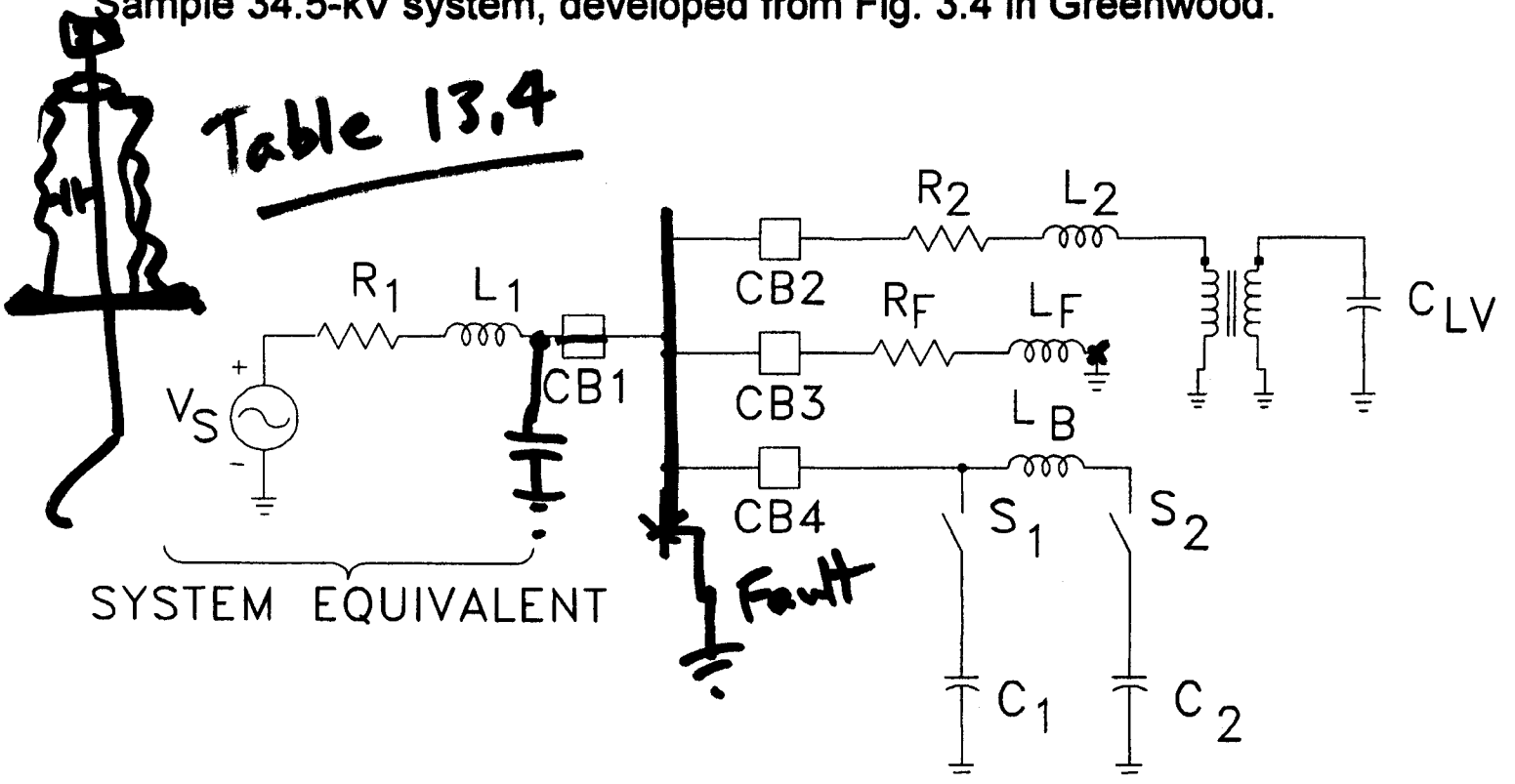

$R_1 = 0.5$ Ohms

$L_1 = 3$ mH

$R_2 = 0.001$ Ohms

$L_2 = 12$ mH

$C_1 = 40.1$ μ F (18 MVAR)


$C_2 = 22.3$ μ F (10 MVAR)

$C_{LV} = 601$ μ F

Dist. Transformer: 4:1 ratio

$L_B = 19$ μ H

$C_{BUSH} = 300$ pF (see p.437)

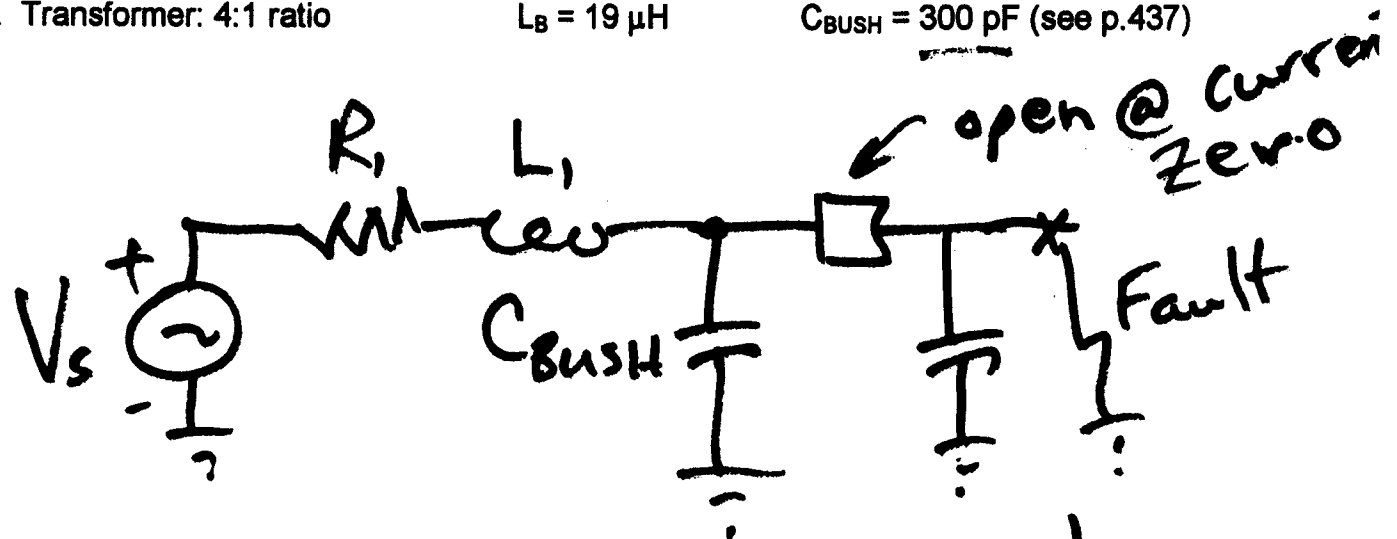

$$\omega_0 = \frac{1}{\sqrt{L_1 C_{BUSH}}} = \frac{1}{\sqrt{.003 \times 300 \times 10^{-12}}}$$

$$V_{peak} = 39.64 \text{ KV}$$

$$V_{peak, Base} = \frac{(34,500)(\sqrt{2})}{\sqrt{3}} = 28.1 \text{ KV}$$

$$V_{pu} = \frac{39.64}{28.1} = 1.4 \text{ p.u.}$$


$$\omega_0 = \frac{1}{\sqrt{L_1 C_{BUSH}}} = 167 \text{ KHz} = 300 \text{ pF}$$

$$\omega_{sim} = \underline{5 \text{ KHz}} (\text{@ } 200 \text{ nF})$$

Capacitances other than C_{BUSH} may be present.


- Cap Bank (like single-Bank energization)
- Transformer Coil Capacitances.
- Transformer Bushing Cap.

Recovery voltage on source side of CB.

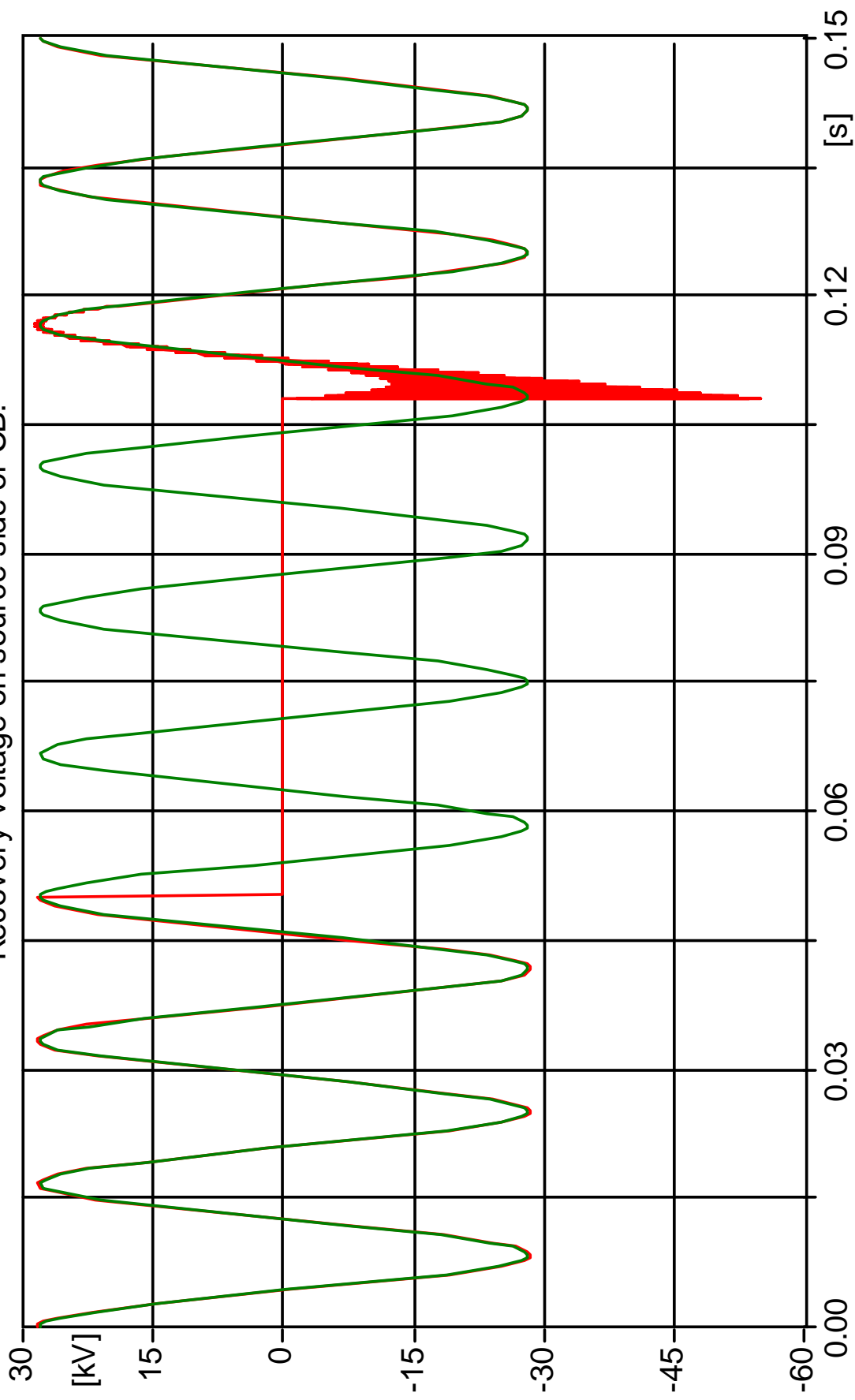


(file sk.pl4; x-var t) v:SEQUIV v:SRC

Recovery voltage on source side of CB.

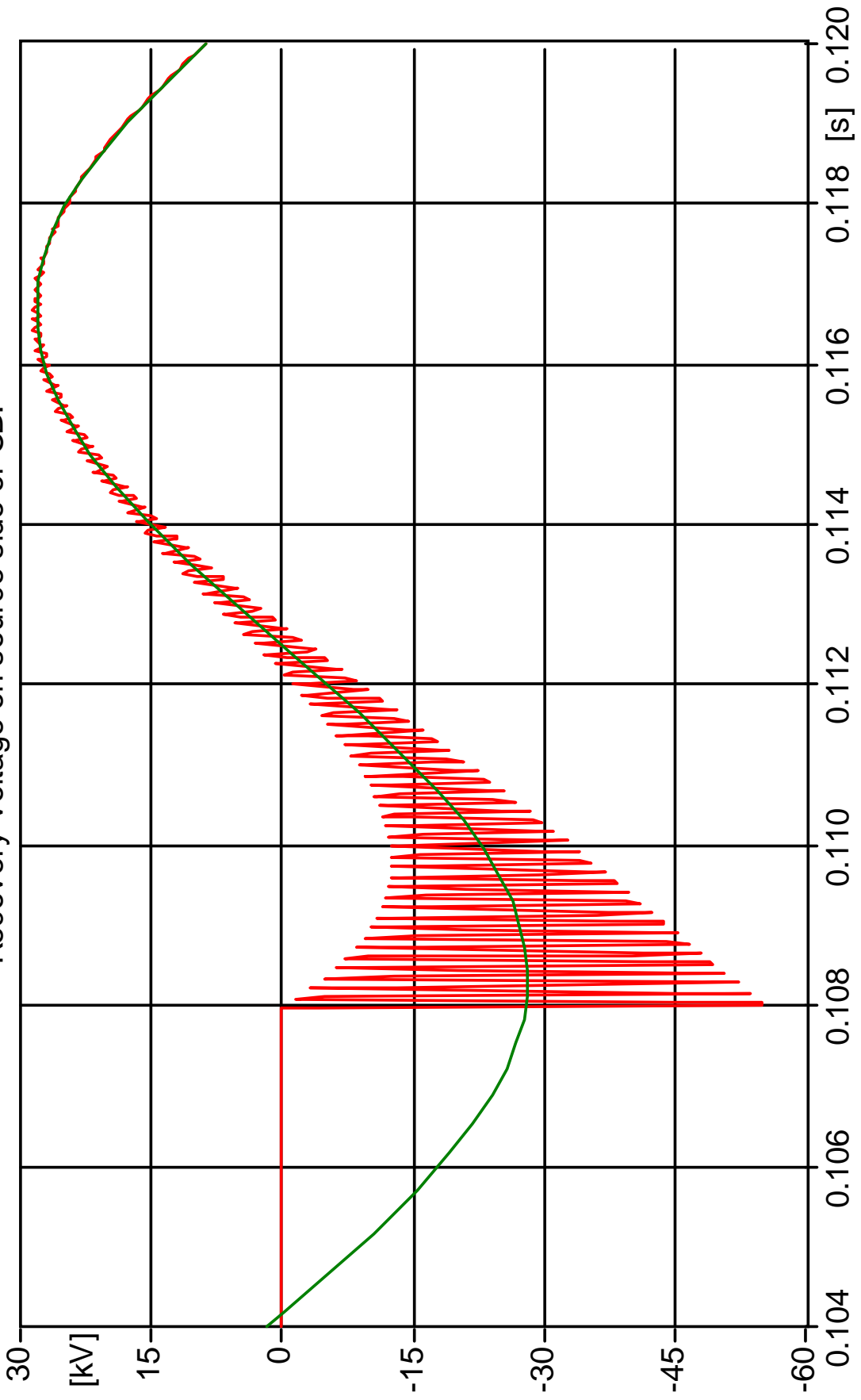

(file sk.pl4; x-var t) v:SEQUIV v:SRC

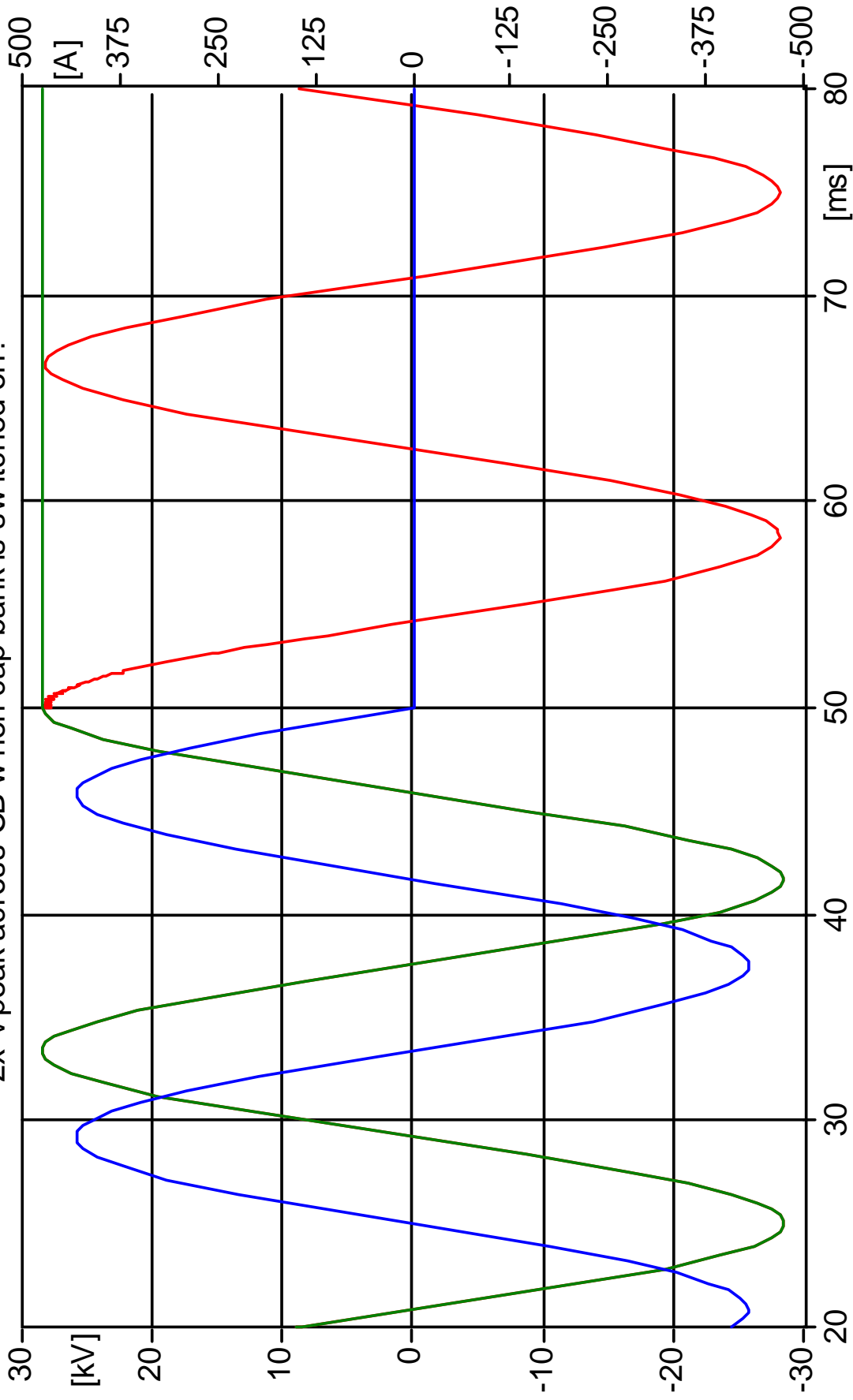
2x V peak across CB when cap bank is switched off!




(file sk.pl4; x-var t) v:SEQUIV v:BUS c:SW1 -C1

Problem 3.3 - Recovery Voltage

5

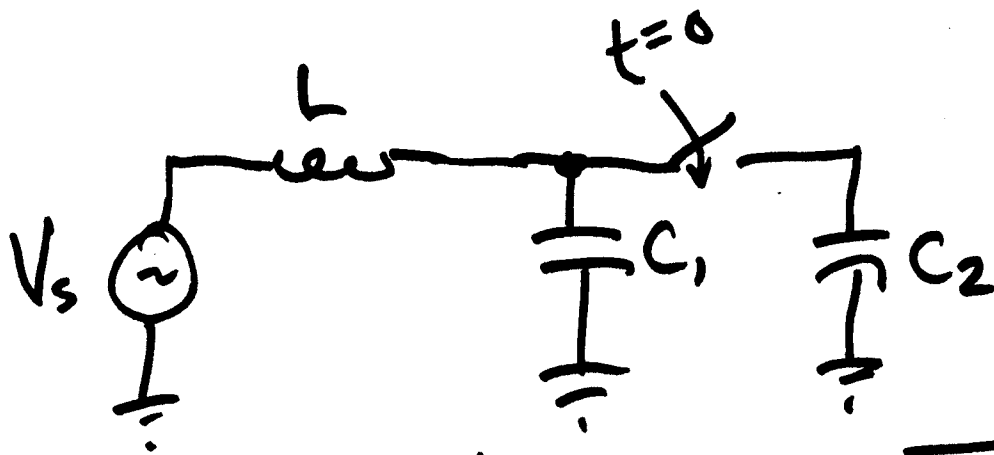

$$Q = CV$$

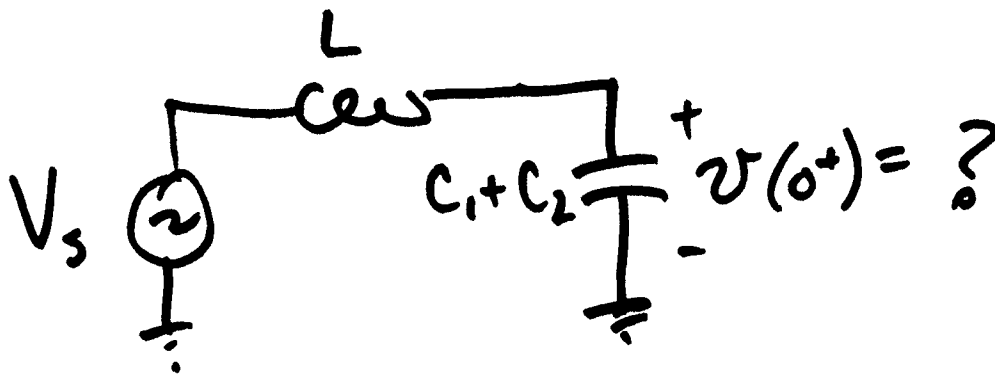


$$C_1 = 69.64 \mu\text{F}$$
$$C_2 = 41.79 \mu\text{F}$$

Conservation of charge:

$$Q(0^-) = Q(0^+) = (C_1)(V_s - \text{PEAK})$$
$$= (69.64 \mu\text{F}) \left(\frac{\sqrt{2} \times 13,800}{\sqrt{3}} \right)$$

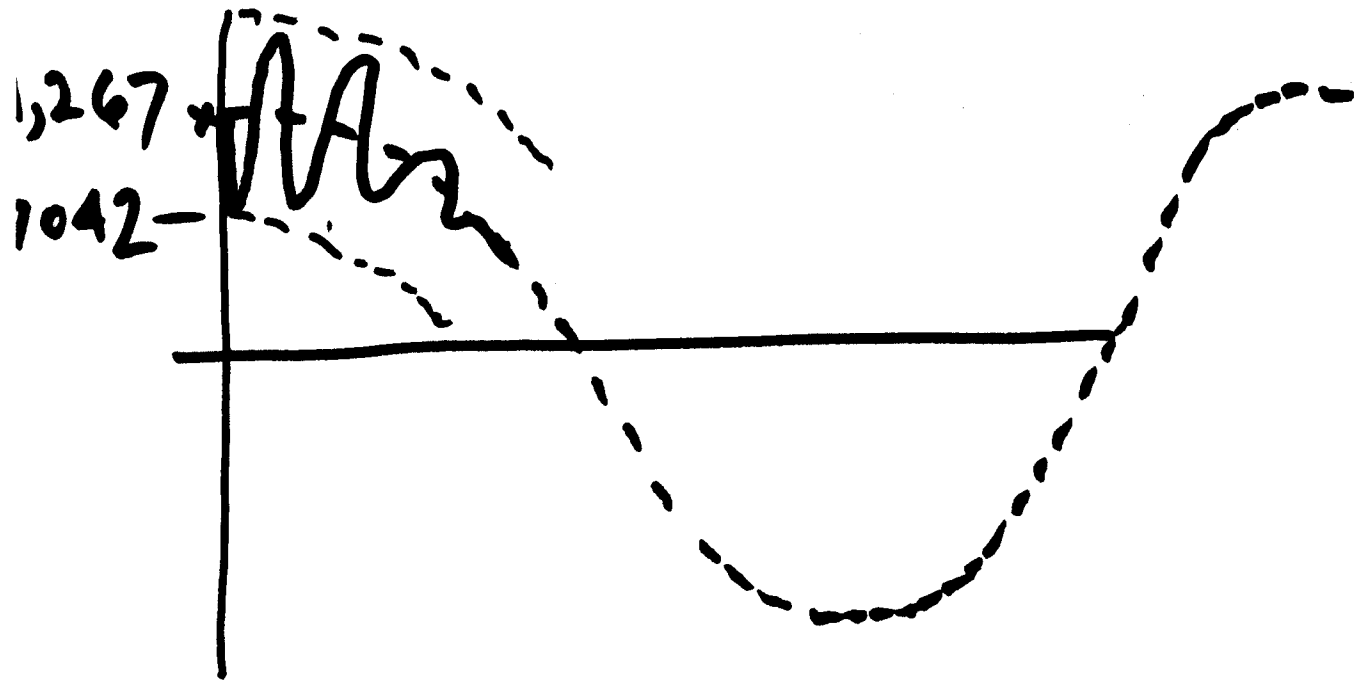
$$v(0^+) = \frac{Q}{C_1 + C_2} \Rightarrow v(0^+) = \underline{7042 \text{ V}}$$



Voltage oscillations: $\pm (11,267 - 7042)$
 $= \boxed{\pm 4225 \text{ V}}$


$$\omega_0 = \frac{1}{\sqrt{L_1(C_1 + C_2)}} \quad Z_0 = \sqrt{\frac{L_1}{C_1 + C_2}}$$

What about current oscillations?

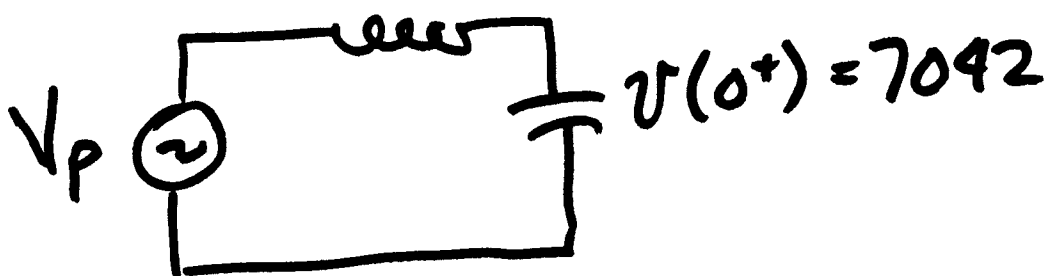


$$\begin{aligned}\Delta V &= V(\infty) - V(0^+) \\ &= 11267 - 7042 \\ &= 4225 \text{ V}\end{aligned}$$
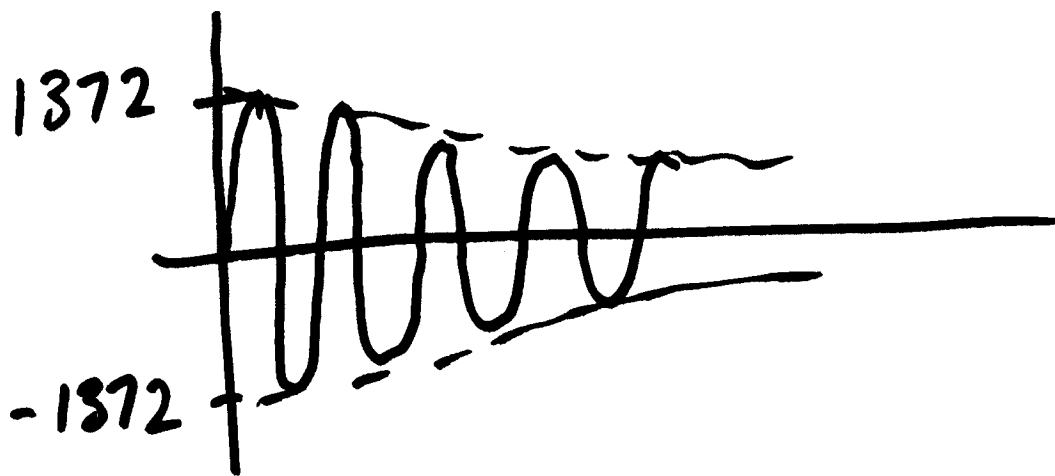
$$I_p = \frac{\Delta V}{Z_0} = \frac{4225}{3.08} = \boxed{1372 \text{ A}}$$



Bus Overvoltages

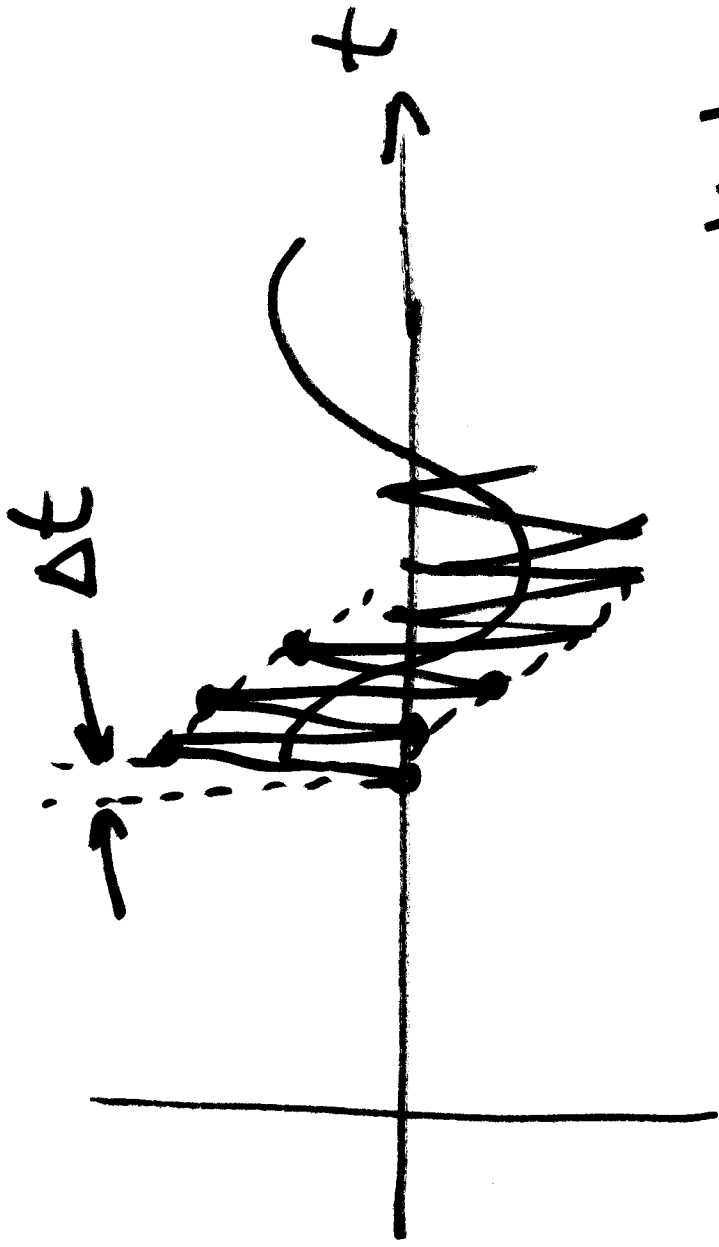- Not usually a concern with B-2-B energization.
- Bigger ~~and~~ worry with single Bank.



- time-step oscillation or
- numerical instability

Numerical Oscillations -


3

(Trapezoidal Method in EMTP)


Typical: Very small L's
Very large C's.

Solution: Place a numerical damping resistor



- a) In parallel w/L
- b) In series w/C

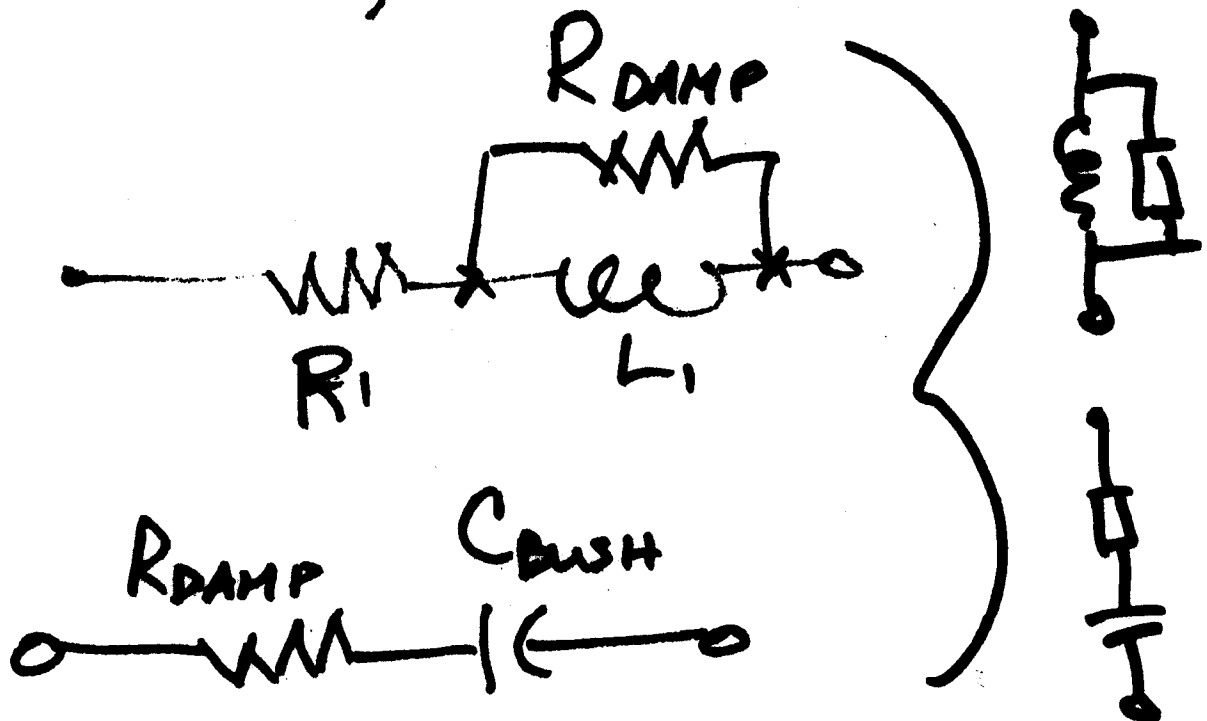

ATP Draw Implementation

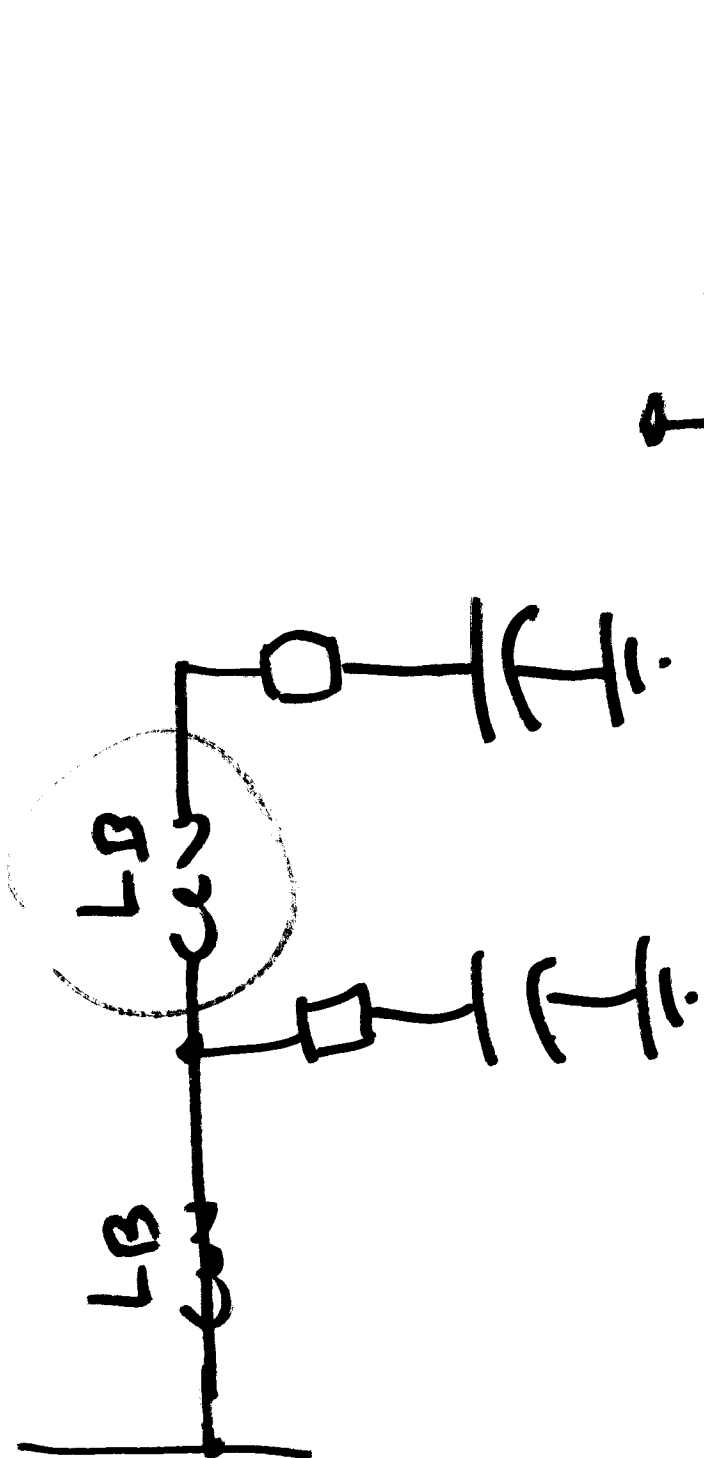

~~trans~~

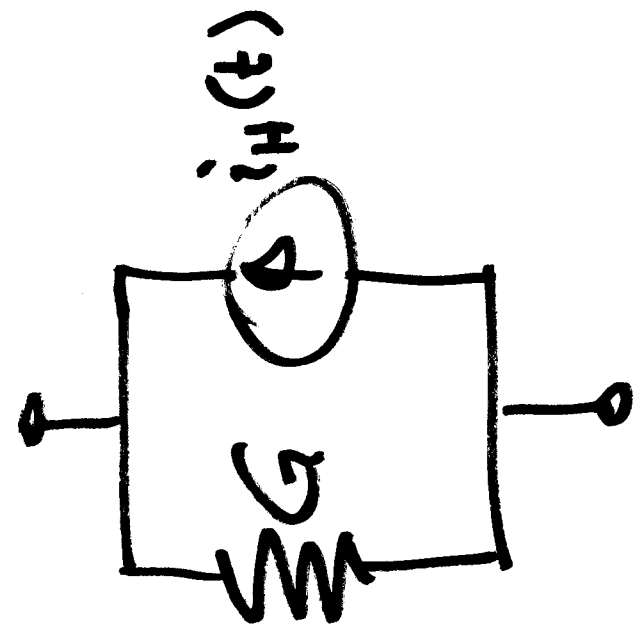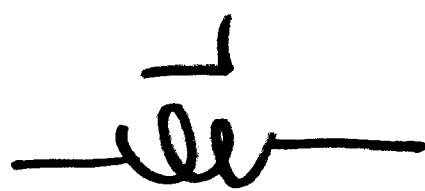

(EE5240, EE5220)

