

Topics for Today:



- Announcements
 - Expanded Term Project outline (i.e. Table of Contents + List of references (suggest about half a dozen to start with) by end of week.
 - Software: online students - apply for ATP/ATPDraw license, verify licensing when you receive it by e-mail, and we will mail you the install CD.
 - Office: EERC 623. Phone: 906.487.2857
 - Recommended problems & all solutions: Ch.6 solns posted.
- Chapter 6 - Using the T-Line models
 - Pi-Equivalent circuit for long-line
 - Characteristic Impedance Z_C
 - Propagation Constant $\gamma = \alpha + j\beta$
 - Surge-Impedance Loading (SIL)
 - Wavelength, velocity
 - Traveling waves, reflections

$$Z_c = \sqrt{\frac{Z}{y}}$$

$$\gamma = \sqrt{ZY} = \alpha + j\beta$$

attenuation

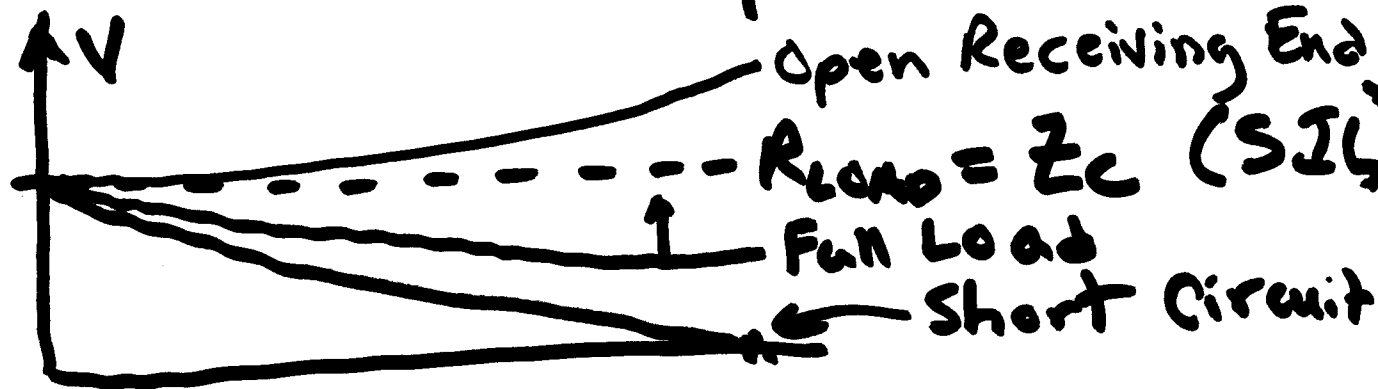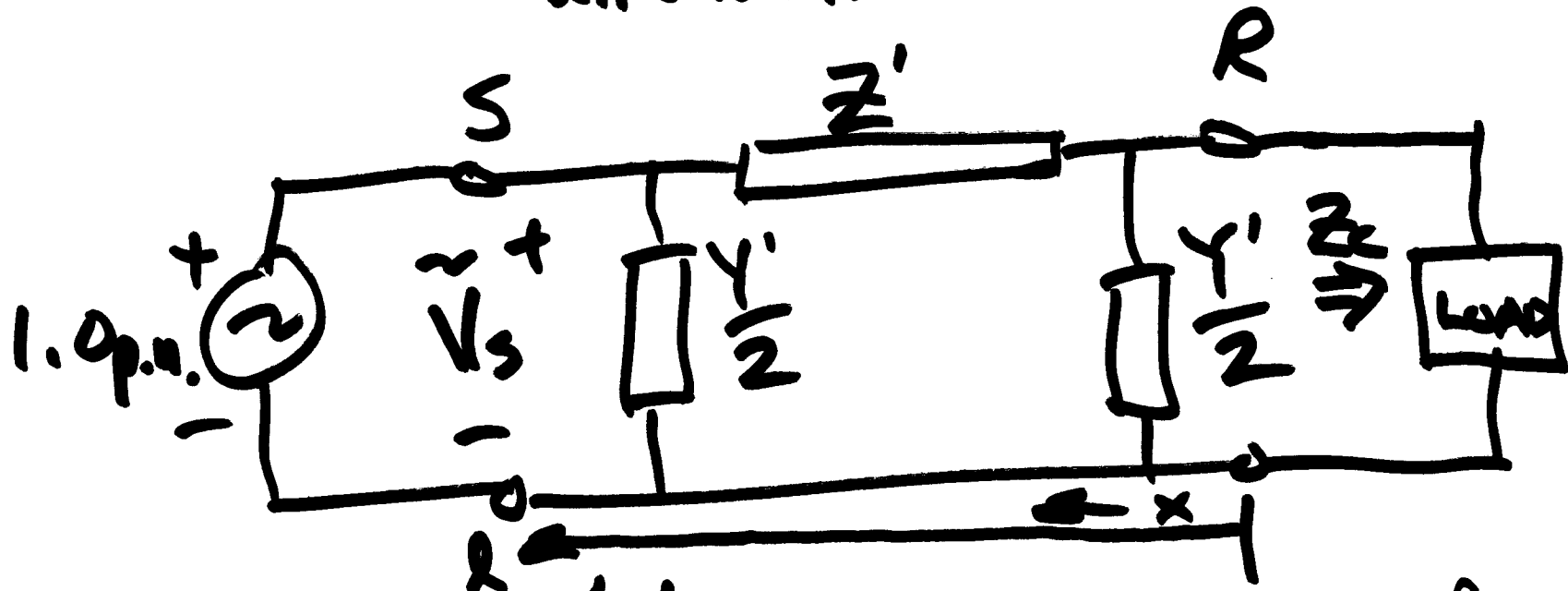Phase angle rotation
How a wave travels down line.



Another Point:

2

- SIL = Surge Impedance Loading

$$- R_{LOAD} = |Z_c|$$

- Total Reactive Power Consumed in Line = 0.


→ "Flat" Line or flat voltage profile.

$$- SIL = \frac{V^2}{Z_c} = \frac{V_s^2}{Z_c} = \frac{V_R^2}{Z_c}$$

Propagation Wavelength λ 3

λ = distance req'd to change $\angle V$ by 360° .

$$\gamma = \sqrt{ZY} = \alpha + j\beta \quad (\text{Assume Lossless})$$



$e^{j\beta x}$: term provides phase rotation in each term of $I(x)$, $V(x)$.

$$\lambda = x = \frac{2\pi}{\beta} \Rightarrow \lambda = \frac{2\pi}{\omega\sqrt{LC}} = \frac{2\pi}{2\pi f\sqrt{LC}}$$

$$\lambda = \frac{1}{f\sqrt{LC}}$$

$$v = f\lambda = \frac{1}{\sqrt{LC}} = 3 \times 10^8 \text{ m/s} = \frac{1}{\sqrt{\epsilon_0 \mu_0}}$$

$$\text{@ } 60 \text{ Hz, } \lambda = \frac{v}{f} = \frac{3 \times 10^8 \text{ m/s}}{60} \quad 4$$

$$\approx 5000 \text{ km}$$

$$\approx 3100 \text{ miles}$$

$$\text{@ } 2 \text{ MHz, } \lambda = \frac{3 \times 10^8}{2 \times 10^6} = 150 \text{ m}$$

- Side Comments (later) on
* T-Line loading limits

- Thermal

- Voltage Limits, $V_S \neq V_R \Rightarrow V_R$
 $.95 < V < 1.05$

- Stability Limits

$$V(x) = \left(\frac{V_R + Z_c I_R}{2} \right) e^{\gamma x} + \left(\frac{V_R - Z_c I_R}{2} \right) e^{-\gamma x} \quad (1)$$

$$I(x) = \left(\frac{V_R + Z_c I_R}{2} \right) e^{\gamma x} - \left(\frac{V_R - Z_c I_R}{2} \right) e^{-\gamma x}$$

best for
Trav. Waves. →

$$Z_c = \sqrt{\frac{Z}{Y}} = \text{Characteristic Impedance.}$$

$$\gamma = \sqrt{ZY} = \alpha + j\beta = \text{Propagation Coefficient}$$


α = attenuation constant

β = angular propagation constant.

(From Lecture 13)

Travelling Waves


5

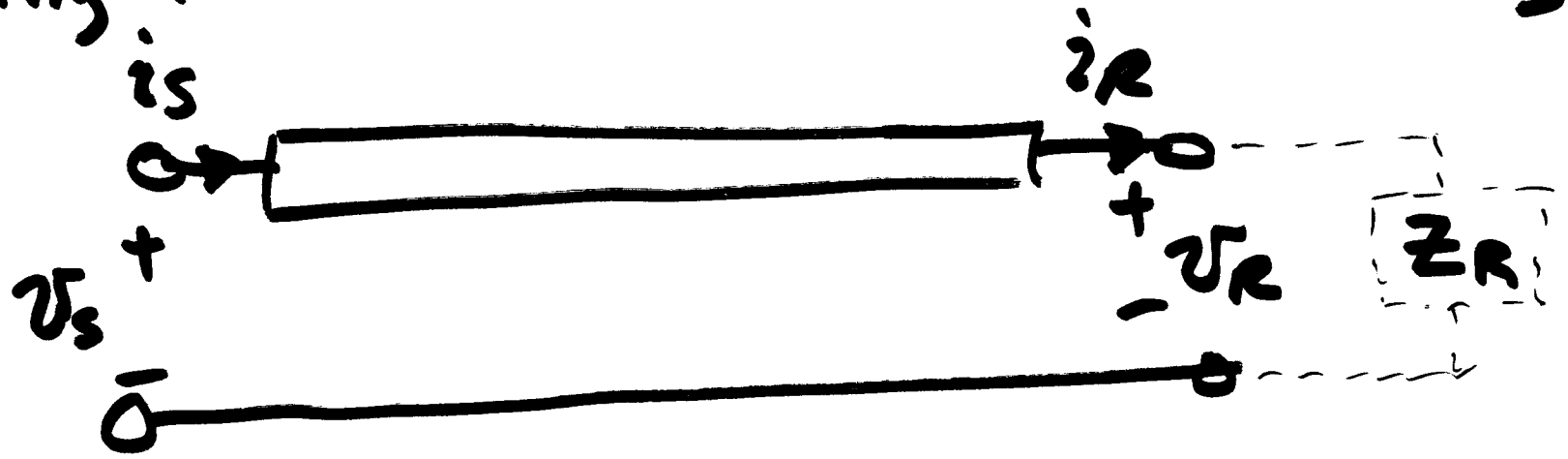

Impedance at receiving end:

$$Z_R = \frac{V_R}{i_R} = \frac{V_R^+ + V_R^-}{i_R^+ + i_R^-} = \frac{V_R^+ + V_R^-}{\frac{V_R^+}{Z_c} - \frac{V_R^-}{Z_c}} = Z_R$$
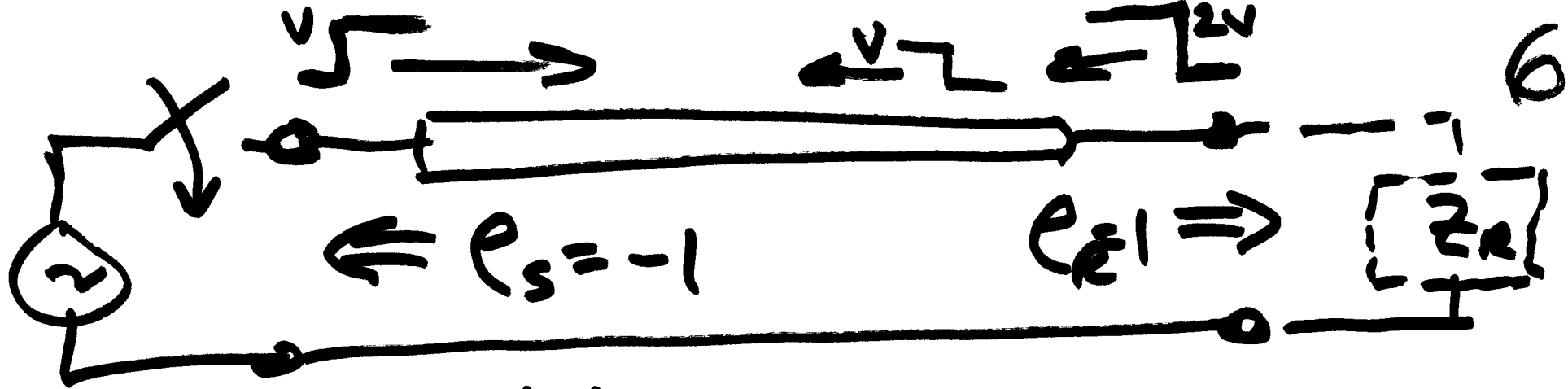
$$\frac{V_R^-}{V_R^+} = \frac{Z_R - Z_c}{Z_R + Z_c} = \rho_{LR} \quad \text{Reflection Coefficient}$$



If receiving end is...

- Open-ckt (i.e. $Z_R = \infty$)

$$\rho_R = \frac{\infty - Z_c}{\infty + Z_c} = +1$$

$$\therefore v_R^- = v_R^+ \rho_R = v_R^+$$

- Short-ckt (i.e. $Z_R = 0$)

$$\rho_R = \frac{0 - Z_c}{\infty + Z_c} = -1$$

Traveling Wave Example (ATPD Draw) 7

See page 14, Lecture 13

$$Z_c = 294.3 \angle -9.22^\circ \Omega$$

$$\gamma = .00215 \angle 80.8^\circ = \underbrace{0.00034}_\alpha + j \underbrace{0.00212}_\beta$$

250-miles long

$$\left. \begin{aligned} z &= 0.2 + j0.6 \Omega/\text{mi} \\ y &= j7.3 \mu\text{S}/\text{mi} \end{aligned} \right\} \Rightarrow$$

$$\left. \begin{aligned} L &= 0.398 \text{ H} \\ C &= 484 \mu\text{F} \\ R &= 50 \Omega \end{aligned} \right\} \text{Total}$$

If losses are ignored,

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi \text{ rad}}{.00209 \text{ rad}/\text{mi}}$$

$$= 3006 \text{ mi}$$

$$\left[\begin{aligned} Z_c &= 286.69 \Omega \\ \gamma &= j0.00209 \text{ rad}/\text{mi} \\ (\alpha &= 0) \end{aligned} \right. \begin{array}{l} \uparrow \\ \beta \end{array}$$

Before creating ATP example, let's predict behavior:

8

Lossless: $\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{.00209} = 3006 \text{ m}$


$f\lambda = v = 2.9 \times 10^8 \text{ m/s}$ ($f = 60 \text{ Hz}$)
← (should be 3×10^8 ... rounding.)

Propagation Time: Approx:

$$t = \frac{x}{v} = \frac{(250 \text{ m})(1.6 \text{ km/m})}{2.9 \times 10^6 \text{ km/s}} = \boxed{138 \mu\text{s}}$$

250-mile transmission line example - traveling wave model in ATP

TravWave.adp

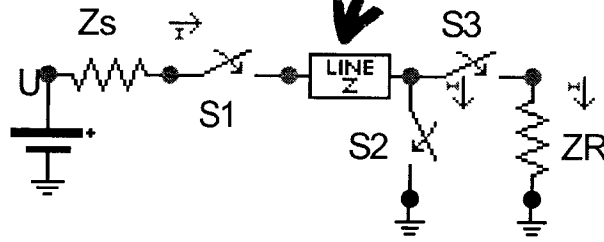

**Select Distributed 1-phase
Clarke Line Model.**

Input (click Help button):


ILINE option: 0

$R/\ell = 0.2$ Ohms/mi

$A = j0.6$ Ohms/mi

$B = 7.3$ μ S/mi

ℓ (length) = 250 mi

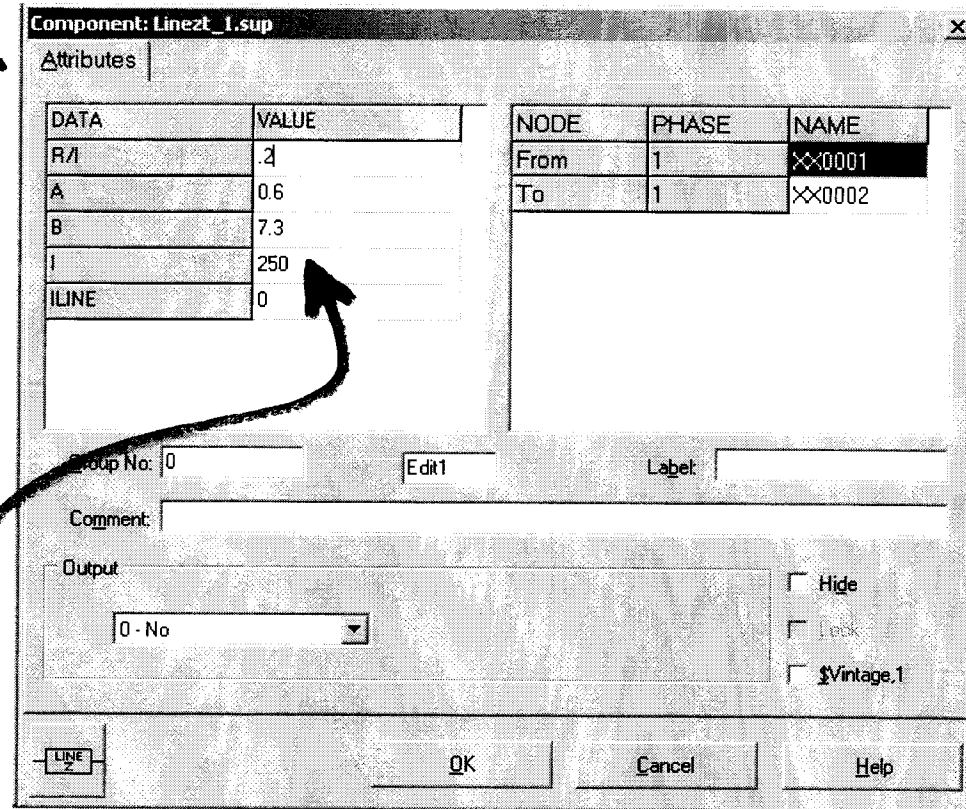

$$z = 0.2 + j0.6 \text{ Ohms/mi}$$

$$y = j7.3 \text{ } \mu\text{S/mi}$$


$$Z_C = 294.3 \text{ } \angle -9.22^\circ \text{ Ohms}$$

$$\gamma = 0.00215 \text{ } \angle 80.8^\circ \text{ /mi}$$

Ref: EE5200 notes, Lectures 13 and 14.

First Case: Lossless. $Z_s = 0$; Receiving end open-circuited.

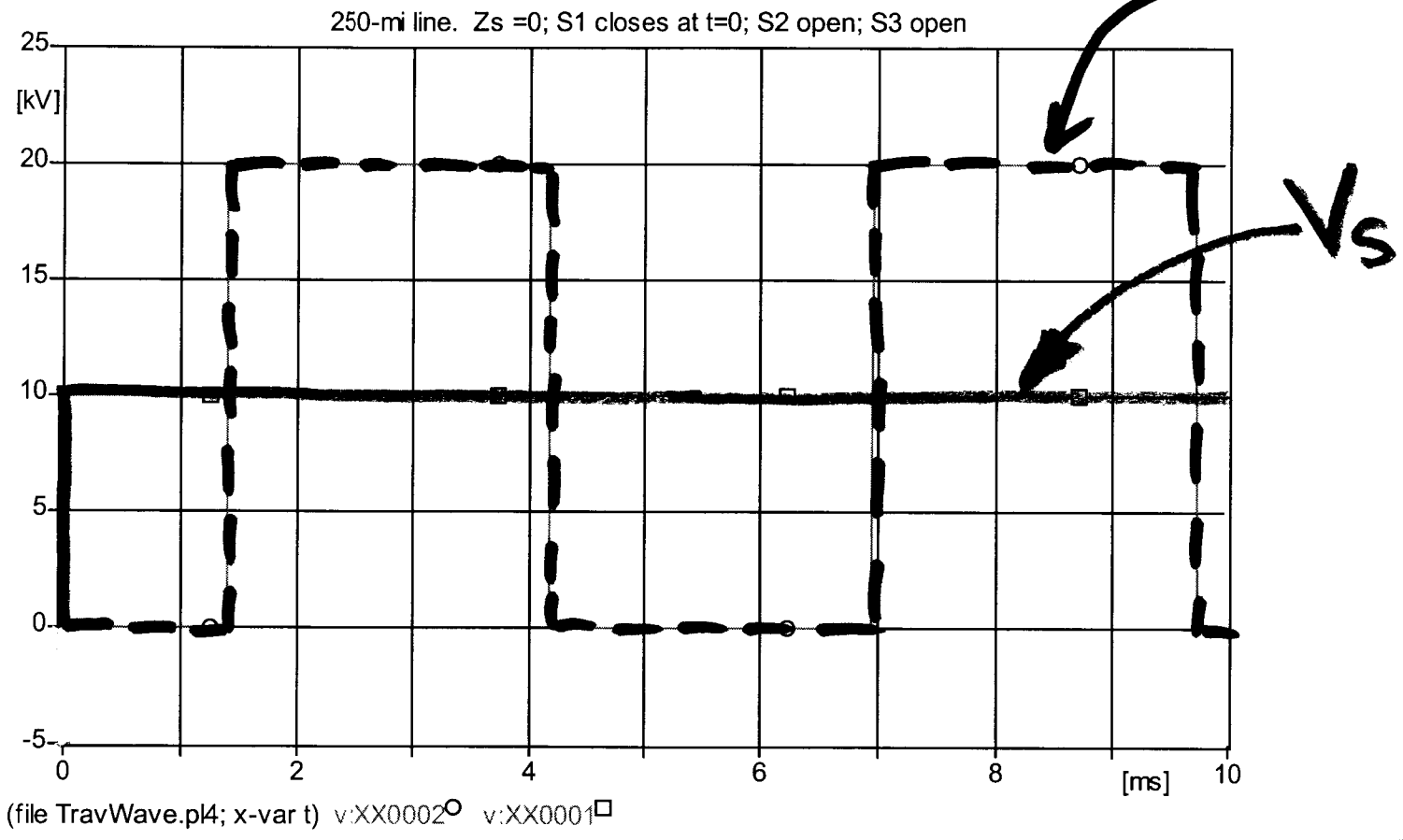Predicted propagation time (rough calculation): 138 μ s.




Actual propagation time: 139 μ s.

$$\rho_s = -1, \rho_R = +1$$

Second Case: $R=0.2$ Ohm/mi; $Z_s = 0$; Receiving end open-circuited.


* 10-kV wave is attenuated 8.5%.
Arrives as 9.15 kV, reflection doubles it, to 18.3 kV.

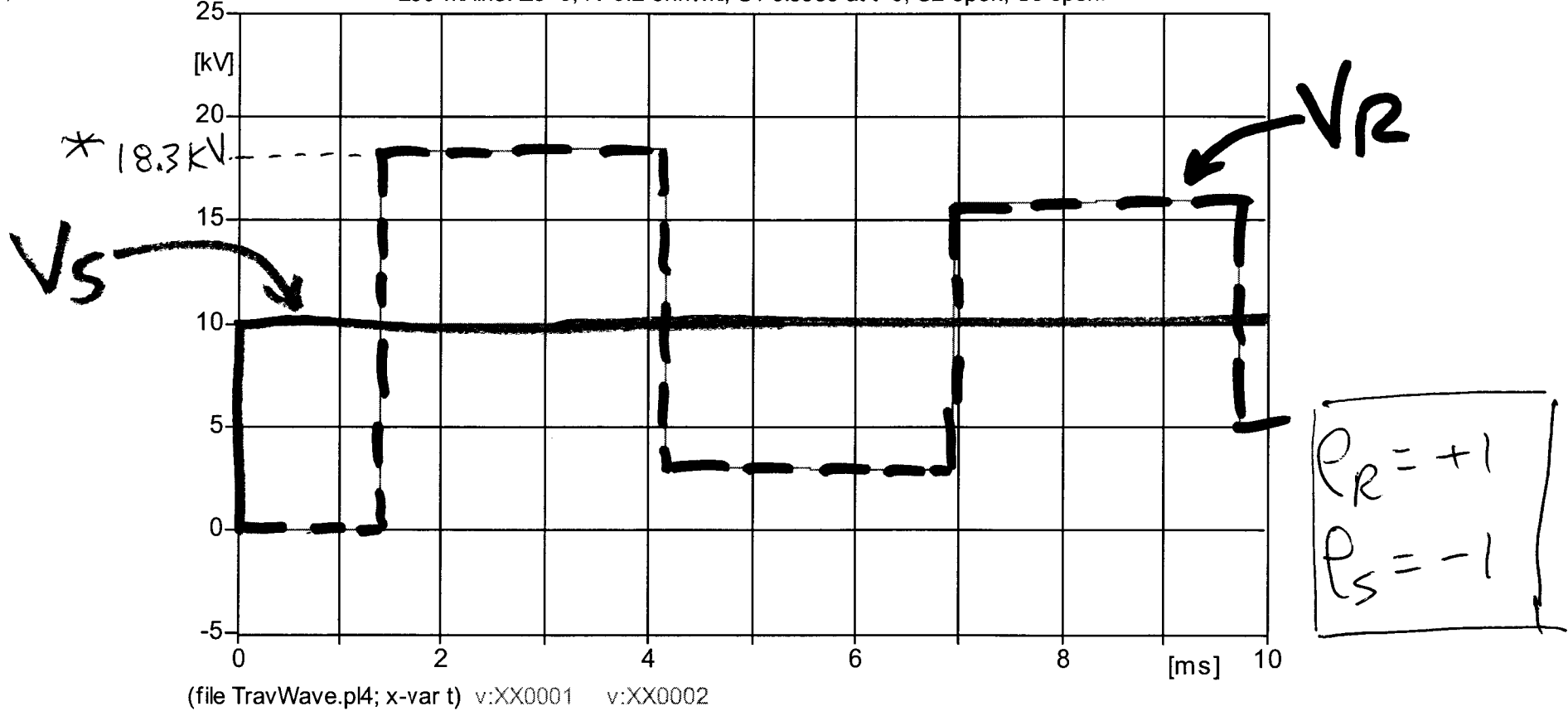250-mi line. $Z_s=0$; $R=0.2$ ohm/mi; S1 closes at $t=0$; S2 open; S3 open.



* Note: Attenuation of voltage wave is $\alpha \times l$
 $= (0.00034/\text{mi})(250\text{mi}) = 0.085$ or 8.5%
 i.e. Mag at end of line is ~~only~~ only 91.5%.

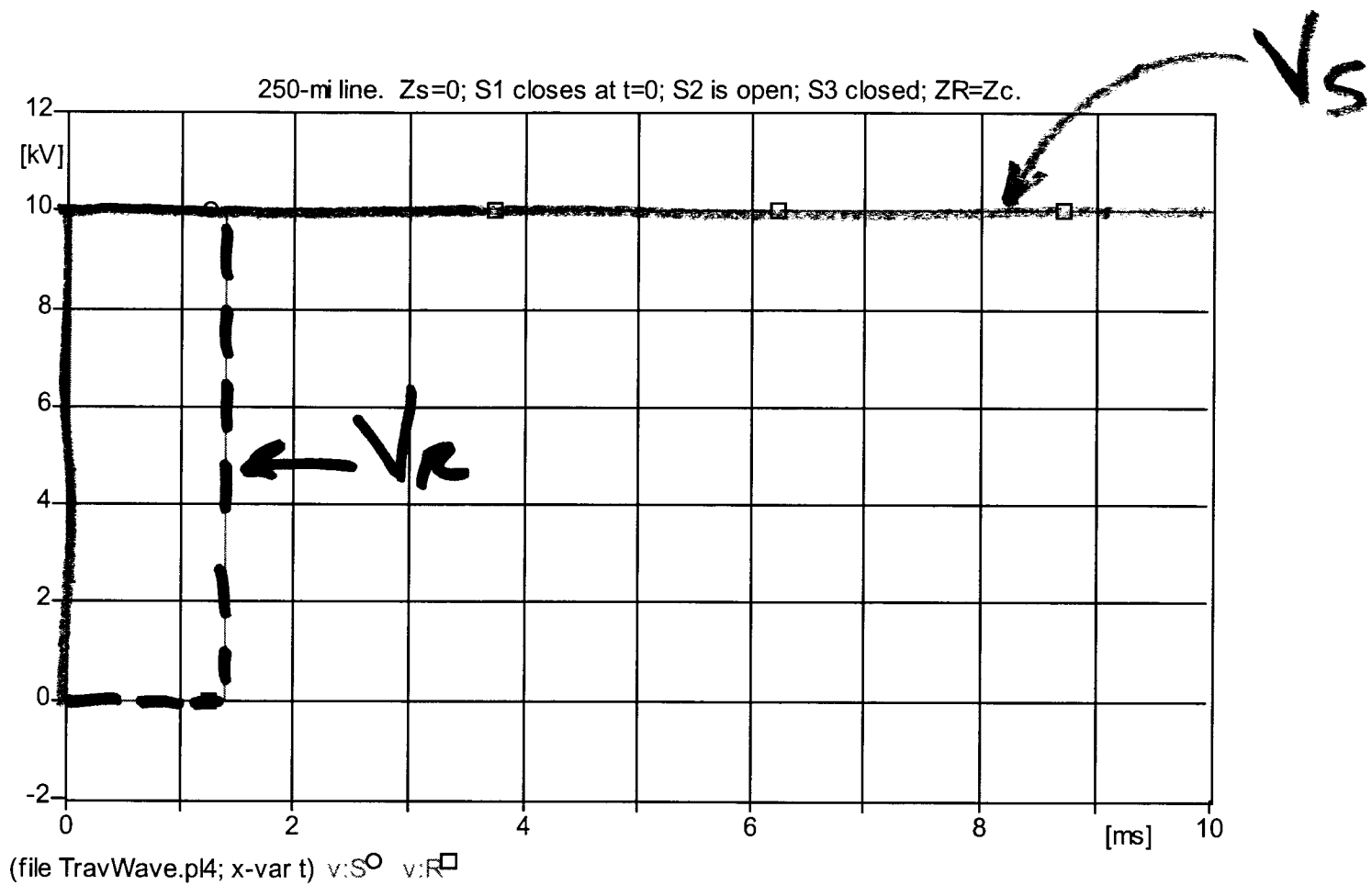Third Case: Lossless line; $Z_s=0$; $Z_R = Z_C$



Note: no reflection or voltage overshoot at receiving end !