

Topics for Today:

- Any Remaining Startup Questions?
- Recap of Mesh and NODE equations from Lecture 1:
 - Symmetric about main diagonal
 - $[Y_{\text{BUS}}]$ is invertible, usually
- More on node equation formulations, sparse storage, etc.
- Possible Solution Methods
 - Brute Force Inversion and pre-multiplication
 - in situ methods:
 - Gauss Elimination
 - Gauss-Jordan Elimination
 - LU Factorization
 - Matrix “manipulations”
 - Kron Reduction
 - Augmentation
 - Adding constraints (add'l variables) to system of equations
 - Adding a source, short circuit, ideal transformer, etc.


- Homework #1 -- To get started:
 - 1) Go thru videotaped EE5200 MatLab tutorials, refer to Matlab online help for matrix operations and take basic notes for your future reference.
 - 2) Use MatLab to solve the matrix equations for the mesh and the node problems in Lecture 1.
 - 3) Go thru the terminology listed in assignment, look up in text or other references. Find corresponding MatLab functions or capabilities. Take notes on MatLab syntax and application “in’s and out’s”
 - 4) Find out how to enter a sparse matrix into MatLab and document the procedure. Learn how to view network topology via the Matlab spy function.
 - Don’t hesitate to send e-mail our group e-mail forum,
 - it can be helpful for everyone to contribute questions and comments.

Implications of symmetry:
i.e. if $y_{nk} = y_{kn}$?

Bilateral vs.

non-Bilateral

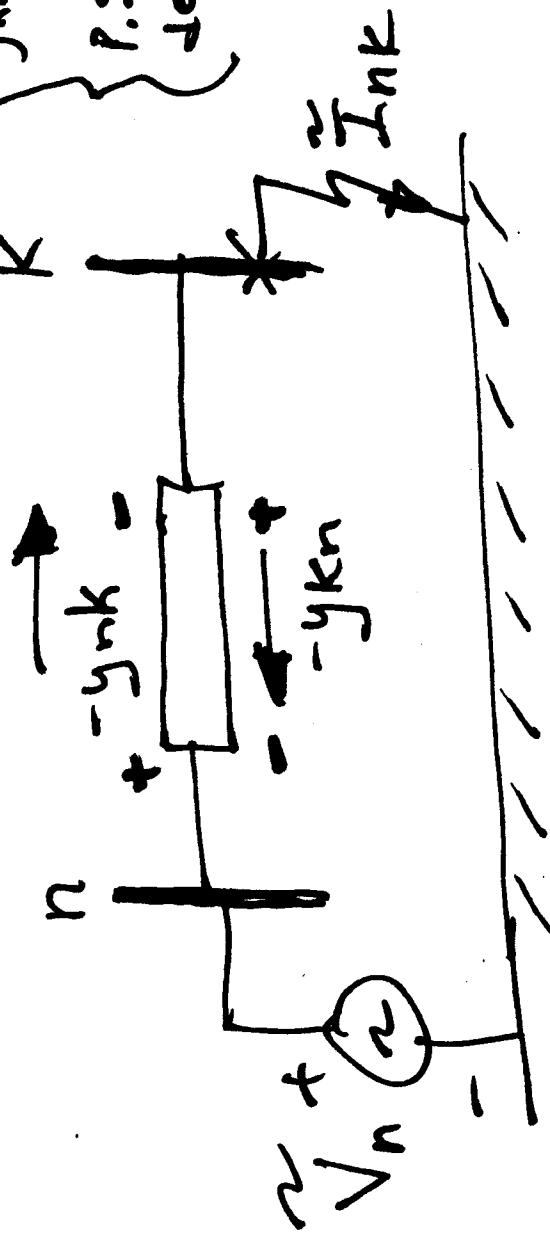$y_{kn} \neq y_{nk}$
 if
 P.S. x fm or
 dependent source



"Transfer admittances"

$$-y_{kn} = \frac{I_{nk}}{V_n}$$

$$-y_{nk} = \frac{I_{kn}}{V_k}$$

- If symmetric about main diagonal,
then might get by with storing only
lower half of off-diagonal terms.
 - Careful!
 - a) in situ methods will produce "fills"
 - b) Can't look statically at storage requirements!
 - b) Produce errors in solution if non-bilateral.
-

Remaining topics:

- Linked list storage
- They \rightarrow Norton form gen's $\notin [\gamma_{\text{bus}}]$
- Augmenting $[\gamma_{\text{bus}}]$
- Partitioning (Kron ~~the~~ Reduction)

Ex: Coefficient matrix


$$A = \begin{bmatrix} 3 & 0 & 0 & 2 & 0 \\ 0 & 5 & 1 & 0 & 0 \\ 0 & 1 & 2 & 7 & 9 \\ 2 & 0 & 7 & 1 & 0 \\ 0 & 0 & 9 & 0 & 4 \end{bmatrix}$$

Full storage:
25 numbers.

Single precision:
Real: 4 bytes
Complex: 8 bytes

$$10,000 - \text{bytes} \Rightarrow [y] : 100,000,000 \text{ entries}$$

Linked List: Storage

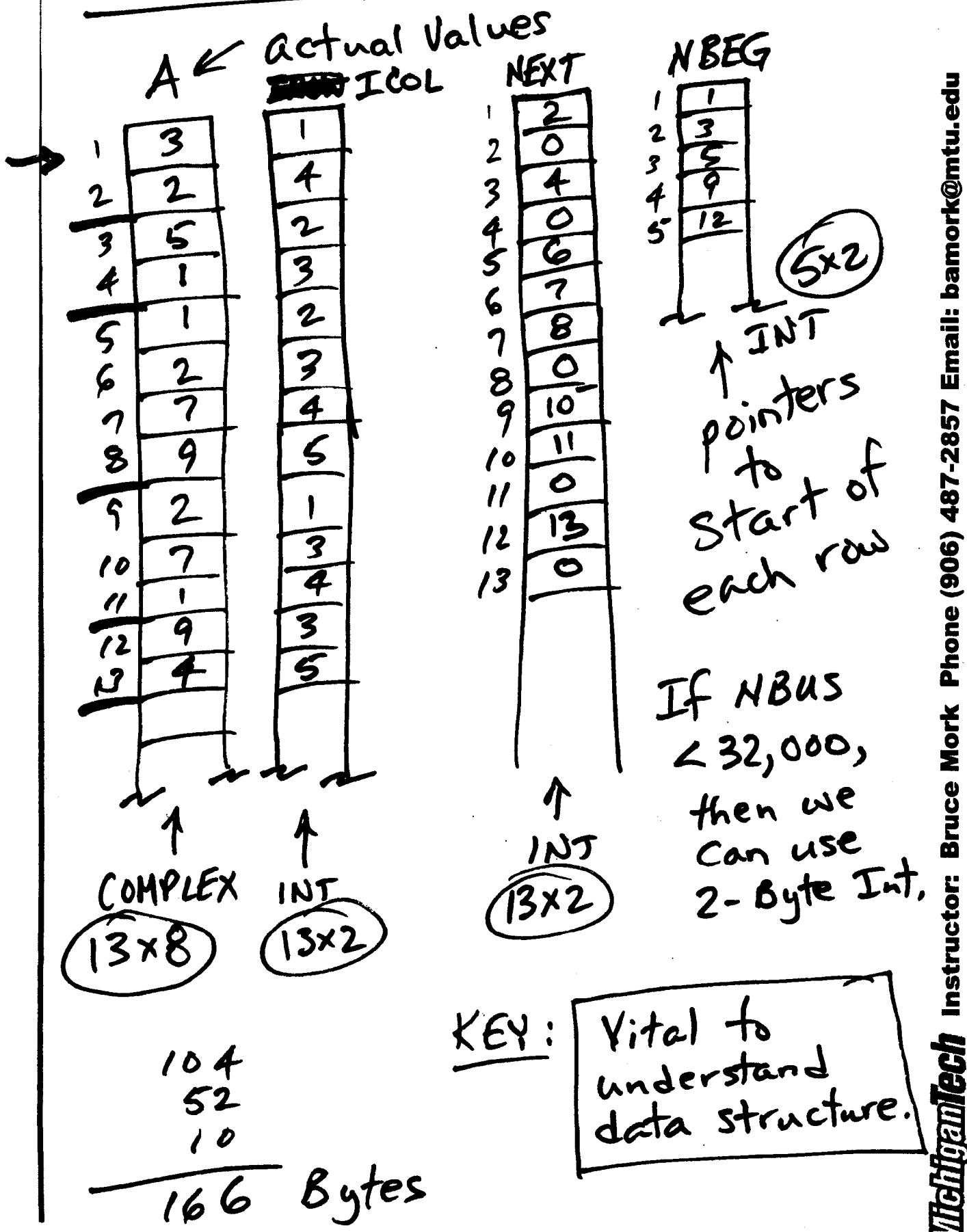


Data Type


$[A]$

- Single-prec Complex A
 " " Int.
 " " Int.
 " " Int.


$A(i) =$

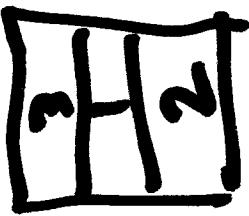

Ex:

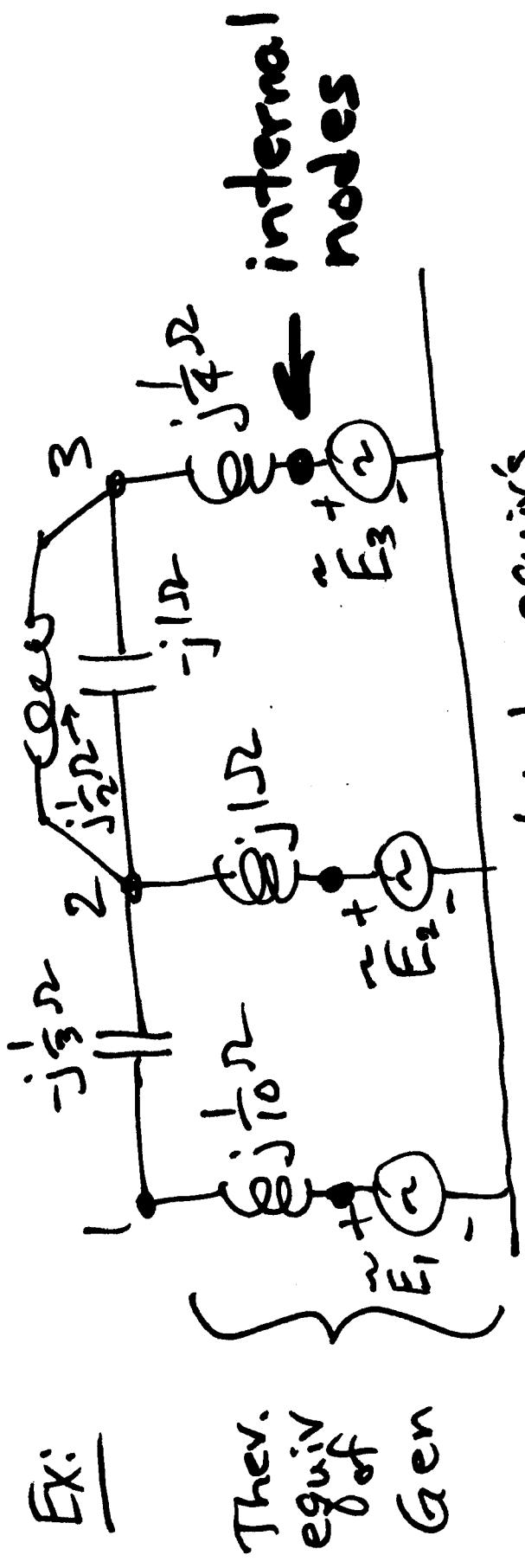

Convert to admittances w/ Norton equiv's

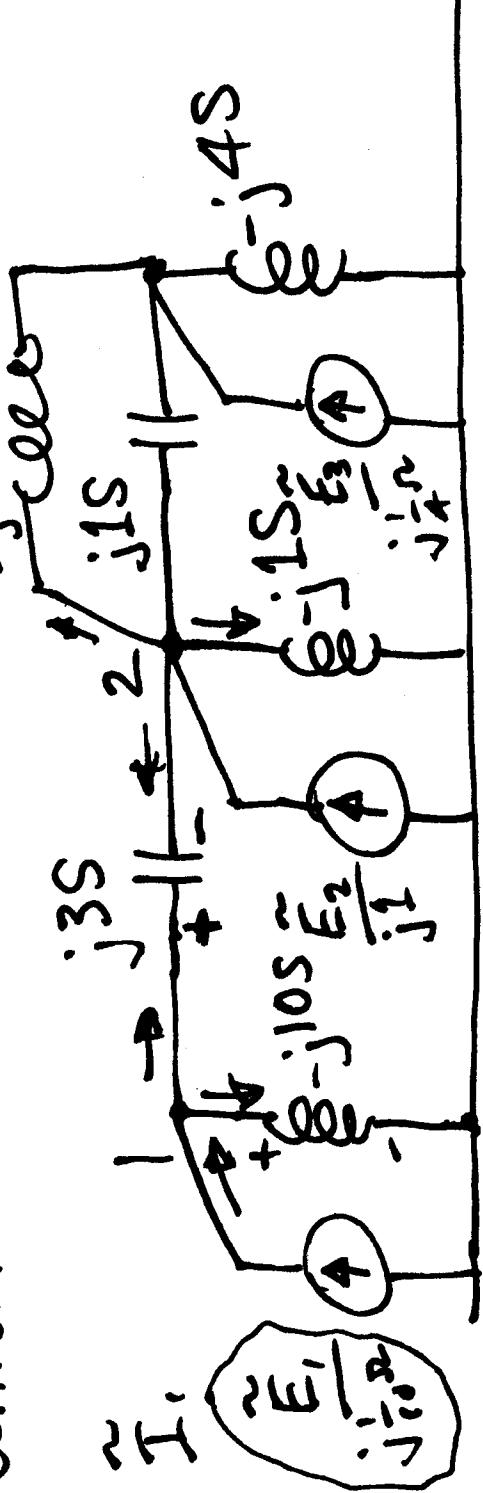

Node 1

$$\begin{aligned}\tilde{I}_1 &= (\tilde{V}_1 - \tilde{V}_2)j_3 + (\tilde{V}_1 - 0)(-j105) \\ \tilde{I}_2 &= (\tilde{V}_1 - \tilde{V}_3)j_1 + (\tilde{V}_2 - \tilde{V}_3)j_1 + (\tilde{V}_2 - 0)(-j1) \\ \tilde{I}_3 &= (\tilde{V}_3 - \tilde{V}_2)(j_1 - j_2) + (\tilde{V}_3 - 0)(-j4)\end{aligned}$$

$$\begin{bmatrix} \tilde{I}_1 \\ \tilde{I}_2 \\ \tilde{I}_3 \end{bmatrix} = \begin{bmatrix} \tilde{V}_1 \\ \tilde{V}_2 \\ \tilde{V}_3 \end{bmatrix} \text{ or, build } \begin{bmatrix} \tilde{V}_1 \\ \tilde{V}_2 \\ \tilde{V}_3 \end{bmatrix} \text{ by inspection.}$$

Continue, see homework.

Admittance Equations

General Form :

$$\begin{bmatrix} Y_{Bus} \end{bmatrix} \begin{bmatrix} V_{Node} \end{bmatrix} = \begin{bmatrix} I_{INJ} \end{bmatrix}$$


Augmentation

We can add constraints:

- \vee source Bus - Bus
- Short
- XMR
- DEPENDENT SOURCES (op-AMP)

Kronen Reduction - System Reduction

- Kronen Elimination

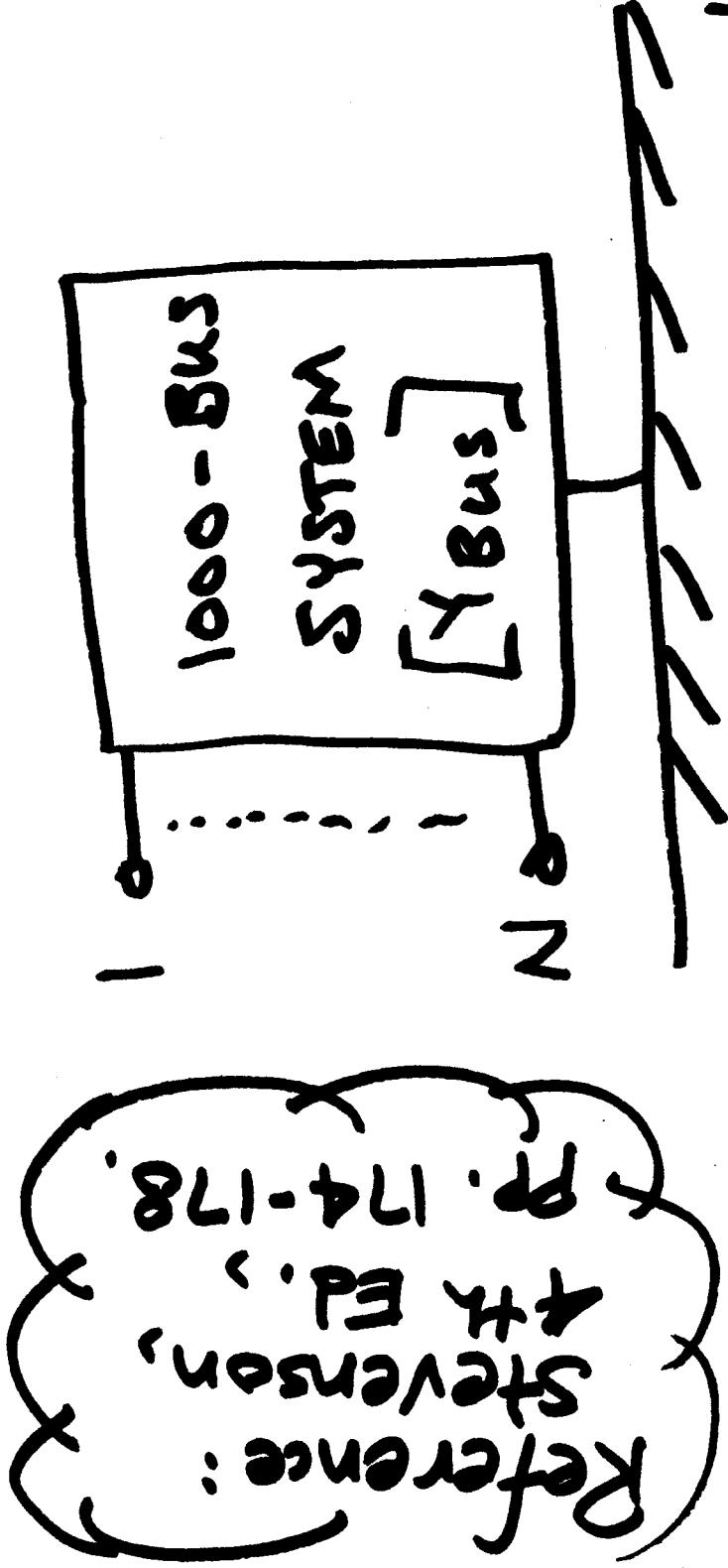

Possible to reduce to
of fewer nodes.

Goal: Only buses of interest need
be observable.

Constraint: Must retain source.
nodes (nodes at which
current is being injected).

STEPS:

- 1) Reorder system to keep to
move buses to $1 \dots K$
top, i.e. $1 \dots K$
Remaining $L \dots Z$ nodes
are absorbed into system.
- 2) Perform Kron Reduction.

$$\begin{bmatrix} K \\ -L \\ -T \end{bmatrix} \begin{bmatrix} L \\ M \\ N \end{bmatrix} = \begin{bmatrix} V_A \\ -V_B \\ V_{Bws} \end{bmatrix}$$

Since $I_x = \begin{bmatrix} 0 & \dots & 0 \end{bmatrix}$

$$\left. \begin{array}{l} I_A = KV_A + LV_B \\ I_x = LV_A + MV_B \end{array} \right\}$$

(1) (2)

$$(3) -L^T V_A = M V_B \leftarrow \text{From Eqn. (2)}$$

for $I_x = 0$.

$$(4) -M^{-1} L^T V_A = V_B \leftarrow \text{premultiplies both sides by } M^{-1}.$$

Substituting V_B into Eqn. (1),

$$I_A = K V_A - L M^{-1} L^T V_A$$

$$\begin{bmatrix} I_A \end{bmatrix} = \underbrace{\begin{bmatrix} K - L M^{-1} L^T \end{bmatrix}}_{\{ \}} \begin{bmatrix} V_A \end{bmatrix}$$

The $[V_{Bns}]$ for this reduced system is thus implied to be $[K - L M^{-1} L^T]$. Derivation assumes bilateral system (note L, L^T)

Reduced $[Y_{bus}]$ is

$$\begin{bmatrix} Y_{bus} \\ \text{Reduced} \end{bmatrix} = K - L M^{-1} L^T$$

IMPORTANT OBSERVATION:
If $L \& L^T$ are off-diagonals,
then this egn. only valid for bilateral
System!