

Topics for Today:

- Questions/Comments on Homework #4 ?
- LU Factorization (needed for each iteration)
- Loadflow Formulation: “NR Details” handout (Week 4)
- NR Algorithm implementation.
- More on Transformers, phase shifters

Coming up:

- More MatLab - build Jacobian, solve for $\Delta\delta$ and ΔV , iterate.
- Data structures
- Reordering to avoid zero divides and/or speed up solution.

LU Factorization (Crout's Method)

There are two approaches:

- "in situ" methods
- Sparse matrix storage.

- By rows (example shown here)
- By columns (your text's approach)

Basic Procedure:

1. Copy Column one
2. Divide Row 1 off-diagonal entries by diagonal term of Row 1.
3. For each element i,j where $i > 1$ and $j > 1$, subtract from it the product of $a_{i1} \cdot a_{ij}$. ~~rank~~
4. If the resulting sub-matrix is of ~~order 2~~ or greater, go back to step 1 and perform the same operations on that sub-matrix.

Example:

$$\begin{aligned}
 [A][X] &= [Y] \\
 \underbrace{[L][U]}_{*}[X] &= [Y] \\
 [L][Z] &= [Y] \rightarrow \text{solve for } Z \quad ① \\
 [U][X] &= [Z] \rightarrow \text{solve for } [X] \quad ②
 \end{aligned}$$

Step 2

$$\left[\begin{array}{cccc|c} 2 & 4 & 4 & 2 & 6 \\ 3 & 3 & 1 & 2 & -1 \\ 2 & 4 & -1 & 2 & 1 \\ 4 & 2 & 1 & 1 & 1 \end{array} \right] \Rightarrow$$

(1) (2) (3)

$$\left[\begin{array}{cccc|c} 2 & 2 & 2 & -1 & 6 \\ 3 & -3 & 0 & 0 & 3 \\ 2 & 0 & -5 & 0 & 0 \\ 4 & -6 & -7 & -3 & 0 \end{array} \right]$$

$$U = \begin{pmatrix} 1 & 2 & 2 & 1 \\ 0 & 1 & -2 & -1 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{pmatrix}$$

CHECK!

$$\underline{\underline{[L][U]}} \stackrel{?}{=} [A]$$

$$L = \begin{pmatrix} 2 & 0 & 0 & 0 \\ 3 & -3 & 0 & 0 \\ 2 & 0 & -5 & 0 \\ 4 & -6 & -19 & -9 \end{pmatrix}$$

$$L = \begin{pmatrix} 2 & 2 & 2 & -1 \\ 3 & -3 & -2 & -1 \\ 2 & 0 & -5 & 0 \\ 4 & -6 & -19 & -9 \end{pmatrix}$$

$$\left[\begin{array}{ccc|c} 2 & 0 & 0 & 6 \\ 0 & 4 & 0 & 8 \\ 0 & 0 & 2 & 4 \\ 0 & 0 & 0 & 6 \\ 0 & 0 & 0 & 4 \end{array} \right] = \left[\begin{array}{c} x_1 \\ x_2 \\ x_3 \\ x_4 \end{array} \right] = \left[\begin{array}{c} 8 \\ 4 \\ 0 \\ 10 \\ 10 \end{array} \right]$$

"A Fill" = changing a zero to non zero entry.

Key: Re-order the equations to minimize fills.

Jacobian Structures

$$\begin{bmatrix} \frac{\partial P}{\partial s} & \frac{\partial P}{\partial v} \\ \frac{\partial Q}{\partial s} & \frac{\partial Q}{\partial v} \end{bmatrix} \begin{bmatrix} \Delta S \\ \Delta V \end{bmatrix} = \begin{bmatrix} \Delta P \\ \Delta Q \end{bmatrix}$$

8 Equation Forms

$\text{Nzr} = \text{find}(\gamma(i:\alpha))$

$\text{Nzr} = \text{find}(\gamma(i:\infty))$

$\text{Nzr} = [1 \ 2 \ 3 \ 4 \ 5]$

```
for n = 1 : length(r)
```


```
    Y(i, n̄r(n))
```

```
end
```


or : for n = n̄r

```
end
```

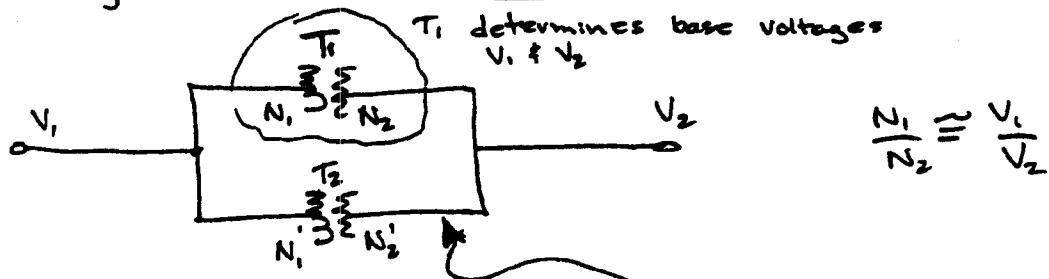Paralleling Transformers of Unlike Turns Ratio



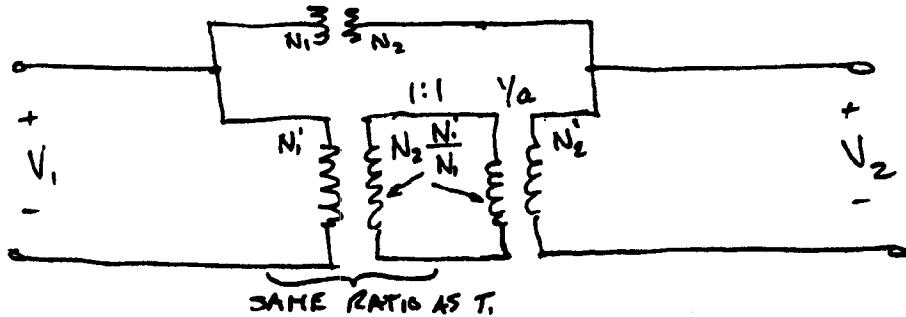What happens for $\frac{N'_1}{N'_2} \neq \frac{N_1}{N_2}$?




Replace T_2 with 2 XFMRS :- First is same ratio

$$\text{as } T_1 \quad \frac{N_1}{N_2} = \frac{N'_1}{X}$$

Second XFMR has ratio of off-nominal turns

$$X = N_2 \frac{N'_1}{N_1}$$

Per unit equivalent:

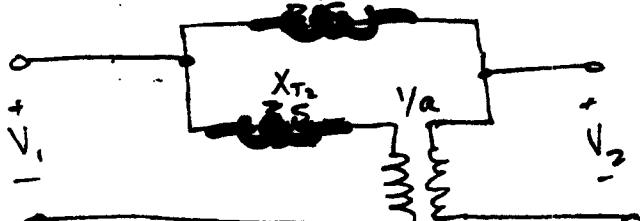


$$\frac{1}{a} = \frac{\left(N_2 \frac{N'_1}{N_1} \right)}{N'_2} = \frac{N_2 N'_1}{N_1 N'_2}$$

$$\therefore a = \frac{N_1}{N_2} \frac{N'_2}{N'_1} = \text{p.u. turns ratio}$$


- Three Methods to Analyze:
- 1) Admittance Method —
 - 2) Circuit Theory —
 - 3) Circulating Current Method (Approximate) —

METHOD 1

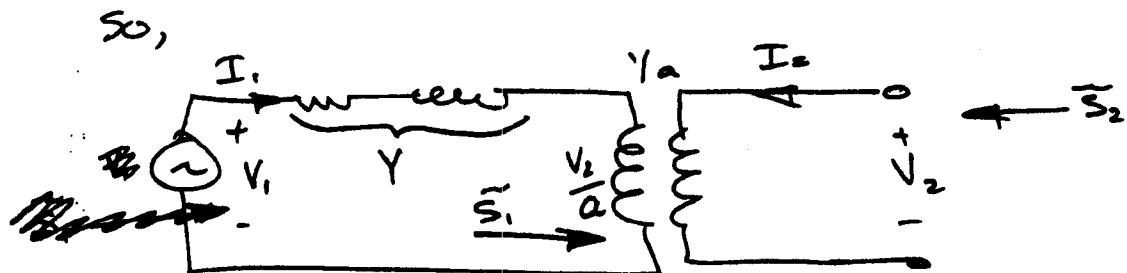

so we must find a way to model Y for Y_{12} as Y_a varies.
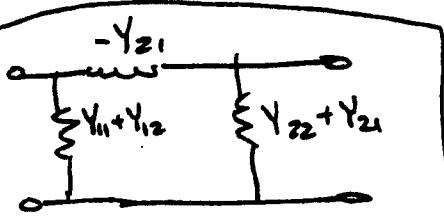
$$\begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{12}V_1 + Y_{22}V_2 \end{aligned}$$



$$\tilde{S}_1 = -\tilde{S}_2$$

$$\tilde{S}_1 = \frac{V_2}{a} I_1^*$$

$$S_2 = V_2 I_2^*$$

$$\frac{V_2}{a} I_1^* = -V_2 I_2^*$$

$$I_1^* = -a I_2^*$$

$$I_1 = -a^* I_2$$

$$I_1 = (V_1 - \frac{V_2}{a})Y = (YV_1 - \frac{Y}{a}V_2) = -a^* I_2 \rightarrow$$


$$I_2 = -\frac{I_1}{a^*} = -\frac{YV_1}{a^*} + \frac{Y}{a a^*} V_2$$


∴

$$Y_{11} = Y \quad Y_{12} = -\frac{Y}{a}$$


$$Y_{21} = -\frac{Y}{a^*}$$

$$Y_{22} = \frac{Y}{a a^*} = \frac{Y}{|a|^2}$$

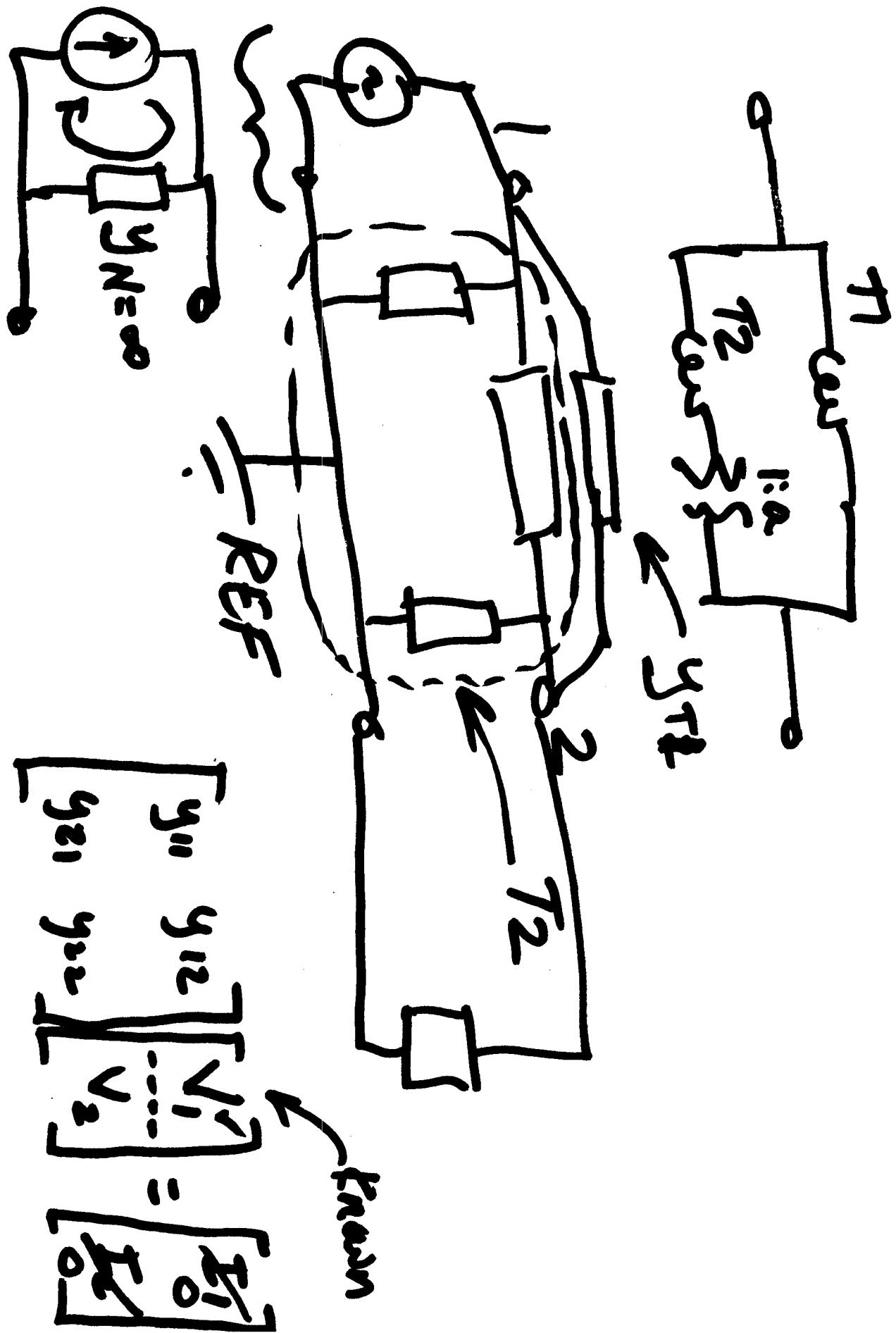

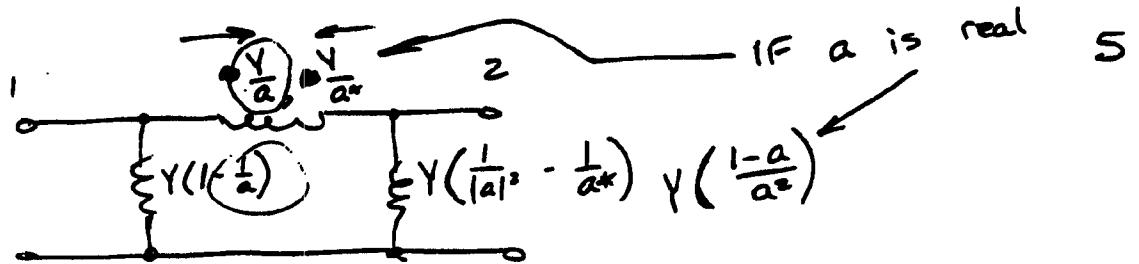

2) CIRCUIT THEORY APPROACH

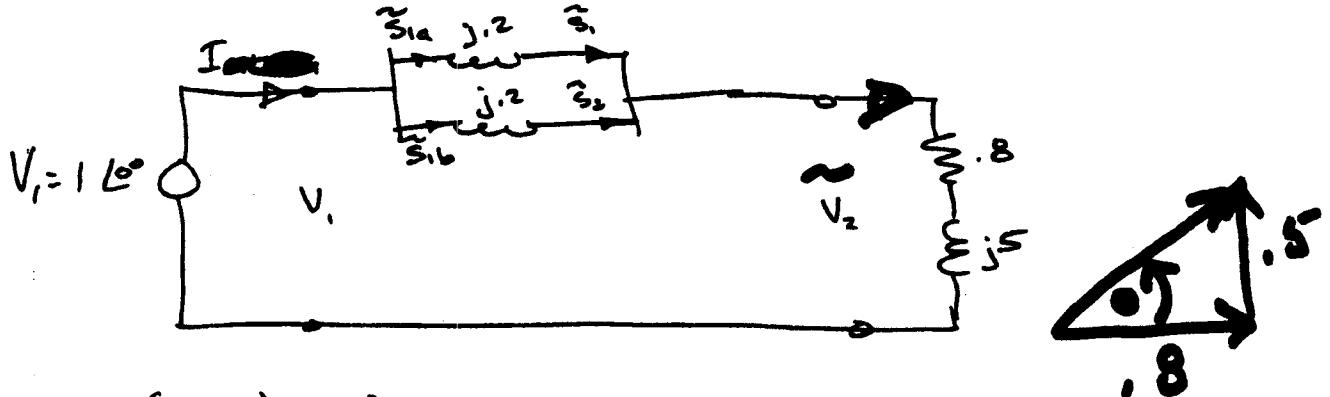

$$V_2 = \frac{(0.8 + j.5)(1(0^\circ))}{0.8 + j.6} = 0.94 - j.08 = 0.9434 \angle -4.86^\circ$$

$$I_2 = \frac{0.94 - j.08}{0.8 + j.5} = 1 \angle -36.87^\circ$$

$$\bar{S}_o = V_I I^* = 0.9434 \angle -4.86^\circ (1 \angle -36.87^\circ) = 0.9434 \angle 32^\circ = 0.8 + j.5$$

$$\begin{aligned} S_1 &= 0.4 + j(25) \\ S_2 &= 0.4 + j(25) \end{aligned} \quad \left. \right\} = \frac{S_{\text{TOTAL}}}{2}$$

$$I_1 = \frac{1}{0.8 + j.6} = 1(0.8 - j.6) = 0.8 - j.6$$


$$S_{1a} = \frac{V_1 I_1^*}{2} = 0.4 + j.3$$

$$S_{1b} = \frac{V_1 I_1^*}{2} = 0.4 + j.3$$

Difference due
to XFMR Inductance

Now add tap changer $a = 1.05$

6

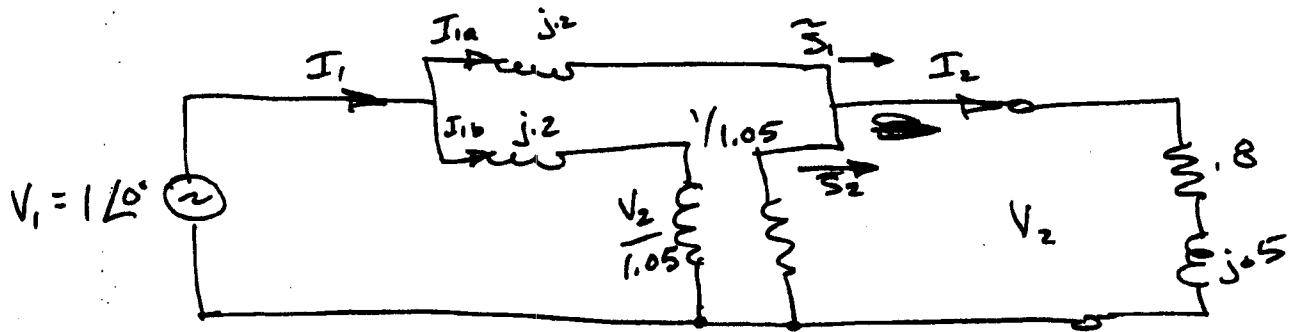

$$I_1 = I_{1a} + I_{1b}$$

$$I_1 = \frac{1 - V_2}{j \cdot 2} + \frac{1 - \frac{V_2}{1.05}}{j \cdot 2}$$

$$I_2 = \frac{1 - V_2}{j \cdot 2} + \frac{1 - \frac{V_2}{1.05}}{j \cdot 2} \left(\frac{1}{1.05} \right)$$

$$V_2 = I_2 (0.8 + j \cdot 5) = \left[\frac{1 - V_2}{j \cdot 2} + \frac{1 - \frac{V_2}{1.05}}{j \cdot 2} \left(\frac{1}{1.05} \right) \right] (0.8 + j \cdot 5)$$

~~$$V_2 = \left(1 - V_2 + \frac{1 - \frac{V_2}{1.05}}{j \cdot 2} \right) \left(0.8 + j \cdot 5 \right) = (1.952 - 1.907 V_2) \left(\begin{matrix} 4.717 \\ -58^\circ \end{matrix} \right)$$~~

~~$$V_2 = -1.907 V_2 (4.717 \angle -58^\circ) + (1.952 \angle 0^\circ) (4.717 \angle -58^\circ)$$~~

~~$$= -8.995 \angle -58^\circ V_2 + 9.207 \angle -58^\circ$$~~

$$V_2 = \frac{9.207 \angle -58^\circ}{1 + 8.995 \angle -58^\circ} = \frac{9.207 \angle -58^\circ}{9.563 \angle -52.9^\circ} = \boxed{.963 \angle -5.1^\circ}$$

$$I_{1a} = \frac{1 - V_2}{j \cdot 2} = \boxed{4.738 \angle -25.54^\circ}$$

$$I_{1b} = \frac{1 - \frac{V_2}{1.05}}{j \cdot 2} = \boxed{.59 \angle -46.75^\circ}$$

$$S_{1a} = V_1 I_{1a}^* = .427 \cancel{\text{}}$$

$$S_{1b} = V_1 I_{1b}^* = .4067 \cancel{\text{}} + j.4324$$

$$\tilde{S}_1 = V_2 I_{1a}^* = (.963 \angle -5.1^\circ) (.4732 \angle 25.53^\circ)$$

$$= .427 + j.16 = S_1$$

$$\tilde{S}_2 = V_2 \frac{I_{1b}^*}{a} = .963 \angle -5.1^\circ \left(\frac{.59 \angle -46.75^\circ}{1.05} \right)^* = .406 + j.3616$$

$$S_2$$

$$\tilde{S} = V_2 I_2^* = (.963 \angle 5.1^\circ) \left(\frac{V_2}{Z} \right)^* = .983 \angle 32^\circ = \tilde{S}_1 + \tilde{S}_2$$

| | <u>Before T.C.</u> | <u>After T.C.</u> | |
|-------|-------------------------|-------------------------|------------------------|
| | | <u>Circ. Approx.</u> | <u>Ckt. Analysis</u> |
| V_1 | 1 | 1 | 1 |
| V_2 | .943 \angle -4.86^\circ | .963 \angle -4.87^\circ | .963 \angle -5.1^\circ |
| P_1 | .4 | .398 | .427 |
| P_2 | .4 | .418 | .406 |
| Q_1 | .25 | .135 | .159 |
| Q_2 | .25 | .375 | .362 |


XFB Top Changer XFMR Shifted
 X to XFMR with top arm to higher
 shifted secondary voltage. higher top setting.

So:

Q is shifted to XFMR of higher top setting.
 P is still divided almost evenly.

Approximate solution:

Superposition of circulating current

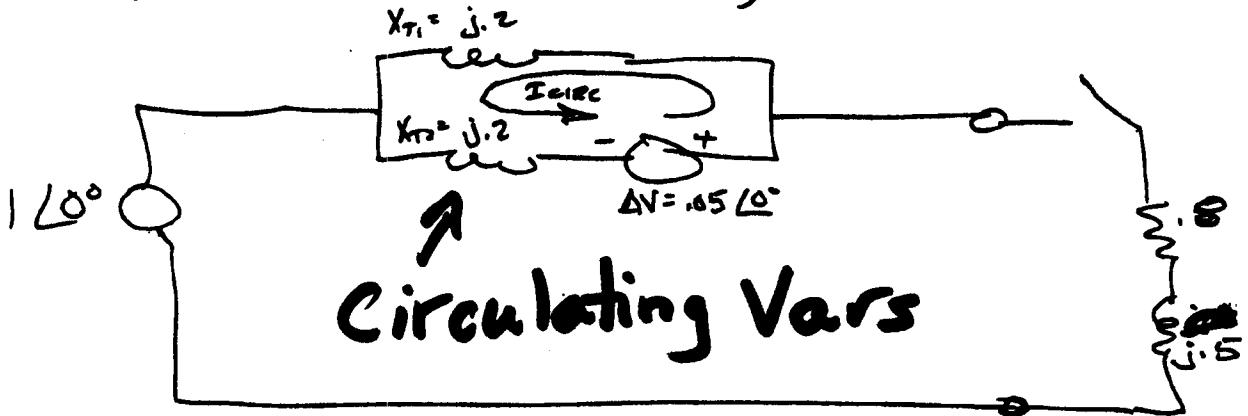

First, look at XFMR before load applied.

$$I_{\text{CIRC}} = \frac{.05 \angle 0^\circ}{j.4} = .125 \angle -90^\circ = -j.125$$

From first example,

~~$$I_{1a} = .4 - j.3 + j.125 = .4 - j.175$$~~

~~$$I_{1b} = .4 - j.3 - j.125 = .4 - j.425$$~~

~~$$\begin{aligned} & I_{1a} = .4 - j.3 + j.125 \\ & I_{1b} = .4 - j.3 - j.125 \\ & \Rightarrow (j.125)(j.2) = .25 \\ & \Rightarrow (j.08 + j.025) = .08 + j.025 \end{aligned}$$~~

By Superposition,

$$\begin{aligned} V_2 &= V_2 \text{ BEFORE } \Delta V \text{ APPLIED} + \frac{\Delta V (jX_{T1})}{jX_{T1} + jX_{T2}} \left[\frac{Z_{\text{LOAD}}}{Z_{\text{TOTAL}}} \right] \\ &= .943 \angle -9.8^\circ + \frac{.05(j.2)}{j.4} \left[\frac{.8 + j.5}{.8 + j.6} \right] \\ &\quad \times \frac{j.5 + (jX_{T1} || jX_{T2})}{(jX_{T1} || jX_{T2})} \end{aligned}$$

$$\begin{aligned} \Delta V_{\text{oc}} &= \frac{\Delta V (jX_{T1})}{(jX_{T1} + jX_{T2})} \\ Z_{\text{TH}} &= jX_{T1} || jX_{T2} \end{aligned}$$

$$V_2 = .963 \angle -4.87^\circ$$


$$S_{1a} = V_2 I_{1a}^* = (.963 \angle -4.87^\circ) (.437 \angle 23.63^\circ)^* = .421 \angle 18.76^\circ$$

$$= .398 + j.135$$

$$S_{2a} = V_2 I_{2a}^* = (.963 \angle -4.87^\circ) (.584 \angle 46.73^\circ)^* = .562 \angle 41.86^\circ$$

$$= .418 + j.375$$

Phase Shifting XFMR

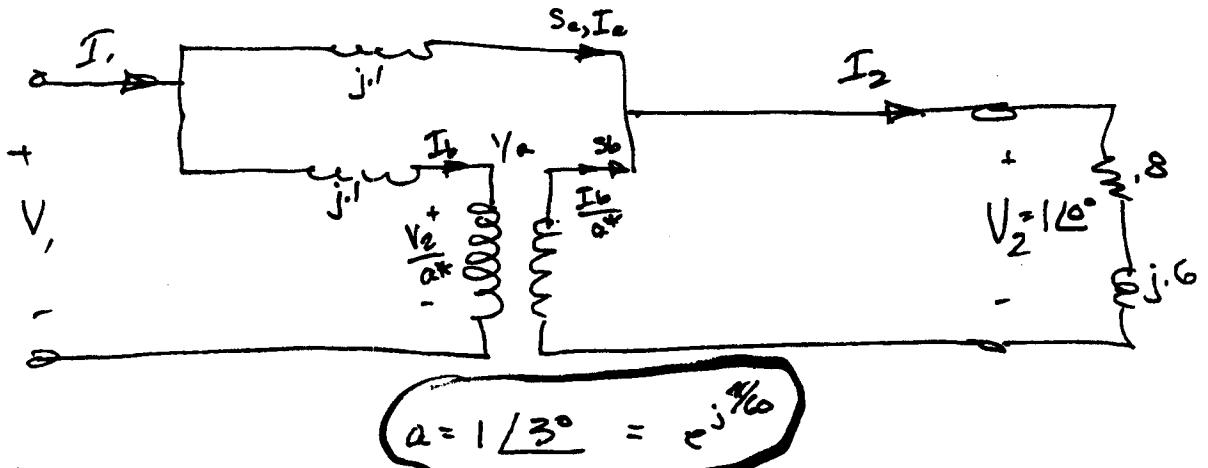

Without phase shifter,

$$P_{LOAD} = \frac{V_2^2}{Z^*} = 1(.8 + j.6) = .8 + j.6$$

$$S_a = .4 + j.3$$

$$S_b = .4 - j.3$$

$$I_a = .4 - j.3$$

$$I_b = .4 - j.3$$

$$V_1 = 1 \angle 10^\circ + (.4 + j.3)(j.1)$$

$$= 1.0307 \angle 22^\circ$$

With Phase Shifter,

$$\frac{V_1 - 1}{j.1} + \frac{V_1 - 1 \angle 10^\circ}{j.1} \left(\frac{1}{1 \angle 3^\circ} \right) = \frac{1}{.8 + j.6} = I_2$$

$$V_1 \left(1 + \frac{1}{1 \angle 3^\circ} \right) - 1 - \left(\frac{1}{1 \angle 3^\circ} \right)^2 = j.1 (.8 + j.6)$$

$$V_1 (1.999 \angle 1.5^\circ) - 1 - \cancel{\left(\frac{1}{1 \angle 3^\circ} \right)^2} = .1 (5.323 + 1.9945 j.4095)$$

$$V_1 = 1.031 \angle 7.3^\circ = 1.031 + j.013$$

~~$$= 1.028 + j.016$$~~

~~$$\frac{1.028 + j.016}{j.1} = 1.922 \angle -60.33^\circ \therefore .159 \angle -5.28^\circ$$~~

$$I_a = \frac{1.031 + j.013 - 1}{j.1} = .131 - j.311$$

$$\frac{I_b}{a^*} = I_2 - I_a = .8 - j.6 - .131 + j.311 = .669 - j.289$$

$$S_a = .131 + j.311$$

$$S_b = .669 + j.289$$


NOTE SHIFT IN POWER FLOW THRU XFRS

| | <u>BEFORE</u> | <u>AFTER</u> |
|-----------|--------------------------|-------------------------|
| I_a | .4 + j.3 | .131 - j.311 |
| I_b/a^* | .4 - j.3 | .669 - j.289 |
| P_a | .4 | .131 |
| P_b | .4 | .669 |
| Q_a | +.3 | .311 |
| Q_b | +.3 | .289 |
| V_1 | $1.031 \angle 2.2^\circ$ | $1.031 \angle 73^\circ$ |
| V_2 | $1.0 \angle 0^\circ$ | $1.0 \angle 0^\circ$ |

if α is at positive angle, power flow through phase shifting XFR increases

Phase-Shifting XFMR:

PS-1

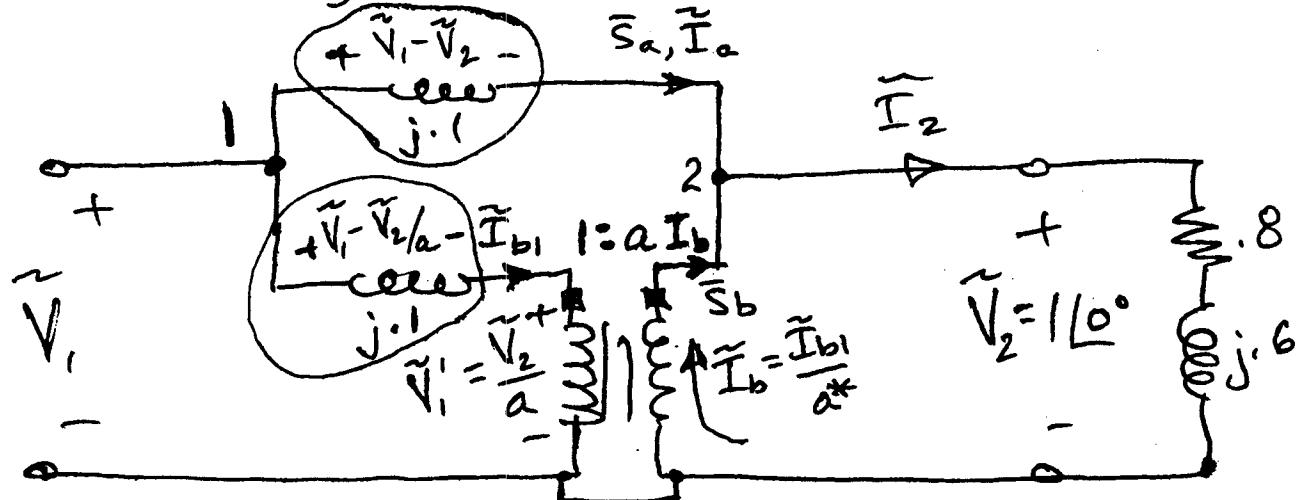

Solve:

KCL at
Node 2

$$\tilde{I}_2 = \frac{\tilde{V}_2}{0.8+j.6} = \frac{\tilde{V}_1 - \tilde{V}_2}{j.1} + \frac{\tilde{V}_1 - \frac{\tilde{V}_2}{a}}{j.1} \left(\frac{1}{\alpha^*} \right)$$

Since \tilde{V}_2 is known (it's typical to state desired load voltage and then solve for required load voltage \tilde{V}_1) we can solve for \tilde{V}_1 . Since $\tilde{V}_2 = 110^\circ$,


$$\frac{1}{0.8+j.6} = \frac{\tilde{V}_1 - 1}{j.1} + \left(\frac{\tilde{V}_1 - \frac{1}{a}}{(j.1)} \right) \frac{1}{\alpha^*}$$

Multiplying through by $j.1$,

$$\frac{j.1}{(0.8+j.6)} = \tilde{V}_1 - 1 + \left(V_1 - \frac{1}{a} \right) \frac{1}{\alpha^*}$$

Grouping, $\tilde{V}_1 \left(1 + \frac{1}{\alpha^*} \right) - 1 - \frac{1}{|a|^2} = \frac{j0.1}{(0.8+j.6)}$

Take a close look at the PS transformer:

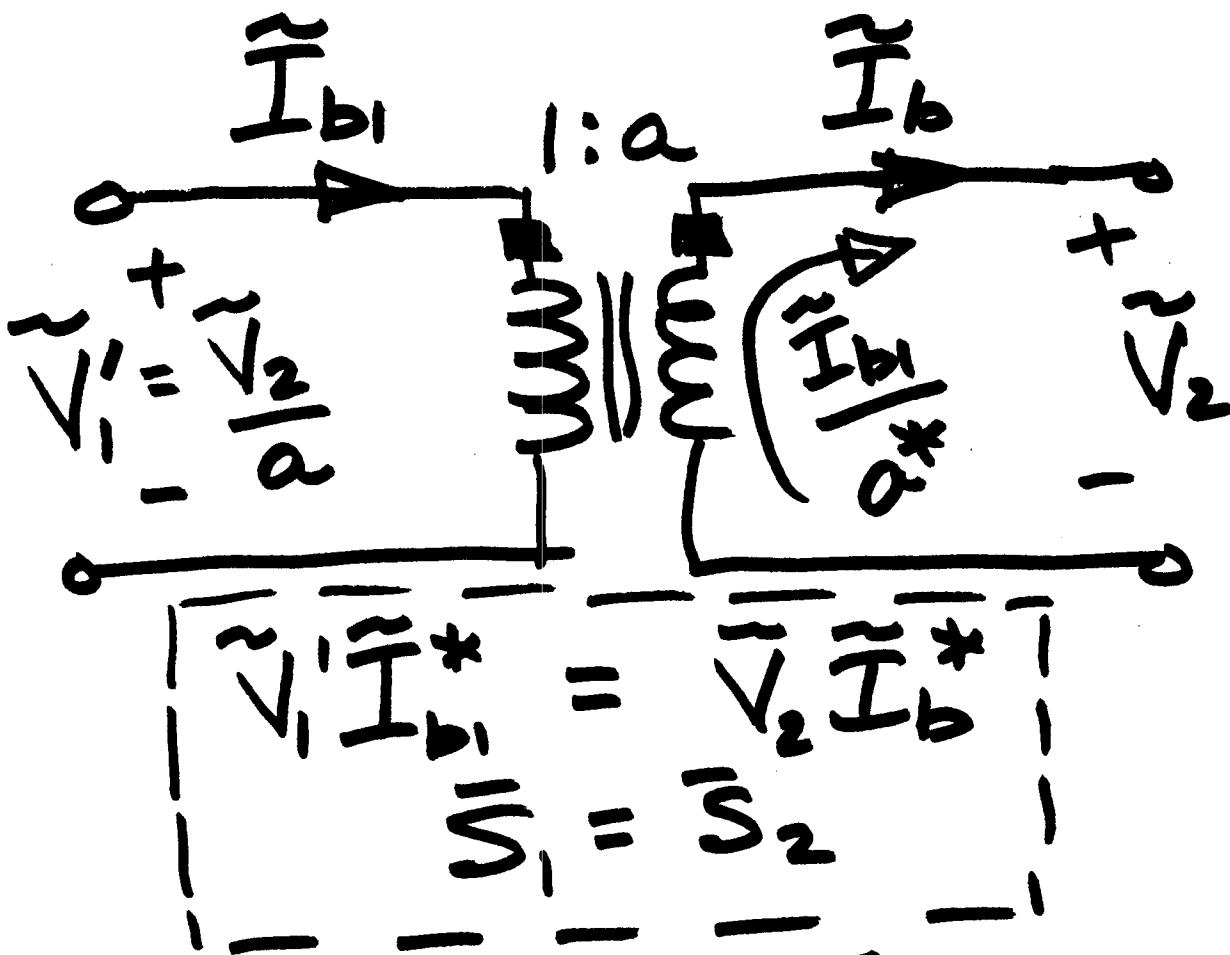

"a" is defined as the voltage ratio:

$$a = \frac{\tilde{V}_2}{\tilde{V}'_1} \Rightarrow \tilde{V}'_1 = \frac{\tilde{V}_2}{a}$$

$$a^* = \frac{\tilde{I}_{b1}}{\tilde{I}_b}$$

$$(\tilde{I}_{b1} = a^* \tilde{I}_b)$$


$$\text{Or, } \tilde{V}_1 = \frac{\frac{j0.1}{(0.8+j1.6)} + 1 + \frac{1}{|\alpha|^2}}{\left(1 + \frac{1}{\alpha^*}\right)}$$

If Load Impedance & transformer reactance are expressed as variables,

$$\tilde{V}_1 = \frac{\frac{jX_T}{Z_{LOAD}} + 1 + \frac{1}{|\alpha|^2}}{1 + \frac{1}{\alpha^*}} \quad \boxed{\tilde{V}_2 = 1 \angle 0^\circ}$$

After \tilde{V}_1 is known, all currents, P_s, Q_s can be solved for. (see next page).

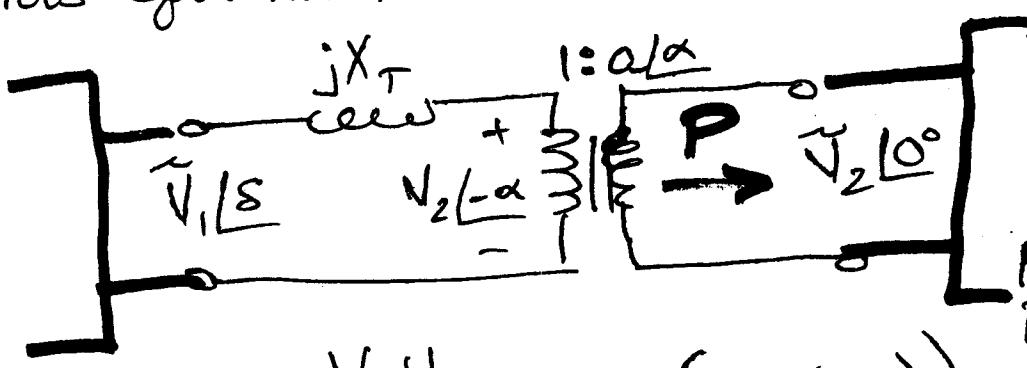We note that, ^{as} the angle of α increases, so does the power flow thru XFMR #2. This is easy to explain using the power flow equation for a short lossless line:




$$P = \frac{V_1 V_2}{X} \sin(S - (-\alpha))$$

Hence, as α increases, so does P .


Summary of Effect of Phase Shift in Parallel Transformers:

| Quantity | Case #1 | Case #2 | Case #3 |
|------------------------------------|----------------|-------------------------------|----------------|
| Turns Ratio "a" | <u>1/-3°</u> | <u>1/0°</u> | <u>1/+3°</u> |
| V ₁ | 1.031 /3.72° | 1.031/2.22° | 1.031/0.72° |
| V ₂ | 1/0° | 1/0° | 1/0° |
| I ₁ | 1.009 /-35.99° | 1.0 /-36.87° = I ₂ | 1.009 /-38.99° |
| I ₂ | 1.0 /-36.87° | 1.0 /-36.87° | 1.0 /-36.87° |
| I _{b1} | 0.337 /-64.23° | 0.5 /-36.87° | 0.730 /-26.38° |
| I _b — | 0.337 /-67.24° | 0.5 /-36.87° | 0.730 /-23.38° |
| I _{a1} = I _a — | 0.730 /-23.38° | 0.5 /-36.87° | 0.337 /-67.24° |
| P ₁ | 0.8000 | 0.8000 | 0.8000 |
| P ₂ | 0.8000 | 0.8000 | 0.8000 |
| P _{a1} | 0.6697 | 0.4000 | 0.1303 |
| P _a — | 0.6697 — | 0.4000 — | 0.1303 — |
| P _{b1} | 0.1303 | 0.4000 | 0.6697 |
| P _b — | 0.1303 — | 0.4000 — | 0.6697 — |
| Q ₁ | 0.6646 | 0.6500 | 0.6646 |
| Q ₂ | 0.6000 | 0.6000 | 0.6000 |
| Q _{a1} | 0.3428 | 0.3250 — | 0.3218 |
| Q _a — | 0.2895 — | — 0.3000 — | — 0.3105 — |
| Q _{b1} | 0.3218 | 0.3250 | 0.3428 |
| Q _b — | 0.3105 — | — 0.3000 — | — 0.2895 — |

$$\begin{aligned}
 Q_{T1} &= \\
 |I_a|^2 X_{T1} \\
 0.5^2 (.1) &= \underline{\underline{.025}}
 \end{aligned}$$

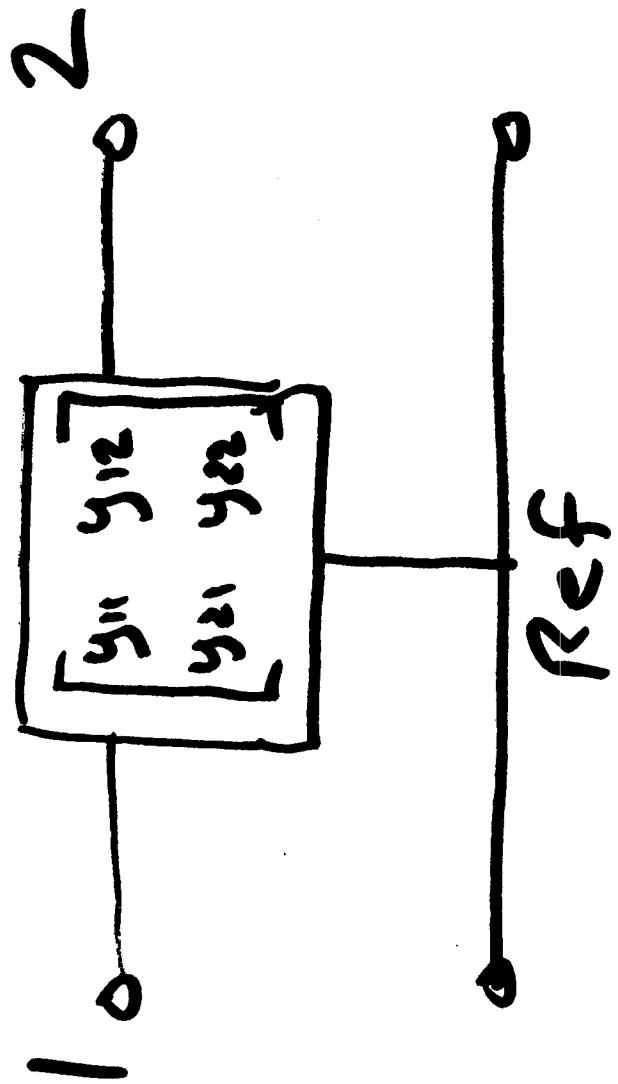
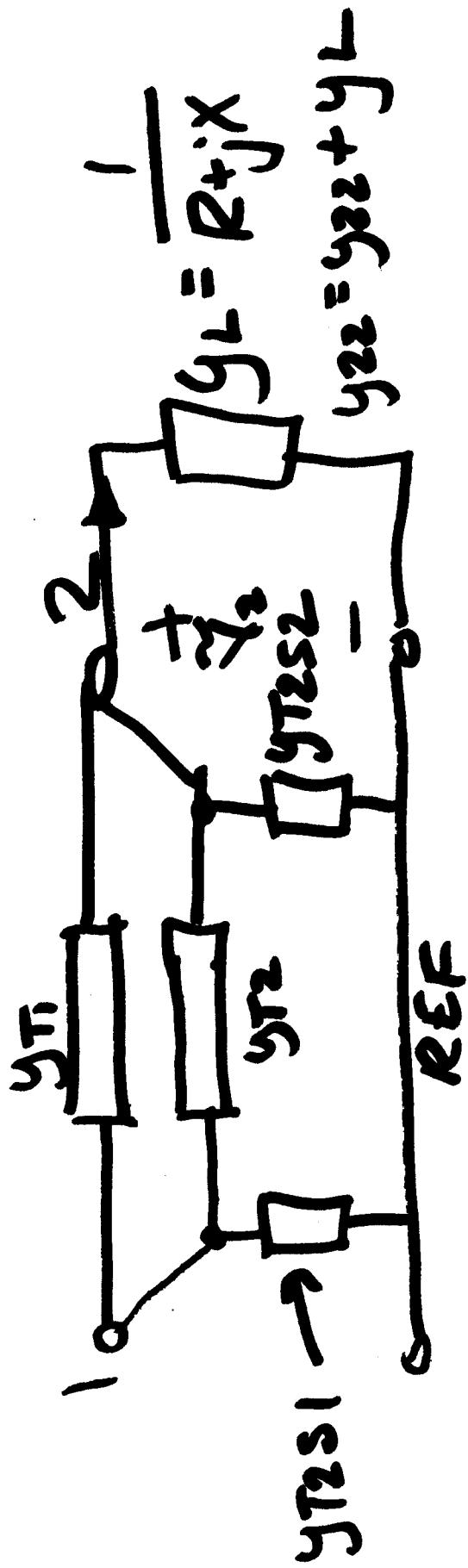
$$\begin{aligned}
 y_{11} &= y_{11} + y_{12} \\
 y_{22} &= y_{22} + y_{12} \\
 y_{12} &= y_{12} - y_{11} \\
 y_{21} &= y_{21} - y_{11}
 \end{aligned}$$



$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} \tilde{I}_1 \\ \tilde{I}_2 \end{bmatrix}$$

$$E_g \angle \sigma = P + V_T \angle 0^\circ$$

$\xrightarrow{\quad}$

$$\frac{jX_s}{\cos \theta} + \frac{V_2^2}{X_s}$$

$\xrightarrow{\quad}$

$$V_1 \angle \delta_1 -$$

$$P = \frac{E_g V_T}{X_s} \sin(\delta)$$

$$P_{1 \rightarrow 2} = \frac{V_1 V_2}{X_s} \sin(\delta_1 - \delta_2)$$