
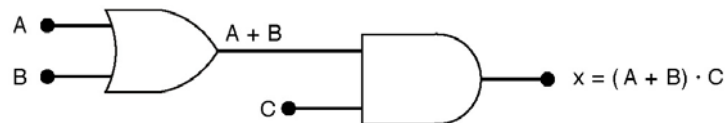


3-6 Describing Logic Circuits Algebraically

- The three basic Boolean operations (OR, AND, NOT) can describe any logic circuit.
- Operator Precedence:
 - If an expression contains both AND and OR gates the AND operation will be performed first, unless there is a parenthesis in the expression.

3-6 Describing Logic Circuits Algebraically

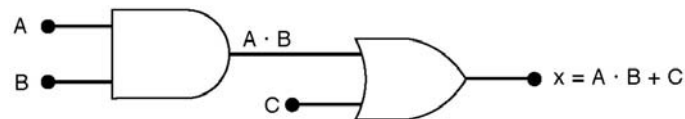- Examples of Boolean expressions for logic circuits:



Example - continued



A	B	C	$X = AB + C$	$X = (A+B).C$
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	0
1	1	1	1	1

EET2141
DIGITAL SYSTEMS/MICROPROCESSORS
BASICS

Slide - 56

3-6 Describing Logic Circuits Algebraically

- The output of an inverter is equivalent to the input with a bar over it. Input A through an inverter is \bar{A}
- Examples using inverters.
- Is $A+B$ equivalent to $\bar{\bar{A}+B}$?

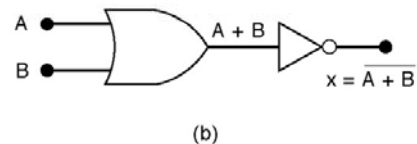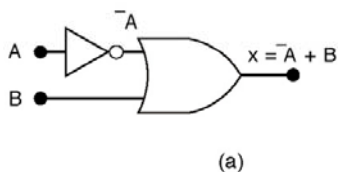

EET2141
DIGITAL SYSTEMS/MICROPROCESSORS
BASICS

Slide - 57

3-7 Evaluating Logic Circuit Outputs

- Rules for evaluating a Boolean expression:
 - Perform all inversions of single terms.
 - Perform all operations within parenthesis.
 - Perform AND operation before an OR operation unless parenthesis indicate otherwise.
 - If an expression has a bar over it, perform the operations inside the expression and then invert the result.

3-7 Evaluating Logic Circuit Outputs

- Evaluate Boolean expressions by substituting values and performing the indicated operations:

$$A = 0, B = 1, C = 1, \text{ and } D = 1$$

$$x = \overline{A}BC\overline{(A + D)}$$

$$x = \overline{0} \cdot 1 \cdot 1 \cdot \overline{(0 + 1)}$$

$$x = 1 \cdot 1 \cdot 1 \cdot \overline{(0 + 1)}$$

$$x = 1 \cdot 1 \cdot 1 \cdot \overline{1}$$


$$x = 1 \cdot 1 \cdot 1 \cdot 0$$

$$x = 0$$

3-7 Evaluating Logic Circuit Outputs

- Output logic levels can be determined directly from a circuit diagram without using the Boolean expression.
- Easy to use method.
- The output of each gate is noted until a final output is found.
- Start from input and proceed through each gate, writing down the corresponding output until the final output is reached

Example

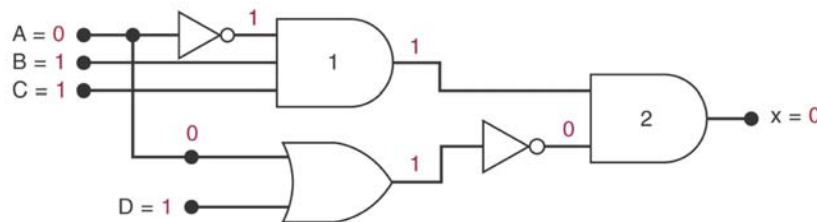

3-8 Implementing Circuits From Boolean Expressions

- It is important to be able to draw a logic circuit from a Boolean expression.
- The expression

$$x = A \cdot B \cdot C$$


Could be drawn as a three input AND gate.

- A more complex example such as

$$y = AC + B\bar{C} + \bar{A}BC$$

Could be drawn as 2, 2-input AND gates and 1, 3 input AND gate feeding into a 3 input OR gate. Two of the AND gates have inverted inputs.


Example - continued

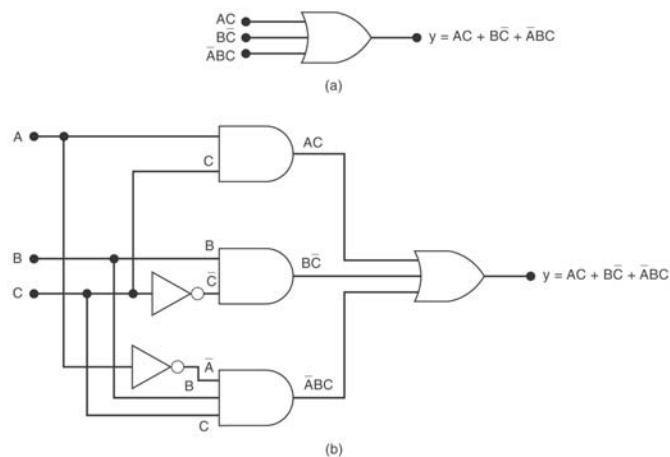


3-9 NOR Gates and NAND Gates

- Combine basic AND, OR, and NOT operations.
- The NOR gate is an inverted OR gate. An inversion “bubble” is placed at the output of the OR gate.
- The Boolean expression is, $x = \overline{A + B}$

NOR - Gate

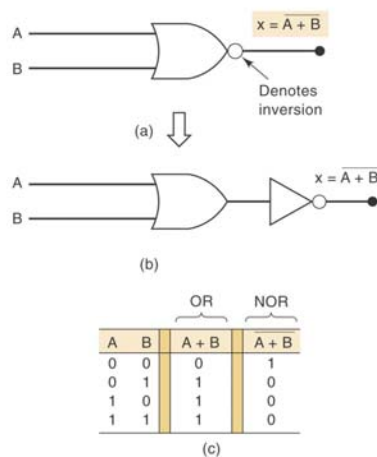

Example 3-8

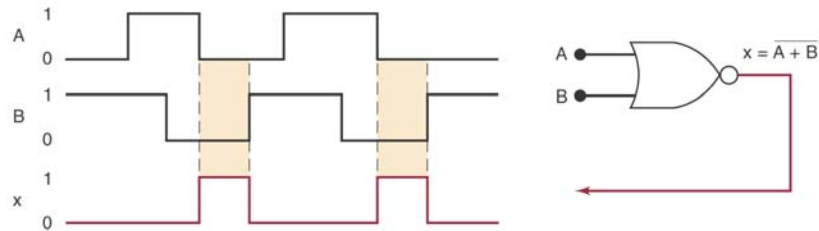


EET2141
DIGITAL SYSTEMS/MICROPROCESSORS
BASICS

Slide - 66

Example 3-9

Determine the Boolean expression for 3-input NOR gate followed by inverter

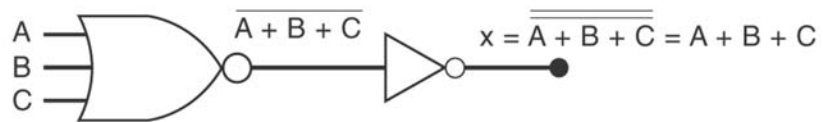


EET2141
DIGITAL SYSTEMS/MICROPROCESSORS
BASICS

Slide - 67


3-9 NOR Gates and NAND Gates - NAND Gate

- The NAND gate is an inverted AND gate. An inversion “bubble” is placed at the output of the AND gate.
- The Boolean expression is, $x = \overline{AB}$

NAND Gate

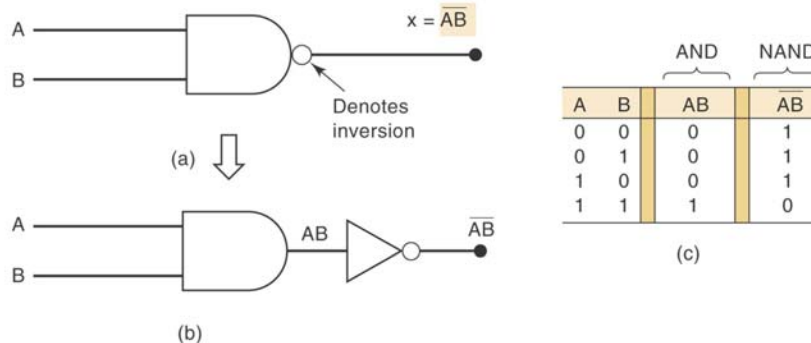

Example 3 -10

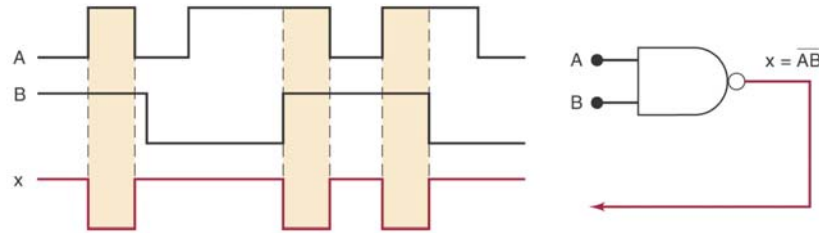

EET2141
DIGITAL SYSTEMS/MICROPROCESSORS
BASICS

Slide - 70

3-9 NOR Gates and NAND Gates


- The output of NAND and NOR gates may be found by simply determining the output of an AND or OR gate and inverting it.
- The truth tables for NOR and NAND gates show the complement of truth tables for OR and AND gates.

EET2141
DIGITAL SYSTEMS/MICROPROCESSORS
BASICS

Slide - 71

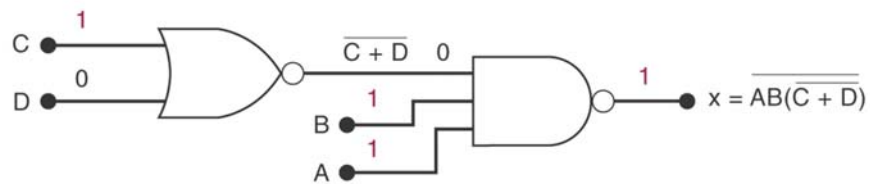Example 3-11

- Implement the logic circuit $X = \overline{AB} \cdot \overline{(C+D)}$



- Determine the output for $A=B=C=1$ & $D=0$