 



7-5 Synchronous Down and Up/Down Counters

- The synchronous counter can be converted to a down counter by using the inverted FF outputs to drive the JK inputs.
- FF B toggles when $A = 0$ on the next NGT CLK.
- The count sequence is 15, 14, 13, ..., 1, 0, 15.



Slide - 225

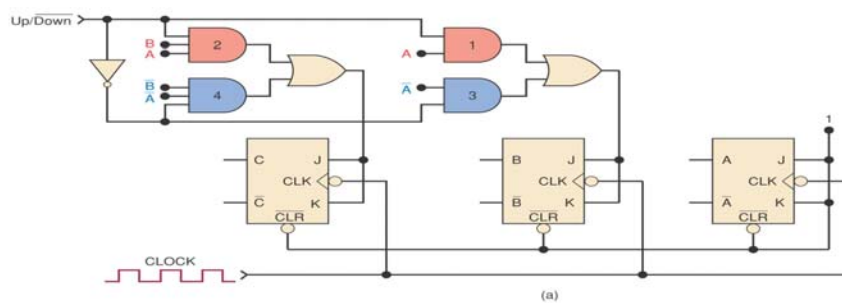7-5 Synchronous Down and Up/Down Counters




- A synchronous counter can be made an up/down counter by connecting as illustrated.
- The control input Up/Down controls whether the normal FF outputs or the inverted FF output are fed to J and K inputs of the successive FFs.

Slide - 226

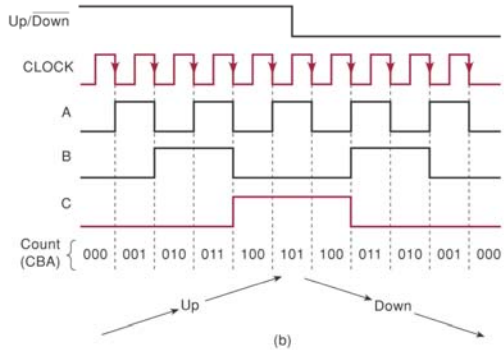
7-5 Synchronous Down and Up/Down Counters

- When the input Up/Down is High, the counter is UP, if it is Low, it is configured as DOWN counter.
- The UP/Down shown is High for 5 pulses (UP) and Low for 5 pulses (DOWN).



 
7-6 Presettable Counters

- A presettable counter can be set to any desired starting point either asynchronously or synchronously.
- The preset operation is also called parallel loading the counter.
- J, K, and CLK are wired as UP counter.
- The counter is loaded with any desired value P_2, P_1, P_0



7-6 Presetable Counters

- A low pulse on PL^* will perform asynchronous transfer into FF Q_2, Q_1, Q_0 . The effect of CLK will be disabled as long as PL^* is active, when PL^* is inactive, counter is Synchronous.
- If $P_2=1, P_1=0, P_0=1$ and PL^* is active, Q_2 will be set, Q_1 will be cleared, and Q_0 will be set which will be held as long as PL^* is active,
- $J, K,$ and CLK are wired as UP counter.
- The counter is loaded with any desired value P_2, P_1, P_0

 


EET2411
DIGITAL ELECTRONICS

Slide - 229

7-8 Decoding a Counter

- Decoding is the conversion of a binary output to a decimal value.
- The active high decoder could be used to light an LED representing each decimal number 0 to 7.
- Each AND gate produces a HIGH output for one particular state, AND 0 represents State 0.
- The 8 AND gates can be used to control 8 LED
- Active low decoding is obtained by replacing the AND gates with NAND gates.

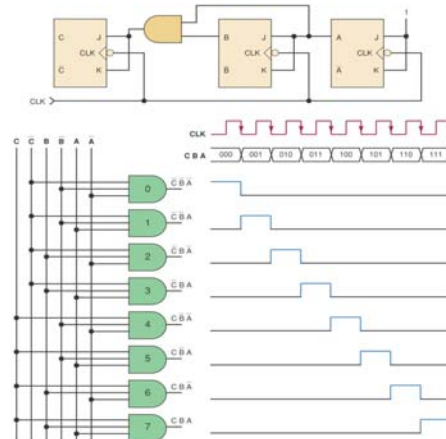

EET2411
DIGITAL ELECTRONICS


Slide - 230

Example 7 -14

- How many AND gates are required to decode completely all the states of a MOD-32 binary counter? What are the inputs to the gate that decodes for the count of 21?
- MOD-32 has 5 FFs, decoder requires 32 AND gates with 5-input, $21_{10} = 10101_2$, inputs are E, D*, C, B*, and A, E is the MSB

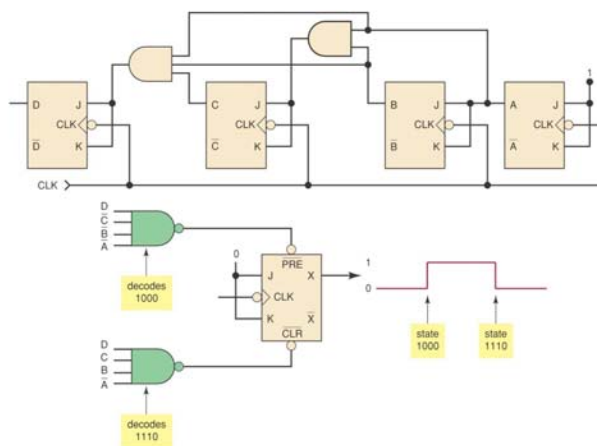Example


- Explain the operation of the following counter?
- X will be HIGH between the count of 8 and 14
- X is a control waveform used to control devices such as a motor



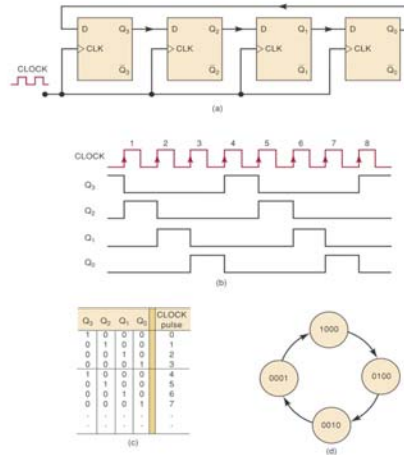7-20 Shift Register Counters

- Ring Counter


- Last FF shifts its value to first FF
- Uses D-type FFs (JK FFs can also be used)
- In most instances, start with only one FF in the 1 state and all others in the 0 state. The waveforms, state diagram and sequence table is shown.
- Information shifts from left to right and back around from Q0 to Q3
- Can function as MOD-4 counter since it has 4 distinct states. How many FFs are needed to construct MOD-8 ring counter.
- Can be decoded without decoding logic.



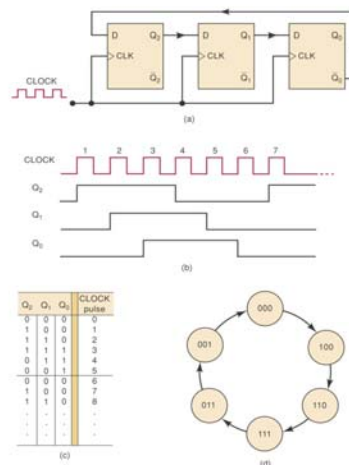7-20 Shift Register Counters

- Johnson counter

- Also called a twisted ring counter
- Same as ring counter but the inverted output of the last FF is connected to input of the first FF
- On each positive CLK, Q2 is shifted to Q1, Q1 is shifted to Q0, and inverse of Q0 is shifted into Q2
- Assuming all FFs are initially 0s, the counter has 6 states – 000, 100, 110, 111, 011, 001. it is MOD-6 (not normal binary count)
- The waveform of each FF is a square wave (50% duty cycle) and 1/6 of the frequency.
- The MOD number is twice the number of FFs



7-20 Shift Register Counters

- Johnson counter
 - For a given MOD number, A Johnson counter requires $\frac{1}{2}$ FFs compared to ring counter. On the other hand, it does require decoding gates.
 - Decoding logic requires only 2-input since in each count, two of the three FFs are in a unique combination of states as shown.

