 


## 5-2 NOR Gate Latch

- The NOR latch is similar to the NAND latch except that the  $Q$  and  $\bar{Q}$  outputs are reversed.
- The set and clear inputs are active high, that is, the output will change when the input is pulsed high.
- In order to ensure that a FF begins operation at a known level, a pulse may be applied to the set or clear inputs when a device is powered up.


### NOR gate latch: truth table and simplified block symbol



Set	Clear	Output
0	0	No change
1	0	$Q = 1$
0	1	$Q = 0$
1	1	Invalid*

\*Produces  $Q = \bar{Q} = 0$ .


(b)

 

- Summary of the NAND latch:
  - Set = clear = 0. Normal resting state, outputs remain in state prior to input.
  - Set = 1, clear = 0. Q will go high and remain high even if the set input goes low.
  - Set = 0, clear = 1. Q will go low and remain low even if the clear input goes low.
  - Set = clear = 1. Output is unpredictable because the latch is being set and cleared at the same time.
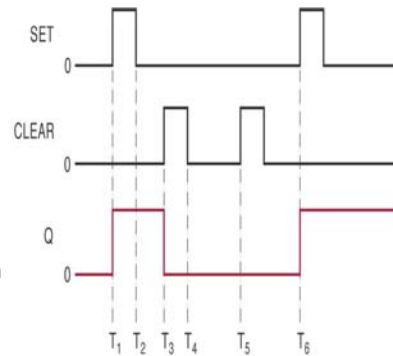
### Example 5-3


- Waveforms are applied at the NOR latch:
  - Assume that initially  $Q=0$ , determine the  $Q$  waveform.
    - $SET=CLEAR=0$ , no change
    - At  $T_1$ , high pulse on  $SET$  causes  $Q$  to go high and remain high
    - At  $T_2$ , low pulse on  $SET$  will cause no effect on  $Q$ .
    - At  $T_3$ , high pulse on  $CLEAR$  will clear  $Q$ ,  $Q=0$  and remains low even after  $CLEAR$  return low at  $T_4$ .
    - At  $T_5$ , high pulse on  $CLEAR$  will have no effect on  $Q$
    - At  $T_6$ , a high pulse on  $SET$  causes  $Q$  to go back High and stays high



Slide - 165
 
## 5-4 Digital Pulses


- Signals that switch between active and inactive states are called pulse waveforms.
  - A positive pulse has an active high level.
  - A negative pulse has an active low level.



Slide - 166
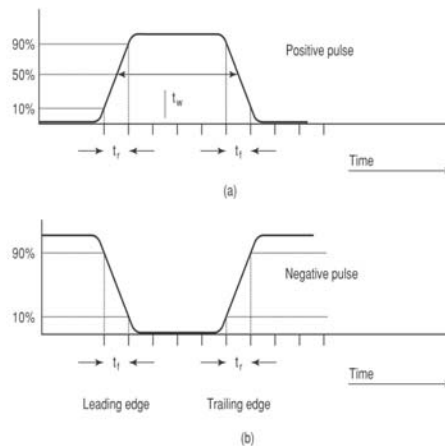
## 5-4 Digital Pulses

- The transition from low to high on a positive pulse is called rise time ( $t_r$ ).
  - Rise time is measured between the 10% and 90% points on the leading edge of the voltage waveform.
- The transition from high to low on a positive pulse is called fall time ( $t_f$ ).
  - Fall time is measured between the 90% and 10% points on the trailing edge of the voltage waveform.
- The pulse width ( $t_w$ ) is defined as the time between the points when the leading and trailing edges are at 50% of the high level.




Slide - 167

EET2411  
DIGITAL ELECTRONICS
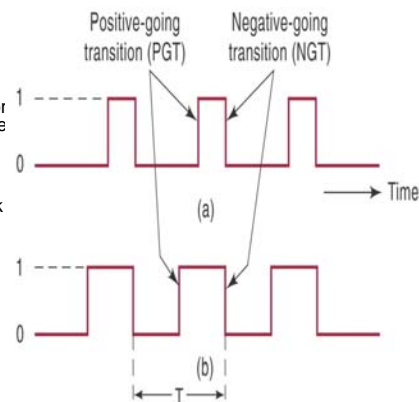
## 5-5 Clock Signals and Clocked Flip-Flops

- Asynchronous system – outputs can change state at any time the input(s) change. Difficult to design and debug.
- Synchronous system – output can change state only at a specific time in the clock cycle.
  - The clock signal is a rectangular pulse train or square wave. It is distributed to all parts of the system.
  - Positive going transition (PGT) – when clock pulse goes from 0 to 1.
  - Negative going transition (NGT) – when clock pulse goes from 1 to 0.
  - Transitions are also called edges.
  - Most digital systems are principally synchronous.
  - The speed of the synchronous system depends on clock speed.
  - A clock period is measured between PGT to the next PGT, seconds/cycle (T).
  - The speed of the system is normally referred as number of cycles in 1 second, Frequency of the clock, (Hertz = 1 cycle/second).




Slide - 168

EET2411  
DIGITAL ELECTRONICS

## 5-5 Clock Signals and Clocked Flip-Flops

- Clocked FFs change state on one or the other clock transitions. Some common characteristics:
  - Clock inputs are labeled CLK, CK, or CP mainly edge-triggered.
  - A small triangle at the CLK input indicates that the input is activated with a PGT.
  - A bubble and a triangle indicates that the CLK input is activated with a NGT.
  - Control inputs have an effect on the output only at the active clock transition (NGT or PGT). These are also called synchronous control inputs.
  - The control inputs get the FF outputs ready to change (determine What), but the change is not triggered until the CLK edge (determine when).

 


EET2411  
DIGITAL ELECTRONICS

Slide - 169

## 5-5 Clock Signals and Clocked Flip-Flops

- Setup time,  $t_s$  is the minimum time interval before the active CLK transition that the control input must be kept at the proper level.
- Hold time,  $t_H$  is the time following the active transition of the CLK during which the control input must be kept at the proper level.

**The control inputs must be stable for at least  $t_s(\text{min})$  prior the clk transition & at least  $t_H(\text{min})$  after the clk transition**

 


EET2411  
DIGITAL ELECTRONICS

Slide - 170

## 5-6 Clocked S-C Flip-Flop

- The set-clear (or set-reset) FF will change states at the positive going or negative going clock edge.
- FF is only affected by PGT transition at points (a, c, e, g, i)

 


EET2411  
DIGITAL ELECTRONICS

Slide - 171

 
### internal circuitry for an edge-triggered S-C flip-flop

- Basic NAND gate latch formed by NAND(3,4)
- Pulse-steering circuit formed by NAND(1,2)
- Edge-detector circuit
- Edge detector produces a narrow positive going spike (CLK\*) that coincident with the PGT of the CLK
- The pulse circuit steers the spike through to the SET or CLEAR input in accordance with the level present on S and C
- When S=1, C=0, the CLK\* produces a low pulse at the SET input of the latch.



Slide - 172

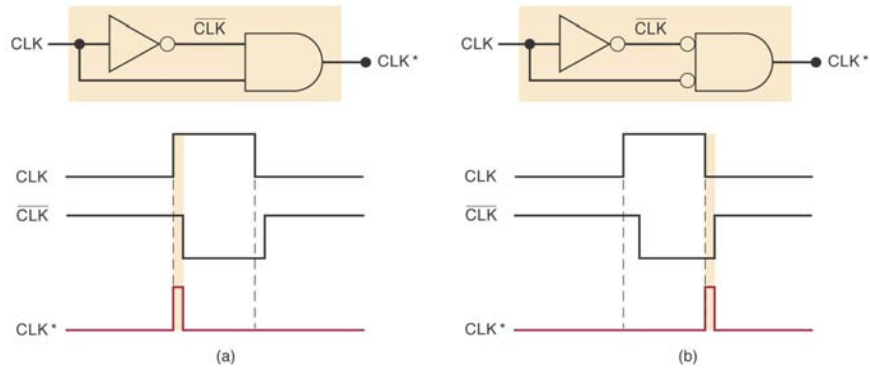
## Implementation of edge-detector circuits used in edge-triggered flip-flops: (a) PGT; (b) NGT.



Slide - 173
 
## 5-7 Clocked J-K Flip-Flop

- Operates like the S-C FF. J is set, K is clear.
- When J and K are both high the output is toggled from whatever state it is in to the opposite state.
- May be positive going or negative going clock trigger.
- Has the ability to do everything the S-C FF does, plus operate in toggle mode.



Slide - 174

## internal circuitry for an edge-triggered J-K flip-flop

- Same as edge-triggered S-C flip-flop
- The only difference is that the  $Q, \bar{Q}$  outputs are fed back to the pulse-steering NAND gate, this causes J-K to toggle for  $J=K=1$
- Assume  $J=K=1$  and  $Q$  is low, NAND gate 1 steers  $CLK^*$  to  $\overline{SET}$  of the NAND latch to produce  $Q = 1$ .
- The opposite will occur if we starts with  $Q=1$

