



Topics for Today:

- Announcements
 - EE5200-L@mtu.edu is soon up and working. Use it.
 - Web page: <http://www.ece.mtu.edu/faculty/bamork/ee5200/>
 - Bring calculator to lectures, for in-class sample calculations.
 - Buy a 3-ring binder for course materials, print 2/page 2-sided.
 - Office hrs: initially set for M,W,F 2-3pm Eastern Time
 - Office: EERC 614. Phone: 906.487.2857
 - Ch.1 Solutions posted on web page, finish review Sept. 13th.
 - First set of graded exercises is posted, due Mon Sept 11th.
 - Ch.2 material - aggressively review it, Ch.2 solutions posted.
- Coverage for Review:
 - Chapter 2 problems (phasors, 3 phase analysis)
 - Click on Pre-Req Mat'ls - Euler's Identity, EE3120 Review
 - Matlab quickstart tutorial, will be using Matlab starting Week 3.
 - Plan on initiating a survey to get a handle on your skill levels.

Prerequisite Material, Useful References (see course web page)

- Euler's Identity - The foundation of phasor analysis, as well as hyperbolic functions (used for long transmission lines)
- Basic Circuit Analysis, Thevenizing, Phasor Analysis, Impedance, P,Q,S, etc.: EE3120 pre-req practice problems | Solutions
- Basic 3-Phase Phasor Analysis - Review problem from EE3120
- Magnetic Circuits - quick review and introduction of how a transformer works
- Mutual Inductance - concept handout from EE3120 (refer to Section 2.2 of your text)
- Transformers 101 - Everything you wanted (or suddenly need to know) about transformers but were afraid to ask...
- Delta-Wye Transformer - detailed example with solution from EE3120
- EE 4221 Pre-Req Course Description
- EE 4222 Pre-Req Course Description
- Pre-Req Review Videos with Notes (from 2003 Archives)
 - Basic Circuit Analysis, Phasors, Three Phase Phasors: Lect 1 (skip first 12 mins) | Lect 1 Notes
 - Phasor Diagrams, Ideal Transformers, Nodal Analysis: Lect 2 (skip first 6:20) | Lect 2 Notes
 - Nodal Analysis, 3-phase circuits, Deltas and Wyes, Per Unit System: Lect 3 (skip first 3 mins) | Lect 3 Notes
 - Active & Passive Sign Convention for power flow, Per Unit, Transformers, Symmetrical Components: Lect 4 (skip first 2 mins) | Lect 4 Notes
 - Transformers, Induced Voltage & Polarity Marks, Phase Shift: Lect 5 (skip 3:45 - 5:20) | Lect 5 Notes
 - Phase Shift in Transformers, Phasor Diagrams, Application of Symmetrical Components: Lect 6 (skip first 3 mins) | Lect 6 Notes
- Matlab Programming (fundamentals). Tutorials: [Part 1 Notes | Part 1 Video]; [Part 2 Notes | Part 2 Video]
 - Sample .m files from above tutorials: | for_ex.m | r2p.m | for_if_ex.m | while_ex.m | ft.m |
- **Symmetrical Components - the basics.**

Transformers -

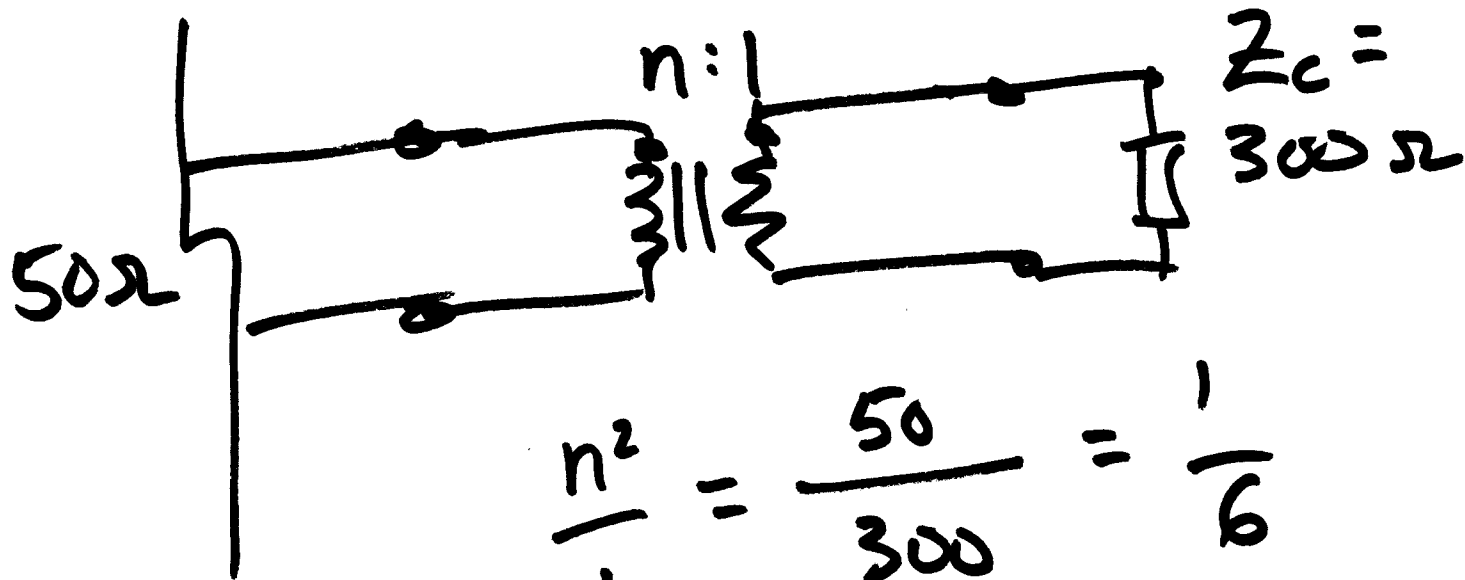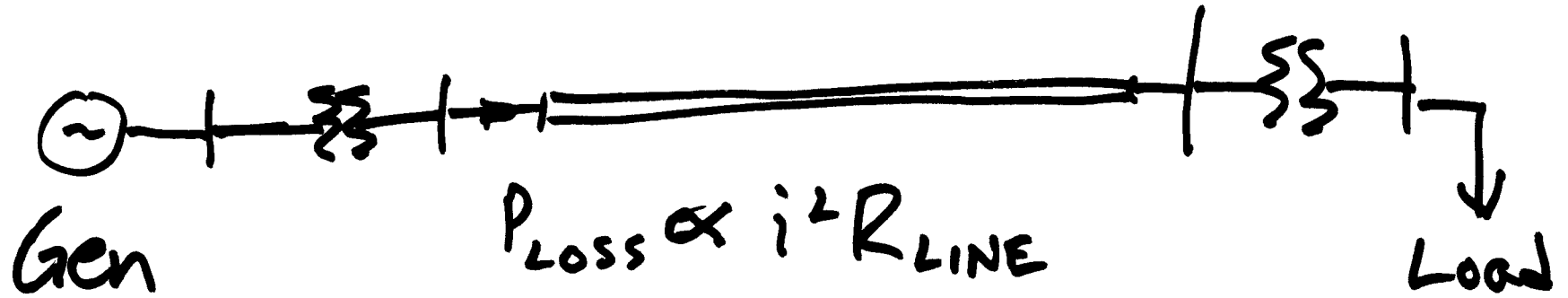

$$\frac{n^2}{1} = \frac{50}{300} = \frac{1}{6}$$

$$\bullet n^2 = \frac{1}{6} \Rightarrow n = \frac{1}{\sqrt{6}}$$




$$\vec{S}_1 = \vec{S}_2$$

(in) (out)


$$\vec{V}_1 \vec{I}_1^* = \vec{V}_2 \vec{I}_2^*$$

IDEAL!

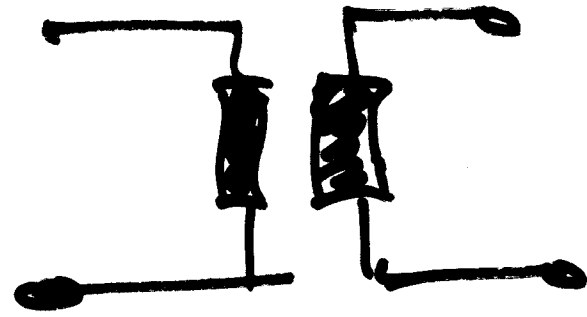

Non-Ideal

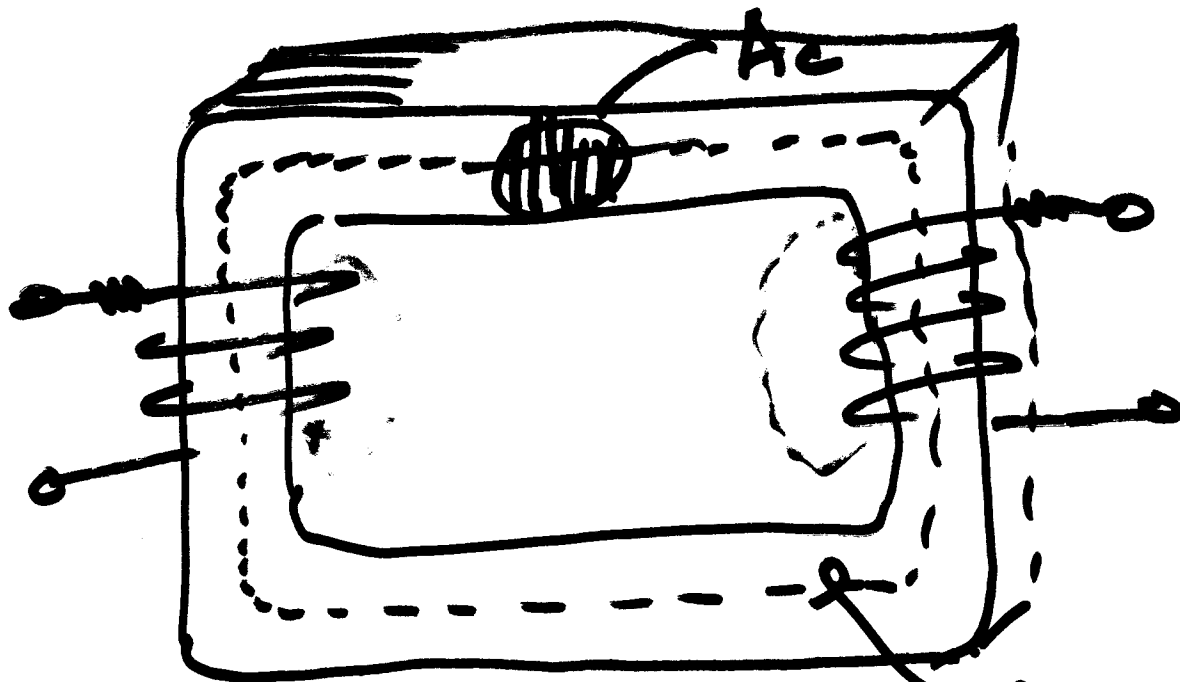- Flux Leakage
- Winding Resistance
- Magnetic Saturation
- Core Losses ← Eddy Currents
Hysteresis






$$R = \frac{l}{nAc}$$

Laminations
 $P_E \propto \frac{1}{\tau^2}$

$$4\pi \times 10^7$$

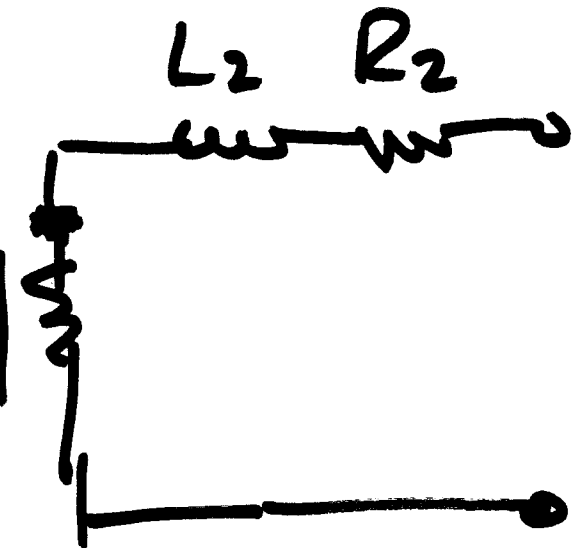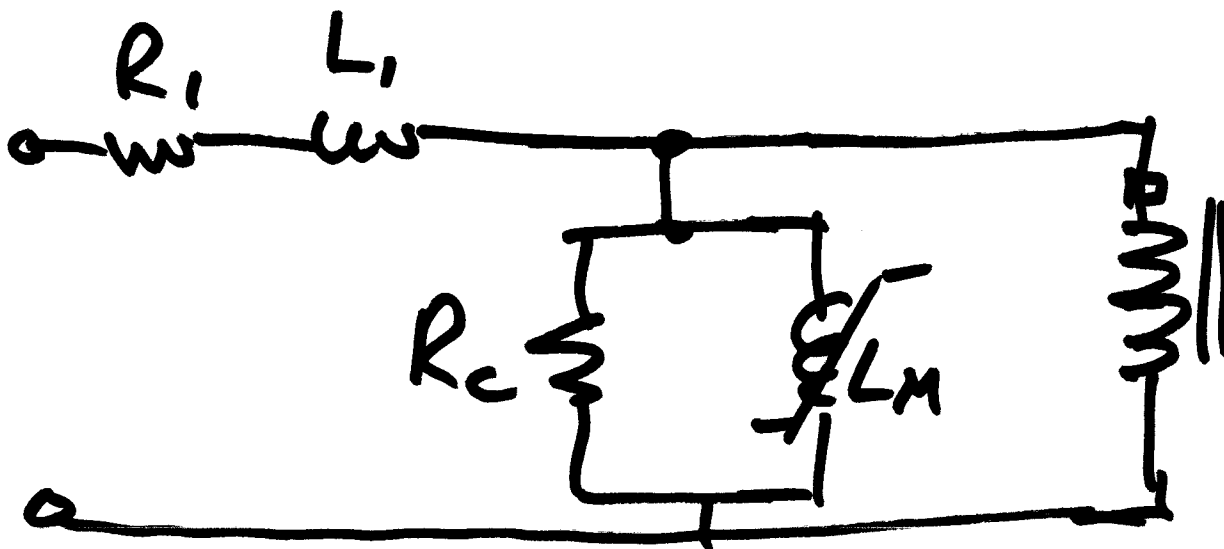
$$\mu = \underline{\underline{\mu_r \mu_0}}$$



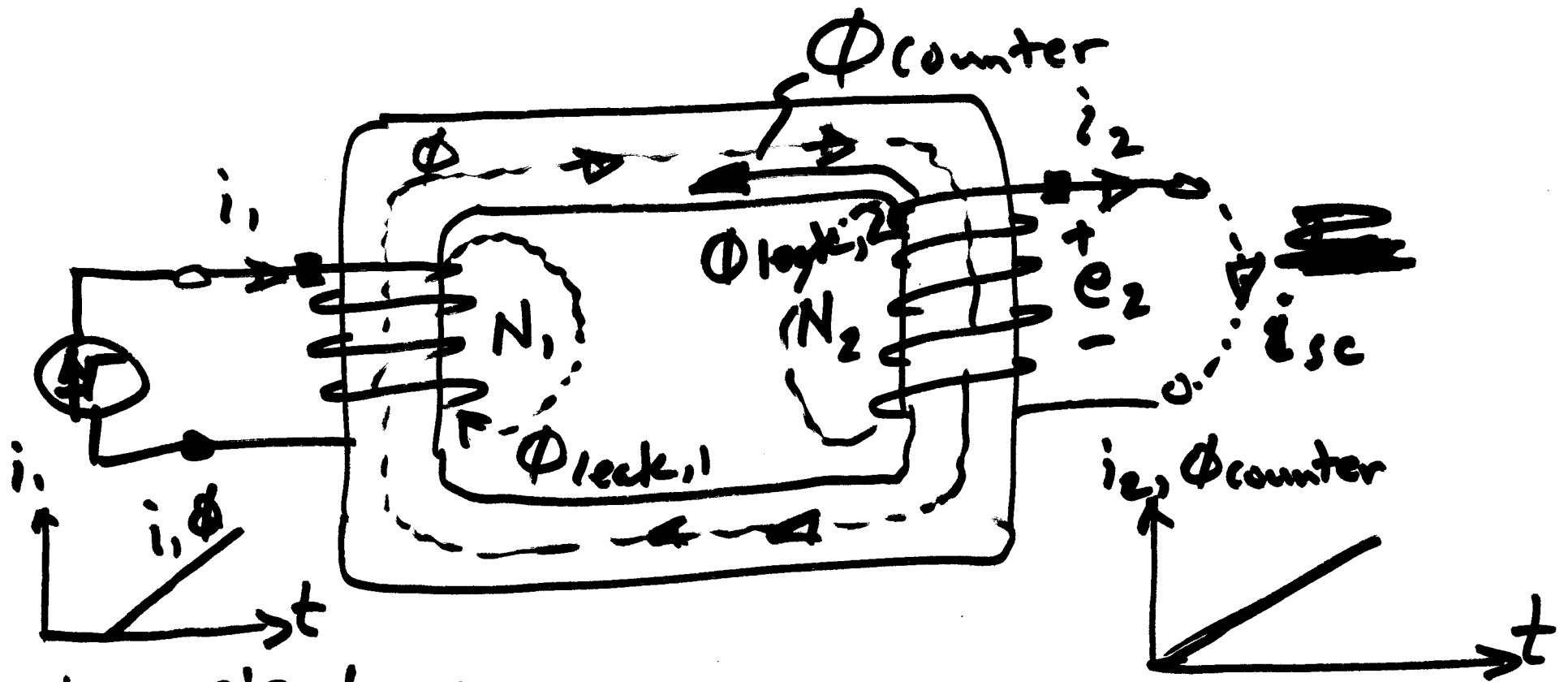

Lenz's Law

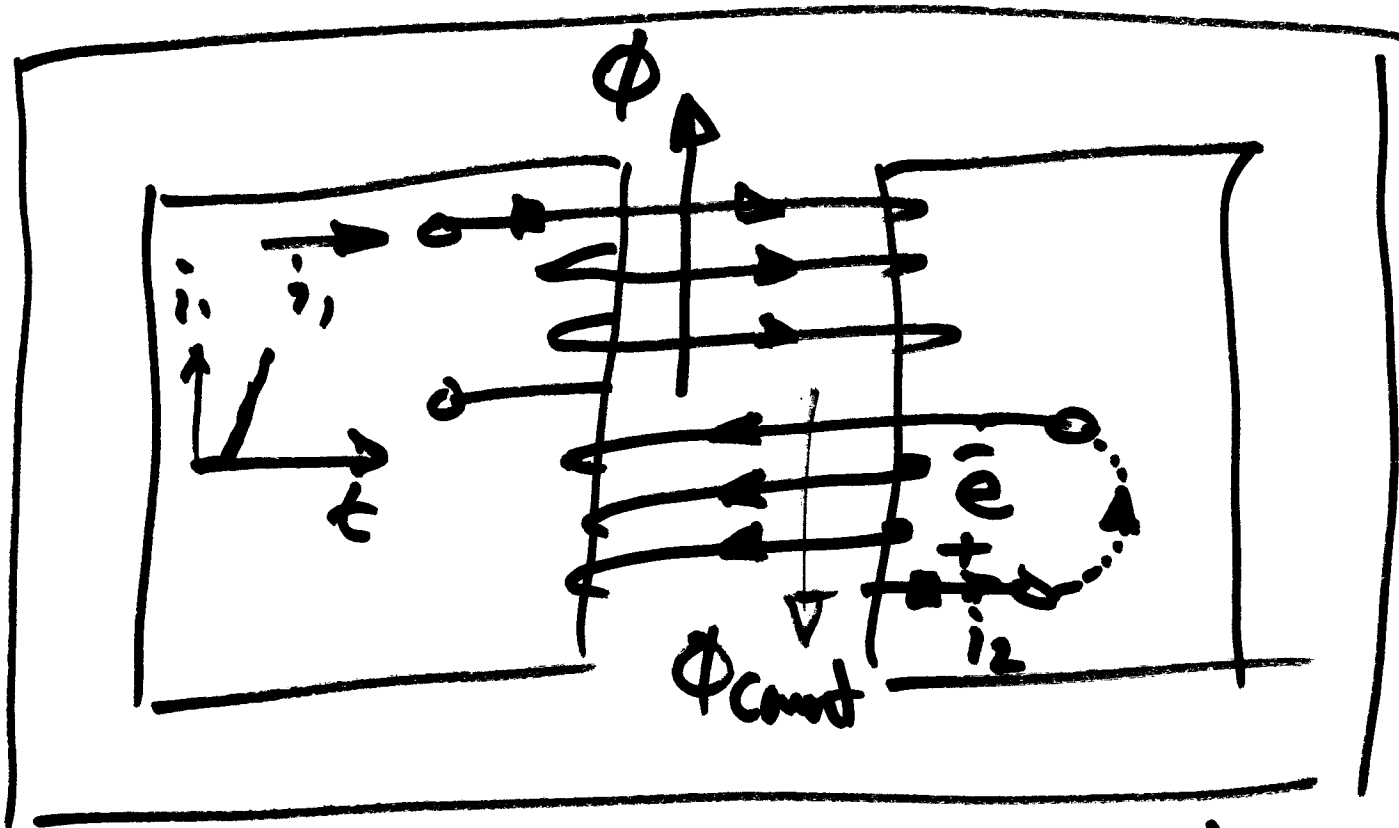
- Induced voltage causes a current, if coil is shorted, that produces a flux which cancels the $\frac{d\Phi}{dt}$ that induced the voltage in first place.



$$e_{\text{ind}} = N \frac{d\Phi}{dt} = - \frac{d\lambda}{dt}$$


Faraday Lenz



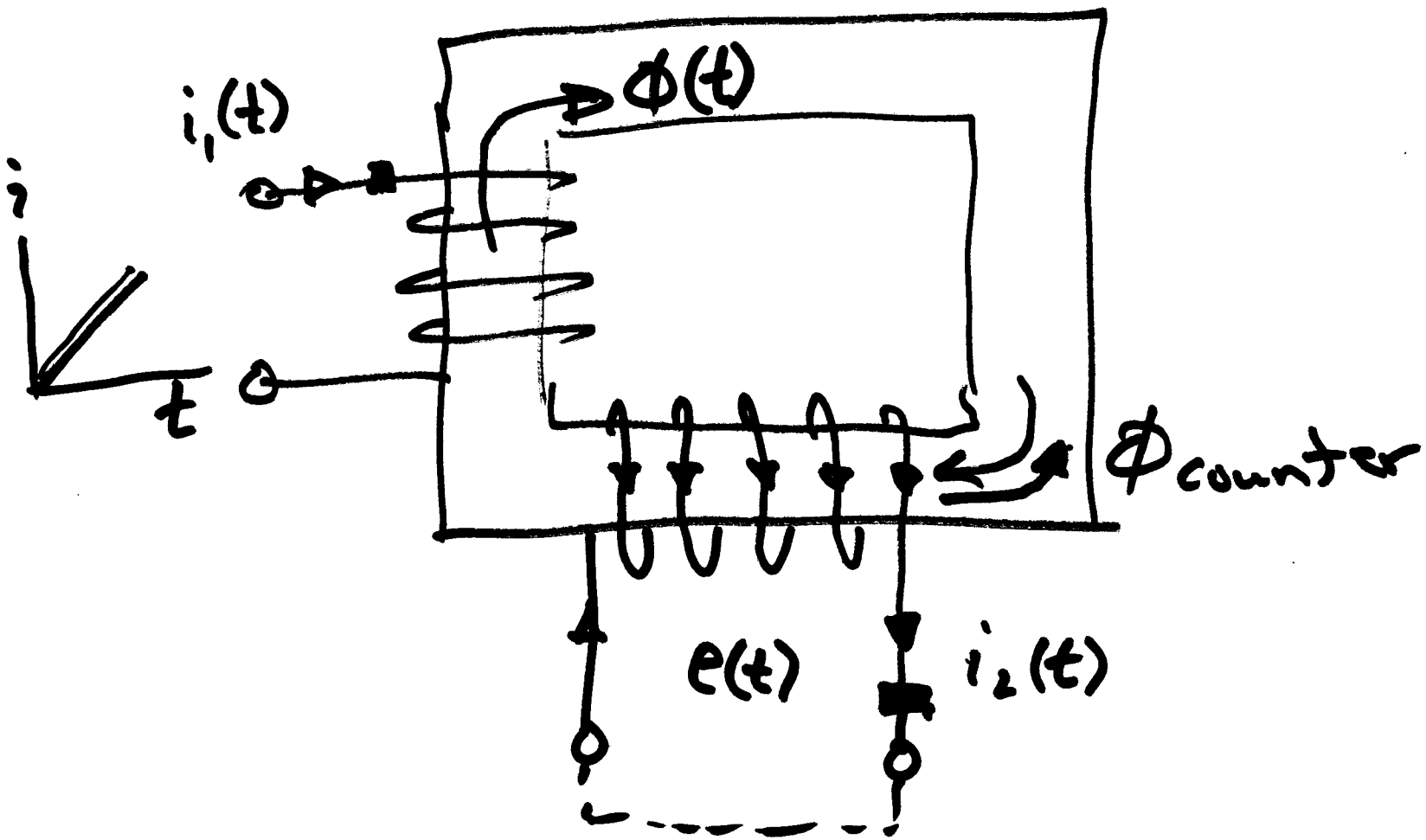


MUTUAL INDUCTANCE

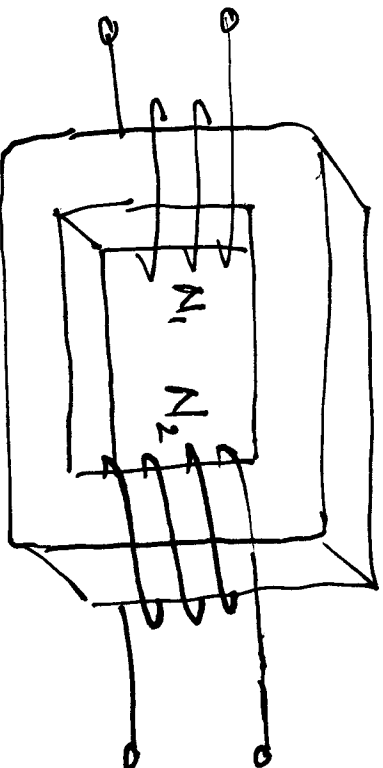- Section 4.4 in text, pp. 73-77.
- See also handout on Basic Magnetic Circuits




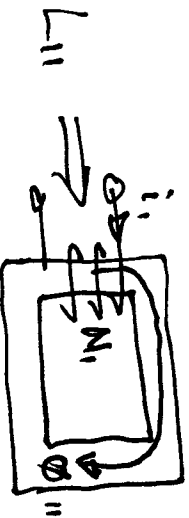- Fundamental definition of inductance: $L = \frac{\tau}{i} = \frac{N\Phi}{i}$




Self-Inductance
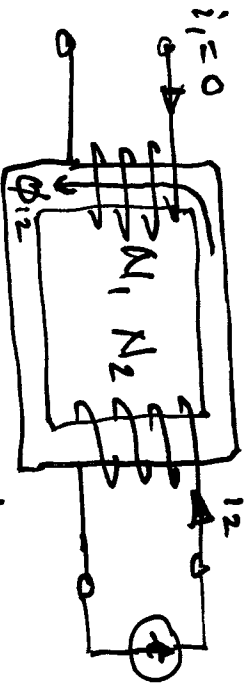
$$L_{11} = \frac{N_1 \Phi_{11}}{i_1} = \frac{\tau_{11}}{i_1} = \frac{N_1^2}{\mathcal{R}}$$



Mutual Inductance

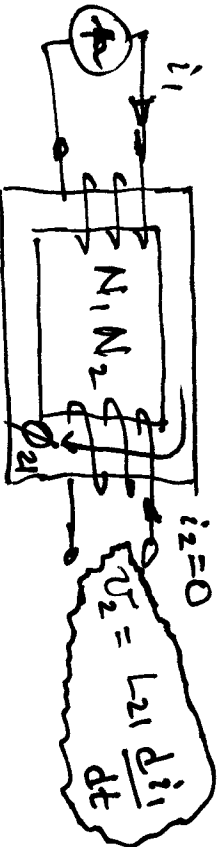
$$L_{12} = \frac{N_1 \Phi_{12}}{i_2} = \frac{\tau_{12}}{i_2} = \frac{N_1 N_2}{\mathcal{R}}$$



Self Inductance

$$L_{21} = \frac{N_2 \Phi_{21}}{i_1} = \frac{\tau_{21}}{i_1} = \frac{N_2 N_1}{\mathcal{R}}$$


Mutual Inductance

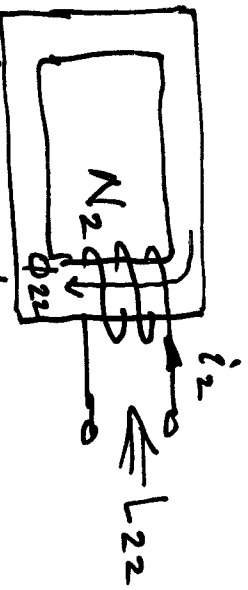

$$L_{22} = \frac{N_2 \Phi_{22}}{i_2} = \frac{\tau_{22}}{i_2} = \frac{N_2^2}{\mathcal{R}}$$

How to Use the Concept of Mutual Inductance

Two-Port Device:

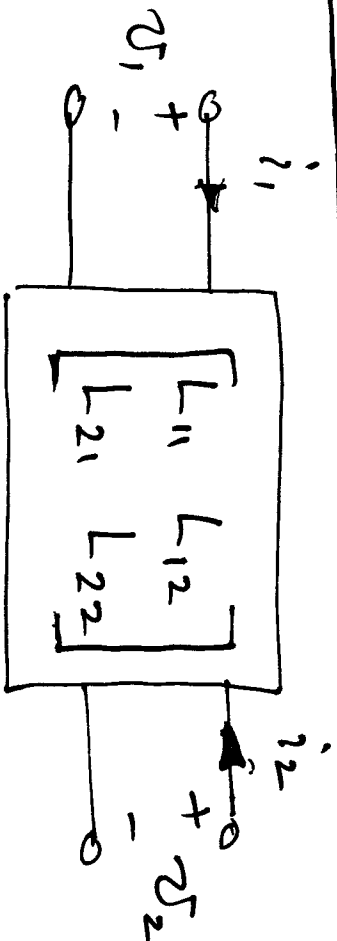

Note: Reference direction of currents is into terminals at (+) side of voltage.

In time domain:


$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} L_{11} & L_{12} \\ L_{21} & L_{22} \end{bmatrix} \begin{bmatrix} \frac{di_1}{dt} \\ \frac{di_2}{dt} \end{bmatrix}$$

In phasor domain:


$$\begin{bmatrix} \tilde{V}_1 \\ \tilde{V}_2 \end{bmatrix} = \begin{bmatrix} j\omega L_{11} & j\omega L_{12} \\ j\omega L_{21} & j\omega L_{22} \end{bmatrix} \begin{bmatrix} \tilde{I}_1 \\ \tilde{I}_2 \end{bmatrix}$$

Also of note:

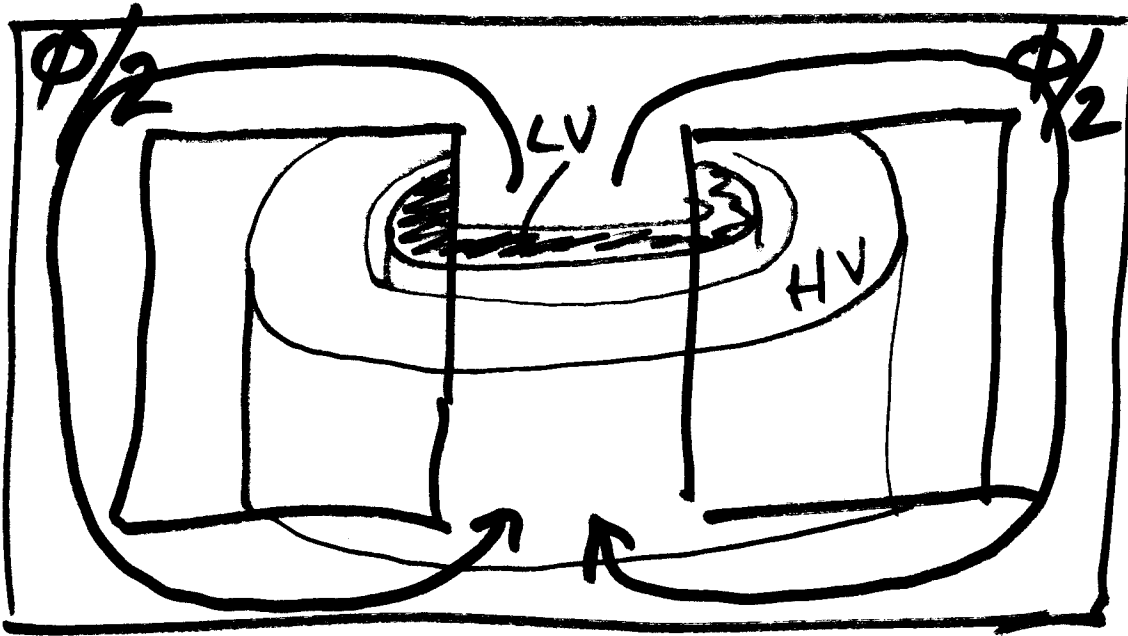In some texts, since \underline{L}_{12} and \underline{L}_{21} are mutual inductances, they are called \underline{M}_{12} and \underline{M}_{21} . Same thing.




Shell-form

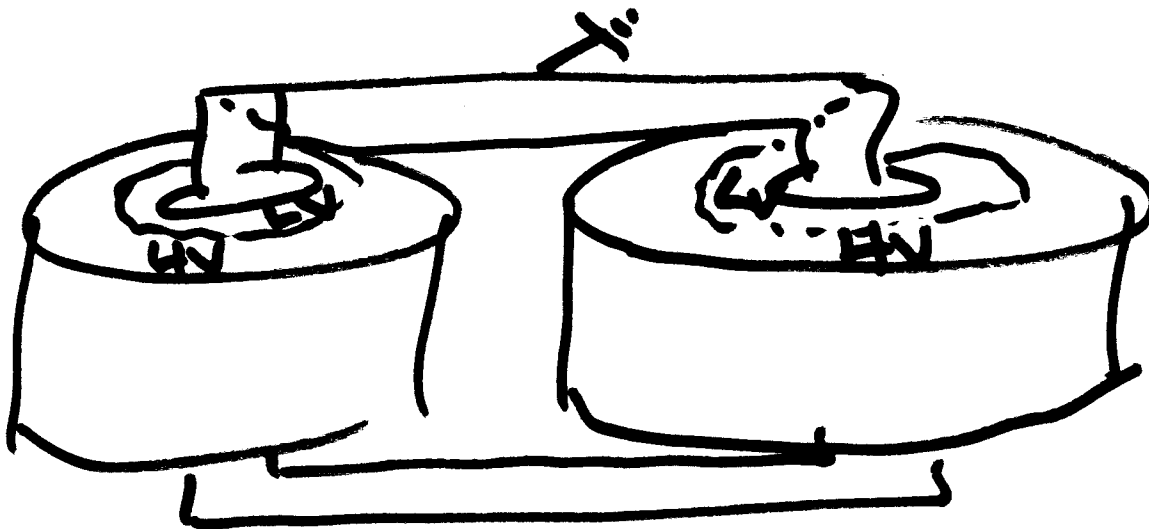

Core form.

Next: Ampere's Law

Next: Ampere's Law

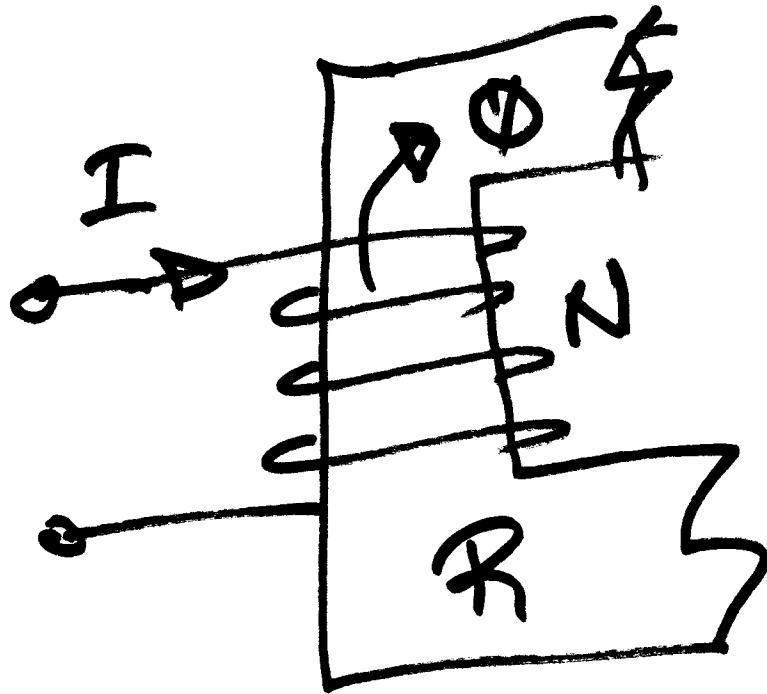


MMF

$$NI = \Phi R$$

Electrical Magnetic


a)

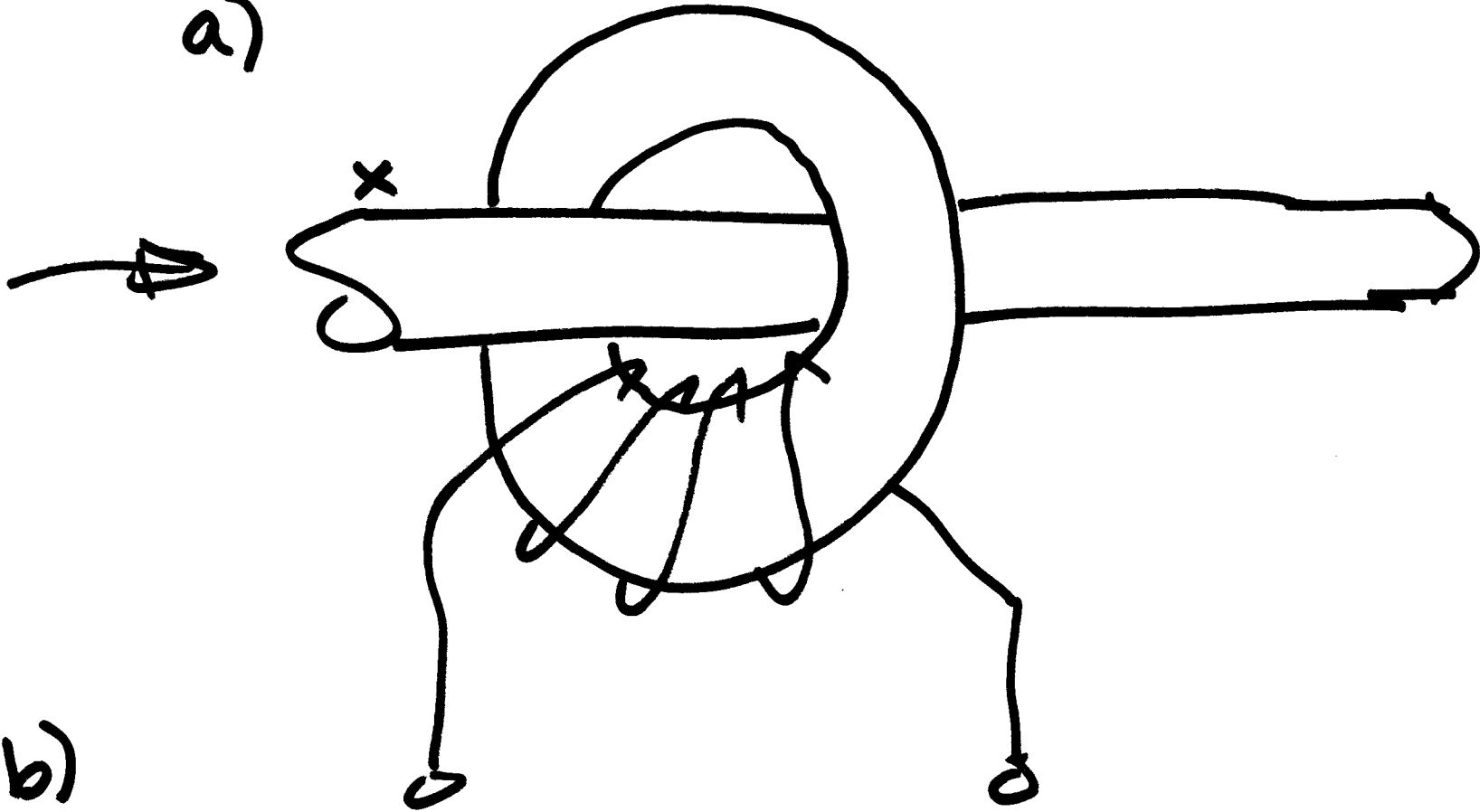

b)

Pri

Sec

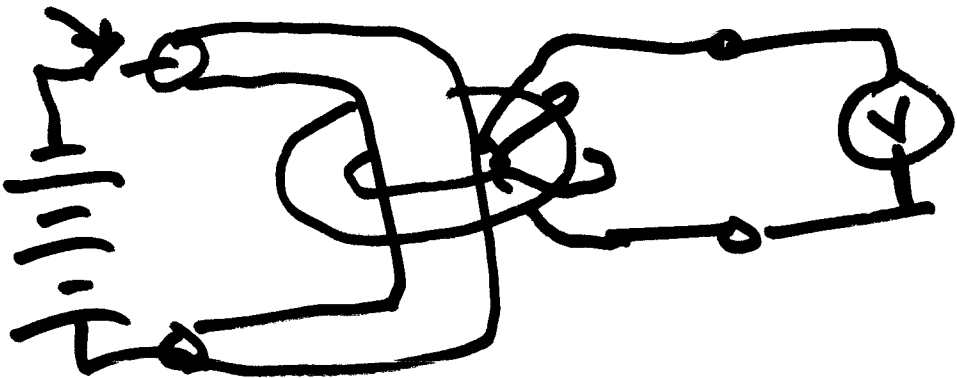


Ampere's Law

$$NI = \Phi R$$

= ?

$$\bar{H} = \frac{I_{ENC}}{2\pi r}$$

$I_{ENCLOSED}$

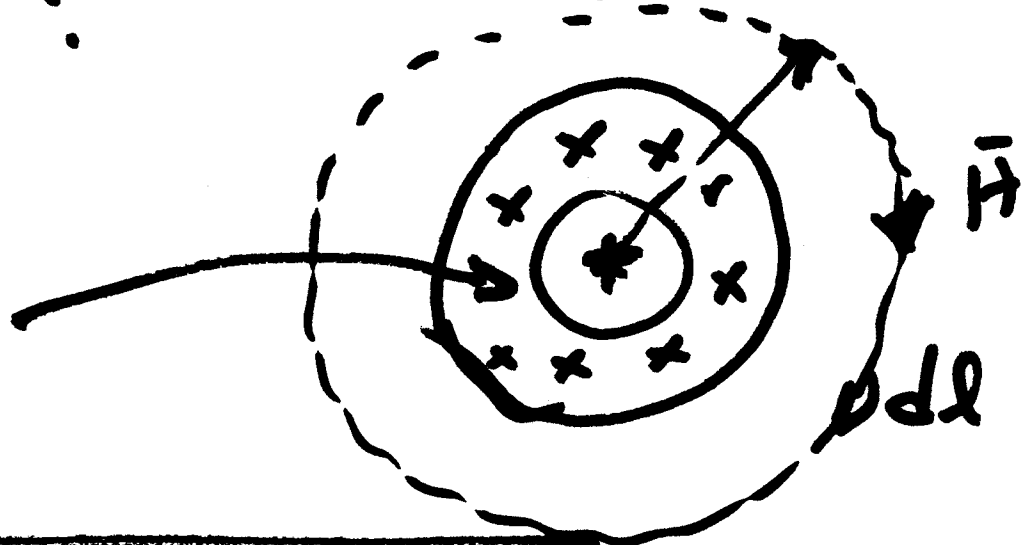

$$I_{ENC} = \oint \bar{H} \cdot dl$$

Clamp-on
ammeter
or
current
probe.