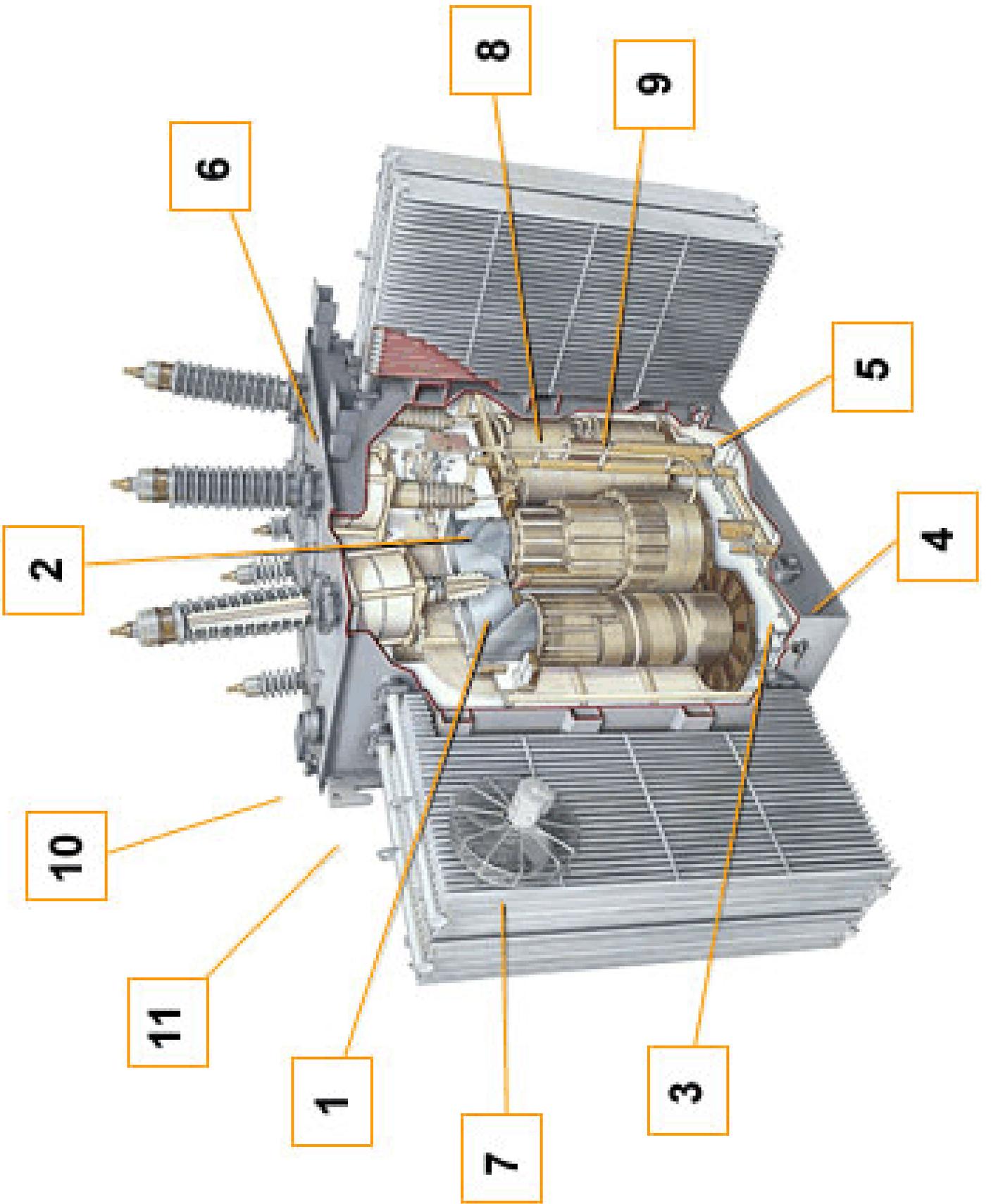


**Topics for Today:**

- Announcements
  - Software: Matlab? Off-campus students have access via Remote Desktop, can optionally buy student edition.
  - Office hrs: 11-12am M,W, 10-11am Fri
  - Office: EERC 614. Phone: 906.487.2857
  - XFMR exercises to be posted on web page
  - Recommended problems from Ch.2, solutions posted
- XFMR, Chapter 2 - Transformers and circuits w/transformers
  - Single phase transformers, basic structure
  - Winding R and Leakage, Core losses and saturation
  - 3-ph transformer banks and phase shifts (ANSI/IEEE vs. IEC)
  - Standard 30° shift transformers, non-standard connections
  - Pos/neg sequence phase shifts, sequence networks
  - Autotransformers
  - Load Tap Changing (LTC) transformers



Test your knowledge: How many of the key features on the previous page could you identify? Source: Waukesha Electric, <http://www.waukeshaelectric.com/peg-T1.shtml>

1. Core (no-load) losses minimized by utilizing laser-scribed, super-grain-oriented steel.
2. Lamination width customized to achieve a near perfect-circle core cross section, resulting in the efficient use of materials plus a lighter, more compact, high performance transformer.
3. Coil assembly rigidly braced in a high-strength frame that distributes clamping forces around the full circumference of the windings.
4. Submerged-arc welding process produces deep penetration welds, virtually eliminating leakage from welded tank joints.
5. Inside tank surfaces are painted white to facilitate internal inspection.
6. Transformer exterior coated to a minimum thickness of 3 mils; this coating has superior endurance characteristics and meets the ANSI C57.12.28 standard.
7. Galvanized radiators provide excellent corrosion resistance and require minimal maintenance (fan guards and blades also galvanized).
8. Material-stabilized coils are pressure-fit within the core frame.
9. Patented DETC (De-Energized Tap Changer) features simple and compact in-line contact arrangement (Patent Number: 5,744,764)
10. Waukesha® Type UZD Load Tap Changer designed to withstand up to a half-million operations without the need for contact replacement.
11. Worldbox® Control Enclosure features IEC standard components and is easy to maintain and service in the field.

Loadflow - Phasor

S.C. - "

Stability - Both Phasor (Grid Cases)  
and time (machine dynamics)

$\Delta t, 2\Delta t, \dots$

Lightning - time (impulse)

Switching - time (step)

Insulation Design -

---

# CONTENTS

---

# EE 5200 TEXT

---

Preface	xvii
<b>1 Basic Concepts</b>	<b>1</b>
1.1 Introduction	1
1.2 Single-Subscript Notation	3
1.3 Double-Subscript Notation	4
1.4 Power in Single-Phase AC Circuits	5
1.5 Complex Power	10
1.6 The Power Triangle	10
1.7 Direction of Power Flow	11
1.8 Voltage and Current in Balanced Three-Phase Circuits	14
1.9 Power in Balanced Three-Phase Circuits	24
1.10 Per-Unit Quantities	25
1.11 Changing the Base of Per-Unit Quantities	29
1.12 Node Equations	30
1.13 The Single-Line or One-Line Diagram	34
1.14 Impedance and Reactance Diagrams	36
1.15 Summary	37
Problems	37
<b>2 Transformers</b>	<b>41</b>
2.1 The Ideal Transformer	41
2.2 Magnetically Coupled Coils	46
2.3 The Equivalent Circuit of a Single-Phase Transformer	51
2.4 Per-Unit Impedances in Single-Phase Transformer Circuits	56
2.5 Three-Phase Transformers	59
2.6 Three-Phase Transformers: Phase Shift and Equivalent Circuits	64
2.7 The Autotransformer	71
2.8 Per-Unit Impedances of Three-Winding Transformers	72
2.9 Tap-Changing and Regulating Transformers	76
2.10 The Advantages of Per-Unit Computations	80
2.11 Summary	82
Problems	82

*Handwritten notes:*

- "Closed"** (circled)
- "Open" V Phasers**
- 6 review videos** (in a box)

EE 4221  
EE 6210  
EE 5230

6.3 The Medium-Length Line 200

6.4 The Long Transmission Line: Solution of the Differential Equations 202

6.5 The Long Transmission Line: Interpretation of the Equations 205

6.6 The Long Transmission Line: Hyperbolic Form of the Equations 207

6.7 The Equivalent Circuit of a Long Line 212

6.8 Power Flow through a Transmission Line 215

6.9 Reactive Compensation of Transmission Lines 218

6.10 Transmission-Line Transients 221

6.11 Transient Analysis: Traveling Waves 222

6.12 Transient Analysis: Reflections 226

6.13 Direct-Current Transmission 231

6.14 Summary 233

Problems 233

EE 5230

4 Series Impedance of Transmission Lines 141

4.1 Types of Conductors 142

4.2 Resistance 143

4.3 Tabulated Resistance Values 146

4.4 Inductance of a Conductor Due to Internal Flux 146

4.5 Flux Linkages between Two Points External to an Isolated Conductor 149

4.6 Inductance of a Single-Phase Two-Wire Line 151

4.7 Flux Linkages of One Conductor in a Group 153

4.8 Inductances of Composite-Conductor Lines 155

4.9 The Use of Tables 159

4.10 Inductance of Three-Phase Lines with Equilateral Spacing 161

4.11 Inductance of Three-Phase Lines with Unsymmetrical Spacing 164

4.12 Inductance Calculations for Bundled Conductors 166

4.13 Summary 167

Problems 170

5 Capacitance of Transmission Lines 171

5.1 Electric Field of a Long, Straight Conductor 172

5.2 The Potential Difference between Two Points Due to a Charge 173

5.3 Capacitance of a Two-Wire Line 177

5.4 Capacitance of a Three-Phase Line with Equilateral Spacing 180

5.5 Capacitance of a Three-Phase Line with Unsymmetrical Spacing 183

5.6 Effect of Earth on the Capacitance of Three-Phase Transmission Lines 186

5.7 Capacitance Calculations for Bundled Conductors 188

5.8 Parallel-Circuit Three-Phase Lines 190

5.9 Summary 191

Problems 193

6 Current and Voltage Relations on a Transmission Line 195

6.1 Representation of Lines 196

6.2 The Short Transmission Line

EE 5230

7 The Admittance Model and Network Calculations 238

7.1 Branch and Node Admittances 239

7.2 Mutually Coupled Branches in  $Y_{bus}$  245

7.3 An Equivalent Admittance Network 251

7.4 Modification of  $Y_{bus}$  255

7.5 The Network Incidence Matrix and  $Y_{bus}$  257

7.6 The Method of Successive Elimination 263

7.7 Node Elimination (Kron Reduction) 271

7.8 Triangular Factorization 274

7.9 Sparsity and Near-Optimal Ordering 279

7.10 Summary 280

Problems 280

EE 5230

8 The Impedance Model and Network Calculations 283

8.1 The Bus Admittance and Impedance Matrices 284

8.2 Thévenin's Theorem and  $Z_{bus}$  287

8.3 Modification of an Existing  $Z_{bus}$  294

8.4 Direct Determination of  $Z_{bus}$  301

8.5 Calculation of  $Z_{bus}$  Elements from  $Y_{bus}$  306

8.6 Power Invariant Transformations 310

8.7 Mutually Coupled Branches in  $Z_{bus}$  316

8.8 Summary 324

Problems 324

EE 5230

9 Power-Flow Solutions 329

9.1 The Power-Flow Problem 329

9.2 The Gauss-Seidel Method 335

9.3 The Newton-Raphson Method 342

9.4 The Newton-Raphson Power-Flow Solution 347

9.5 Power-Flow Studies in System Design and Operation 356

9.6 Regulating Transformers 361

9.7 The Decoupled Power-Flow Method 368  
 9.8 Summary 374  
 Problems 376

10 Symmetrical Faults

10.1 Transients in RL Series Circuits 380  
 10.2 Internal Voltages of Loaded Machines under Fault Conditions 383  
 10.3 Fault Calculations Using  $Z_{bus}$  390  
 10.4 Fault Calculations Using  $Z_{bus}$  Equivalent Circuits 395  
 10.5 The Selection of Circuit Breakers 402  
 10.6 Summary 411  
 Problems 412

11 Symmetrical Components and Sequence Networks

11.1 Synthesis of Unsymmetrical Phasors from Their Symmetrical Components 416  
 11.2 The Symmetrical Components of Unsymmetrical Phasors 417  
 11.3 Symmetrical Y and  $\Delta$  Circuits 418  
 11.4 Power in Terms of Symmetrical Components 422  
 11.5 Sequence Circuits of Y and  $\Delta$  Impedances 427  
 11.6 Sequence Circuits of a Symmetrical Transmission Line 429  
 11.7 Sequence Circuits of the Synchronous Machine 435  
 11.8 Sequence Circuits of Y- $\Delta$  Transformers 442  
 11.9 Unsymmetrical Series Impedances 449  
 11.10 Sequence Networks 459  
 11.11 Summary 461  
 Problems 467

12 Unsymmetrical Faults

12.1 Unsymmetrical Faults on Power Systems 470  
 12.2 Single Line-to-Ground Faults 470  
 12.3 Line-to-Line Faults 482  
 12.4 Double Line-to-Ground Faults 488  
 12.5 Demonstration Problems 494  
 12.6 Open-Conductor Faults 500  
 12.7 Summary 512  
 Problems 517

13 Economic Operation of Power Systems

13.1 Distribution of Load between Units within a Plant 531  
 13.2 Distribution of Load between Plants 532  
 13.3 The Transmission-Loss Equation 540  
 13.4 An Interpretation of Transformation C 543  
 13.5 Classical Economic Dispatch with Losses 552  
 13.6 Automatic Generation Control 555  
 13.7 Unit Commitment 562  
 572

13.8 Solving the Unit Commitment Problem 578  
 13.9 Summary 586  
 Problems 587

14  $Z_{bus}$  Methods in Contingency Analysis

14.1 Adding and Removing Multiple Lines 591  
 14.2 Piecewise Solution of Interconnected Systems 592  
 14.3 Analysis of Single Contingencies 601  
 14.4 Analysis of Multiple Contingencies 611  
 14.5 Contingency Analysis by de Model 620  
 14.6 System Reduction for Contingency and Fault Studies 626  
 14.7 Summary 628  
 Problems 636

15 State Estimation of Power Systems

15.1 The Method of Least Squares 641  
 15.2 Statistics, Errors, and Estimates 642  
 15.3 Test for Bad Data 650  
 15.4 Power System State Estimation 655  
 15.5 The Structure and Formation of  $H_1$  664  
 15.6 Summary 677  
 Problems 687  
 688

16 Power System Stability

16.1 The Stability Problem 695  
 16.2 Rotor Dynamics and the Swing Equation 695  
 16.3 Further Considerations of the Swing Equation 702  
 16.4 The Power-Angle Equation 707  
 16.5 Synchronizing Power Coefficients 714  
 16.6 Equal-Area Criterion of Stability 717  
 16.7 Further Applications of the Equal-Area Criterion 724  
 16.8 Multimachine Stability Studies: Classical Representation 727  
 16.9 Step-by-Step Solution of the Swing Curve 734  
 16.10 Computer Programs for Transient Stability Studies 741  
 16.11 Factors Affecting Transient Stability 743  
 16.12 Summary 745  
 Problems 746


Appendix A

A.1 Distributed Windings of the Synchronous Machine 748  
 A.2 P-Transformation of Stator Quantities 754  
 763

Appendix B


B.1 Sparsity and Near-Optimal Ordering 766  
 B.2 Sparsity of the Jacobian 766  
 771

Index 777

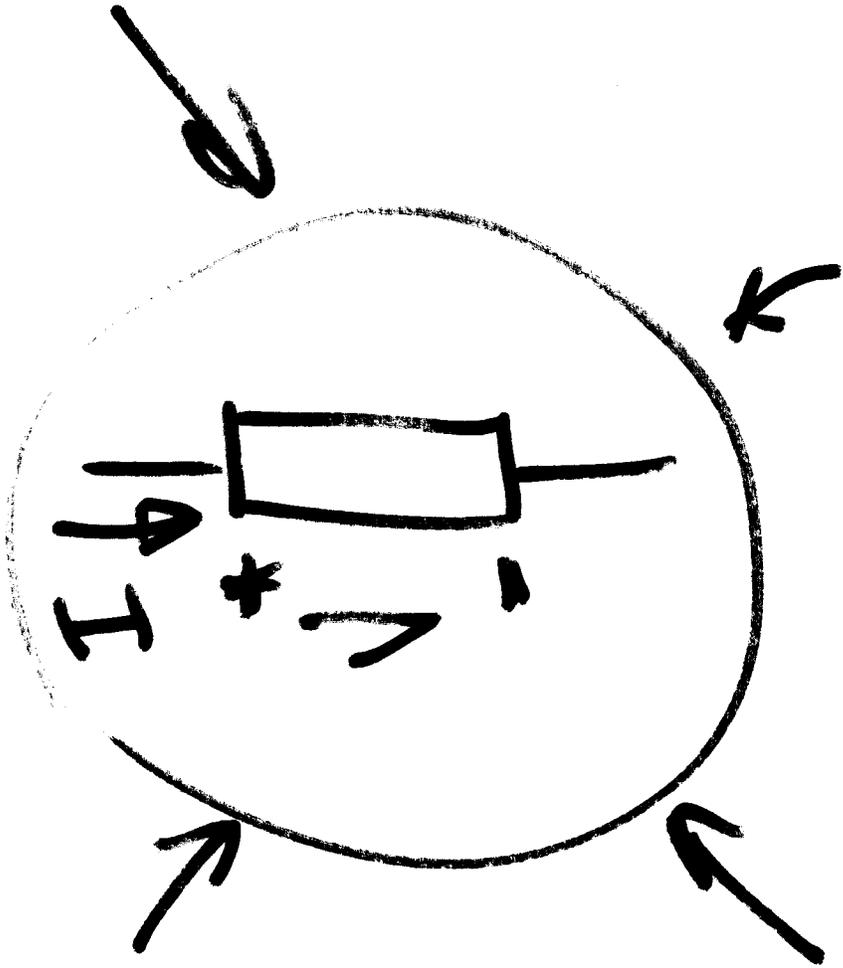

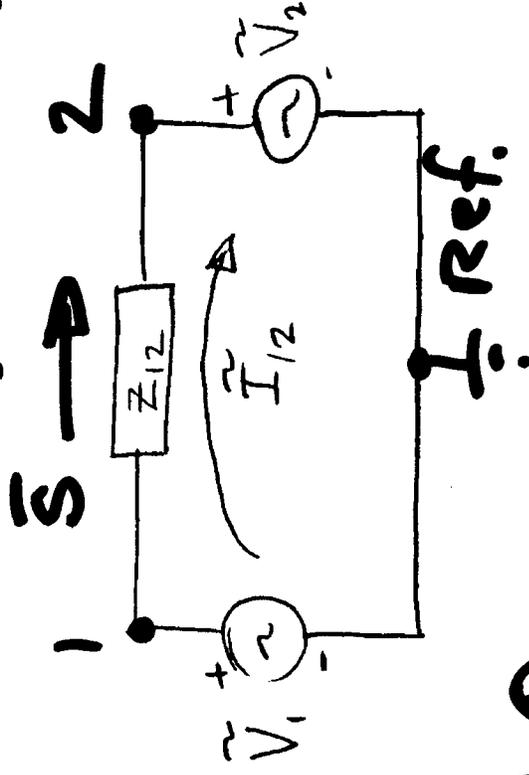1) [15pts] For the following circuit,  $v_1(t) = 100 \cos(\omega t + 0^\circ)$ ,  $v_2(t) = 120 \sin(\omega t - 30^\circ)$  and  $Z_{12} = 0.5 - j0.5\Omega$ .

- Convert  $v_1(t)$  and  $v_2(t)$  to their phasor equivalents  $\tilde{V}_1$  and  $\tilde{V}_2$ .
- Calculate  $\tilde{I}_{12}$ .
- Calculate the complex power  $S$  consumed by "source 2".
- In terms of generator or load, what are sources 1 & 2? Was the correct guess made in labeling current direction?
- What is the power factor of "source 1"?



- Phasor Analysis

-  $\tilde{V}$ ,  $\tilde{I}$ , Subscripts


- Polarity

- Flow direction of P, Q



$$S_{in} = VI^*$$

or  
 $Q_{ijx}$

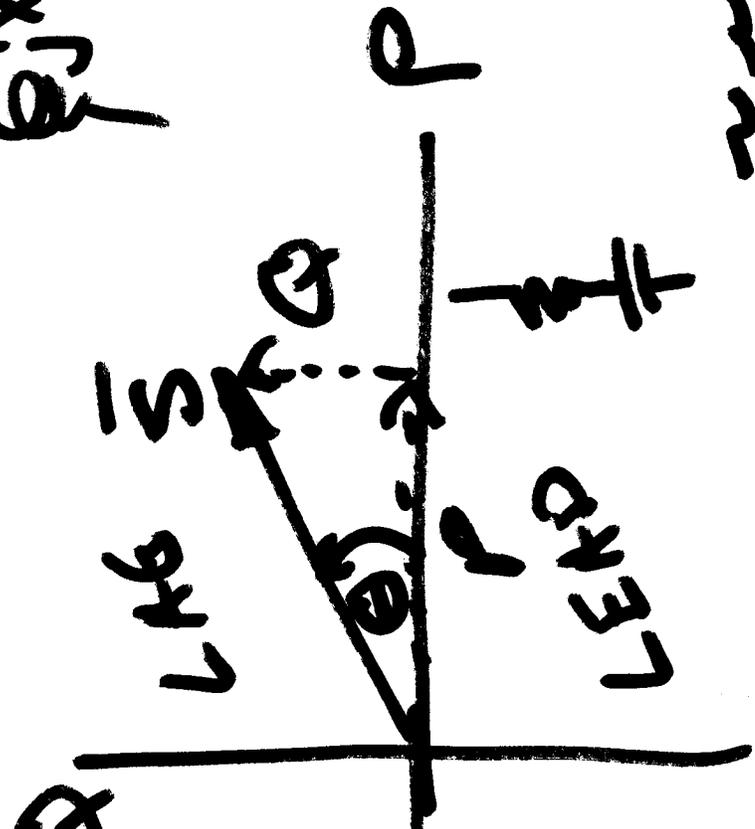


$$\theta = \angle \vec{V} - \angle \vec{I} \text{ (passive)}$$

$$= \angle \vec{S} - \angle \vec{P}$$


$$S = VI \cos \theta + j VI \sin \theta = \underline{\underline{VI^*}}$$
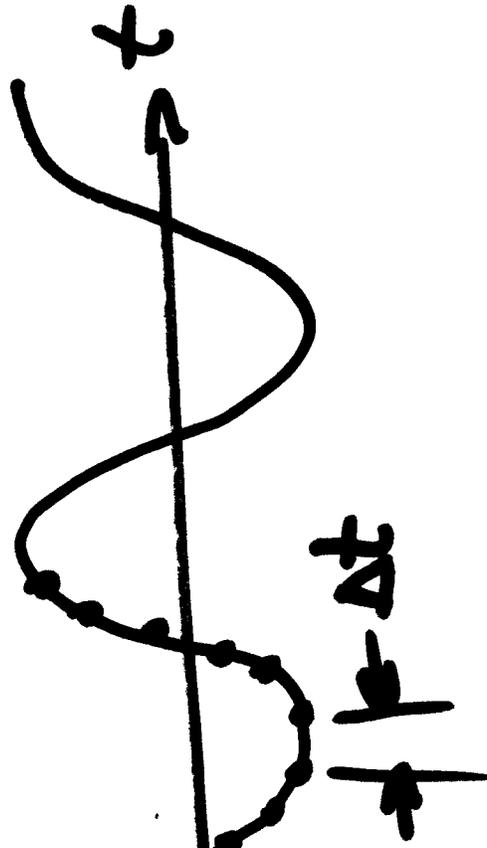
# Time Domain - Simulation

- ATP
  - Matlab
- $\Delta t = \text{uniform timestep}$




real no:

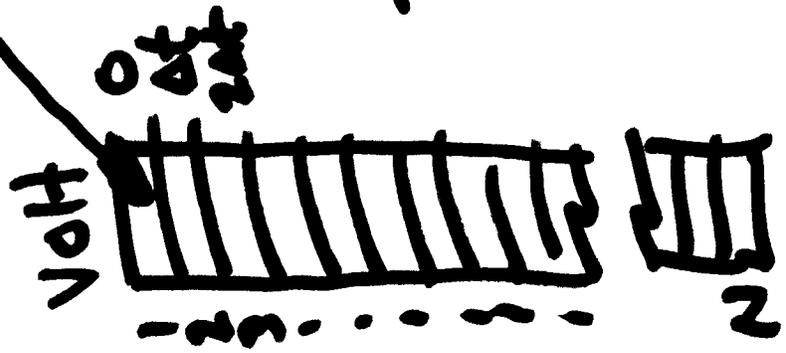


time series


Phasor Domain

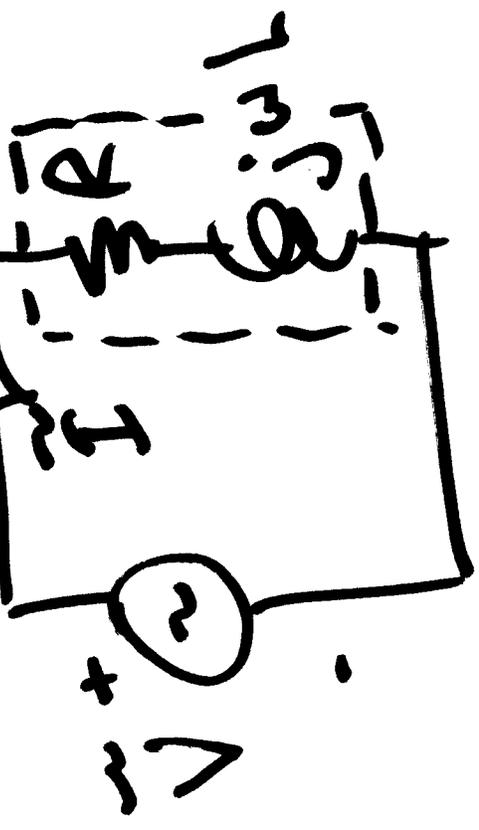


Time Domain

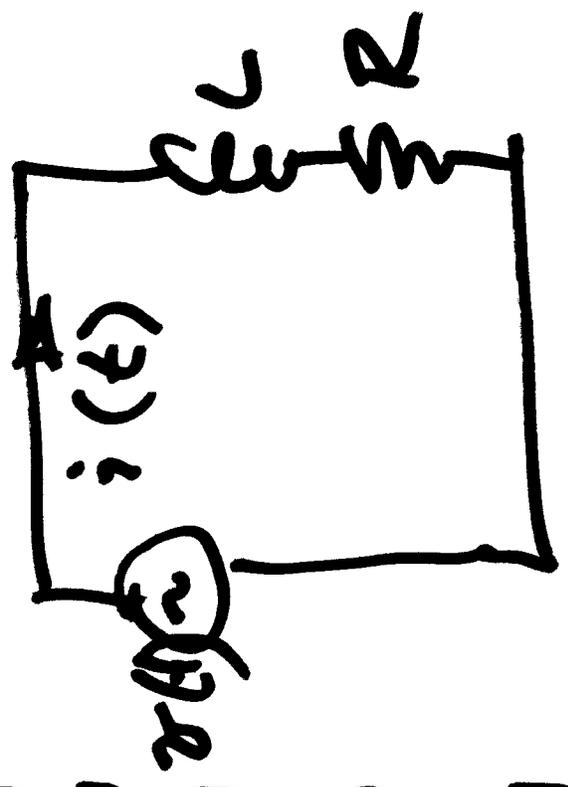
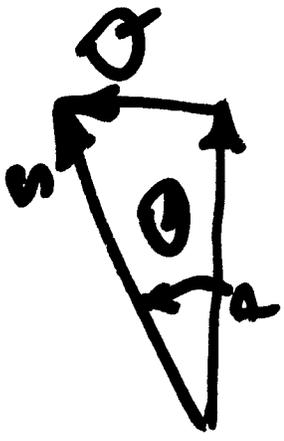
$$\angle \vec{I} - \angle \vec{V} = \phi = -\theta$$




$$v(t) = V_p \cos(\omega t)$$



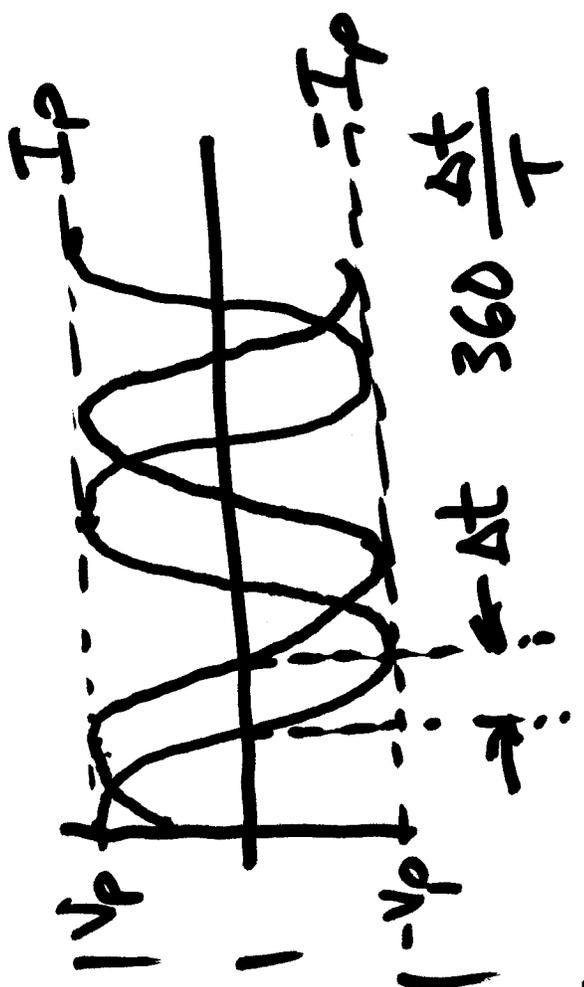


# Power

## Matlab

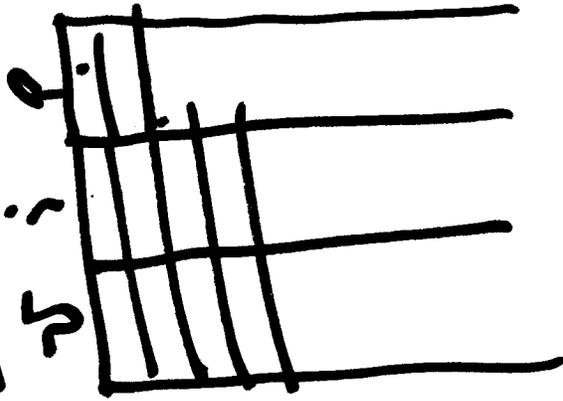

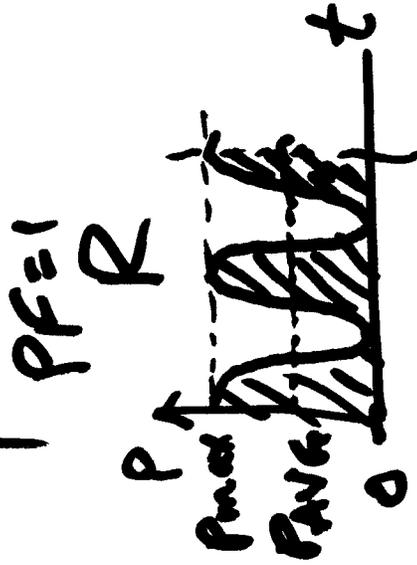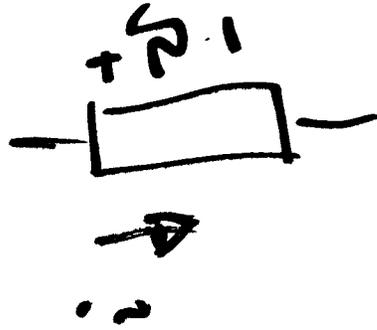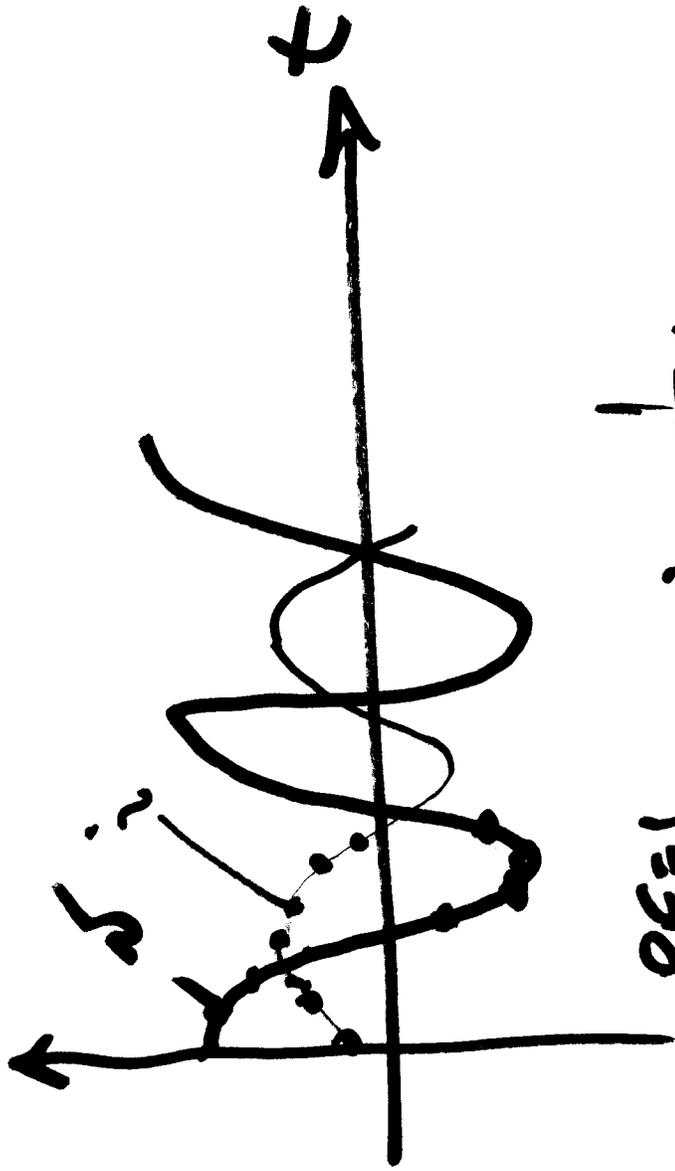
$$P_{AVG} = \frac{1}{T} \int_0^T P(t) dt$$



$$P(t) = v_i(t) i(t)$$

$P_{AVG} = 0$

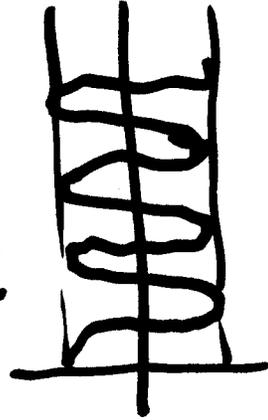

$P_{AVG} = 0$

# Waukesha Quality Inside

## Means Reliability Is On Your Side


Low no-load losses result from use of laser-scribed, super-grain-oriented steel.

Transformer exterior is coated to a minimum thickness of 3 mils. This coating has superior endurance characteristics and meets the ANSI C57.12.28 standard.

Load Tap Changer is designed to withstand up to a half-million operations without need for contact replacement.

Lamination width customized to achieve a near perfect-circle core cross section, resulting in the most efficient use of materials plus a lighter, more compact high-performance transformer.

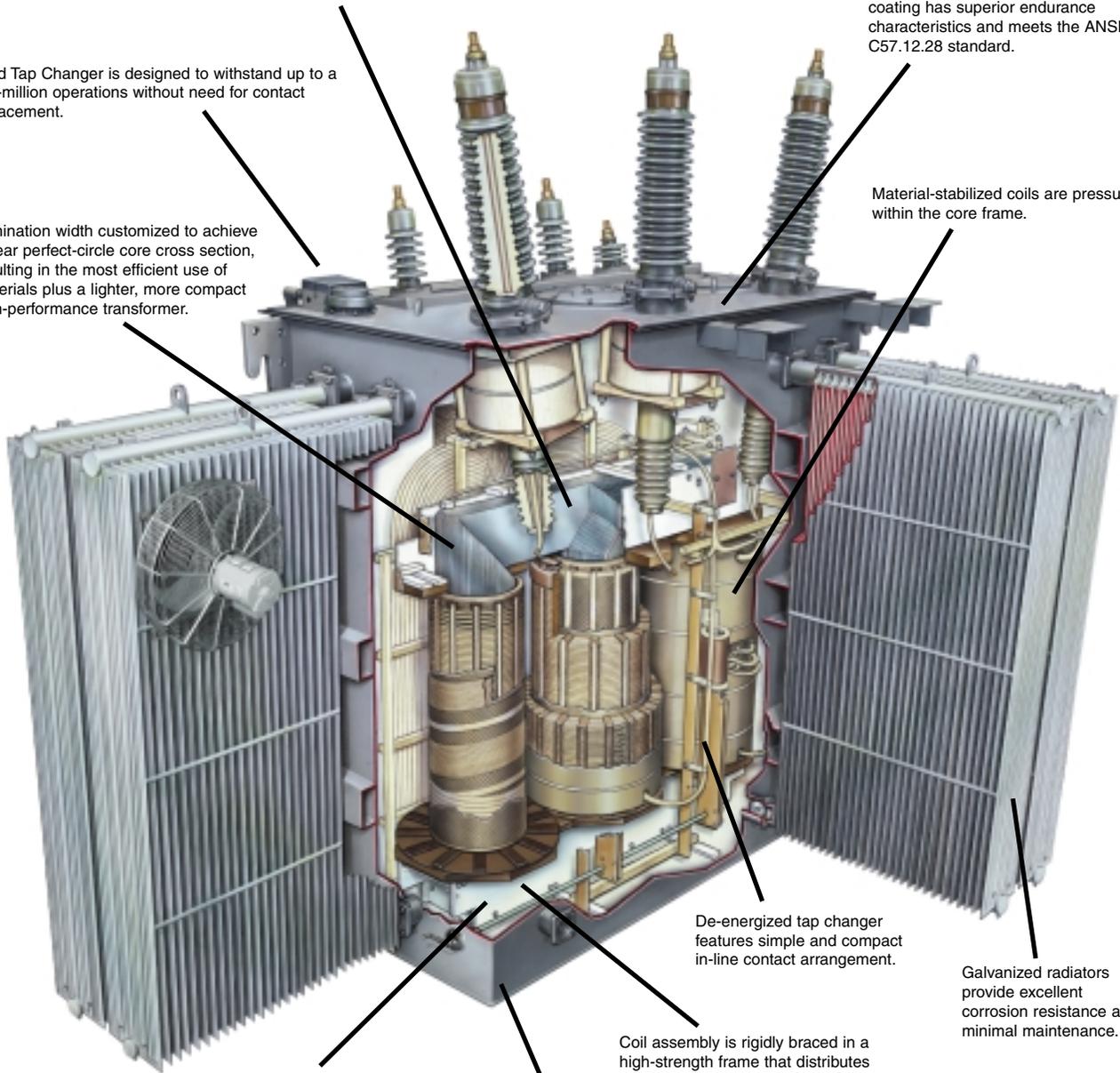Material-stabilized coils are pressure-fit within the core frame.



Inside tank surfaces are painted white to facilitate internal inspection.

De-energized tap changer features simple and compact in-line contact arrangement.

Galvanized radiators provide excellent corrosion resistance and minimal maintenance.

Coil assembly is rigidly braced in a high-strength frame that distributes clamping forces around the full circumference of the windings.

Submerged-arc process produces deep weld penetration, virtually eliminating leakage from welded tank joints.

Waukesha Electric Systems offers component parts for transformer upgrades and repair, as well as extensive field service support that includes transformer moving, hauling and rigging, vacuum filling and oil processing, inspection, testing and customer training.




### WAUKESHA ELECTRIC SYSTEMS

World Headquarters:  
400 S. Prairie Avenue  
Waukesha, WI 53186-5940  
800.835.2732

U.S. Manufacturing:  
Waukesha, WI 800.835.2732  
Goldsboro, NC 800.758.4384

Service, Parts, Training:  
High Voltage Supply  
Dallas, TX 800.338.5526

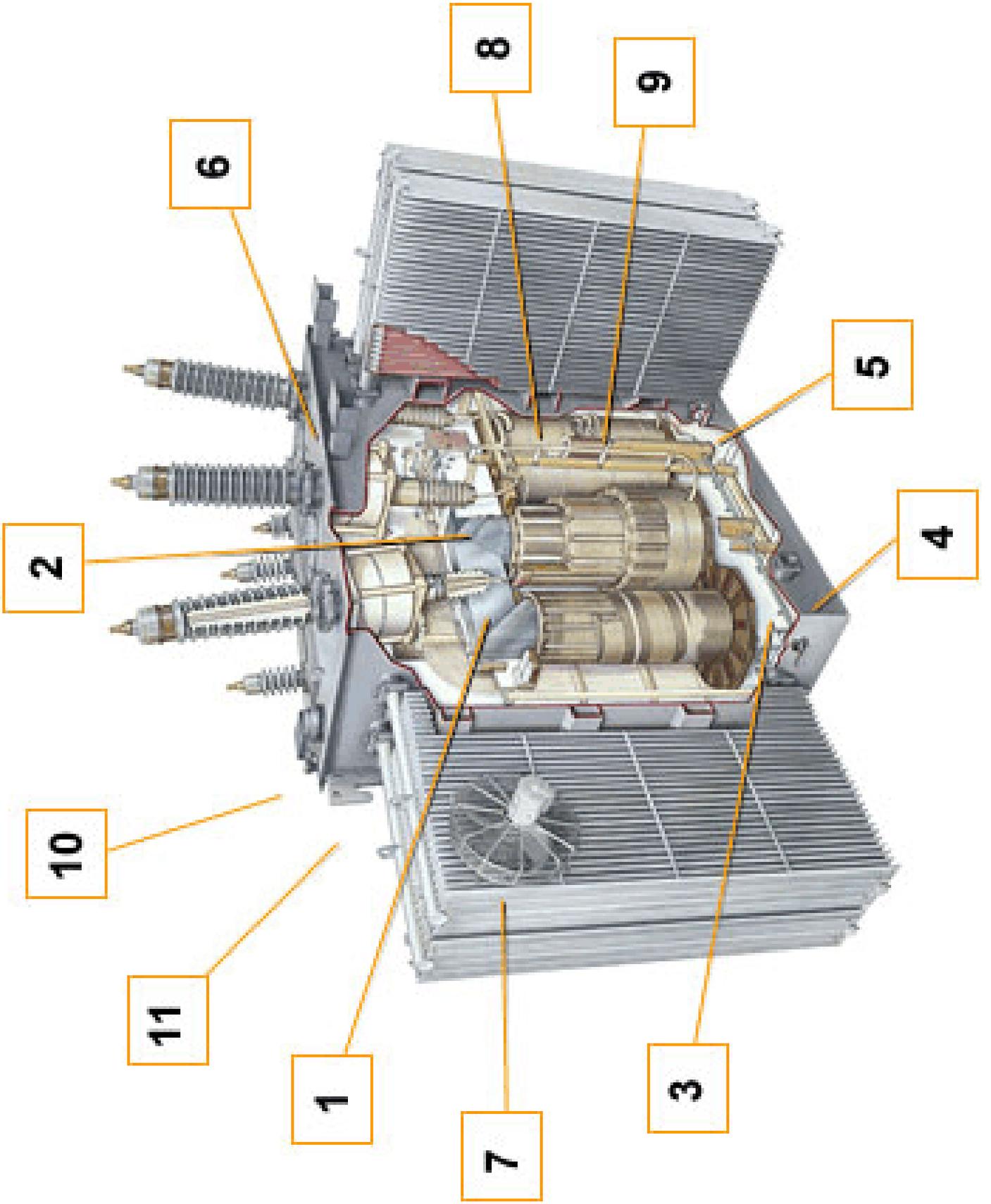*energy solutions* ...to power your future



Test your knowledge: How many of the key features on the previous page could you identify? Source: Waukesha Electric, <http://www.waukeshaelectric.com/peg-T1.shtml>

1. Core (no-load) losses minimized by utilizing laser-scribed, super-grain-oriented steel.
2. Lamination width customized to achieve a near perfect-circle core cross section, resulting in the efficient use of materials plus a lighter, more compact, high performance transformer.
3. Coil assembly rigidly braced in a high-strength frame that distributes clamping forces around the full circumference of the windings.
4. Submerged-arc welding process produces deep penetration welds, virtually eliminating leakage from welded tank joints.
5. Inside tank surfaces are painted white to facilitate internal inspection.
6. Transformer exterior coated to a minimum thickness of 3 mils; this coating has superior endurance characteristics and meets the ANSI C57.12.28 standard.
7. Galvanized radiators provide excellent corrosion resistance and require minimal maintenance (fan guards and blades also galvanized).
8. Material-stabilized coils are pressure-fit within the core frame.
9. Patented DETC (De-Energized Tap Changer) features simple and compact in-line contact arrangement (Patent Number: 5,744,764)
10. Waukesha® Type UZD Load Tap Changer designed to withstand up to a half-million operations without the need for contact replacement.
11. Worldbox® Control Enclosure features IEC standard components and is easy to maintain and service in the field.


## Cooling

- Oil
- Heat exch
- pumps, fans

$\pm 10\%$  LTC's - LV  
 $\pm 5\%$  NLTC's - HV  
(off-nominal  
turns ratio)
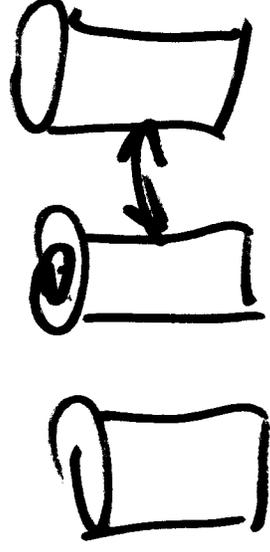
## Monitoring

- Temp: oil, coils
- Oil gases
- N<sub>2</sub>




## Coil Design

- insulation:


$\Phi$  } coil-core; coil-coil, phase-phase

} Higher V



BIT  
Bst

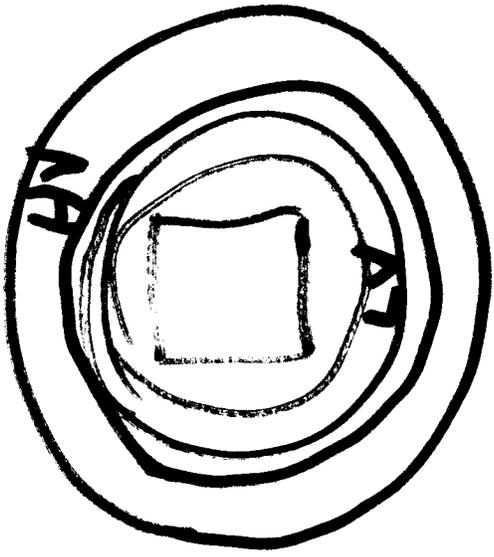

S-P

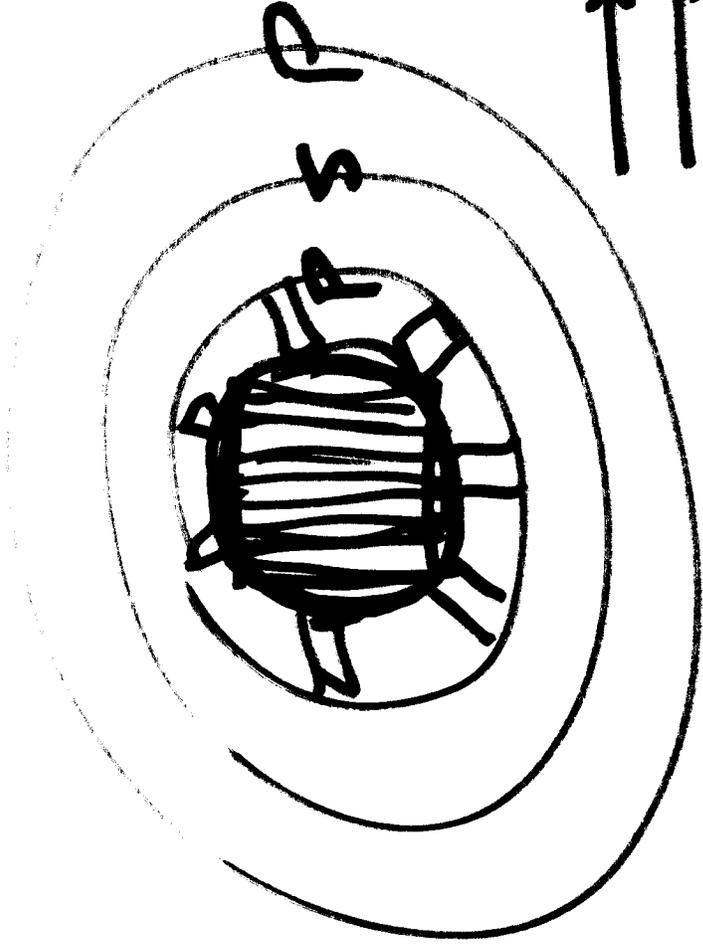

P-S-P

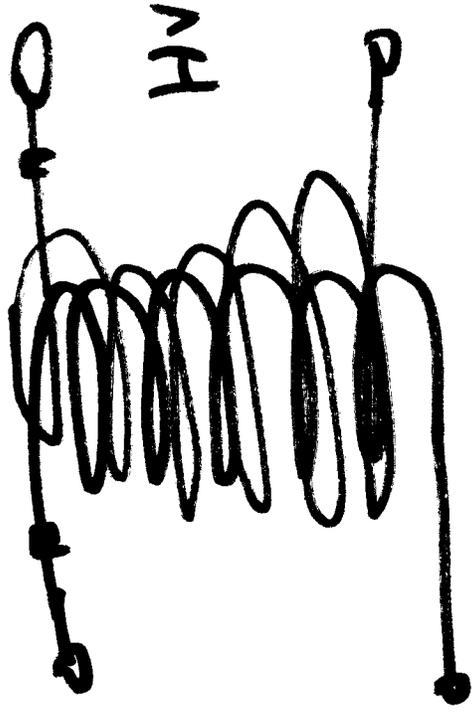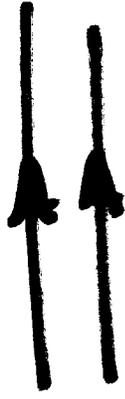

cylindrical



How many possibilities are there  
for  $\Delta$ - $\gamma$  or  $\gamma$ - $\Delta$  phase shifts?

$\pm 30^\circ$   
 $\pm 90^\circ$   
 $\pm 150^\circ$

) 6 each

$\Rightarrow$  12 total.

Auto- $\Delta$

Zig-Zig


Extended  $\Delta$ .

- Three-Phase Transformers


Mark

All of these can and are used to indicate the same winding connections:


IEEE Stds:

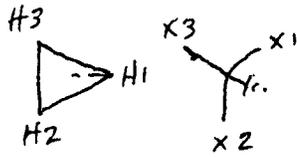


One-Line:

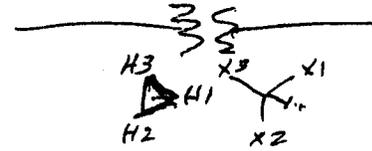

Schematic

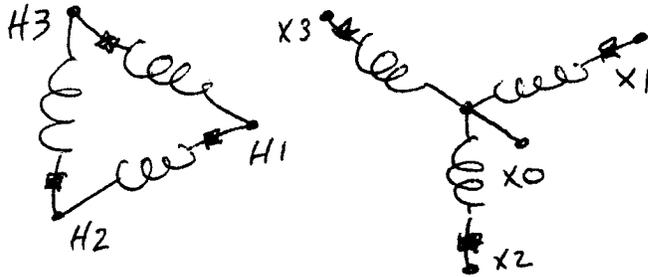

Circuit 3-line diagram

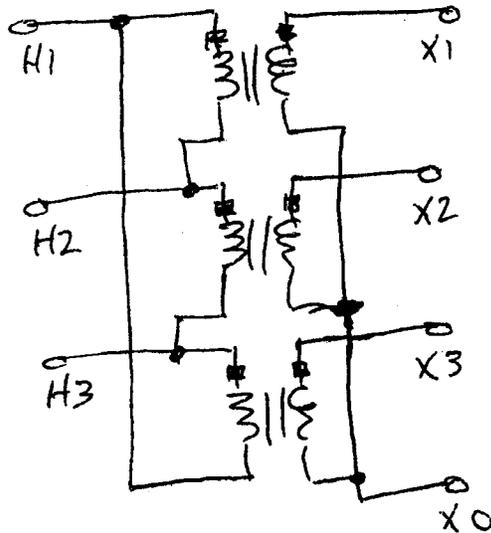


In Europe and much of the world:

IEC Stds:


Dyn11




One-Line:

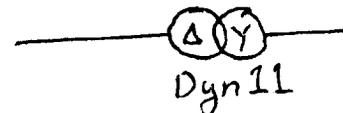



"old-down" diagram

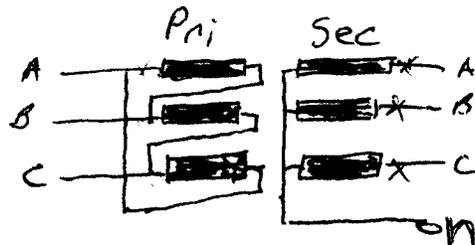


Delta

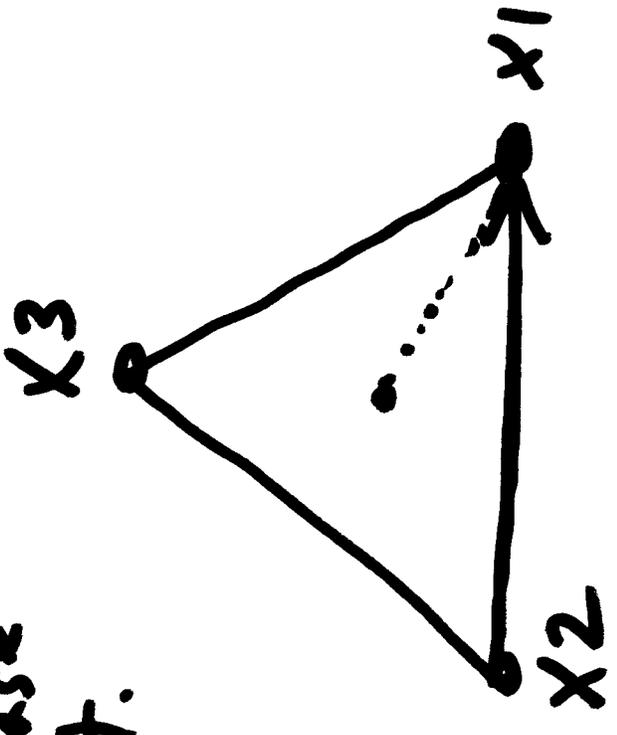


Zig-Zag 0° phase shift.

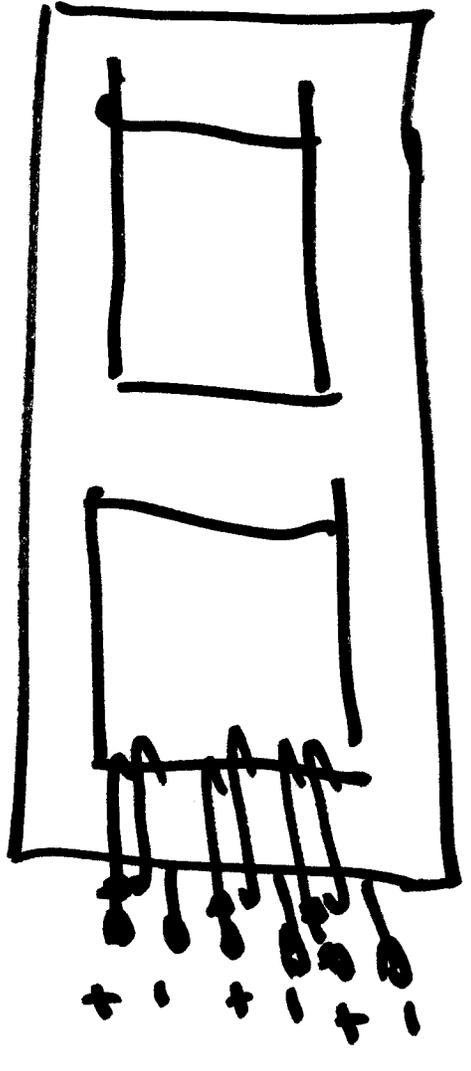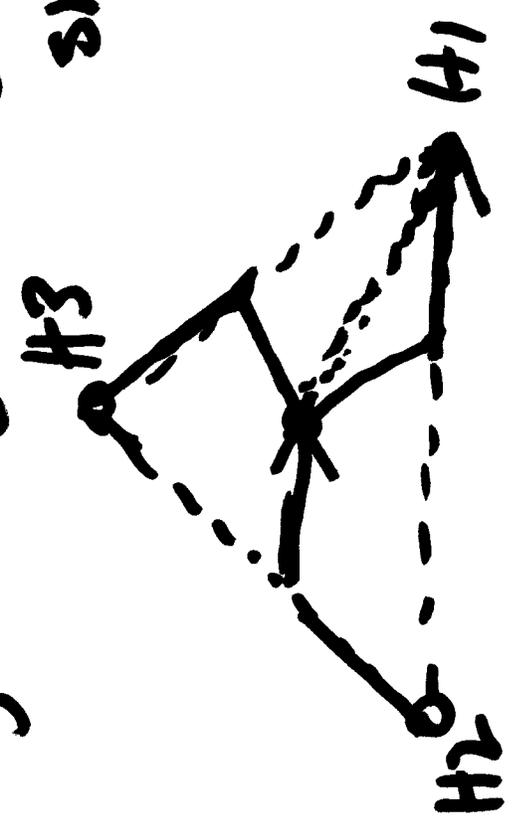


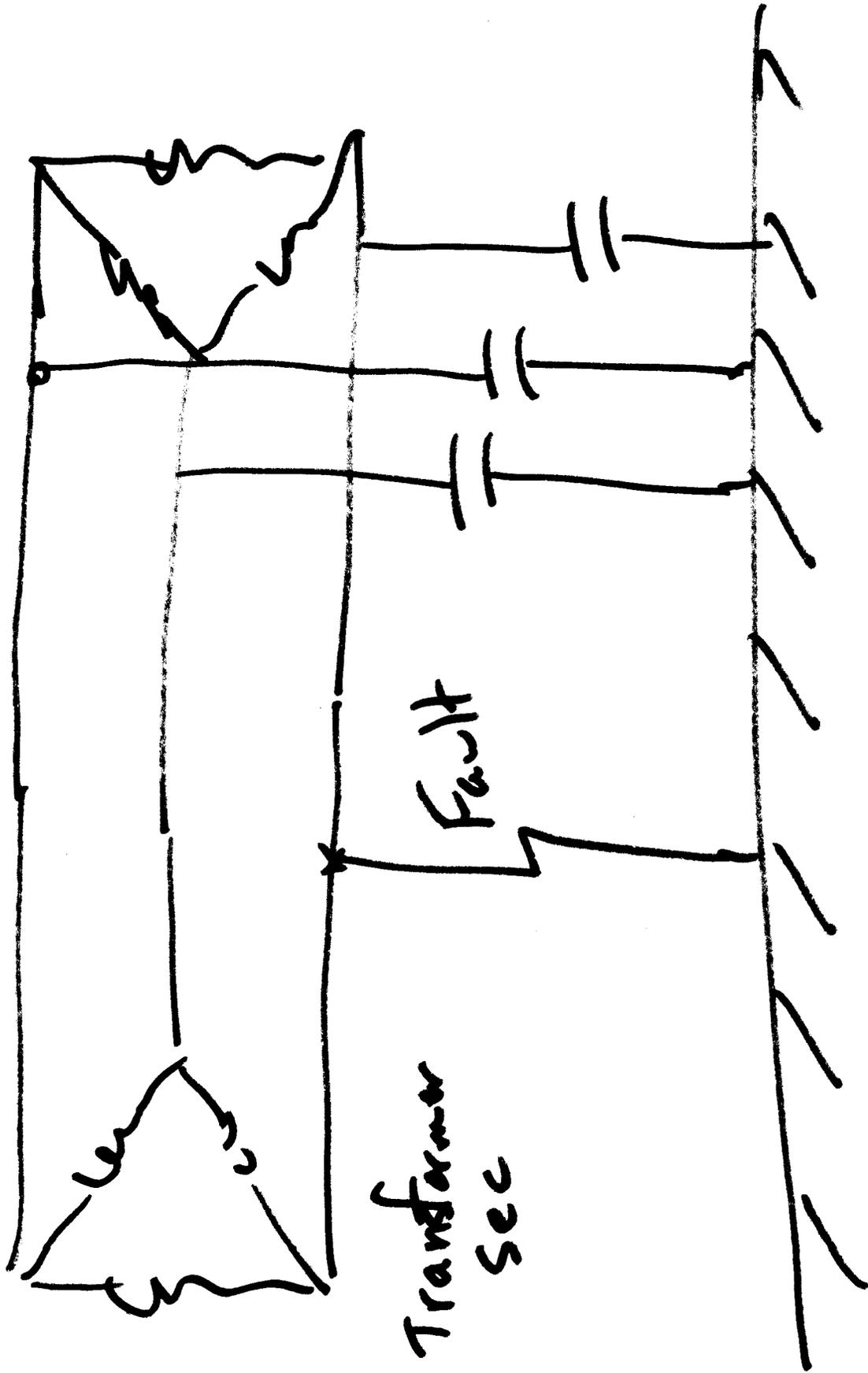



Balanced 3-ph voltages:

$$|\tilde{V}_{AG}| = |\tilde{V}_{BG}| = |\tilde{V}_{CG}|$$

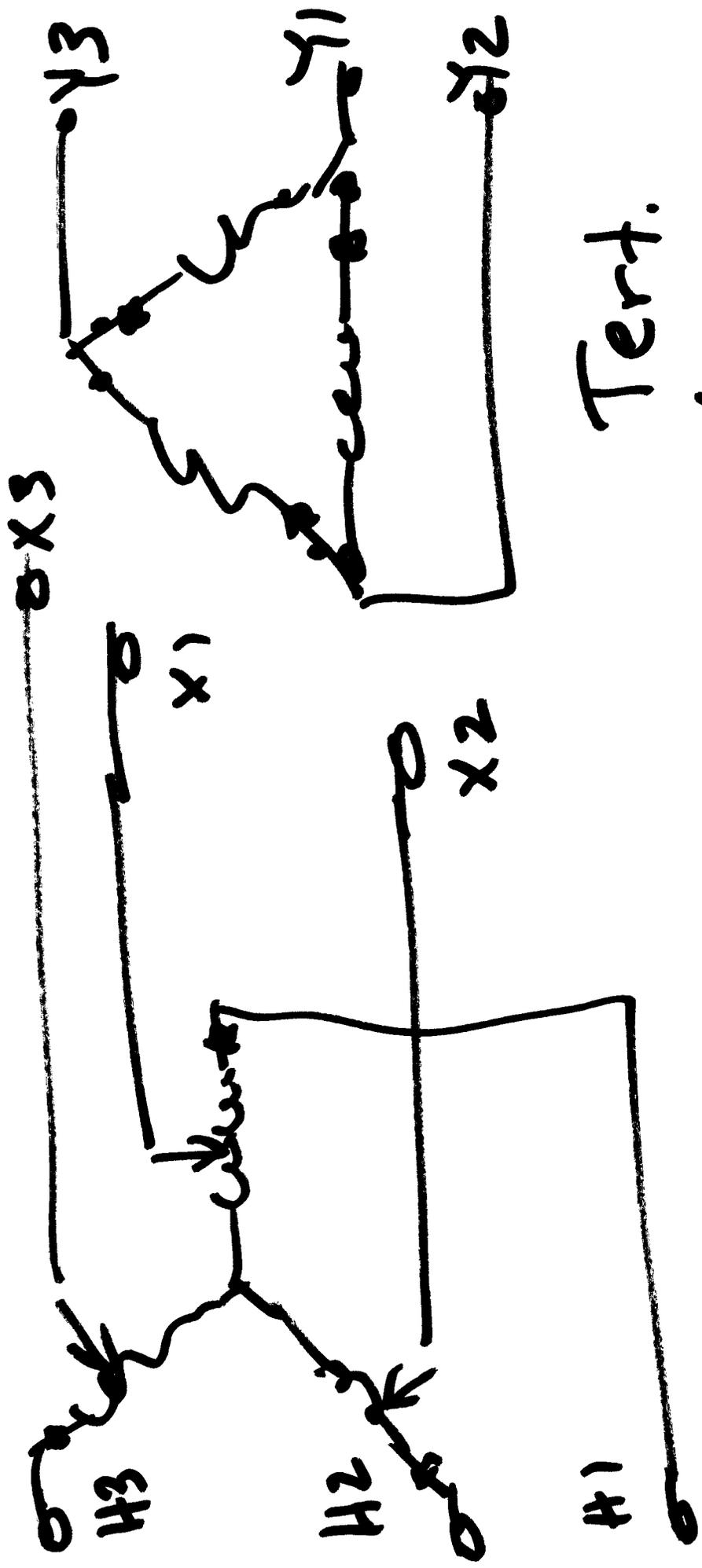

Tert.

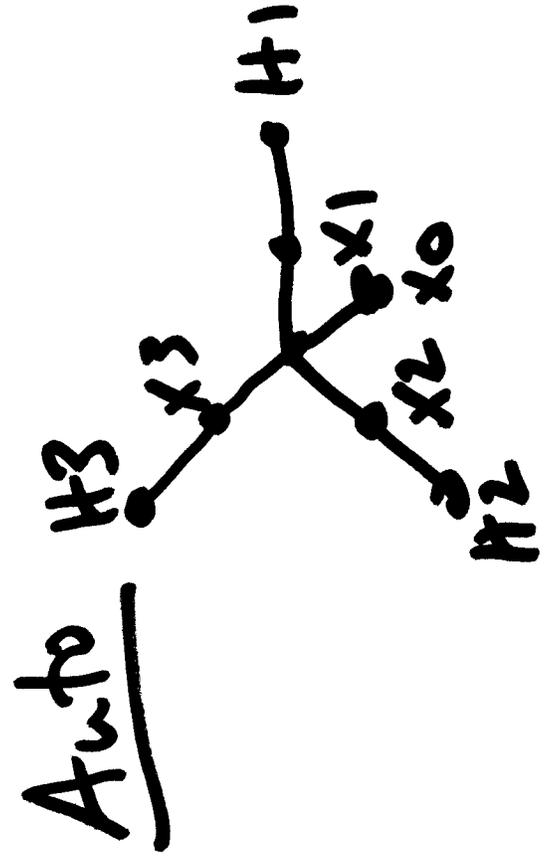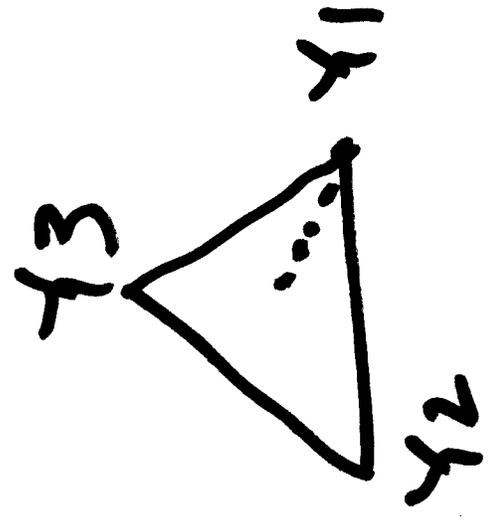


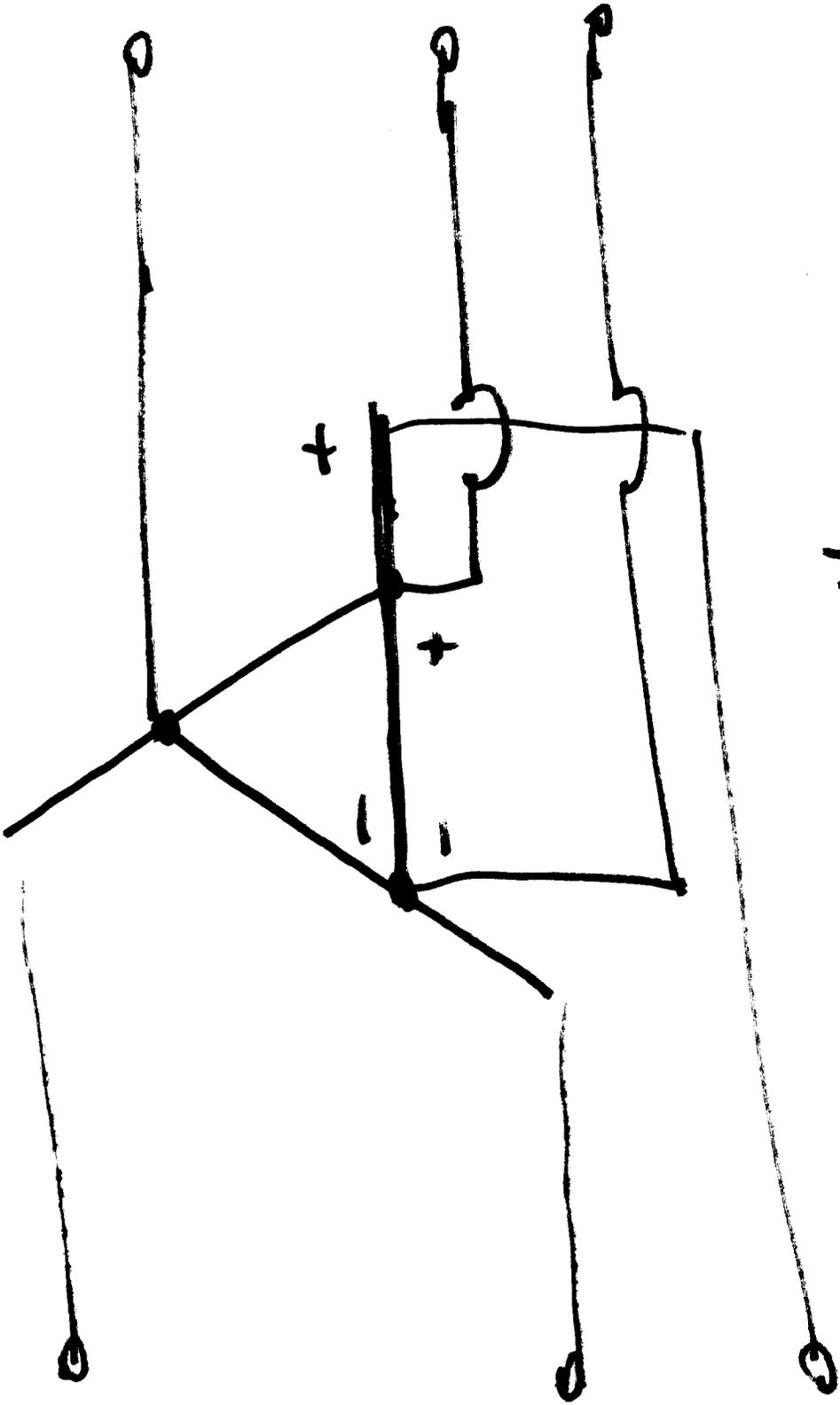

Extend Delta


# Transformer Phase Shifts


- See  $\Delta$ -Y transformer nameplate

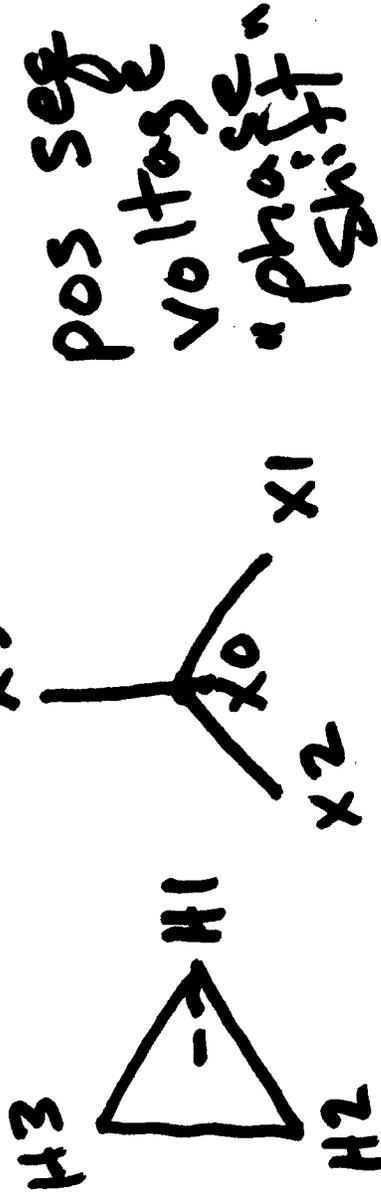

$$\vec{I}_1 \rightarrow \vec{V}_1 = \vec{V}_2 \vec{I}_2$$
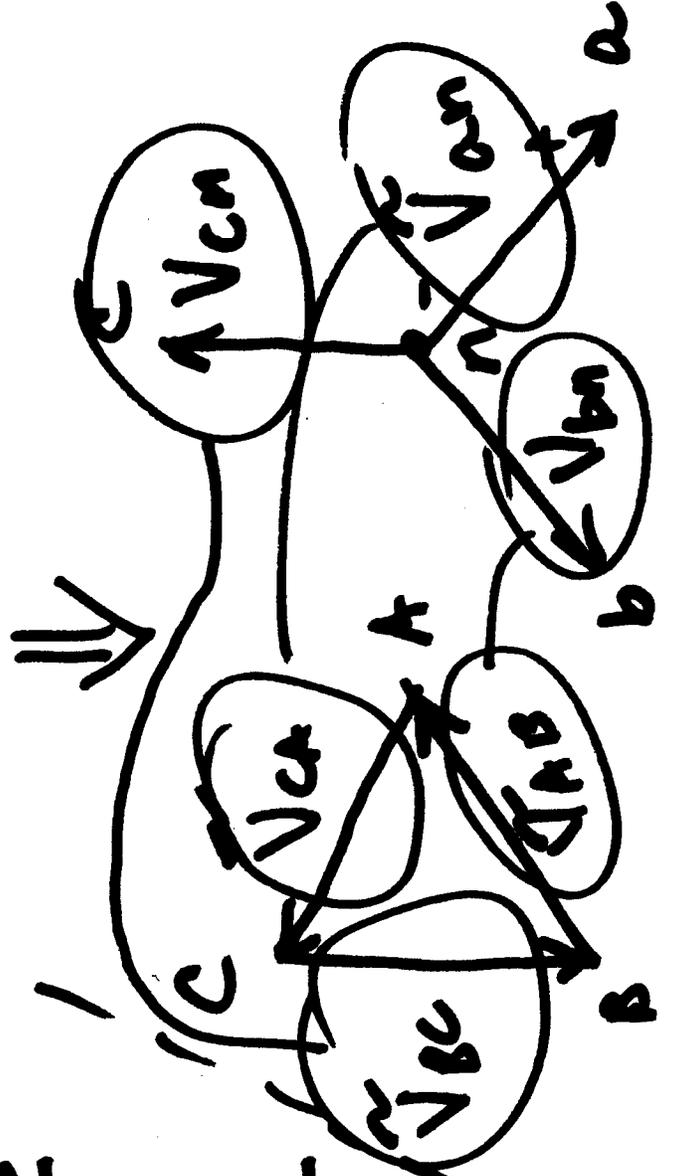
$$\vec{I}_2 \rightarrow \vec{V}_2 = \vec{V}_1 \vec{I}_1$$



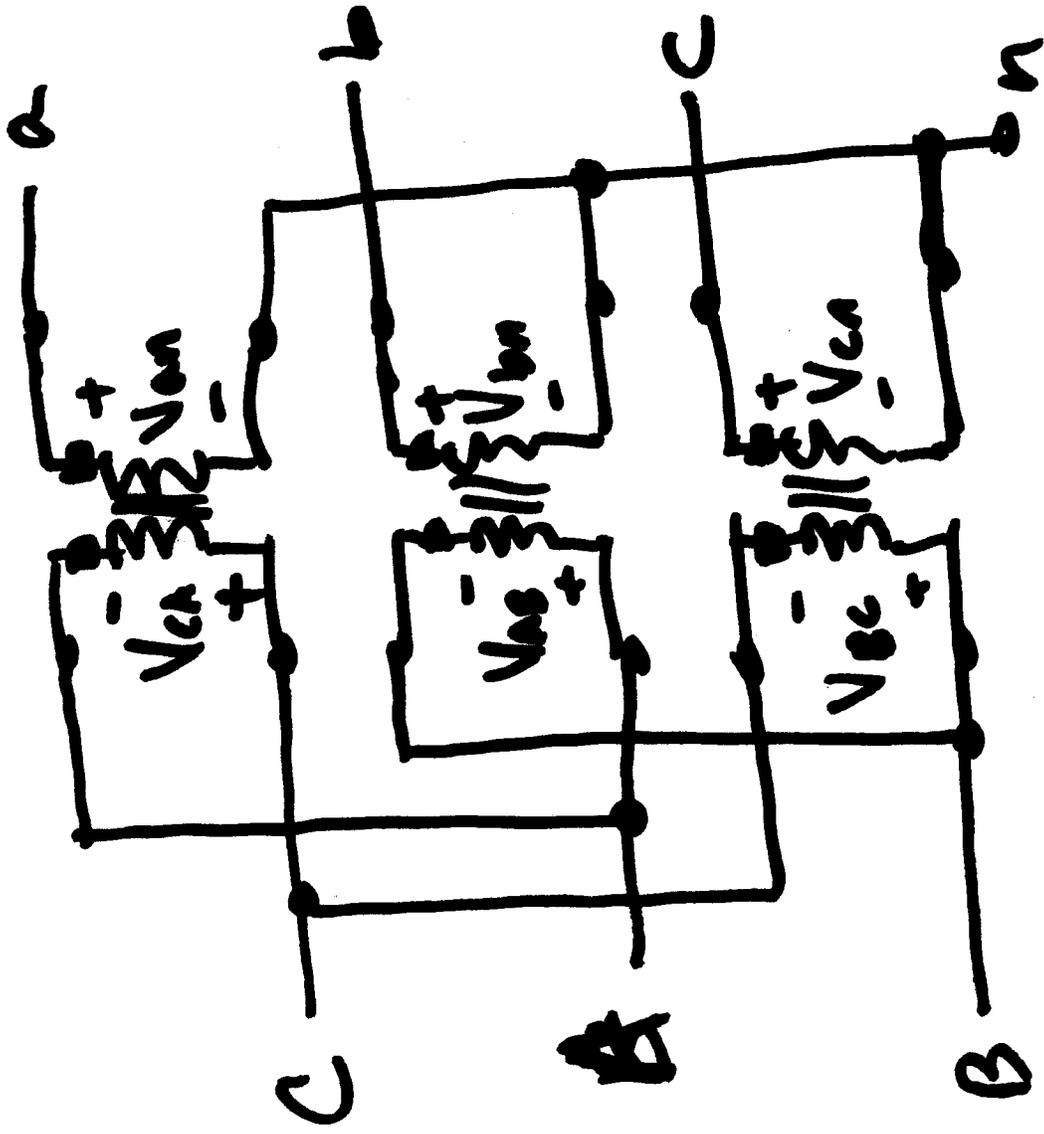


1


# 3-PHASE XFMR BANK

Ex:  $\Delta$ -Y

(Dyn1)



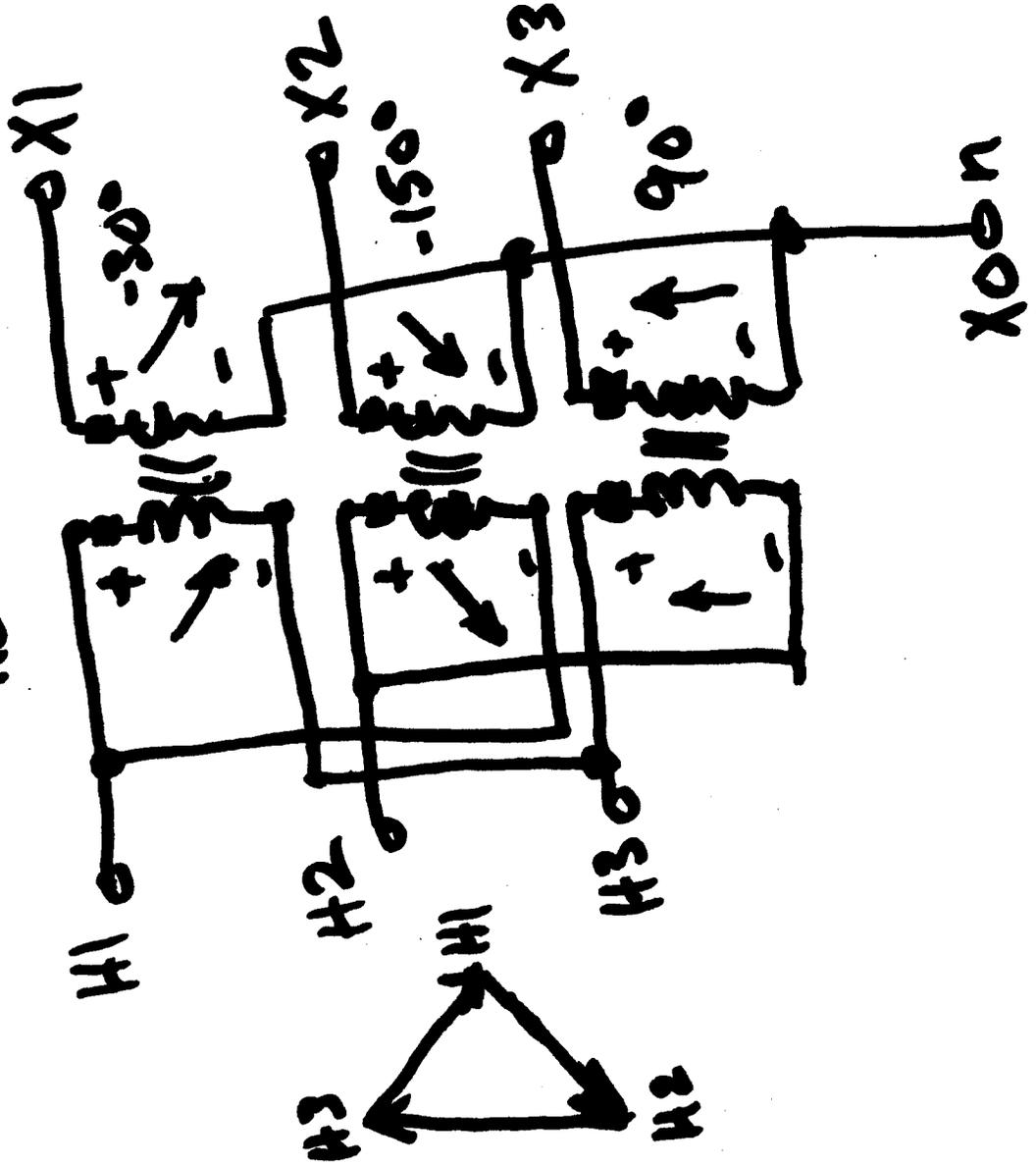



From:  
Review  
Lecture 5

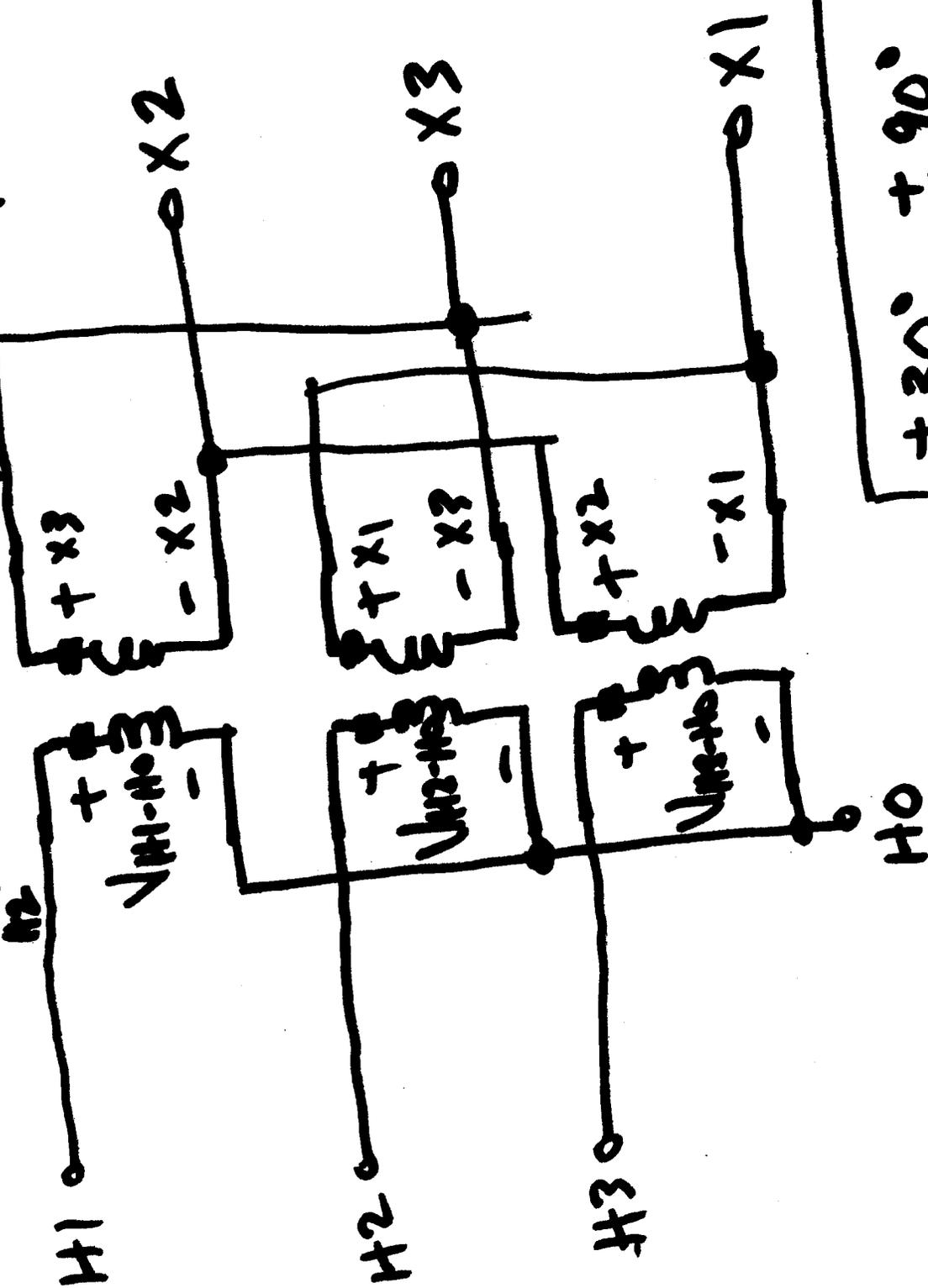

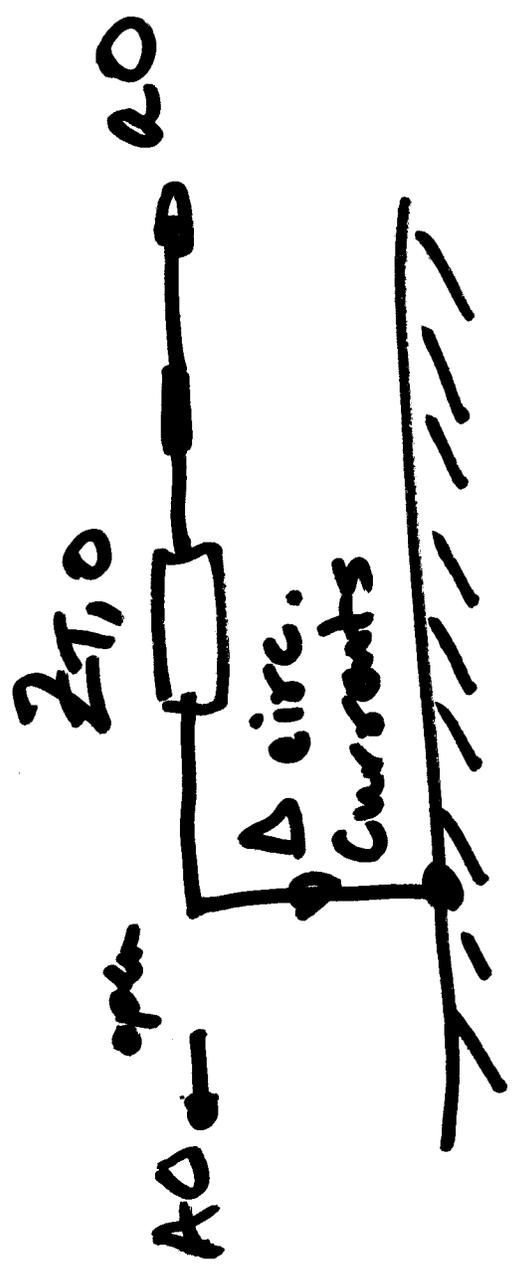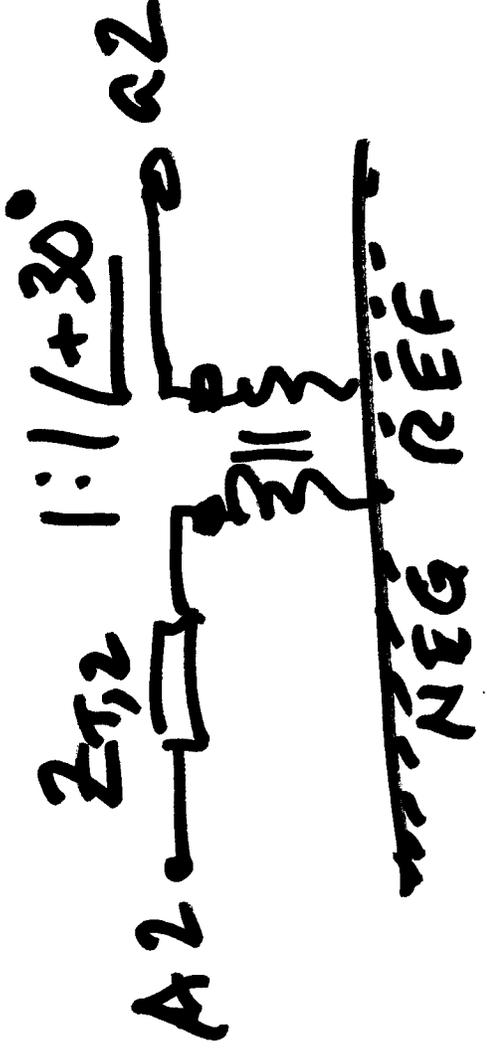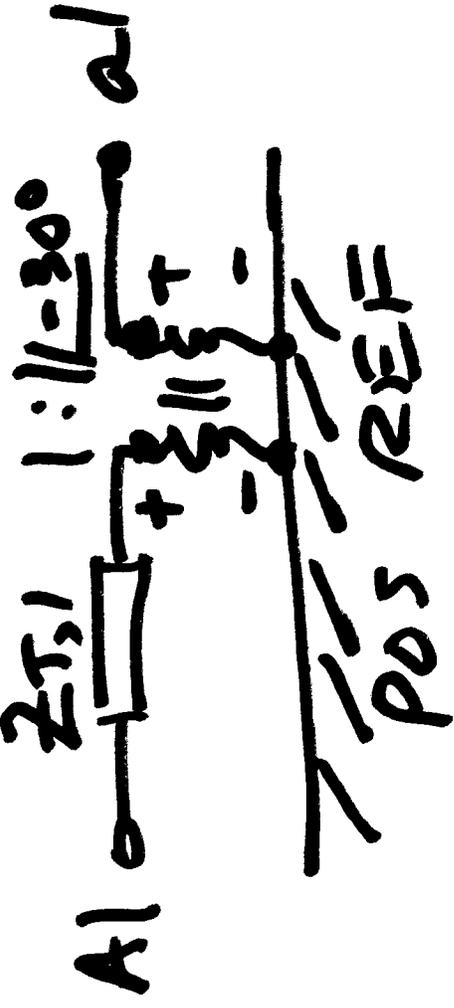
$\pm 30^\circ, \pm 90^\circ, \pm 150^\circ$





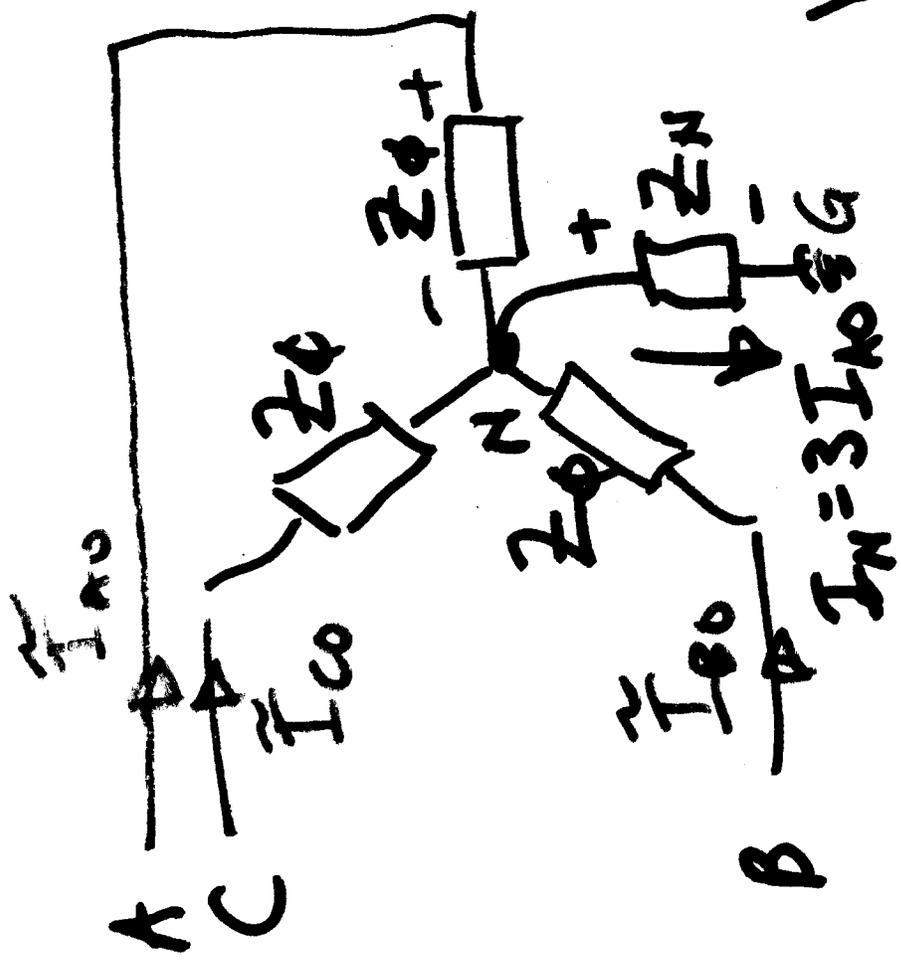

$= V_{NG}$

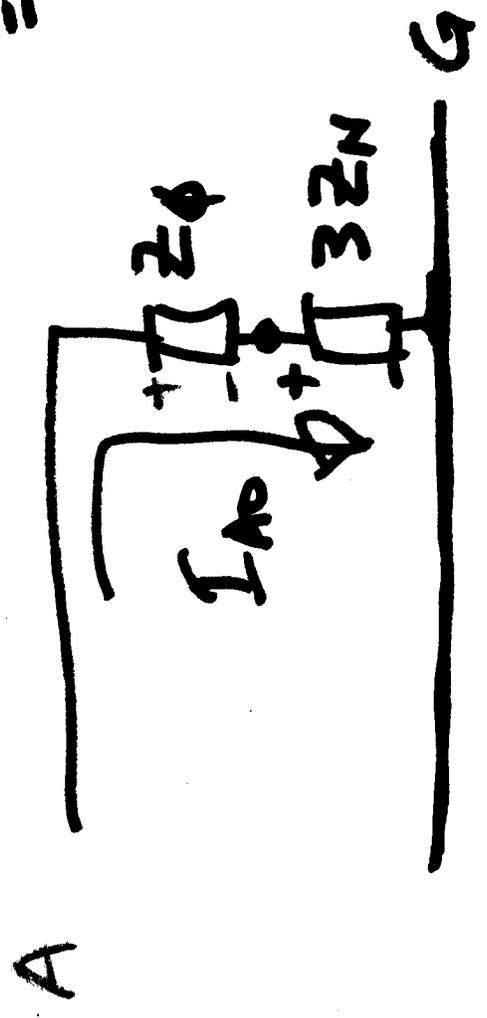

triplex harmonics

buried tertiary

buried delta

---


delta: - trap triplen harmonics

- zero seq circ path



- Aux power (station service)

- Protection

- CTS

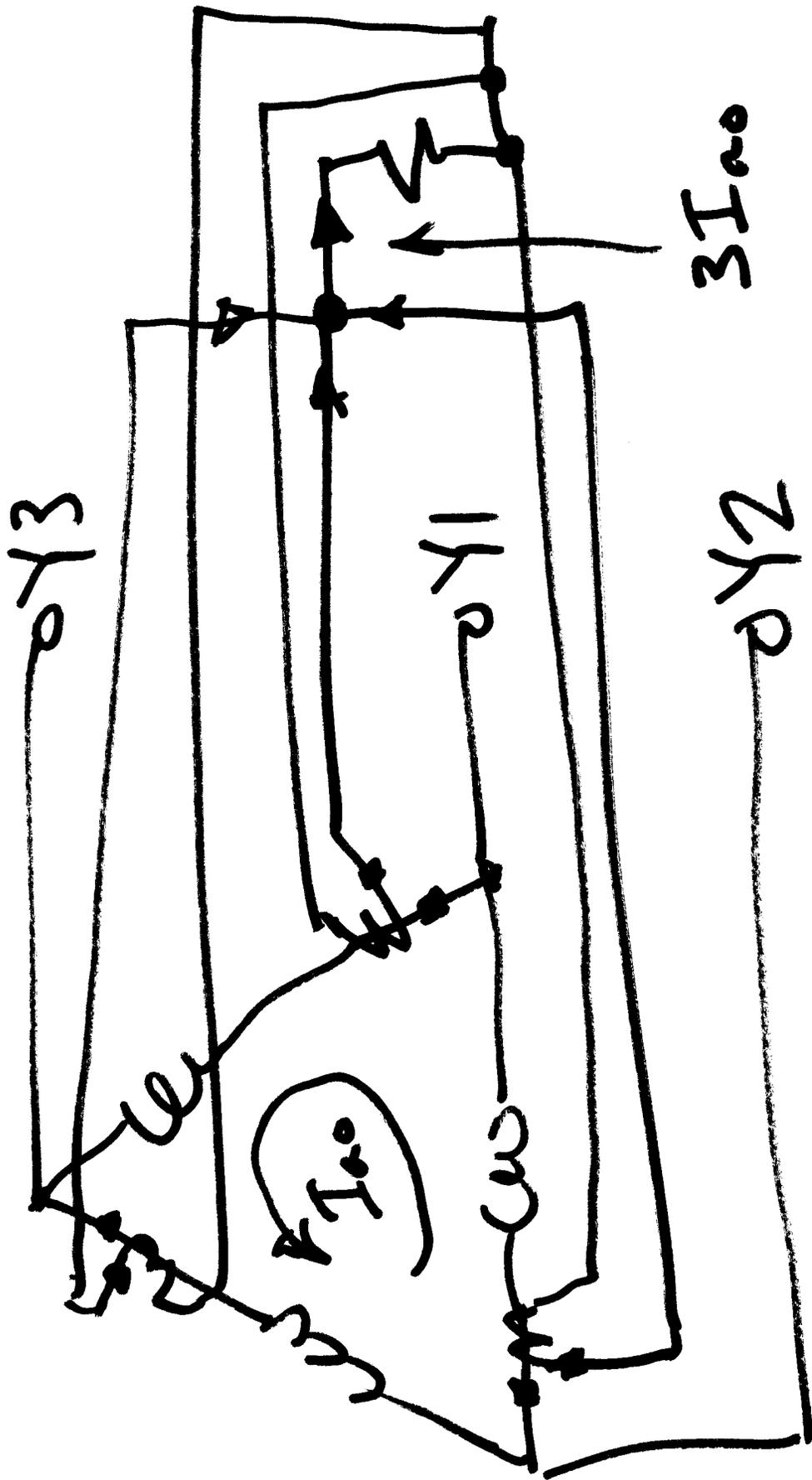


WORK

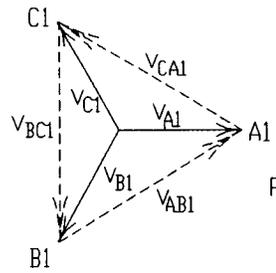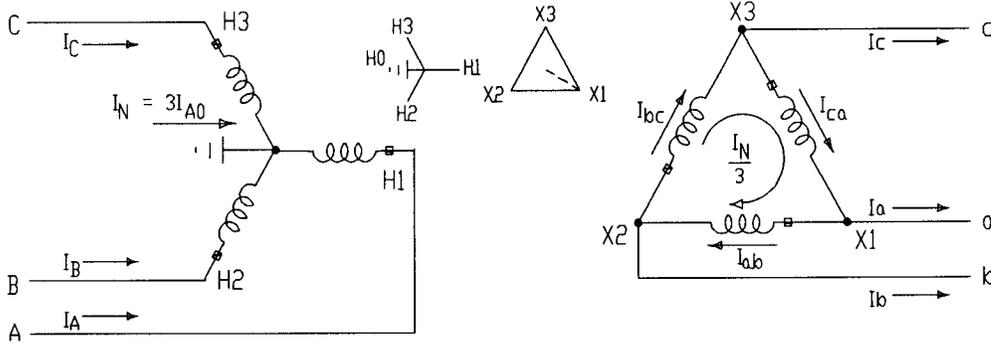


$$V_{A1} = V_{a1} (\angle 30^\circ)$$


PRI POS SEQ VOLTAGES

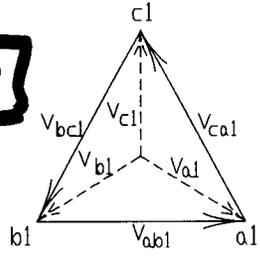


SEC POS SEQ VOLTAGES

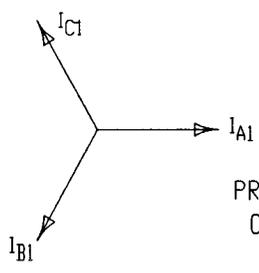

PRI POS SEQ CURRENTS

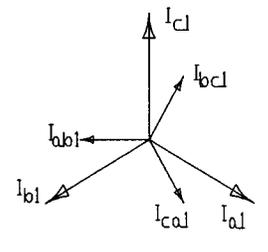


SEC POS SEQ CURRENTS

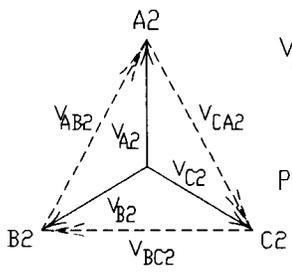


$$V_{A2} = V_{a2} (\angle -30^\circ)$$


PRI NEG SEQ VOLTAGES

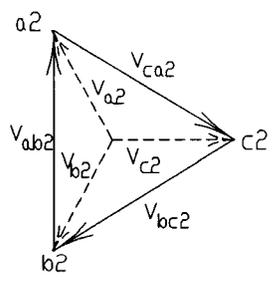

SEC NEG SEQ VOLTAGES

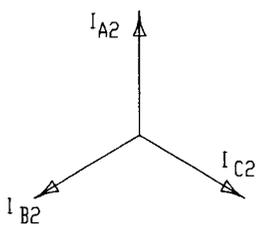



PRI NEG SEQ CURRENTS

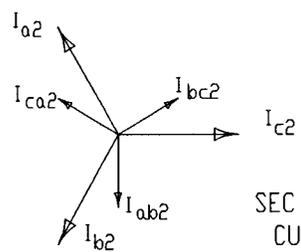

SEC NEG SEQ CURRENTS


ANSI STANDARD 30-DEGREE SHIFT WYE-DELTA

WORK

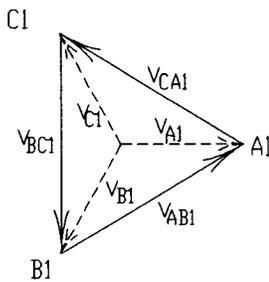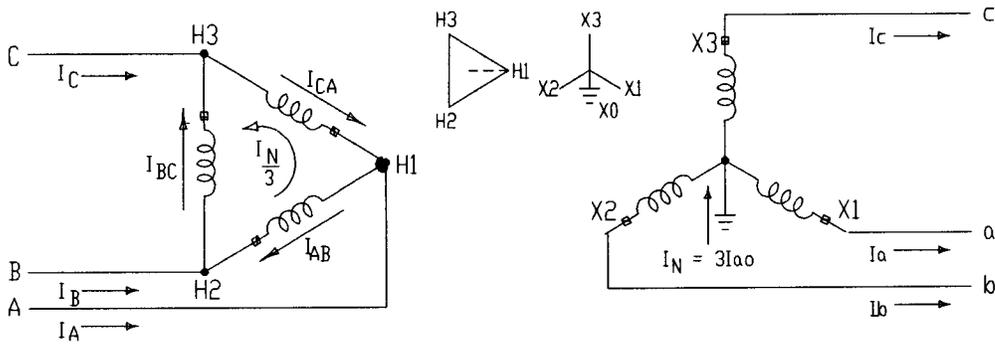


$$V_{A1} = V_{a1} (\angle 30^\circ)$$


PRI POS SEQ VOLTAGES

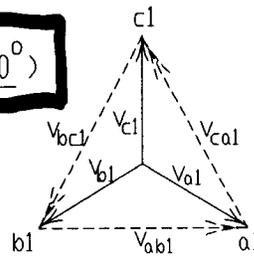


SEC POS SEQ VOLTAGES

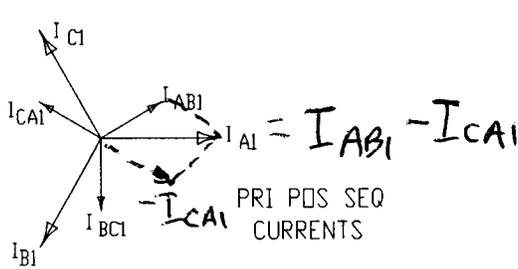

PRI POS SEQ CURRENTS

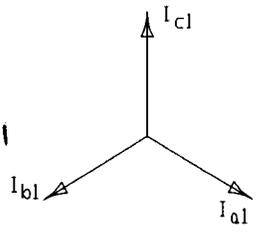


SEC POS SEQ CURRENTS

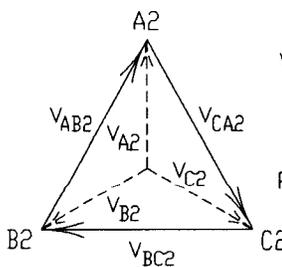


$$V_{A2} = V_{a2} (\angle -30^\circ)$$


PRI NEG SEQ VOLTAGES

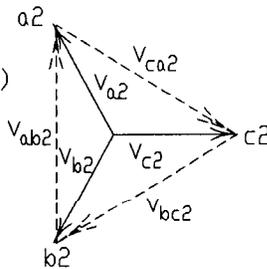

SEC NEG SEQ VOLTAGES

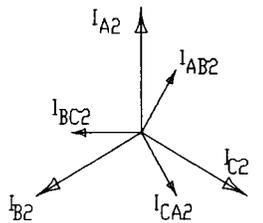

PRI NEG SEQ CURRENTS

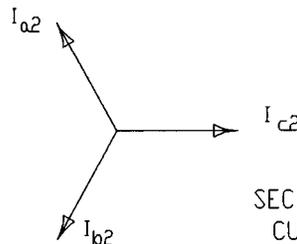

SEC NEG SEQ CURRENTS

ANSI STANDARD 30-DEGREE SHIFT DELTA-WYE