



Topics for Today:

- Announcements
 - Matlab - use remote.mtu.edu remote desktop server...
 - See IEEE Std IEEE Std. 605-2008, Section 11.3.1, for short circuit forces.
 - Office hrs: 11:05-11:55pm W,F in EERC 214
 - Office: EERC 614. Phone: 906.487.2857
 - Recommended problems from Ch.3
- Transformers and circuits w/transformers
 - An example of phase shift, using VTs system protection
 - Paralleling of transformers
 - Proportioning of MVA flow for unequal MVA size, unlike impedances
 - Circuit calculations for above cases
 - Design and operations issues
 - Phase shifting transformers
 - Remaining topics will be covered in context of system operation & analysis, i.e. Chapters 7 and 8.
 - Per phase Pi-equivalent for off-nominal turns ratio, phase shifts, etc.
 - Incorporation in system admittance matrix for short-circuit and load flow

Next: Synchronous Machines - Chapter 3 (starting with Section 3.9)


- Recommended problems & solns for Ch.3 are posted.
- Phasor diagrams - unity, lag, lead
- Salient rotor machines - calculation with X_d and X_q .
- Calculation Example(s)
- P & Q flows thru transmission lines
- More on admittance matrix [Y] construction



USE THIS

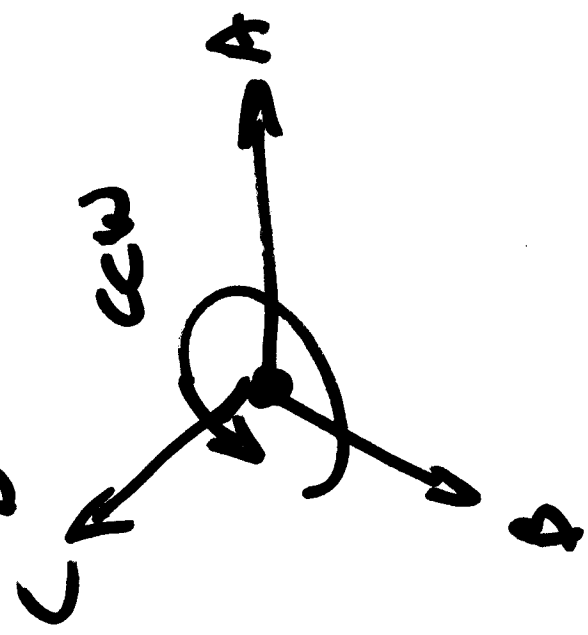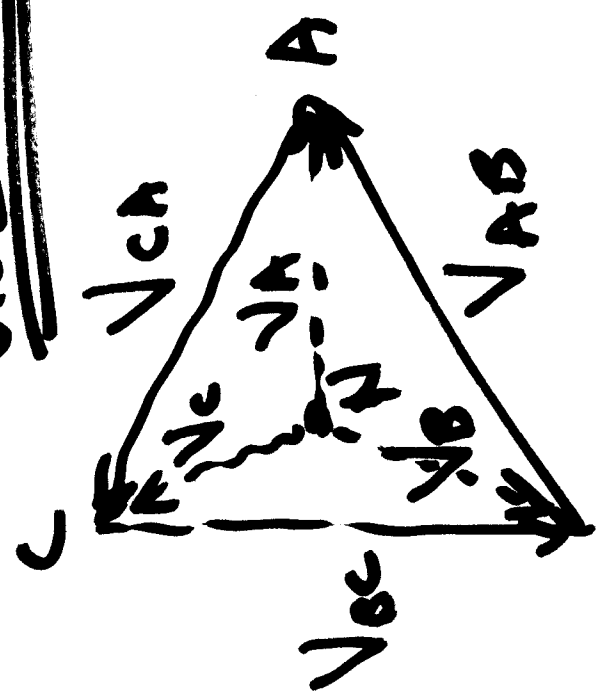

NOT THIS!


See pp. 19, 20
Fig 1.16, 1.17

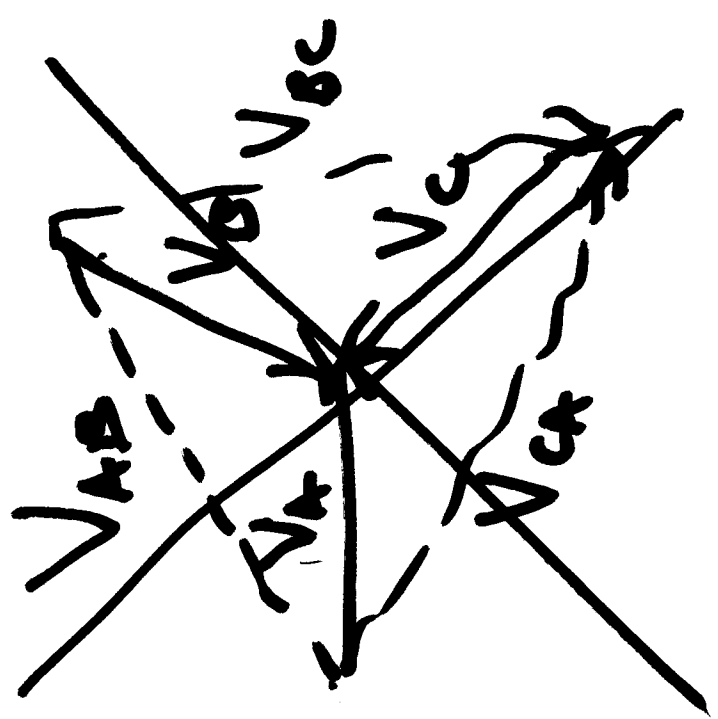


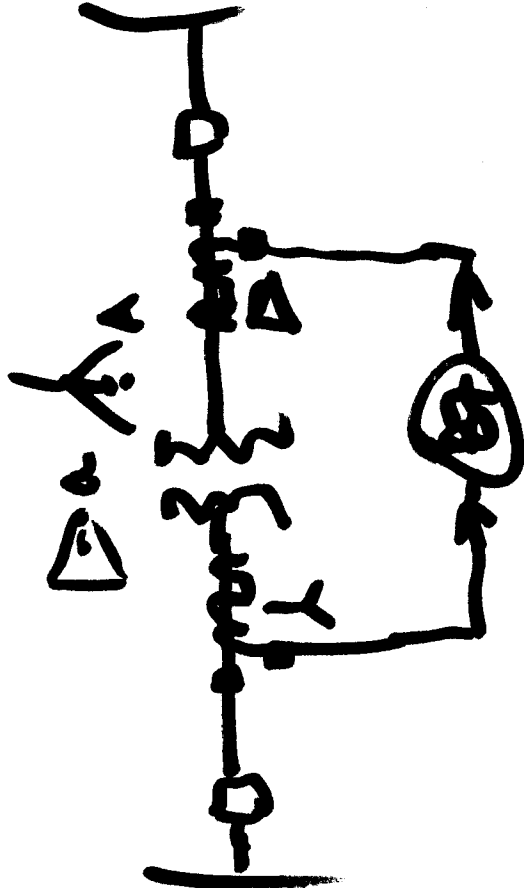
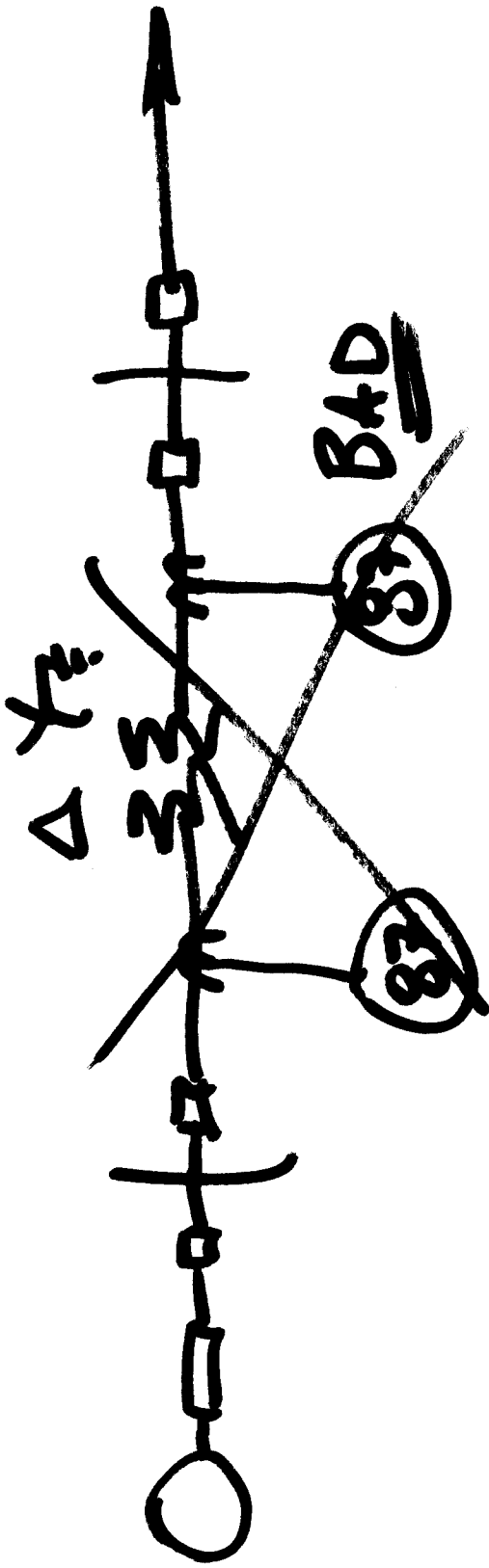


MECT


~~MECT~~

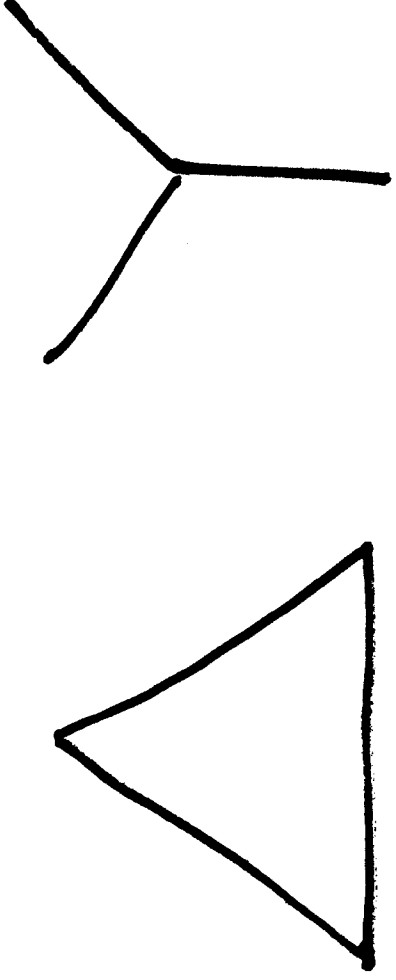

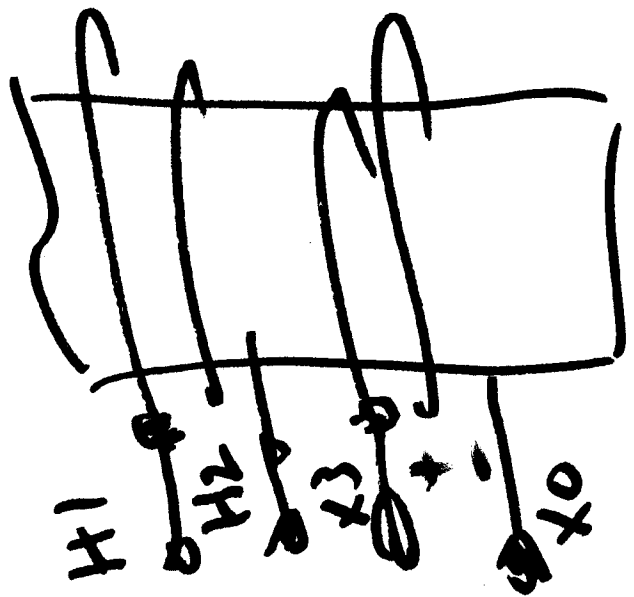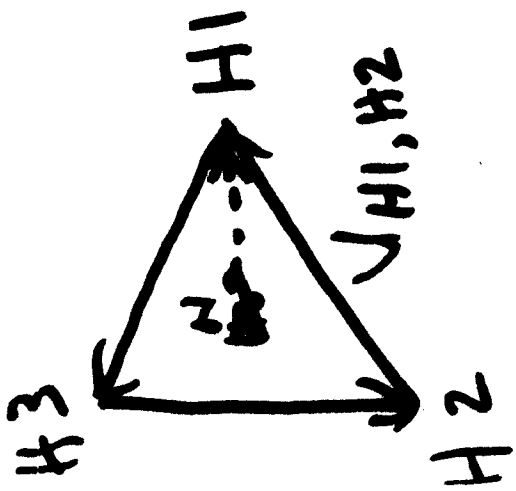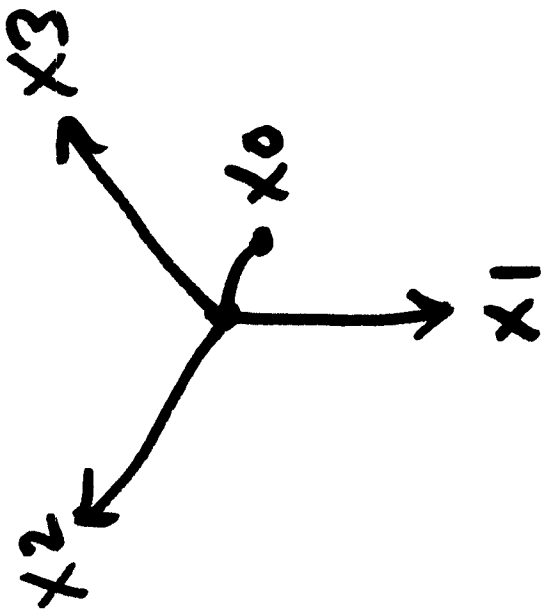- H1 & X1 "corners" not labelled!
- Dashed line missing (H1)
- Applied & induced voltages not aligned!



→ L-G Fault 3

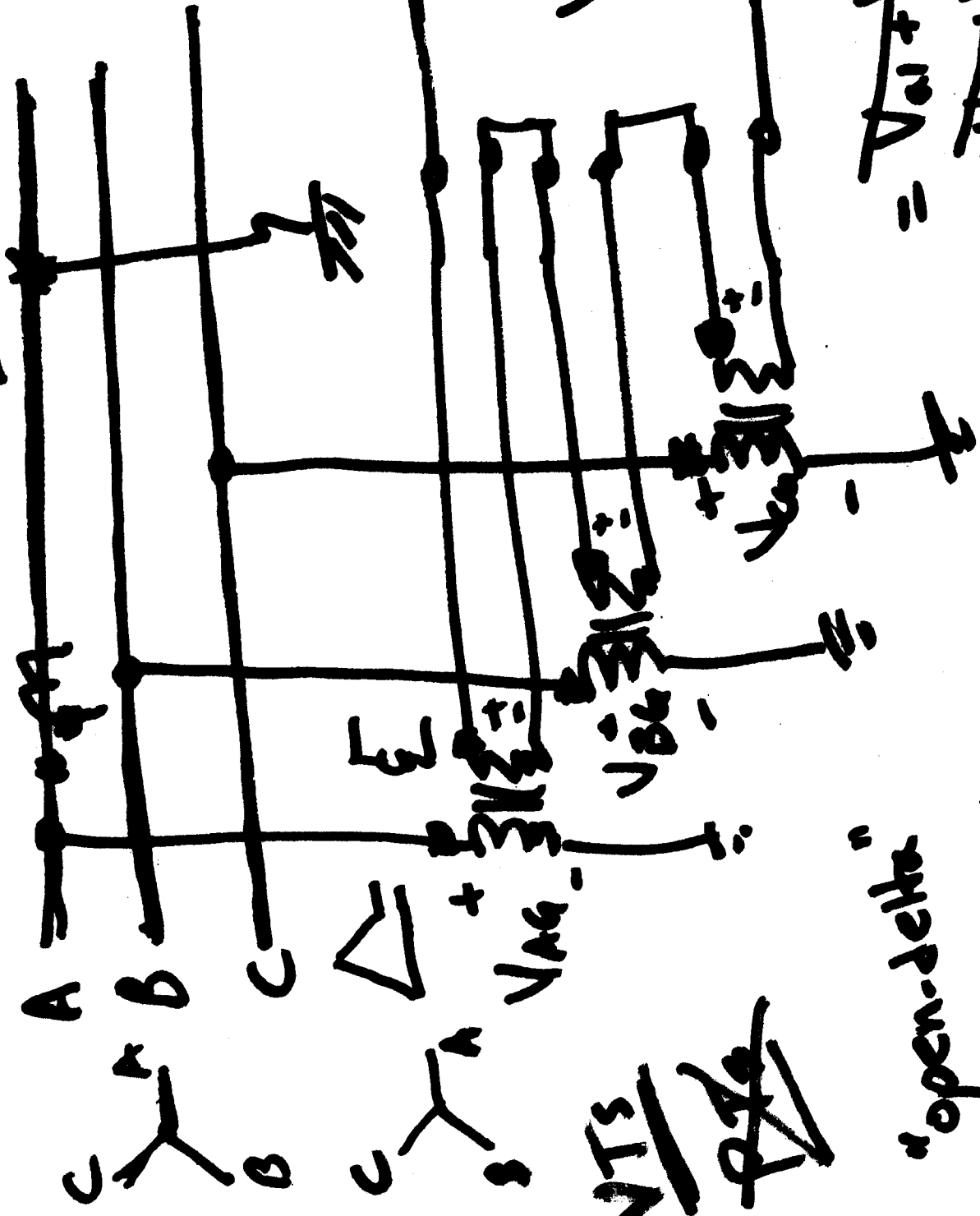

~~VTS~~
~~PTG~~

$$= V_{a1} + V_{a2} + V_{c0} = 0$$



$$+ V_{a2} + V_{a2} + V_{c0} = 0$$

$$+ V_{a0} + V_{b0} + V_{c0} = 3V_{ao}$$



"open-delta"
or "broken delta"

3a


A-6 Fault

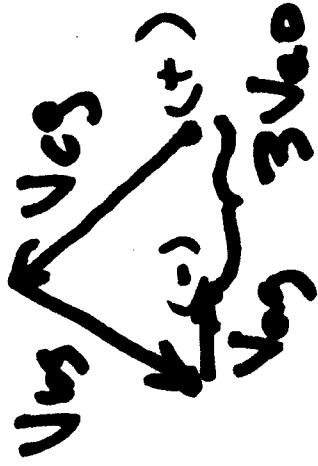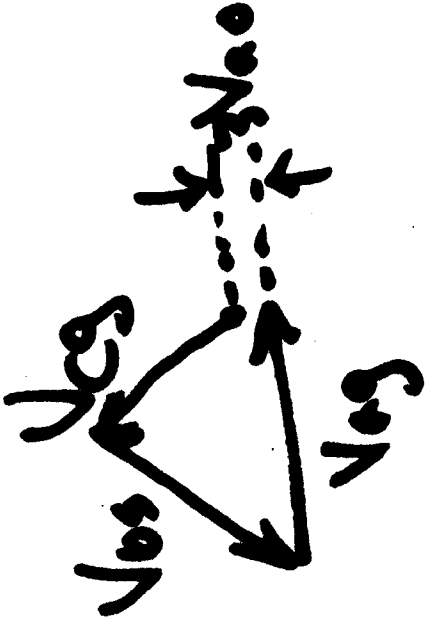


Normal

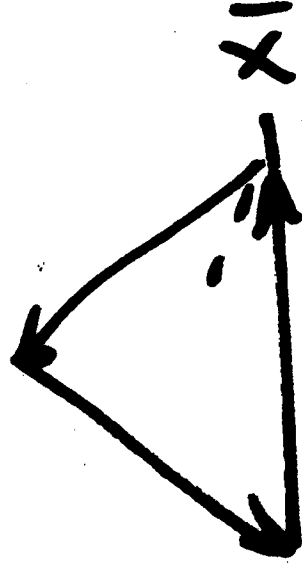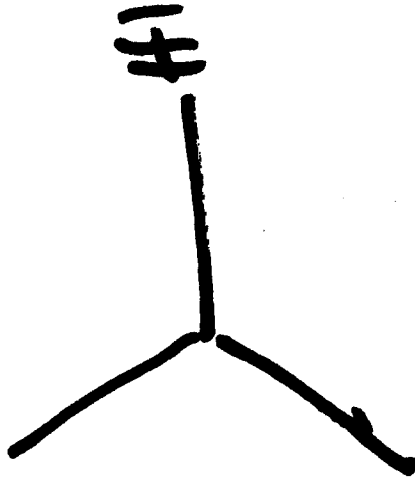



CUST
LOAD


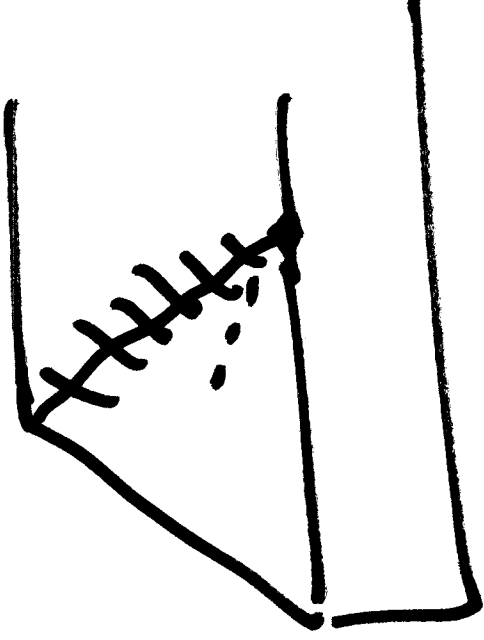


579.0
C


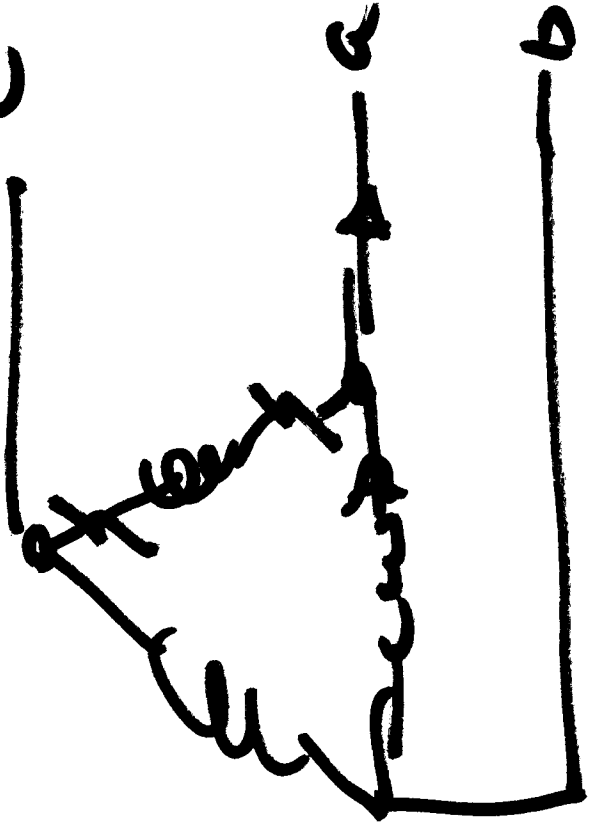


OPEN
DELTA

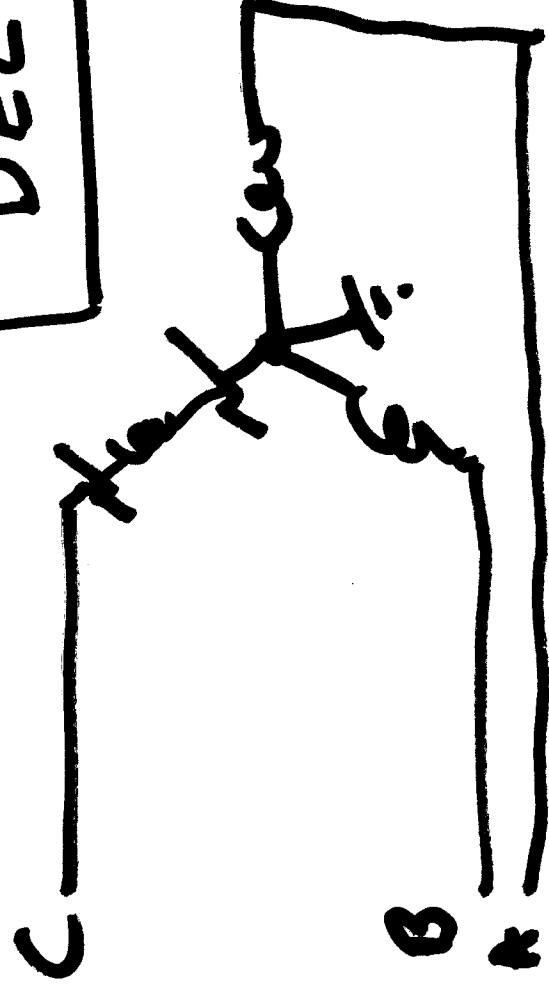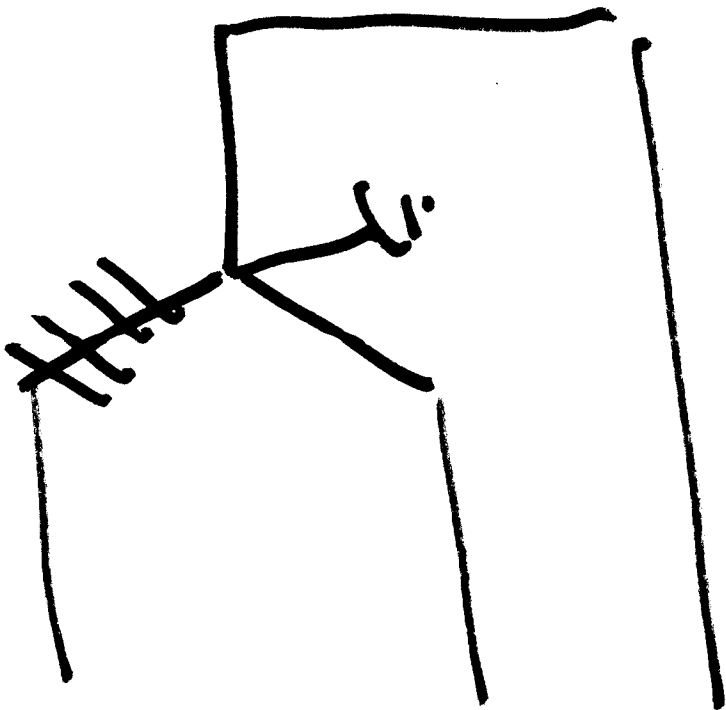


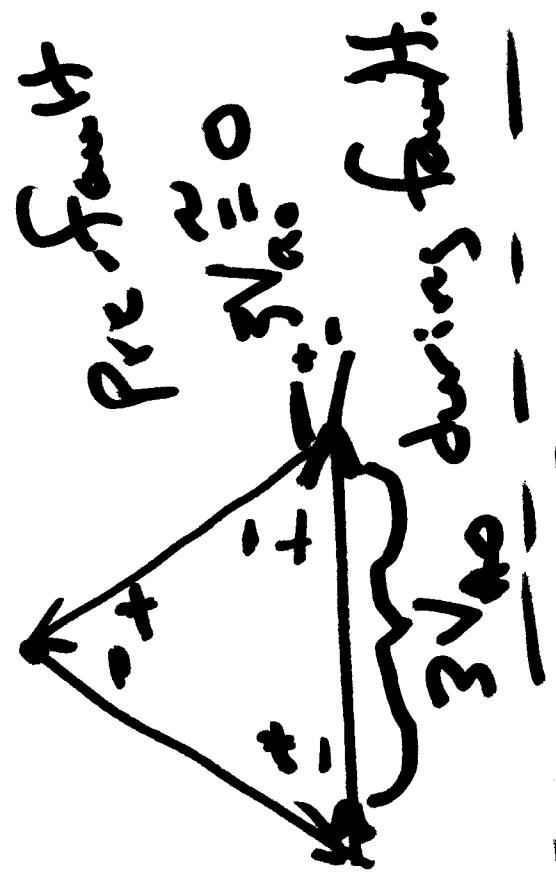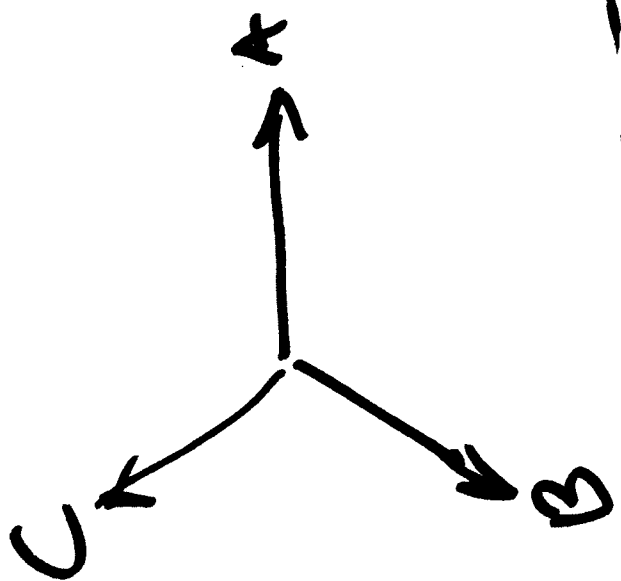

reverse

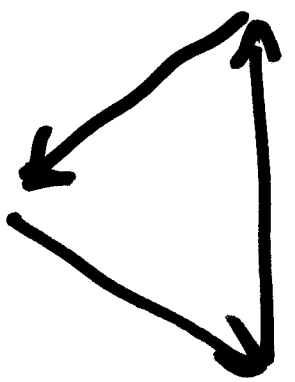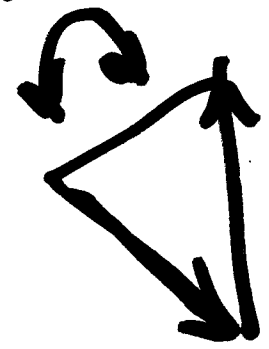


8	Feb.16, '08	MSLEE	HUSONG	J.SLEE	ADDED NEW CONNECTION DIAGRAMS & DETAILS	DSN	CHK	APP	PROJ. 3RD	TITLE : 3PH 60HZ 2688/258/448VA 345/115/24KV CONNECTING PLATE
7	Feb.16, '08	MSLEE	HUSONG	J.SLEE	REVISED TV BUSING POSITION AND CT RATIO(CT33)	DSN	CHK	APP	UNIT Inch	PROJECT NO. 200702171003-001 200706271009 & 010
6	Nov.21, '07	MSLEE	HUSONG	J.SLEE	ADDED THERMAL RATING FACTOR	DSN	CHK	APP	SCALE 1/1	CAD LM/1388&12
5	Nov.04, '07	MSLEE	HUSONG	J.SLEE	REVISED TV CONNECTION	DSN	CHK	APP	SIZE A3	REF. ND. LM/1388&12
4	Sep. 18, '07	MSLEE	HUSONG	J.SLEE	REVISED TV BUSING POSITION AND CONNECTION DIAGRAM	DSN	CHK	APP	REF. ND. TL1388-A11	SHEET 1 OF 1
3	Sep. 18, '07	MSLEE	HUSONG	J.SLEE	REVISED SINGLE PHASE CT CLASS AND BURDEN	DSN	CHK	APP	REF. ND. TL1388-A12	REV. 8
2	Aug. 18, '07	MSLEE	HUSONG	J.SLEE	REVISED CT RATIO CT31 TO CT33	DSN	CHK	APP	DESCRIPTION	
1	JULY 16, '07	MSLEE	HUSONG	J.SLEE	ADDED SERIES REACTOR	DSN	CHK	APP		

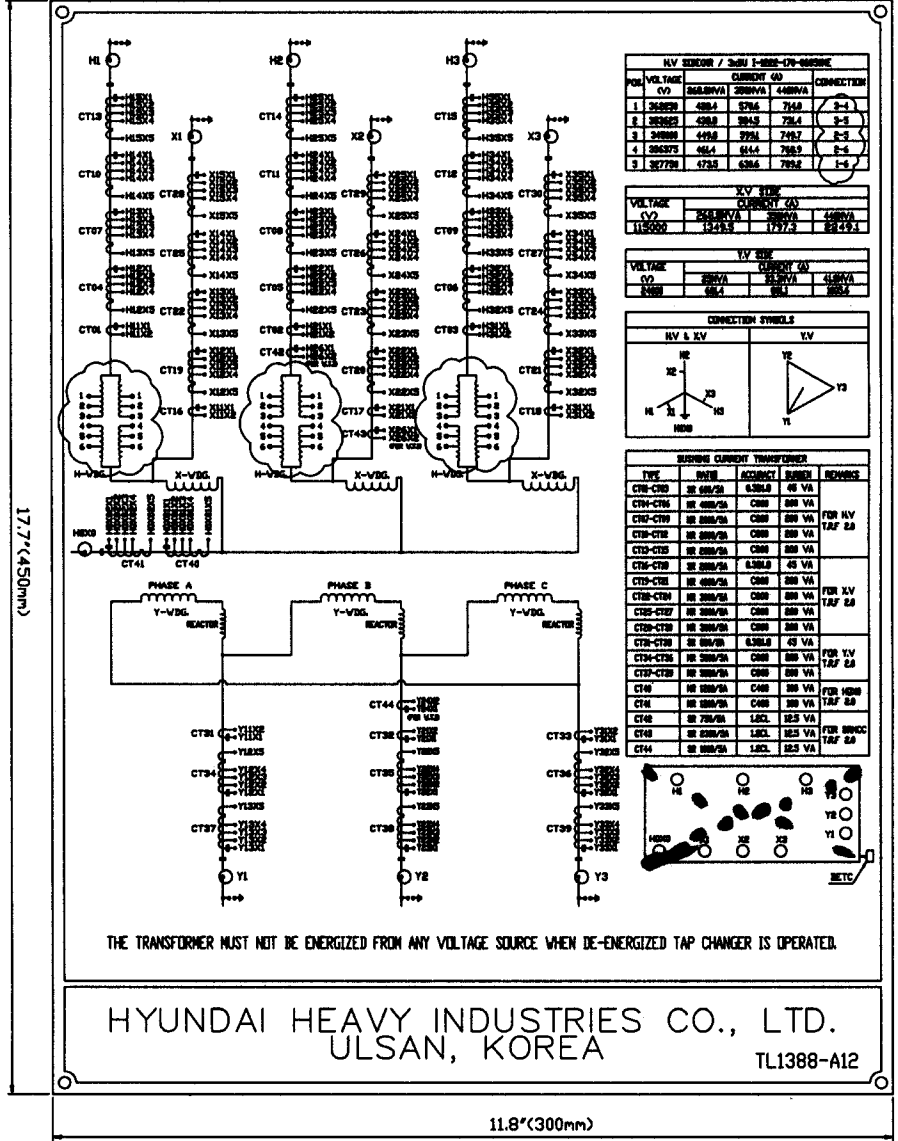

- * NOTE
1. MATERIAL : STAINLESS STEEL
 2. DIMENSION : T.0.4(1.0) x 11.8(300) x 17.7(450) Inch(mm)
 3. NATURAL FACE, DARK LETTER AND LINE

PHASE SHIFTING:


Mathematically: Sequence networks

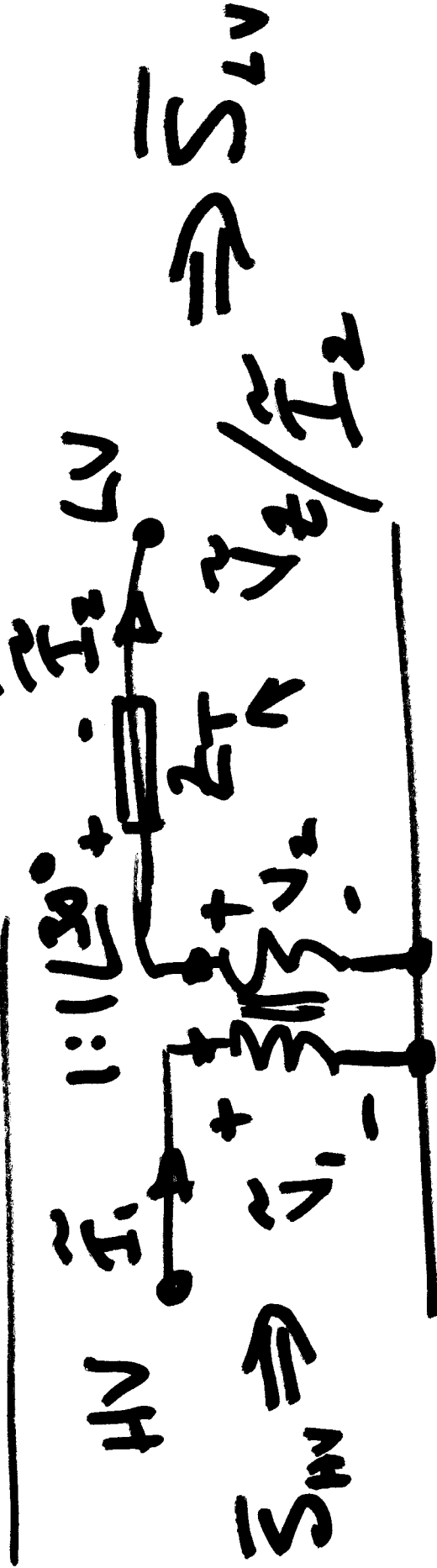

$$S_{HV} = S_{LV}$$

$$V_1 I_1^* = V_2 I_2^*$$

Can prove that if $\left| \frac{V_1}{V_2} \right| = 1$, then Z_T is same on HV side.

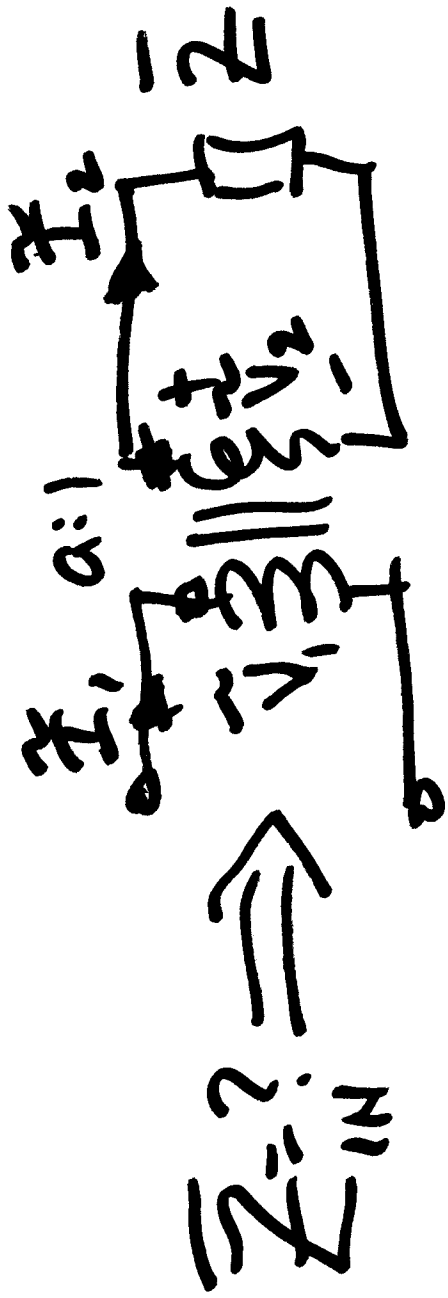

$$Z_{IN} = \frac{V_1}{I_1} = \frac{V_2 + aV_1}{I_2} = \frac{V_2 + aI_2 Z}{I_2} = \frac{V_2}{I_2} + aZ$$


$$\boxed{Z_{IN} = Z}$$

$$\boxed{I_1 = \frac{I_2}{a}}$$

$$\boxed{V_1 I_1^* = V_2 I_2^*}$$

$$\Rightarrow \frac{I_1^*}{I_2^*} = \frac{1}{a} \Rightarrow \frac{1}{a}$$

POWER TRANSFORMERS (w/ PHASE SHIFT)

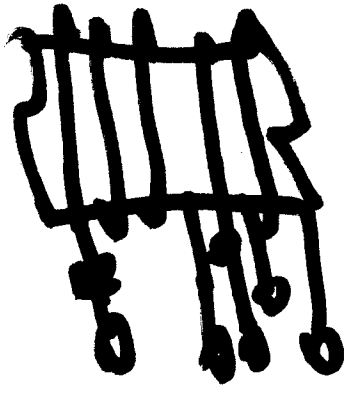

"PS" C § 2.9 of text



Fig 2.22


OUTPUT

INPUT





Errata

Fig. 2.23

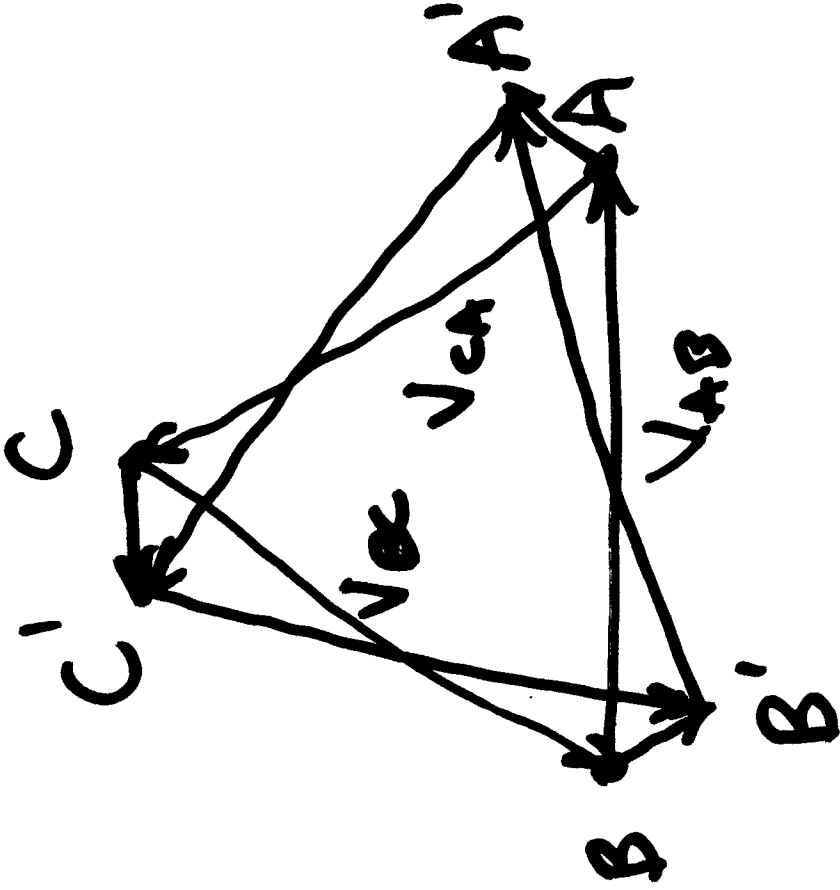

Typically:
 ± 50

(See also Fig. 2.21)

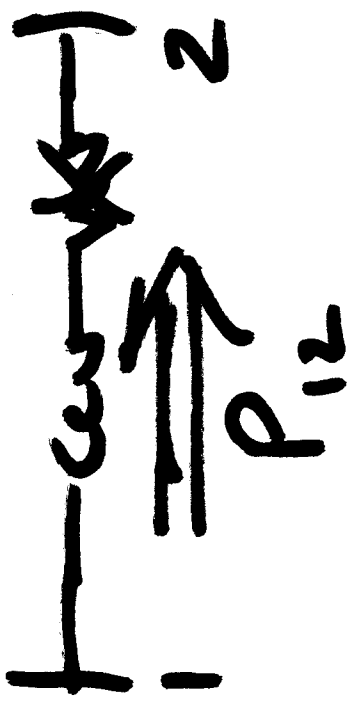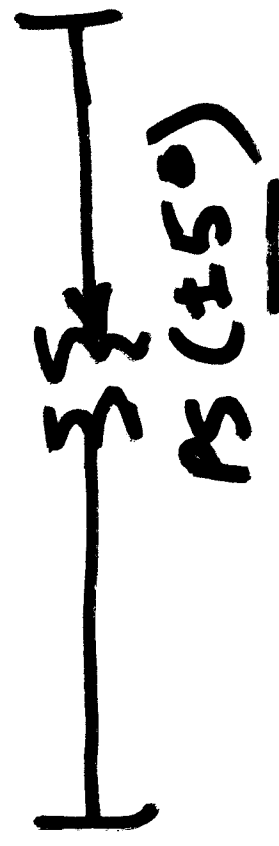


$$I_1 \rightarrow jX_T \rightarrow \cos \rightarrow \frac{1}{\sqrt{2}} I_1 I_2$$

$$V_1 \cos \alpha = V_2 \cos \beta \Rightarrow V_2 = V_1 \frac{\cos \alpha}{\cos \beta}$$

$$P_{1 \rightarrow 2} = \frac{V_1 V_2}{X_T} \sin(\alpha - \beta)$$

Increase $P_{1 \rightarrow 2}$: decrease β (increase $\alpha - \beta$)
 Decrease $P_{1 \rightarrow 2}$: increase β (decrease $\alpha - \beta$)

Next: Paralleling Transformers

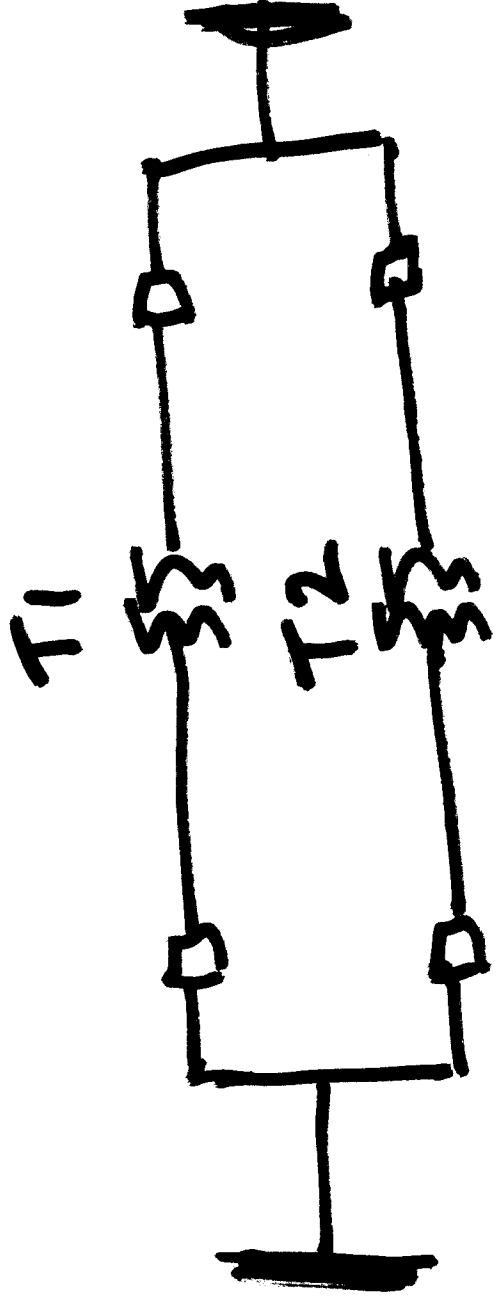

Works well if T1 & T2 are "matched"


- ISSUES:
- Impedances
- Exact voltage ratios

Paralleling XFMRs:

- Unlike impedances, same voltage ratio

Base: on 100MVA

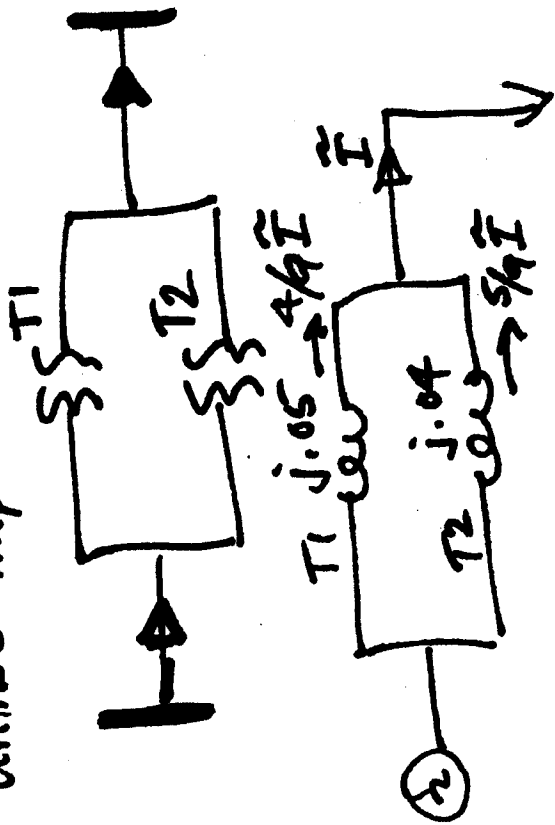T1: 90 MVA $j.05$ p.u.
 T2: 100 MVA $j.04$ p.u.



Ratings
 (90 MVA)
 (100 MVA)

Constraints
 $\frac{I_{T1}}{I_{T2}} = \frac{4}{5}$

LOAD


If T1 @ 90 MVA, T2 @ ~~90~~ 77.5 MVA
 BAD

If T2 @ 100 MVA, T1 @ 80 MVA
 GOOD/OK

Key: Spec same %Z on Base of indiv XFMRs!
 i.e. T2: j.04 @ 100 MVA BASE
 T1: j.04 @ 90 MVA BASE

Michigan Tech Instructor: Bruce Mork Phone (906) 487-2857 Email: bamork@mtu.edu

However, can't use 10MVA of T1 capacity.


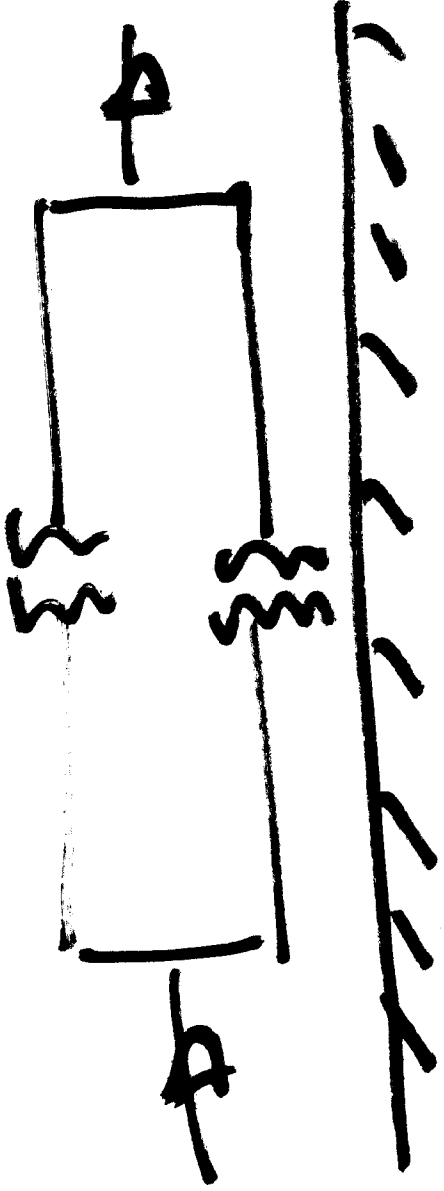


In general, voltage ratios & impedances may not be matched.

Then what?

- Circuit analysis ✓
- Network $[Y]$ - Ch. 7, 8

CASE 1

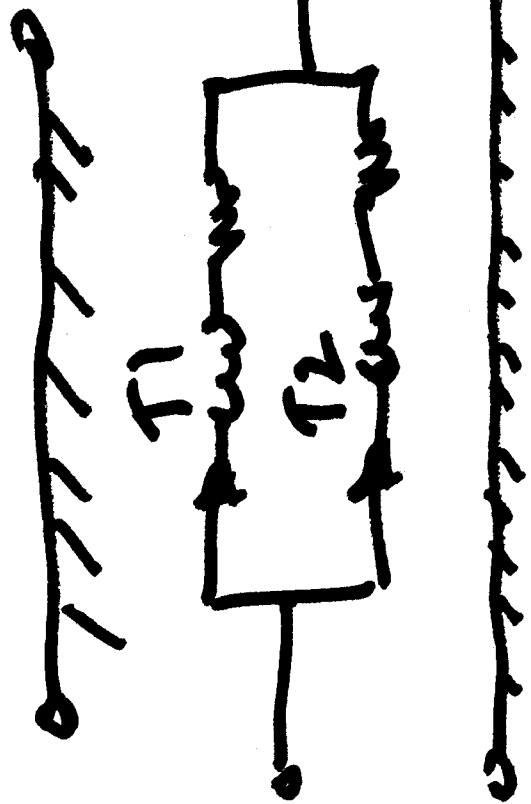
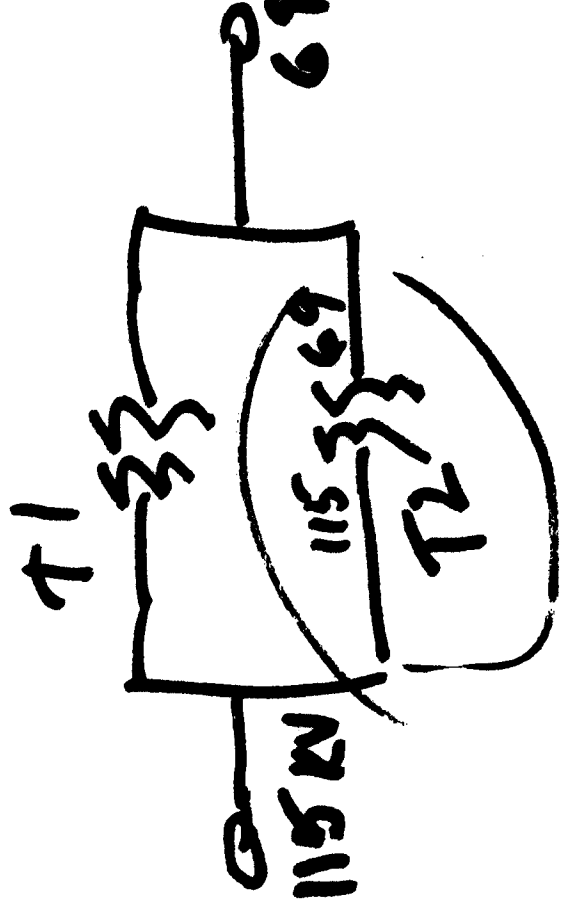


Paralleling
- "unlike"
- impedances.

- Equal turns ratios which match VBASE of system.


Key: Zsc of $T1 \neq T2$ equal on base of respective xbars.

CASE 1

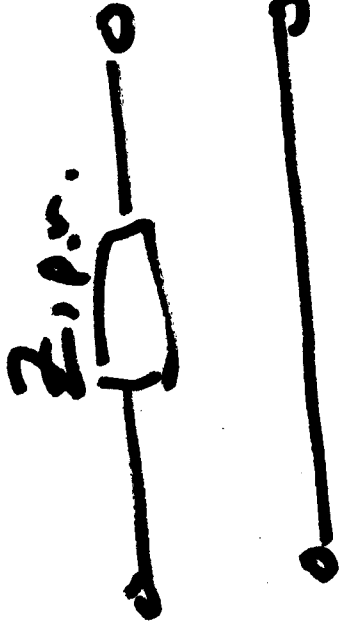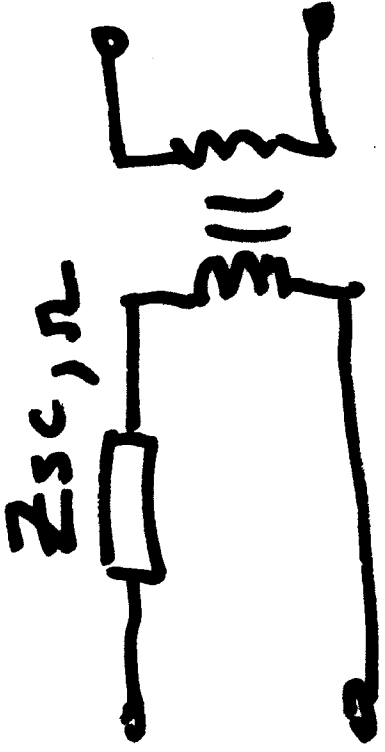

$p.u. \Rightarrow$

CASE 2

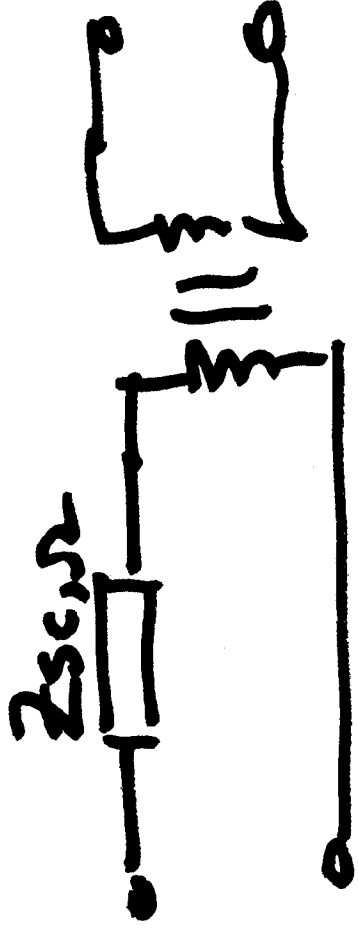


$p.u. \Rightarrow$? .

CASE 2

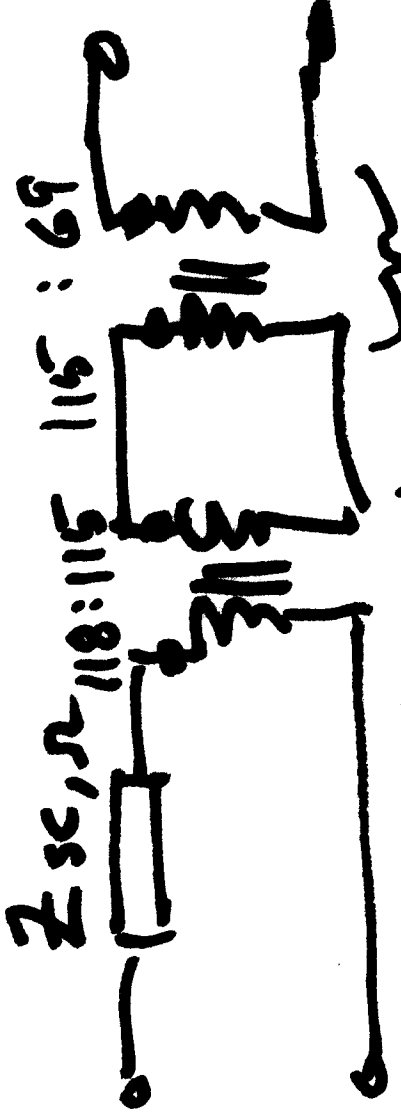
- Turns ratio (voltage ratio) of x_{fmr} is not equal to ratio of V_{BASE} of system.






off-nominal Voltage Ratio
 off-nominal Voltage Ratio

per unit

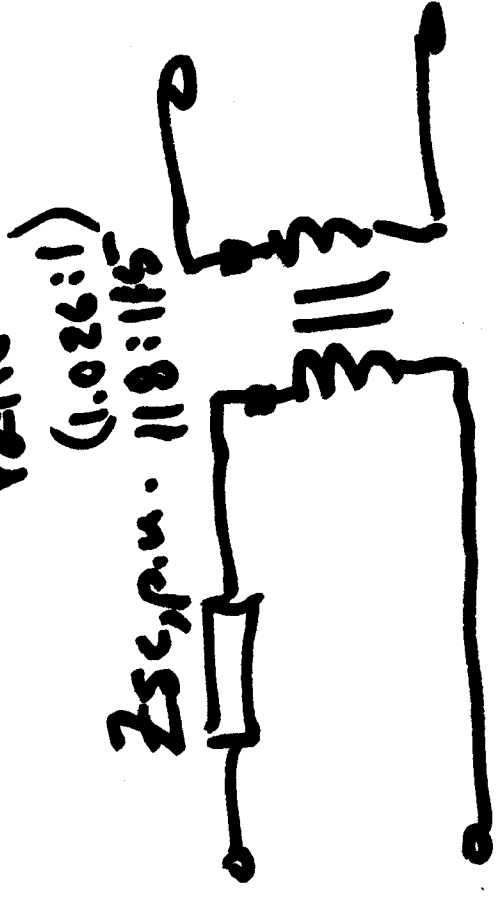


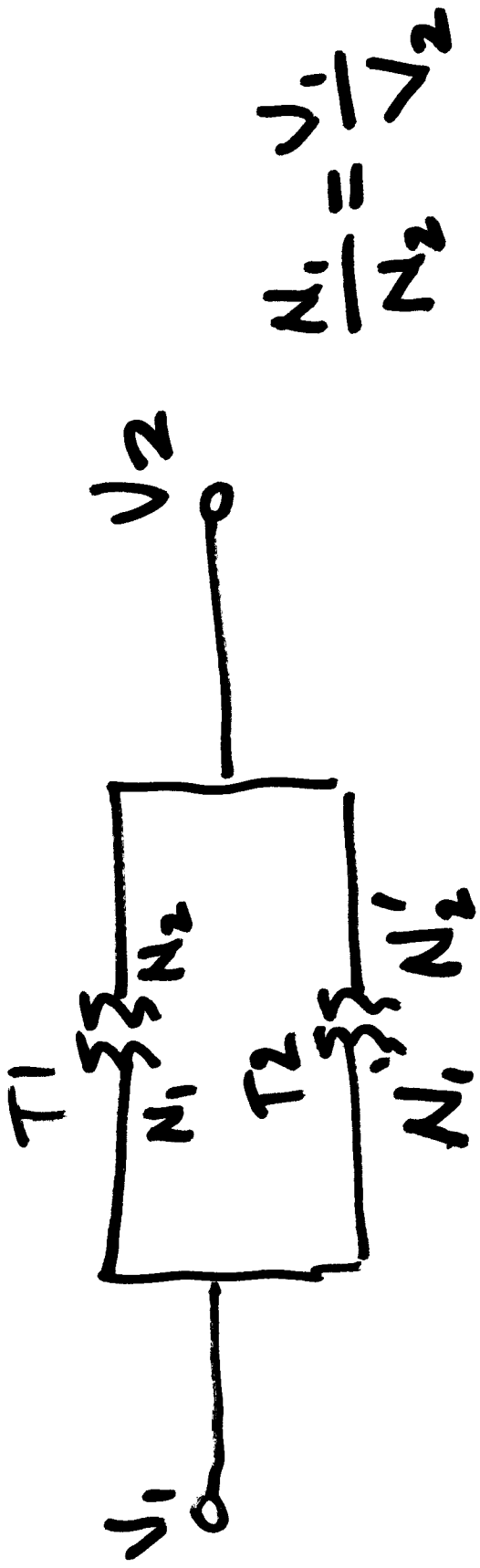

$$\frac{N_1}{N_2} = \frac{V_1}{V_2}$$


What happens if $\frac{N_1}{N_2} \neq \frac{V_1}{V_2}$?

Per Unit Equiv is thus:

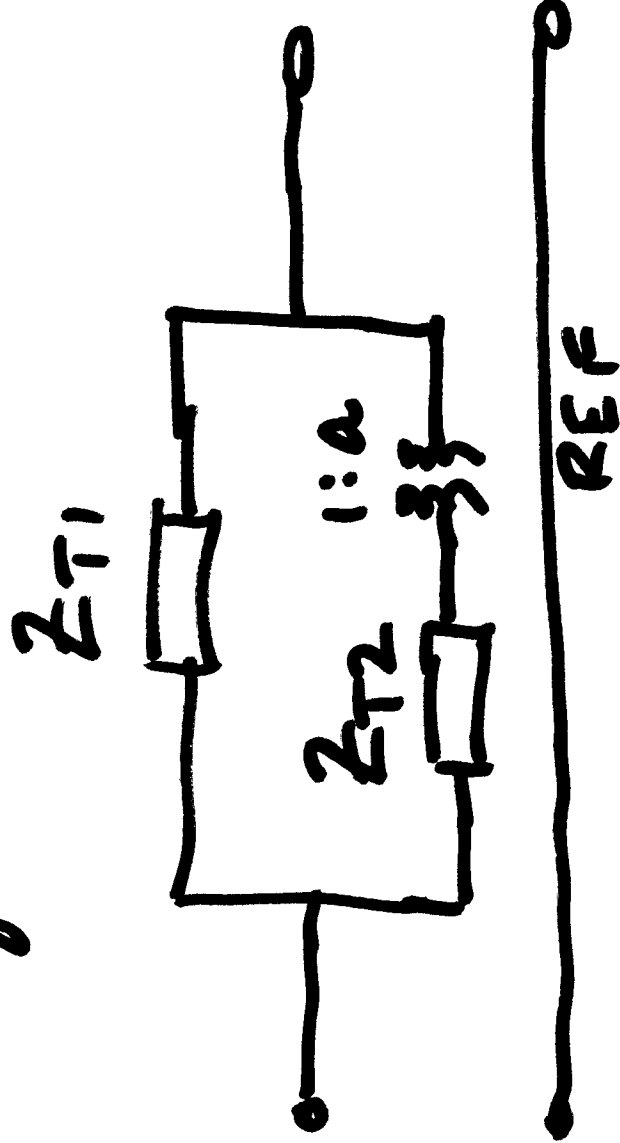

3 Methods:

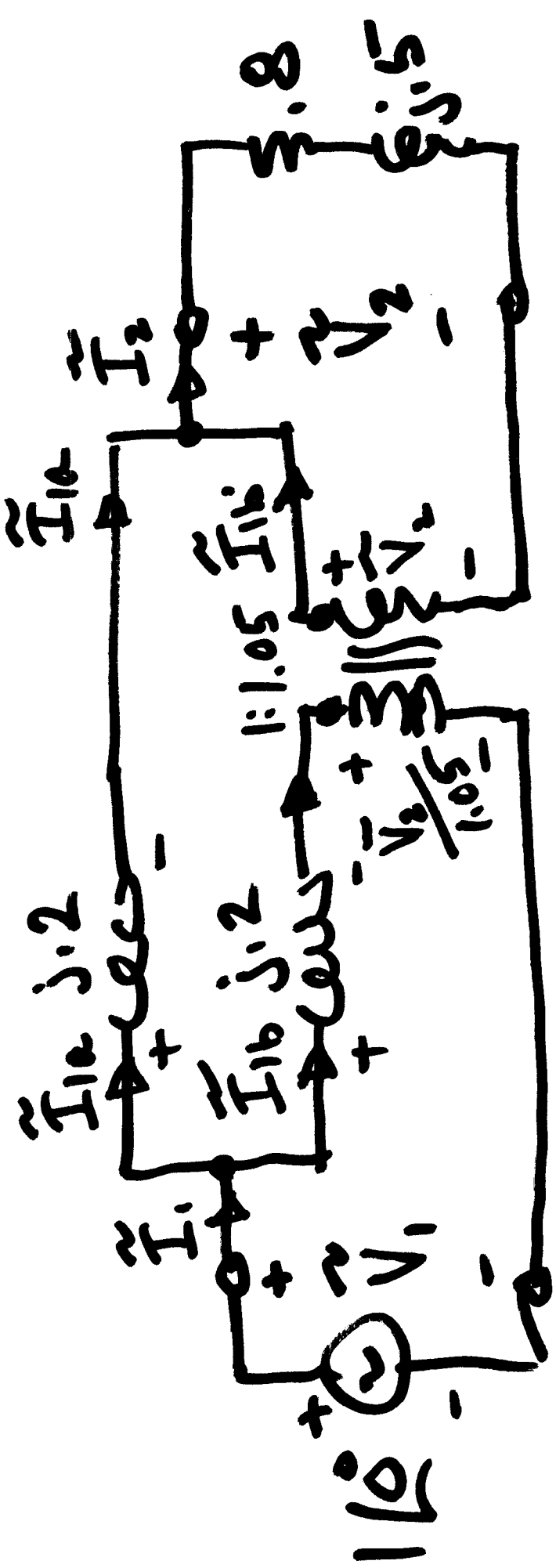- 1) ckt Theory
- 2) [Y] method
- 3) Circulating current method.




$$\tilde{I}_1 = \tilde{I}_{1a} + \tilde{I}_{1b}$$

$$\tilde{I}_2 = \tilde{I}_{1a} + \tilde{I}_{1b} =$$

$$\frac{\tilde{V}_1 - \tilde{V}_2}{j \cdot 2} + \frac{(\tilde{V}_1 - \tilde{V}_2 / 1.05) \left(\frac{1}{1.05} \right)}{j \cdot 2} = \frac{\tilde{V}_2}{8 + j1.5}$$

$$\Rightarrow \underline{\underline{\tilde{V}_2 = 9.63 \angle -5.1^\circ \text{ p.u.}}}$$

$[Y]$ method:

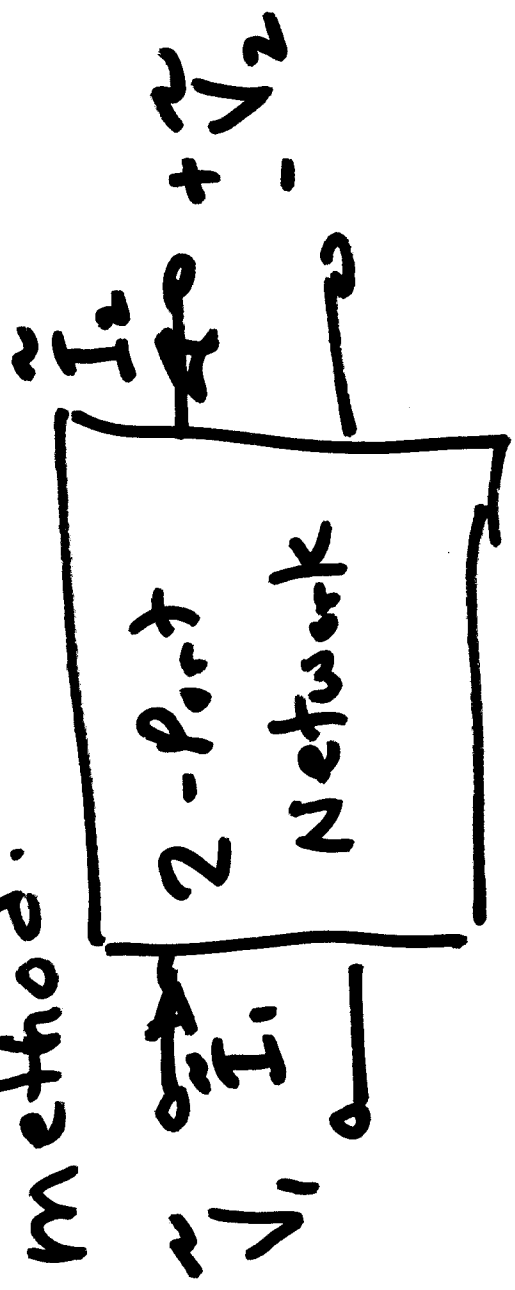

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[Y_{bus}] [V] = [I_{inj}]$$

Prob 2
(Hmwk#3)

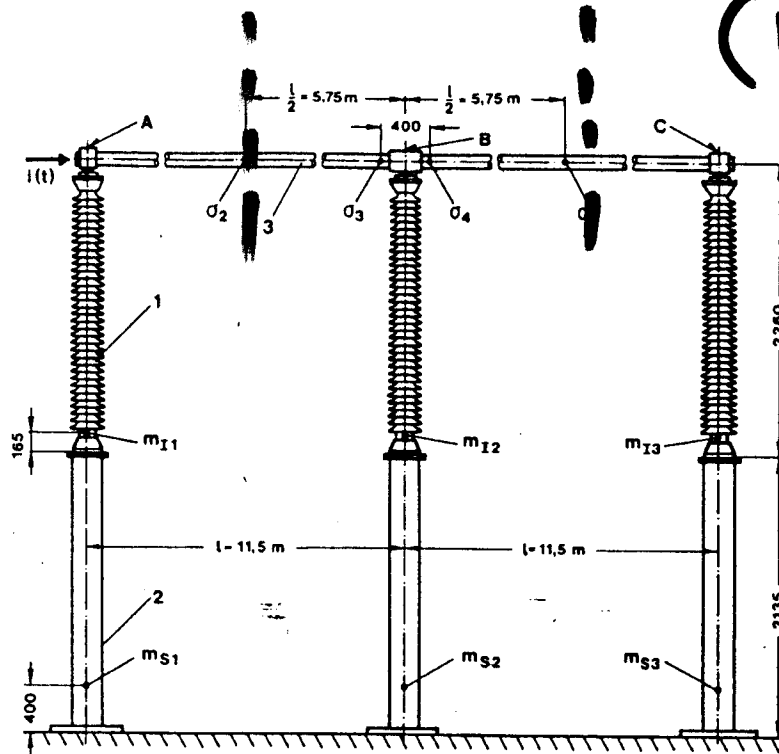


Figure F.1—CIGRE structure D (from Hosemann and Tsanakas [B14])

The structural data used in calculations is presented in Table F.1. The fault parameters are presented in Table F.2.

Table F.1—Structural data

Characteristic	Conductor	Insulator	Support
Length L	span of 11.5 m (including portion in conductor clamps)	2.10 m	2.135 m
Material	Aluminum	Porcelain	Steel
Young's modulus E	70 GPa	30.6 GPa	206 GPa
Area A	2.238E-3 m ²	36.14E-3 m ²	4.714E-3 m ²
Moment of inertia I	3.704E-6 m ⁴	76.08E-6 m ⁴	26.83E-6 m ⁴
Mass	6.04 kg/m	180 kg	36.8 kg/m

NOTE 1—In the finite-element model, the insulator length was extended to 2.26 m in order to reach the midconductor position.

NOTE 2—For the insulator and support, the moment of inertia used was obtained from measurements on equivalent spring stiffness ($3EI/L^3$) as provided in Hosemann and Tsanakas [B14]; this is why in Table F.1 the values given do not necessarily correspond to the actual dimensions.

NOTE 3—The bending stiffness for the insulator is assumed constant along its length to correspond to an equivalent beam of constant section although its shape is conical.

NOTE 4—In the finite-element model, lumped masses of 13.8 kg, 18.2 kg, and 13.8 kg have been added at the top of columns 1, 2, and 3, respectively, to account for actual clamp masses. Lumped masses of 36.8 kg have been added to the top of each steel support to account for mass of top plate.

NOTE 5—Conductor is assumed to be pinned at top of columns 1 and 3 and fixed at top of column 2.

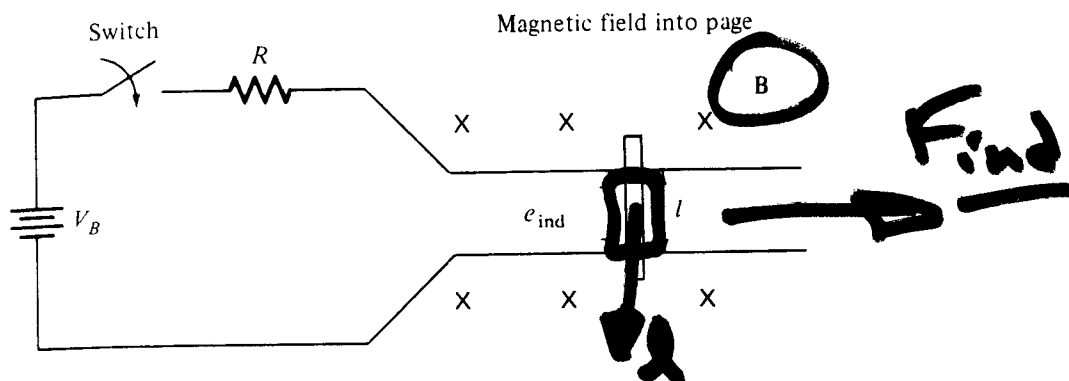


FIGURE 4-1
A linear dc machine. The magnetic field points into the page.

1. The equation for the force on a wire in the presence of a magnetic field:

$$\mathbf{F} = i(\mathbf{l} \times \mathbf{B}) \quad (1-43)$$

where \mathbf{F} = force on wire

i = current flowing in wire

\mathbf{l} = length of wire, with direction of \mathbf{l} in the direction of current flow

\mathbf{B} = magnetic flux density vector

2. The equation for the voltage induced in a wire moving in a magnetic field:

$$e_{\text{ind}} = (\mathbf{v} \times \mathbf{B}) \cdot \mathbf{l} \quad (1-45)$$

where e_{ind} = voltage induced in wire

\mathbf{v} = velocity of wire

\mathbf{B} = magnetic flux density vector

\mathbf{l} = length of conductor in magnetic field

3. Kirchhoff's voltage law for this machine. From Fig. 4-1 this law gives


$$V_B - iR - e_{\text{ind}} = 0$$

$$V_B = e_{\text{ind}} + iR \quad (4-1)$$

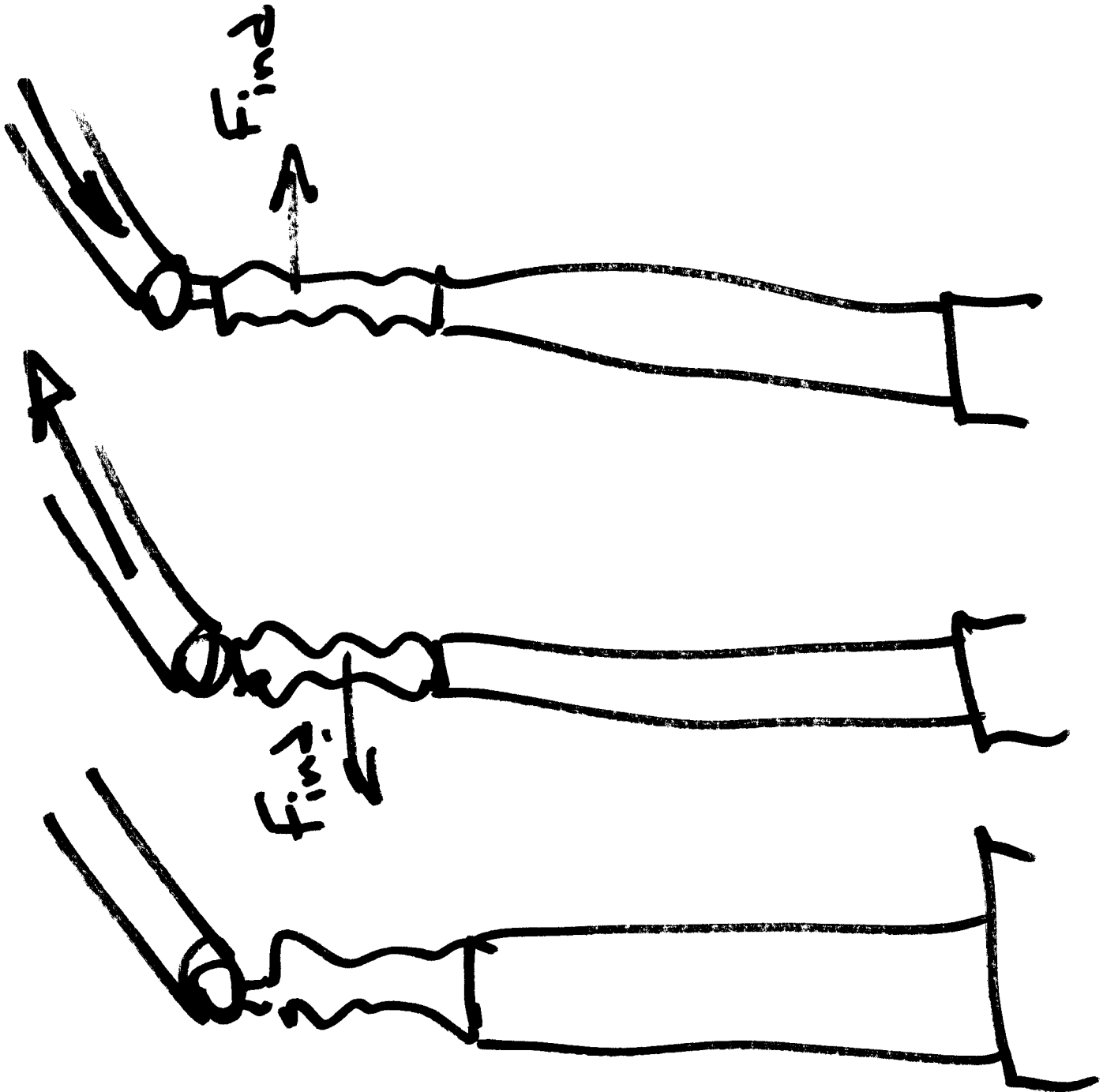4. Newton's law for the bar across the tracks:

$$F_{\text{net}} = ma \quad (1-7)$$

The fundamental behavior of this simple dc machine will now be explored by using these four equations as tools.



The flow of high levels of current generates forces on the current carrying conductors. The basic physical law is expressed with the *Biot-Savart* equation as below, which is explained with the aid of Figure 19. The figure shows two segments of conductors of lengths d_1 and d_2 , respectively and carrying electric current i_1 and i_2 , respectively. The force that will act on each one of these two segments is as follows:

$$F(t) = \frac{\mu}{4\pi r^2} i_1(t) i_2(t) [d_1 \otimes (u_r \otimes d_2)] \quad (13)$$

where

- μ is the magnetic permeability equal to $4\pi \times 10^{-7}$ V-s/(A-m)
- r is the distance between the two conductor segments
- u_r is the unit directional vector in the direction r
- d_1 is a vector of length d_1 in the direction of the current flow in conductor segment 1
- d_2 is a vector of length d_2 in the direction of the current flow in conductor segment 2

NOTE—The symbol \otimes is the vectorial cross product.

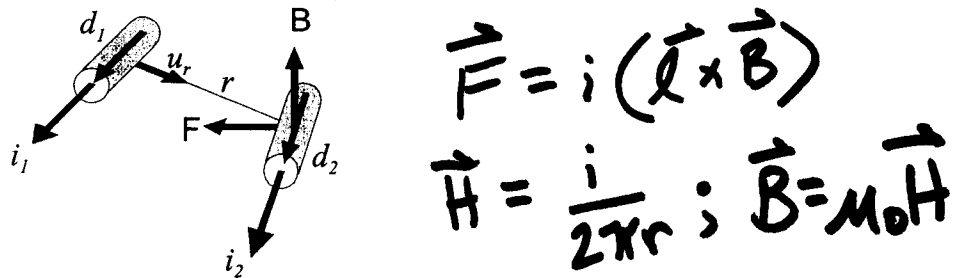


Figure 19—Illustration of two conductor segments carrying electric current

In the case of two parallel conductor segments, the cross products simply become the product of the conductor segment lengths and the force is along the line between the two segment centers, either attracting the two conductor segments or repelling them depending on the direction of the current.

This physical law is applicable to rigid bus structures as well as flexible bus structures. In the case of a rigid bus, the geometry of the bus remains practically invariant as the displacements tend to be very small. In the case of a flexible bus, the geometry of the bus varies as the forces from the fault current move the conductors around. As the distances between conductors change, so do the forces from the currents.

11.3.2 Maximum fault condition parameters

In the design process, one must consider the worst possible scenario. In terms of forces from fault currents, the fault initiation instance with respect to the source waveform is very important. Depending on the type of fault considered (phase to phase or three phased), appropriate electrical parameters need to be fixed in numerical calculations as to generate maximum fault conditions for design. The voltage angle at the initiation of fault is random in nature and should thus be fixed to:

- a) 0 for phase-to-phase fault for any conductor geometry