
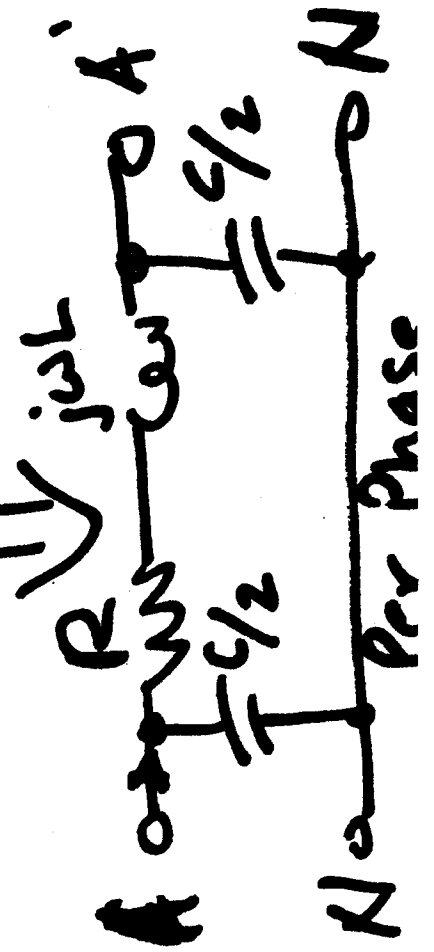


## Topics for Today:


- Announcements - T-Line Hmwk due 9am Monday
- **ATP program: remote desktop to "remote.mtu.edu"**
- Office: EERC 614. Phone: 906.487.2857
- Recommended problems from Ch.6, solutions posted
- Next: Transmission Lines as 2-port networks
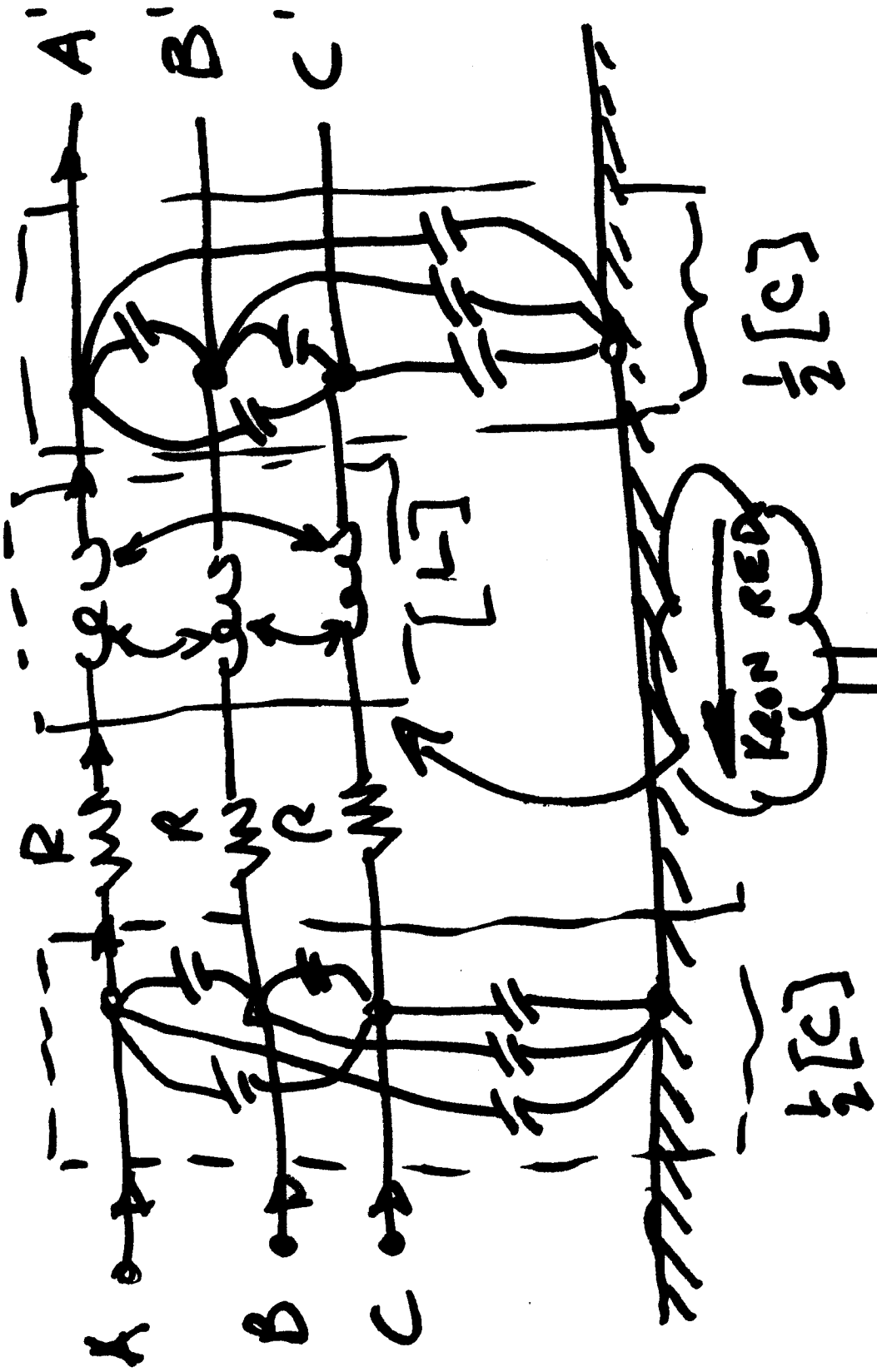
## Chapter 6 - Shunt Capacitance Transmission Lines

- Capacitance of 3-phase overhead lines, [C] matrix.
- Double-circuit lines
- Using the T-Line models
  - Short Transmission Lines - up to 50 miles (80 km)
  - Voltage Regulation, phasor diagrams
  - Per-phase impedance diagrams (positive seq only)
  - Medium-Length Lines (50 - 150 miles)
  - ABCD parameters for Medium-lines, power flow (L18).
  - Long Lines - more than 150 miles (240 km)
  - Derivation of long-line equations, meaning of equations
  - Characteristic Impedance  $Z_C$
  - Propagation Constant  $\gamma = \alpha + j\beta$



↙ Nodal inductance matrix

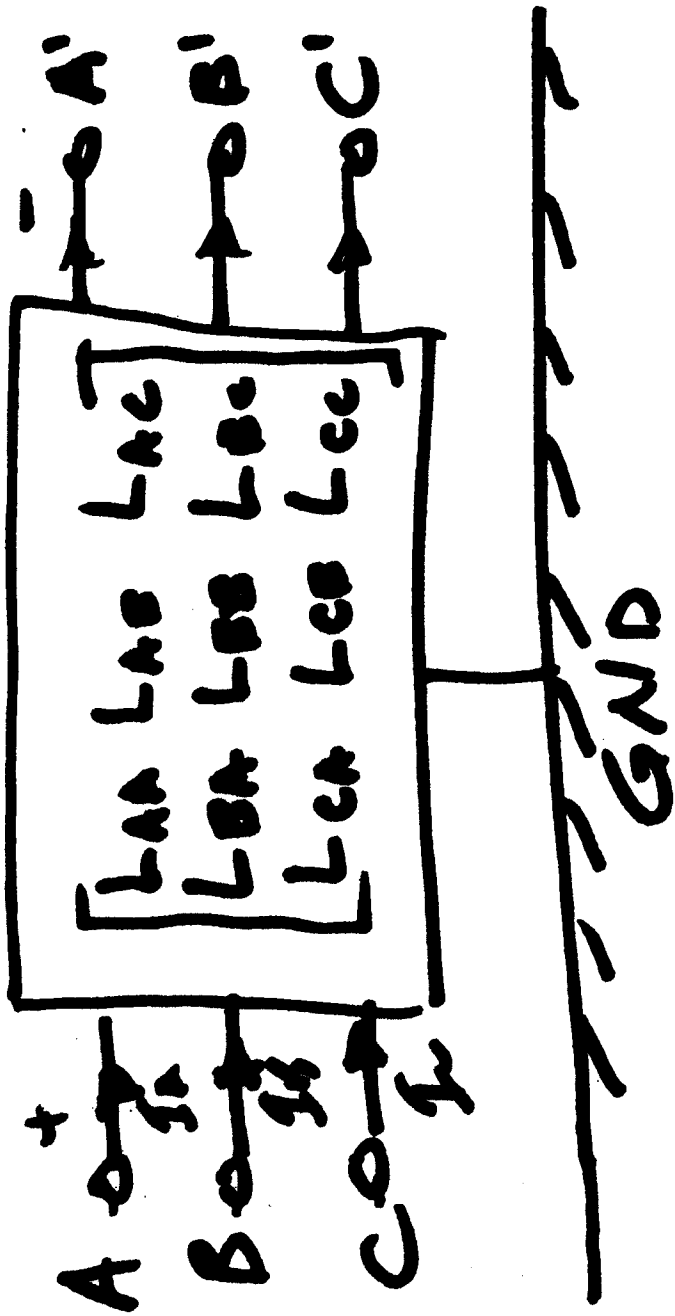

$$\begin{bmatrix} V_{A-A'} \\ V_{B-B'} \\ V_{C-C'} \end{bmatrix} = j\omega \begin{bmatrix} L \\ L \\ L \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix}$$

$$\begin{bmatrix} V_A \cdot A' \\ V_B \cdot B' \\ V_C \cdot C' \end{bmatrix}$$


 $j\omega$  $=$ 

$$\begin{bmatrix} L_{AA} & L_{AB} & L_{AC} \\ L_{BA} & L_{BB} & L_{BC} \\ L_{CA} & L_{CB} & L_{CC} \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix}$$

$$+ \begin{bmatrix} R_{AA} & 0 & 0 \\ 0 & R_{BB} & 0 \\ 0 & 0 & R_{CC} \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix}$$

# Capacitance

$$C \propto \ln \frac{r}{D}$$

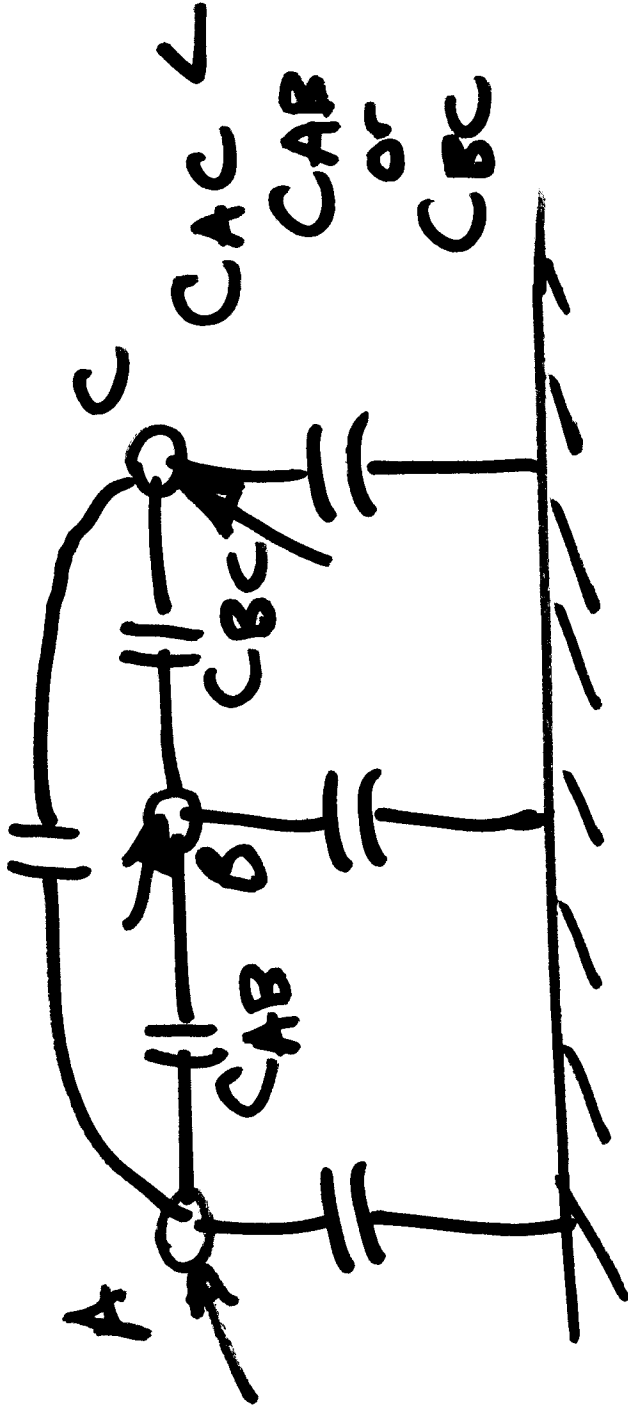

$$[C] = \omega [C]$$

$$[B] = j\omega [C]$$

$$[Y] = j\omega [B]$$

Full-line


vs.

Half-line (Pi-Equin)

Line Charging Current

Cy Effects:

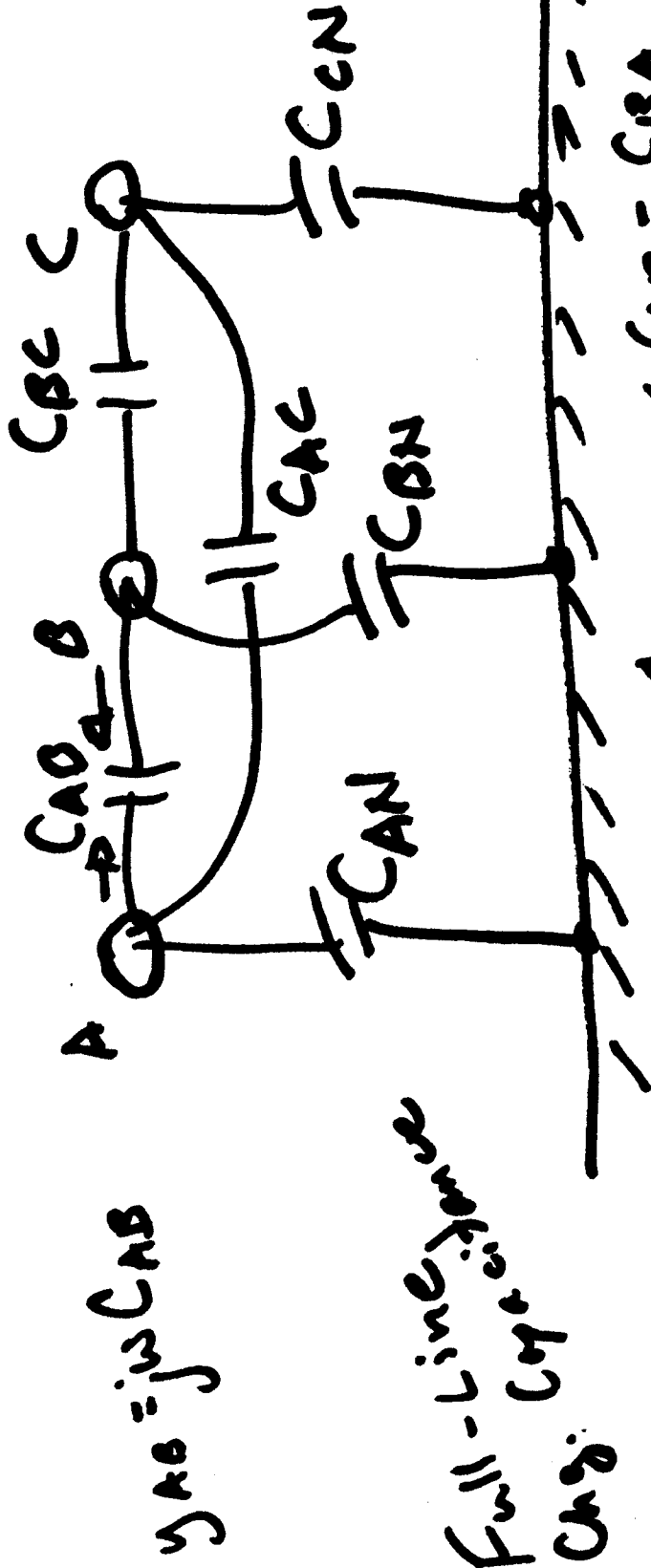Note:  $(C_{AC} \leftarrow C_{AB}, C_{BC})$



$$C_{AB} = C_{BA}$$


$$-C_{AB} - C_{AC}$$

$$[C] =$$

$$\begin{bmatrix} C_{AB} + C_{AC} + C_{AN} & & \\ & -C_{AB} - C_{AC} & \\ & & -C_{BA} - C_{CB} - C_{CN} \end{bmatrix}$$


$$-C_{BA} \quad C_{AB} + C_{BC} + C_{BN} \quad -C_{BC}$$

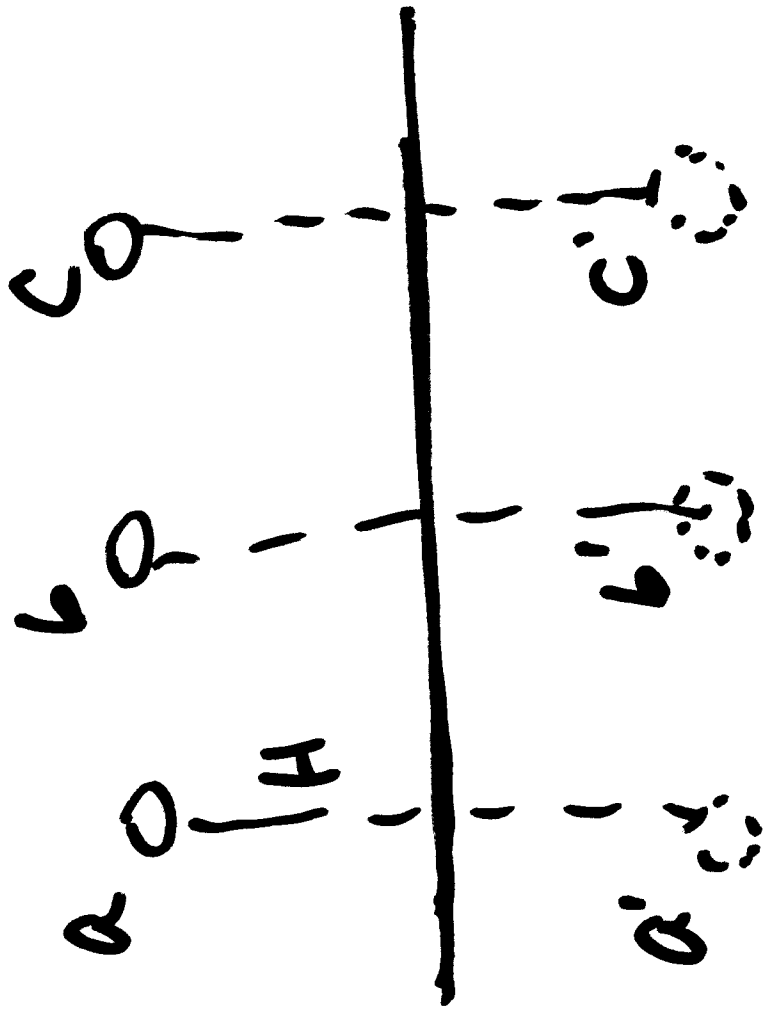
$$-C_{CA} \quad -C_{CB} \quad C_{BC} + C_{AC} + C_{CN}$$



$$C_{aa'} = \frac{\pi \epsilon_0 F/m}{\ln \frac{2H}{r}}$$


method of images.  $\Rightarrow [C]$

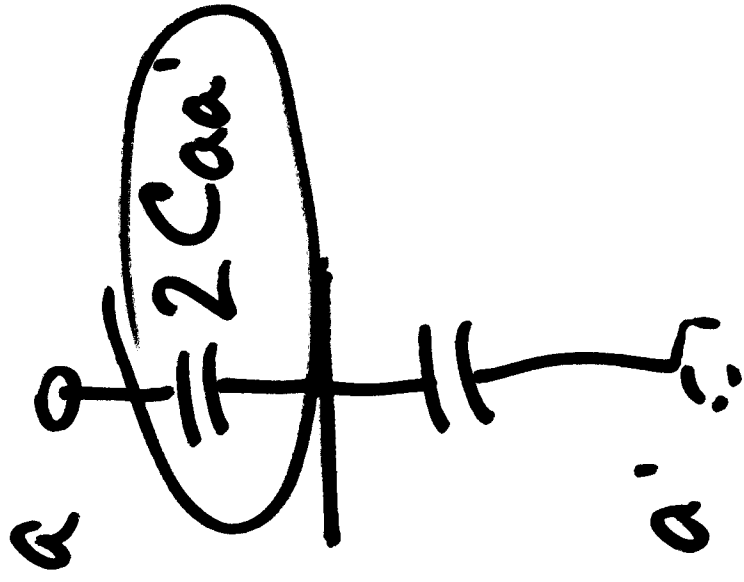

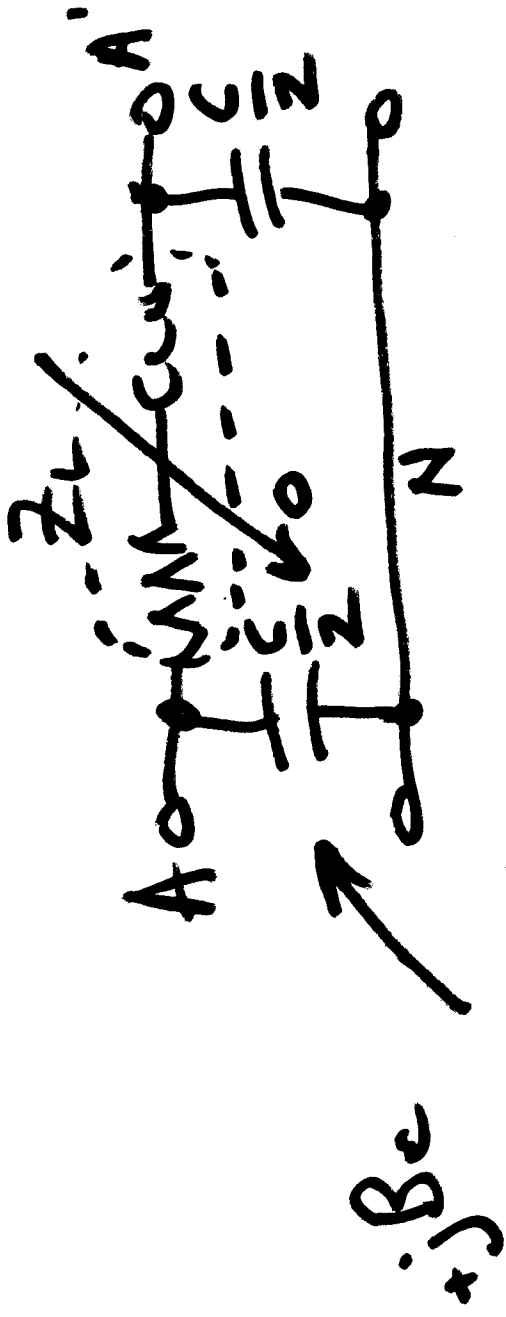


$$Z = \frac{1}{j\omega C/2} = -jx_C$$

$$|-jx_C| \gg |Z_L|$$

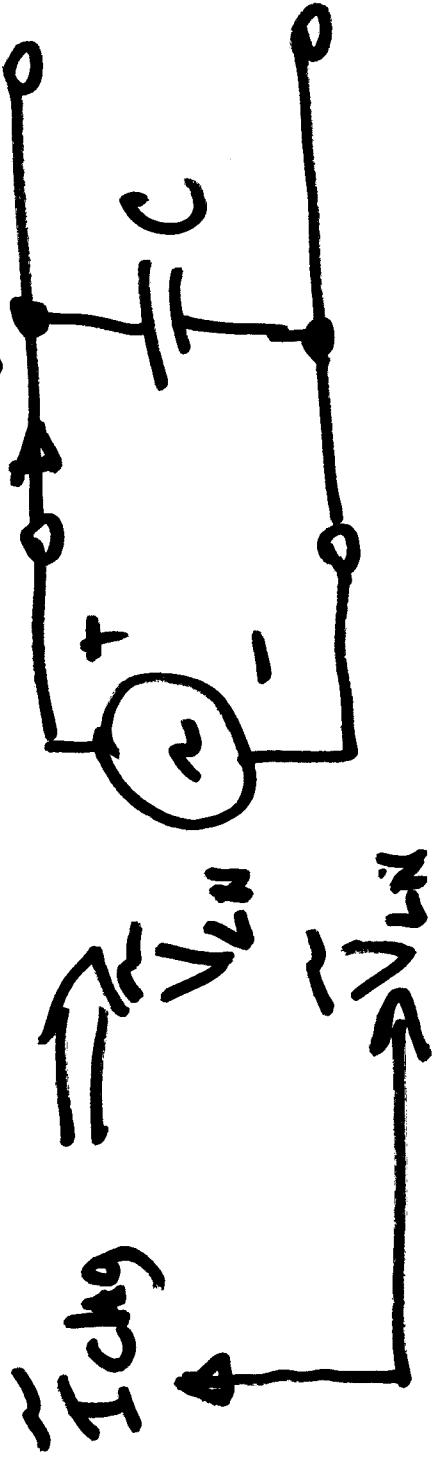



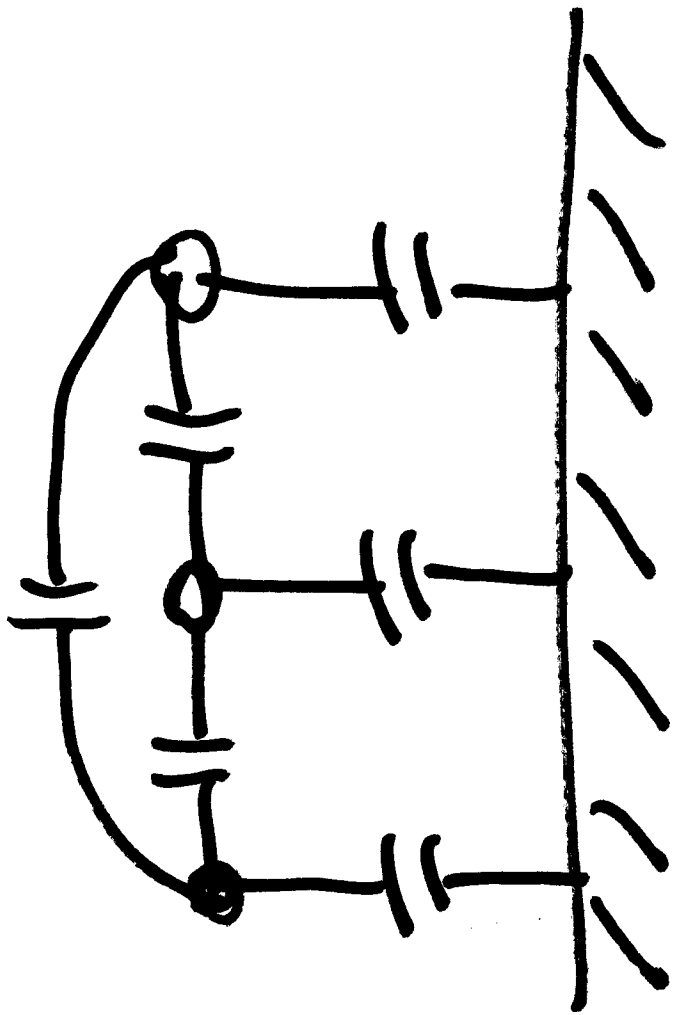

$$\frac{7P}{(7)2P} = C(7)?$$

$$V = 0$$

$$V = \frac{2}{(7)?} +$$

$$Z = \frac{1}{j\omega C}$$




Apply Bal. 3 $\phi$  Source Voltages.

$$C \propto \ln \frac{r}{D}$$

$I_b$  is larger than  $I_a$  or  $I_c$

$$L \propto \ln \frac{D}{r} \quad |I_a| = |I_c| \quad \dots \quad 120^\circ \text{ phase shift}$$

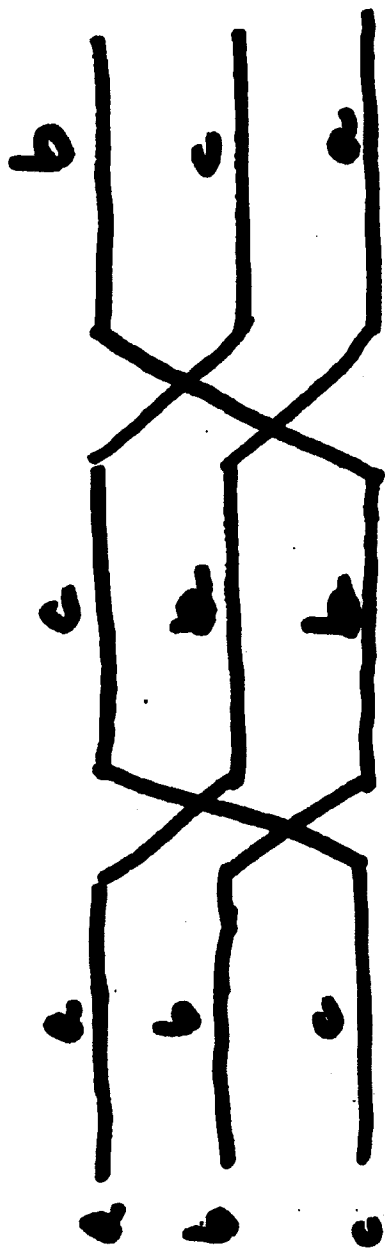Solution: Transposition, then all  $I_{avg}$  are equal.





$D =$  phase spacing

$r =$  radius

$$C \propto \ln \frac{r}{D} \Rightarrow \{C_{AB} \text{ or } C_{BC}\} > C_{AC}$$

$$L \propto \ln \frac{D}{r}$$

# Energize Line:

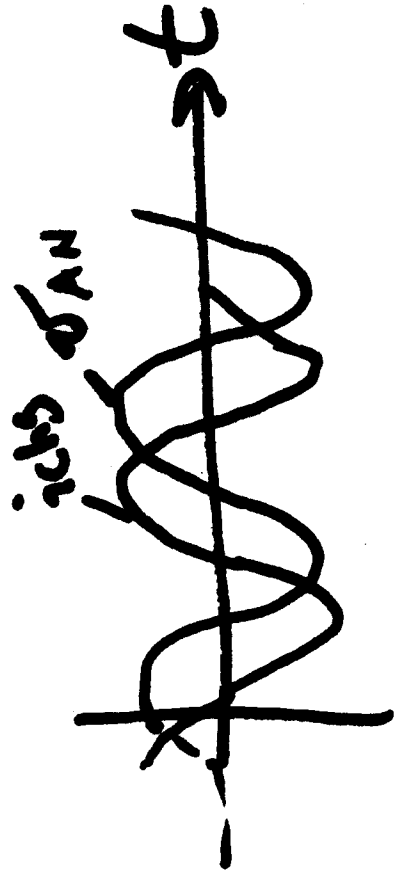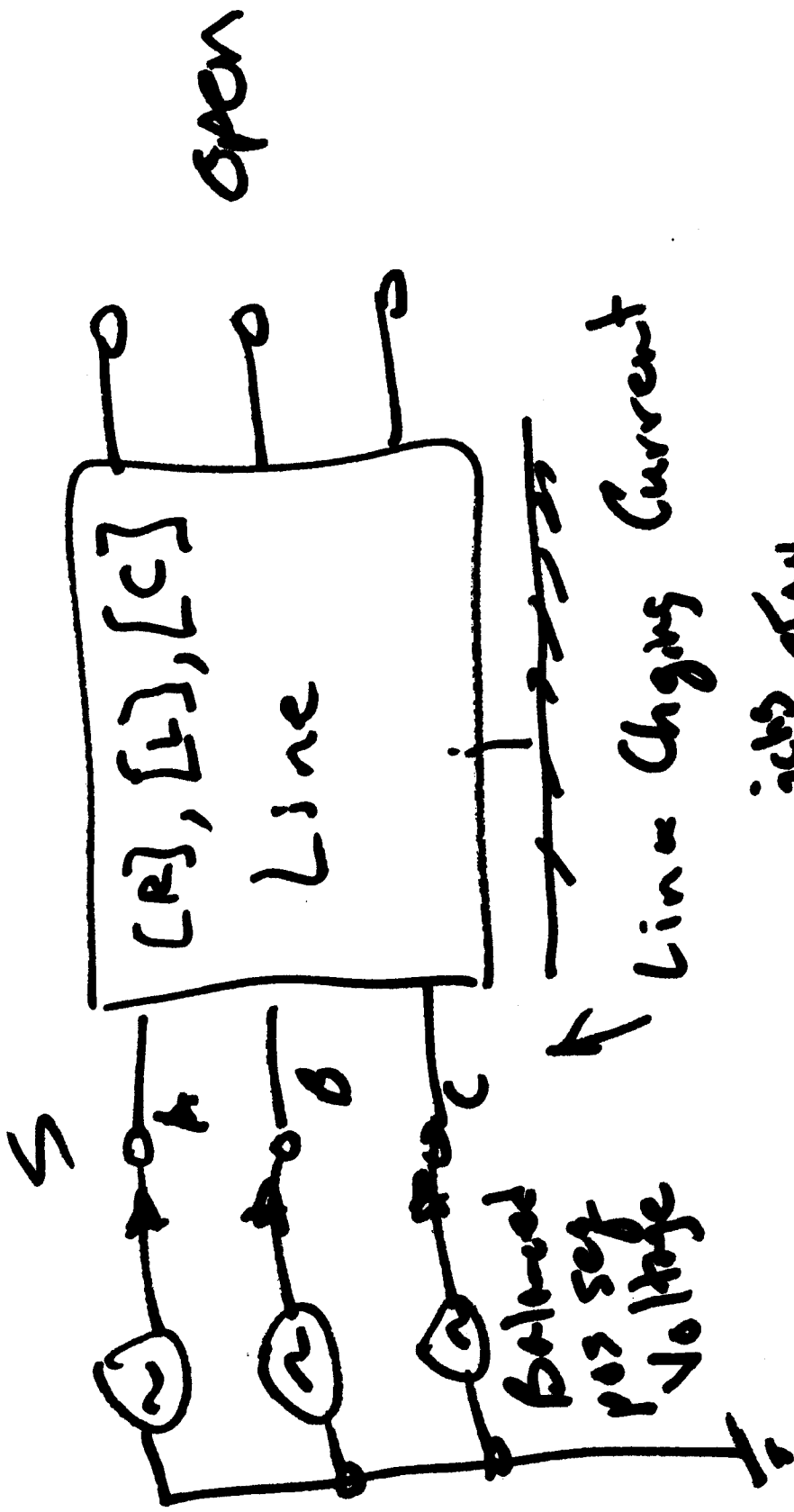


$$[Z_P] = \begin{bmatrix} Z_{AA} & Z_{AB} & Z_{AC} \\ Z_{BA} & Z_{BB} & Z_{BC} \\ Z_{CA} & Z_{CB} & Z_{CC} \end{bmatrix}$$

$$[Z_S] = \bar{A}' [Z_P] A$$


$$[Z_P] = A [Z_S] \bar{A}'$$

$$\Rightarrow [Z_S] = \begin{bmatrix} Z_{00} & & \\ & Z_{10} & \\ & & Z_{20} \end{bmatrix}$$
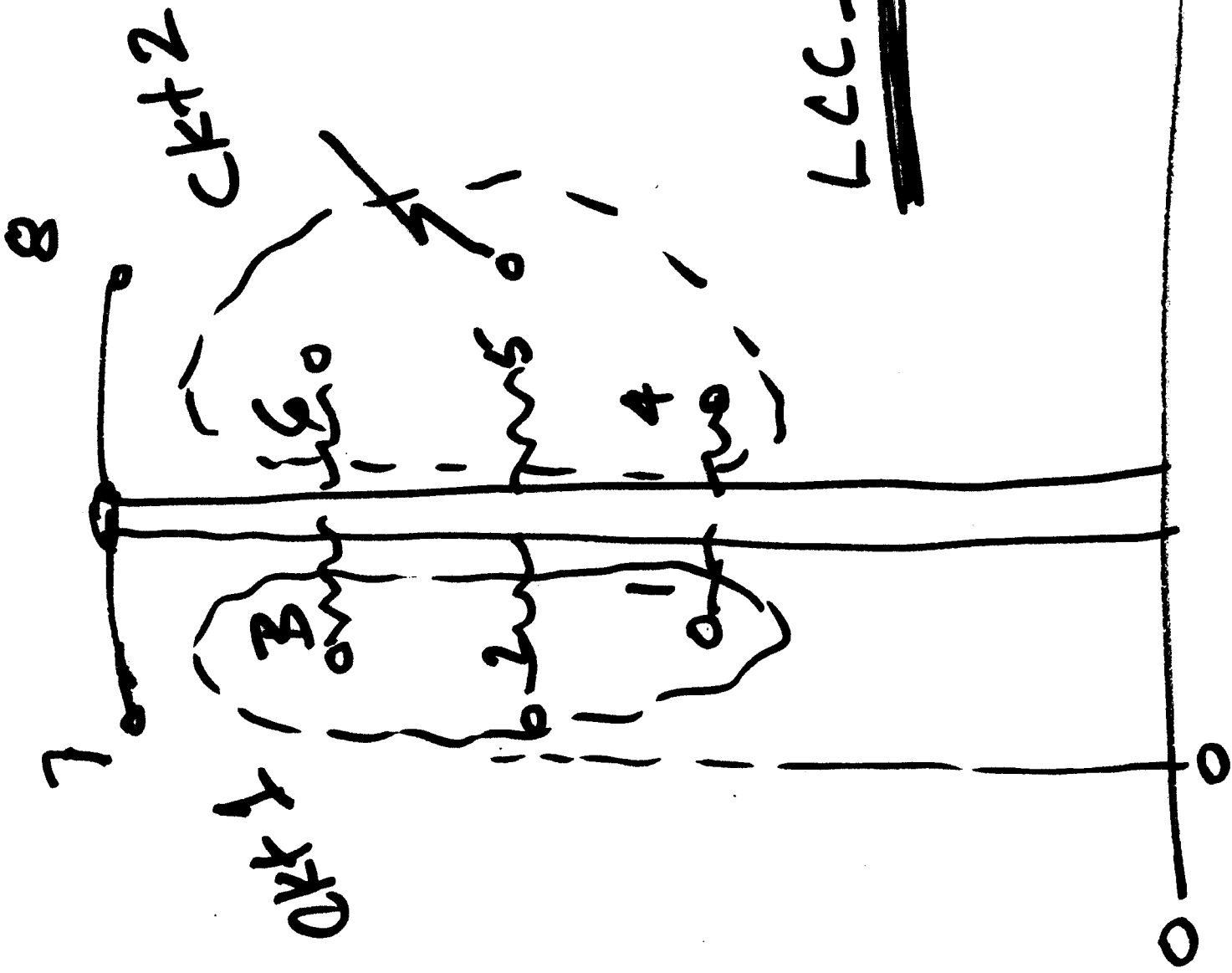
$$\begin{bmatrix} Z_{01} & Z_{02} \\ Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$



LCC-6.alc

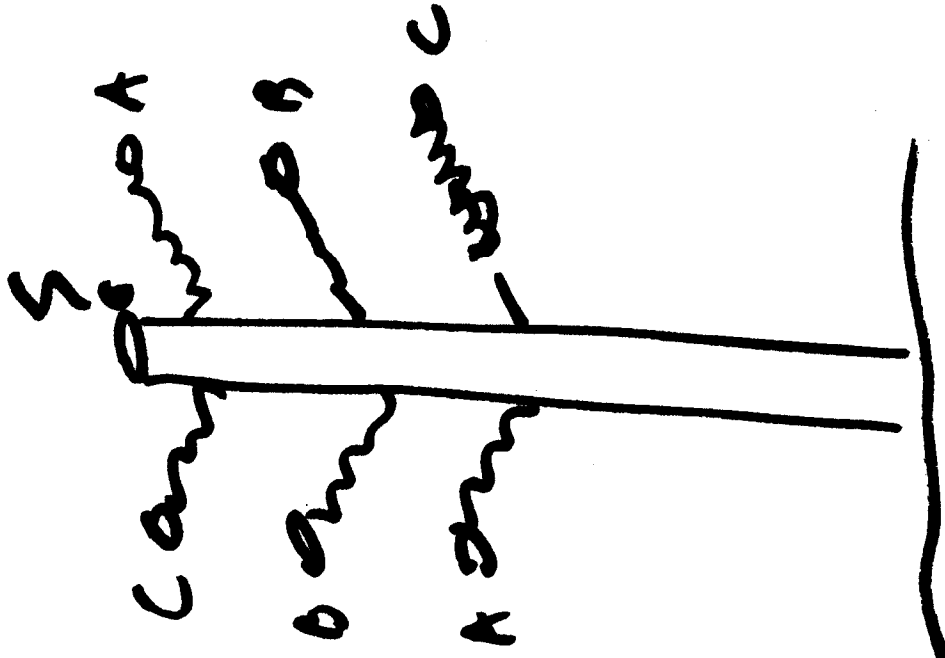

$$6 \times 6 \begin{bmatrix} C_{AA} & C_{AB} & C_{AC} & C_{BA} & C_{BB} & C_{BC} \\ C_{BA} & C_{BB} & C_{BC} & C_{CA} & C_{CB} & C_{CC} \\ C_{CA} & C_{CB} & C_{CC} & C_{AA} & C_{AB} & C_{AC} \\ C_{AC} & C_{AB} & C_{AC} & C_{BA} & C_{BB} & C_{BC} \\ C_{BA} & C_{BB} & C_{BC} & C_{CA} & C_{CB} & C_{CC} \\ C_{CA} & C_{CB} & C_{CC} & C_{AA} & C_{AB} & C_{AC} \end{bmatrix}$$

Double-Circuit Lines

$$[C] = \begin{bmatrix} \textcircled{x} & x & x \\ x & \textcircled{x} & x \\ x & x & \textcircled{x} \end{bmatrix}$$

$[C]$

$Z_0$

$Z_1$

$Z_2$

Fully Decoupled:

$$[Z_s] = \begin{bmatrix} \textcircled{Z_{00}} & 0 & 0 \\ 0 & \textcircled{Z_{11}} & 0 \\ 0 & 0 & \textcircled{Z_{22}} \end{bmatrix}$$



$[Z_s]$

only if  $Z_A, Z_B, Z_C$  are equal (Balanced)



# Series Impedance

$R + j\omega L$

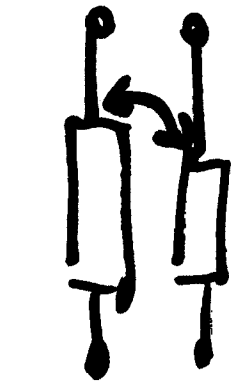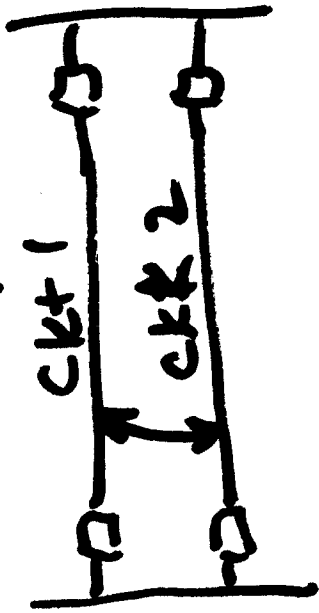


0




pos




neg

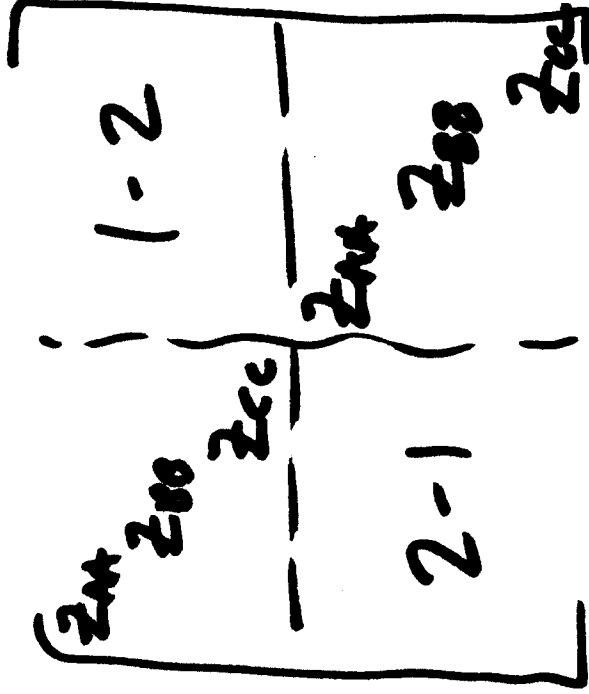


Phase transformation to seq

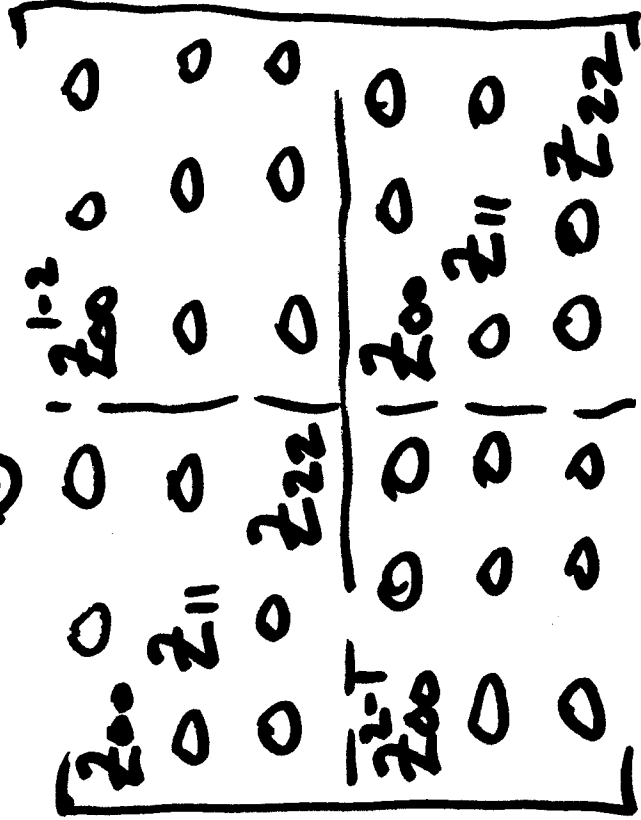


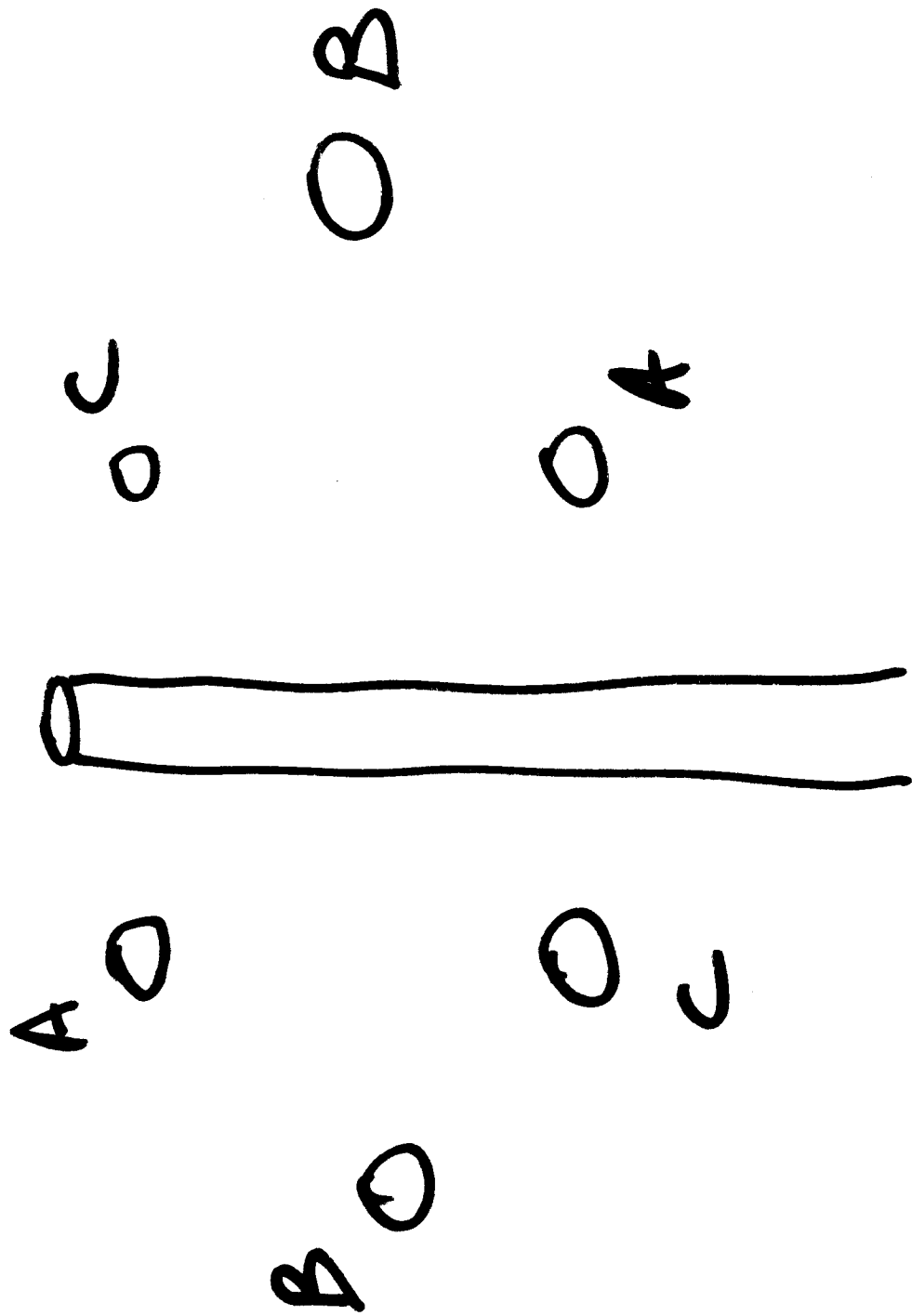



Transposition:
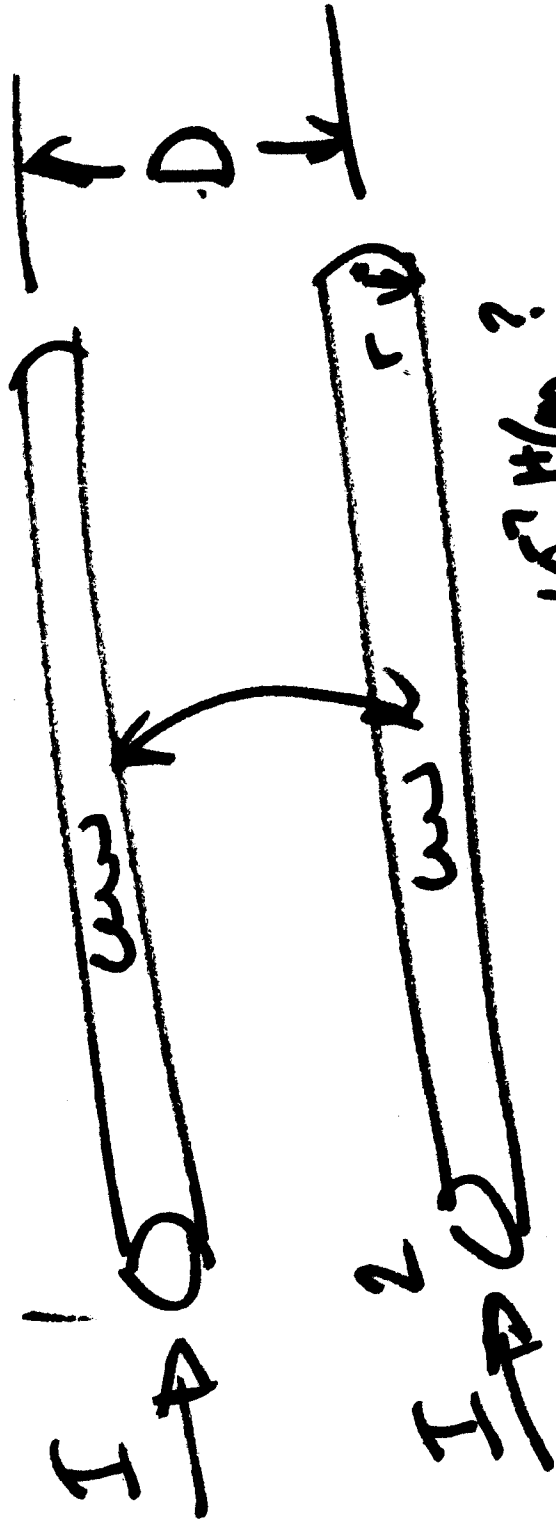
$$\underline{\underline{[Z_P] \Rightarrow [Z_S]}}$$


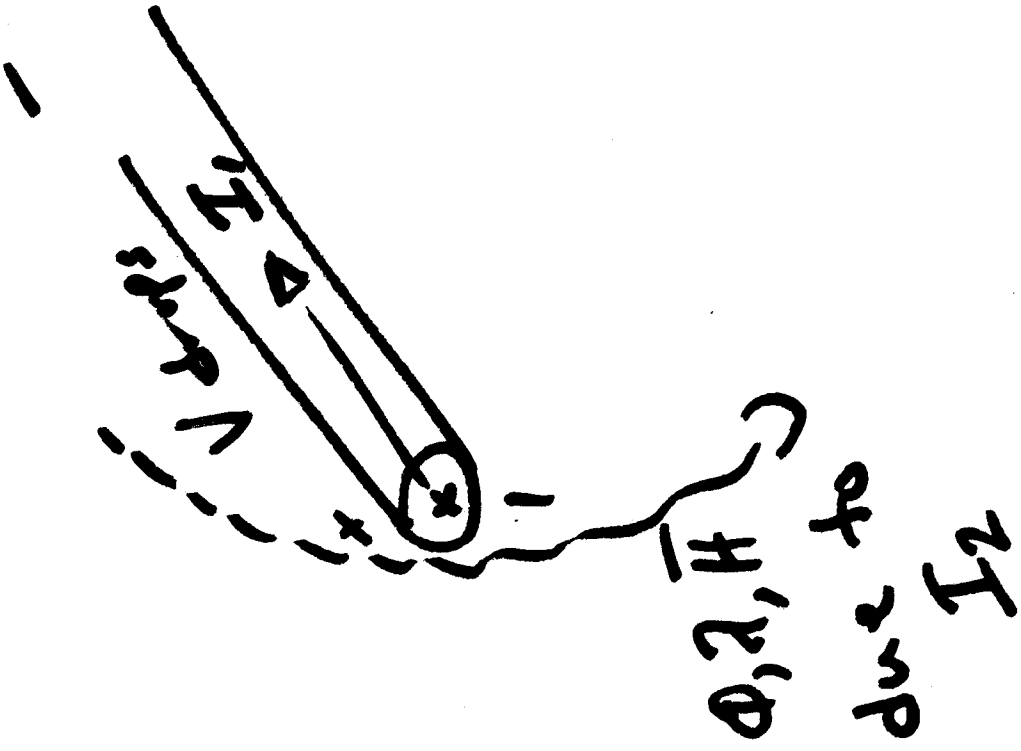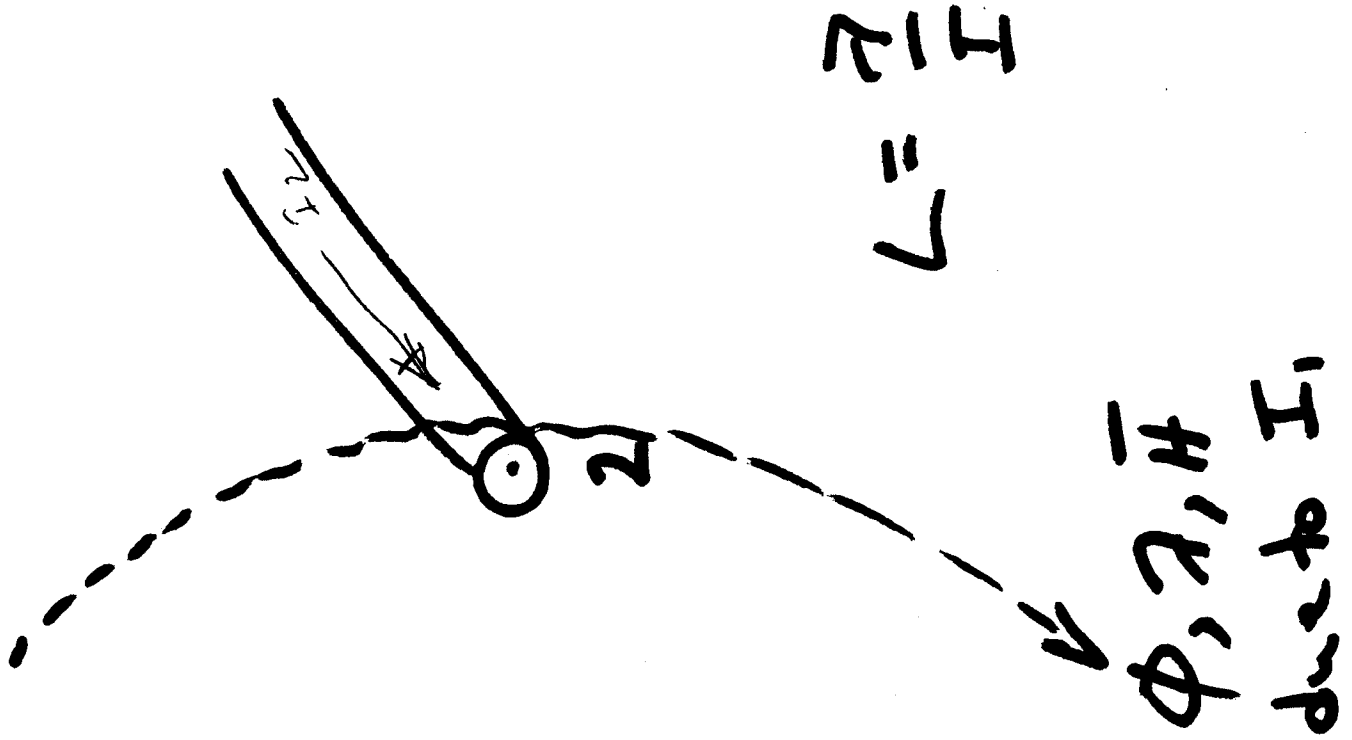
$$\begin{aligned}
 L_i &= L_{int} + L_{mut} \\
 &= 2 \times 10^{-7} \ln \frac{D}{r_1}, \text{ or} \\
 &= 2 \times 10^{-7} \ln \frac{D}{GMR}
 \end{aligned}$$



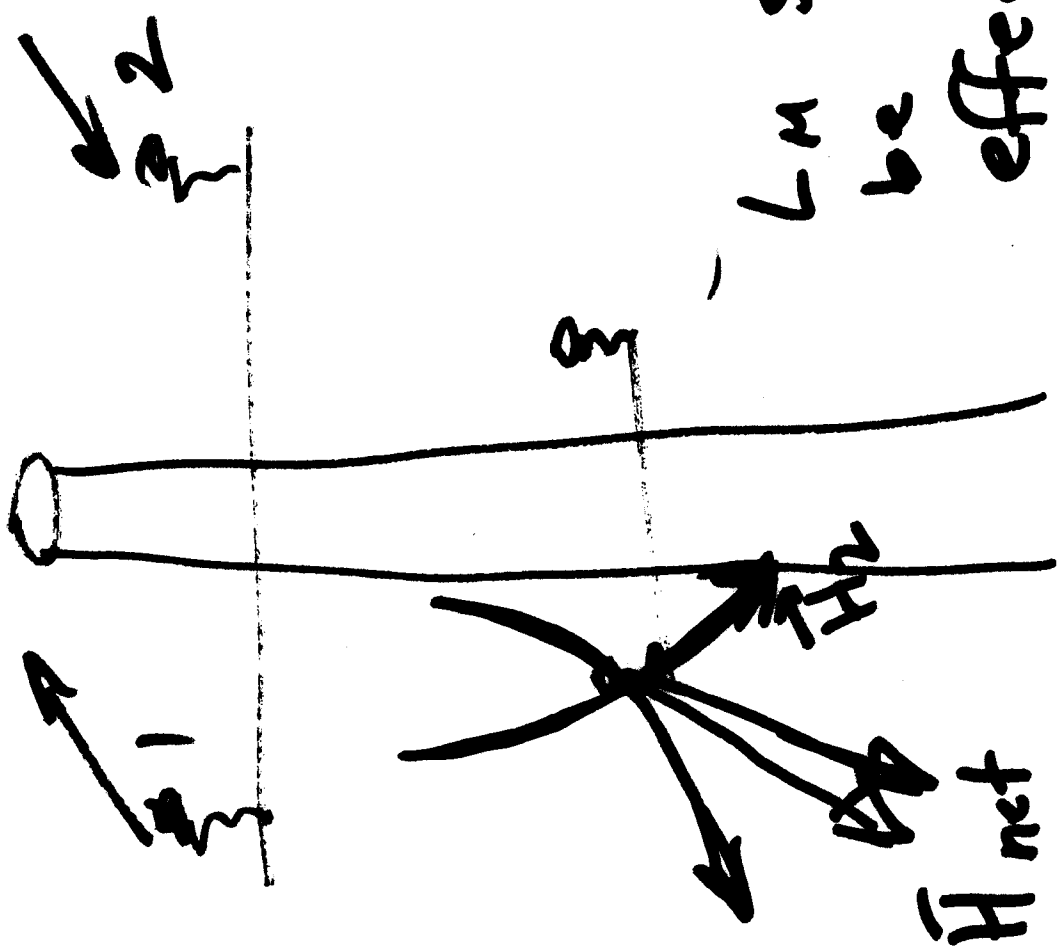

$EMF_1$   
 $EMF_2$   
 $H_1$

LM should ideally  
 be zero, or  
 effects of  $H$   
 should cancel.

