

Topics for Today:

- Announcements
 - ATP availability is being confirmed. V7.0 is being requested.
 - Term project detailed outline due Mon Oct 23rd, extension given
 - Office: EERC 614. Phone: 906.487.2857
 - Book exercises from Ch.6,7 solutions posted - required to go thru
 - Upcoming hmwks: Transmission Lines as 2-port networks. Matlab.

Chapter 6 - Shunt Capacitance Transmission Lines

- Using the T-Line models
 - Short Transmission Lines - up to 50 miles (80 km)
 - Voltage Regulation, phasor diagrams
 - Per-phase impedance diagrams (positive seq only)
 - Medium-Length Lines (50 - 150 miles)
 - ABCD parameters for Medium-lines, power flow
 - Long Lines - more than 150 miles (240 km)
 - Derivation of long-line equations, meaning of equations
 - Characteristic Impedance Z_C
 - Propagation Constant $\gamma = \alpha + j\beta$
 - Surge-Impedance Loading (SIL)
 - Wavelength, velocity, Traveling waves, reflections

T-Line Performance

Sagging

S - heat/amp/losses $\Rightarrow \pi$

M - Voltage Regulation, VR, 0.95 - 1.05 pu.

L - Stability - EEG210

MYL - Power Flow limits



- ...

- EEG220 - insulation / over-voltage


Ex: $1 \rightarrow 3$ -174.88 -40.45
 $3 \rightarrow 1$ 179.54 49.24

$\Delta P = 4.66$ $\Delta Q = 8.79$

$\bar{S} = \tilde{V}_3 \tilde{I}_3^*$

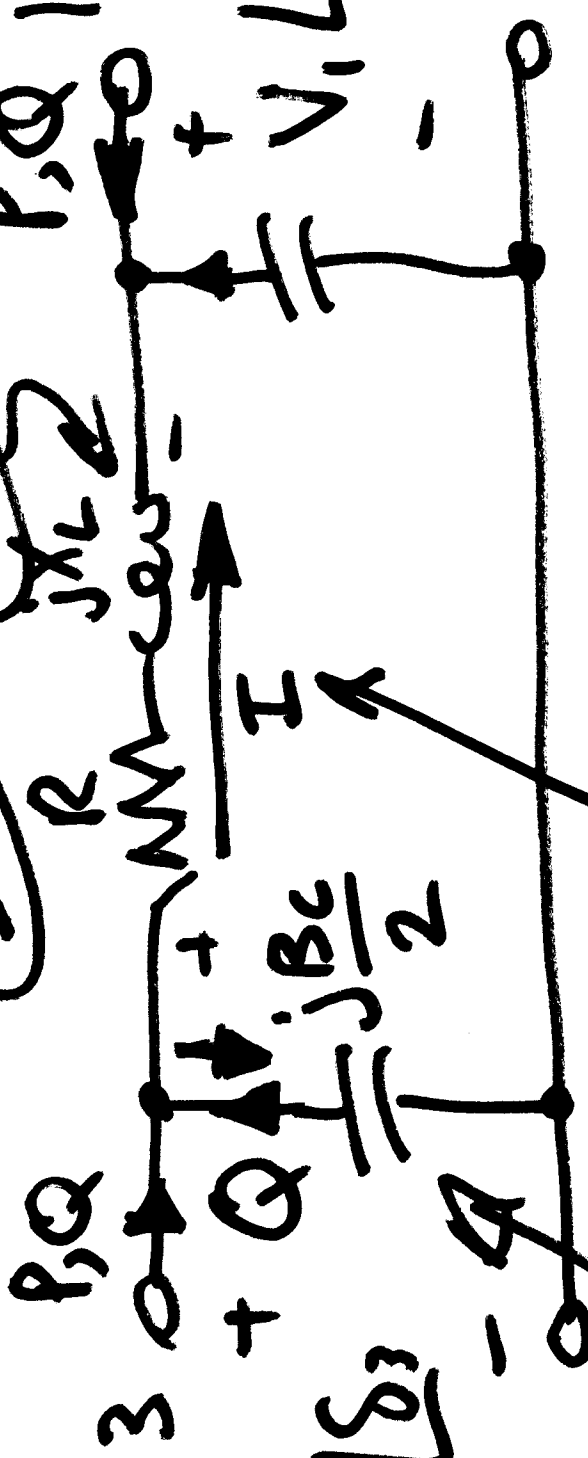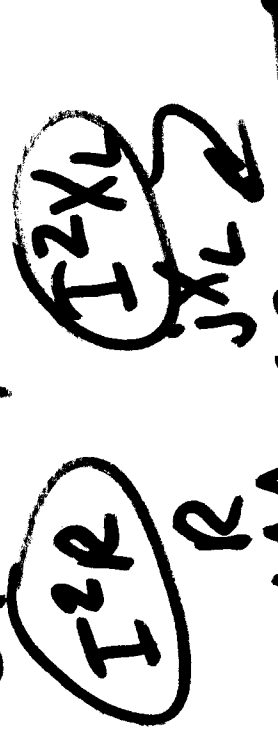

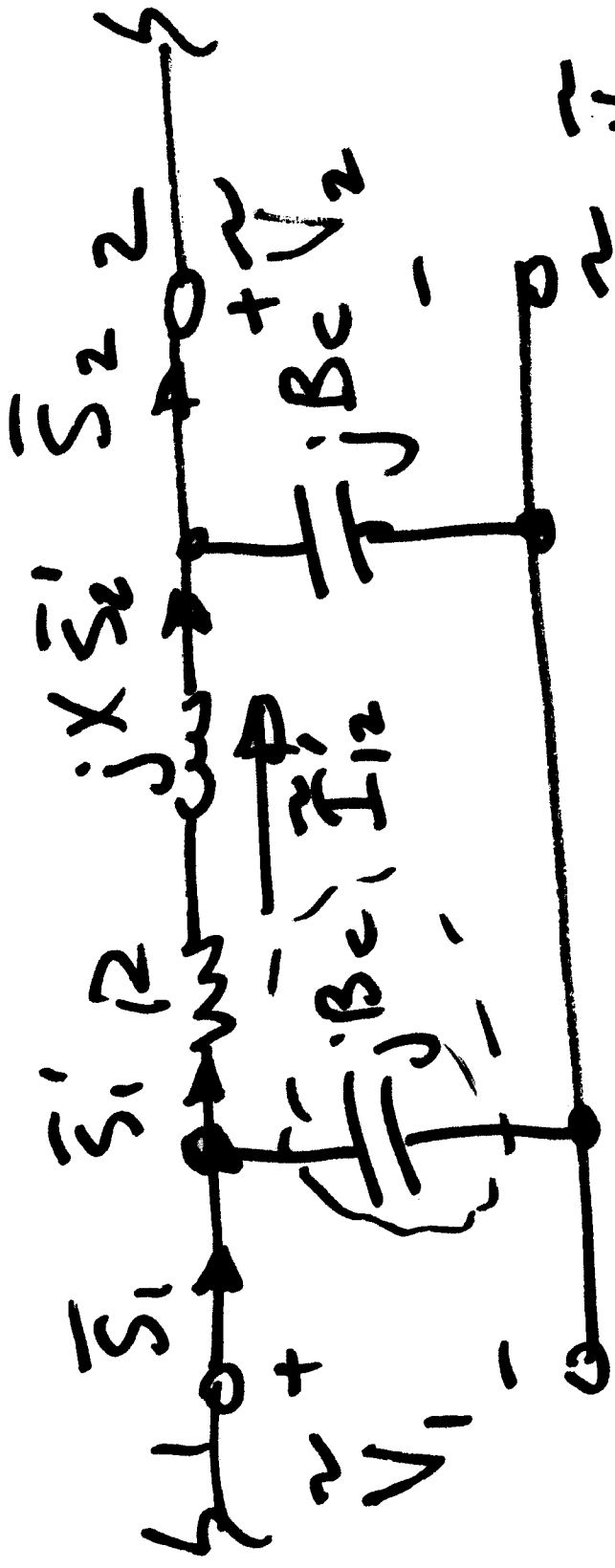$\tilde{I} = \frac{\tilde{V}_3 - \tilde{V}_1}{R + jX_L}$




$$\bar{I}_{12} = \frac{V_1 - V_2}{R + jX}$$


$$Q = V_1^2 B_c$$

$$\bar{S}_1 = \bar{S}_1 + V_1^2 B_c$$
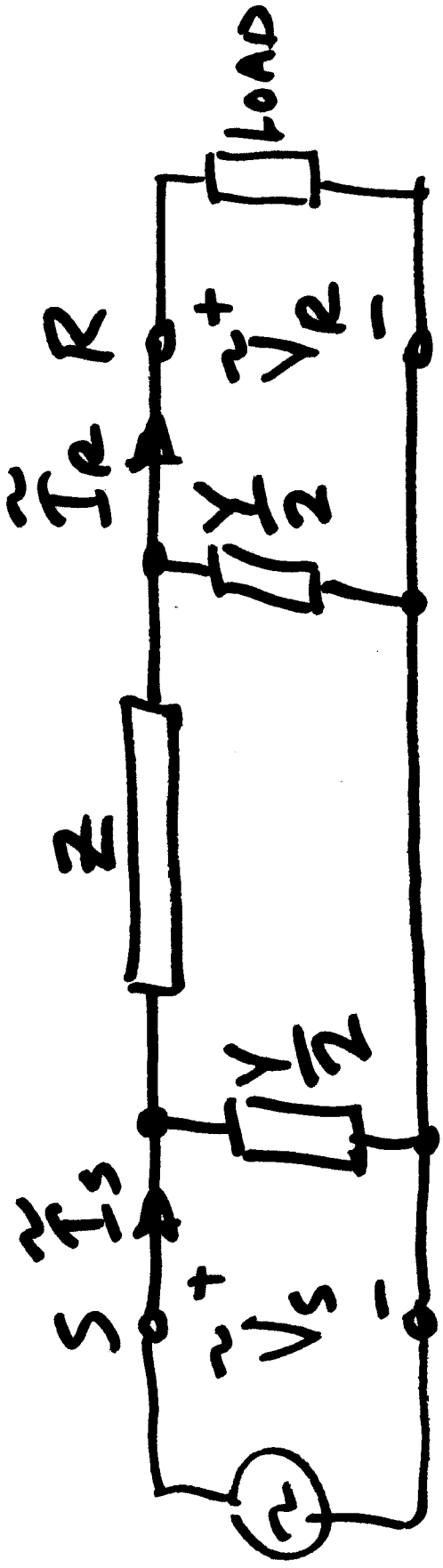
$$\begin{aligned} \bar{S}_2 &= \bar{S}_1 - P_R - Q_x \\ &= \bar{S}_1 - (\bar{I}_{12})^2 (R) - (I_{12})^2 X \end{aligned}$$



Generically...

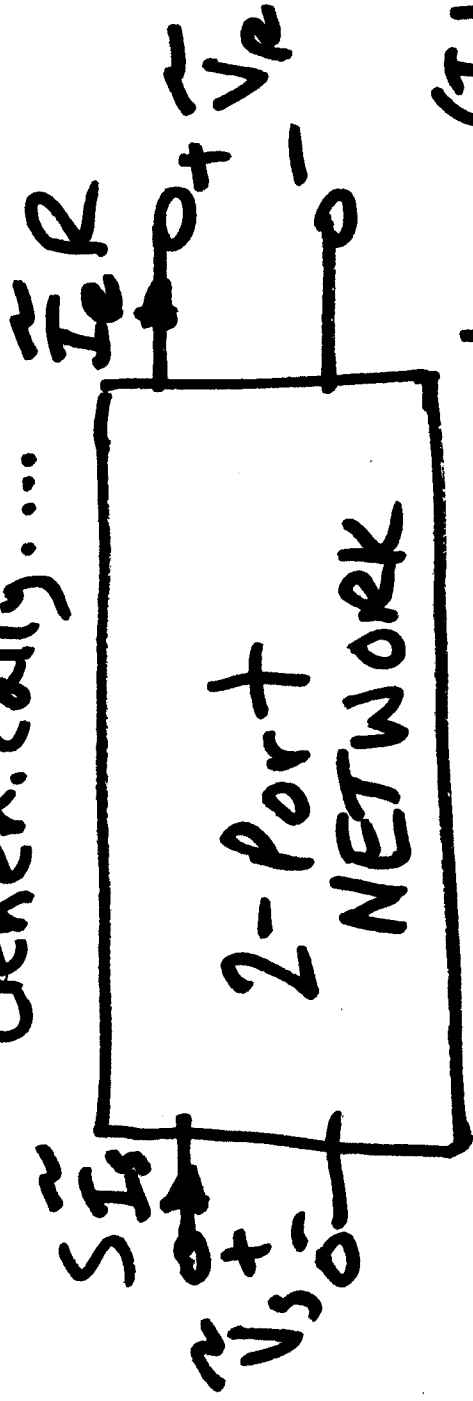

- ABCD Parameters (T-lines)
- H parameters (electronics)
- Many others.

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$$A = \frac{V_s}{V_r} \Big|_{I_r=0} \text{ (No-load)} \quad \text{(O.C. Receiving end)}$$


$$B = \frac{V_s}{I_r} \Big|_{V_r=0} \text{ (S.C.)} \quad \text{'' ''}$$

$$C = \frac{I_s}{V_r} \Big|_{I_r=0} \text{ (O.C.)} \quad \text{'' ''}$$

$$D = \frac{I_s}{I_r} \Big|_{V_r=0} \text{ (S.C.)} \quad \text{'' ''}$$

TABLE A.6
ABCD constants for various networks


Egn. 6.8, 6.9

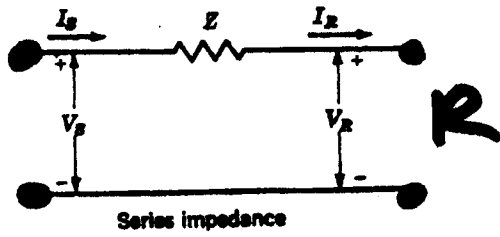

$A = 1$
 $B = Z$
 $C = 0$
 $D = 1$


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \bar{V}_R \\ \bar{I}_R \end{bmatrix} = \begin{bmatrix} \bar{V}_S \\ \bar{I}_S \end{bmatrix}$$

Series impedance

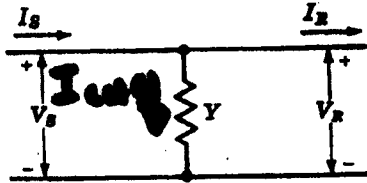


$A = 1$
 $B = 0$
 $C = Y$
 $D = 1$

Shunt admittance

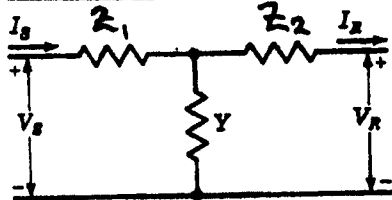


$A = 1 + YZ_1$
 $B = Z_1 + Z_2 + YZ_1Z_2$
 $C = Y$
 $D = 1 + YZ_2$

Unsymmetrical T

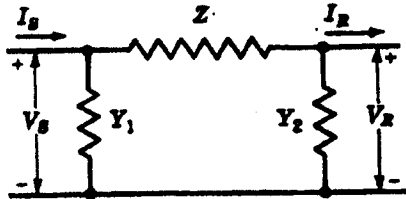


$A = 1 + Y_2Z$
 $B = Z$
 $C = Y_1 + Y_2 + ZY_1Y_2$
 $D = 1 + Y_1Z$

Unsymmetrical pi

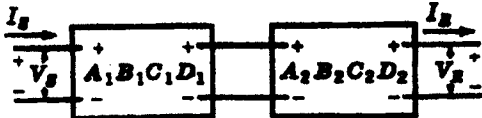

$A = A_1A_2 + B_1C_2$
 $B = A_1B_2 + B_1D_2$
 $C = A_2C_1 + C_2D_1$
 $D = B_2C_1 + D_2D_1$

Networks in cascade

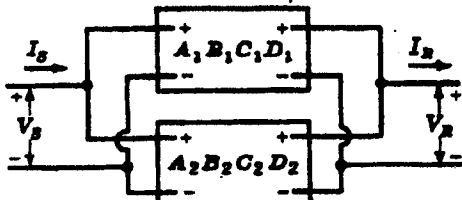


$A = (A_1B_2 + A_2B_1)/(B_1 + B_2)$
 $B = B_1B_2/(B_1 + B_2)$
 $C = C_1 + C_2 + (A_1 - A_2)(D_2 - D_1)/(B_1 + B_2)$
 $D = (B_2D_1 + B_1D_2)/(B_1 + B_2)$

Networks in parallel

Voltage Regulation

$$V_{drop} = I_{jL} r \Rightarrow V_R$$

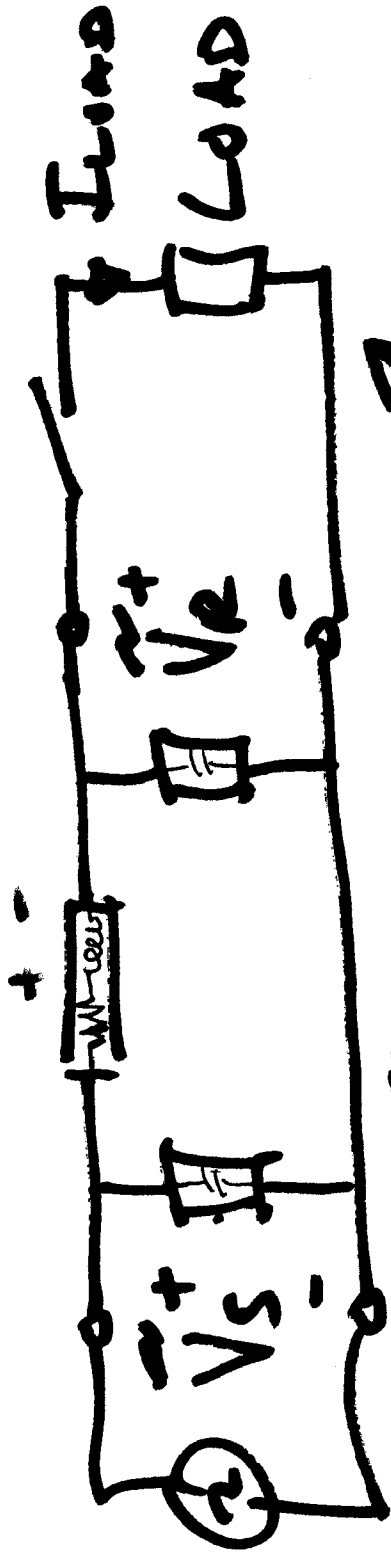


$$V_R = \frac{V_{NL} - V_{FL}}{V_{FL}}$$


Load Voltages!

Most Loads are Lagging PF $\Rightarrow V_{NL} > V_{FL}$
 $V_R > 0$.

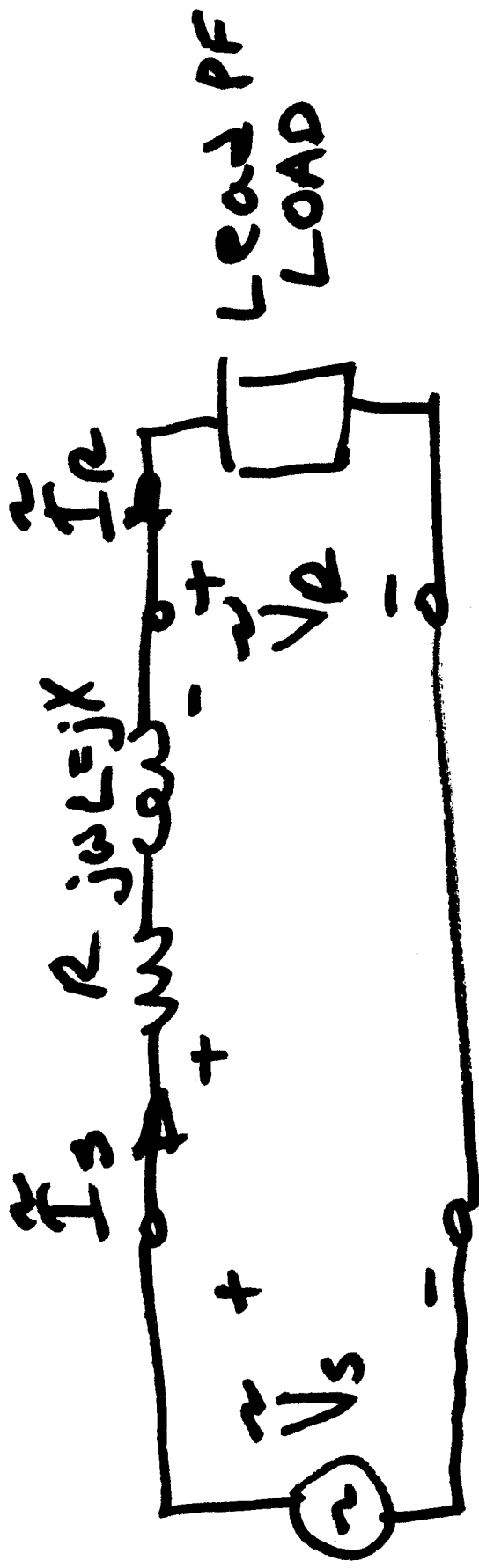If Load is Leading PF $\Rightarrow V_{NL} < V_{FL} \Rightarrow V_R < 0$.



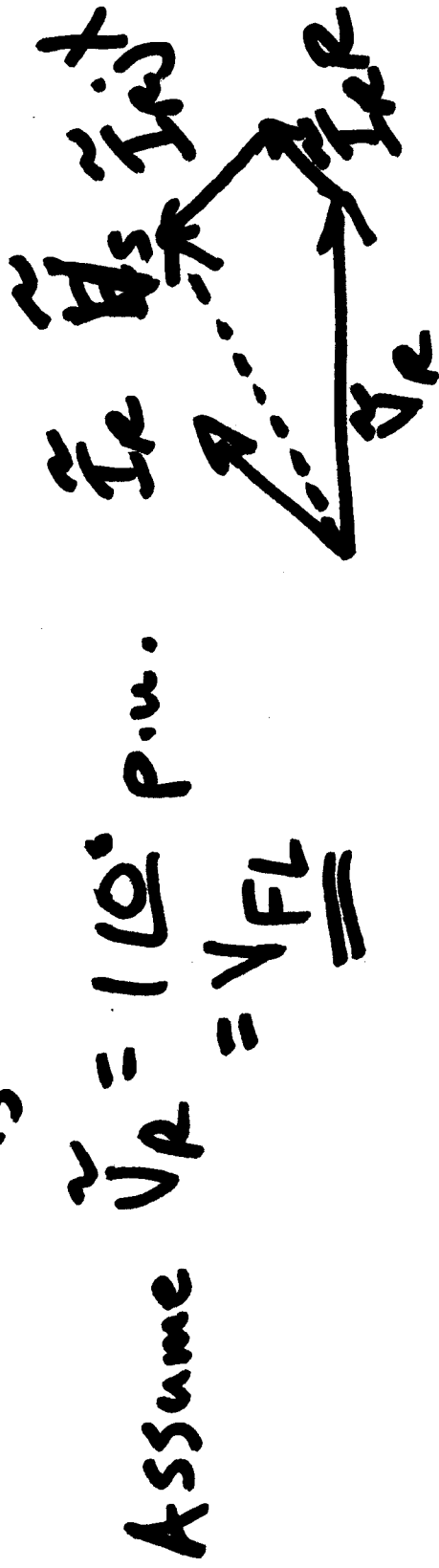
$$\tilde{V}_s = \tilde{I}_R (R + jX) + \tilde{V}_R = \sqrt{V_L}$$




V_R is neg if $V_s < V_R$.
 ($V_{NL} < V_{FL}$)

"NEG VOLT DROP"


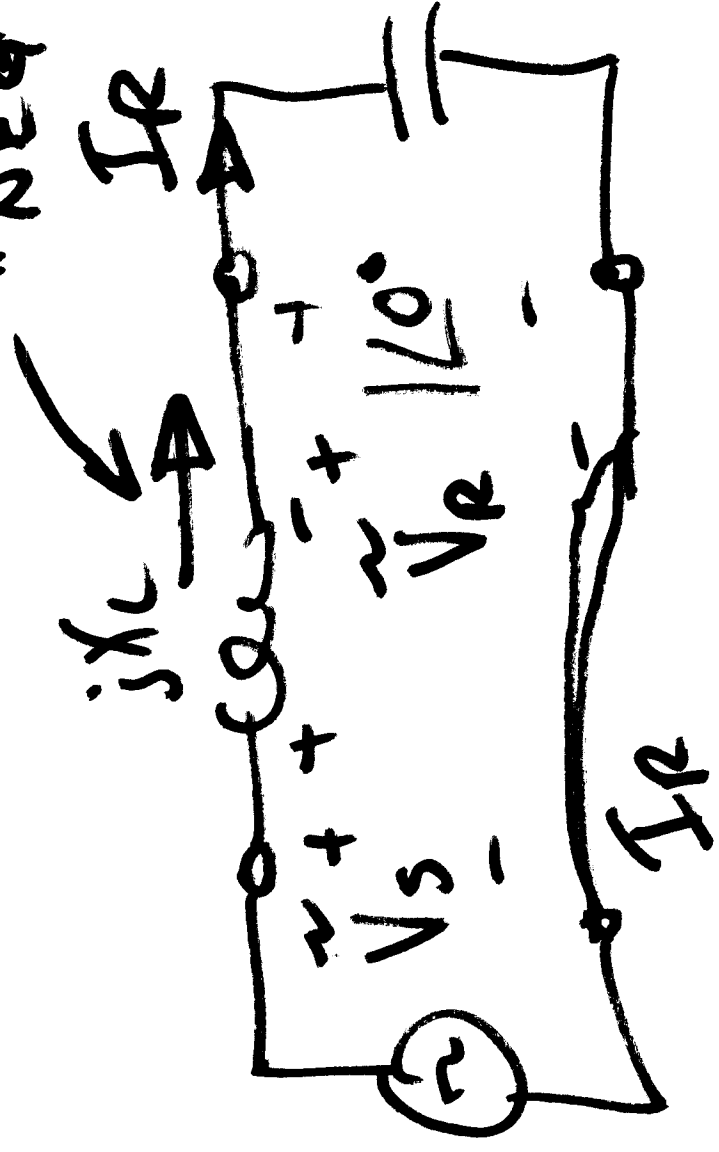


$$\tilde{V}_R = \tilde{V}_s + \tilde{I}RjX_L$$
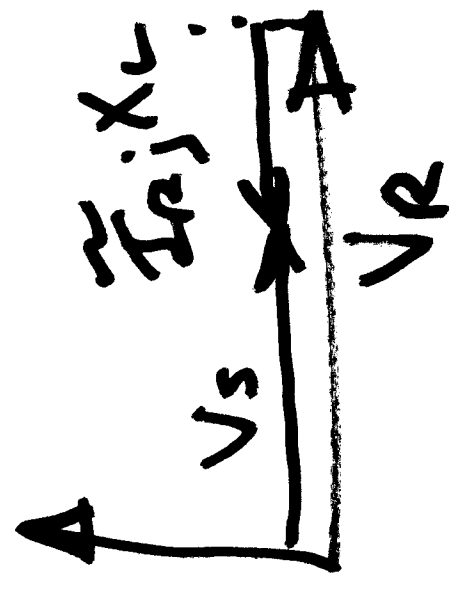
$$\tilde{V}_s = \tilde{V}_R + \tilde{I}RjX_L \quad 180^\circ$$




VOLTAGE PROFILE

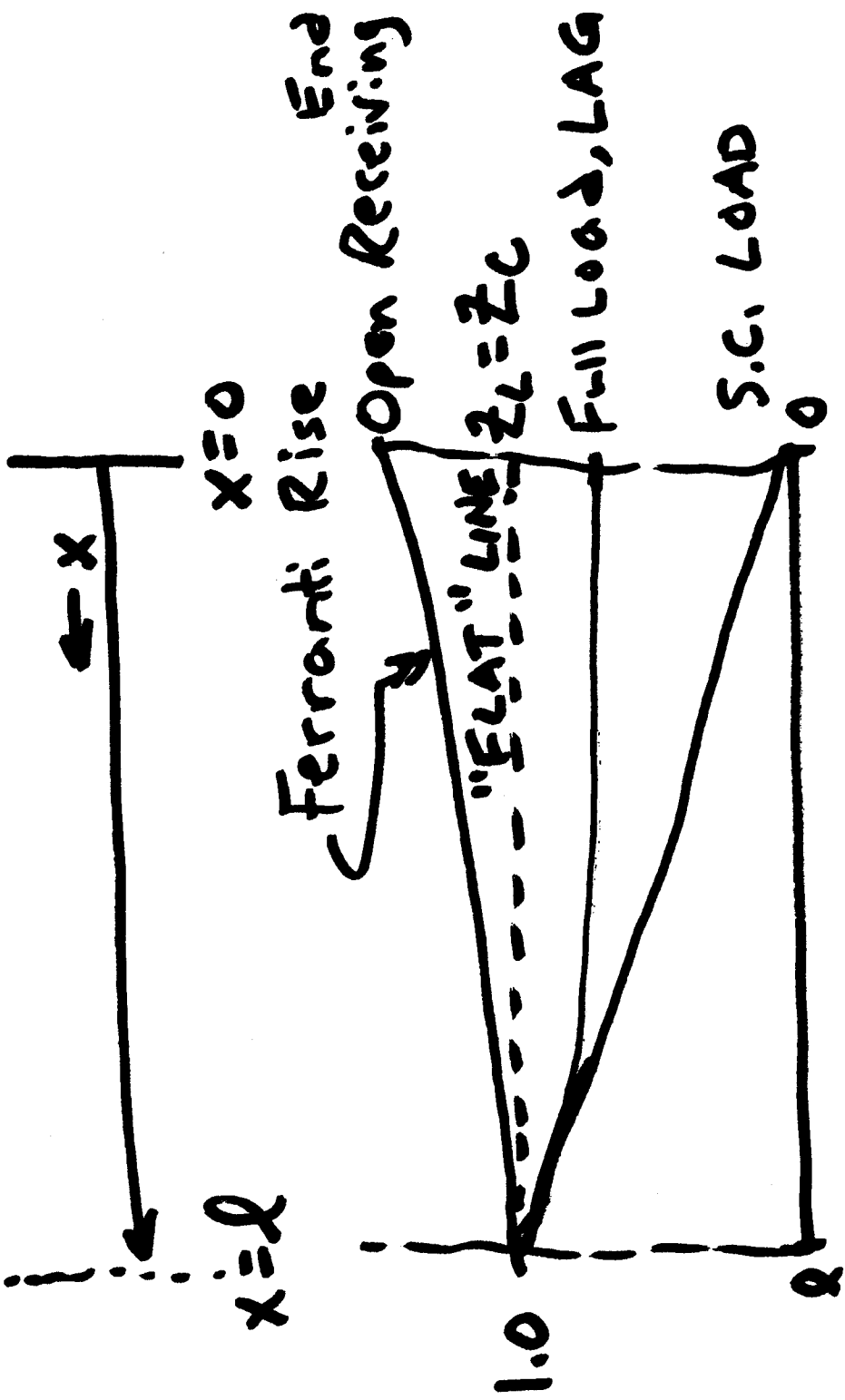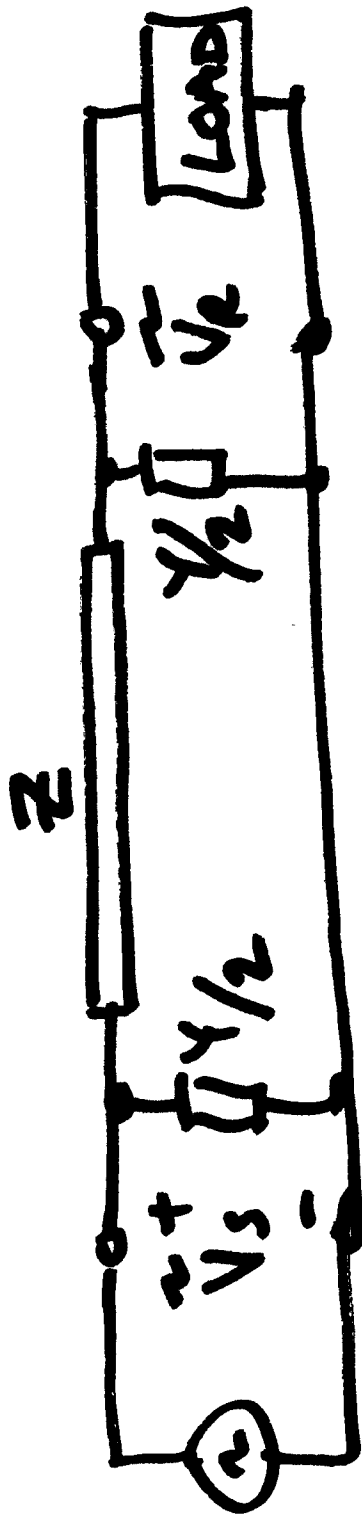

FERRANTI RISE
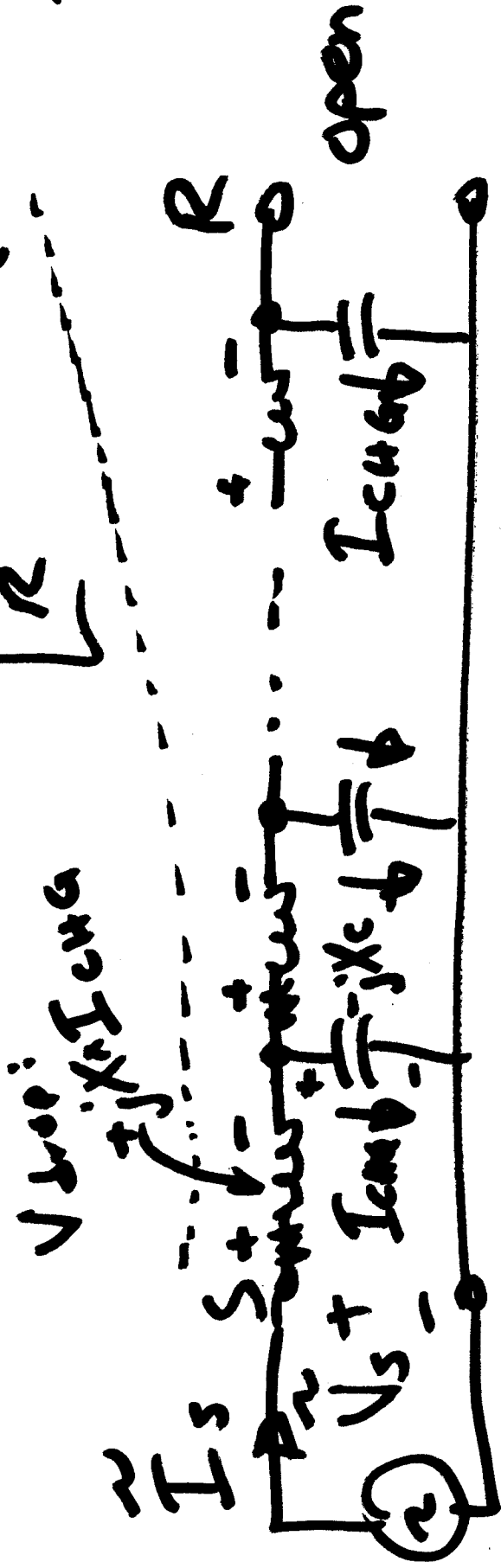
$$\left[\frac{X}{R} \approx 20 @ 345KV \right]$$



$$X_c \gg X_L$$

$$\tilde{V}_s = I_{CHG}$$

$$V_{CAP} = \tilde{V}_s - I_{CHG} jX_L$$

hence the "negative voltage drop"

