


Topics for Today:

- Announcements
- ATP is on remote.mtu.edu. You may apply for ATP/ATPDraw license, verify licensing when you receive it by e-mail, and we will mail you an install CD.
- Office: EERC 614. Phone: 906.487.2857
- Book exercises from Ch.6,7 solutions posted, part of homework.
- Next homework: Transmission Lines as 2-port networks. Matlab.

Chapter 6 - Shunt Capacitance Transmission Lines


• Using the T-Line models

- Short Transmission Lines - up to 50 miles (80 km)
- Voltage Regulation, phasor diagrams, Per-phase impedance diagrams (positive seq only)
- Medium-Length Lines (50 - 150 miles)
- ABCD parameters for Medium-lines, power flow
- Long Lines - more than 150 miles (240 km)
- Compensation - shunt and series
- Derivation of long-line equations, meaning of equations
- Characteristic Impedance Z_C
- Propagation Constant $\gamma = \alpha + j\beta$
- Surge-Impedance Loading (SIL)
- Wavelength, velocity, Traveling waves, reflections

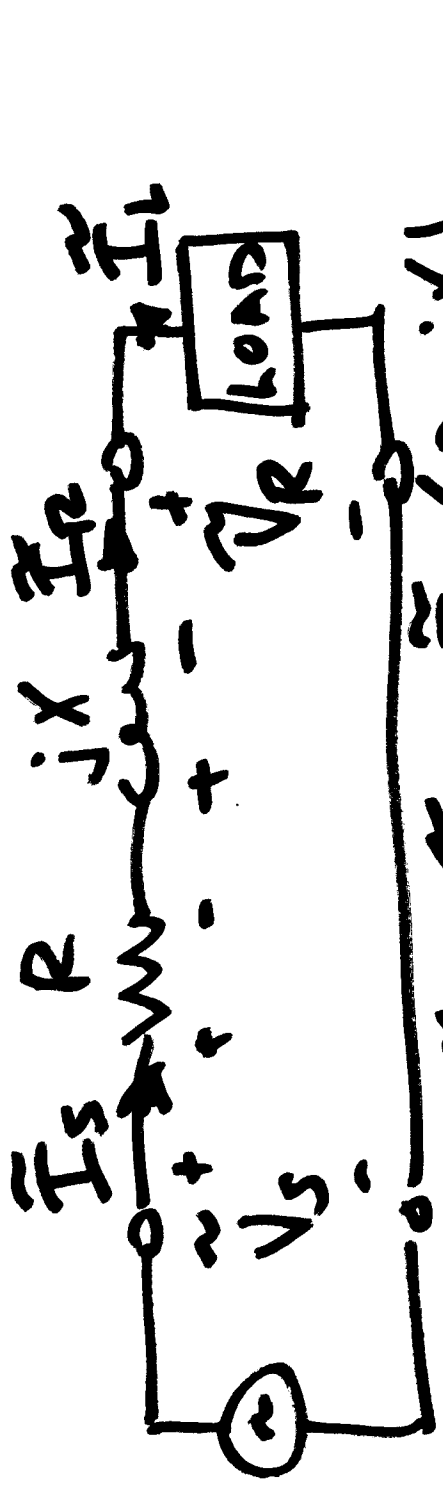

$$\tilde{V}_r = \tilde{V}_s - \tilde{I}_r(R + jX)$$

LAG PF
(VR pos)

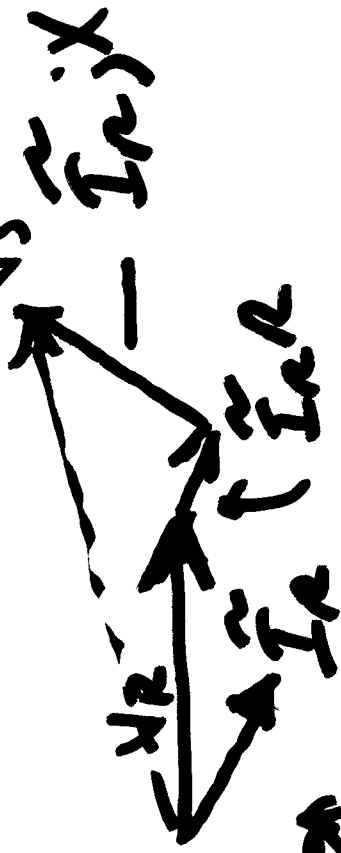

UNITY PF
(VR pos)



LEAD PF





VR often neg.



Reactive Compensation

2

- Add a series cap

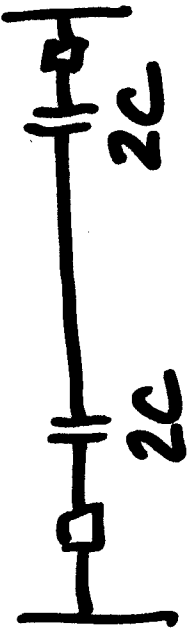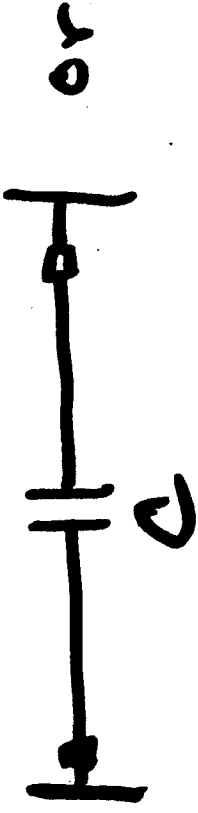

- Shunt Compensation

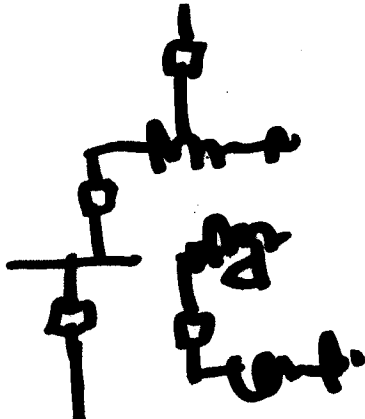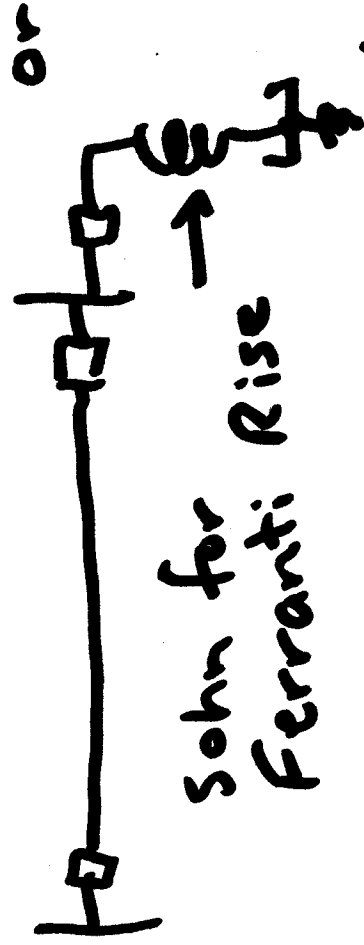


- First, review key concepts

- Power Flow Limits

- Ferranti Rise

Power Flow thru T-Line
 ... if we neglect the effects of R, C

3

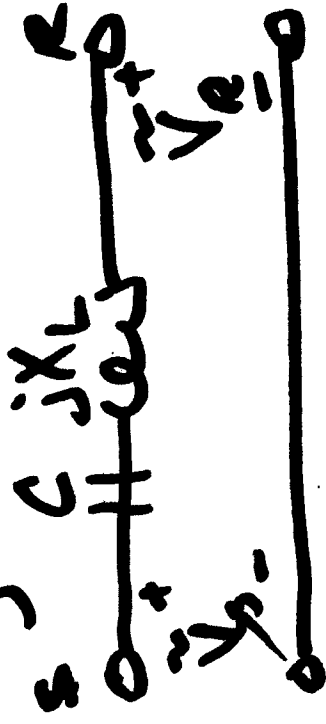


Power transferred:

$$P = \frac{V_s V_r \sin \delta}{X_L} \quad \underbrace{V_s V_r \sin \delta}_{S}$$

$$P_{max} = \frac{V_s V_r}{X_L}$$

use same equation for P_{out} of a synch machine:
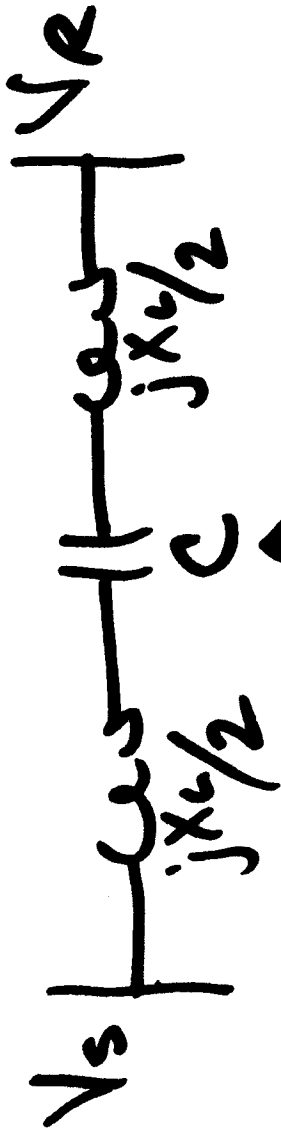
$$P_{out} = \frac{V_g V_T \sin \delta}{X_s} \quad \underbrace{V_g V_T \sin \delta}_{\text{output}}$$



Series Compensation

$$\frac{1}{j\omega C} = -jX_C$$

$$P_{MAX} = \frac{V_s V_r}{(X_L - X_C)}$$

$$X_C = X_L$$

then 100% comp.


$$P_{MAX} = \infty \quad (\text{neglecting } R, \text{ Shunt } C)$$

Compensation Factor:

$$\boxed{\frac{X_C}{X_L}}$$

typically $0.2 \rightarrow 0.7$

Problem: Subsynchronous Resonance

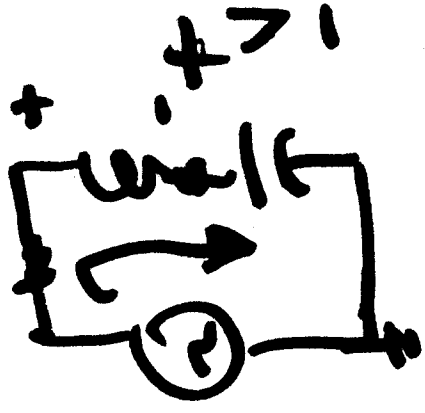

Ex: 30% compensation

ie. $\frac{x_c}{x_L} = 0.3$


$$P_{MAX I} = \frac{V_s V_r}{x_L}$$

$$P_{MAX (comp)} = \frac{V_s V_r}{0.7 x_L} = 1.43 P_{MAX I}$$

70% comp $\Rightarrow P_{MAX (comp)} = \frac{V_s V_r}{0.3}$

$$\Rightarrow 3.33 P_{MAX I}$$

But...
 ==

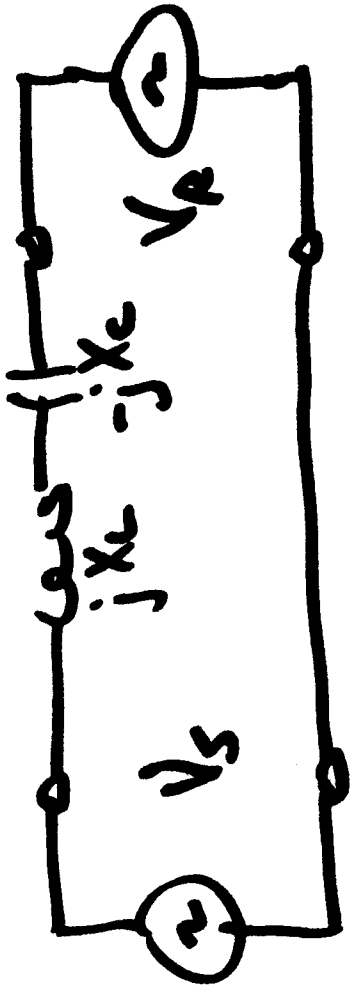

6


$$f_p = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{\frac{3}{\omega^2} X_C}}$$

$$X_L = 2\pi fL$$

$$X_C = \frac{1}{2\pi fC}$$


for 30% comp $f_r = f_{\text{sync}} \sqrt{1.3} = f_0 \sqrt{\frac{X_C}{X_L}}$
 $= 33 \text{ Hz}$


70% comp $f_r = 50 \text{ Hz}$

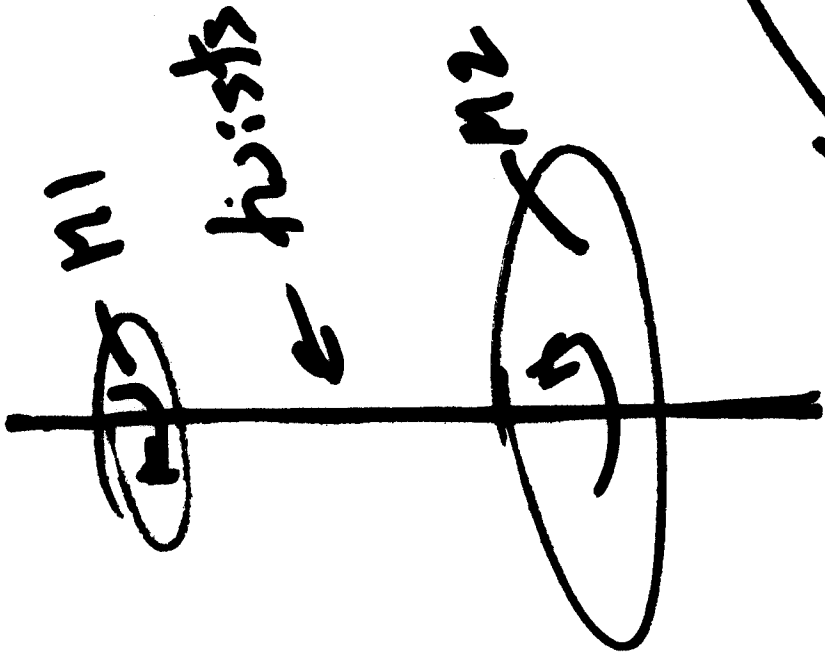

33 Hz

torsional oscillations

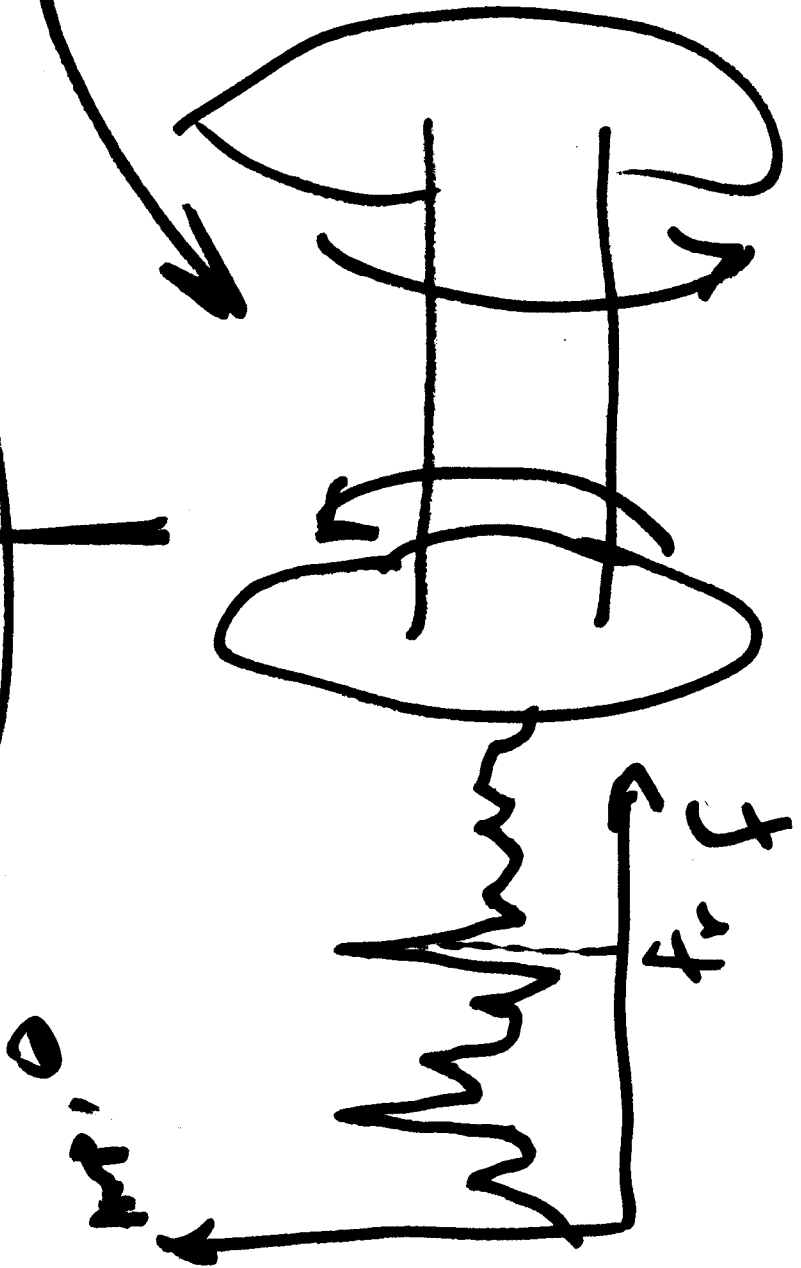

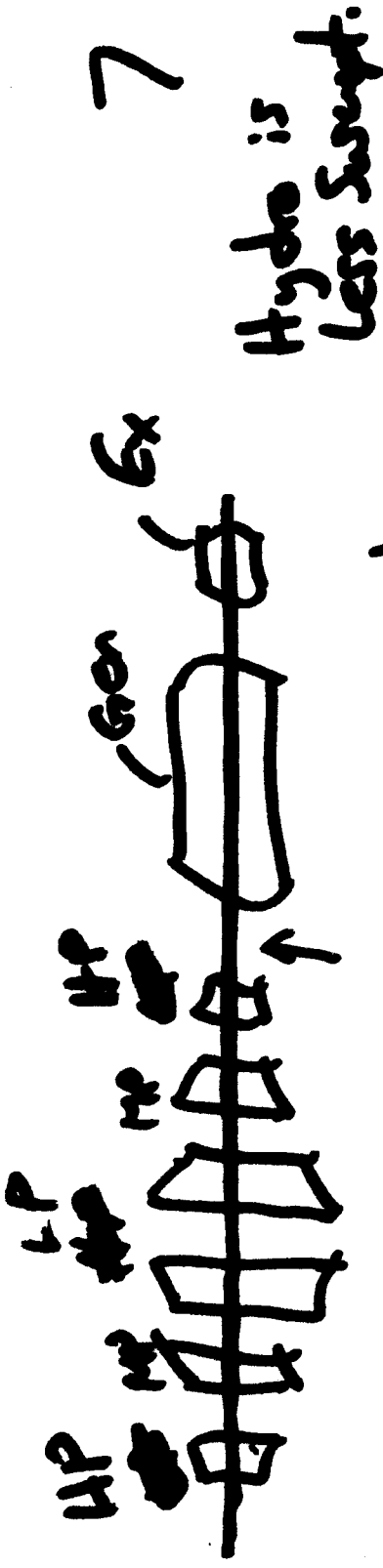

Not Freq, if mechanically excited

i.e. if some mech natural freq matches an electrical nat'l freq then we will "excite" this resonance.



First well-documented case:

- Salt River Project

- Careful!
- Long HV compensated Line
- Lots of local Gen
- Lots of remote Load

Ferranti Rise


8

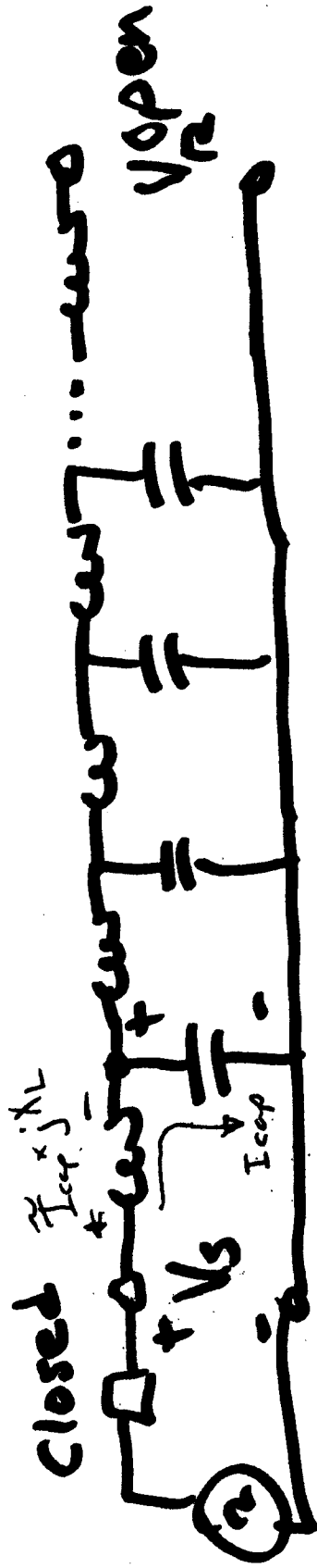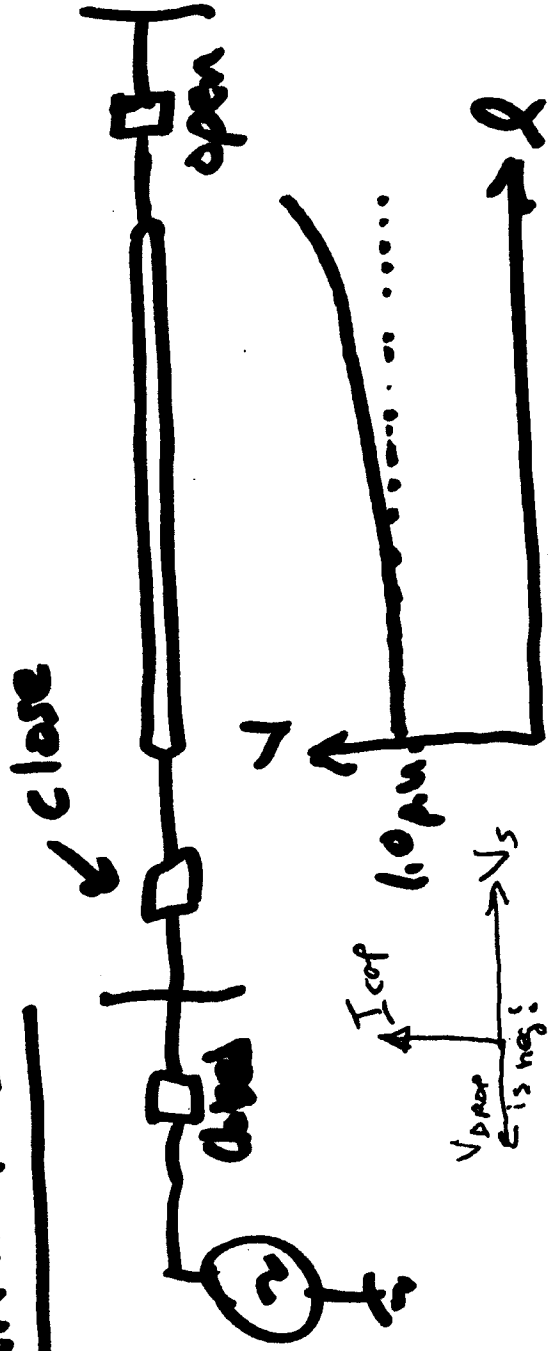

$$V_{out} = V_s \frac{-jX_C}{j(X_L - X_C)}$$

$X_C \gg X_L$

Some value $\gg 1$.

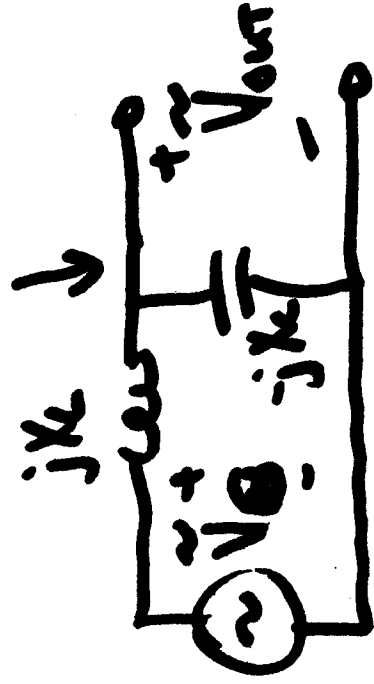


Shunt Compensation:

9

$$I_{\text{shunt}} = I_{\text{line}} \sin \phi$$



Connect Shunt Reactor at receiving end.

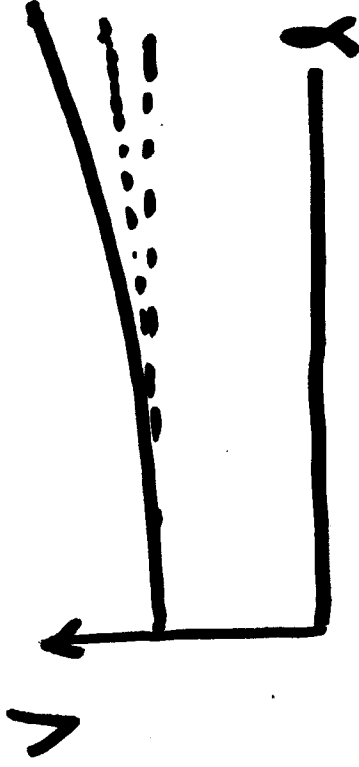

Limit to

$$\leq 1.10 \text{ pu}$$

Compensates for Ferranti rise.


- Can also use Shunt Reactor (inductor)

- to hold V_r down during lightly-loaded cases.

- Too heavily loaded, low voltage

- add cap in shunt.

Shunt Compensation

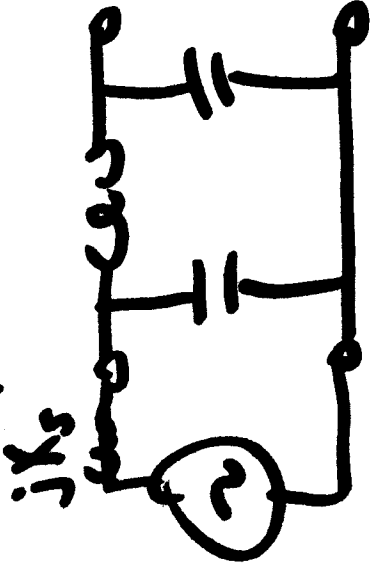


100 mi Bluebird

$D_{eq} = 20 \text{ ft.}$

$X_c = 1665 \Omega$


$X_s = 120 \Omega \text{ (typ)}$

Line Chg:

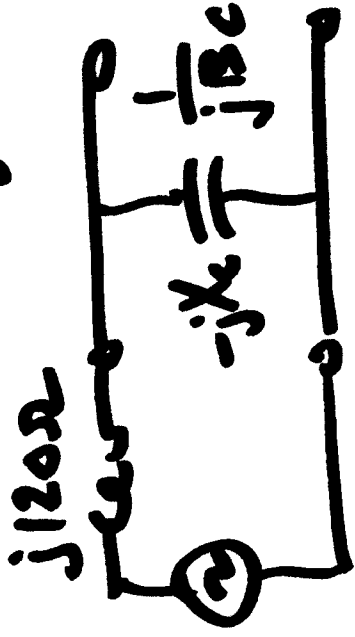

$Y_{cap} = jB_c$

$Z_{cap} = -jX_c$

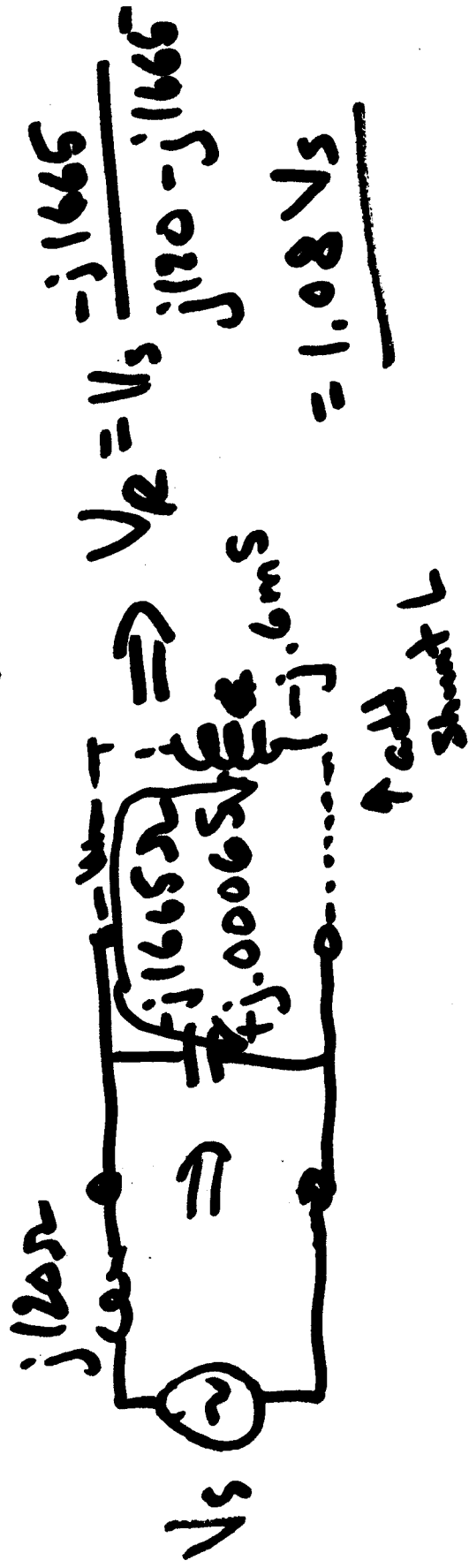

$V_R = V_s \frac{-j1665}{j120 - j1665}$

$= 1.08 V_s$

$$\text{Shunt Comp Factor} = \frac{B_L}{B_C} = \frac{1/\omega L}{\omega C_{CHG}} \parallel$$

Total Compensation:

Add a reactor $B_L = B_C$

Total Shunt Admittance = 0




$$Y_{\text{TOTAL}} = jB_C - jB_L = 0$$

($Z_{\text{SHUNT}} = \infty$)

$$P_{1 \rightarrow 2} = \frac{V_1 V_2}{X_L} \sin(\alpha - \beta)$$

Power Transfer Capability.

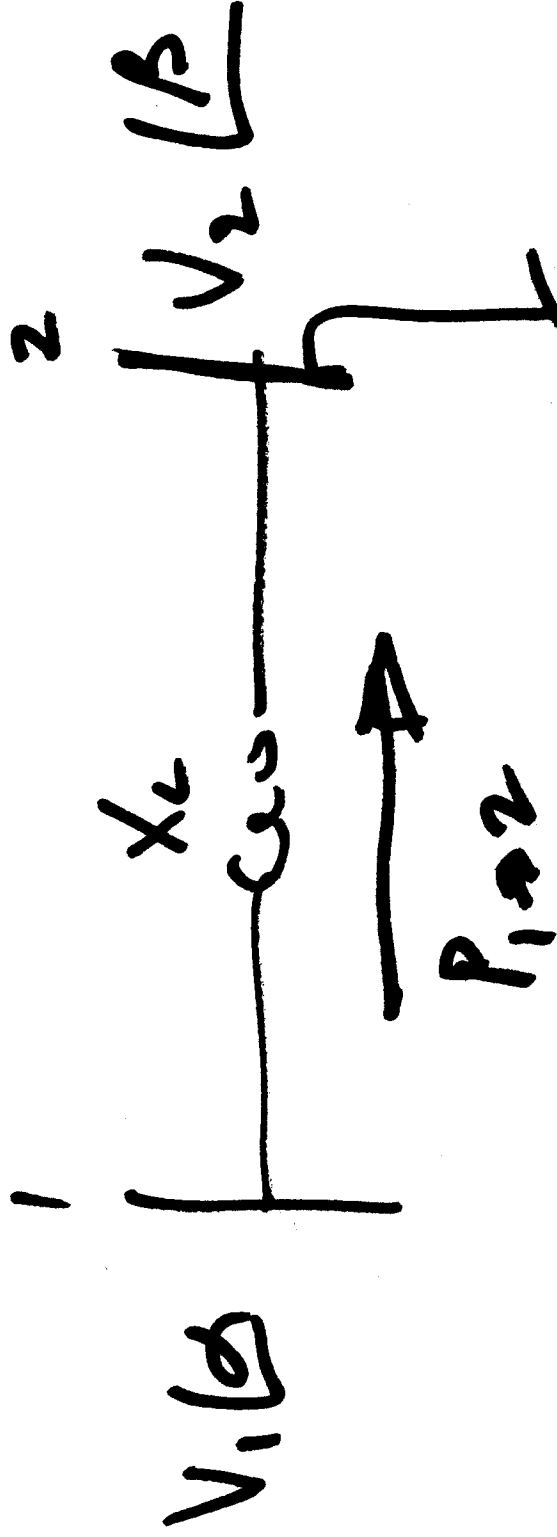

$$V_1 V_2 : \text{min} : \frac{(95)(501)}{9185} = 5.176$$

$$: \text{max} : \frac{(105)(501)}{9185} = 5.818$$

min \Rightarrow increase!

SHUNT CAPS:


- P.F. correction (on consumer side of meter)





- Voltage Support
- Max Power Transfer (see next slide.)

Voltage Regulation:

③

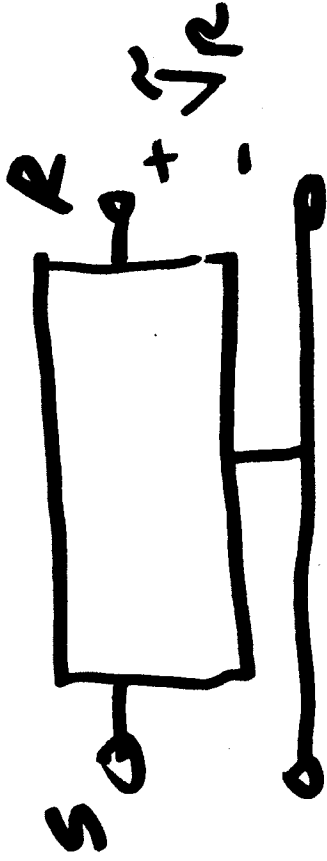


$$VR = \frac{|\tilde{V}_{R, NL}| - |\tilde{V}_{R, FL}|}{|\tilde{V}_{R, FL}|}$$

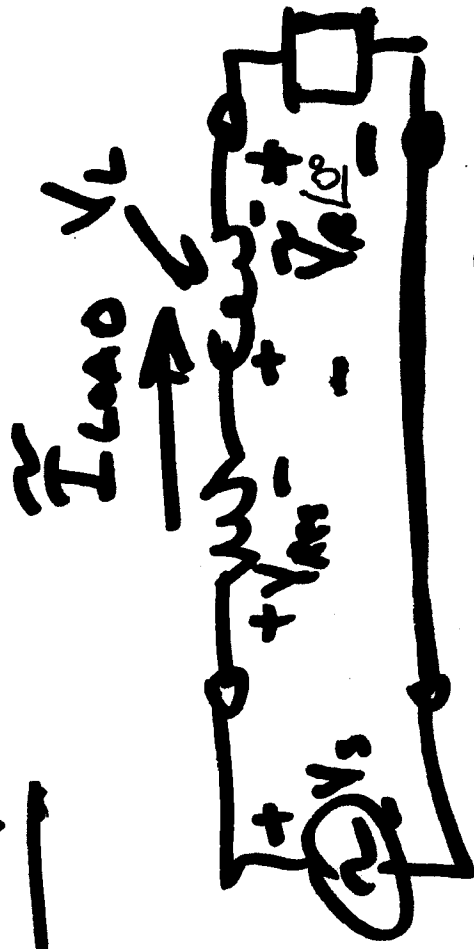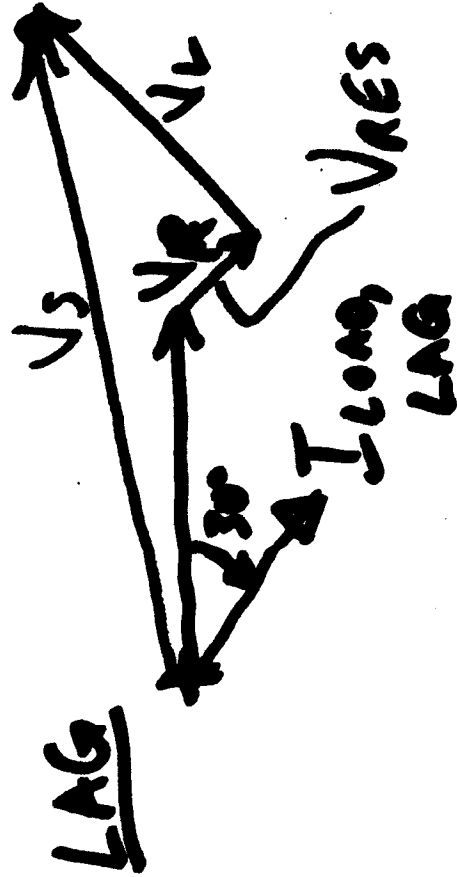


$$\begin{aligned} \tilde{V}_S &= \tilde{V}_{RES} + \tilde{V}_L + \tilde{V}_R \\ &= \tilde{I}_{Load} R + \tilde{I}_{Load} jX + \tilde{V}_R \end{aligned}$$

LEAD

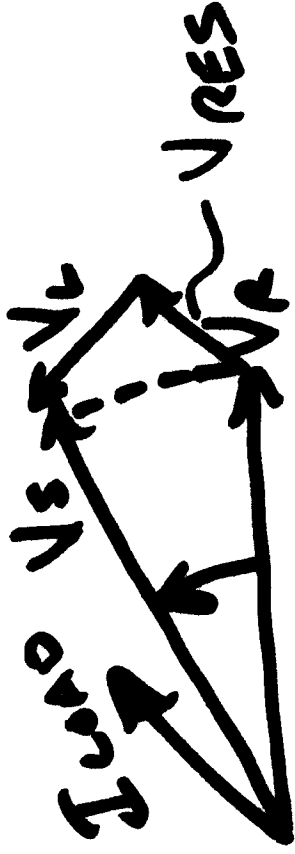

Note: V_R can
be negative
for leading
P.F. load.

UNITY P.F.

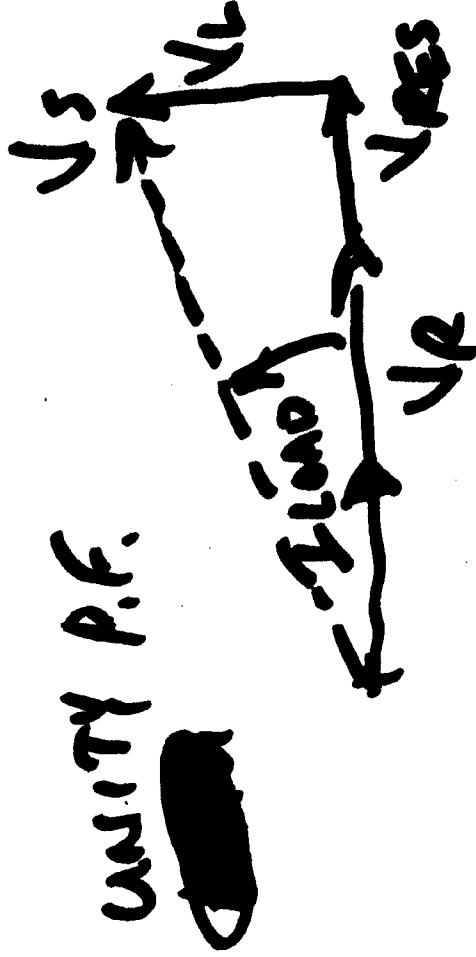

$$V_R = \frac{V_{Ll} - V_{Fc}}{V_{Fc}} = \frac{V_s - V_R}{V_R} = \text{---} \text{---} \text{---} \text{---}$$

pos. no.
for lag, unity.


V_R in terms of $\underline{A-B-C-D}$.

5

Recall: $V_R = \frac{V_{R,NL} - V_{R,FL}}{V_{R,FL}}$

$$= \frac{V_s/A + V_{R,FL}}{V_{R,FL}}$$

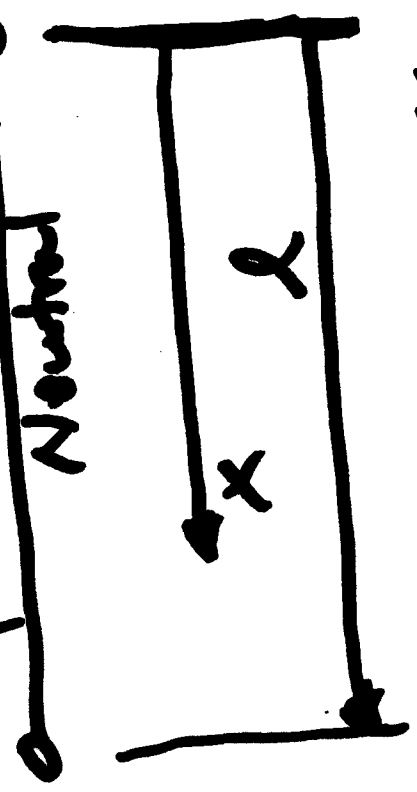In General, $A \rightarrow \frac{R}{s} + jX$ $\rightarrow A'$ ②



Short Line

$\leq 50 \text{ mi (80 km)}$


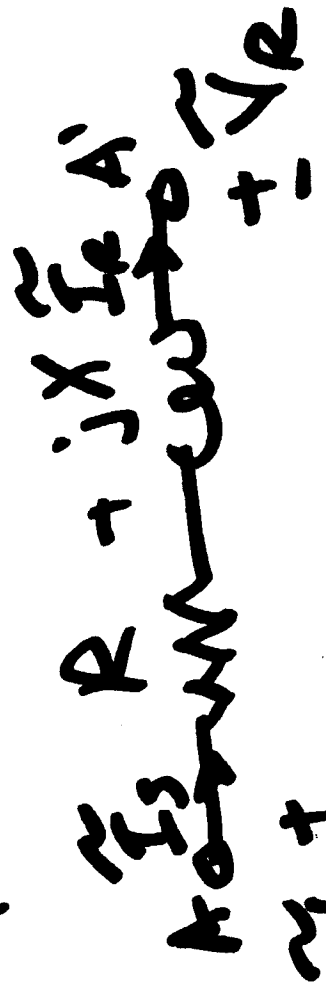
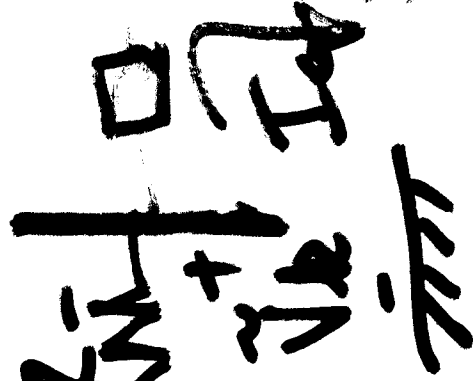


Fig. 6.3
Ex. 6.1

$\frac{X}{R}$ ratio determines
effectiveness of

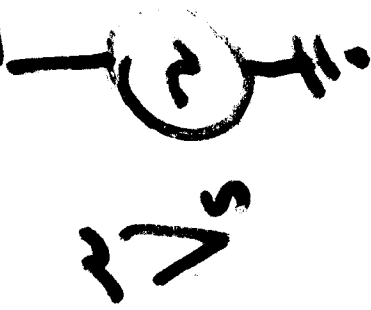shunt $C \rightarrow i_{cr} \rightarrow i_{cr} \rightarrow i_{cr}$



i_{cr}



If $\frac{X}{R} = 0 \rightarrow i_{cr} \rightarrow i_{cr}$