

Topics for Today:

- Announcements
- Software: We will be opening EERC 134 Lab to this class. Aspen, ATP will be installed there (to reduce IT issues with support).
- Learning Center next week: require you and your partner to visit!
- Office: EERC 614. Phone: 906.487.2857
- Book exercises from Ch.6,7 solutions posted
- Next homework: Transmission Lines as 2-port networks. Matlab.

Chapter 6 - Transmission Lines

- Using the T-Line models
 - Short Transmission Lines - up to 50 miles (80 km)
 - Voltage Regulation, phasor diagrams
 - Per-phase impedance diagrams (positive seq only)
 - Medium-Length Lines (50 - 150 miles)
 - ABCD parameters for Medium-lines, power flow
 - Long Lines - more than 150 miles (240 km)
 - Derivation of long-line equations, meaning of equations
 - Characteristic Impedance Z_C
 - Propagation Constant $\gamma = \alpha + j\beta$
 - Surge-Impedance Loading (SIL)
 - Wavelength, velocity, Traveling waves, reflections

$$Z_C = \sqrt{\frac{Z}{y}}$$


Imp per unit length
Admitt "

$$\gamma = \sqrt{ZY} = \alpha + j\beta$$

phase angle
rotation

Has a wave
travels down line.

attenuation

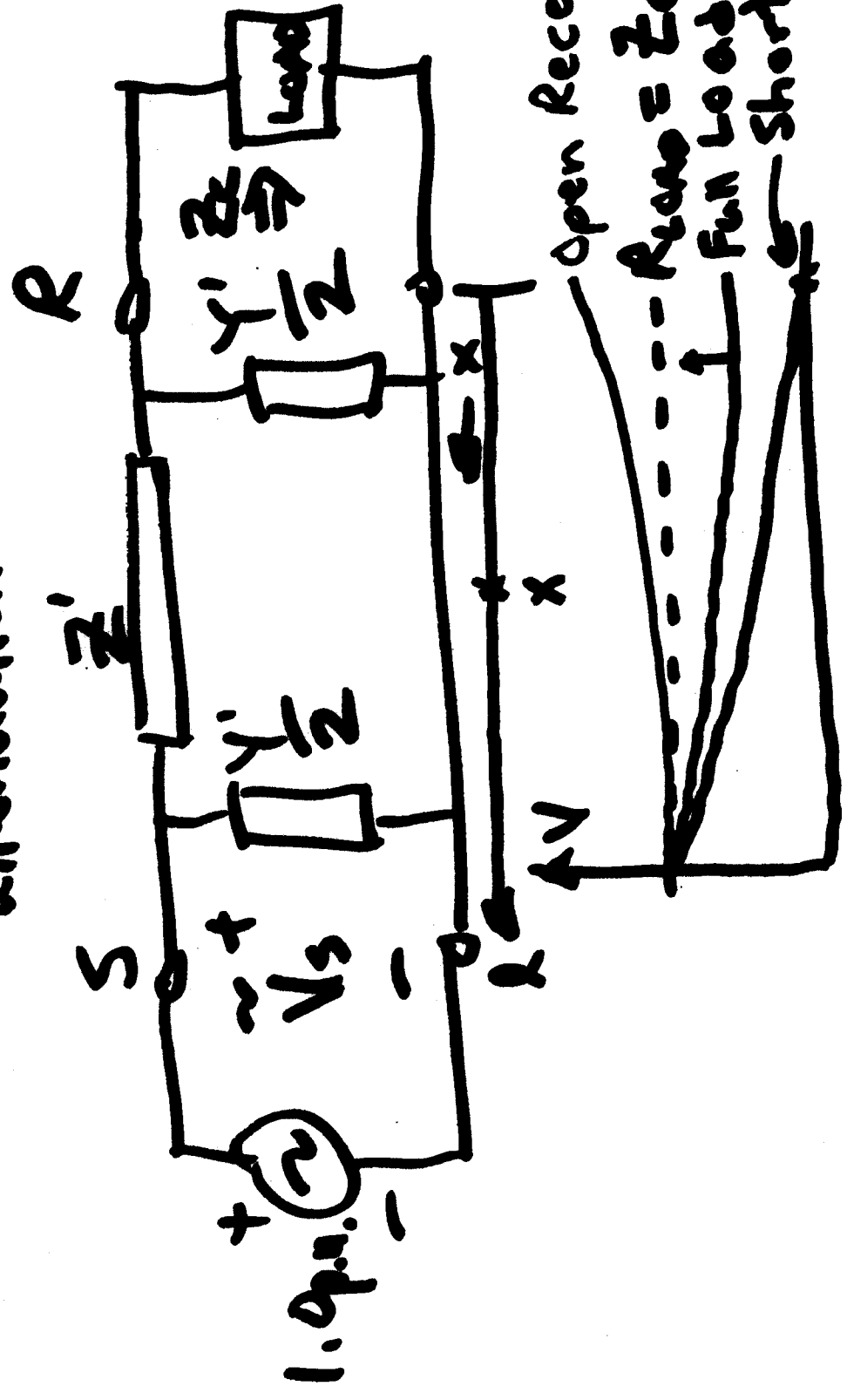

Another Point:

- SIL = Surge Impedance Loading

$$- R_{LOAD} = |Z_C|$$


- Total Reactive Power Consumed in Line = 0.

→ "Flat" Line or flat voltage profile.


$$- SIL = \frac{V^2}{Z_C} = \frac{V_S^2}{Z_C} = \frac{V_R^2}{Z_C}$$

High x/R :


$$\bar{z}_c = \sqrt{\frac{z}{y}}$$

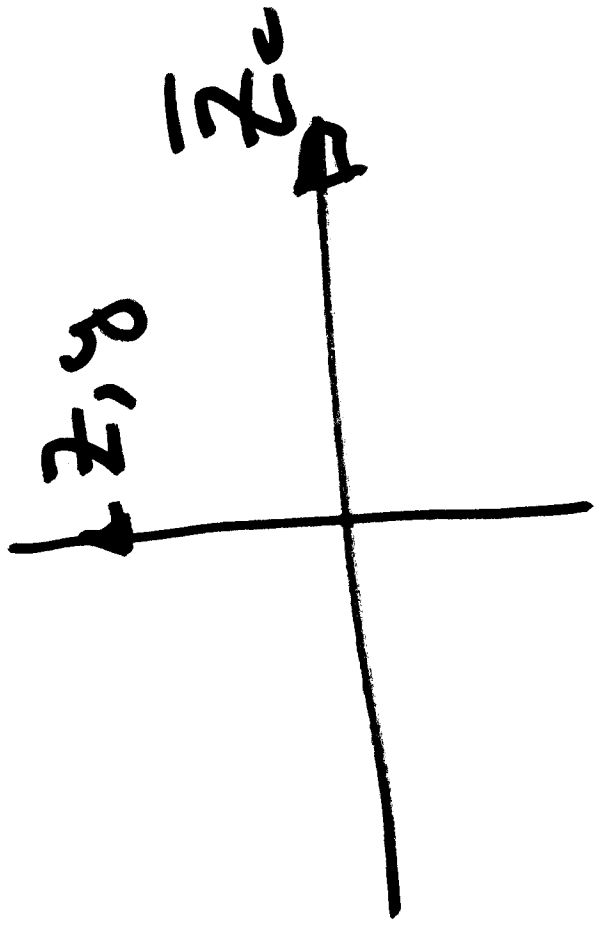

Low x/R :

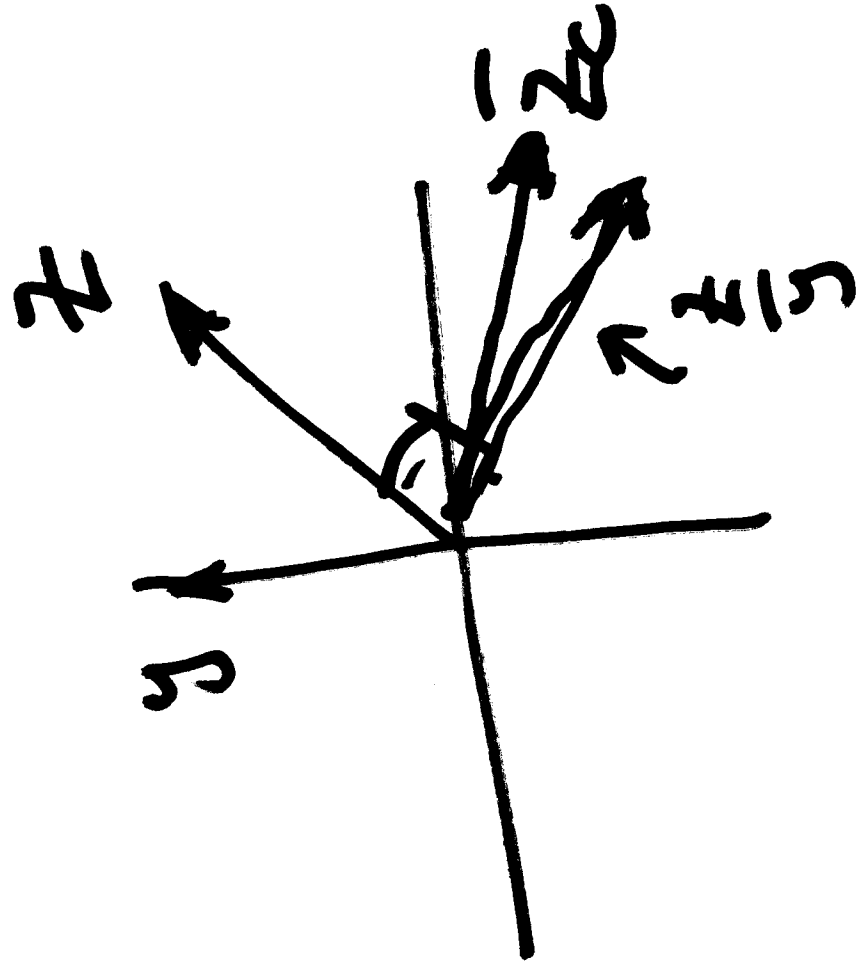

$$\bar{Z}_c = \sqrt{\frac{Z}{Y}}$$

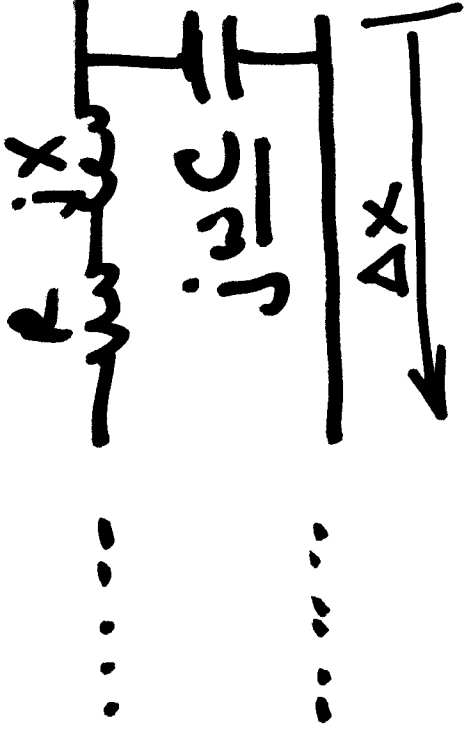

$$Z = R + jX_c \text{ per unit length}$$

$$Y = jB_c = j\omega C \quad \text{" "}$$

Observations: for high X/R ratio:

$$\bar{Z}_c \approx \text{Real} \Rightarrow 100\text{'s KV: } X/R = 10-20$$

$$\bar{Z}_c \Rightarrow 10\text{'s KV: } X/R \leq 1$$

Propagation Wavelength λ

3

λ = distance req'd to change $\angle V$ by 360° .

$$\gamma = \sqrt{ZY} = \alpha + j\beta \quad (\text{Assume Lossless})$$


α ← per unit length

$e^{j\beta x}$: term provides phase rotation in each term of $I(x), V(x)$.

$$\lambda = x = \frac{2\pi}{\beta} \Rightarrow \lambda = \frac{2\pi}{\omega\sqrt{LC}} = \frac{2\pi}{2\pi f\sqrt{LC}}$$

$$\lambda = \frac{1}{f\sqrt{LC}}$$
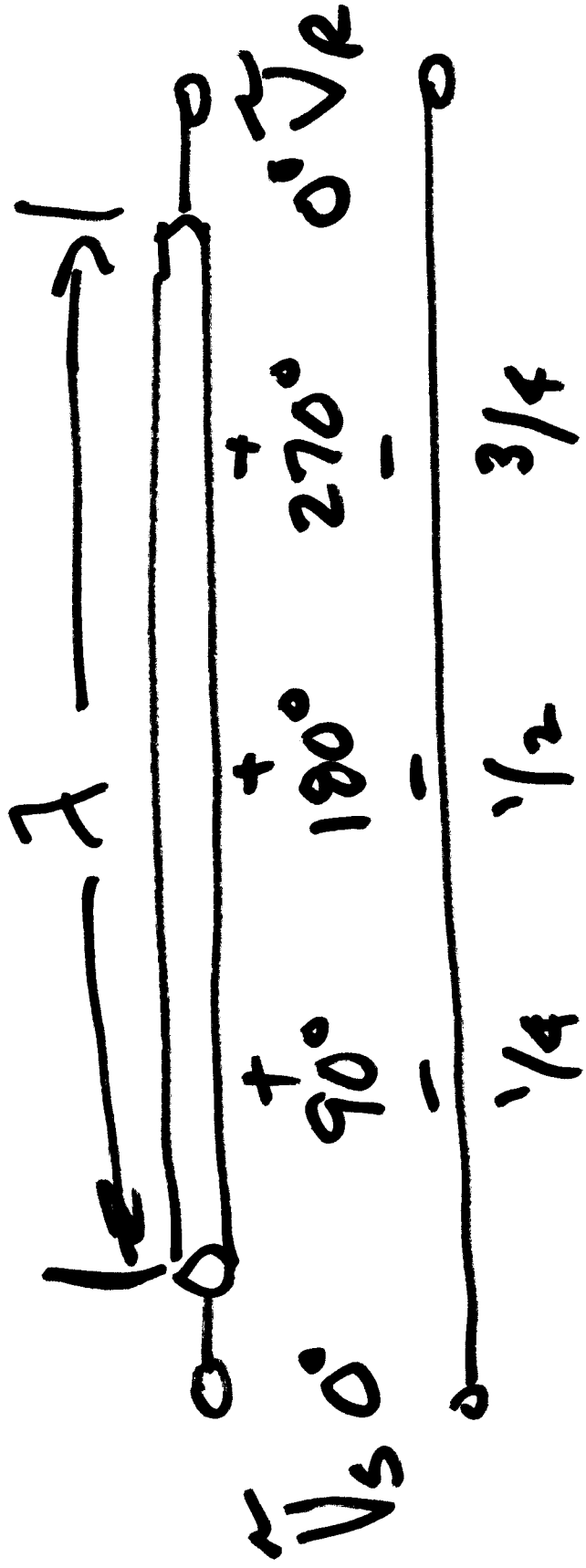
$$v = f\lambda = \frac{1}{\sqrt{LC}} = 3 \times 10^8 \text{ m/s} = \frac{1}{\sqrt{\epsilon_0 \mu_0}}$$



$$\text{@ } 60 \text{ Hz, } \lambda = \frac{v}{f} = \frac{3 \times 10^8 \text{ m/s}}{60}$$

4

$$\text{BPL: } \frac{2-40 \text{ MHz}}{\approx 5000 \text{ km}} \approx 3100 \text{ miles}$$

$$\text{@ } 2 \text{ MHz, } \lambda = \frac{3 \times 10^8}{2 \times 10^6} = 150 \text{ m}$$

- Side Comments (later) on
* T-line loading limits

- 1) - Thermal
- 2) - Voltage Limits, $V_s \neq V_R \Rightarrow V_R$
 $.95V < 1.05$
- 3) - Stability Limits

(From Lecture 15)

$$V(x) = \left(\frac{V_R + Z_C I_R}{2} \right) e^{+\gamma x} + \left(\frac{V_R - Z_C I_R}{2} \right) e^{-\gamma x}$$

$$I(x) = \left(\frac{V_R + Z_C I_R}{2} \right) e^{+\gamma x} - \left(\frac{V_R - Z_C I_R}{2} \right) e^{-\gamma x}$$

best for
freq. waves.

$$Z_C = \sqrt{\frac{Z}{Y}} = \text{Characteristic Impedance.}$$


$$\gamma = \sqrt{ZY} = \alpha + j\beta = \text{Propagation Coefficient}$$

α = Attenuation constant

β = Angular propagation constant

Travelling Waves

5

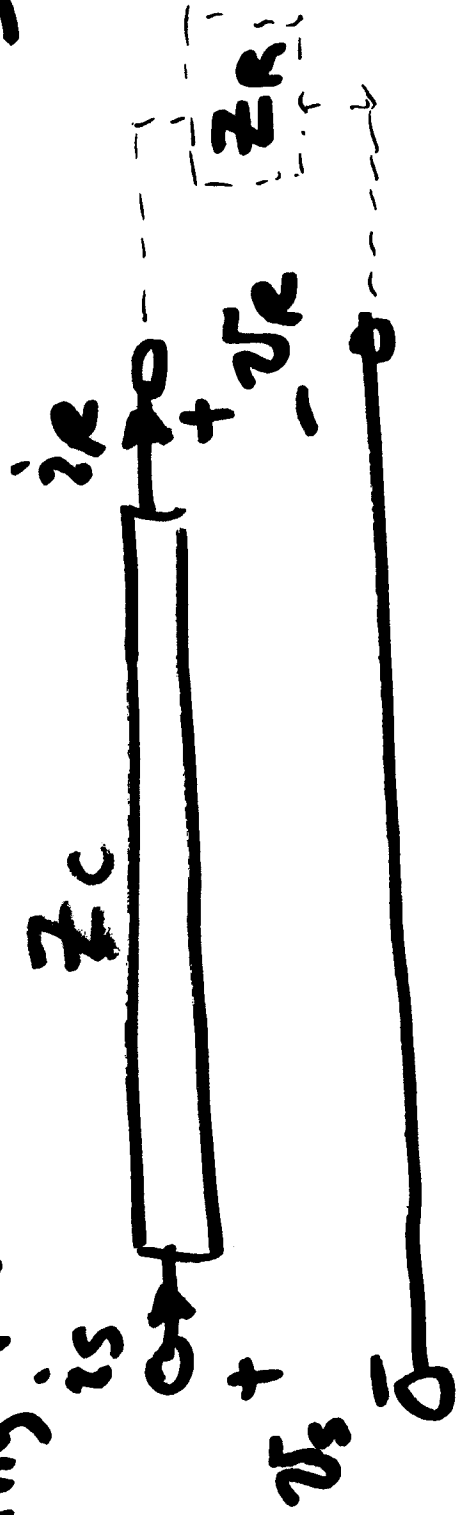


Impedance at receiving end:

$$Z_R^- = \frac{V_R^-}{I_R^-} = \frac{V_R^+ + V_R^-}{I_R^+ + I_R^-} =$$

$$\frac{V_R^+ + V_R^-}{\frac{V_R^+}{Z_c} - \frac{V_R^-}{Z_c}} = Z_R$$

$$\frac{V_R^-}{V_R^+} = \frac{Z_R - Z_c}{Z_R + Z_c} = \rho$$

Reflection Coefficient

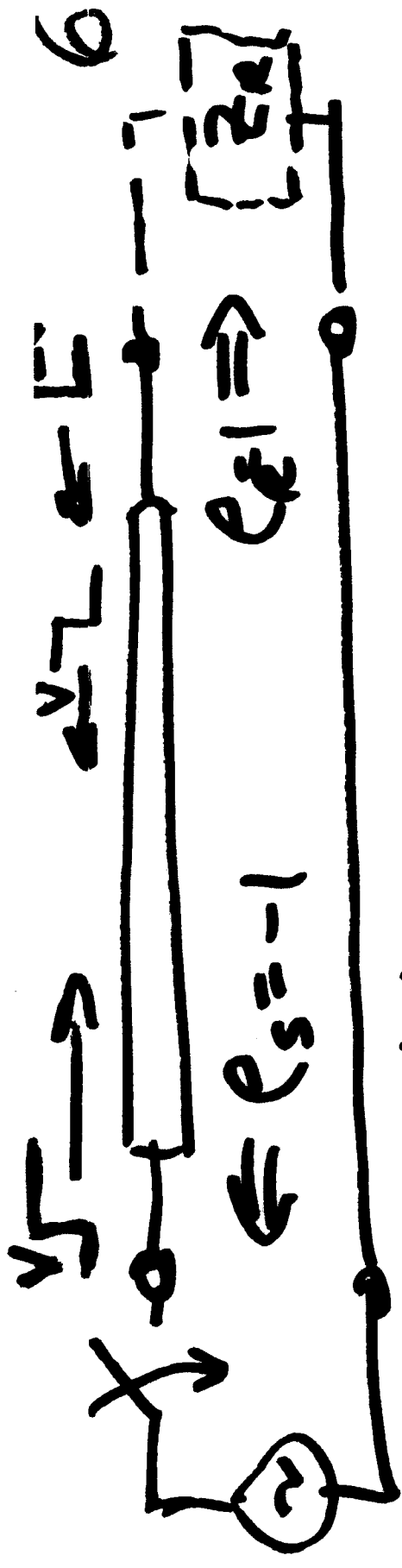

If receiving end is...

- Open-ckt (i.e. $Z_R = \infty$)

$$\Gamma_R = \frac{\infty - Z_c}{\infty + Z_c} = +1$$

$$\therefore V_R^- = V_R^+ \Gamma_R = V_R^+$$

- Short-ckt (i.e. $Z_R = 0$)

$$\Gamma_R = \frac{0 - Z_c}{0 + Z_c} = -1$$