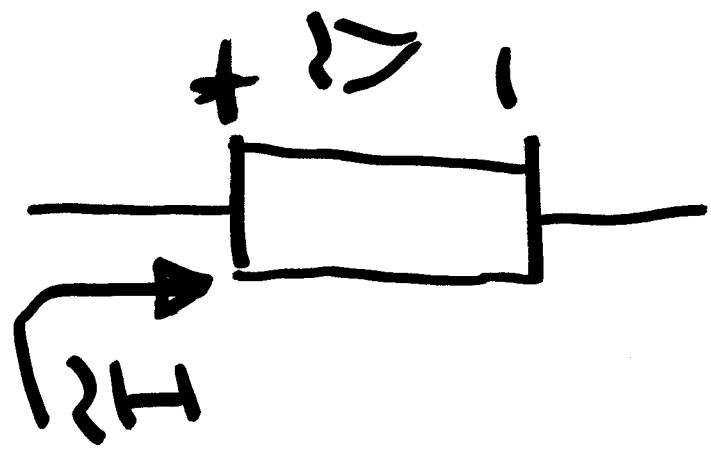


- Quick Review of circuit basics:
 - Active vs. passive sign convention
 - Dual-subscript notation, single-subscript (implied reference)
 - Closure of subscripts in mesh equation
 - Euler's Identity - basis for phasor analysis! See handout.
 - Drawing phasor diagrams, arrowheads
 - Three-phase, "open" vs. "closed" voltage phasor diagrams
 - Errata in text book - Figs. 1.16, 1.17.
- Study Chapters 1 and 2 for Thursday

**Do Practices
Exercises at
end of Chapter!**


SIGN CONVENTION



PASSIVE

"Motor Convention"

"Load Convention"

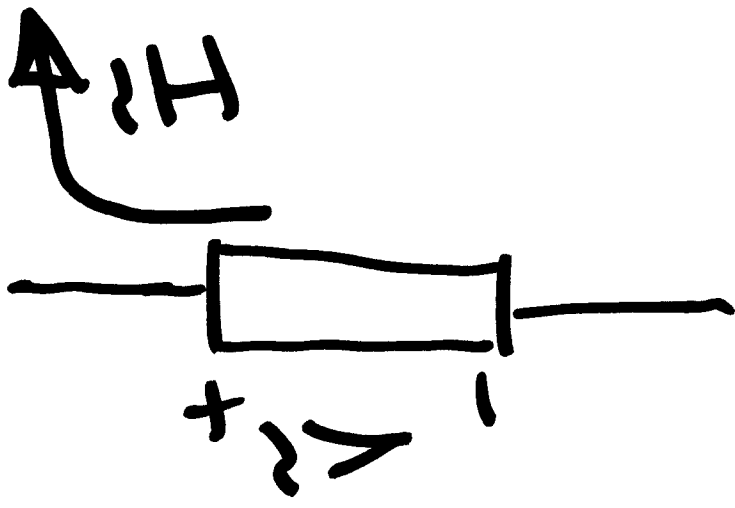


ACTIVE

"Generator Convention"

"Source Convention"


Subscripts

Double-Subscript

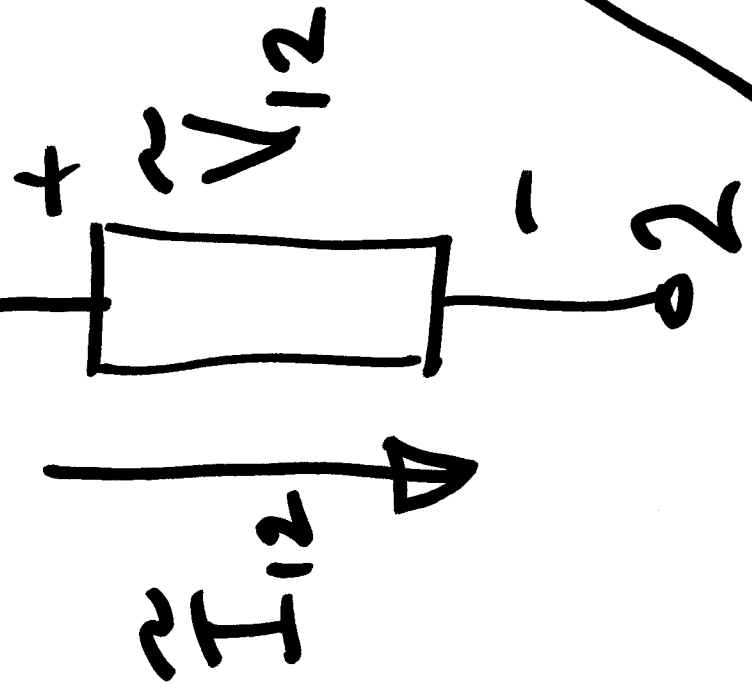


Single subscript notation:
Second subscript is assumed.

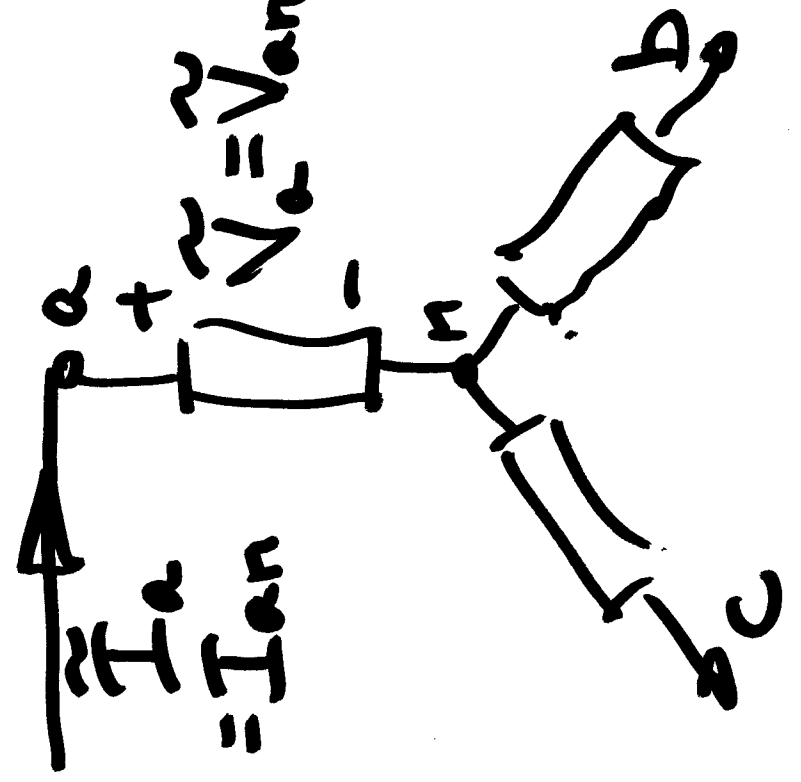Always use \vec{I}
Voltage drops!
(Voltage rises seen in old texts).



Closure in subscripts:

5

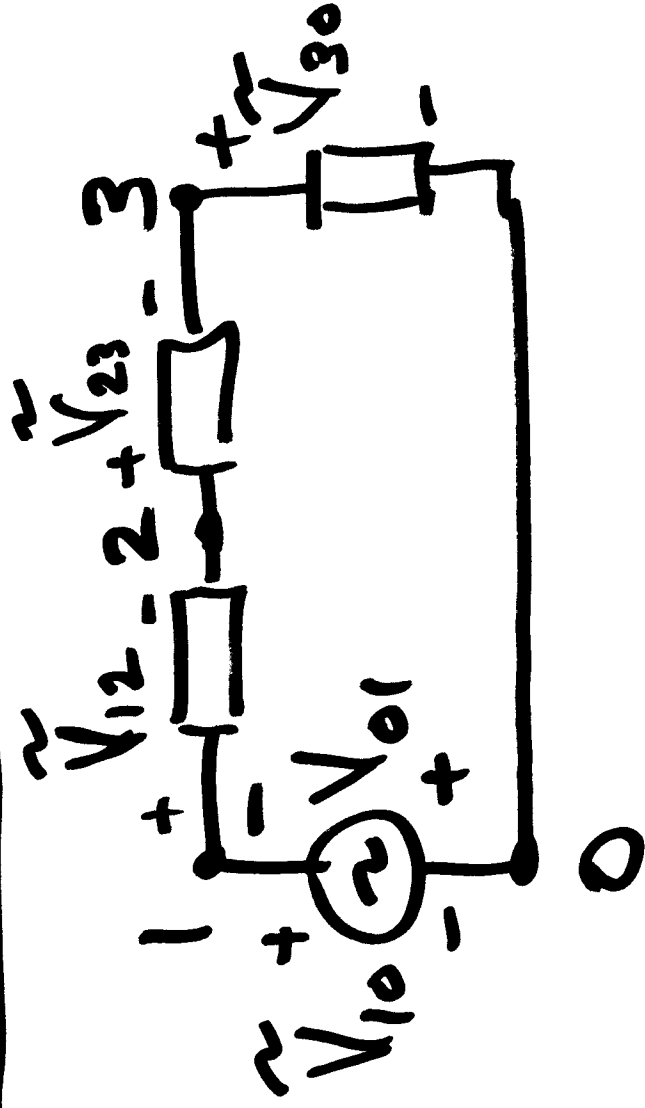

KVL: $\sum V_s = 0$ (Sum of V drops!)

starting at node 0:

$$-V_{10} + V_{12} + V_{23} + V_{30} = 0$$

$$V_{10} = V_{12} + V_{23} + V_{30}$$


Or: $0 = V_{10} + \underbrace{V_{12} + V_{23} + V_{30}}$

Phasor Analysis (use "cos reference") 6

see next 5

pages,
ins. 1 → ins. 5
for Euler's
Identity.

RMS Phasors

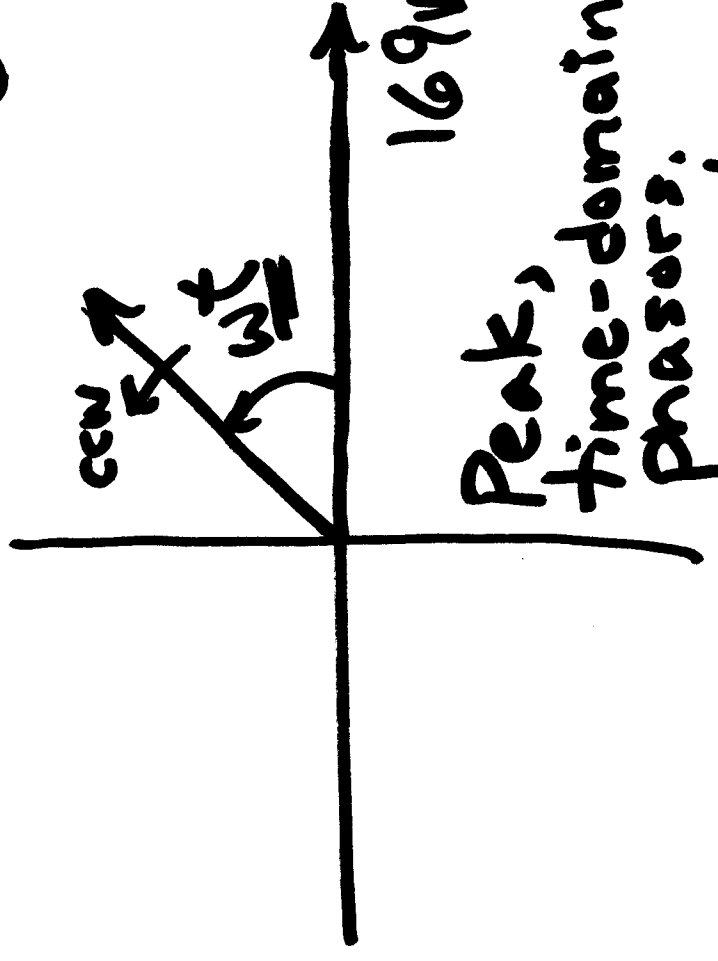


$\tilde{V} = \cancel{\# \cos \omega t} ?$

$v(t) = 120\sqrt{2} \cos \omega t$


$120 \angle 0^\circ$ VRMS

Phasors

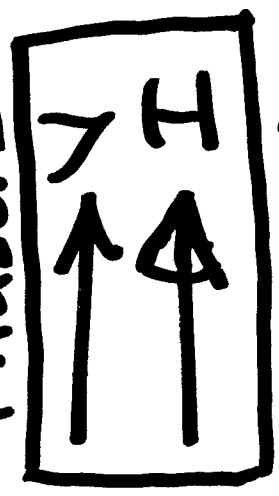

P, θ, S

V_{peak}

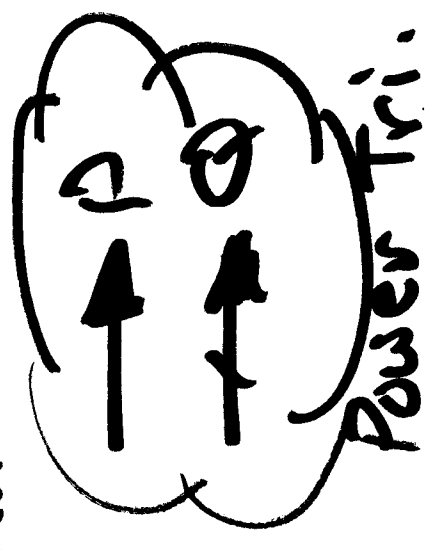


Power Tri.

Euler's Identity


ins. 1

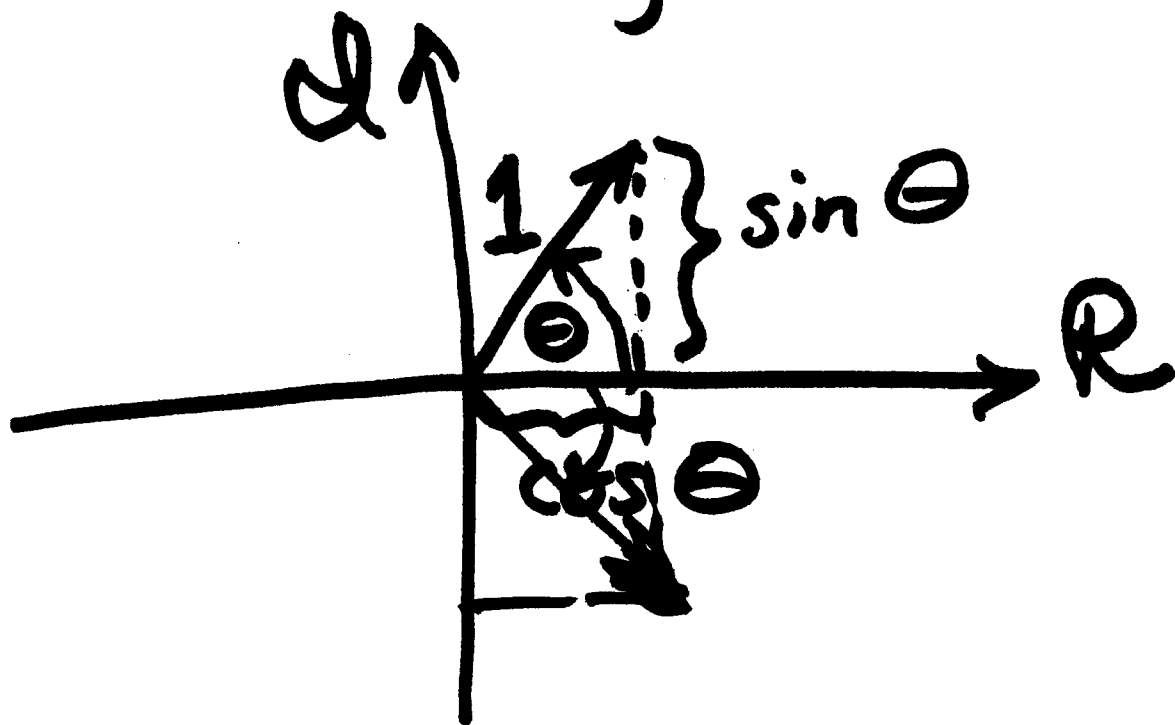$e^{j\theta} =$ Unit vector at
an angle θ .



$$\therefore e^{j\theta} = \cos \theta + j \sin \theta \quad (1)$$
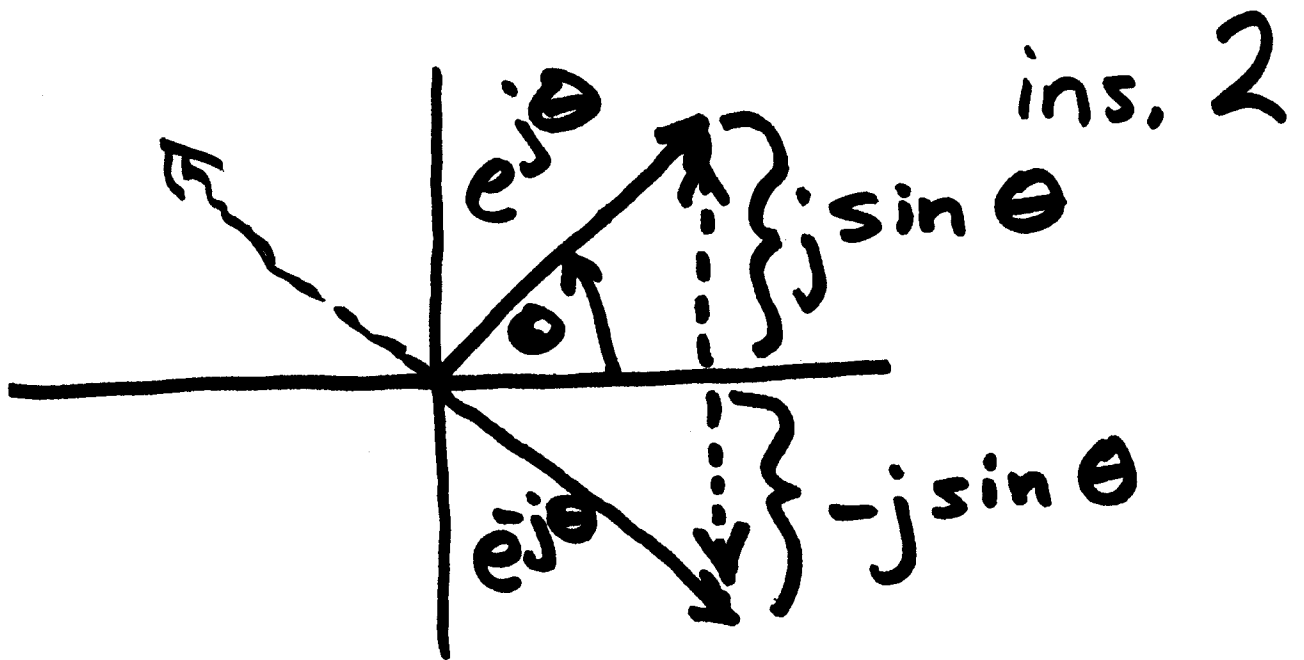
$$e^{-j\theta} = \cos \theta - j \sin \theta \quad (2)$$



If we add the 2 eqns

(1) + (2)


$$e^{j\theta} + e^{-j\theta} = 2 \cos \theta$$

$$\Rightarrow \boxed{\cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}}$$

Subtracting,

$$\boxed{\sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{j2}}$$

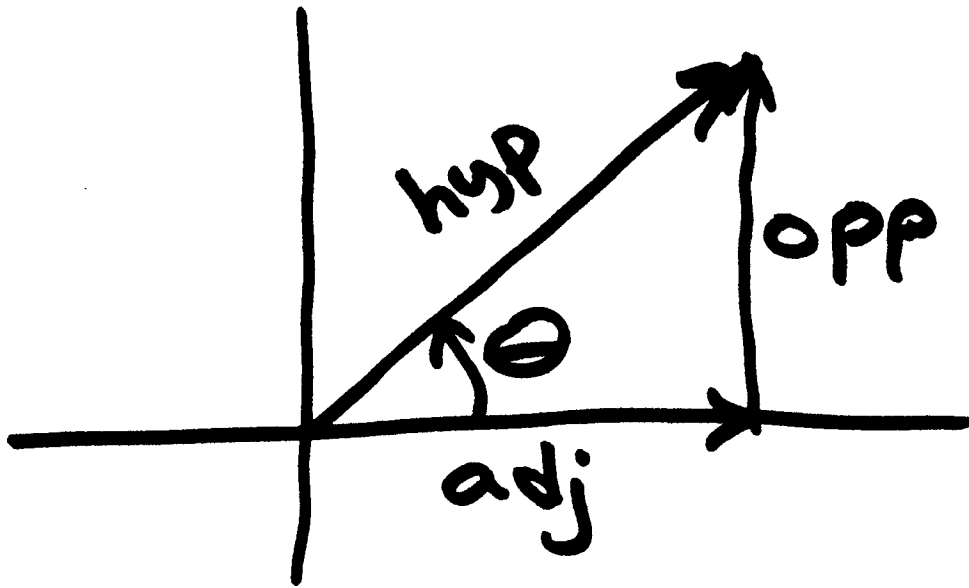Referring back to figure ^{ins, 3} on preceding page, this matches with the basic trig you learned:



$$\sin \theta = \frac{\text{opp}}{\text{hyp}} \quad \cos \theta = \frac{\text{adj}}{\text{hyp}}$$

$$\tan = \frac{\text{opp}}{\text{adj}} = \frac{\sin \theta}{\cos \theta}$$

Hyperbolic Functions are ^{ins.} 4 similar exponential functions, where the exponent of e is, in general, a complex number, $z = a + jb$

$$\begin{aligned}\sinh(z) &= \frac{e^z - e^{-z}}{2} \\ &= \frac{e^a e^{jb} - e^{-a} e^{-jb}}{2}\end{aligned}$$

$$\begin{aligned}\cosh(z) &= \frac{e^z + e^{-z}}{2} \\ &= \frac{e^a e^{jb} + e^{-a} e^{-jb}}{2}\end{aligned}$$

74 6.09 HYPERBOLIC FUNCTIONS

Elementary Functions

(1) Definitions

A hyperbolic function is a combination of e^x and e^{-x} and is introduced as follows:

Hyperbolic sine of $x = \sinh x = \frac{e^x - e^{-x}}{2}$


Hyperbolic cosine of $x = \cosh x = \frac{e^x + e^{-x}}{2}$

Hyperbolic tangent of $x = \tanh x = \frac{e^x - e^{-x}}{e^x + e^{-x}}$

Hyperbolic cotangent of $x = \coth x = \frac{e^x + e^{-x}}{e^x - e^{-x}}$

Hyperbolic secant of $x = \operatorname{sech} x = \frac{2}{e^x + e^{-x}}$

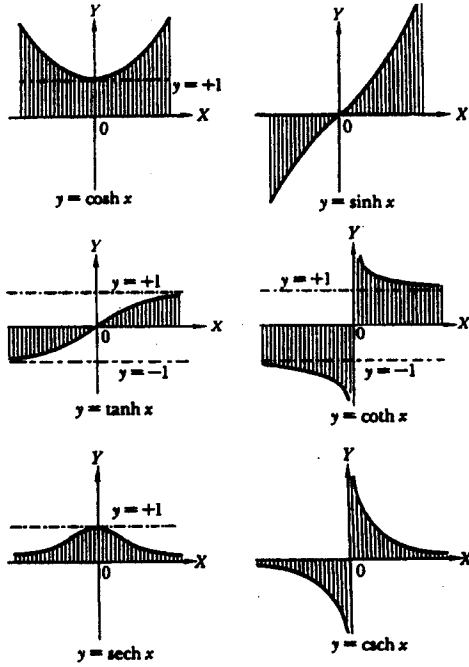Hyperbolic cosecant of $x = \operatorname{csch} x = \frac{2}{e^x - e^{-x}}$



Examples for real values of z :

~~z = a + jb~~
 $z = a + jb$
 $z = a + x$

(2) Relationships

$\cosh^2 x - \sinh^2 x = 1$
 $\tanh^2 x + \operatorname{sech}^2 x = 1$
 $\coth^2 x - \operatorname{csch}^2 x = 1$

$\tanh x = \frac{\sinh x}{\cosh x}$
 $\coth x = \frac{\cosh x}{\sinh x}$

$\operatorname{sech} x \cosh x = 1$
 $\operatorname{csch} x \sinh x = 1$
 $\tanh x \coth x = 1$

$\sinh(-x) = -\sinh x$
 $\operatorname{sech}(-x) = \operatorname{sech} x$

$\tanh(-x) = -\tanh x$
 $\coth(-x) = -\coth x$


$\cosh(-x) = \cosh x$
 $\operatorname{csch}(-x) = -\operatorname{csch} x$

(3) Limit Values

x	$\sinh x$	$\cosh x$	$\tanh x$	$\coth x$	$\operatorname{sech} x$	$\operatorname{csch} x$
$-\infty$	$-\infty$	$+\infty$	-1	-1	0	0
-1	-1.1752	$+1.5431$	-0.7616	-1.3130	$+0.6480$	-0.8509
0	0	$+1$	0	$\mp\infty$	$+1$	$\mp\infty$
$+1$	$+1.1752$	$+1.5431$	$+0.7616$	$+1.3130$	$+0.6480$	$+0.8509$
$+\infty$	$+\infty$	$+\infty$	$+1$	$+1$	0	0

7

$169 \cos \omega t$

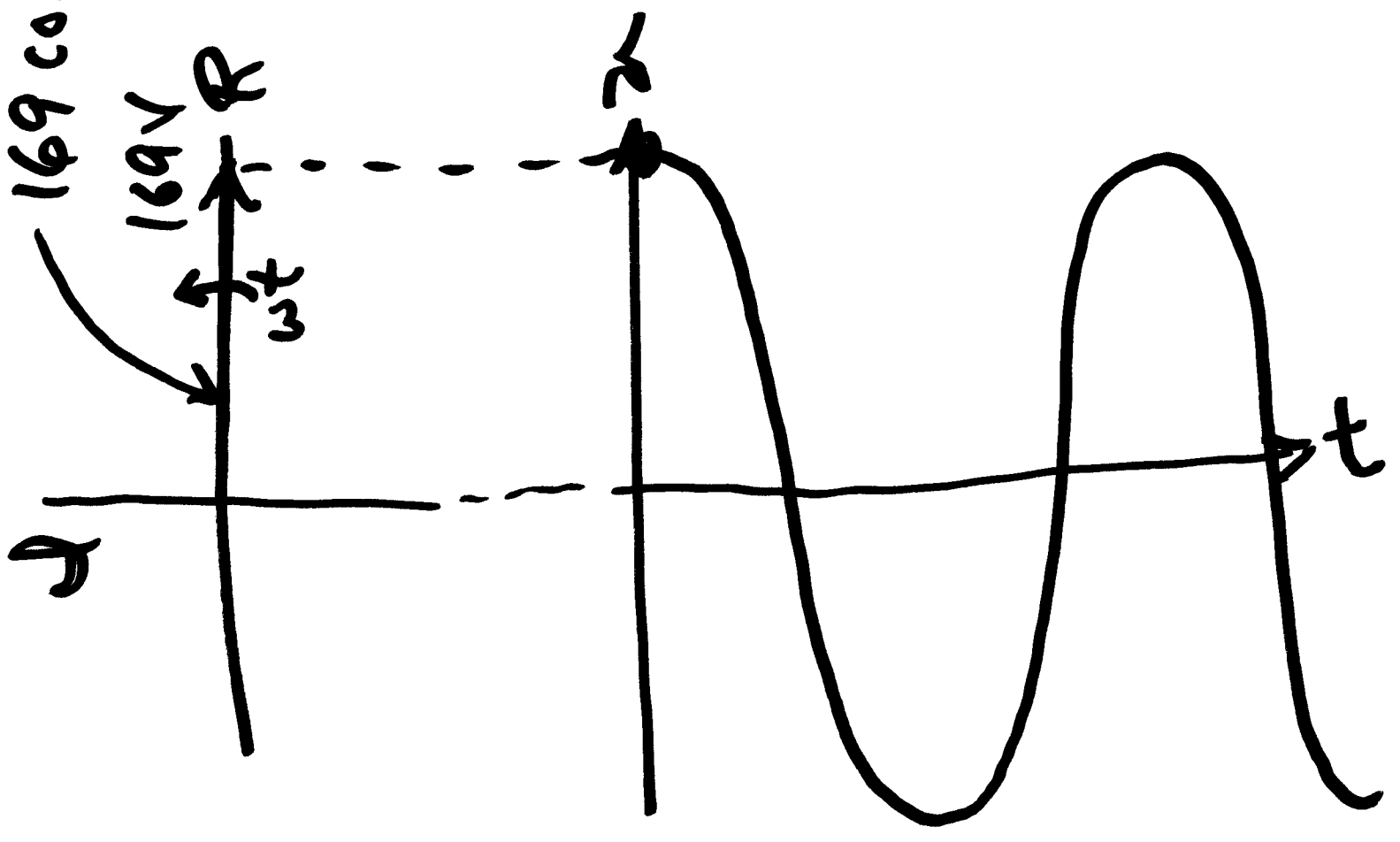

Three Phase Phasor Analysis 8



- Must deal with all Vs & Is

Don't!

- Say "Line Voltage"
- Say "Phase Voltage" unless you also say whether it is Δ or Y.

ALWAYS!

- Say V_{LN} or V_{LL}
- say I_{LINE} ($= I_{\phi}$ in Y)

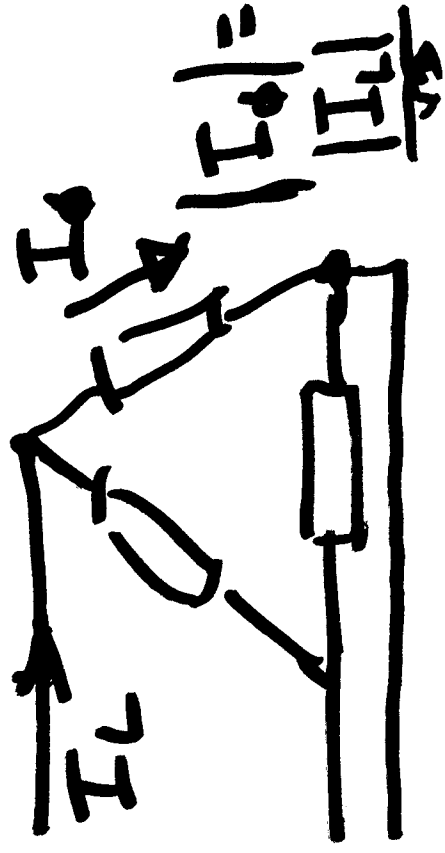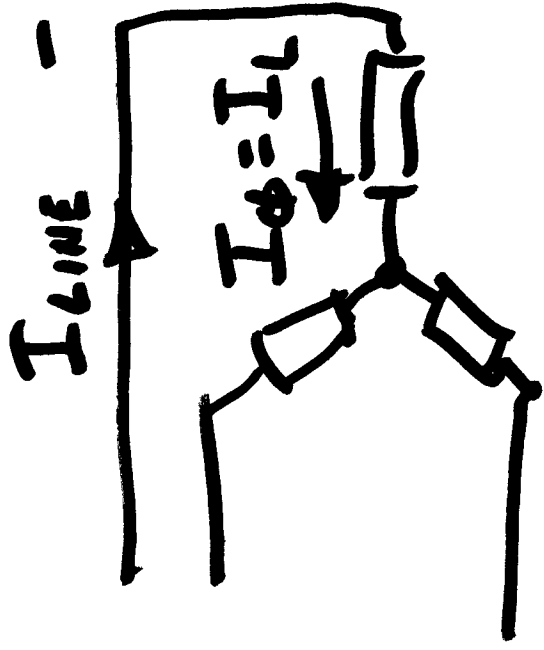

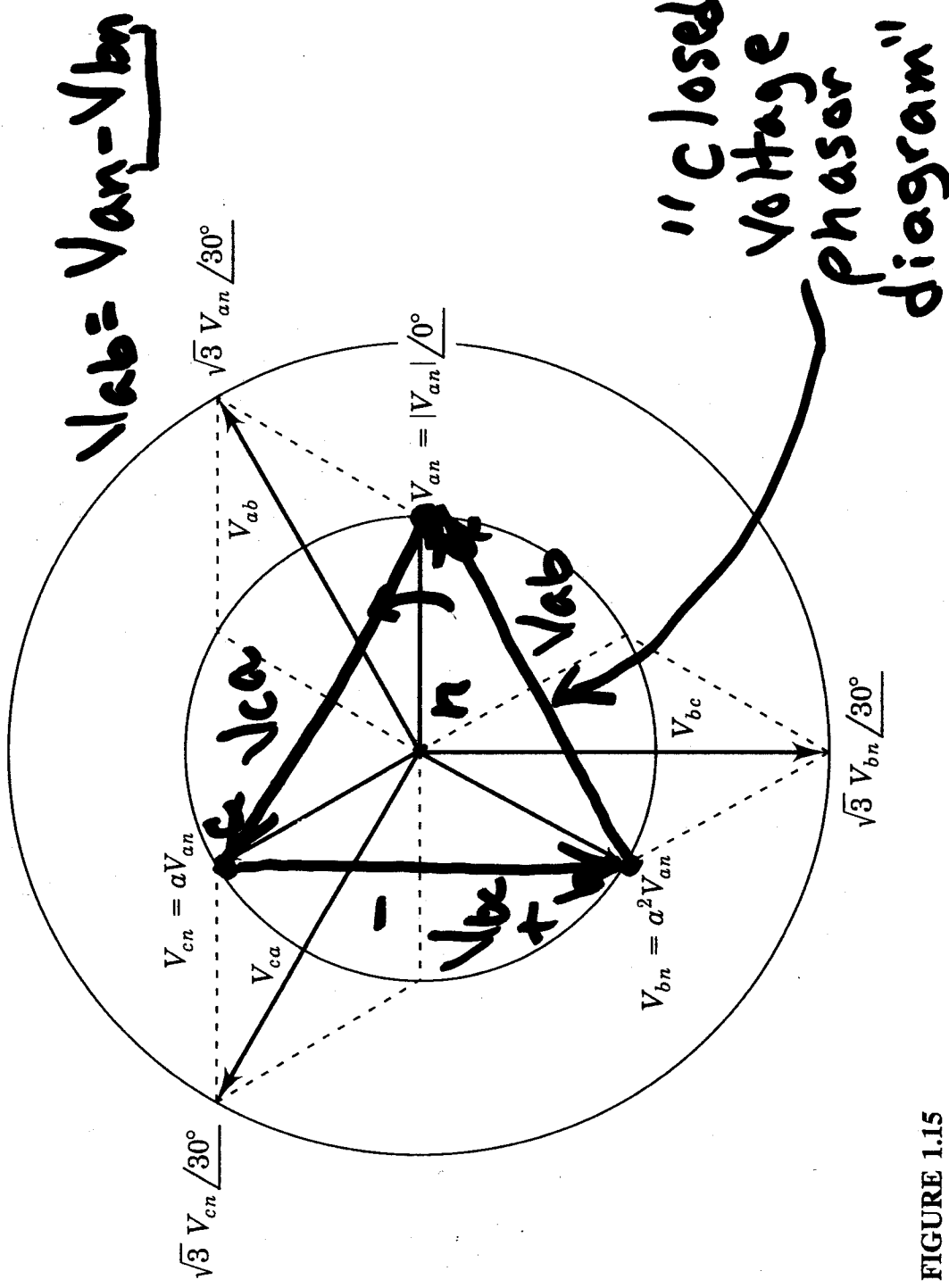


FIGURE 1.15

Phasor diagram of line-to-line voltages in relation to line-to-neutral voltages in a balanced three-phase circuit.

("open" voltage phasor diagram)

10

construction is mathematical correct, but not common practice!


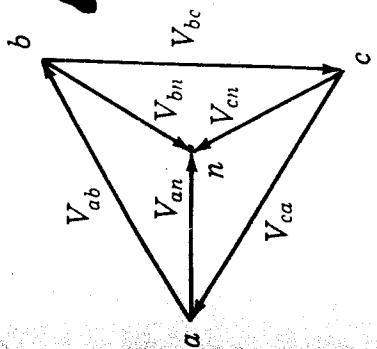


FIGURE 1.16 also Fig 1.17

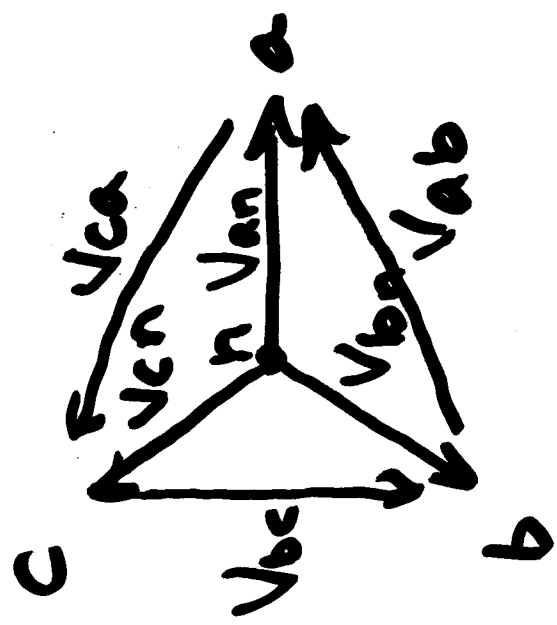Alternative method of drawing the phasors of Fig. 1.15.



"Correct" ← common practice.