




Topics for Today:

- Announcements
 - Everyone have a book now? 
 - Room B45 is open from 9am onward.
 - Office hrs: 1:30-2:30pm, Mon, Wed, Fri
 - Office: EERC 623. Phone: 906.487.2857
 - Ch.1 Solutions posted on web page. Finish by Sept. 5th.
 - Set of pre-req / review exercises given by tomorrow 
- Completing the Chapter 1 / Review:
 - Per Unit system
 - Symmetrical Components: a, [A], pos, neg, zero components
 - Sequence networks
- Chapter 2 - Transformers and circuits w/transformers 

2


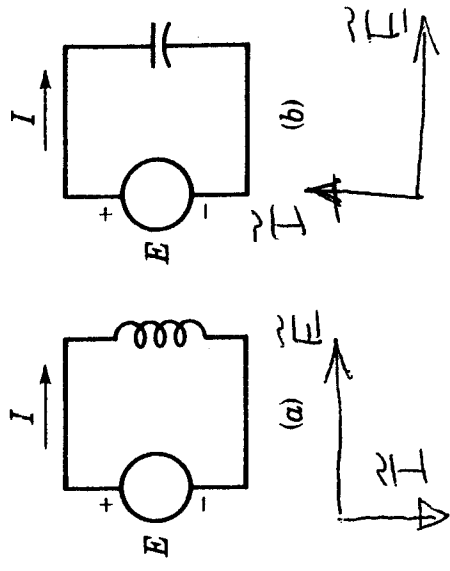
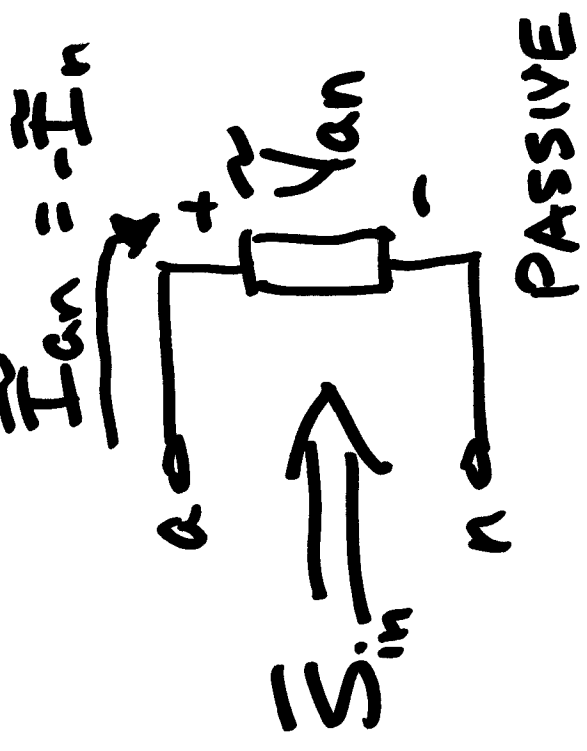


Figure 2.11 Alternating emf applied (a) to a purely inductive element and (b) to a purely capacitive element.

Table 2.1

Circuit diagram	Calculated from EI^*
<p>(Active)</p> <p>Generator action assumed</p> <p>SOURCE</p>	<p>$S = P + jQ$</p> <p>If P is +, emf supplies power If P is -, emf absorbs power If Q is +, emf supplies reactive power (I lags E) If Q is -, emf absorbs reactive power (I leads E)</p>
<p>(Passive)</p> <p>Motor action assumed</p> <p>LOAD</p>	<p>If P is +, emf absorbs power If P is -, emf supplies power If Q is +, emf absorbs reactive power (I lags E) If Q is -, emf supplies reactive power (I leads E)</p>

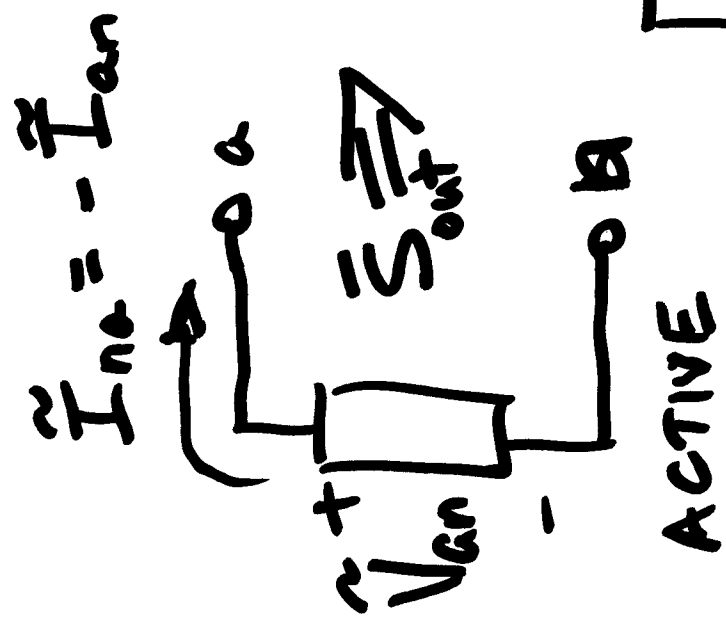


$$\tilde{S} = \tilde{V} \tilde{I}^* = P + jQ$$

But... How to apply?

$$\tilde{S}_{out} = \tilde{V}_{an} \tilde{I}_{na}^* = P_{out} + jQ_{out}$$

$$\tilde{S}_{in} = \tilde{V}_{an} \tilde{I}_{an}^* = P_{in} + jQ_{in}$$

Per Unit Quantities

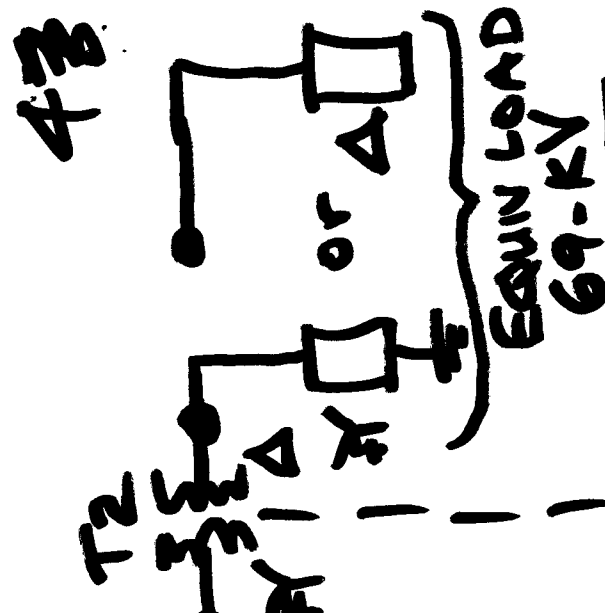

BASE	100 MVA	100 MVA	100 MVA
QTY	22 KV	345 KV	69 KV
SENSE	250 MVA	199.2 KV	39.8 KV
V _{LL}	26.24 A	167.4 A	836.7 A
V _{LN}	1515 A	96.6 A	483.1 A
I _{LINE}	4.84 Ω	1190 Ω	47.6 Ω
I _{φ, A}	14.5 Ω	3571 Ω	142.8 Ω
Z _L			
Z _Δ			

EXPLANATION OF BASE VALUES GIVEN ON FOLLOWING PAGES...

5

$$\text{Per Unit Value} = \frac{\text{"Actual Value"}}{\text{Base Value}} \text{ pu or P.u. or } \%$$

$$\text{P.u.} \times 100 = \%$$

Base MVA usually 100 MVA (Given)

Base Voltage: $V_{LL, \text{BASE}} = \frac{\text{Nominal VLL in a particular part/zone of system}}$

KEY Point:

$V_{LN, \text{BASE}} = \text{Nominal } V_{LN} \dots$


$$|S| = |3 \tilde{V}_\phi \tilde{I}_\phi^*| = 3 V_\phi I_\phi = \sqrt{3} V_{LL, \text{LINE}} = 3 V_{LN, \text{LINE}}$$

$$\therefore I_{\text{BASE, LINE}} = \frac{S_{3\phi}}{\sqrt{3} V_{LL}} = \frac{100 \times 10^6}{\sqrt{3} \times 345,000} = \underline{\underline{167.4 \text{ A}}}$$

ALONG

LINE

I_{LINE}

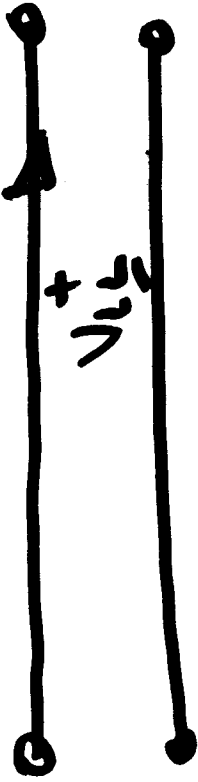

$$I_{BASE, LINE} = I_{\phi, WYE}$$

$$V_{BASE, LL} = V_{\phi, DELTA}$$

$$V_{BASE, LN} = V_{\phi, WYE}$$


$$I_{BASE, DELTA} = \frac{I_{BASE, LINE}}{\sqrt{3}}$$

$$Z_{BASE, WYE} = \frac{V_{LN}}{I_{LINE}} = \frac{199.2KV}{167.9} = 1190\Omega$$


IN EACH "ZONE"

$$Z_{B, \Delta} = \frac{\sqrt{3}L}{I_{\phi, \Delta}}$$

Sources, Loads,
XFERS, Rev. Equiv.

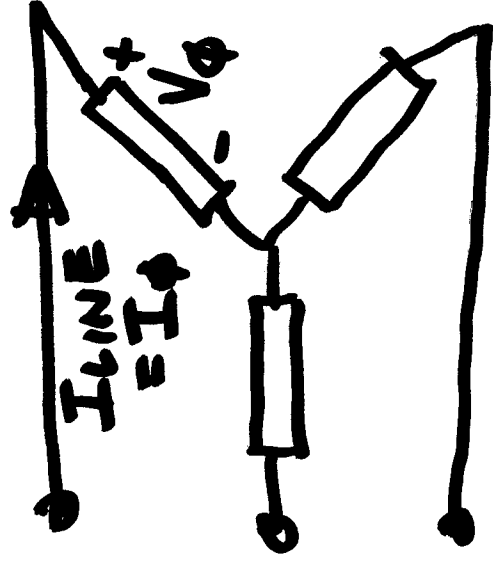


AT
WYE

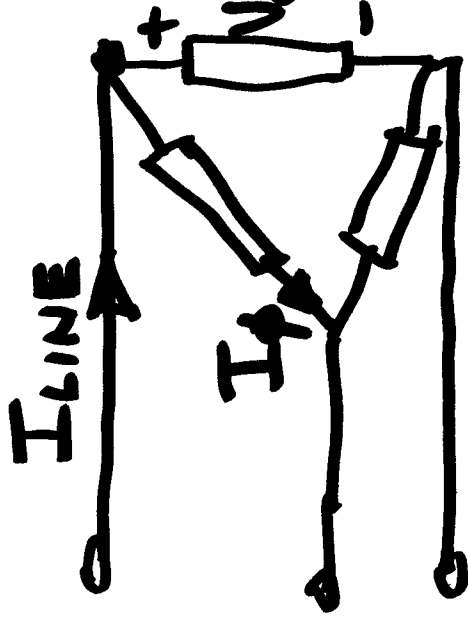

AT
DELTA

Transformers


7

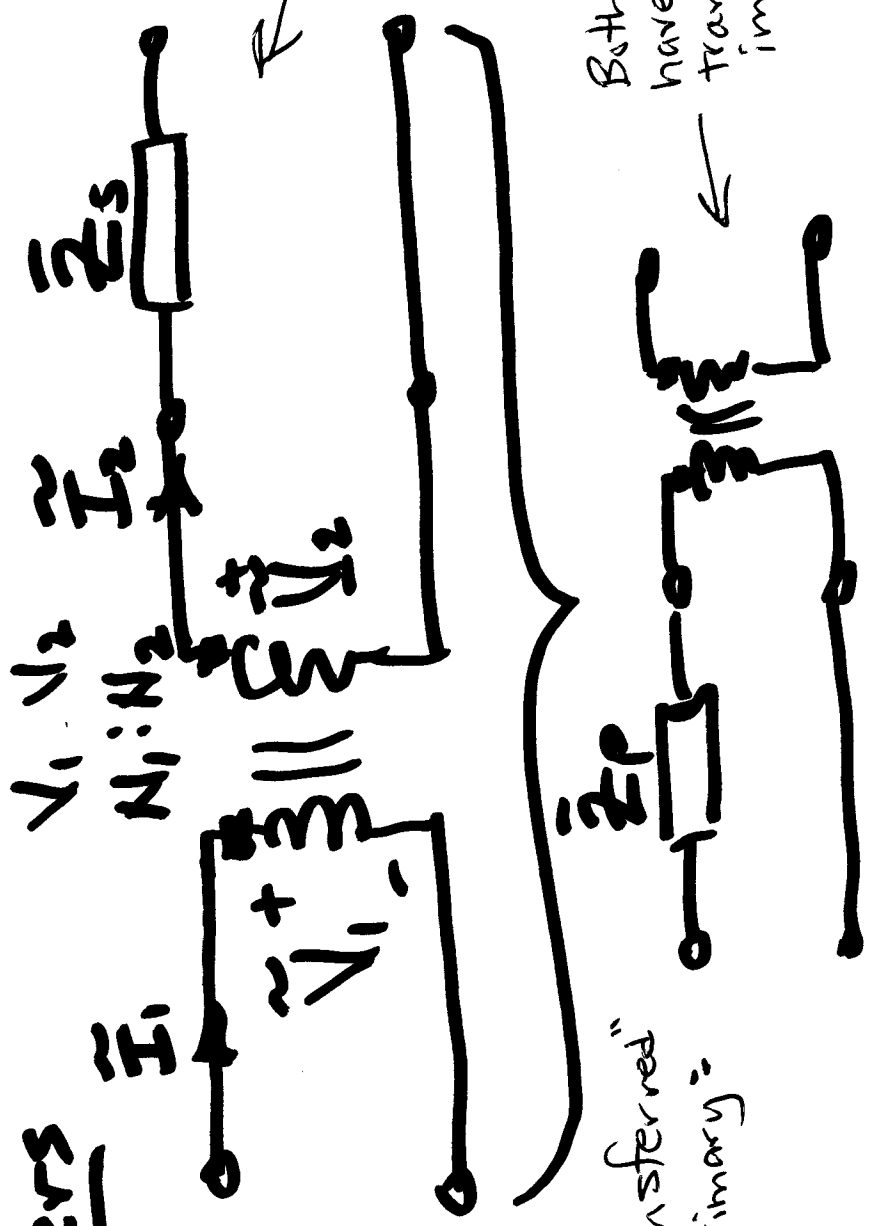

Z_s can be "transferred" or referred to primary:

Transferring Z_s to primary:
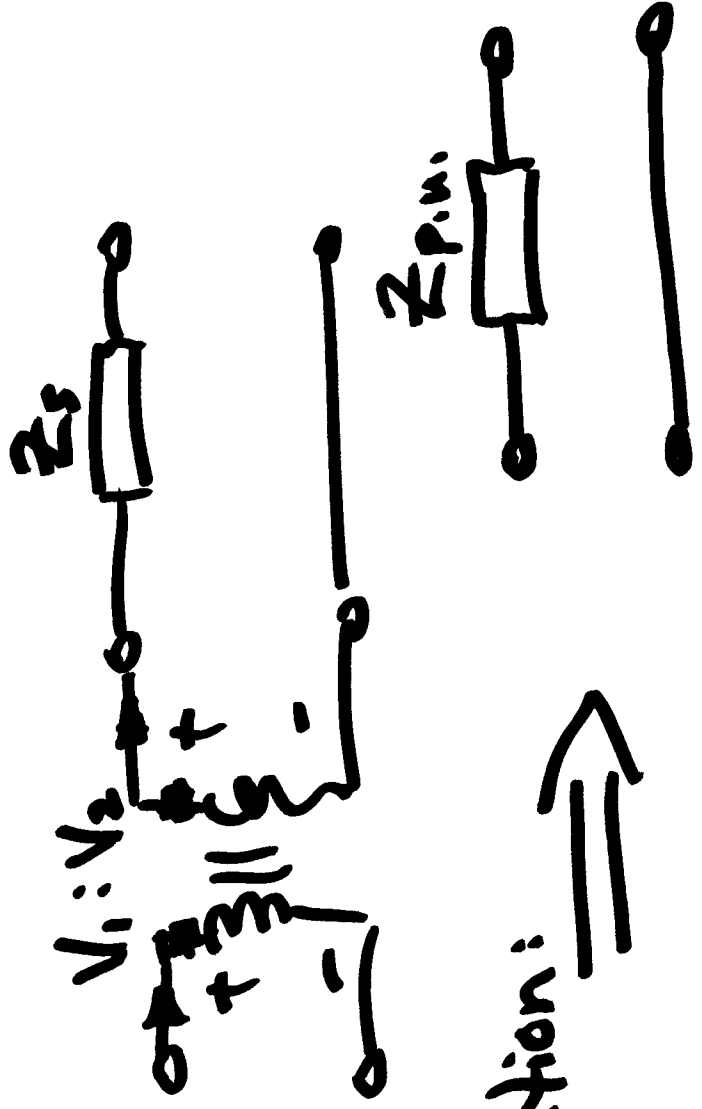
$$Z_p = Z_s \left[\frac{N_1}{N_2} \right]^2 = Z_s \left[\frac{V_1}{V_2} \right]^2$$



Per Unit Representation: \Rightarrow

Per unit V_s & I_s are same on each side, \therefore "get rid" of x_{fmr} when we do p.u. calculations.

Exception: phase shifts in Δ -Y x_{fms} , PS x_{fms} , etc.

Symmetrical Components







9

- Deal w/ unbalanced 3 ϕ situations.

- Real-world situation: unbalanced

load currents flowing thru system,

also unbalanced faults: L-G, L-L, L-L-G

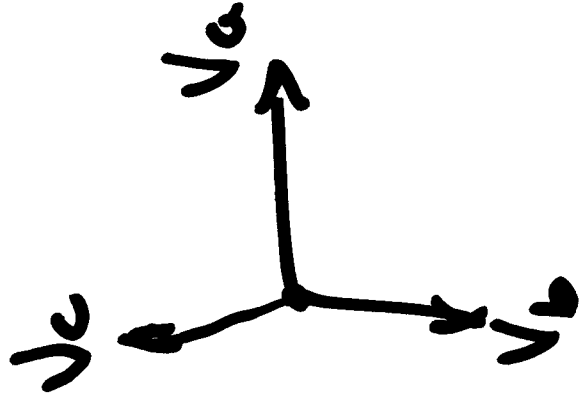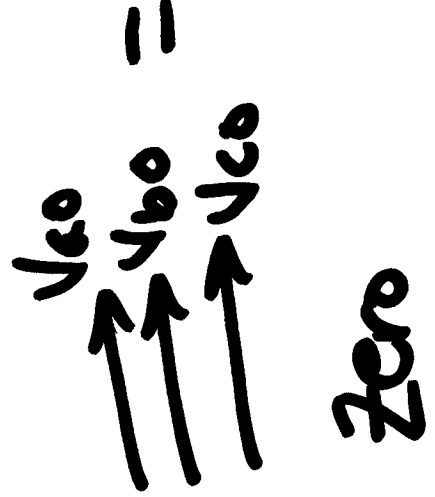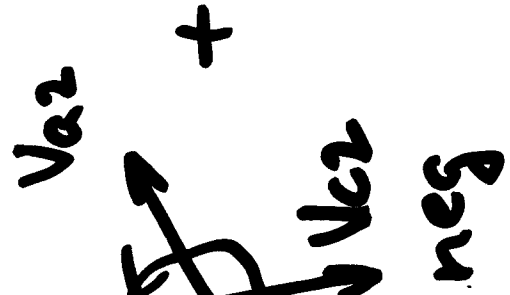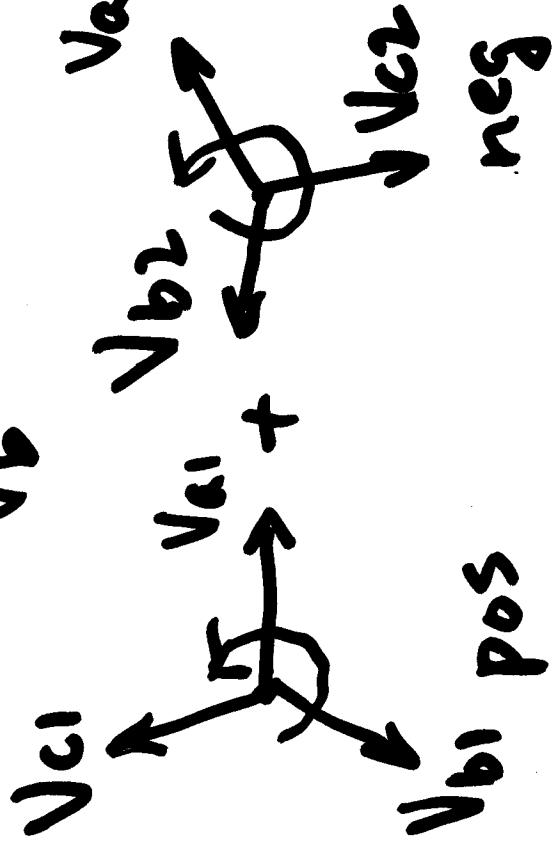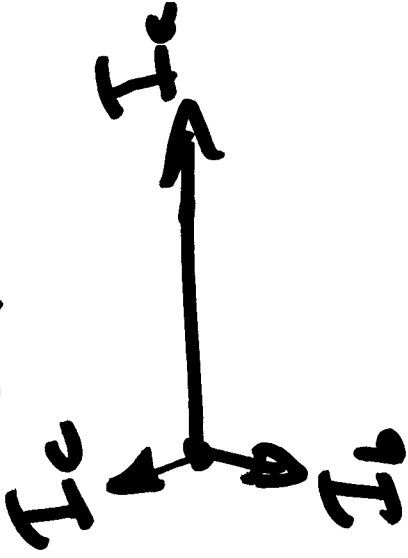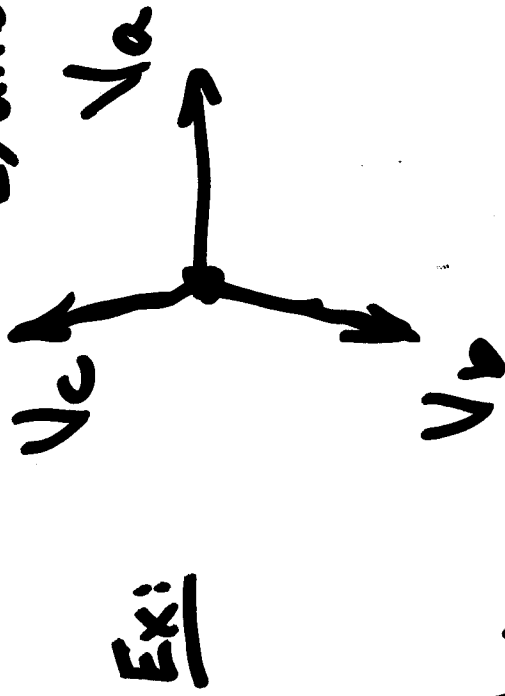

Per Phase Analysis is typical - no need to track ϕ_b & ϕ_c giv's if ϕ_a is known and each "group" (i.e. pos, neg, zero) is symmetric/balanced.

Convenience to define "a":

$$\begin{aligned} \tilde{V}_{b1} &= \tilde{V}_{a1} a^2 & \tilde{V}_{b2} &= \tilde{V}_{a2} a \\ \tilde{V}_{c1} &= \tilde{V}_{a1} a & \tilde{V}_{c2} &= \tilde{V}_{a2} a^2 \end{aligned}$$

$$\tilde{a} = 1 \angle 120^\circ$$

$$a = 1 \angle 120^\circ$$

$$a^2 = 1 \angle -120^\circ$$


$$\begin{aligned} \begin{bmatrix} \tilde{V}_a \\ \tilde{V}_b \\ \tilde{V}_c \end{bmatrix} &= \begin{bmatrix} \tilde{V}_{a0} + \tilde{V}_{a1} + \tilde{V}_{a2} \\ \tilde{V}_{b0} + \tilde{V}_{b1} + \tilde{V}_{b2} \\ \tilde{V}_{c0} + \tilde{V}_{c1} + \tilde{V}_{c2} \end{bmatrix} = \begin{bmatrix} \tilde{V}_{a0} + \tilde{V}_{a1} + \tilde{V}_{a2} \\ \tilde{V}_{a0} + a^2 \tilde{V}_{a1} + a \tilde{V}_{a2} \\ \tilde{V}_{a0} + a \tilde{V}_{a1} + a^2 \tilde{V}_{a2} \end{bmatrix} \end{aligned}$$

Note: $V_{a0} = V_{b0} = V_{c0}$

$$\begin{bmatrix} \bar{V}_c \\ \bar{V}_c \\ \bar{V}_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} \bar{V}_{a0} \\ \bar{V}_{a1} \\ \bar{V}_{a2} \end{bmatrix} = [A] \bar{V}_a$$

$$[V_P] = [A][V_S]$$

$$[I_P] = [A][I_S]$$

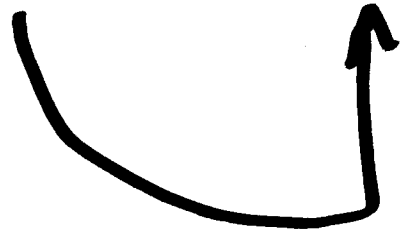

$$[A]^{-1}[V_P] = [A]^{-1}[A][V_S]$$



$$[V_S] = [A]^{-1}[V_P]$$

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix}$$

$$= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

i.e.


Sequence Networks
Per Phase, 4A.M, P.V.

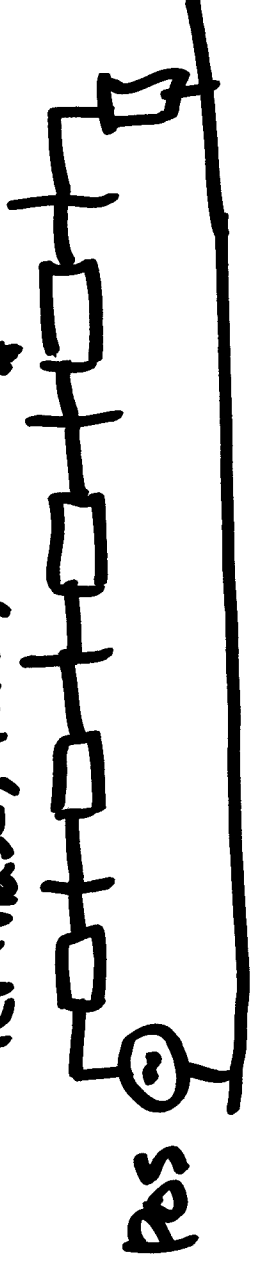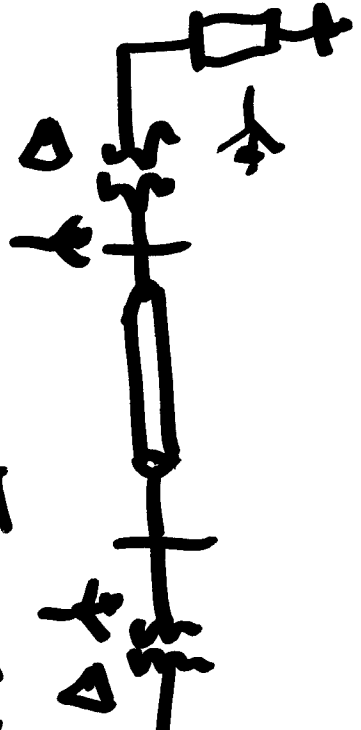


Pos



Neg

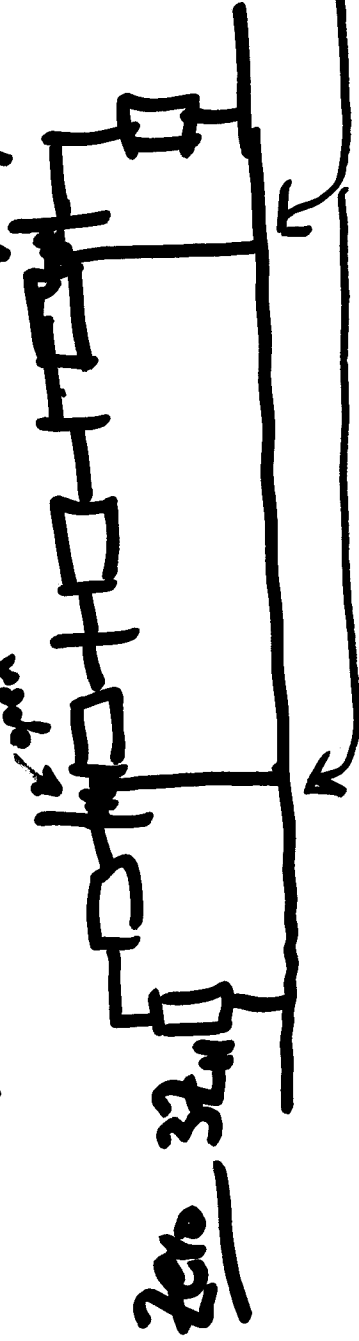

Zero

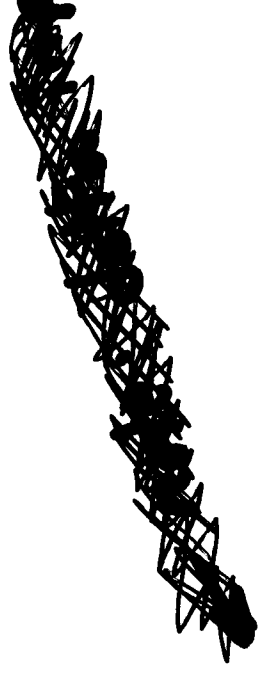

See details on next page.

From: Galo r & Sarma.
3rd Ed.

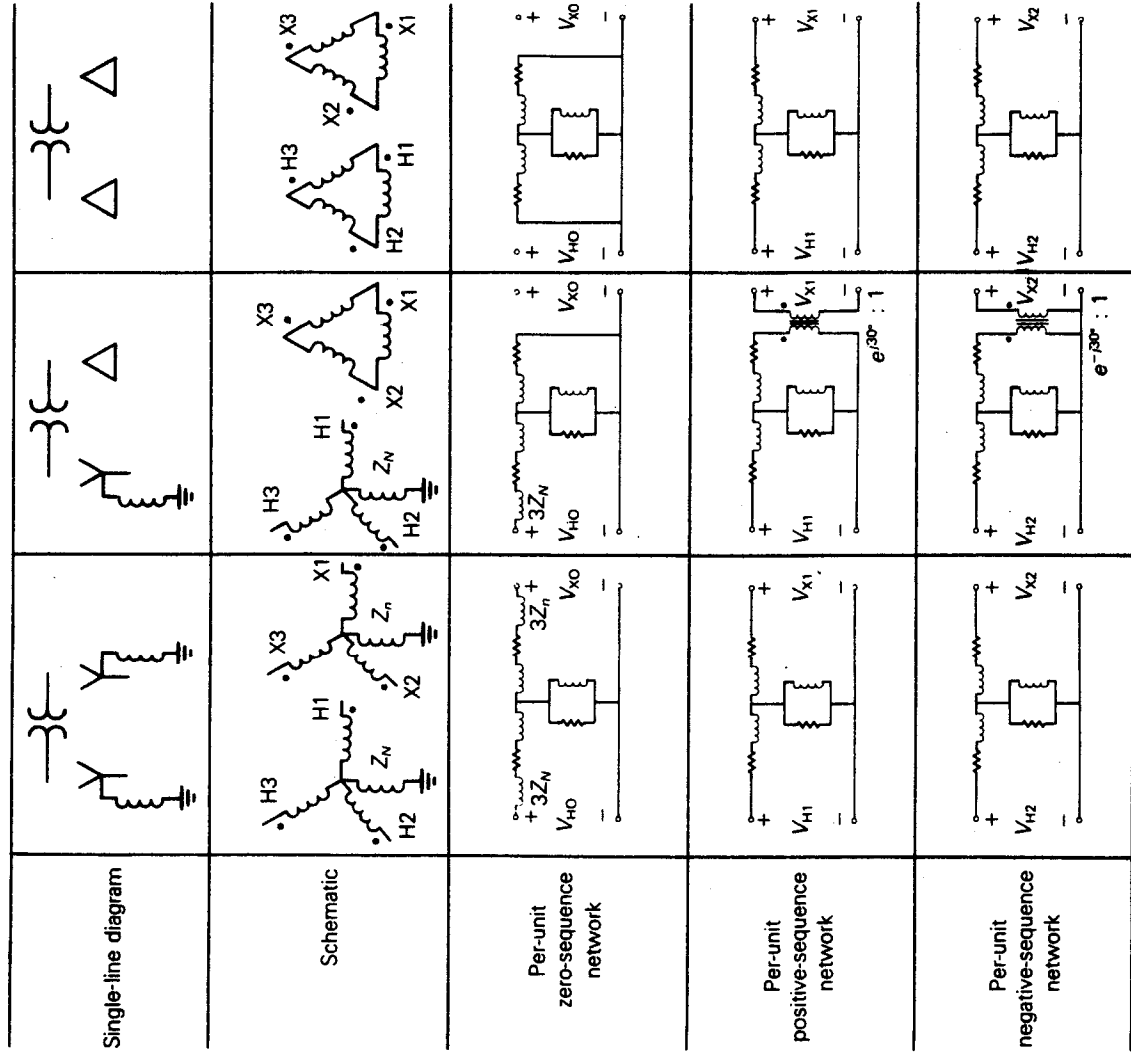


FIGURE 8.19 Per-unit sequence networks of practical Y-Y, Y-Delta, and Delta-Delta transformers

branches are also shown in Figure 8.19(a). Note that $(3Z_N)$ and $(3Z_{N'})$ have already been included in the zero-sequence network.

The per-unit positive- and negative-sequence transformer impedances of the practical Y-Y transformer in Figure 8.19(a) are identical, which is always true for nonrotating equipment. The per-unit zero-sequence network, how-

The per-unit sequence networks in Figure 8.19(b), have the following features:

1. The per-unit impedances do not depend on the winding connection. That is, the per-unit impedances for Y-Y, Y-Delta, Delta-Y, or Delta-Delta are the same.
2. A phase shift is included in the per-unit sequence networks. For the Delta-Delta connection, the phase shift is 30 degrees. For the Y-Delta and Delta-Y connections, the phase shift is 0 degrees.
3. Zero-sequence currents can flow in the per-unit sequence networks only if there is a zero-sequence current source in the network.

The phase shifts in the per-unit sequence networks are represented by the phase shifters in Figure 8.19(b) and (c). Also, the zero-sequence network is shown in Figure 8.19(c).

1. The positive- and negative-sequence currents are the same as those for the original network, but the zero-sequence current is zero.
2. Zero-sequence currents cannot flow in the per-unit sequence networks unless there is a zero-sequence current source in the network.

EXAMPLE 8.7 Solving unbalanced three-phase network using per-unit sequence components

A 75-kVA, 480-volt Delta/208-volt Y transformer is connected between the source and the load. The per-unit sequence impedances are $X_{eq} = 0.10$ pu. The zero-sequence impedance is neglected. Using the per-unit sequence networks and the

SOLUTION The base quantities are