

EE 5200 - Traveling Wave Example, Intro to ATP

Referring to: Chapter 6 notes - T-Line models
T-Lines considering, distributed z, y , traveling waves
ATP Quick Start Handout



- a. Pi-Equivalent circuit for long-line
- b. Characteristic Impedance Z_c
- c. Propagation Constant $\gamma = \alpha + j\beta$
- d. Surge-Impedance Loading (SIL)
- e. Wavelength, velocity
- f. Traveling waves, reflections
- g. Bounce diagrams (also called Bewley diagrams)

$$Z_c = \sqrt{\frac{Z}{Y}}$$

$$\gamma = \sqrt{ZY} = \alpha + j\beta$$

attenuation

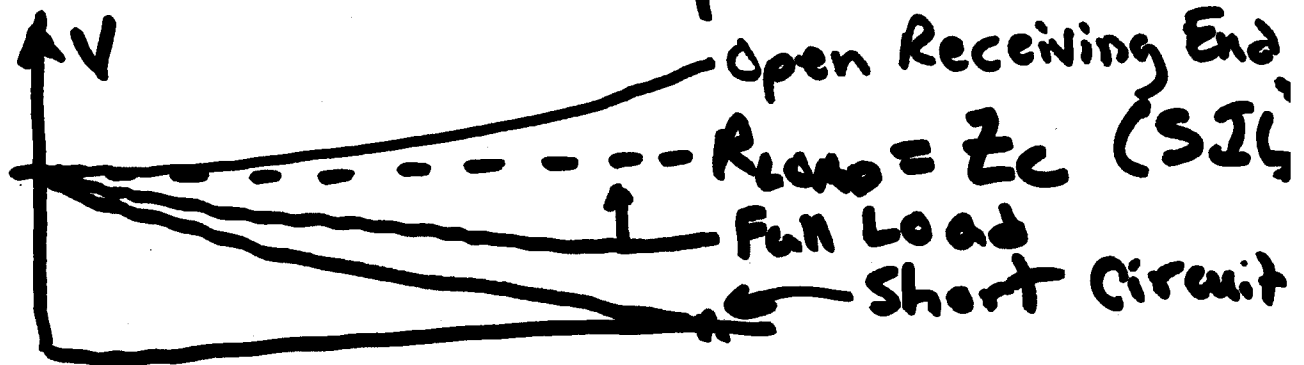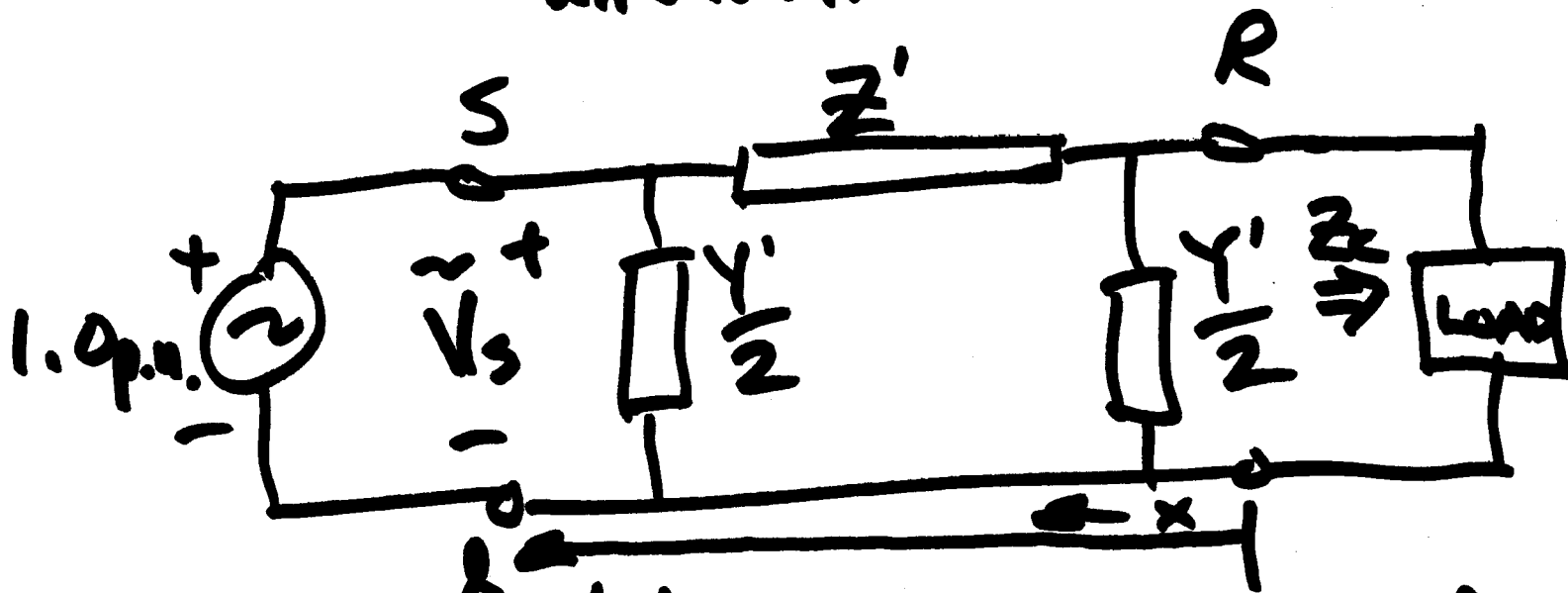Phase angle rotation
How a wave travels down line.



Another Point:

2

- SIL = Surge Impedance Loading

$$- R_{LOAD} = |Z_c|$$

- Total Reactive Power Consumed in Line = 0.


→ "Flat" Line or flat voltage profile.

$$- SIL = \frac{V^2}{Z_c} = \frac{V_s^2}{Z_c} = \frac{V_R^2}{Z_c}$$

Propagation Wavelength λ 3

λ = distance req'd to change $\angle V$ by 360° .

$$\gamma = \sqrt{ZY} = \alpha + j\beta \quad (\text{Assume Lossless})$$



$e^{j\beta x}$: term provides phase rotation in each term of $I(x)$, $V(x)$.

$$\lambda = x = \frac{2\pi}{\beta} \Rightarrow \lambda = \frac{2\pi}{\omega\sqrt{LC}} = \frac{2\pi}{2\pi f\sqrt{LC}}$$

$\lambda = \frac{1}{f\sqrt{LC}}$

$$v = f\lambda = \frac{1}{\sqrt{LC}} = 3 \times 10^8 \text{ m/s} = \frac{1}{\sqrt{\epsilon_0 \mu_0}}$$

$$\text{@ } 60 \text{ Hz, } \lambda = \frac{v}{f} = \frac{3 \times 10^8 \text{ m/s}}{60} \quad 4$$

$$\approx 5000 \text{ km}$$

$$\approx 3100 \text{ miles}$$

$$\text{@ } 2 \text{ MHz, } \lambda = \frac{3 \times 10^8}{2 \times 10^6} = 150 \text{ m}$$


- Side Comments (later) on
* T-Line loading limits

- Thermal

- Voltage Limits, $V_S \neq V_R \Rightarrow V_R$
 $.95 < V < 1.05$

- Stability Limits


Travelling Waves

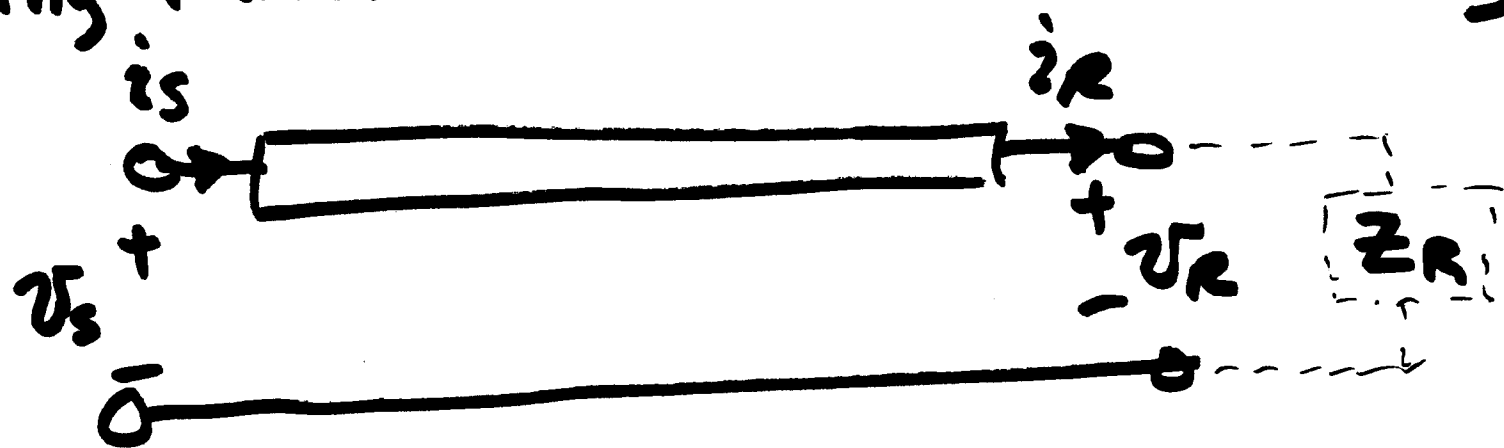

Impedance at receiving end:

$$Z_R = \frac{v_R}{i_R} = \frac{v_R^+ + v_R^-}{i_R^+ + i_R^-} = \frac{v_R^+ + v_R^-}{\frac{v_R^+}{Z_c} - \frac{v_R^-}{Z_c}} = Z_R$$
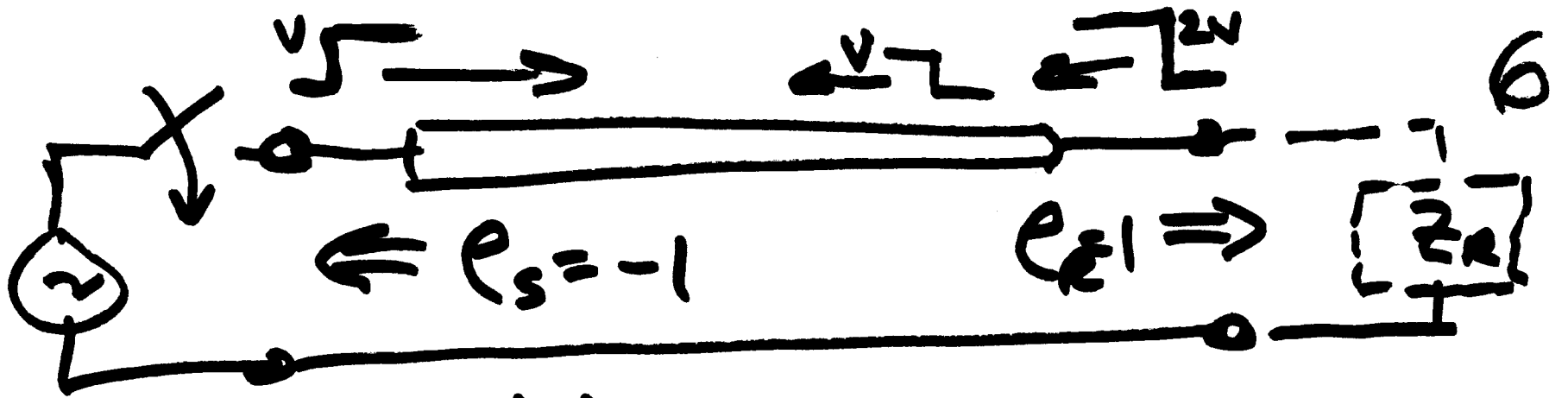
$$\frac{v_R^-}{v_R^+} = \frac{Z_R - Z_c}{Z_R + Z_c} = \rho_{LR} \quad \text{Reflection Coefficient}$$



If receiving end is...

- Open-ckt (i.e. $Z_R = \infty$)

$$P_R = \frac{\infty - Z_c}{\infty + Z_c} = +1$$

$$\therefore V_R^- = V_R^+ P_R = V_R^+$$

- Short-ckt (i.e. $Z_R = 0$)

$$P_R = \frac{0 - Z_c}{\infty + Z_c} = -1$$

$$V(x) = \left(\frac{V_R + Z_C I_R}{2} \right) e^{\gamma x} + \left(\frac{V_R - Z_C I_R}{2} \right) e^{-\gamma x} \quad (1)$$

$$I(x) = \left(\frac{V_R + Z_C I_R}{2} \right) e^{\gamma x} - \left(\frac{V_R - Z_C I_R}{2} \right) e^{-\gamma x}$$

best for
Trav. Waves. →

$$Z_C = \sqrt{\frac{Z}{y}} = \text{Characteristic Impedance.}$$

$$\gamma = \sqrt{zy} = \alpha + j\beta = \text{Propagation Coefficient}$$

α = attenuation constant

β = angular propagation constant.

(From Lecture 13)

Traveling Wave Example (ATPDraw) 7

~~See page 14, Lecture 13~~

$$Z_c = 294.3 \angle -9.22^\circ \Omega$$

$$\gamma = .00215 \angle 80.8^\circ = \frac{0.00034}{\alpha} + j \frac{0.00212}{\beta}$$

250-miles long

$$\begin{aligned} z &= 0.2 + j0.6 \Omega/\text{mi} \\ y &= j7.3 \mu\text{S}/\text{mi} \end{aligned}$$

$$\Rightarrow \left. \begin{aligned} L &= 0.398 \text{ H} \\ C &= 484 \mu\text{F} \\ R &= 50 \Omega \end{aligned} \right\} \text{Total}$$

If losses are ignored,

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi \text{ rad}}{.00209 \text{ rad}/\text{mi}}$$


$$= 3006 \text{ mi}$$

$$\left[\begin{aligned} Z_c &= 286.69 \Omega \\ \gamma &= j0.00209 \text{ rad}/\text{mi} \\ (\alpha &= 0) \end{aligned} \right. \begin{matrix} \uparrow \\ \beta \end{matrix}$$

250-mi Line

$$z = 0.2_r + j0.6_x \Omega/\text{mi}$$

$$y = j7.3 \mu\text{S}/\text{mi}$$

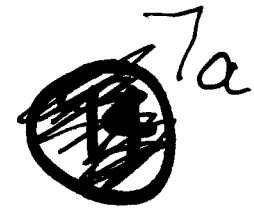

0° for lossless

a) $z_c = \sqrt{\frac{z}{y}}$ $294.3 \angle -9.22^\circ \Omega$

Note: Very typical for H.V. old line to have $300 < z_c < 350$

b) $\gamma = \sqrt{zy}$
 $= .00215 \angle 80.8^\circ$
 $= .00034 + j.00212$
 $\alpha \quad \beta$

90° for lossless.

Typical: $\frac{x}{R}$ ratio $\cong 20$ for E.H.V. Line

Before creating ATP example, let's predict behavior:

8

Lossless: $\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{.00209} = 3006 \text{ mi}$


$f\lambda = v = 2.9 \times 10^8 \text{ m/s}$ ($f = 60 \text{ Hz}$)
 \leftarrow (should be 3×10^8 ... rounding.)

Propagation Time: Approx:

$$t = \frac{x}{v} = \frac{(250 \text{ mi})(1.6 \text{ km/mi})}{2.9 \times 10^6 \text{ km/s}} = \boxed{138 \mu\text{s}}$$

250-mile transmission line example - traveling wave model in ATP


TravWave.adp

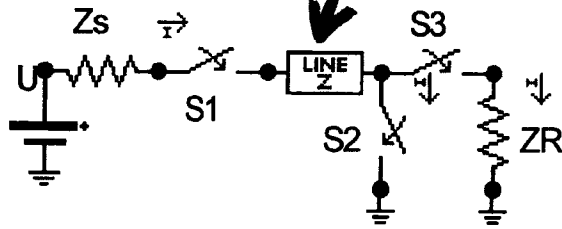

Select Distributed 1-phase Clarke Line Model.

Input (click Help button):

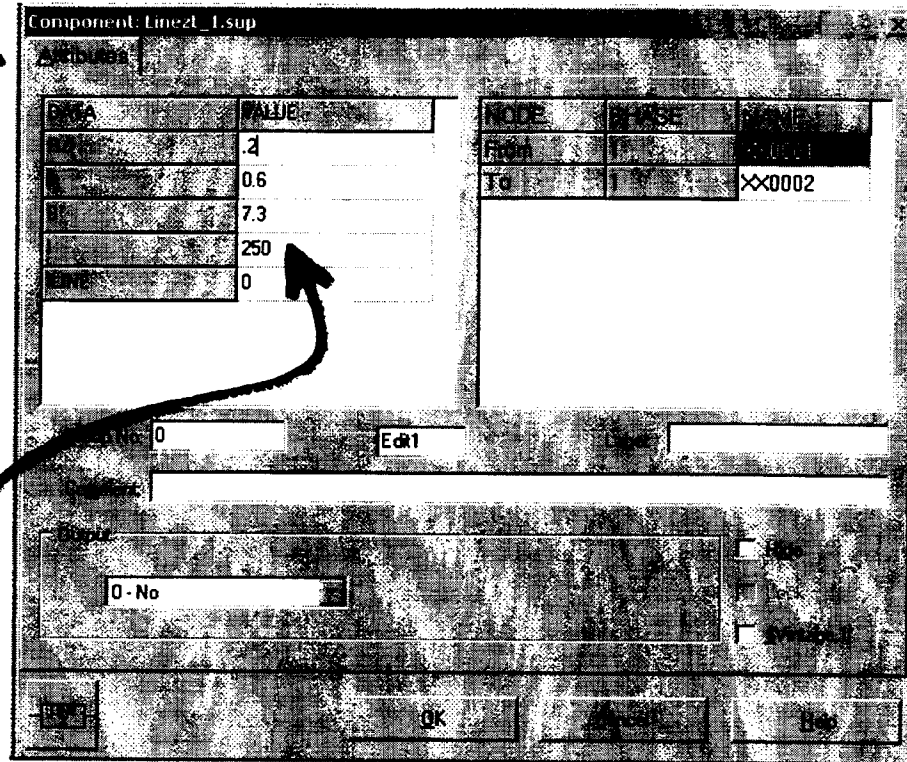- ILINE option: 0
- $R/l = 0.2$ Ohms/mi
- $A = j0.6$ Ohms/mi
- $B = 7.3$ μ S/mi
- l (length) = 250 mi



$$z = 0.2 + j0.6 \text{ Ohms/mi}$$

$$y = j7.3 \mu\text{S/mi}$$

$$Z_C = 294.3 \angle -9.22^\circ \text{ Ohms}$$

$$\gamma = 0.00215 \angle 80.8^\circ / \text{mi}$$

Ref: EE5200 notes, Lectures 13 and 14.

Name : LINEZT_1 - Distributed parameters, single phase

Card : BRANCH

Data : R/= Resistance pr. length in [Ohm/m]

The lossless part can be described in three ways

0. Inductance L' in [mH/m] if Xopt=0 or in [ohm/m] if Xopt=power frequency

Capacitance C' in [uF/m] if Copt=0 or in [uMho/m] if Copt=power frequency

1. Modal surge impedance in [ohms]; Z=sqrt(L'/C')

Modal propagation velocity in [m/s]; v=1/sqrt(L'*C')

2. Modal surge impedance in [ohms]

Modal propagation time in [s]; T=sqrt(L'*C')*length

Xopt. and Copt. are set in menu: ATP/Settings/Simulation.

The user can choose conductance modeling G=0 (the usual case) and G=R*C/L (distortionless)

length=length of line in [m]

Node : From= Start node of line

To= End node of line

SENDING
RECEIVING


Only branch voltage output is reliable.

RuleBook: IV.D.1

HELP

First Case: Lossless. $Z_s = 0$; Receiving end open-circuited.

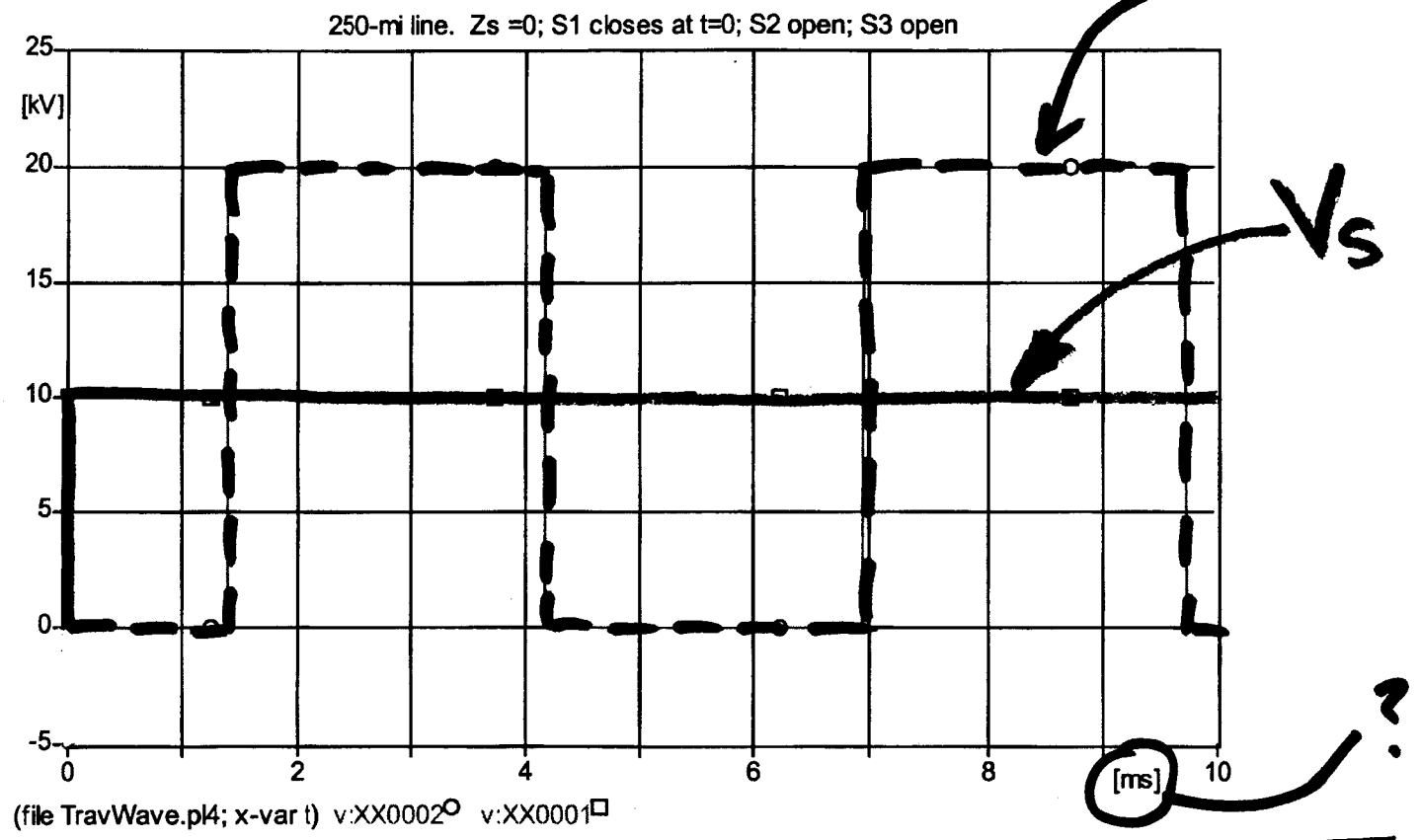Predicted propagation time (rough calculation): 138 μ s.




Actual propagation time: 139 μ s.

$\rho_s = -1, \rho_R = +1$

Second Case: $R=0.2$ Ohm/mi; $Z_s = 0$; Receiving end open-circuited.

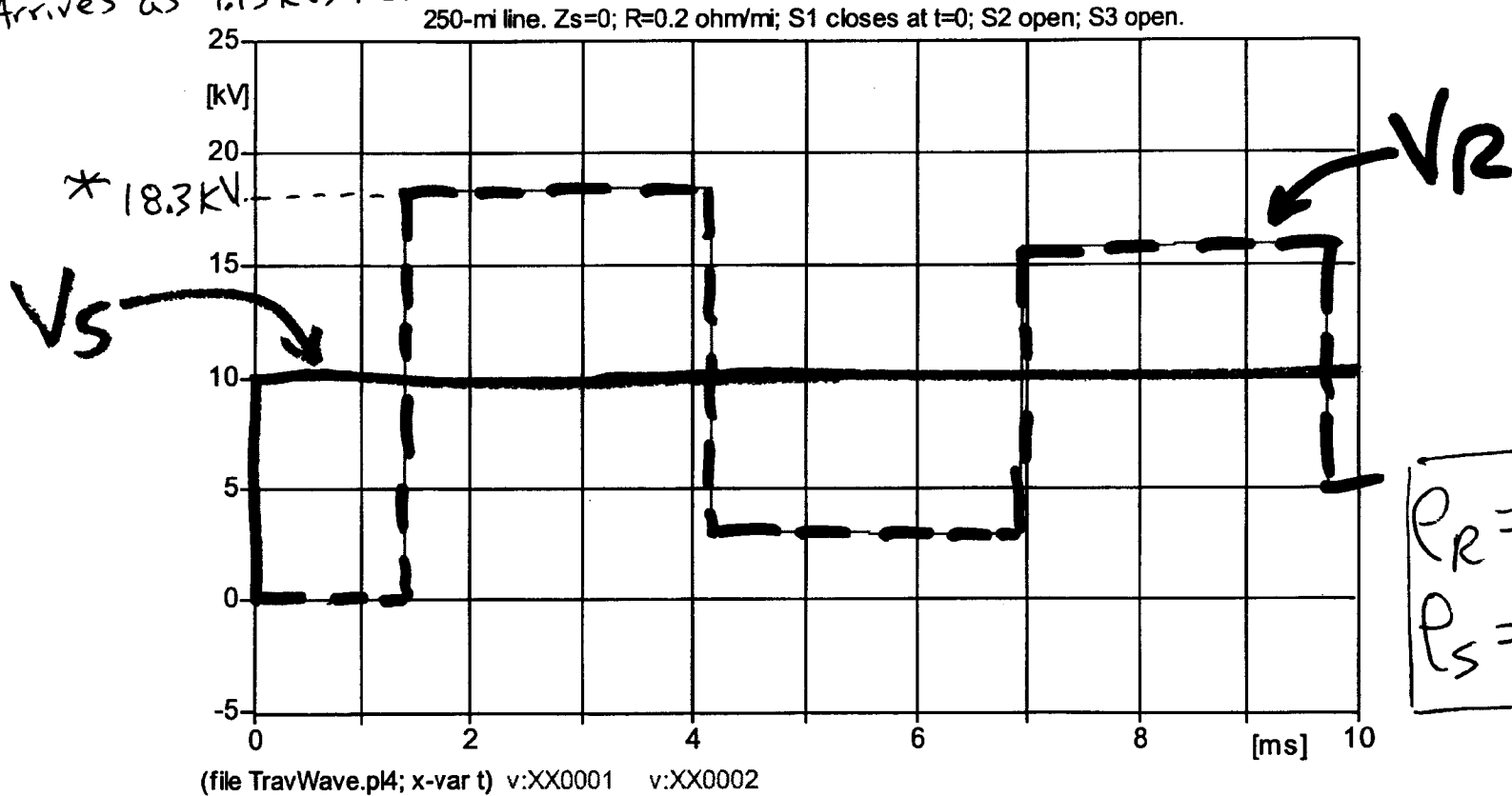* 10-kV wave is attenuated 8.5%.
 Arrives as 9.15 kV, reflection doubles it, to 18.3 kV.



* Note: Attenuation of voltage wave is $\alpha \times l$
 $= (0.00034/\text{mi})(250\text{mi}) = 0.085$ or 8.5%
 i.e. Mag at end of line is only 91.5%.

Close look at $\gamma = \alpha + j\beta$

11a
~~11a~~

$$\begin{aligned}\gamma &= \sqrt{ZY} = \sqrt{(.2 + j.6) \Omega/\text{mi} * j7.3 \mu\text{S}/\text{mi}} \\ &= .00034 / \text{mi} + j0.00212 \text{ rad}/\text{mi} \\ &= \underbrace{.00034 \frac{\text{neper}}{\text{mi}}}_{\text{attenuation}} + j0.00212 \text{ rad}/\text{mi}\end{aligned}$$


Tells us how much attenuation/mi
the wave will experience.

$$\begin{aligned}\text{For } 250 \text{ mi: } \text{Atten} &= (.00034 \frac{\text{neper}}{\text{mi}})(250 \text{ mi}) \\ &= 0.085 \text{ or } 8.5\%.\end{aligned}$$


"Bounce Diagrams"

Refer to end of Lecture 14 notes...

11b 

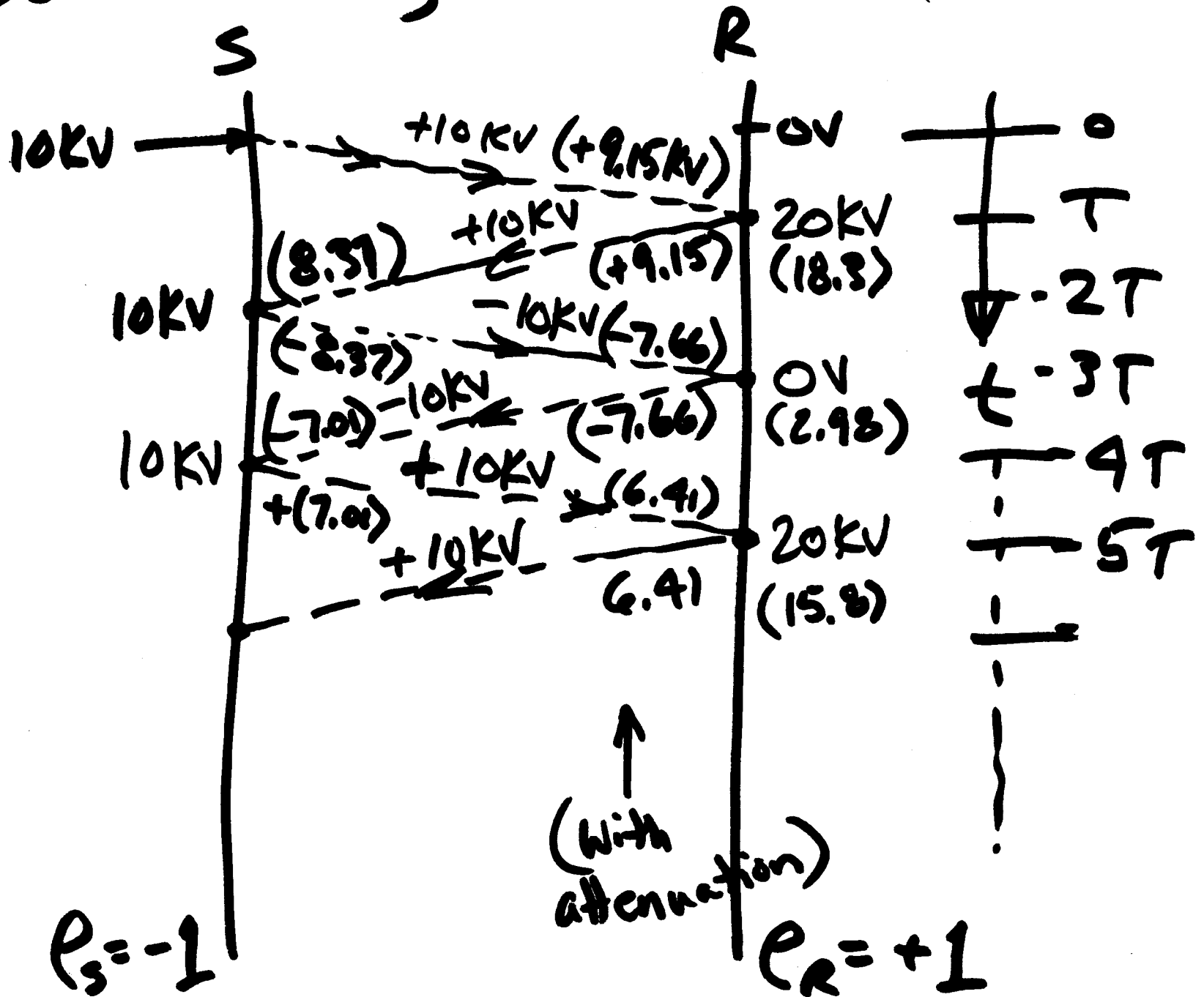

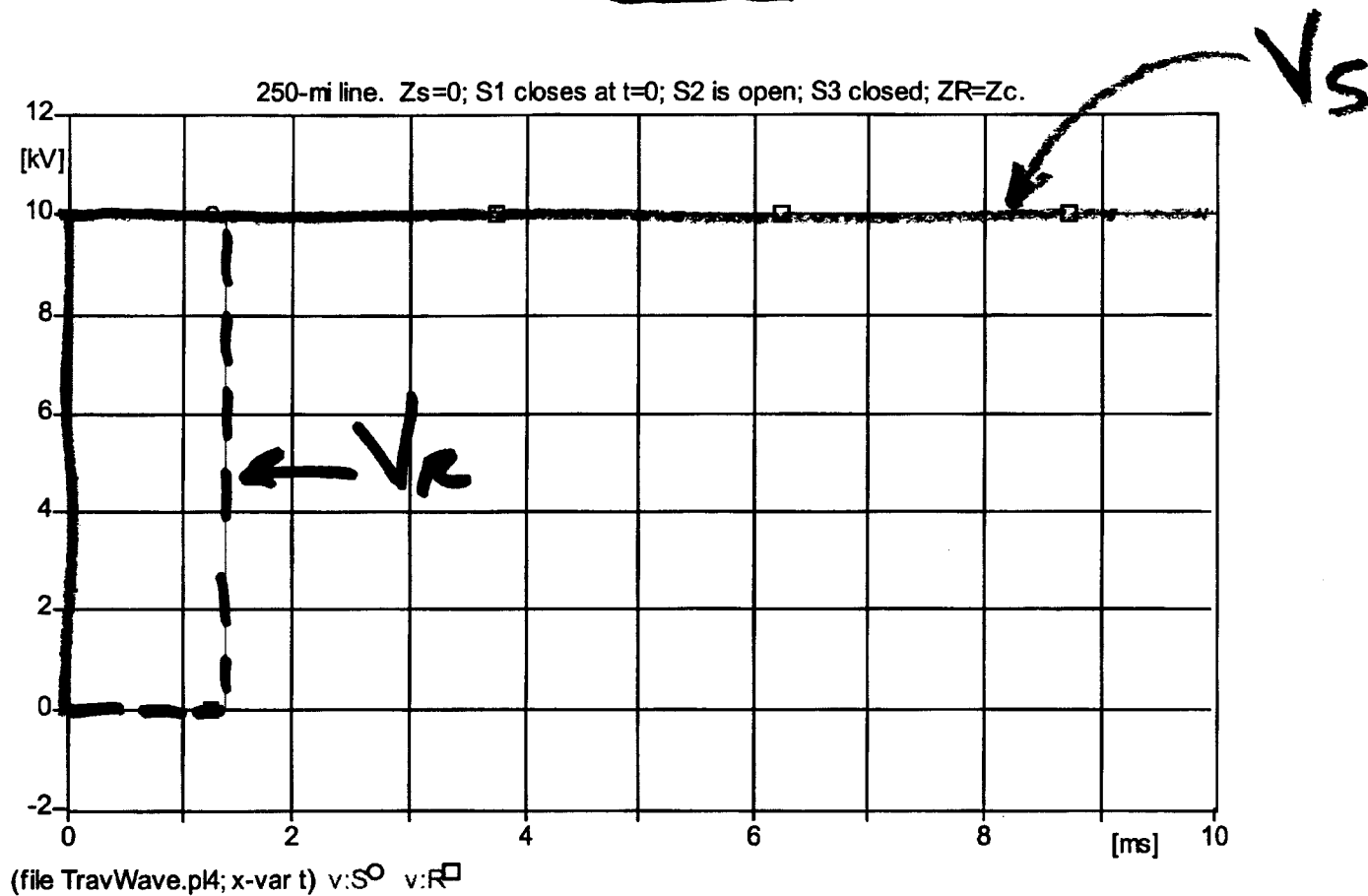Third Case: Lossless line; $Z_s=0$; $Z_R = Z_C$



Note: no reflection or voltage overshoot at receiving end !