


## Topics for Today:

- Startup
  - Web page: <https://pages.mtu.edu/~bamork/ee5220/>
  - Software - Matlab. ATP/EMTP [ License - [www.emtp.org](http://www.emtp.org) ]
  - ATP tutorials posted on our course web page
  - [EE5220-L@mtu.edu](mailto:EE5220-L@mtu.edu) (participation = min half letter grade)
- HW#4 parameters soon posted. Partnered exercise. Due Tues Feb 15<sup>th</sup>
- ATP Simulation pointers
- Cap Bank Switching (continued)
  - Circuit Breaker ratings - Capacitive Switching
  - Parameters
    - Cap Bank configurations
    - Current Limiting Reactors
- ATP - how it works internally
  - Conductance matrix formulation
  - Rs, Ls, Cs
  - Transmission lines
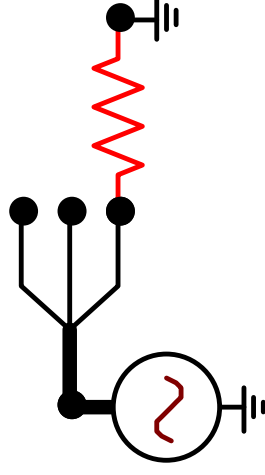
## ATP Simulation Pointer for the day:



When building 3-phase circuits, you are actually drawing a one-line which represents the L-G per-phase equivalent of the system. Node names have a base name 5 characters long, with the 6<sup>th</sup> character A, B, C automatically added. Click on the 3-phase end of the splitter if you want to define the base node name.

If you need to make single-phase connection(s) to individual phases, use the splitter. When drawing a connecting line to a splitter, start at the node of the single-phase element and connect **to** the splitter. If you need to ground one phase, you can do that at the single phase element, but not at the splitter.




# 3-PHASE ELEMENTS


2

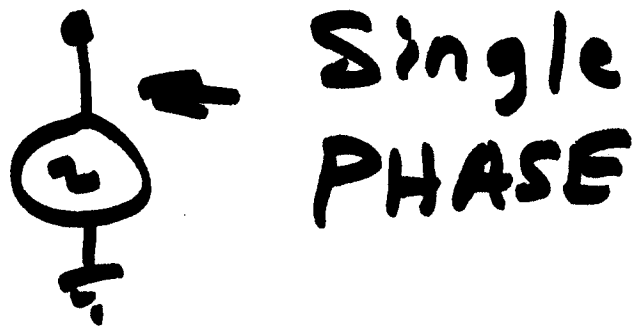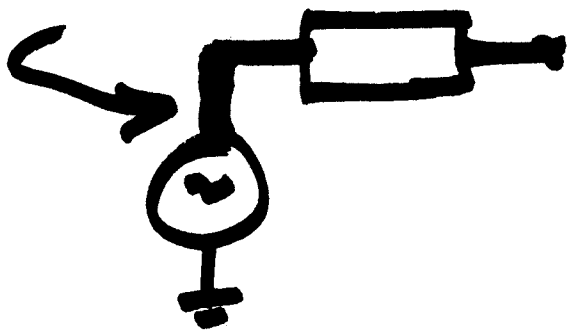

SPLITTER - 3ph  $\rightarrow$  1ph

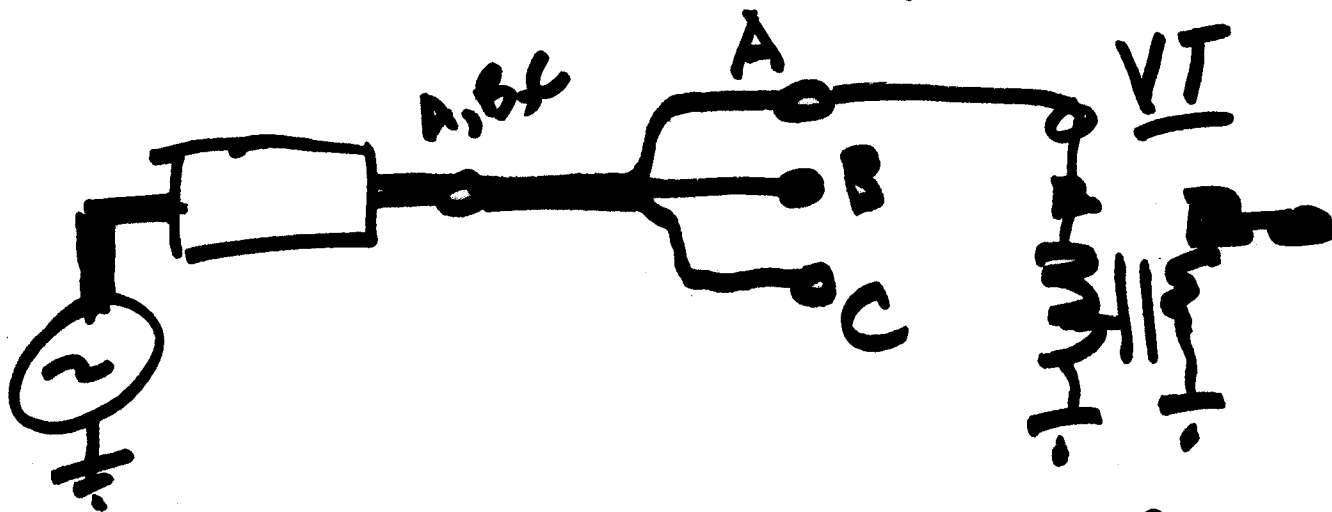

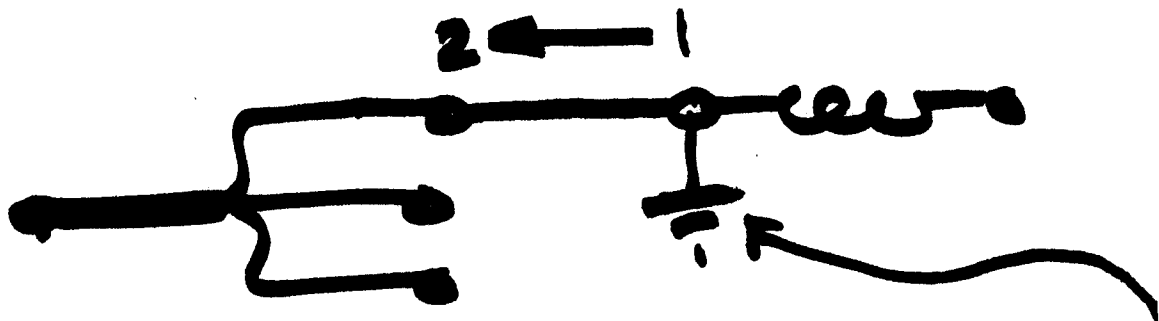
CONNECTING: Draw from 1  $\rightarrow$  2



Ground - Connect at 1  $\phi$  element
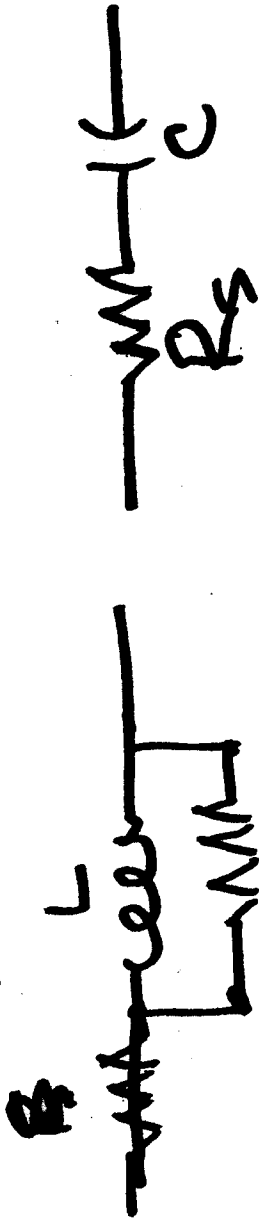
# ATP Simulation Pointer for the day:

What are the best values of numerical damping resistances to add to small L's and large C's? This turns out to be a function of the integration timestep and the value of the L or C.



"EMTP Theory Book"


$$R_p = \frac{2L}{0.15 \Delta t}$$

$$K_p \approx 7.5$$

$$R_s = \frac{0.15 \Delta t}{2C}$$

$$K_s \approx 0.15$$

$$\frac{1}{0.15}$$

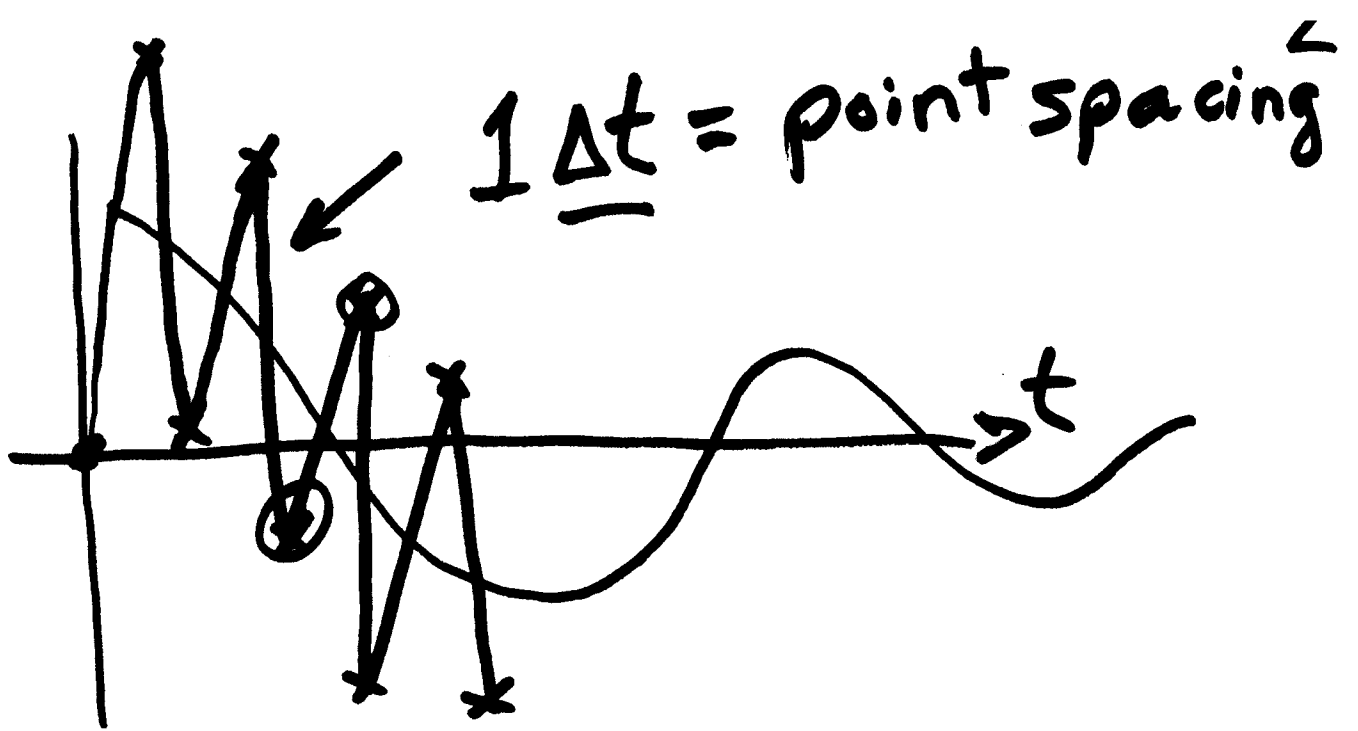


Key: Look at ATP Settings  
 Set Integer Parameter  
 "Plot Freq" = 1

(often set to larger odd  
 number to reduce PL4  
 file size).


Be careful of aliasing  
 errors! Use odd number,  
 and not too large!

\*.lis = text log

\*.pl4 = binary plot

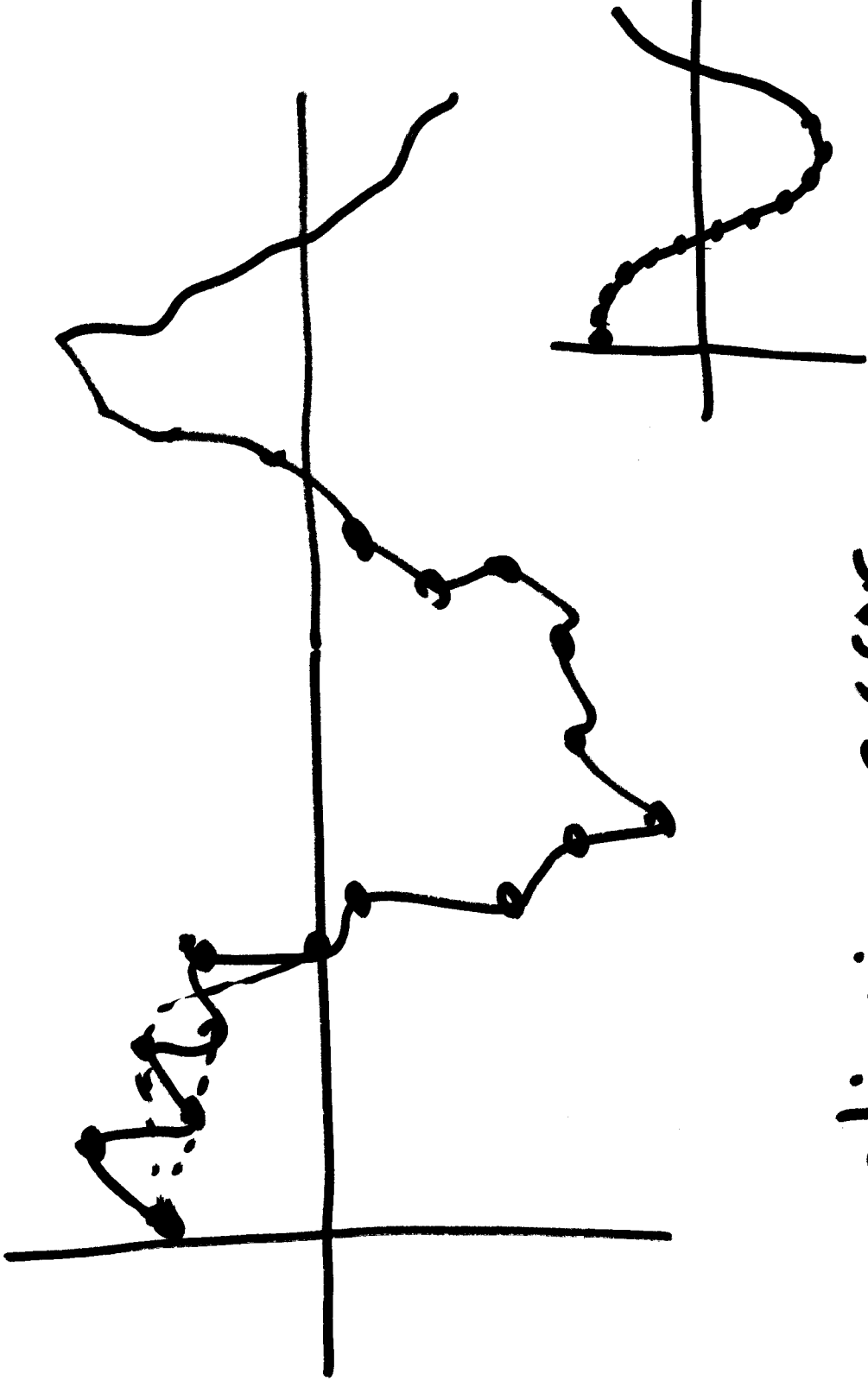

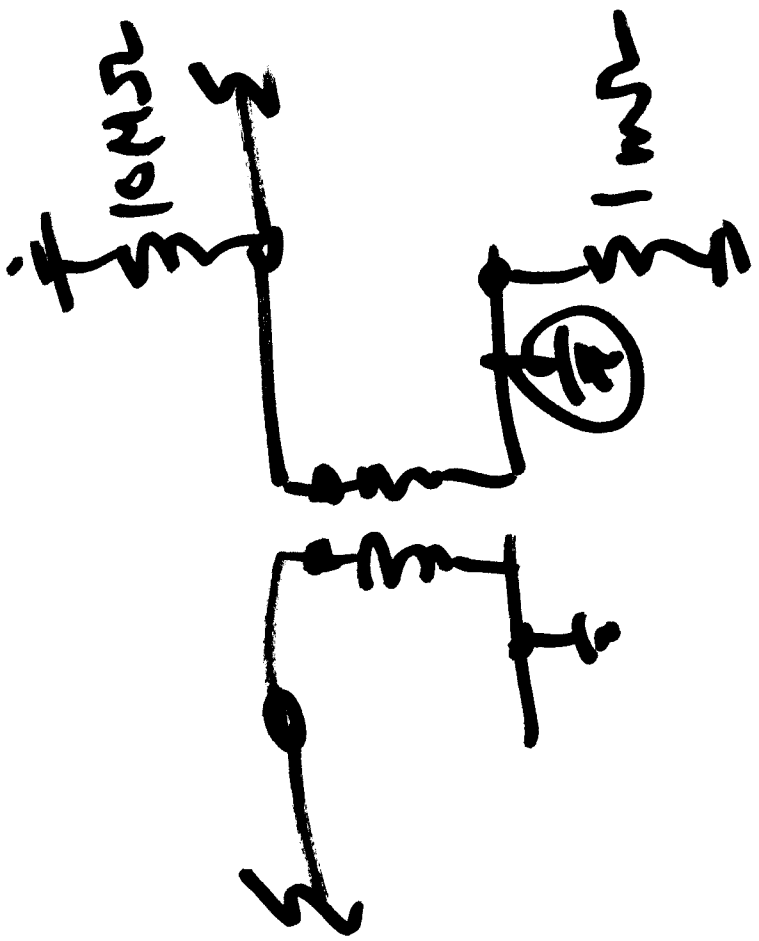aliasing error  
 - always skip odd # pts.




# Current-Limiting Reactors (CLRs)

- Back-to-Back Switching
- Outrush

$$I_p \times f_o \leq \frac{\text{A. Hz}}{\text{A. Hz}}$$

Gen:  $2 \times 10^7$   
Def:  $6.8 \times 10^7$

LB (if needed)  
Add CLR

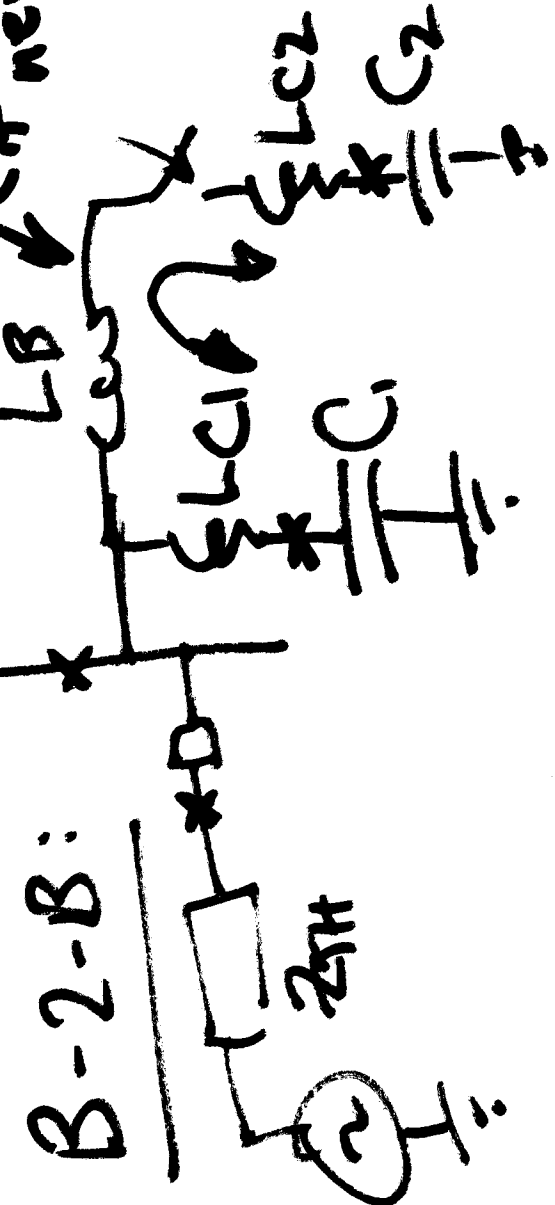

$$L_{EQ} = L_{C1} + L_B + L_{C2}$$

$$C_{EQ} = \frac{C_1 C_2}{C_2 + C_1}$$



$$I_p = \frac{V_p}{Z_0}$$


$$V_p = \frac{34,500}{\sqrt{3}} \sqrt{2} = 28.1 \text{ kV}$$

$$f_0 = \frac{1}{2\pi\sqrt{L_0 C_0}}$$

$$I_{p f_0} = \frac{V_p}{Z_0} \cdot \frac{1}{2\pi\sqrt{L_0 C_0}}$$

$$I_{p f_0} = \frac{V_p}{\sqrt{\frac{L_0}{C_0}}} \cdot \frac{1}{2\pi\sqrt{L_0 C_0}}$$


$$\frac{V_p}{2\pi\sqrt{L_0 C_0}}$$

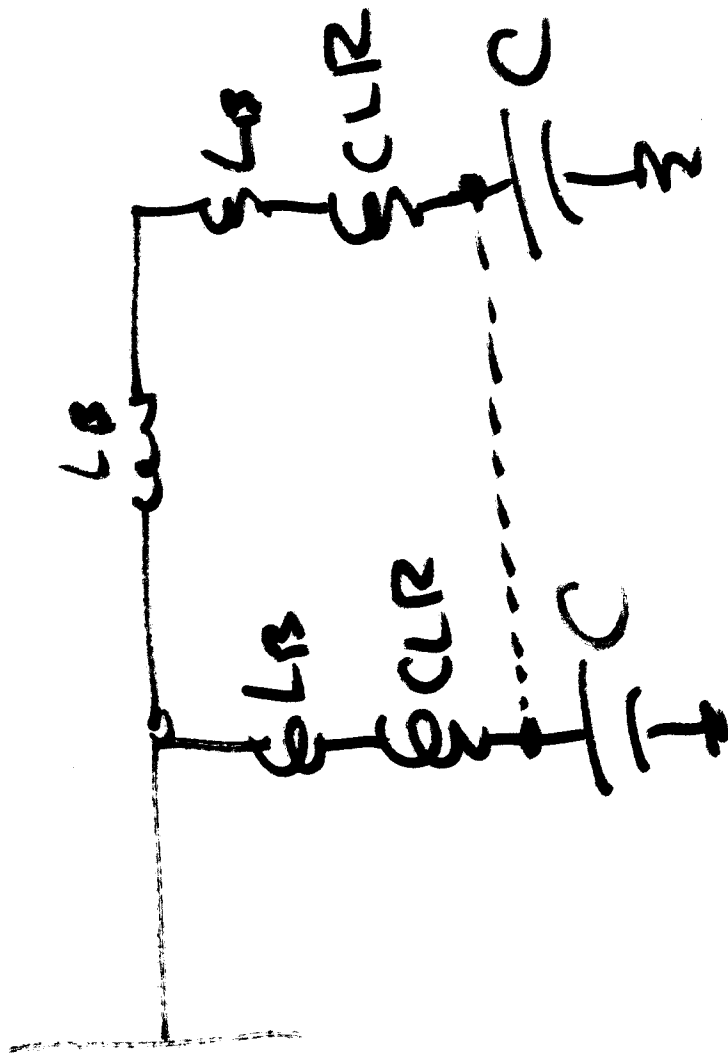


CLR Parallel Banks =  $Np \times$  CLR single bank

# Circuit Switcher

12-20 kA

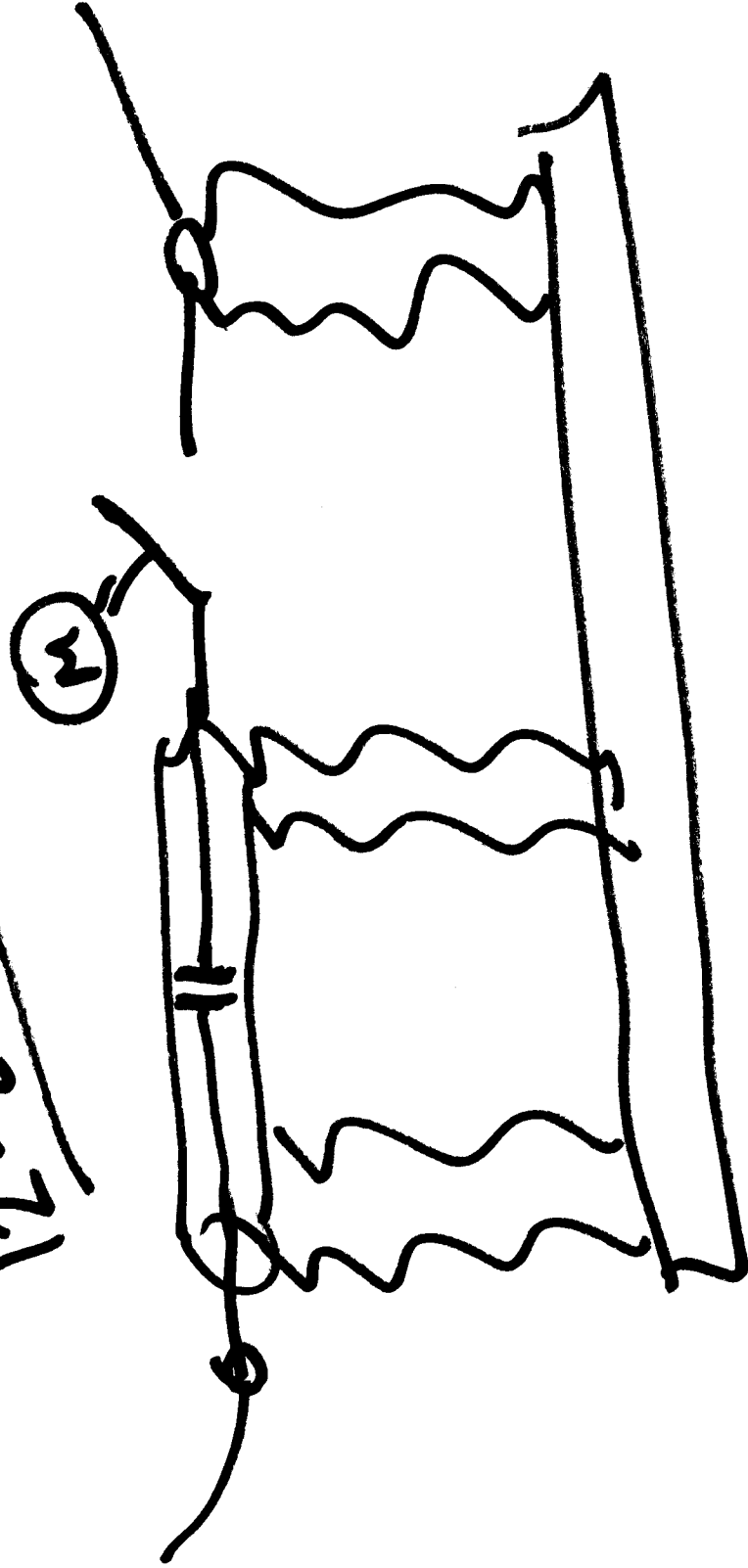

# New Cap Installation -

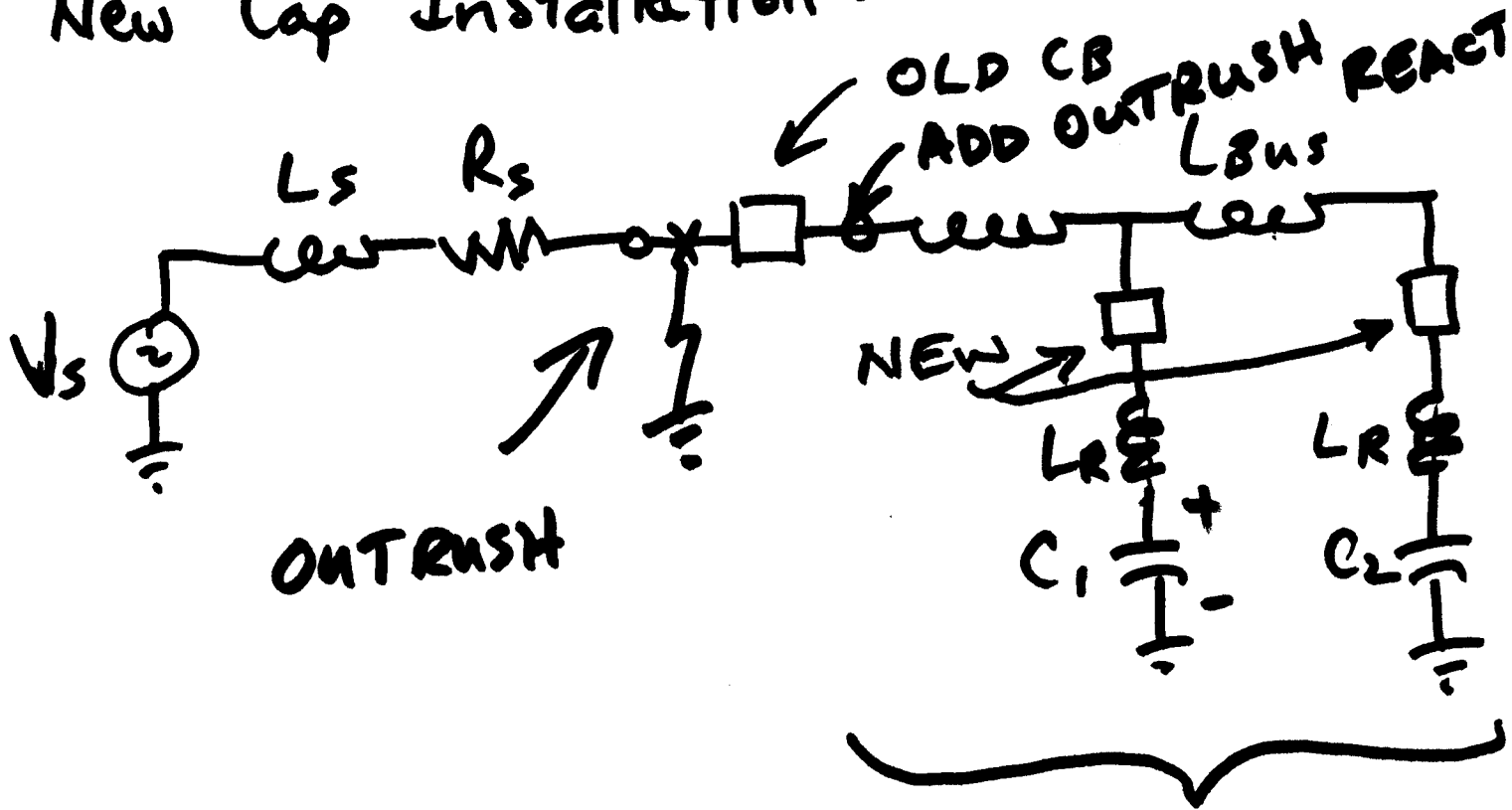

B2B

Add current limiting reactors


$$\omega_0 = \frac{1}{\sqrt{(L_{bus} + 2L_R) \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$

∴  $\omega_0$  decreases.

$$Z_0 = \sqrt{\frac{L_{bus} + 2L_R}{\frac{C_1 C_2}{C_1 + C_2}}} \Rightarrow Z_0 \text{ increase}$$

GREAT!

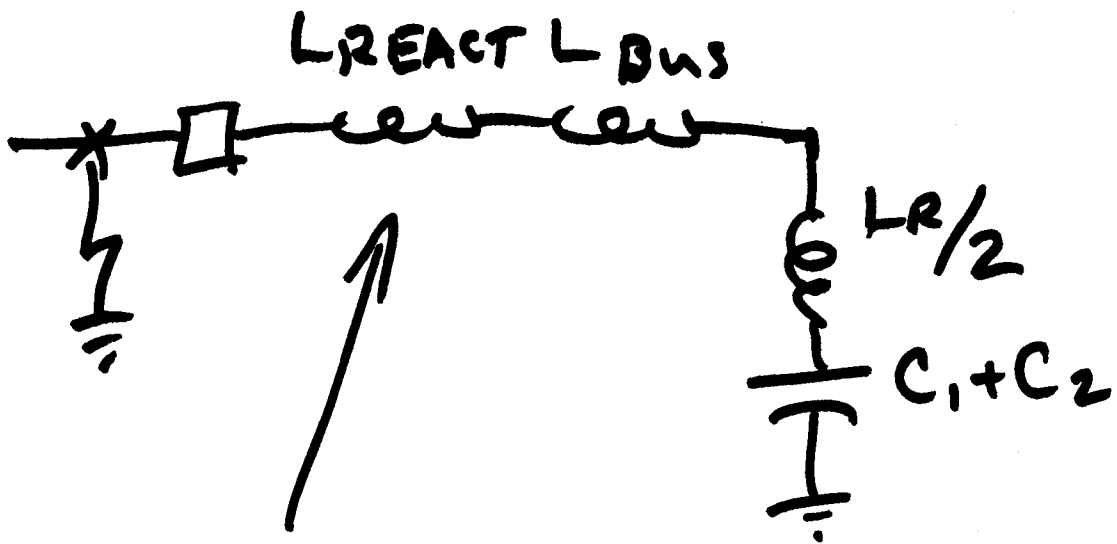CB's are rated in terms of  $I_p \times f_0$



ADD OUTRUSH  
REACTOR

Common Approach for all RLC ckts:


- Define operative  $L, C$
- Find  $\omega_0, Z_0$
- Find  $\Delta V = V(\infty) - \mathcal{U}(0^+)$
- Find  $I_p$
- Sketch waveforms -
- Check w/ ATP

$$I_p \times f_0 \leq \underline{2 \times 10^7}$$

$$I_p = \frac{V_p}{\sqrt{\frac{L}{C}}} \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

ADD

Lowpass?  
?

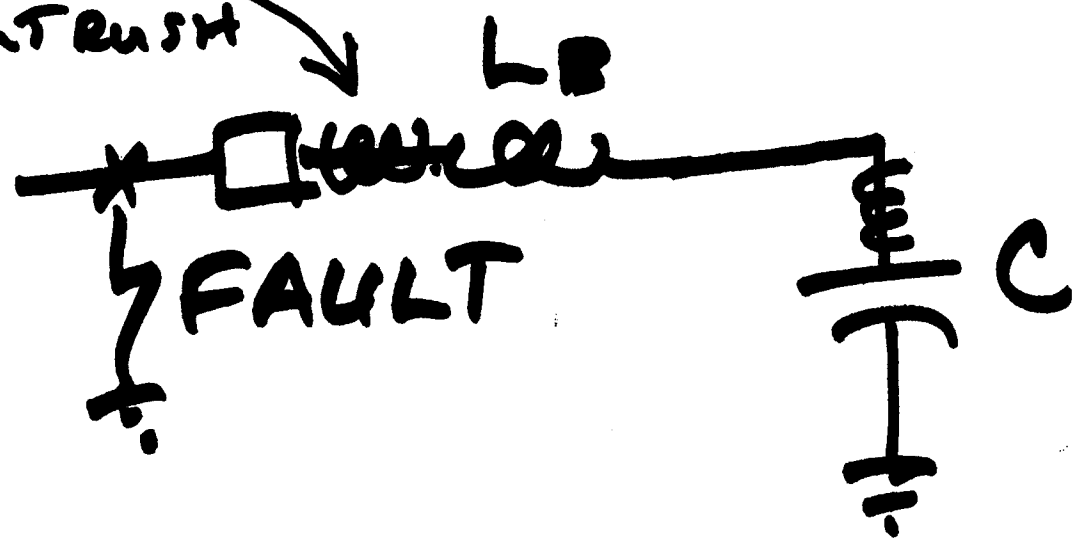

$$\frac{V_p}{\sqrt{\frac{L}{C}}} \times \frac{1}{2\pi\sqrt{LC}} \leq 2 \times 10^7$$

$$\frac{V_p}{2\pi L} \leq 2 \times 10^7$$

Solve for  $L \leftarrow$  Min required

$$L = L_{BUS} + L_{REACT} \quad (11)$$

IF  $L \leq L_{BUS} \Rightarrow$  No Reactor Needed!

IF  $L > L_{BUS}$

$$\Rightarrow L_{REACT} = L - L_{BUS}$$

For definite purpose:

a)  $w_0 < w_{rated}$

~~$f$~~   
b)  ~~$f$~~   $I_p < I_{rated}$

$I_p w_0 < rated.$

# RS, L's & C's in EMTIP 3

## Notes

EMTP - BPA, 1970 → '85

1985 EPRI ↓ DCG

EPRI EMTP  
or DCG EMTP

- TACS ↓

EMTP/RV

F.O.I.

1987

ATP

## OTHERS:


- EMTDC / Psca
- Micro-Tran ✓
- ABB/Siemens
- EDF - MORGAT

## Different:

- TACS
- MODELS

Controls



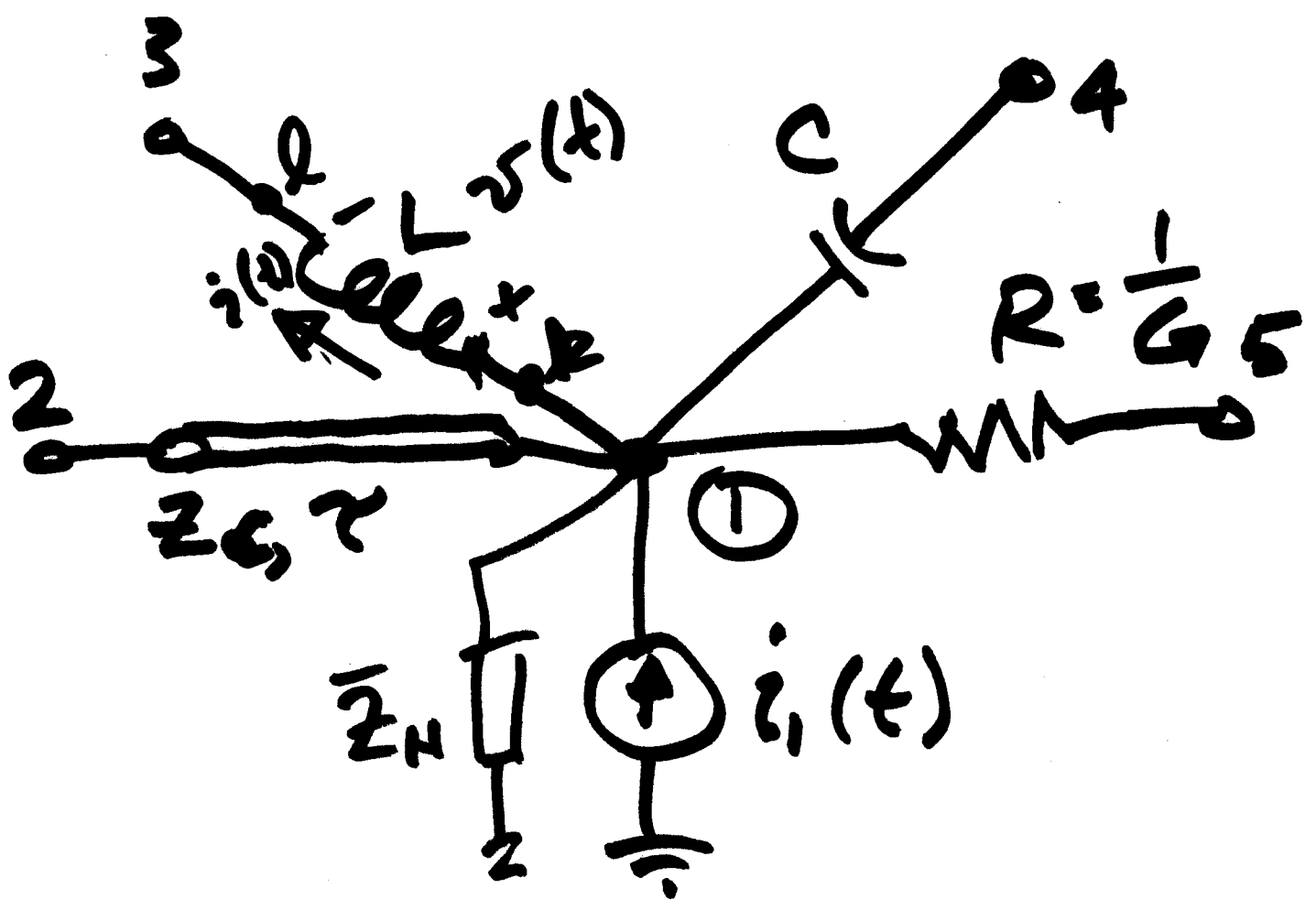


Side Note:

Mathematical Structure is

$$\text{Sparse} \rightarrow [Y][V] = [I]$$
  
 ↑ node Vs                      ↑ injected currents


# Injected Currents!


5

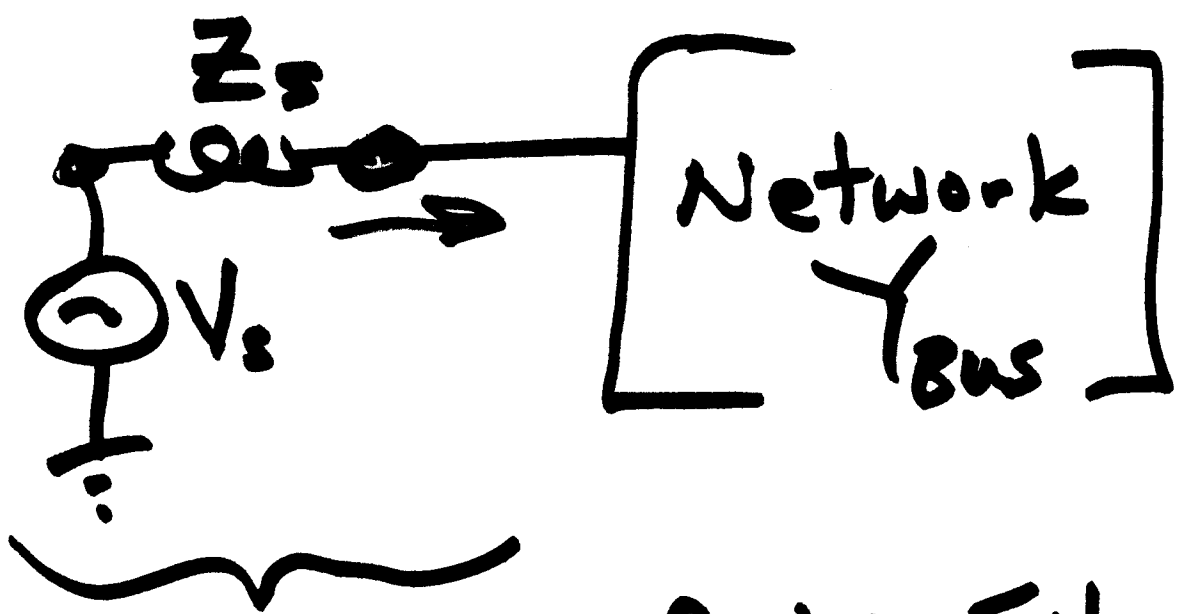

Thevenin = Bad: Extra Node  
 $V = \text{Fixed}$

Instead, convert to Norton:  
NORTON

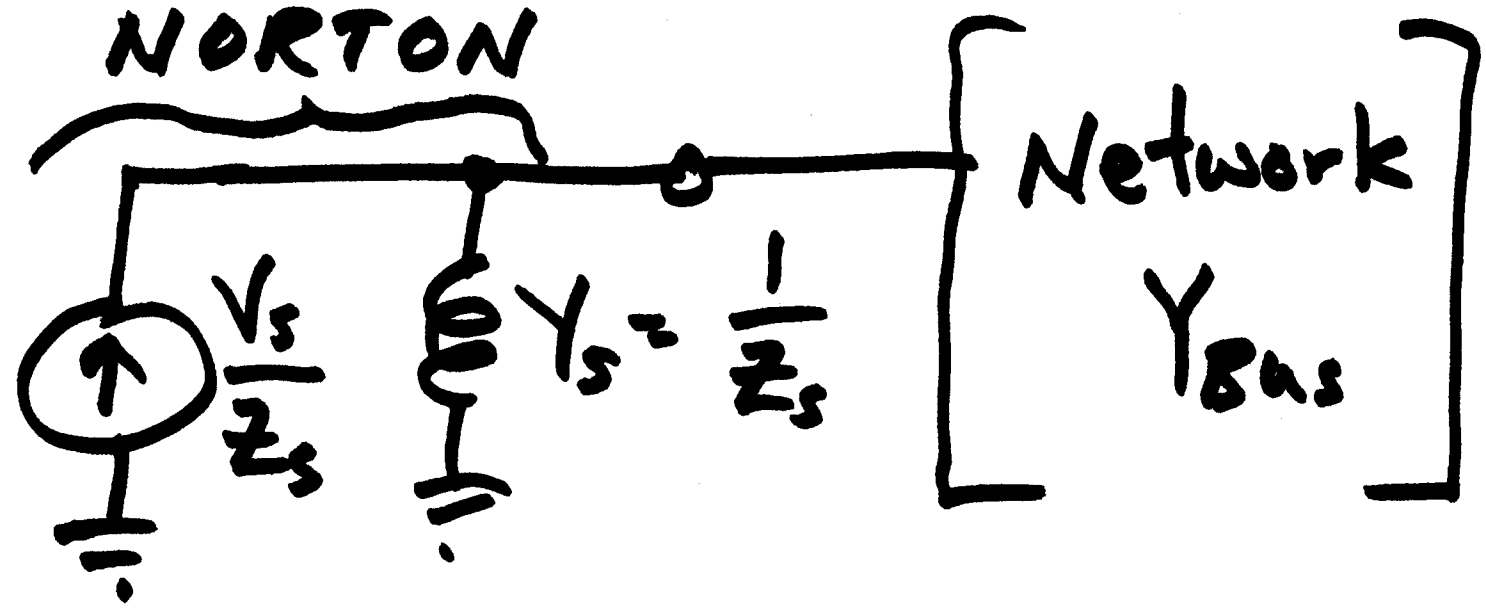

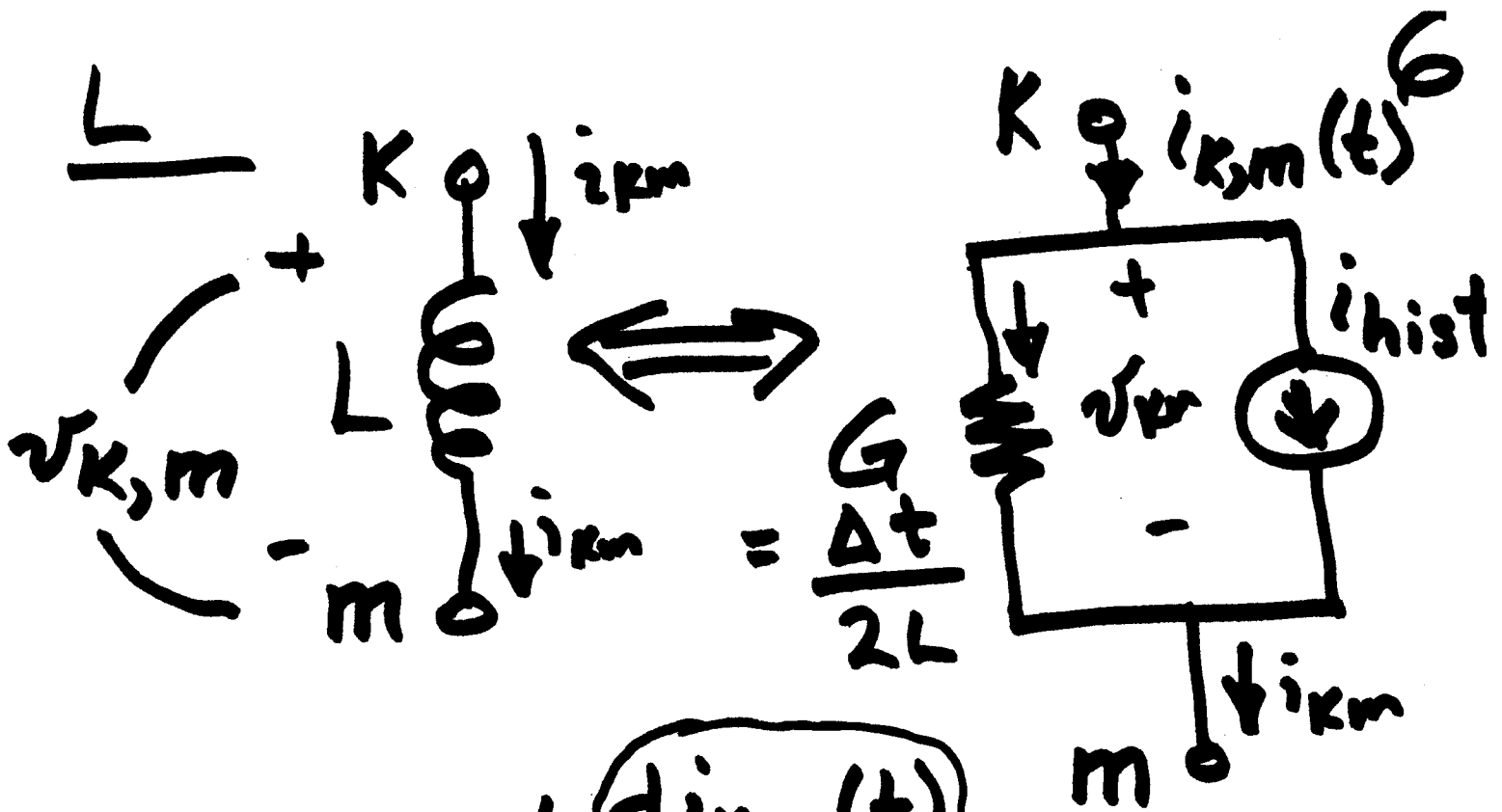


$$v_K - v_m = L \frac{di_{K,m}(t)}{dt}$$

$$di_{K,m}(t) \approx \underbrace{\{i_{K,m}(t) - i_{K,m}(t - \Delta t)\}}_{\Delta i}$$

$$dt \approx \Delta t$$

Trapezoidal  
Integration

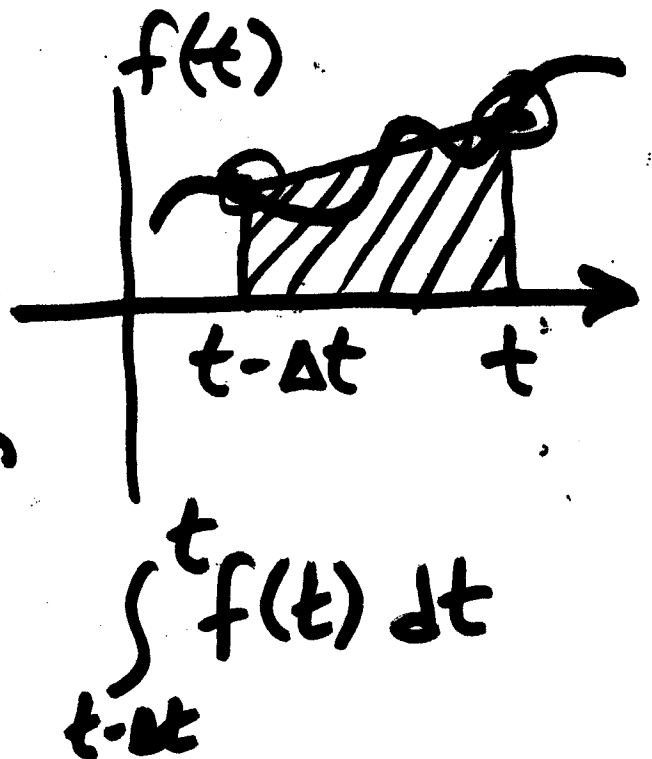

$$i \downarrow \frac{d}{dt} v = L \frac{di}{dt}$$

$$v dt = L di$$

$$di = \frac{1}{L} v dt$$

$$i = \frac{1}{L} \int_0^t v dt$$

$$i = ?$$

$\Delta t$  in EMTP

cannot be

as small as  $dt$ ,

$\Delta t$  is finite.


6A

Look at Trapezoidal  
implementation of eqn:

~~GB~~  
GB

$$v_k(t) - v_m(t) = L \frac{d i_{k,m}(t)}{dt}$$
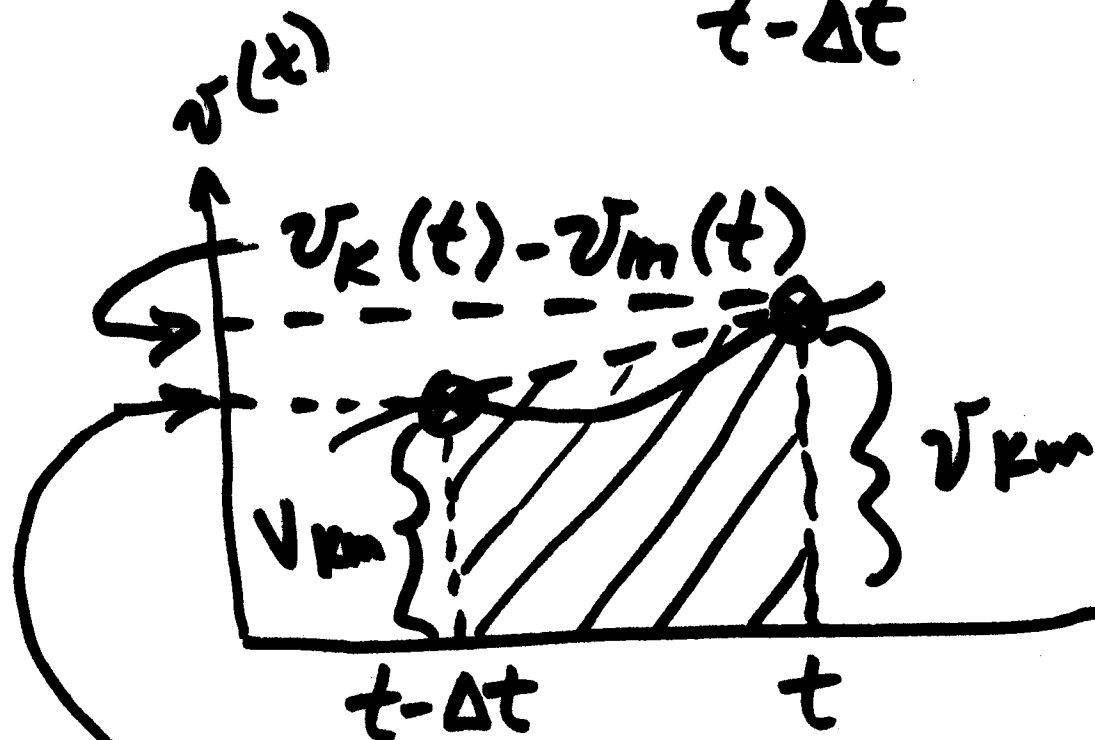
$$d i_{k,m}(t) = \frac{1}{L} \int_{t-\Delta t}^t [v_k(t) - v_m(t)] dt$$



$$v_k(t - \Delta t) - v_m(t - \Delta t)$$

The integral can then be approximated as the area of the trapezoid:

7

$$\frac{1}{L} \int_{t-\Delta t}^t [v_k(t) - v_m(t)] dt$$

$$\approx \frac{\Delta t}{L} \left[ \frac{v_k(t) - v_m(t) + v_k(t-\Delta t) - v_m(t-\Delta t)}{2} \right]$$

(i.e. area of trapezoid =  $\Delta t \times$  average height of sides)

$$di_{Km}(t) = \frac{1}{L} \int_{t-\Delta t}^t [\sigma_r(t) - \sigma_m(t)] dt$$



$$\underline{\underline{i_{Km}(t) - i_{Km}(t-\Delta t)}}$$

Integral is:

8

$$\frac{1}{L} \left[ \begin{array}{l} v_k(t) - v_m(t) + v_k(t-\Delta t) \\ - v_m(t-\Delta t) \end{array} \right] \frac{\Delta t}{2}$$

Putting pieces together,

$$i_{k,m}(t) \equiv i_{k,m}(t-\Delta t) \quad \swarrow \text{ok}$$
$$+ \frac{\Delta t}{2L} \left[ \begin{array}{l} v_k(t) - v_m(t) + v_k(t-\Delta t) \\ - v_m(t-\Delta t) \end{array} \right]$$

Separating  $(t)$  &  $(t-\Delta t)$  terms,



$$i_{m,k}(t) \approx \left( \frac{\Delta t}{2L} \right) \left[ v_k(t) - v_m(t) \right]$$

9  
Current  
at time = t  
for present  
voltage drop

$$+ i_{k,m}(t-\Delta t) + \frac{\Delta t}{2L} \left[ v_k(t-\Delta t) - v_m(t-\Delta t) \right]$$


$I_{hist} = I_{k,m} =$  Summation of all currents  
at past time steps. i.e.  
 $t-\Delta t, t-2\Delta t, t-3\Delta t, \dots$

Initialization:


$$I_{hist}(0) = i(0).$$

$[Y_{bus}]$  is augmented ~~to~~ 10 according to system elements needed.

R:

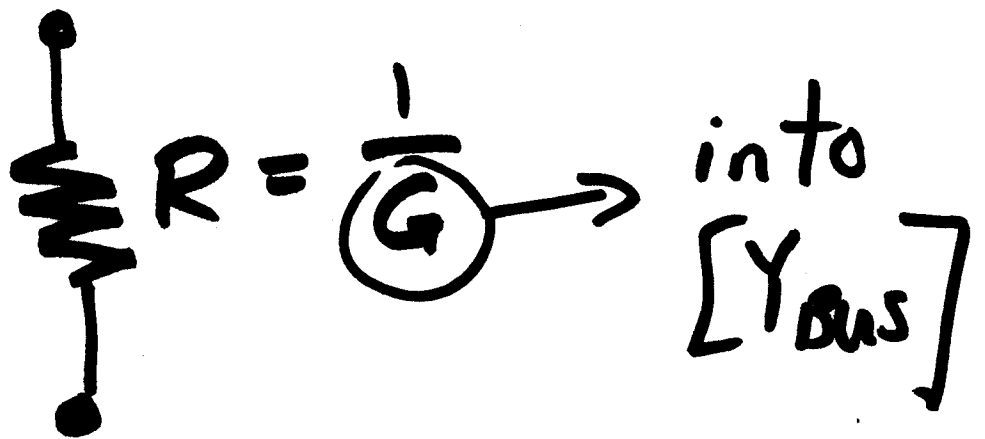

C:

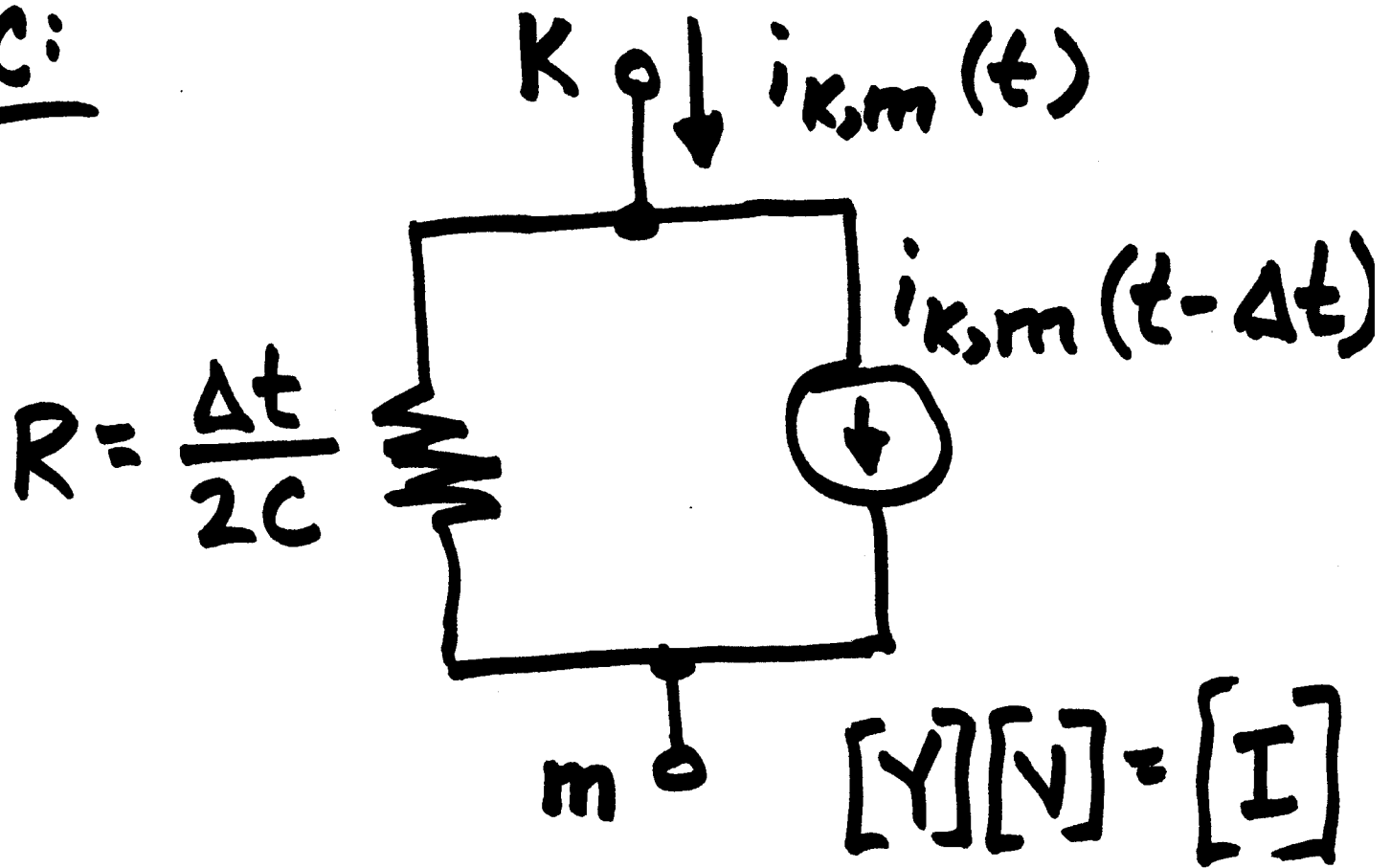

$L_i$

$K \circ b \ i_{k,m}(t)$

~~11~~  
11

