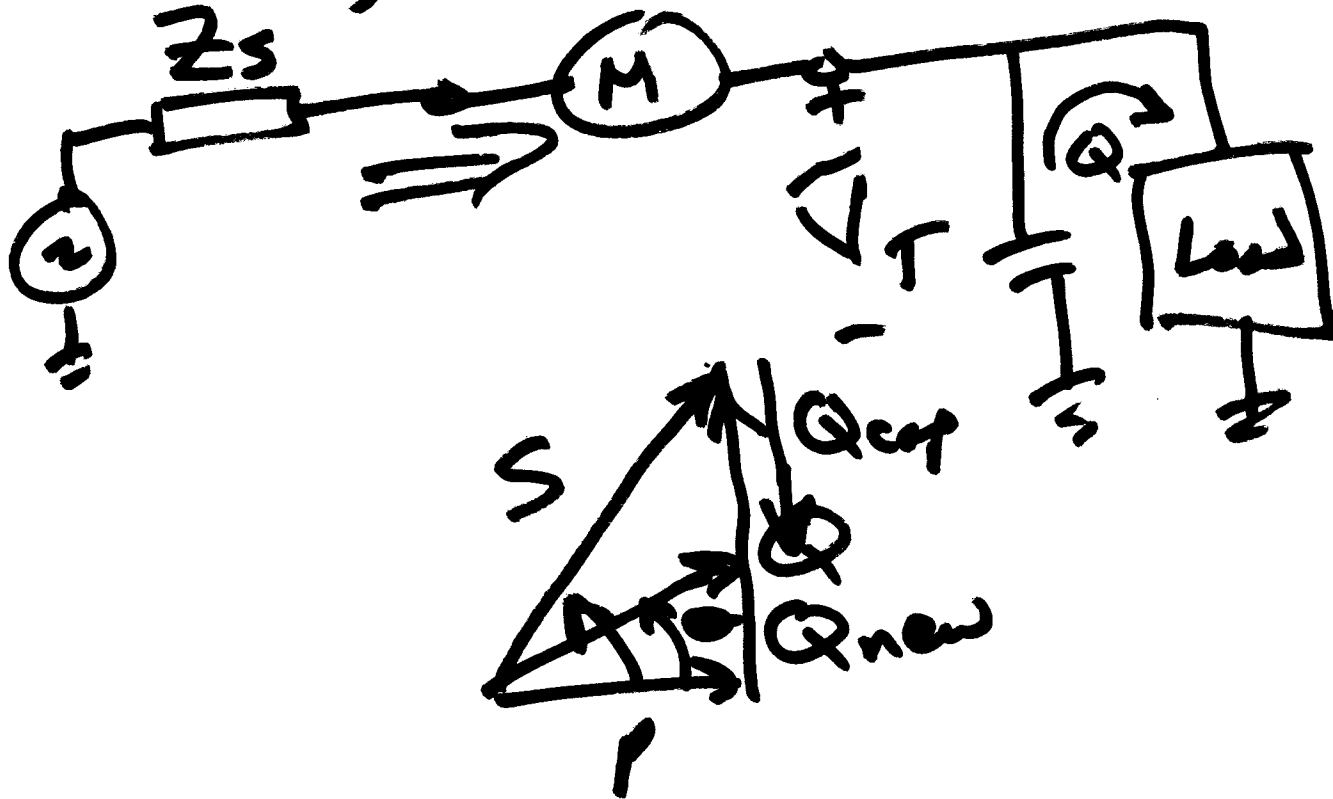


Topics for Today:

- Course Info:
 - Web page: <https://pages.mtu.edu/~bamork/ee5220/index.htm>
 - Software - Matlab. ATP/EMTP [License - www.emtp.org] ATP tutorials posted on our course web page
 - EE5220-L@mtu.edu (participation = min of half letter grade, 5%)
- HW#5 will be posted. Partnered exercise. Due latest Tues Feb 20th 9am.
 - Section 12.4 - detailed derivation for capacitor
 - Prob 5.3 - first do ATP simulation, then Hand Calculations
 - Prob 5.6
- Term Project - proposed topic(s) by end of next week, via short e-mail.
- Circuit Breakers - Interruption issues
 - Restrike
 - Reignition
- Cap and Reactor application (term projects similar to Hmwk4 are discouraged)
 - Dist system
 - Autotransformer tertiary
 - HV direct connection
- Transmission Lines - development of T-Line equations, traveling wave relays
- Transformers - hybrid model, inrush, GIC, ferroresonance


Cap_Application

- LV, on customer side of meter
 \Rightarrow Penalty for Low P.F. \Rightarrow P.F. Correction



Compensation, VR.

2b

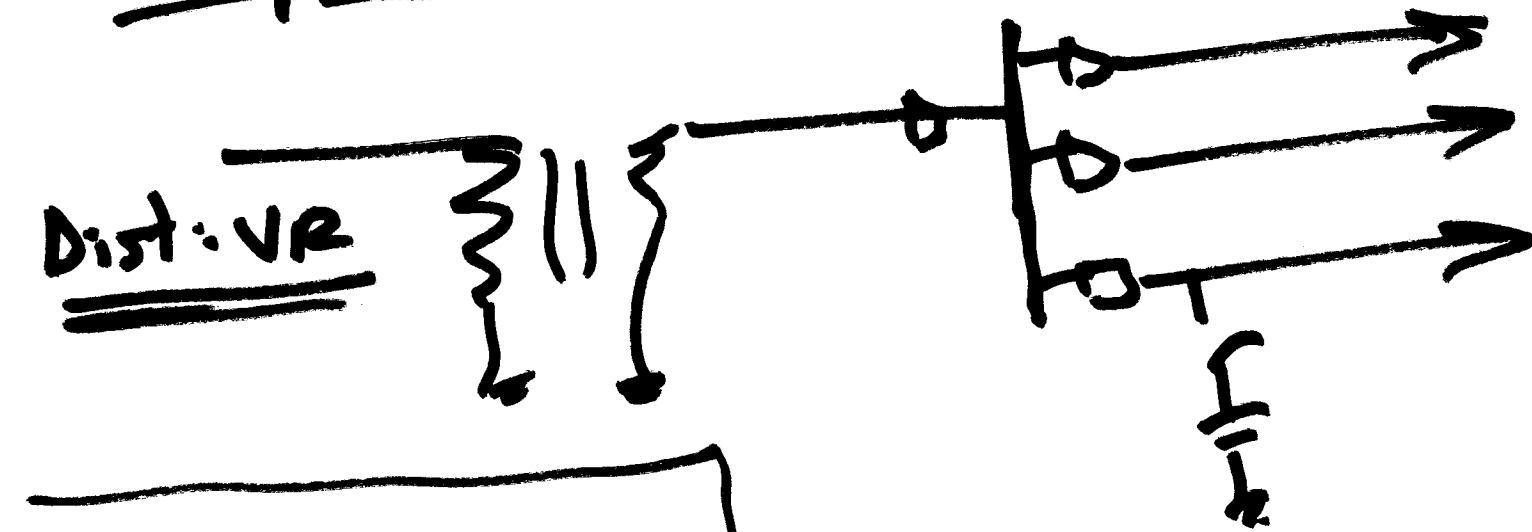

Trans. Tie

L.V. Caps are cheaper to mfr.

Compensation

2c

Shunt

- Voltage Support
- Power Transfer


$$P_{1-2} = \frac{V_1 V_2}{X_{12}} \sin(\delta_1 - \delta_2)$$

- Stability




21% increase
(.95 \rightarrow 1.05 pu. V)

Shunt Comp: Reactors

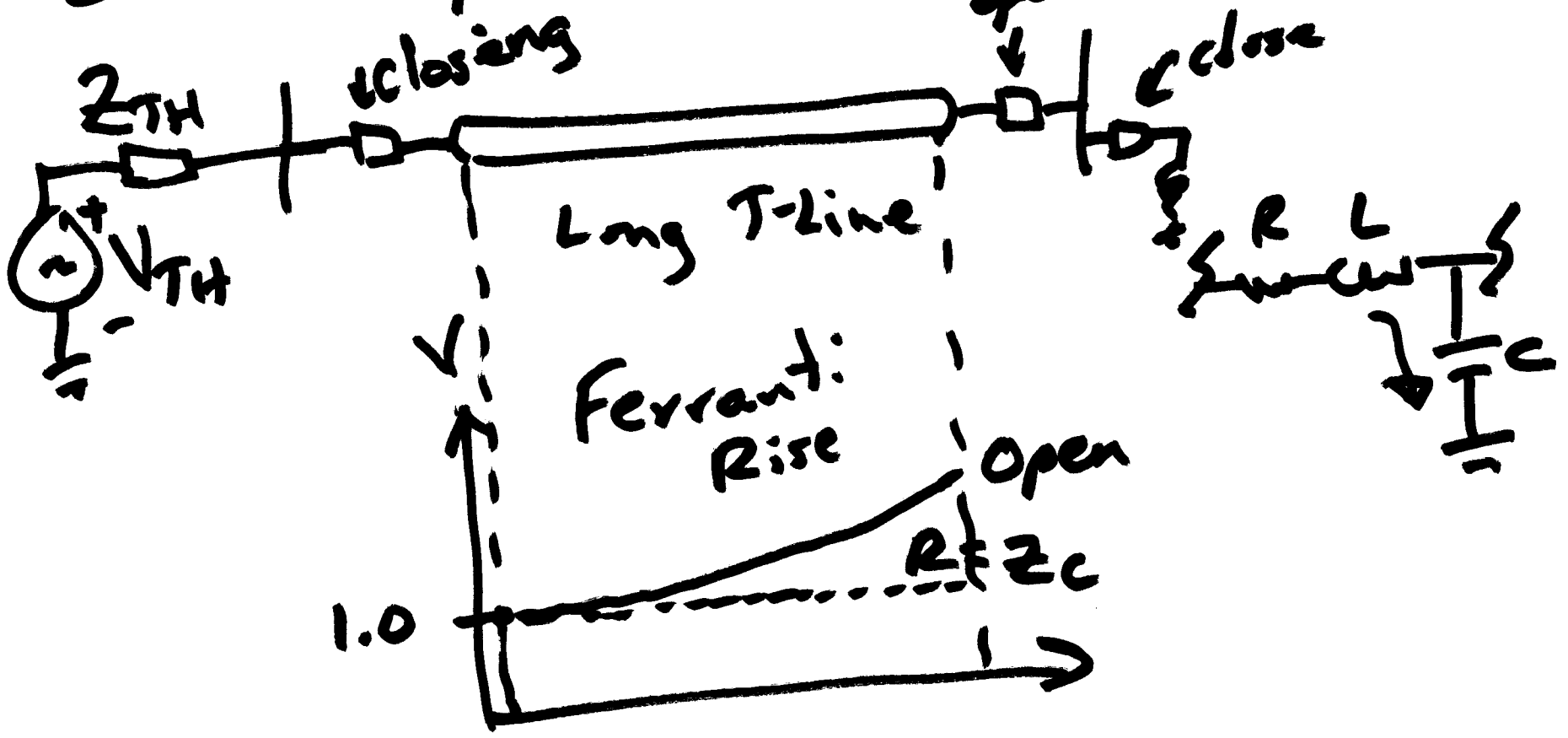


Ref: EE5200

Series Comp:

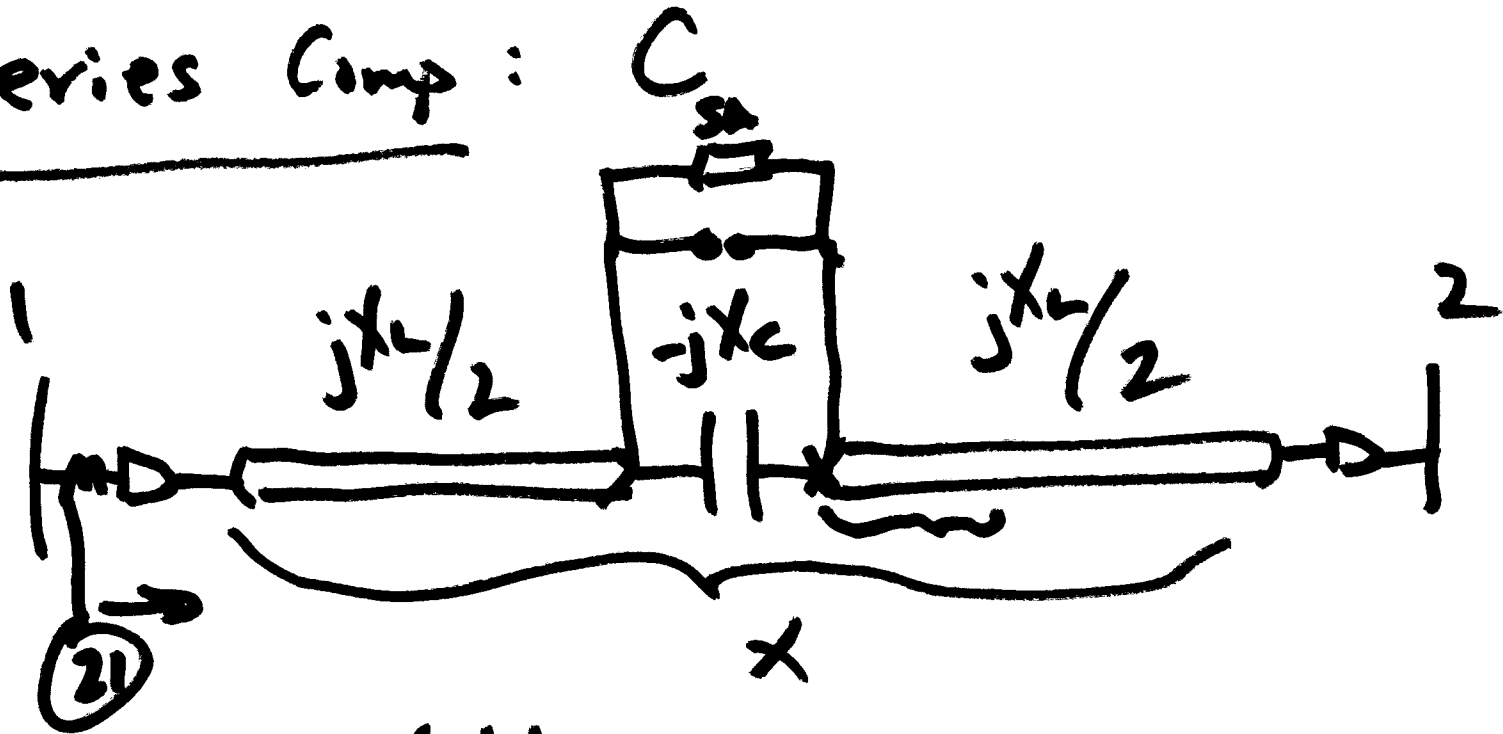


$$P_{1-2} = \frac{V_1 V_2}{X} \sin(\delta_1 - \delta_2)$$

X
 $X_c - X_c$

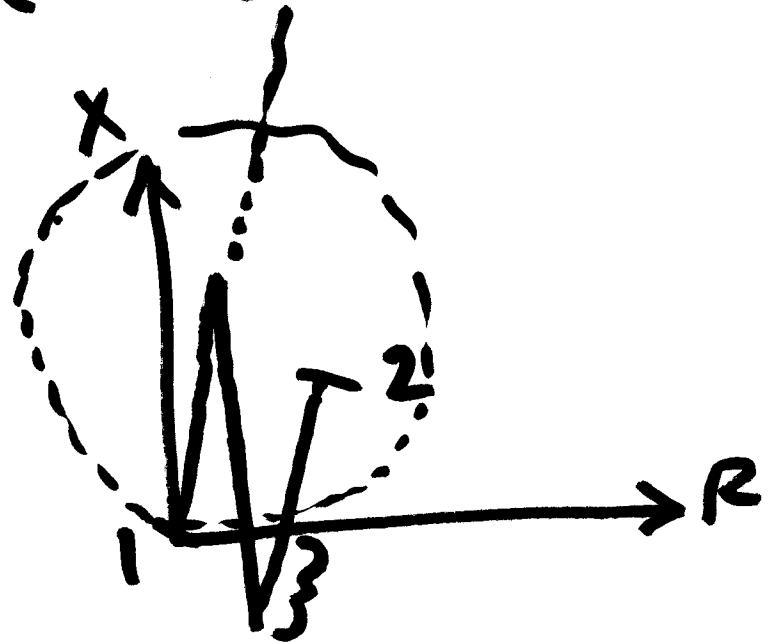


Lightning -

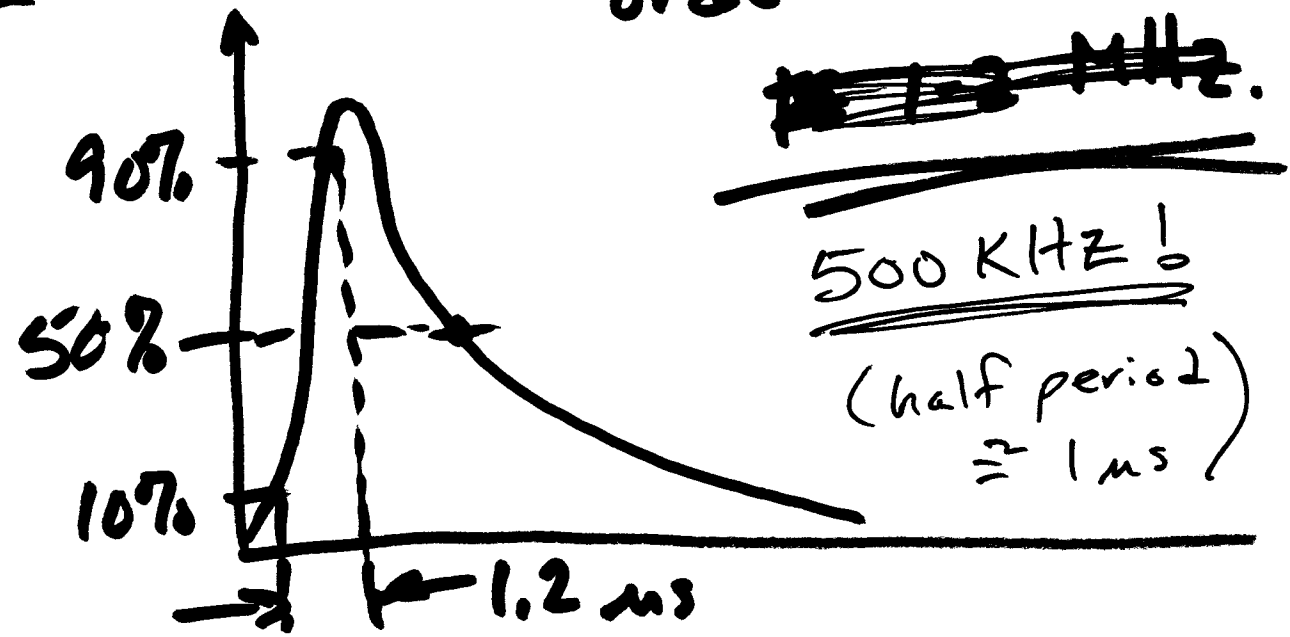

order of ~~1-3 MHz~~
500 kHz!
 (half period)
 $\Rightarrow 1 \mu s$


Switching -

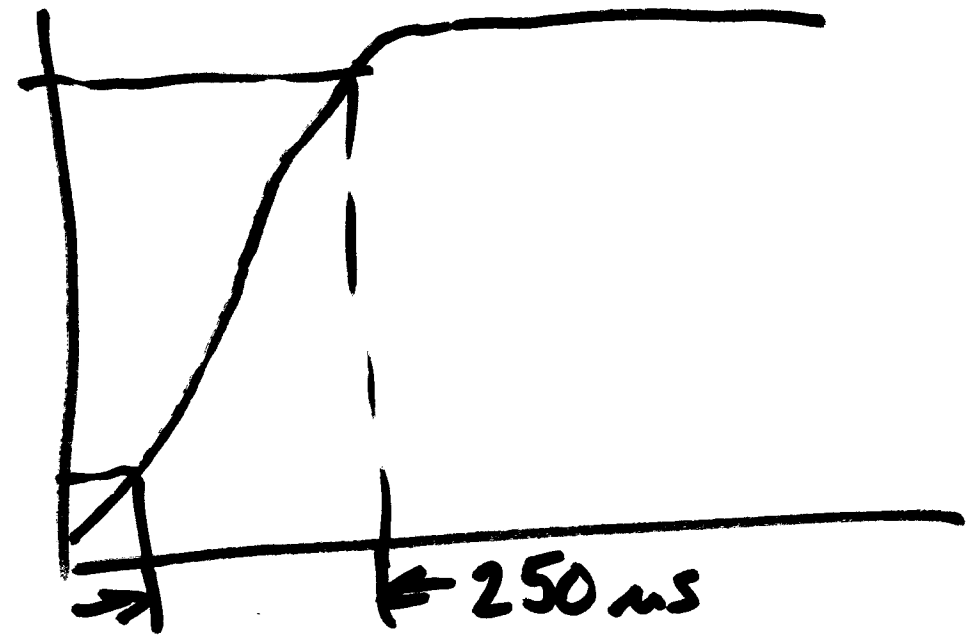

DISTRIBUTED - PARAMETER T-LINES 4

- "LONG LINES" ($> 250\text{km}$ @ 60Hz)
- FOR LIGHTNING, EVEN VERY SHORT LINES ARE MODELED AS DIST-PARAM.

FOR INCREMENTAL LENGTH:

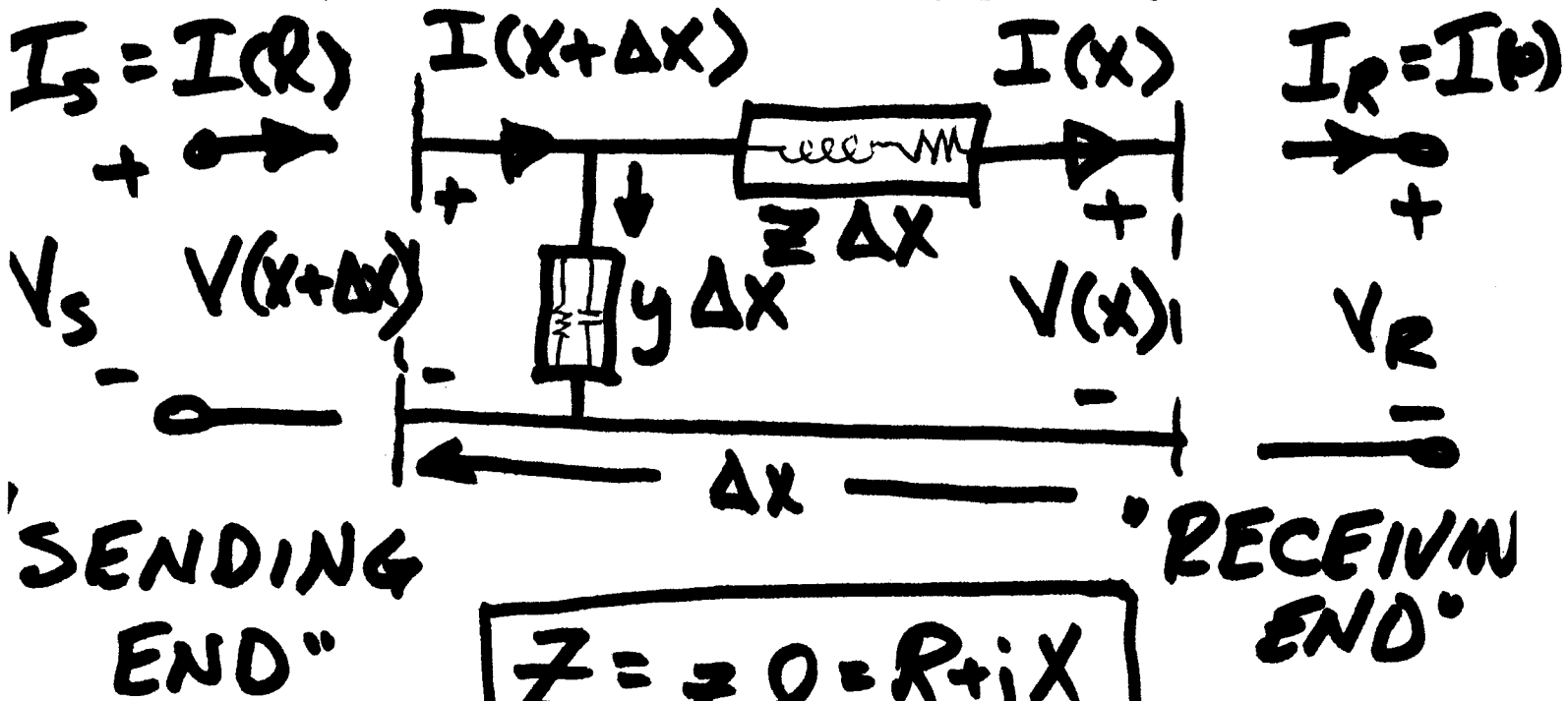

$$Z = z \ell = R + jX$$

$$Y = y \ell = G + jB$$

Making Δx very small,

$$\begin{cases} dV = IZ dx \\ dI = V_y dx \end{cases} \quad \leftarrow \text{(small } z)$$

Rearranging,

$$\begin{cases} \frac{dV}{dx} = IZ & (1) \\ \frac{dI}{dx} = V_y & (2) \end{cases}$$

Taking derivative of (1),

$$\frac{d^2V}{dx^2} = \frac{dI}{dx} Z$$

Substituting into (2) 6

$$\boxed{\frac{d^2 V}{dx^2} = V \gamma z^2}$$

This implicit gen'l sol'n:

$$\underline{V} = A_1 e^{\sqrt{\gamma z^2} x} + A_2 e^{-\sqrt{\gamma z^2} x}$$

Since $I = \frac{dV}{dx} / z$

$$I = A_1 \sqrt{\frac{\gamma}{z}} e^{\sqrt{\gamma z^2} x} - A_2 \sqrt{\frac{\gamma}{z}} e^{-\sqrt{\gamma z^2} x}$$

at $x=0$, $V = V_R$, $I = I_R$

$$V(0) = V_R = A_1 + A_2$$

$$I(0) = I_R = \sqrt{\frac{\gamma}{z}} A_1 - \sqrt{\frac{\gamma}{z}} A_2$$

Defining $Z_c = \sqrt{\frac{Z}{Y}} = \text{Char Imp.}$

$\gamma = \sqrt{Y Z} = \text{Propagation Const.}$

$$\begin{aligned} V_R &= A_1 + A_2 \\ I_R &= \frac{A_1 - A_2}{Z_c} \end{aligned}$$

$$\Rightarrow \begin{aligned} A_1 &= (V_R + Z_c I_R) / 2 \\ A_2 &= \frac{V_R - Z_c I_R}{2} \end{aligned}$$

**This form is best
for traveling waves**

$$V(x) = \frac{\overset{\text{Incident voltage}}{(V_R + Z_c I_R)} e^{\gamma x}}{2} + \frac{\overset{\text{Reflected voltage}}{(V_R - Z_c I_R)} e^{-\gamma x}}{2}$$

$$I(x) = \left(\frac{\overset{\text{Incident current}}{V_R + Z_c I_R}}{2 Z_c} \right) e^{\gamma x} - \left(\frac{\overset{\text{Reflected Current}}{V_R - Z_c I_R}}{2 Z_c} \right) e^{-\gamma x}$$

$$V_s = V(l) \leftarrow \underline{\underline{x=l}}$$

$$I_s = I(l) \leftarrow \underline{\underline{x=l}}$$


**This form is best
for S-S 60 Hz
using ABCD**

$$V(x) = V_R \underbrace{\cosh(\gamma x)}_A + \underbrace{Z_c I_R \sinh(\gamma x)}_B$$

$$I(x) = \frac{V_R}{Z_c} \underbrace{\sinh(\gamma x)}_C + I_R \underbrace{\cosh(\gamma x)}_D$$

In hyperbolic form,

9

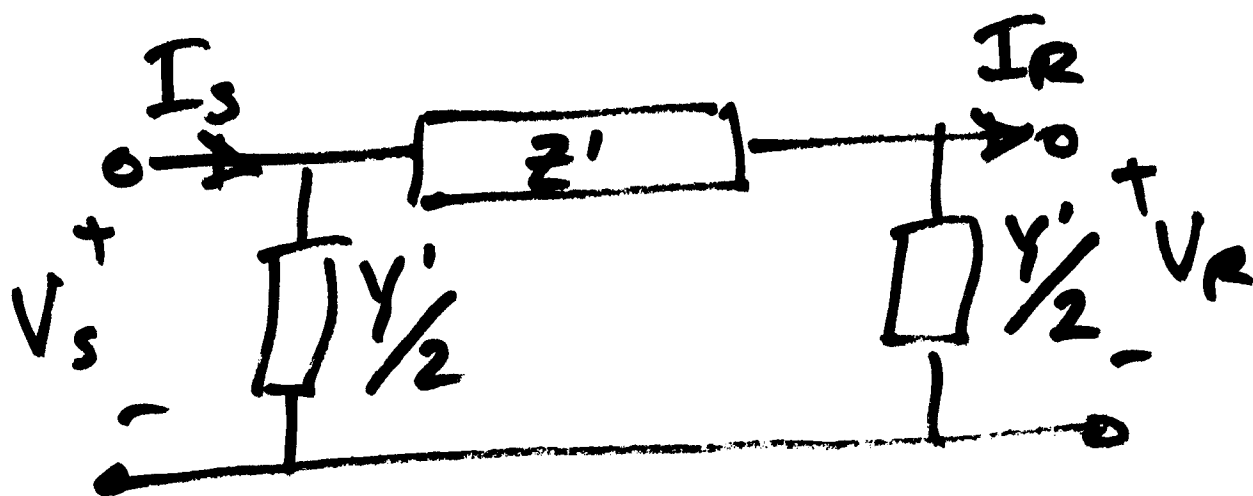

From EQNs:

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

If we match $\begin{bmatrix} A & B \\ C & D \end{bmatrix}$ with π -Equiv

$$Z' = Z \left[\frac{\sinh(\gamma l)}{\gamma l} \right]$$

$$\frac{Y'}{2} = \frac{Y}{2} \left[\frac{\tanh(\gamma l/2)}{\gamma l/2} \right]$$