
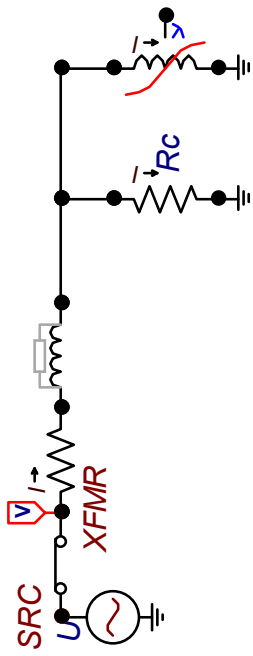


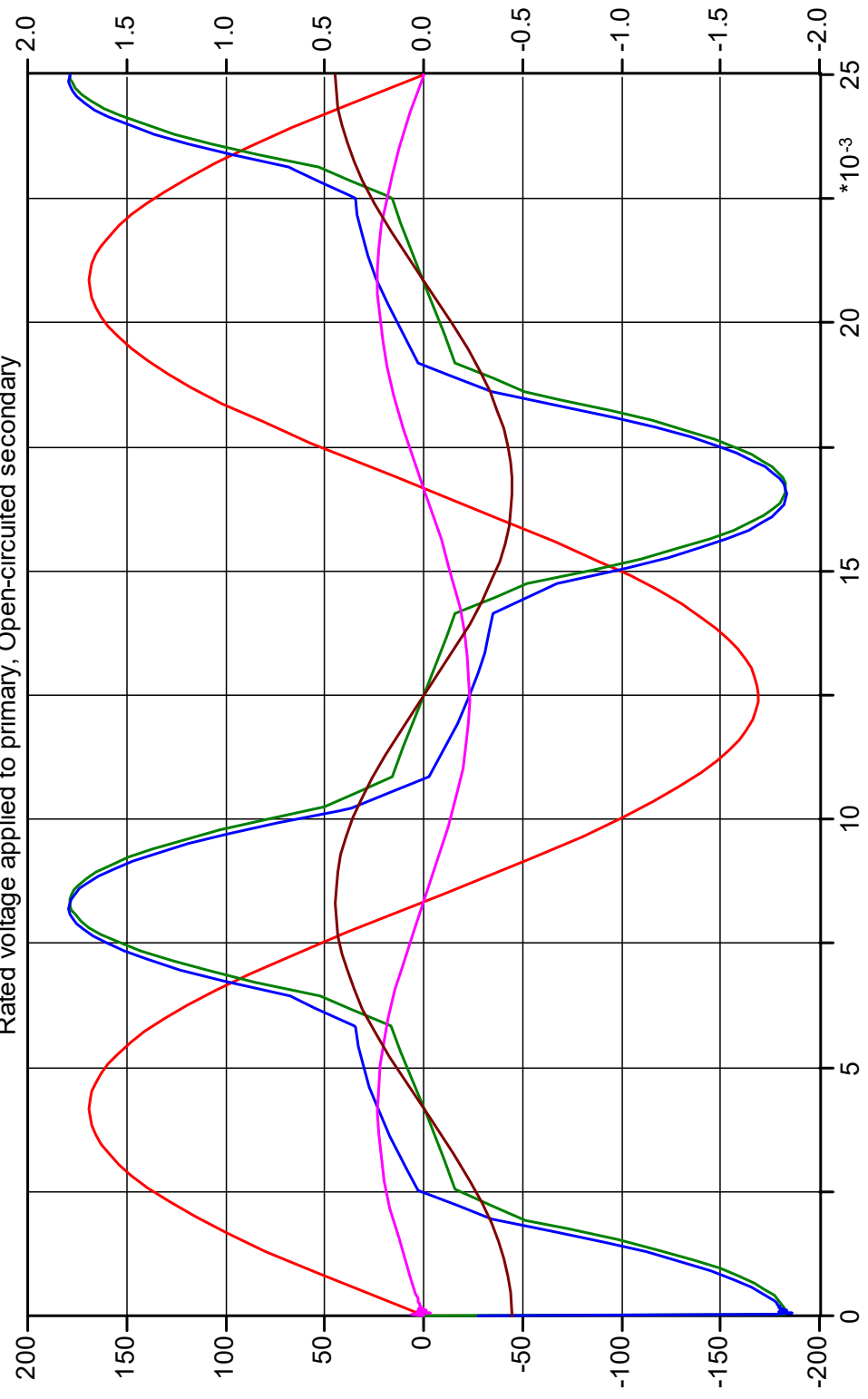**Topics for Today:**

- Course Info:
  - Web page: <https://pages.mtu.edu/~bamork/ee5220/index.htm>
  - Book, references, syllabus, more are on web page.
  - Software - Matlab. ATP/EMTP [ License - [www.emtp.org](http://www.emtp.org) ] ATP tutorials posted on our course web page
  - [EE5220-L@mtu.edu](mailto:EE5220-L@mtu.edu) (participation = min half letter grade)
- HW#8 - Probs. 9.6, 9.12 due Tues Mar 22<sup>nd</sup> 9am.
- HW#9 - Probs. 9.2, 9.3, 9.4 due Tues Mar 29<sup>th</sup> 9am.
- Week 9 deliverables for Term Project - Mar 21<sup>st</sup> - a) complete reference list and b) fully-detailed table of contents, format given in Term Project Guidelines.
- Transmission line modeling, cascaded PI sections
- Modeling Lighting surges, impulses in general (ATP type-15).
- Transformer modeling - Section 11.1 of text, plus lecture notes
  - Review pre-req mats on mag circuits(as posted under Pre-Req Mat'ls)
    - Ampere's Law, Lenz' Law, magnetic circuit parameters
  - Example of single-phase transformer, Excitation
    - Waveforms for voltage,  $I_{EX}$ ,  $I_R$ ,  $I_C$ ,  $\lambda$
- Next - take stock of available ATP transformer models




Steady-State Excitation of Single Phase Transformer  
 Rated voltage applied to primary, Open-circuited secondary




(file 1\F\FMR\_ex.pl4; x-var t) v:XFMR c:XX0004 c:XFMR -XX0001 c:XX0004 t:XX0003

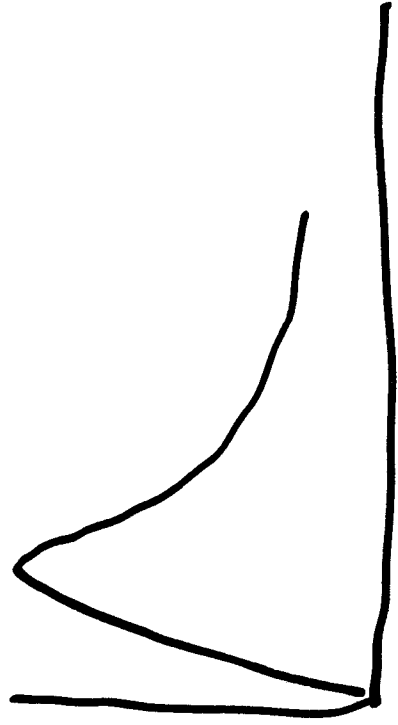ATP Pointers - Lighting Surges  
"Type-15"



# Actual Lightning or Switching Surges:

12

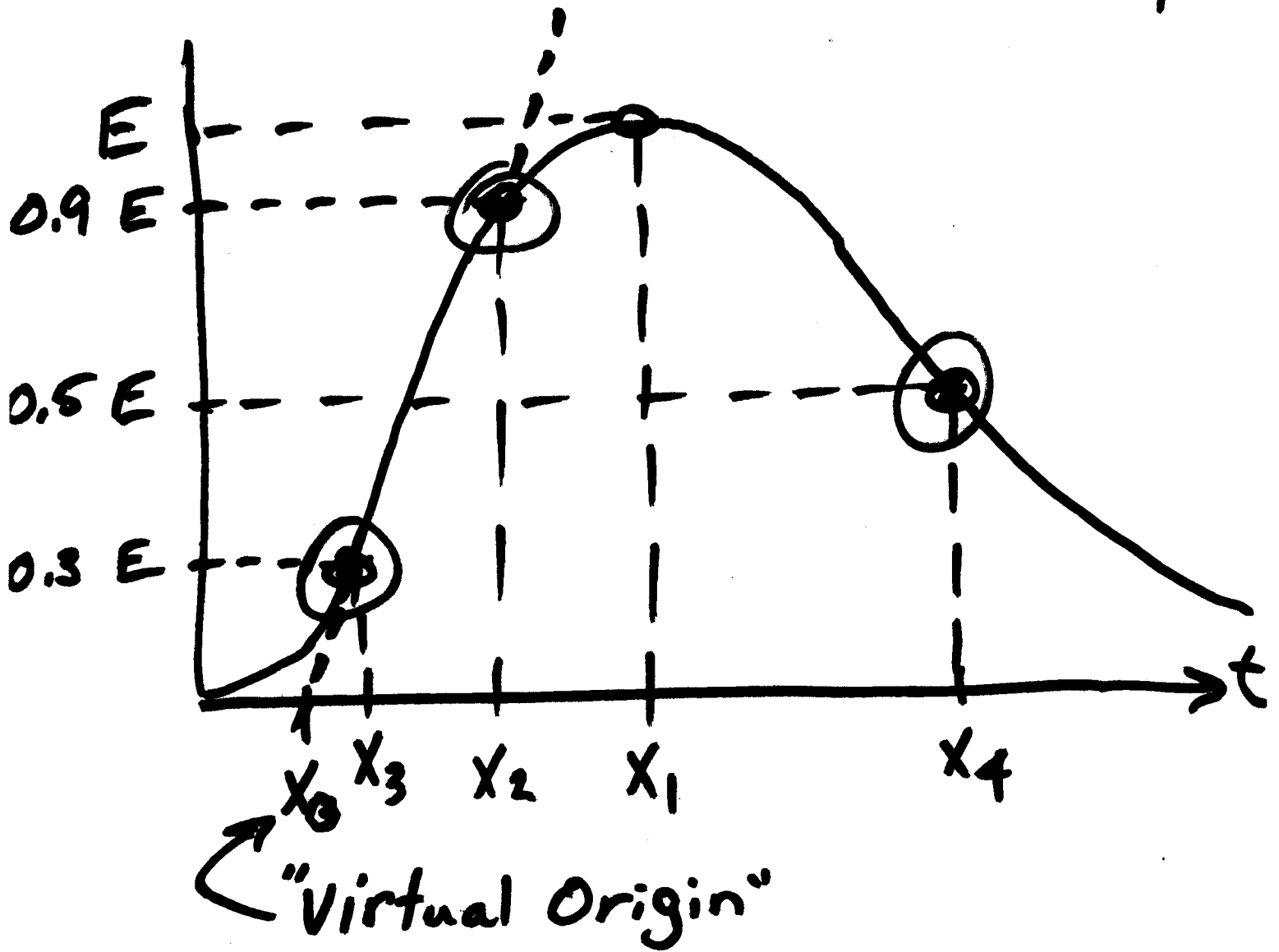

Standard Reference:

" $t_f \times t_t$ "  $t_f = 1.6(x_2 - x_3)$

$t_t = (x_4 - x_0)$


57.12.90

Stds:  $1.2 \times 50 \mu s$  (Lightning Surges)  
 $5 \times 200 \mu s$  (impulse)

# Waveshapes:


11

- "Double Exponential"

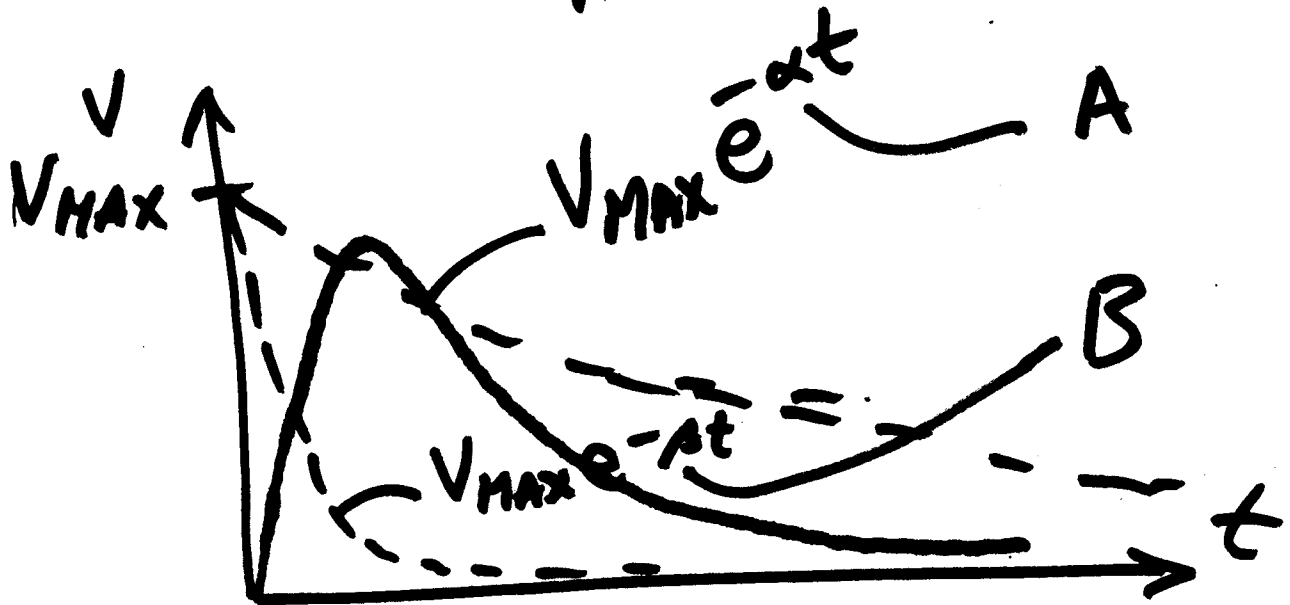


Difference:  $v(t) = V_{MAX}(e^{-at} - e^{-bt})$

CRUDE APPROX:

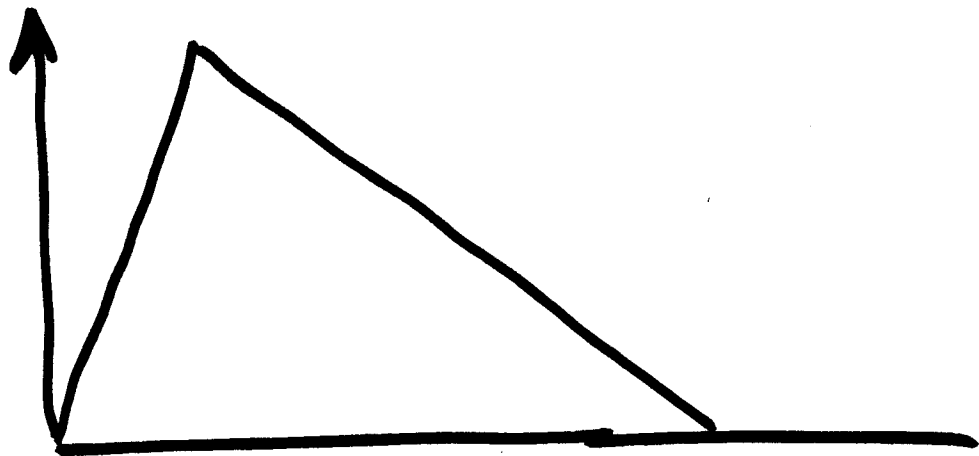

Type 15  
SURGE

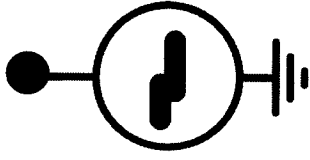

Name : SURGE - Surge function. Two exponentials. TYPE 15.

Card : SOURCE

Data : U/I= 0: Voltage source.

-1: Current source.

Amp= Constant in [A] or [V].

Does not exactly correspond to the peak value of surge.

A= Negative number specifying falling slope.

B= Negative number specifying rising slope.

Tsta= Starting time in [sec.]. Source value zero for  $T < Tsta$ .

Tsto= Ending time in [sec.]. Source value zero for  $T > Tsto$ .

Node : SU= Positive node of exponential surge function.

Negative node is grounded.

$SU = Amp * (exp(A*t) - exp(B*t))$

RuleBook: VII.C.5

Component: SURGE

Attributes

DATA	UNIT	VALUE	NODE	PHASE	NAME
Amplitude	Volt	200000	SU	1	SRC
A	1/s	-20000			
B	1/s	-100000			
Tstart	s	0.01			
Tstop	s	1000			

Copy Paste enter data grid Order: 0 Label:

Comment:

Type of source  
 Current  
 Voltage

High   
 Lock

Edit definitions OK Cancel Help

- ATP Sim Pointer
- Concept...

## Cascading Line Section




How to model?

See Figs 11.32  $\rightarrow$  11.35

Options:

- Cascading  $\pi$  Section (TNA)
- Distributed parameter "long line" models.

consisting of three sections as shown in Figure 3.2. In this case the line is energized at one end and open at the far end. For this example we consider the very first time step when  $t = t_1$  and  $t - \Delta t = t_0 = 0$ .

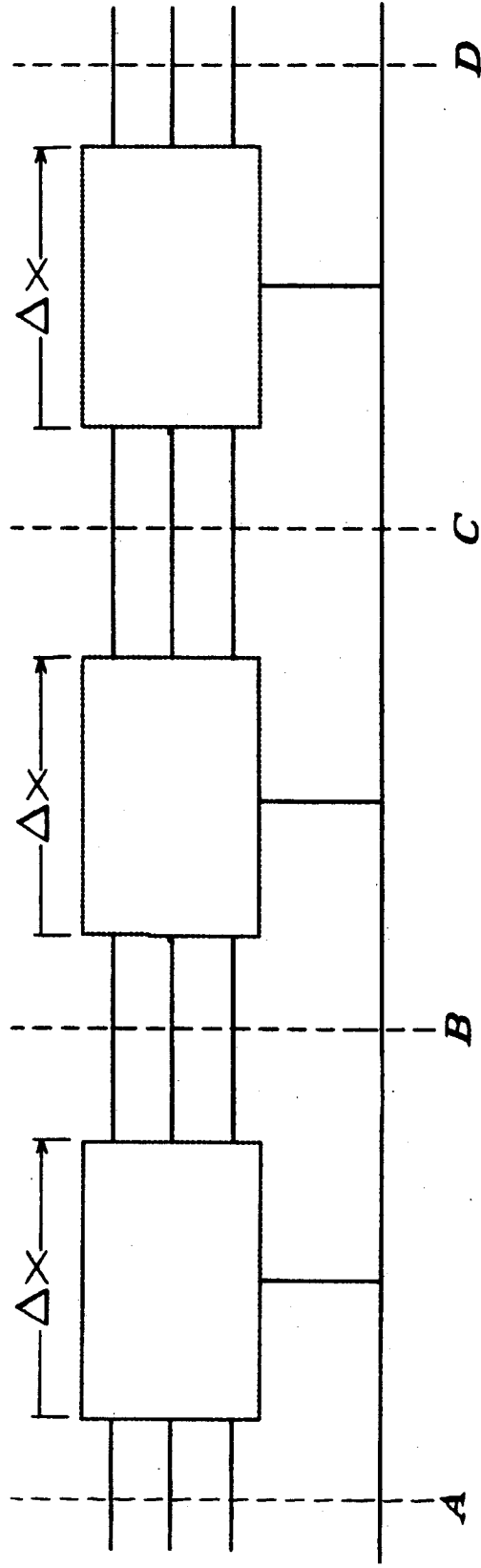

**Figure 3.2** Transmission line divided into three sections.

Equations (3.18)-(3.23) are a set of six equations (two for each section) which describe the current and voltage relations along the line. They are listed here as follows:





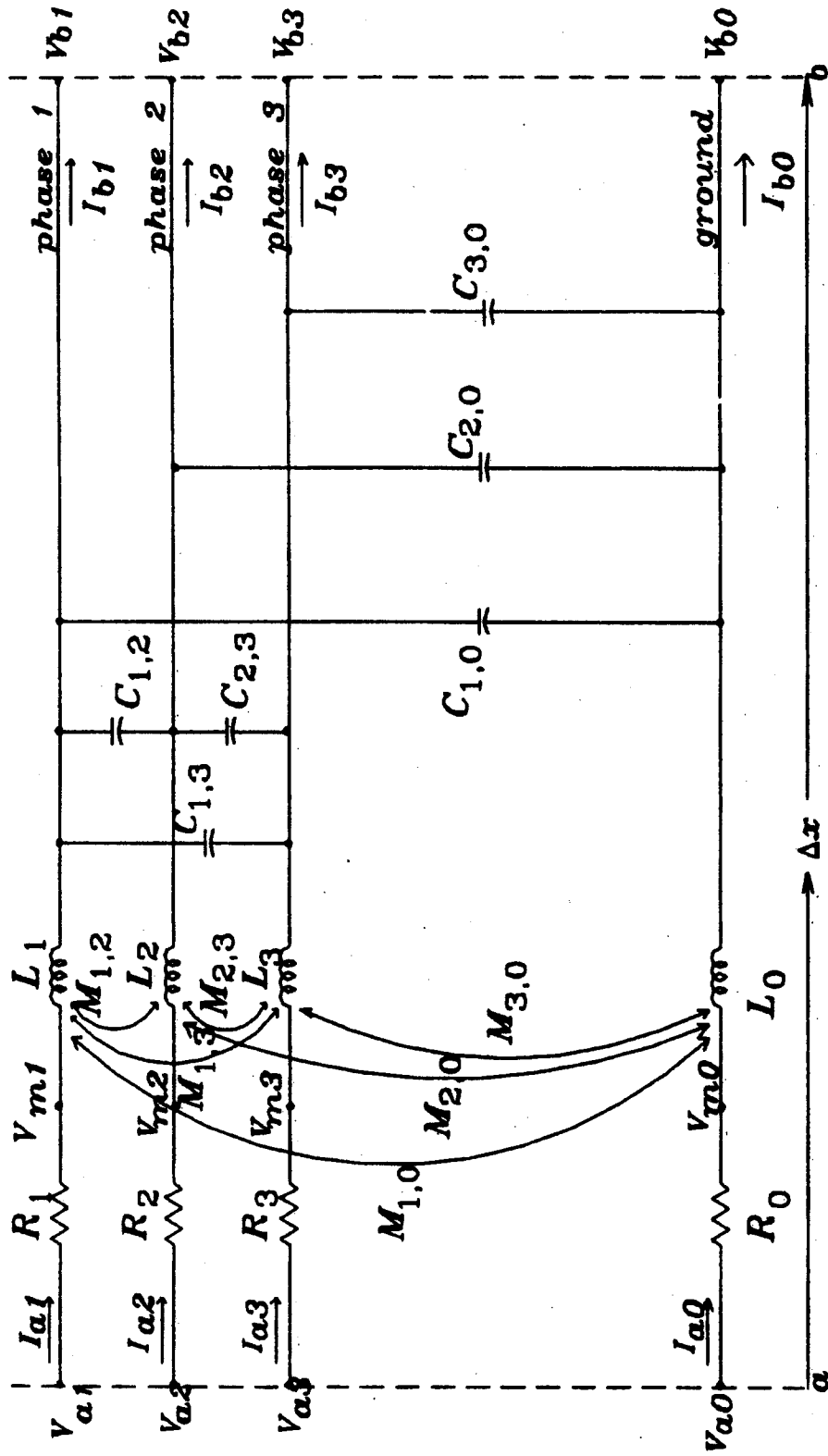



Figure 3.1 Detailed Representation of a transmission line element

1999 MS Thesis - 21 MORK / GORAKUMAR ✓

$$\underbrace{[G]}_{\text{near-singular}} [A]^{-1} = [F]$$

near-singular  
 How does  $\Delta t$  affect  $G$ ?

$$\frac{\Delta t}{2C_H}$$

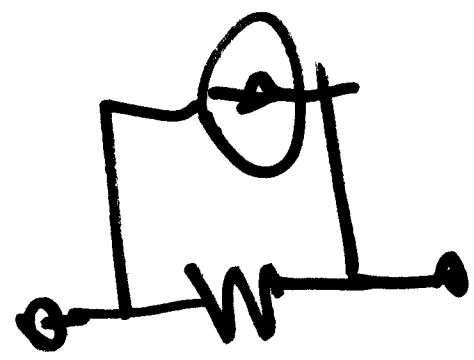

$\{ \} \Rightarrow$  function of  $\Delta t$

size in the stable range is much larger than required for most transient studies.


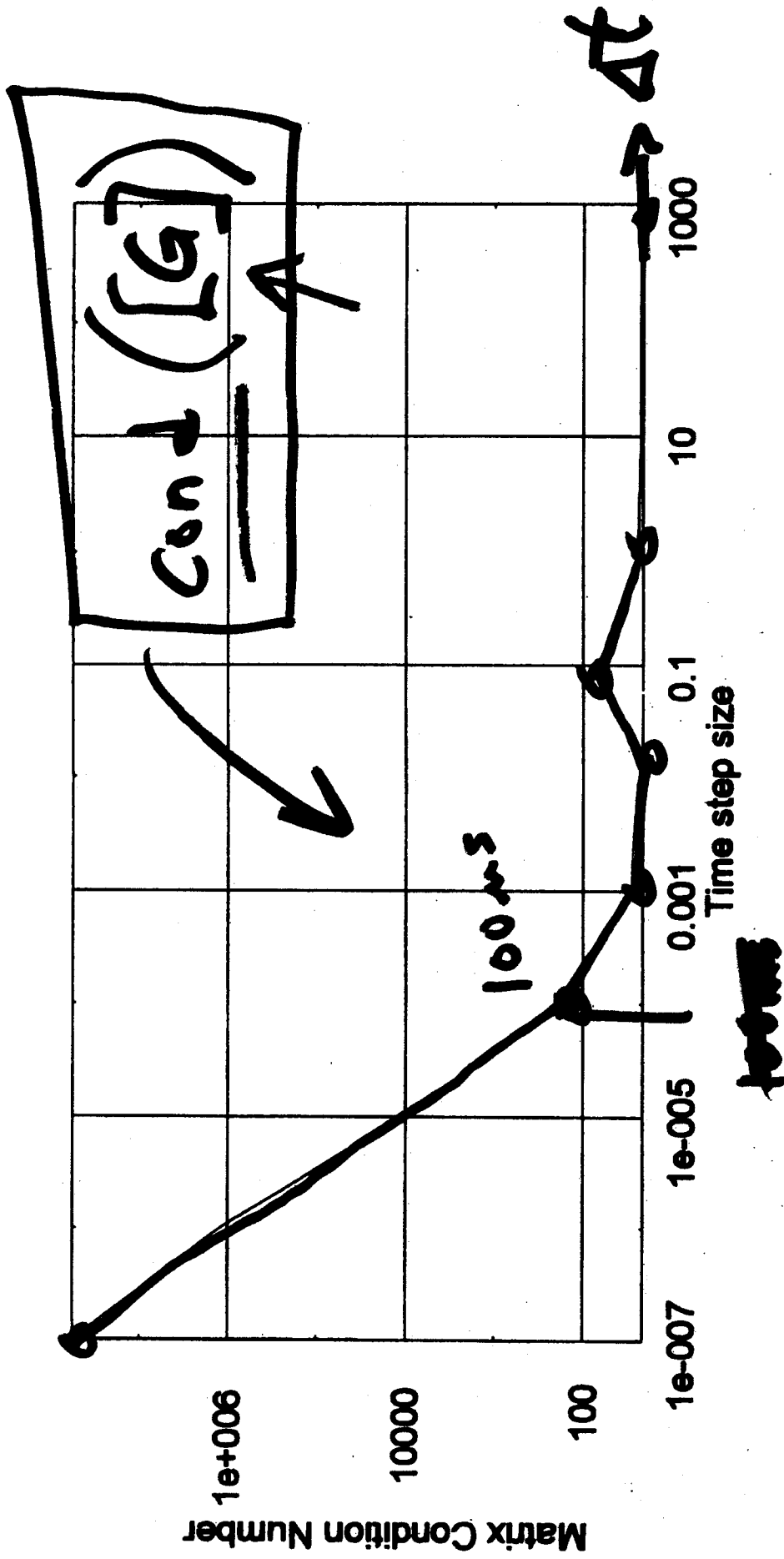


Figure 4.4 Variation of the coefficient matrix condition number with time step size.

Cond( $\gamma$ )

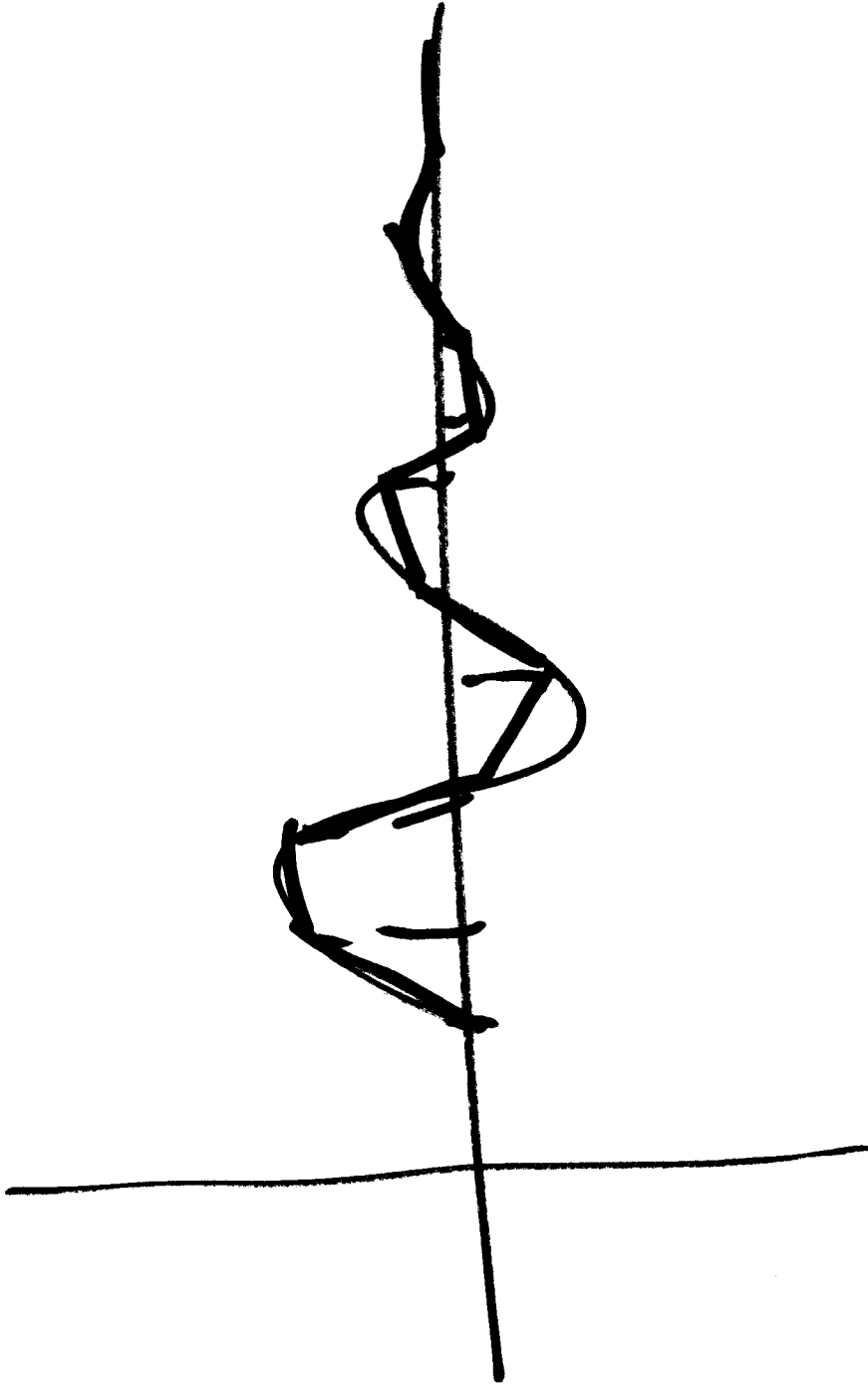

Note: Therefore, at a given value of  $\omega$ , can exactly represent a T-line by equiv  $Z \approx \frac{Y}{2}$ .


Error at other frequencies depends on parts of eqn that are in the brackets.

$$\text{If } \frac{\sinh j\omega\sqrt{L_1C_1}}{j\omega\sqrt{L_1C_1}} \approx 1 \approx \frac{\tanh \frac{1}{2} j\omega\sqrt{L_1C_1}}{\frac{1}{2} j\omega\sqrt{L_1C_1}}$$

then error is small. (Happens when  $\sqrt{L_1C_1}$  is small)

if  $\sqrt{L_1C_1} = x\sqrt{LC}$  ( $L \neq C$  are  $\mu/m$  &  $F/m$ )

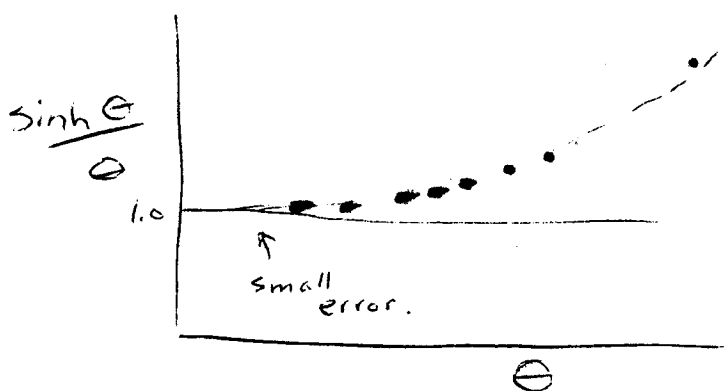\* then freq error is related to length  $x$  of line. (Error is usually small if  $x < \frac{2}{7}$  for highest freq being considered.)



$f$	$\frac{2}{7}$
100 Hz	745 km
1000 Hz	74.5 km
3 kHz	24.8 km
10 kHz	7.45 km
30 kHz	2.48 km
100 kHz	.745 km

To increase accuracy, we can cascade  $\pi$ -equiv sections. (p. 368). (fig 11.33) Practical soln if using TNA.

$$I_{nx} = E Z_0 (t - \tau) \text{ i.e. step function.}$$

Fig. 11.35 - 8  $\pi$ -sections  $\Rightarrow$  8 resonances.  
Only valid up to about 2 kHz.

... in the absence of losses, a step travels along the line undistorted. In Section 9.1 we pointed out in connection with Fig. 9.1b that when a ladder network is energized, some influence, no matter how slight, is felt at the remote end immediately after energization. The question is, how big is this effect? Carslaw and Jaeger [32] have addressed themselves to this problem.

They consider a step of voltage  $E$  applied to a line with  $n$  sections per unit length. A line of length  $x$  will therefore have  $nx$  sections. If the inductance

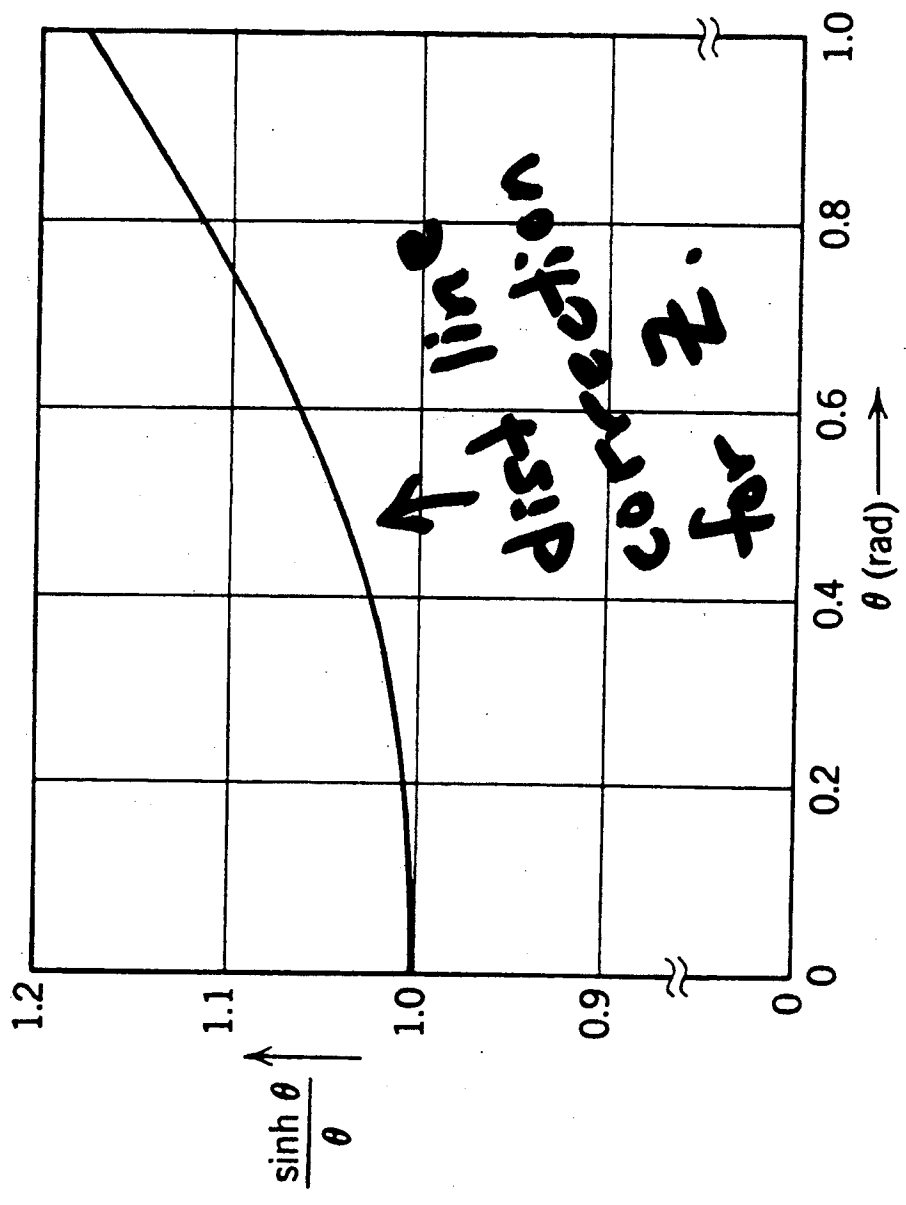


Fig. 11.32. Function  $\sinh \theta / \theta$  plotted against  $\theta$ .

are perhaps better illustrated in Fig. 11.34, which shows the response of an artificial transmission line made up of  $\pi$  sections to a step of voltage applied

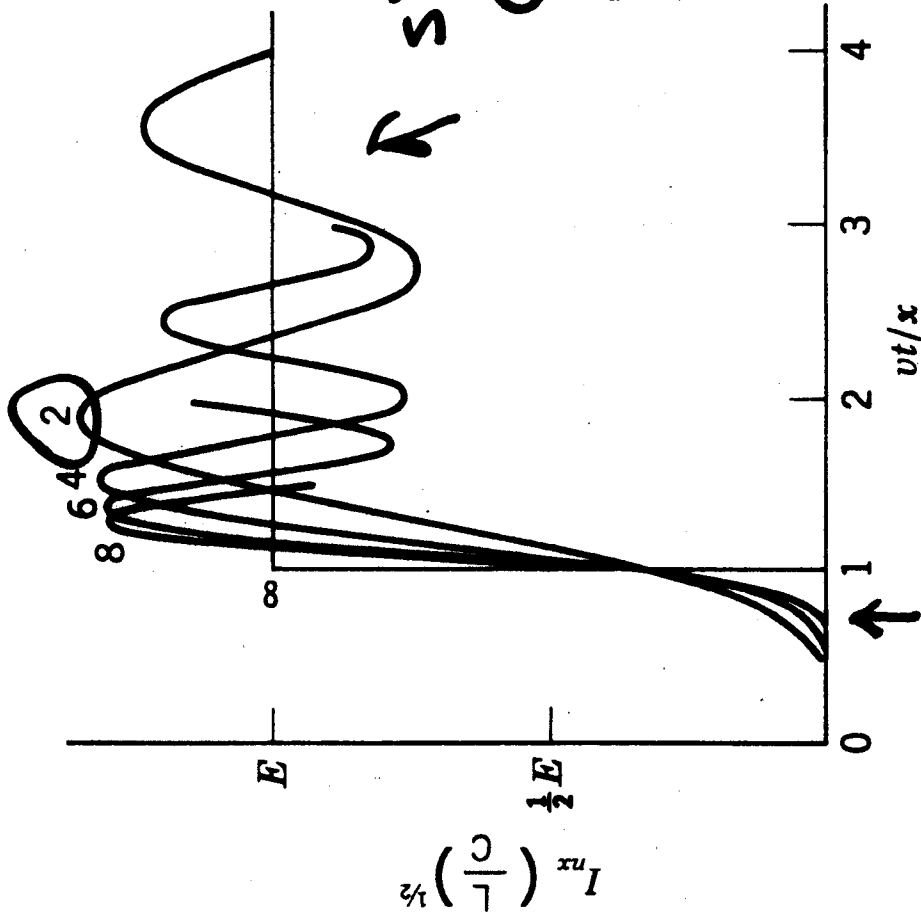


Fig. 11.33. Current leaving the  $n$ th section of an artificial line as a consequence of a step stimulus.

9




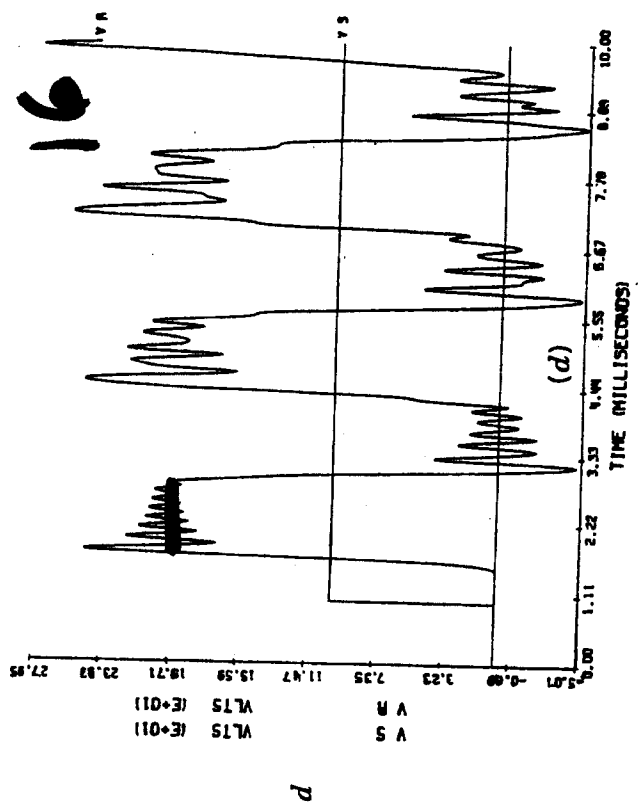
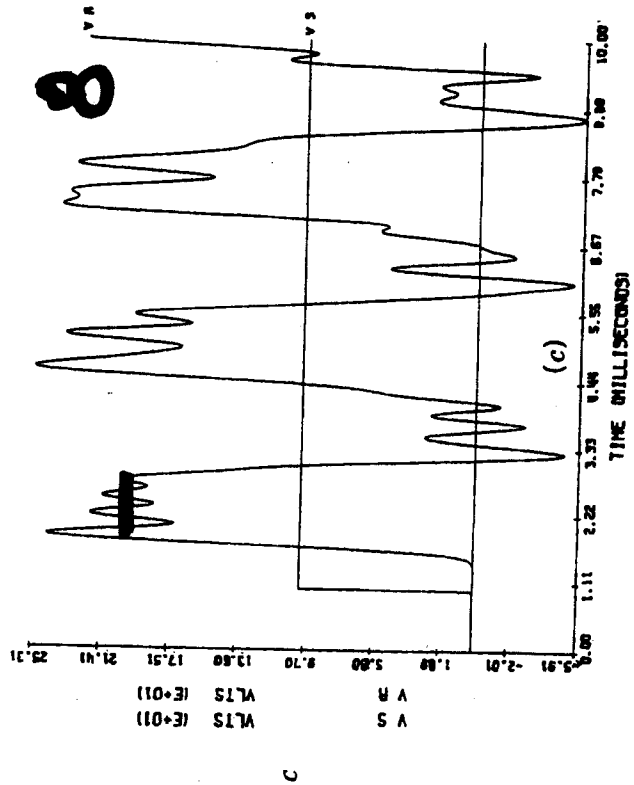
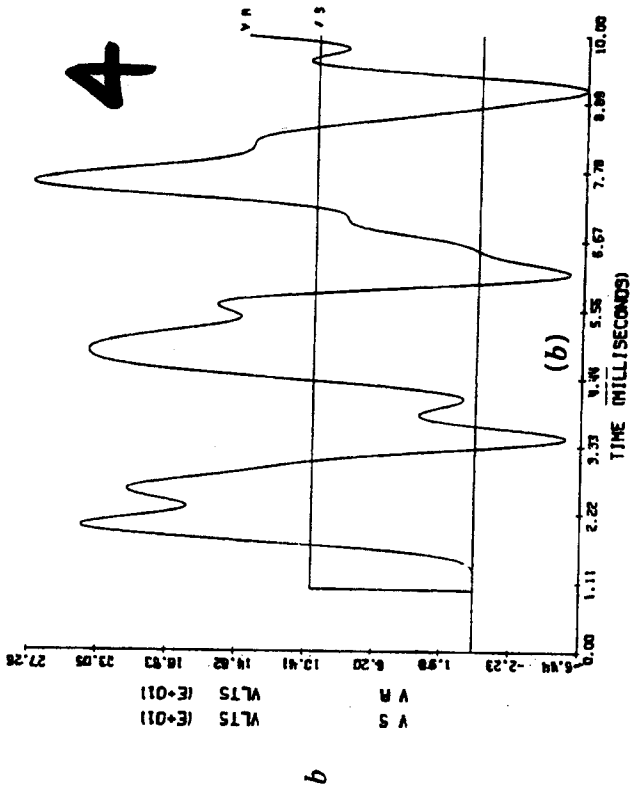
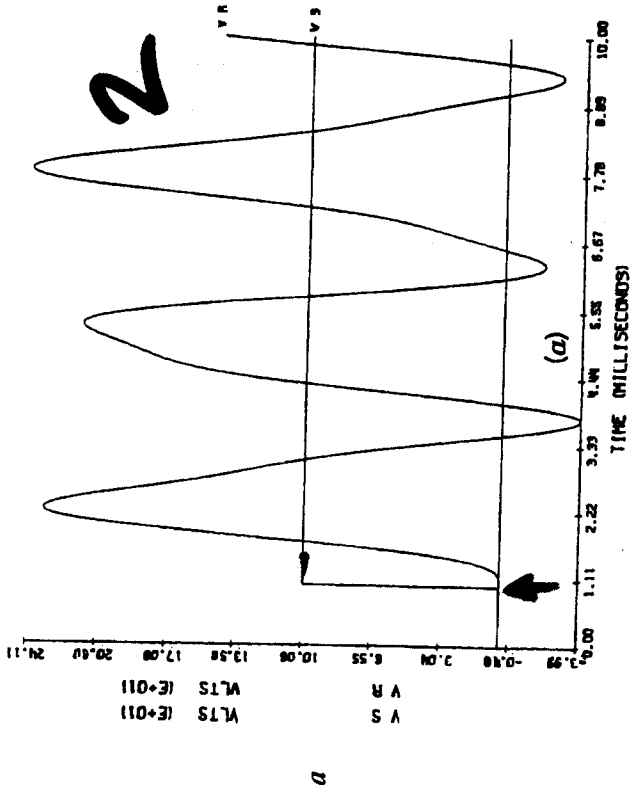


Fig. 11.34. Voltage at the remote end of a 200 km artificial line made up of  $\pi$  sections, following the application of a voltage step at the sending end: (a)  $2\pi$  sections, (b)  $4\pi$  sections, (c)  $8\pi$  sections, (d)  $16\pi$  sections (Courtesy of August6 Brandão).

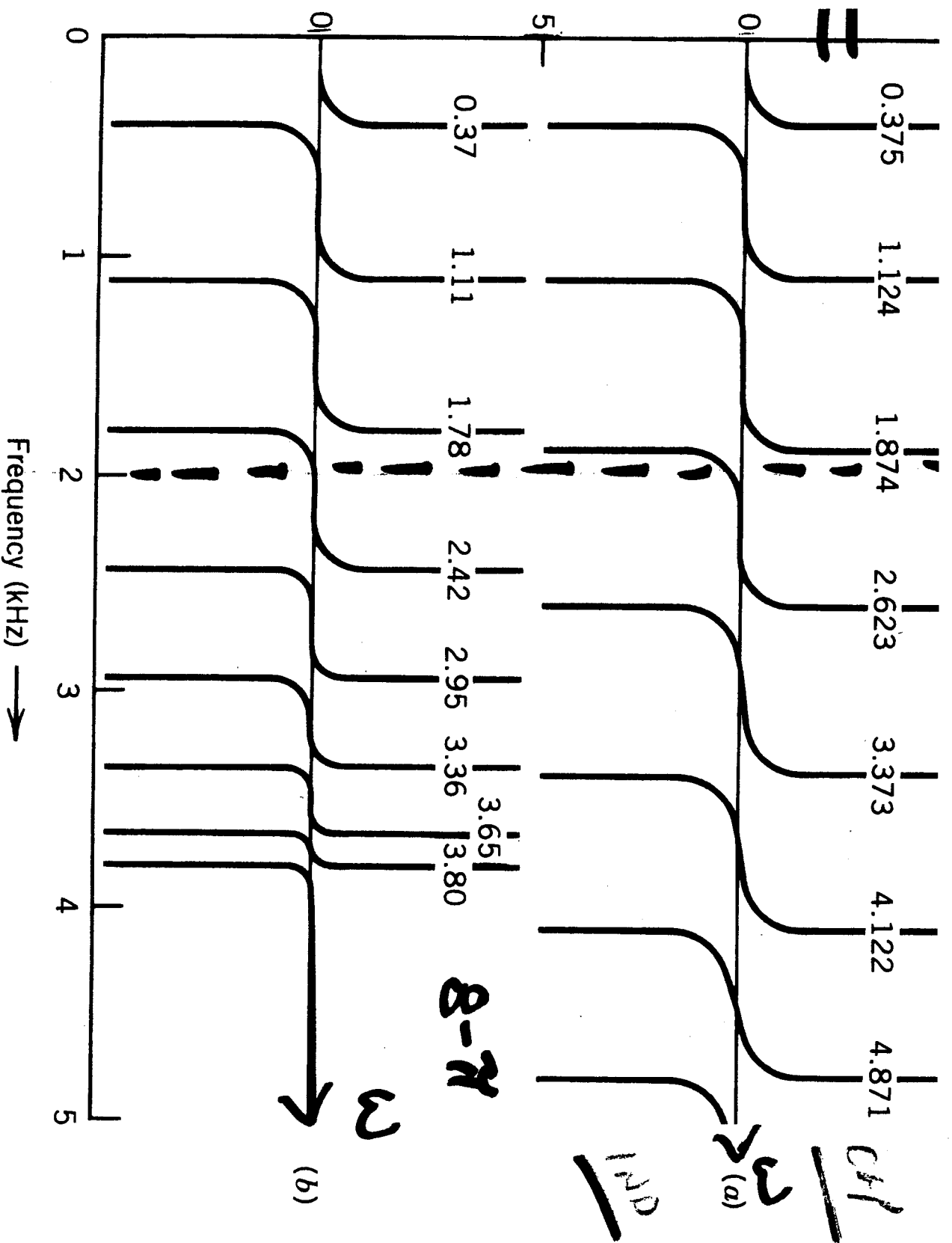

1.35. Admittance versus frequency plot for a 200 km single phase transmission  
 a) true line, (b) model comprising eight  $\pi$  sections.

# Electric Circuit

# Controls

## MODELS

- Language

## TACS

- S-Block

- Functional blocks

