

Topics for Today:

- Introductions: course syllabus (being updated)
- Startup
 - Book
 - Software: Matlab, (Cyme, Aspen may be used for benchmarking)
 - Access to EERC 134 (SGOC - Smart Grid Operations Center)
 - May be useful to buy 3-ring binder
 - Use grid paper or white paper for homework submissions.
- Quick Review of Mesh and NODE equations
- Matrix formulations
- Possible Solution Methods
- Buy book, scan through Chapters 1 and 2 for Wed
- Matlab tutorials for beginners, posted on EE5200 web page.
- Pre-Req review notes and video, posted on EE5200 web page

1/2

Traditional

- Data Structures
- Algorithms
- Applications

"BIG DATA"

[Y]

Matlab


- Cyme
- Aspen

New

- Servers
- Dynamic Flow of data
- Dist Process Algorithms

1/2



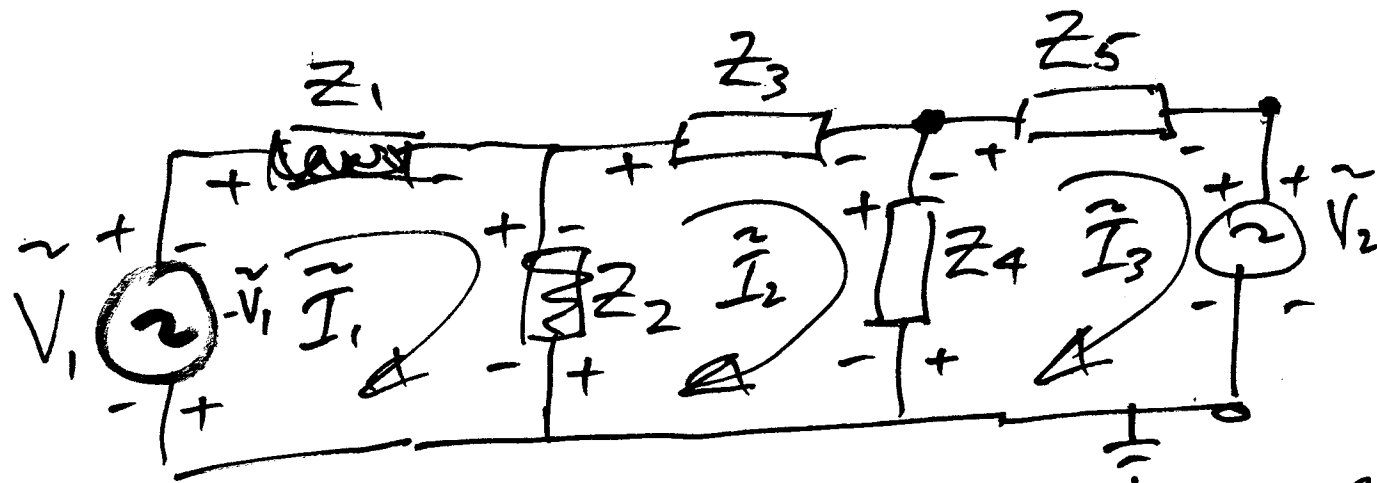

Mesh 1: $\tilde{V}_1 = Z_1 \tilde{I}_1 + Z_2 (\tilde{I}_1 - \tilde{I}_2)$
Mesh 2: $0 = Z_2 (\tilde{I}_2 - \tilde{I}_1) + Z_3 \tilde{I}_2 + Z_4 (\tilde{I}_2 - \tilde{I}_3)$
Mesh 3: $-\tilde{V}_2 = Z_4 (\tilde{I}_3 - \tilde{I}_2) + Z_5 \tilde{I}_3$

KVL
 $\sum V_s = 0$

In Matrix Form:

$$\begin{bmatrix}
 \underline{z_1 + z_2} & -z_2 & 0 \\
 -z_2 & \underline{z_2 + z_3 + z_4} & -z_4 \\
 0 & -z_4 & \underline{z_4 + z_5}
 \end{bmatrix}
 \begin{bmatrix}
 \tilde{I}_1 \\
 \tilde{I}_2 \\
 \tilde{I}_3
 \end{bmatrix}
 =
 \begin{bmatrix}
 \tilde{V}_1 \\
 0 \\
 -\tilde{V}_2
 \end{bmatrix}$$


$\underbrace{\hspace{15em}}_{Z_{\text{LOOP or } \underline{\underline{Z_{\text{MESH}}}}}}$
Mesh Currents
Mesh Voltage Sources
(usually L-G)

$Z_{NN} = \sum Z_s$ around mesh N (Self-impedance of mesh)
 $Z_{NK} = -\sum Z_s$ that are mutual to meshes N & K ,

\tilde{I}_s are mesh currents - not much use in power system analysis.

\tilde{V}_s usually node voltages, but at inner node of Gen.

Node Egn.

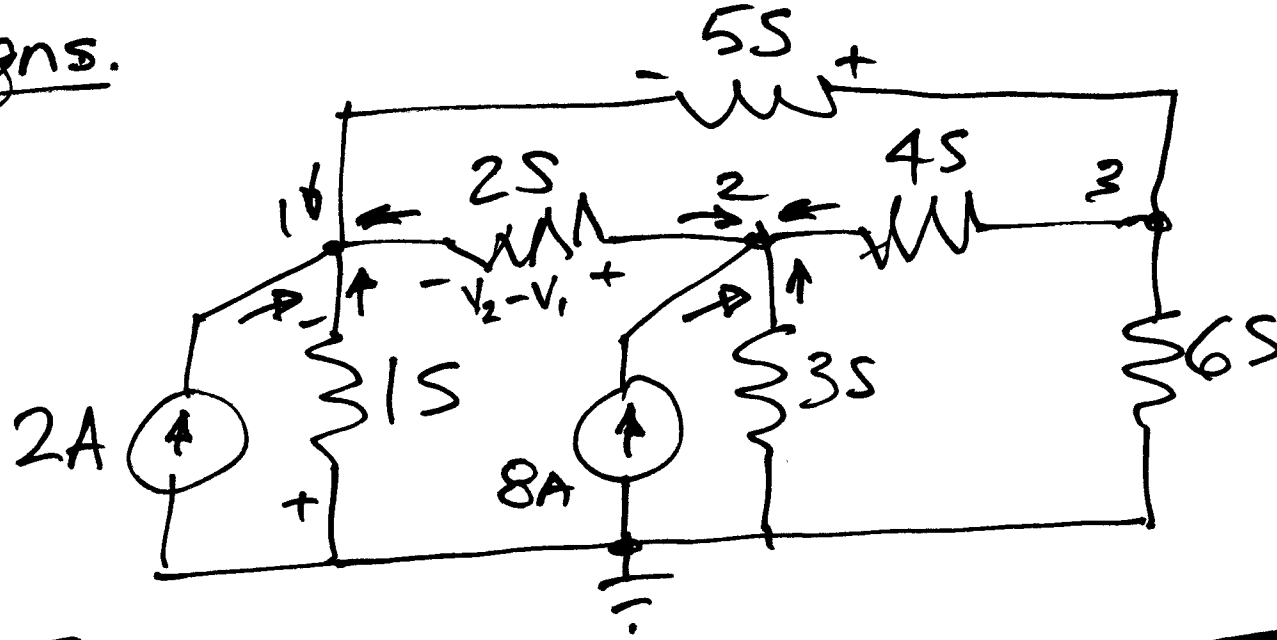

KCL: $\sum I_S(I_N) = 0$

Node 1

Node 2

Node 3

$$\begin{aligned} 2 + (V_2 - V_1)2 + (V_3 - V_1)5 + (-V_1)1 \\ 8 + (V_1 - V_2)2 + (V_3 - V_2)4 + (-V_2)3 \\ 0 + (V_2 - V_3)4 + (V_1 - V_3)5 + (-V_3)6 \end{aligned}$$

In Matrix Form:

$$\begin{bmatrix} 8 & -2 & -5 \\ -2 & 9 & -4 \\ -5 & -4 & 15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 8 \\ 0 \end{bmatrix}$$

Nodal Admitt. Matrix Node Vs Injected Currents

$$[Y_N] \text{ or } [Y_{Bus}]$$

$y_{NN} = + \sum$ Admittances "landing" on node N

$y_{NK} = - \sum$ Admittances "spanning" between nodes N & K.

Typical System: Lots of zeroes in off-diagonal elements

Exploit this by not store zero values.

Use SPARSE Matrix methods

Key Points:

$$\begin{aligned} [Z_{\text{MESH}}]^{-1} &= [Y_{\text{MESH}}] \\ \underbrace{[Y_{\text{BUS}}]^{-1}}_{\text{SPARSE}} &= \underbrace{[Z_{\text{BUS}}]}_{\text{FULL}} \end{aligned}$$

From previous example:

$$\underbrace{[Y_{\text{BUS}}]}_{\text{KNOWN}} \underbrace{[V_{\text{BUS}}]}_{\text{UNKNOWN}} = \underbrace{[I_{\text{INJ}}]}_{\text{Knowns (Generators)}}$$

How to solve?

- Brute force
- en situ methods

$$[Y_{\text{BUS}}]^{-1} [Y_{\text{BUS}}] [V_{\text{BUS}}] = [Y_{\text{BUS}}]^{-1} [I_{\text{INJ}}]$$


- Gauss Elimination
- Gauss-Jordan
- LU Factorization

Preferred for large systems

Review -


Passive Voltage Drop
Sign convention

- Motors
- Loads (Impedances)

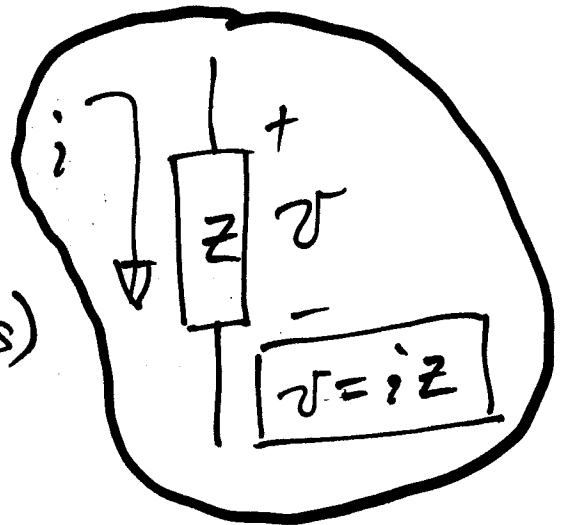

Active Sign Convention

- Generators
(Sources)

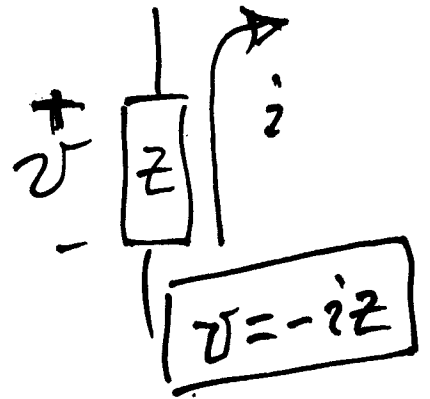


Observations on topology of $[Y_{bus}]$

- Main diagonal is non-zero
- Most off-diagonal terms are zero
(sparse systems) most $y_{nk} = 0$
- Can $[Y_{bus}]$ always be inverted?
(i.e. nonsingular). Singular matrices will produce "divide by zero overflow" and crash program.

Answer: Make sure you have at least one branch to ground/reference!

Ex:

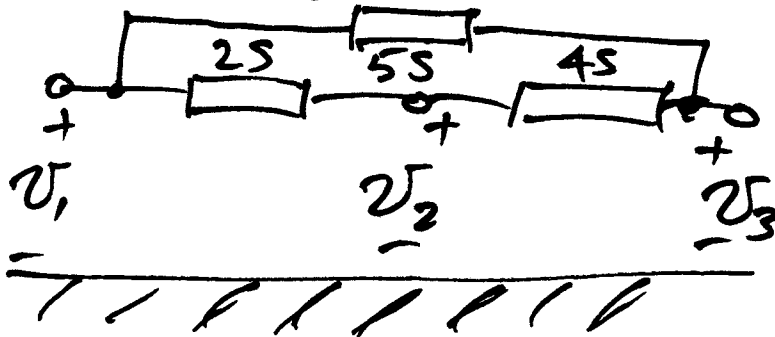

$$[Y_{Bus}] = \begin{bmatrix} +7 & -2 & -5 \\ -2 & +6 & -4 \\ -5 & -4 & +9 \end{bmatrix}$$




Problem to look for:

If Σ of terms in a row is zero, then you're probably dealing with a singular matrix!

TRY TO INVERT with MATLAB!

- Symmetry about main diagonal

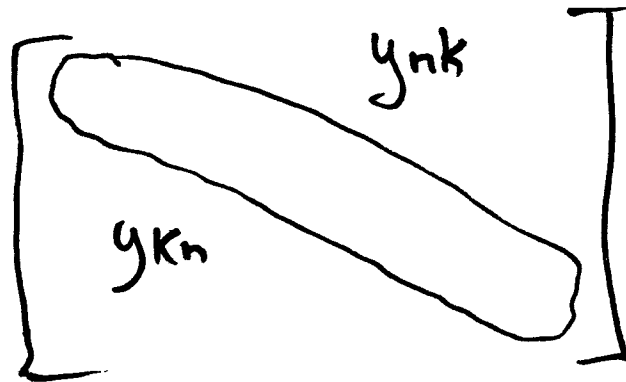

If no dependent sources, ~~transformers~~ or phase-shifting xfmrs, then it will be symmetric.