

- Questions from last lecture?
- How are your matrix math skills?
- Questions on Hmwk #1 ? (Due 5pm Wed).
- Everybody all set w/text, matlab, etc?
- Web page ok? May want 3-ring binder - lots of papers!

TODAY:

- Kron Reduction (network reduction) – refer to Lecture 2.
- Modifications to  $[Y]$  according to system changes
- Switching things in and out: lines, shunt reactors/caps, gens.
- Augmenting the admittance matrix
  - Ungrounded Voltage Source
  - Short Circuit
  - Two-winding Transformer
- Next: in situ methods to solve  $[Y_{bus}] [V_{bus}] = [I_{inj}]$

# Admittance Equations

General Form:

$$\begin{bmatrix} Y_{\text{BUS}} \end{bmatrix} \begin{bmatrix} V_{\text{NODE}} \end{bmatrix} = \begin{bmatrix} I_{\text{INJ}} \end{bmatrix}$$

We can add constraints:


- V source Bus-Bus
- Short
- XFMR
- DEPENDENT SOURCES (OP-AMP)

# SWITCHING LINES, ETC, in and out:

From Lecture 1:

$$[Y] =$$
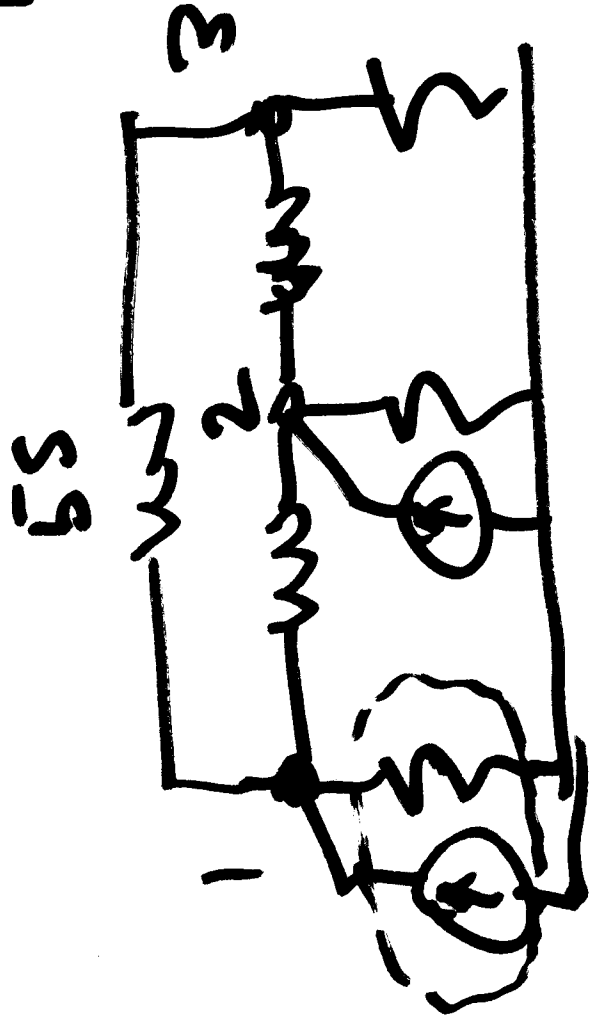
$$\begin{bmatrix} 8 & -2 & -5 \\ -2 & 9 & -4 \\ -5 & -4 & 15 \end{bmatrix}$$



Switch out  
Line 1-3:

$$\begin{bmatrix} 3 & -2 & 0 \\ -2 & 9 & -4 \\ 0 & -4 & 10 \end{bmatrix}$$

$$y_{1-3} = 5S$$

$$\bar{y}_{11} = \bar{y}_{11} - \bar{y}_{1-3}$$



$$\bar{y}_{22} = \bar{y}_{22} - \bar{y}_{2-3}$$

$$\bar{y}_{33} = \bar{y}_{33} - \bar{y}_{3-1}$$

$$\bar{y}_{12} = \bar{y}_{12} + \bar{y}_{1-3}$$

$$\bar{y}_{31} = \bar{y}_{31} + \bar{y}_{3-1}$$

How about a T-Line?

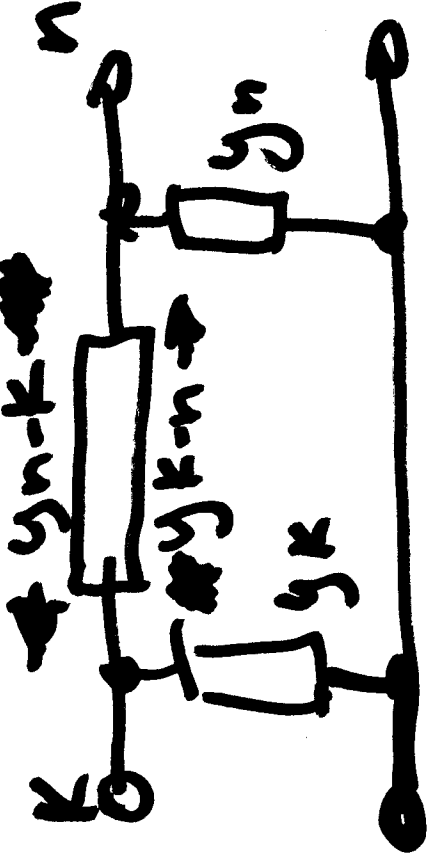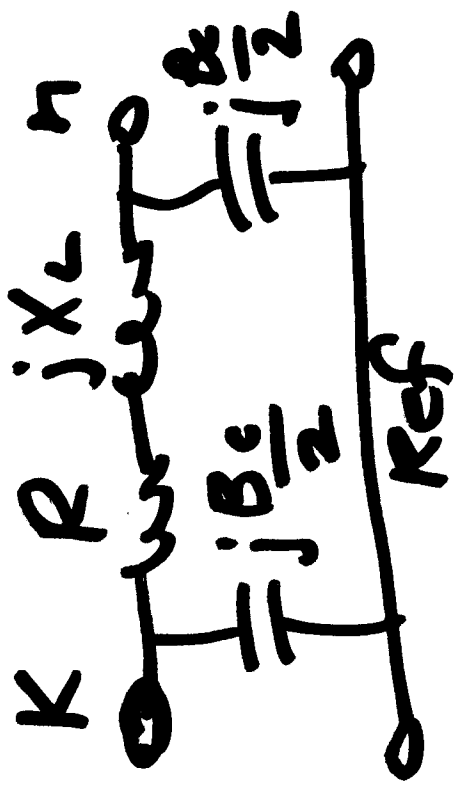

Modify [Y], switch out...?  $C_e$  is full-line Charging susceptance.

$\bar{y}_{kk} = \bar{y}_{kk} - y_k - y_{k-n}$	$\bar{y}_{nn} = \bar{y}_{nn} - y_n - y_{n-k}$
$\bar{y}_{kn} = \bar{y}_{kn} + y_{kn}$	$\bar{y}_{nk} = \bar{y}_{nk} + y_{nk}$

# AUGMENTING $[Y_{bus}]$

$$[Y_{bus}] \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \times$$


$$V_{max} = \begin{bmatrix} 1.00 \\ \vdots \\ 1.00 \end{bmatrix}$$

$$I_{MS} = \begin{bmatrix} 0.00 \\ \vdots \\ 0.00 \end{bmatrix}$$



**COEFFICIENTS  
OF ADD'L EQNS**

# NODE-NODE VOLTAGE SOURCE

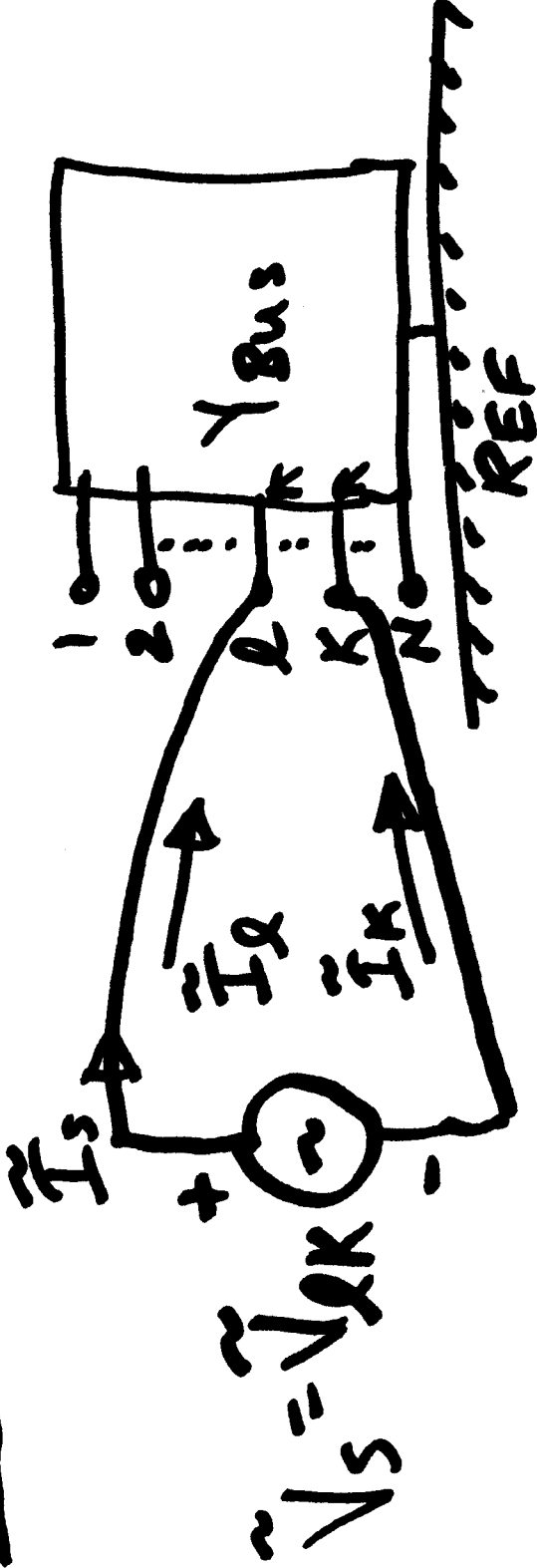


New constraints being added:

$$\textcircled{1} \quad \tilde{V}_s = \tilde{V}_l - \tilde{V}_k = \text{Known (forced voltage)}$$

$$\textcircled{2} \quad \tilde{I}_l = +\tilde{I}_s$$
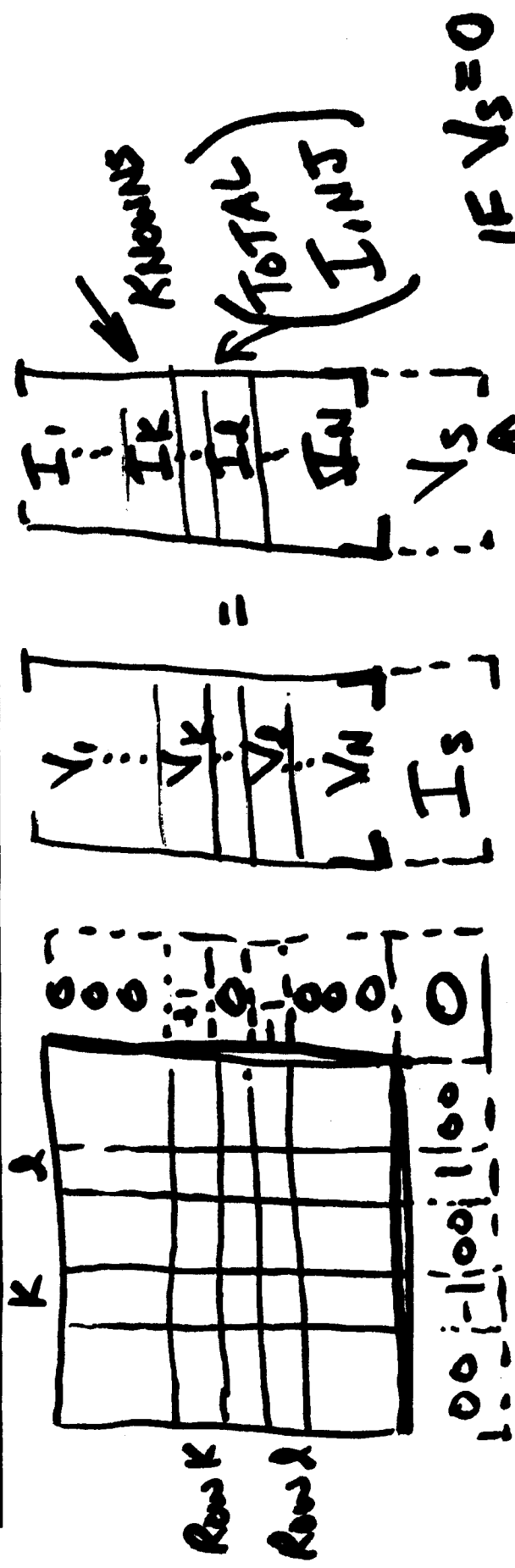
$$\textcircled{3} \quad \tilde{I}_k = -\tilde{I}_s$$




$$\tilde{V}_S = \tilde{V}_l - \tilde{V}_k$$

Note: This effect is on left side of eqn.!

$\left\{ \begin{array}{l} \tilde{I}_l (INS) \text{ is increased by } +\tilde{I}_S \\ \tilde{I}_k (INS) \text{ is "increased" by } -\tilde{I}_S \end{array} \right.$

∴ Change sign when entering in Column  $N+1$  of  $[Y]$ !

# XFMR - IDEAL 2-WINDING

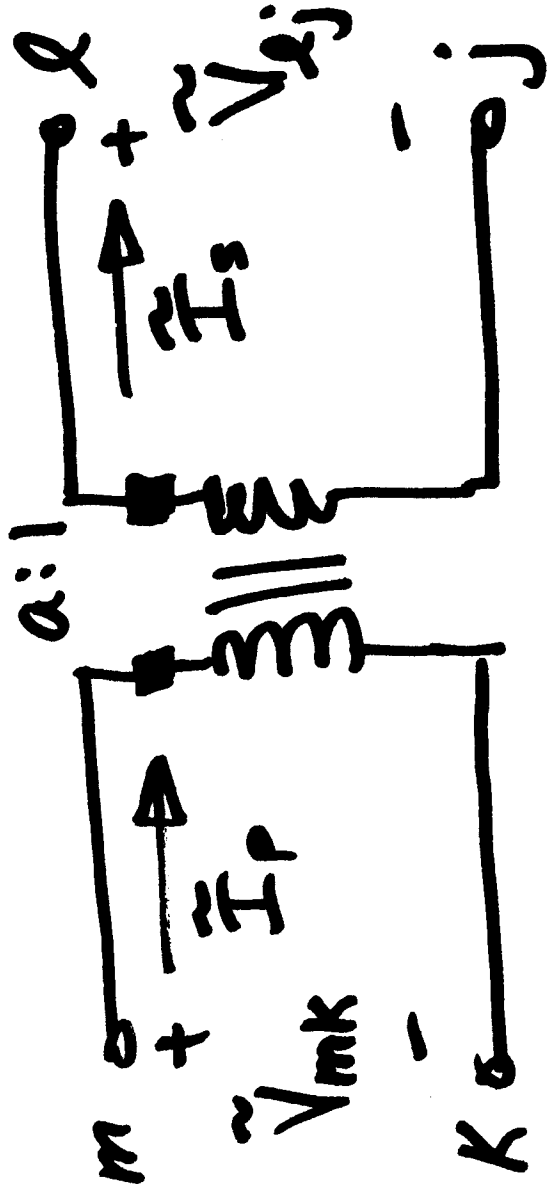


Polarity Marks:  $\vec{I}_p = \vec{I}_s$

$$\tilde{V}_{mk} = \tilde{V}_{sj}$$

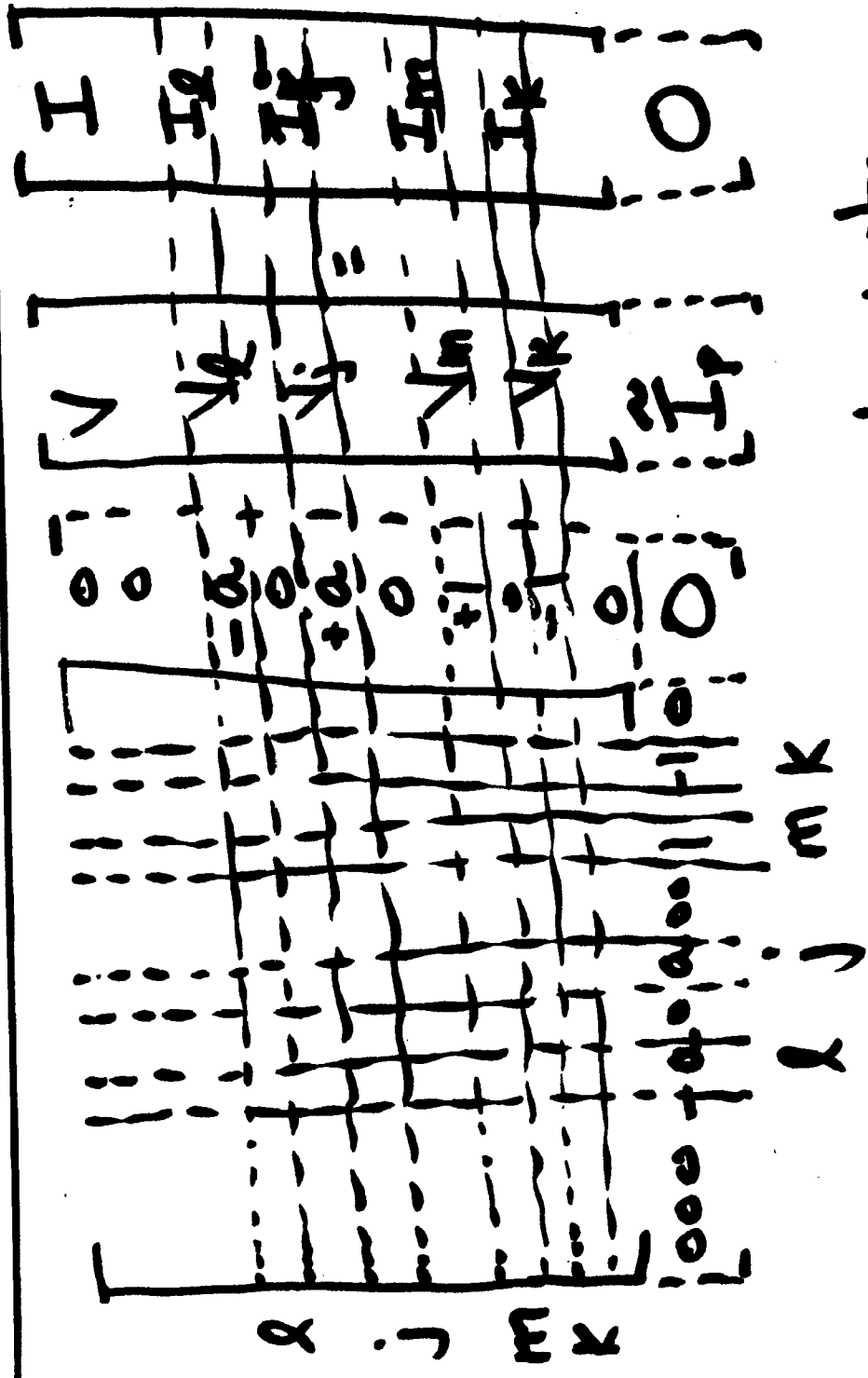The turns ratio "a" is in general, complex.





Aug Row  $\rightarrow$  voltage constraints

Aug Col  $\rightarrow$  current constraints

TYPICAL: INTRODUCE ZERO IN MAIN DIAG!

## Constraints

## Injected Currents: (ADD'L)

$$l: +I_s = a\tilde{I}_P$$

$$j: -\tilde{I}_s = -a\tilde{I}_P$$

$$m: -\tilde{I}_P$$

$$k: +\tilde{I}_P$$

Agg'n in  
effect side  
left side  
of eqns  
Change signs  
in Column N+1  
8 [T]

## NODE VOLTAGES

$$\tilde{V}_m - \tilde{V}_k = a(\tilde{V}_l - \tilde{V}_j)$$

i.e.  $\tilde{V}_{mk} = a\tilde{V}_{lj}$

$$\tilde{V}_m - \tilde{V}_k + a\tilde{V}_j - a\tilde{V}_l = 0$$

General Reference for this is on next page.  
(From Vlach - refer to syllabus reference list).

ELEMENT	SYMBOL	MATRIX	EQUATIONS
CURRENT SOURCE		$\begin{bmatrix} j & -j \\ j' & j \end{bmatrix}$	$I_j = J$ $I_{j'} = -J$
VOLTAGE SOURCE		$\begin{bmatrix} V_j & V_{j'} & I \\ j & j' & I \\ m+1 & 1 & -1 \end{bmatrix}$	$V_j - V_{j'} = E$ $I_j = I$ $I_{j'} = -I$
OPEN CIRCUIT		—	$V = V_j - V_{j'}$
SHORT CIRCUIT		$\begin{bmatrix} V_j & V_{j'} & I \\ j & j' & I \\ m+1 & 1 & -1 \end{bmatrix}$	$V_j - V_{j'} = 0$ $I_j = I$ $I_{j'} = -I$
ADMITTANCE		$\begin{bmatrix} V_j & V_{j'} \\ j & j' \\ y & -y \end{bmatrix}$	$I_j = y(V_j - V_{j'})$ $I_{j'} = -y(V_j - V_{j'})$
IMPEDANCE		$\begin{bmatrix} V_j & V_{j'} & I \\ j & j' & I \\ m+1 & 1 & -1 \end{bmatrix}$	$V_j - V_{j'} - zI = 0$ $I_j = -I_{j'} = I$
NULLATOR		$\begin{bmatrix} V_j & V_{j'} \\ j & j' \\ 1 & -1 \end{bmatrix}$	$V_j - V_{j'} = 0$ $I_j = I_{j'} = 0$
NORATOR		$\begin{bmatrix} I \\ j & j' \\ 1 & -1 \end{bmatrix}$	$V_j, I \text{ ARE ARBITRARY}$
VCT		$\begin{bmatrix} V_j & V_{j'} & I \\ j & j' & I \\ m+1 & 1 & -1 \end{bmatrix}$	$I_j = 0$ $I_{j'} = 0$ $I_k = g(V_j - V_{j'})$ $I_{k'} = -g(V_j - V_{j'})$

Fig. 4.4.1. Ideal elements in the modified nodal formulation without graphs.

ELEMENT	SYMBOL	MATRIX	EQUATIONS
VVT		$\begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I \\ j & j' & k & k' & I \\ m+1 & 1 & \mu & 1 & -1 \end{bmatrix}$	$-\mu V_j + \mu V_{j'} + V_k - V_{k'} = 0$ $I_k = I$ $I_{k'} = -I$
CCT		$\begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I \\ j & j' & k & k' & I \\ m+1 & 1 & 1 & -1 \end{bmatrix}$	$V_j - V_{j'} = 0$ $I_j = -I_{j'} = I$ $I_k = -I_{k'} = \alpha I$
CVT		$\begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I_1 & I_2 \\ j & j' & k & k' & I_1 & I_2 \\ m+1 & 1 & -1 & -1 & -r_1 & -r_2 \end{bmatrix}$	$V_j - V_{j'} = 0$ $V_k - V_{k'} - r_1 I_1 = 0$ $I_j = -I_{j'} = I_1$ $I_k = -I_{k'} = I_2$
OPERATIONAL AMPLIFIER		$\begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I \\ j & j' & k & k' & I \\ m+1 & 1 & -1 & -1 \end{bmatrix}$	$V_j - V_{j'} = 0$ $I_k = -I_{k'} = I$
CONVERTOR		$\begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I \\ j & j' & k & k' & I \\ m+1 & 1 & -1 & -K_1 & K_2 \end{bmatrix}$	$V_j - V_{j'} - K_1 V_k + K_2 V_{k'} = 0$ $I_j = -I_{j'} = I$ $I_k = -I_{k'} = -K_2 I$ FOR IDEAL TRANSFORMER $K_1 = K_2 = n$
TRANSFORMER		$\begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I_1 & I_2 \\ j & j' & k & k' & I_1 & I_2 \\ m+1 & 1 & -1 & -1 & 1 & -1 \\ m+2 & 1 & -1 & -1 & -\alpha L_1 & -\alpha M \\ & & & & & -1 & -1 & -\alpha M & -\alpha L_2 \end{bmatrix}$	$V_j - V_{j'} - \alpha L_1 I_1 - \alpha M I_2 = 0$ $V_k - V_{k'} - \alpha M I_1 - \alpha L_2 I_2 = 0$ $I_j = -I_{j'} = I_1$ $I_k = -I_{k'} = I_2$

Fig. 4.4.1. (Continued)