

Introduction to Resistor Circuits

(Tom Co 1/17/2008)

I. Voltage and Current

A. Definitions and Units

1. Current (I) = amount of electrical charge flowing per unit time

Units: 1 ampere (A) = 1 coulomb/second

2. Voltage (V): potential energy per unit charge
(also known as electromotive force, emf)

Units: 1 volt (V) = 1 joule/coulomb

3. Power (P): power (energy per unit time)

Units: 1 watt (W) = 1 joule/second

$$P = VI$$

B. Conventions

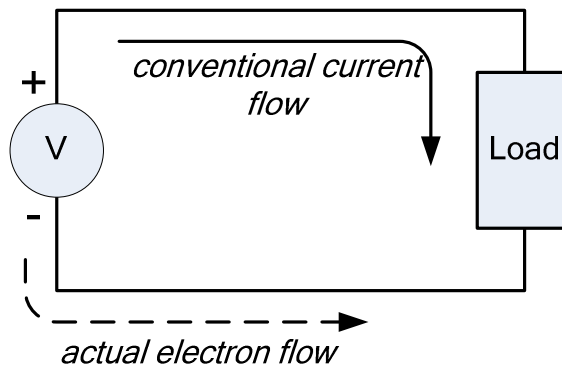


Figure 1. Electrical Loop

II. Resistors and Ohm's Law:

$$\text{Resistance (R)} = \frac{V}{I}$$

Units: 1 ohm (Ω) = 1 volt/ampere

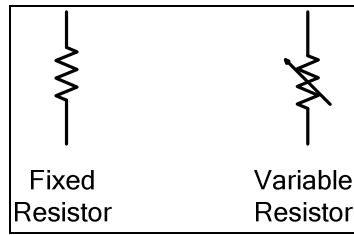


Figure 2. Symbols for Resistors.

Main application of resistors: to set the current flow in a wire for a given voltage.

An Analogy with Pipe Flow:

Voltage	Differential pressure (driving force)
Current	Volumetric flow rate
Resistance	Flow resistance

Main application of resistors: to set the current flow in a wire for a given voltage.

III. Kirchoff's Laws

a) Sum of voltage around a closed loop is zero

b) Sum of current at a junction is zero

Some conventions:

a) V_a = voltage at point a with respect to ground.

b) V_{ab} = $V_a - V_b$.

c) I_{ab} = current flow from point a to point b .

d) V_{ab} = $-V_{ba}$

e) I_{ab} = $-I_{ba}$

f) P_{ab} = $V_{ab} I_{ab}$

Loop A: $V_{ga} + V_{ab} + V_{bd} + V_{de} + V_{ef} + V_{fg} = 0$

Loop B: $V_{db} + V_{bc} + V_{ce} + V_{ed} = 0$

Junction a: $I_{ga} + I_{ba} = 0$

Junction b: $I_{ab} + I_{db} + I_{cb} = 0$

Junction c: $I_{bc} + I_{ec} = 0$

Junction d: $I_{bd} + I_{ed} = 0$

Junction e: $I_{de} + I_{ce} + I_{fe} = 0$

Junction f: $I_{ef} + I_{gf} = 0$

Junction g: $I_{ag} + I_{fg} = 0$

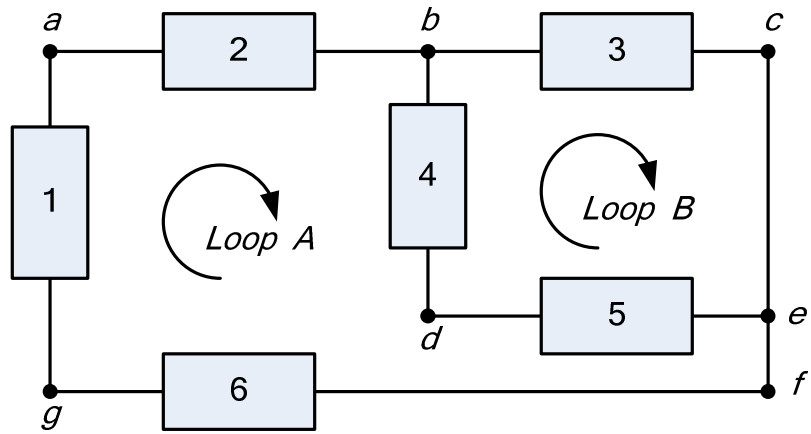


Figure 3.

Example 1:

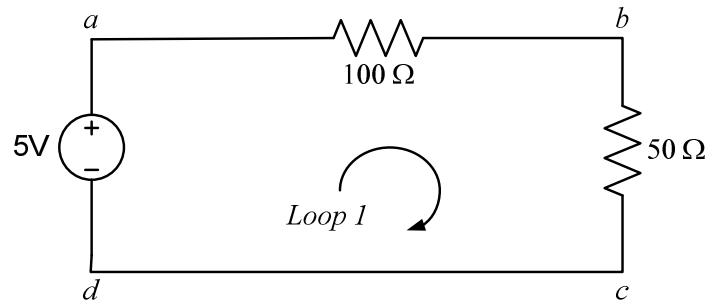


Figure 4.

Determine: V_{ab} , V_{bc} and P_{bc}

Solution:

Step 1. Write out Kirchoff's Law for Voltage and Current

$$\text{Loop 1: } V_{da} + V_{ab} + V_{bc} + V_{cd} = 0$$

$$\text{Junction } a: I_{da} + I_{ba} = 0$$

$$\text{Junction } b: I_{ab} + I_{cb} = 0$$

$$\text{Junction } c: I_{bc} + I_{cd} = 0$$

$$\text{Junction } d: I_{ad} + I_{cd} = 0$$

Step 2. Substitute given voltage sources, implement Ohm's law and rewrite in terms of current with subscripts in set order (e.g. alphabetical in our case).

$$\text{Loop 1: } -5 + 100I_{ab} + 50I_{bc} + 0I_{cd} = 0$$

$$\text{Junction } a: -I_{ad} - I_{ab} = 0 \rightarrow -I_{ad} = I_{ab}$$

$$\text{Junction } b: I_{ab} - I_{bc} = 0 \rightarrow I_{bc} = I_{ab}$$

$$\text{Junction } c: I_{bc} - I_{cd} = 0 \rightarrow I_{cd} = I_{bc} = I_{ab}$$

$$\text{Junction } d: I_{ad} - I_{cd} = 0 \rightarrow I_{ad} = I_{ab}$$

Step 3. Solve for all the currents I_{ij} and calculate the desired values in the circuit.

$$I_{ab} = \frac{1}{30} \text{ amp} = I_{bc} = I_{cd} = I_{da}$$

$$\rightarrow V_{ab} = \frac{10}{3} \text{ volts}, \quad V_{bc} = \frac{5}{3} \text{ volts}, \quad P_{bc} = \frac{5}{90} \text{ watts}$$

Remarks:

1. Let a circuit consists of one voltage source V_1 and a set of resistors R_1, R_2, \dots, R_n . Then the voltage across resistor R_k is given by

$$V_{(R_k)} = \left(\frac{R_k}{R_1 + \dots + R_n} \right) V_1$$

2. At points that connect only two wires: current flow in = current flow out.
Thus, at point j ,

$$I_{ij} = I_{jk}$$

Example 2:

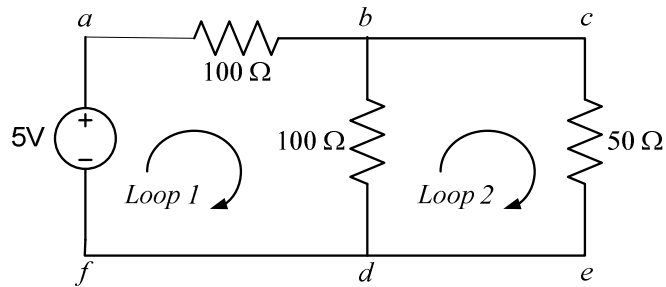


Figure 5.

Determine: V_{ab} , V_{bd} , V_{ce} , I_{bd} , I_{ce} , P_{ce}

Solution:

Step 1. Write out Kirchoff's Law for Voltage and Current

$$\text{Loop 1: } V_{fa} + V_{ab} + V_{bd} + V_{df} = 0$$

$$\text{Loop 2: } V_{bc} + V_{ce} + V_{ed} + V_{db} = 0$$

$$\text{Junction } b: I_{ab} - I_{bd} - I_{bc} = 0$$

$$\text{Junction } d: I_{bd} - I_{de} - I_{df} = 0$$

$$\text{Junction } a \text{ and } f: I_{df} = I_{fa} = I_{ab}$$

$$\text{Junction } c \text{ and } e: I_{bc} = I_{ce} = I_{ed}$$

Step 2. Substitute given voltage sources and implement Ohm's law

$$\text{Loop 1: } -5 + 100I_{ab} + 100I_{bd} = 0$$

$$\text{Loop 2: } 50I_{ce} - 100I_{bd} = 0$$

$$\text{Junction } b: I_{ab} - I_{bd} - I_{ce} = 0$$

$$\text{Junction } d: I_{bd} - I_{ce} - I_{ab} = 0$$

Step 3. Solve for all the currents I_{ij} and calculate the desired values in the circuit.

$$I_{bd} = \frac{1}{80} \text{ amp}$$

$$I_{ce} = I_{bc} = I_{ed} = \frac{2}{80} \text{ amp}$$

$$I_{ab} = I_{fa} = I_{df} = \frac{3}{80} \text{ amp}$$

$$\rightarrow V_{ab} = \frac{300}{80} \text{ volts}; \quad V_{bd} = \frac{100}{80} \text{ volts}; \quad V_{ce} = \frac{100}{80} \text{ volts}$$

Consequence of Kirchoff's law:

a) Series

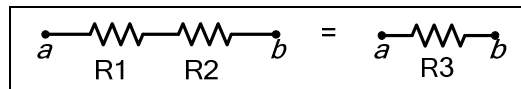


Figure 6.

$$R3 = R1 + R2$$

b) Parallel

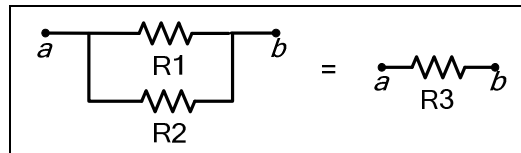


Figure 7.

$$\frac{1}{R3} = \frac{1}{R1} + \frac{1}{R2}$$

$$\rightarrow V_{(R_1)} = V_{(R_2)} = \frac{R_1 R_2}{R_1 + R_2} I_{ab}$$

$$I_{(R_1)} = \frac{R_2}{R_1 + R_2} I_{ab}$$

$$I_{(R_2)} = \frac{R_1}{R_1 + R_2} I_{ab}$$

Example 2 (revisited) :

Using the parallel circuit formula above,

$$V_{bd} = \frac{100 \cdot 50}{100 + 50} I_{ab}$$

Substituting into Loop 1:

$$\begin{aligned} -5 + 100I_{ab} + V_{bd} &= 0 \\ 100I_{ab} + \left(\frac{5000}{150}\right)I_{ab} &= 5 \rightarrow I_{ab} = \frac{5}{100 + \frac{5000}{150}} = \frac{3}{80} \text{ amp} \end{aligned}$$

Drills:

1. Find V_{ab} and V_{bc} for the circuit in Figure 8.

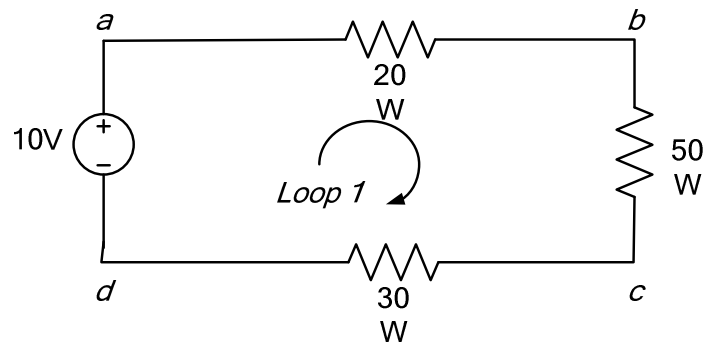


Figure 8.

Answer: $V_{ab}=2$ volts, $V_{bc}=5$ volts

2. Find V_{be} and V_{ef} for the circuit in Figure 9.

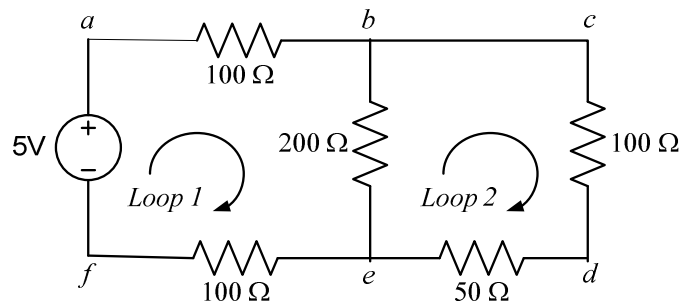


Figure 9.

Answer: $V_{be}=1.5$ volts, $V_{ef}=1.75$ volts